

EE 100/42 Spring 2009
Solutions to Homework 6

1.71)

$$v_x + 2v_x = 18V$$

$$v_x = 6V$$

$$i_x = 6V/2 \Omega = 3A$$

$$i_z = 12V/12 \Omega = 1A \text{ (} i_z \text{ defined as flowing down from top node)}$$

$$i_y = 3A - 1A = 2A$$

2.56)

Using KCL at v_1 :

$$5A = \frac{v_1}{10} + \frac{v_1 - v_2}{16} - i_z$$

Using KCL at v_2 :

$$3A = \frac{v_2}{20} + \frac{v_2 - v_1}{16} + i_z$$

$$v_1 - v_2 = 5i_x = 5(v_1/10) = v_1/2$$

Plug in, solve, $v_1 = 64V$

$$v_2 = v_1/2 = 32V$$

$$\text{Power at } 16 \Omega \text{ resistor} = (v_1 - v_2)^2/16 = 32^2/16 = 64W$$

2.58)

Let the left top node be v_1 , right top node be v_2 . Use KCL:

$$1A = \frac{v_1}{20} + \frac{v_x}{10}$$

$$0 = \frac{v_2}{5} - \frac{v_x}{10} + \frac{v_x}{5}$$

$v_2 = v_1 - v_x$, plug into #2:

$$2v_1 = v_x$$

Plug into #1:

$$1A = \frac{v_1}{20} + \frac{2v_1}{10} = \frac{v_1}{20} + \frac{4v_1}{20} = \frac{v_1}{4}$$

$$v_1 = 4V$$

$$R = 4V/1A = 4 \Omega$$

5.54)

$$I_2(-j15 + j10) + 10\angle 180^\circ = 0 \longrightarrow I_2 = j2$$

$$I_1(5 + j15) = 20\angle 0^\circ \longrightarrow I_1 = \frac{2}{5} - \frac{j6}{5}$$

$$v_1 = j15(I_1 - I_2) = (6j + 18) + 30 = 48 + 6j = 6\sqrt{65}\angle 7.125^\circ$$

5.76)

$$I = \frac{V}{Z} = \frac{240\sqrt{2}\angle 50^\circ + 220\sqrt{2}\angle 30^\circ}{1 + j2} = \frac{-51.27 + j104.44}{1 + j2} = \frac{116.35\angle 116.15^\circ}{\sqrt{5}\angle 63.43^\circ} = 52.03\angle 52.72^\circ$$

$$\text{Power } P = \frac{V_m I_m}{2} \cos(\theta)$$

$$\text{Source A: } P = \frac{240\sqrt{2} * -52.03}{2} \cos(2.72^\circ) = -8819.84\text{W}$$

$$\text{Source B: } P = \frac{220\sqrt{2} * -52.03}{2} \cos(22.72^\circ) = 7465.90\text{W}$$

Source A is delivering energy; source B is absorbing energy.

5.89)

a)

$$Z_{th} = 100 + j50$$

$$V_{oc} = 200\angle 0^\circ$$

$$I_{sc} = V_{oc}/Z_{th} = \frac{200\angle 0^\circ}{50\sqrt{5}\angle 26.57^\circ} = \frac{4}{\sqrt{5}} \angle -13.28^\circ$$

Set up Thevenin and Norton equivalent circuits as usual, with Z_{th} in place of R_{th} .

b)

For maximum power with reactive loads, make the load's impedance the complex conjugate of Z_{th} .

$$Z_{load} = 100 - j50 \Omega$$

$$I = \frac{200\angle 0^\circ}{(100 + j50) + (100 - j50)} = \frac{200\angle 0^\circ}{200} = 1\angle 0^\circ$$

$$I_{rms} = \frac{I}{\sqrt{2}}$$

$$P = I_{rms}^2 R = \left(\frac{1}{\sqrt{2}}\right)^2 100 = 50\text{W}$$

c)

For maximum power with resistive loads, make the load's resistance the amplitude of Z_{th} .

$$R_{load} = \sqrt{100^2 + 50^2} = 50\sqrt{5} \Omega$$

$$I = \frac{200\angle 0^\circ}{(100 + j50) + (50\sqrt{5})} = \frac{200\angle 0^\circ}{217\angle 13.28^\circ} = 0.92\angle -13.28^\circ$$

$$I_{rms} = \frac{I}{\sqrt{2}}$$

$$P = I_{rms}^2 R = \left(\frac{0.92}{\sqrt{2}}\right)^2 50\sqrt{5} = 47.32\text{W}$$

6.42)

$ H(f) $	0.5	2	$1/\sqrt{2}$	$\sqrt{2}$
$ H(f) (\text{db})$	-6	6	-3	3

6.53)

Treat the circuit like a voltage divider:


$$V_{out} = V_{in} \frac{1/j\omega 10^{-10}}{50 + 1/j\omega 10^{-10}} = V_{in} \frac{1}{1 + \frac{j50\omega}{10^{10}}} = V_{in} \frac{1}{1 + \frac{j\pi f}{10^8}}$$

$$(2\pi f = \omega)$$

$$H(f) = \frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{j\pi f}{10^6}}$$


corner frequency (break frequency): $\frac{j\pi f_B}{10^8} = j \Rightarrow f_B = \frac{10^8}{\pi}$

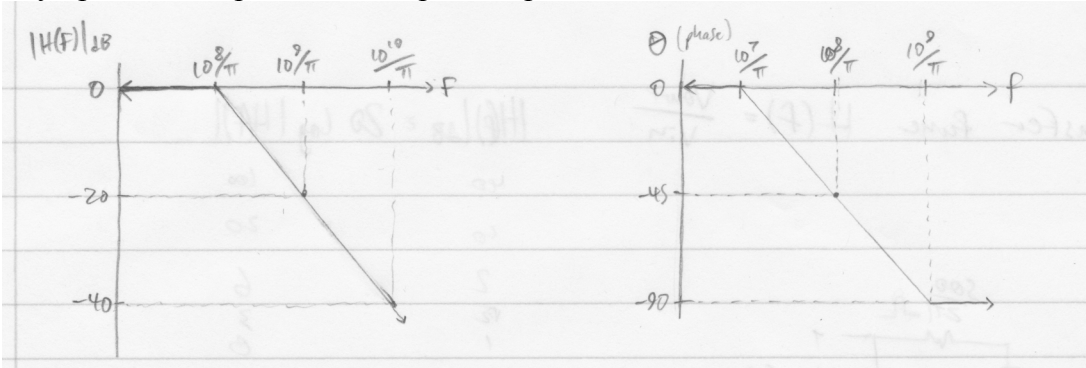Asymptotic Bode plots for a simple low-pass filter:



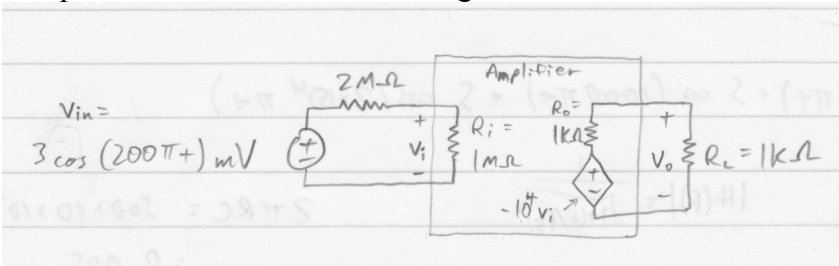11.7)

The problem describes the following circuit:



$$V_i = V_{in} \frac{1M\Omega}{1M\Omega + 2M\Omega} = 1 \cos(200\pi t) \text{ mV}$$

$$V_o = (-10^4) V_i \frac{1K\Omega}{1K\Omega + 1K\Omega} = (-10^4) 0.5 \cos(200\pi t) \text{ mV} = -5 \cos(200\pi t) \text{ V}$$

$$G = \frac{P_o}{P_i} = \frac{V_o^2/R_L}{V_i^2/R_i} = \left(\frac{V_o}{V_i}\right)^2 \frac{R_i}{R_L} = \left(\frac{-5 \cos(200\pi t) \text{ V}}{1 \cos(200\pi t) \text{ mV}}\right)^2 \frac{1M\Omega}{1K\Omega} = 25 \times 10^9$$

A.4)

Complex number	Polar form	Exponential form
$5-j5$	$\sqrt{50}\angle -45^\circ$	$\sqrt{50}e^{-j45^\circ} = \sqrt{50}e^{-j0.79}$
$-10+j5$	$25\sqrt{5}\angle 153.43^\circ$	$25\sqrt{5}e^{j153.43^\circ} = 25\sqrt{5}e^{j2.68}$
$-3-j4$	$5\angle 233.13^\circ$	$5e^{j233.13^\circ} = 5e^{j4.07}$
$-j12$	$12\angle -90^\circ$	$12e^{-j90^\circ} = 12e^{-j\frac{\pi}{2}}$