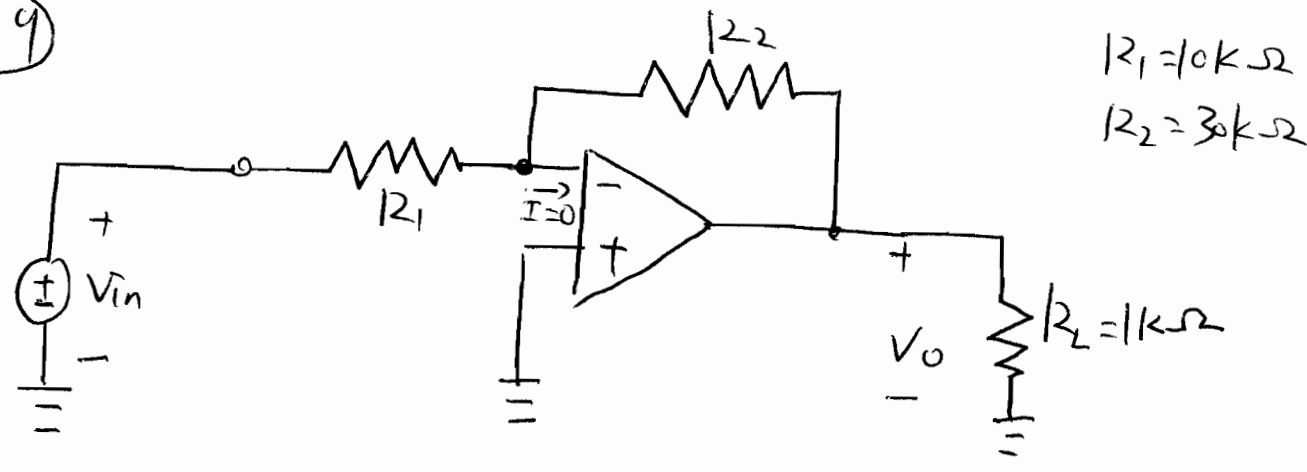


P 14.9





$R_1 = 10k\Omega$   
 $R_2 = 30k\Omega$

This is inverting amplifier. the voltage gain is given by:


$$A_v = \frac{-R_2}{R_1} = \frac{-30}{10} = \boxed{-3}$$
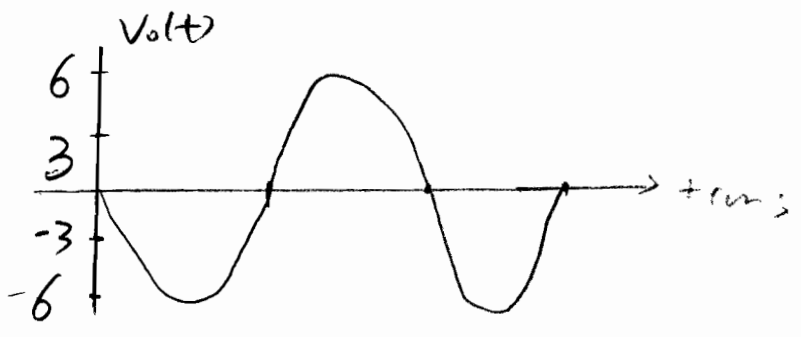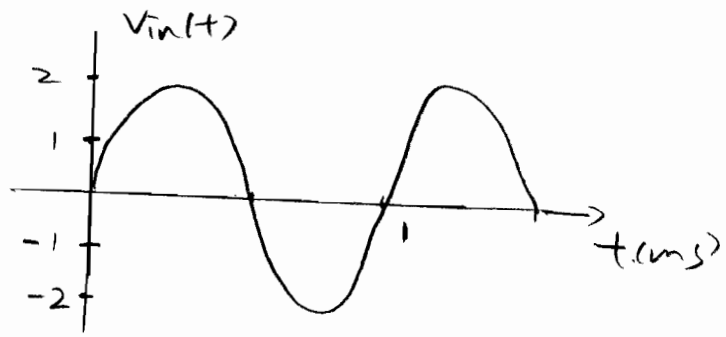
$$V_{in}(t) = 2 \sin(2000\pi t) \Rightarrow V_o(t) = -3 \cdot [2 \cdot \cos(2000\pi t)]$$
$$= \boxed{-6 \cdot \cos 2000\pi t}$$



They are not drawn on scale!


P. 14.10

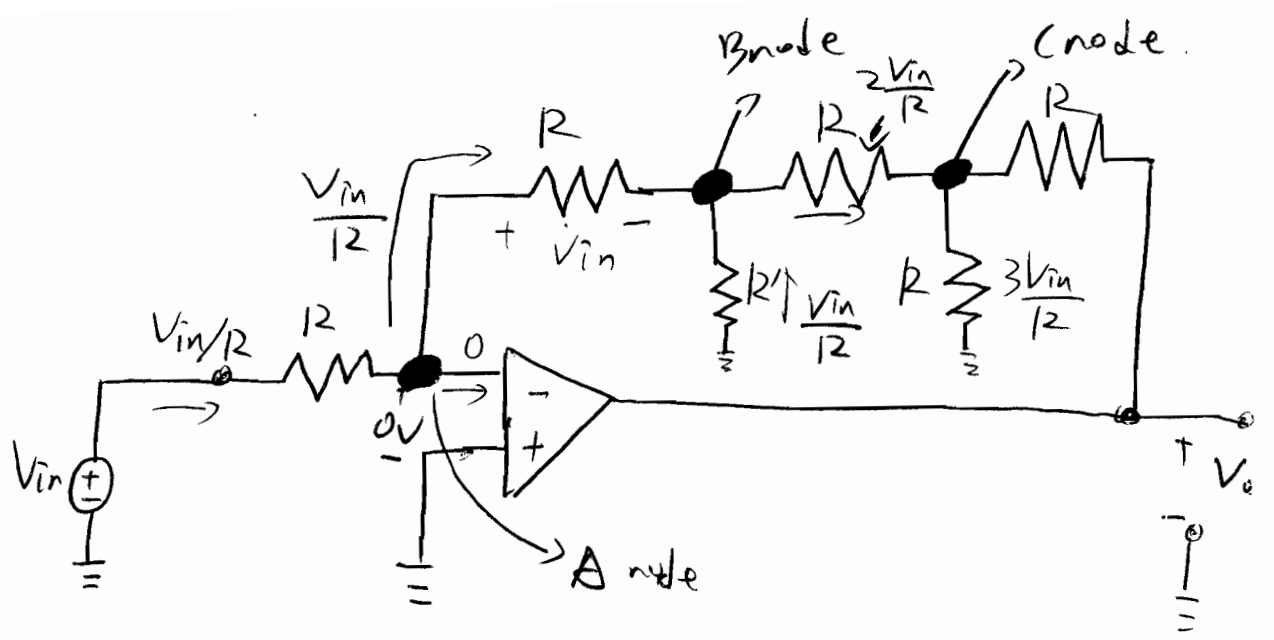


We can use KCL at each node to find the current.

At: node A:  $I_A = \frac{V_{in} - 0}{R} = \frac{V_{in}}{R}$  voltage drop across  $\begin{matrix} - \\ + \end{matrix}$  terminals of Amplifier is 0V.

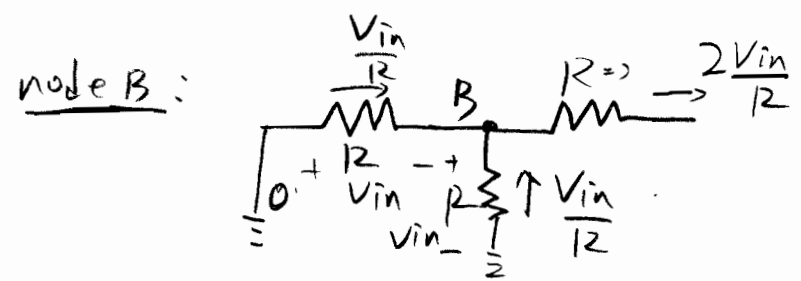Since no current flow into amplifier, we have  $\frac{V_{in}}{R}$  flows to the next R resistor:



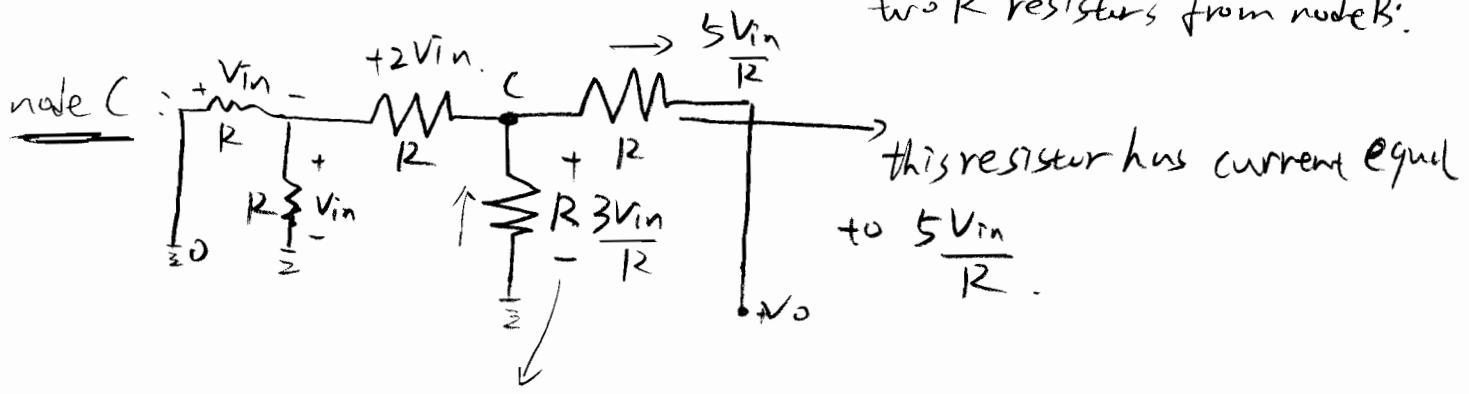summing constraint: same voltage drop seems across the two R resistors from node B:




this resistor has  $\frac{3V_{in}}{R}$  voltage drop.

this resistor has current equal to  $\frac{5V_{in}}{R}$ .


2.14.10 continue:

use KVL at the  $V_o$  node:

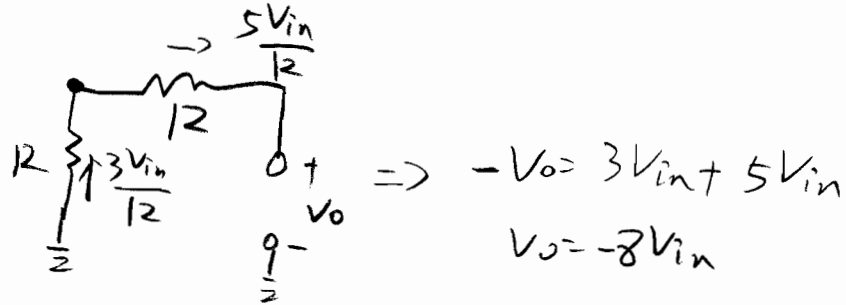

$$A_v = \frac{V_o}{V_{in}} = \boxed{-8}$$

2.14.21

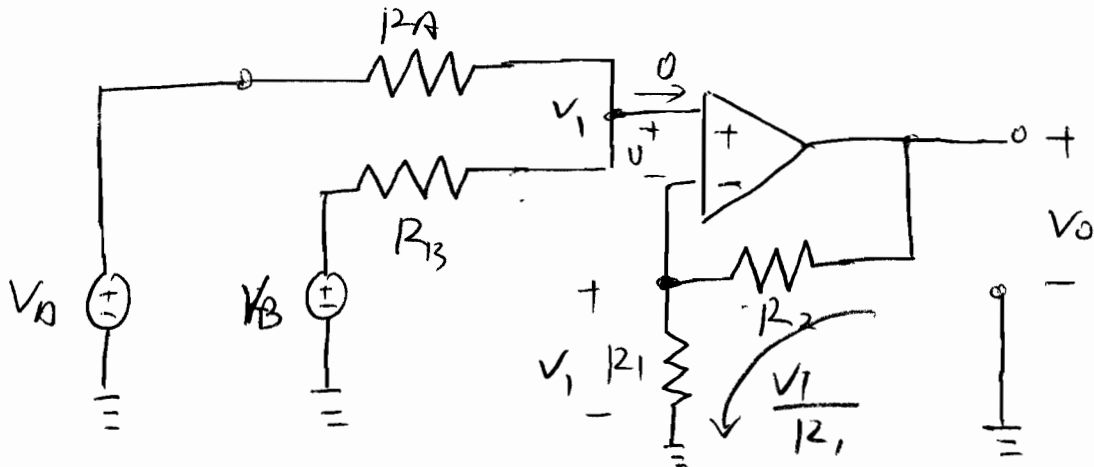


Let us assume the voltage drop across  $R_1 \Rightarrow V_1$ , then the current flows

through  $R_1$  is  $= \frac{V_1}{R_1}$

$\Rightarrow$  for KCL at the  $-$  input of amplifier.

$$\Rightarrow \frac{V_A - V_1}{R_A} + \frac{V_B - V_1}{R_B} = 0 \quad (1)$$

P.14.21  
 continue.

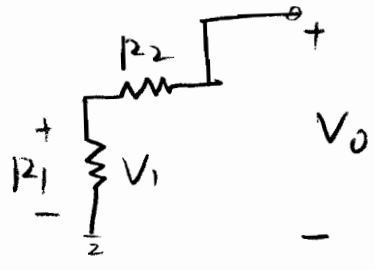


$$V_1 = \frac{V_0 \cdot R_1}{R_1 + R_2} \quad (2)$$

we then can substitute equation (1) into (2)

$$V_0 = \left( \frac{R_1 + R_2}{R_1} \right) \frac{V_A R_B + V_B R_A}{R_A + R_B}$$

P.14.23

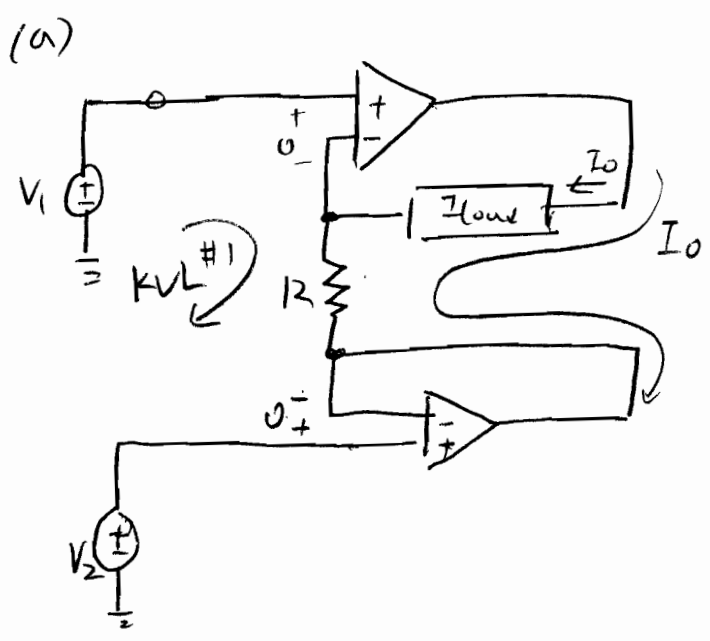


$V_1 = 0 + R_2 I_0 + 0 + V_2 \Rightarrow$  write a KVL at mesh #1

$$I_0 = \frac{V_1 - V_2}{R_2}$$

the  $I_0$  is independent of  $I_{load}$ , so the output impedance is infinite

P14.23 (b)

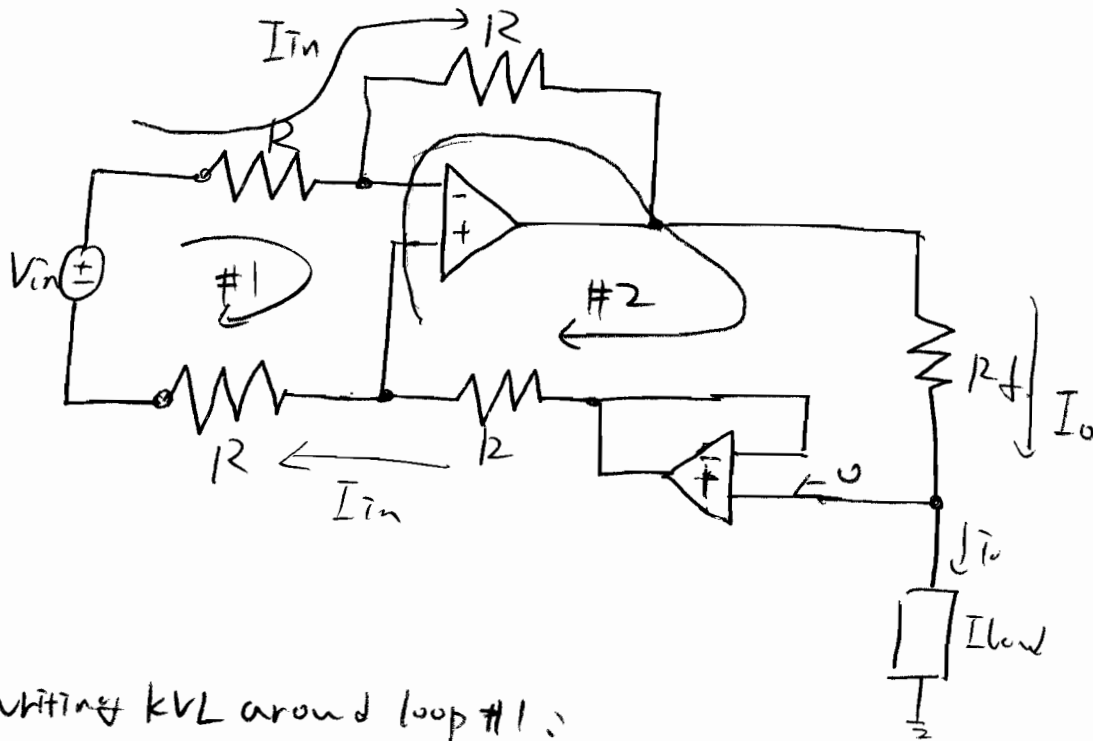

Writing KVL around loop #1:

$$V_{in} = RI_{in} + 0 + RI_{in} \rightarrow V_{in} = 2RI_{in}$$

Writing KVL around loop #2:


$$RI_{in} + R_f I_0 + RI_{in} = 0$$

$$\Rightarrow V_{in} + R_f I_0 = 0$$

$$\boxed{I_0 = -\frac{V_{in}}{R_f}}$$

$I_0$  is independent of the load, so the output impedance is infinite.

(P14.27)

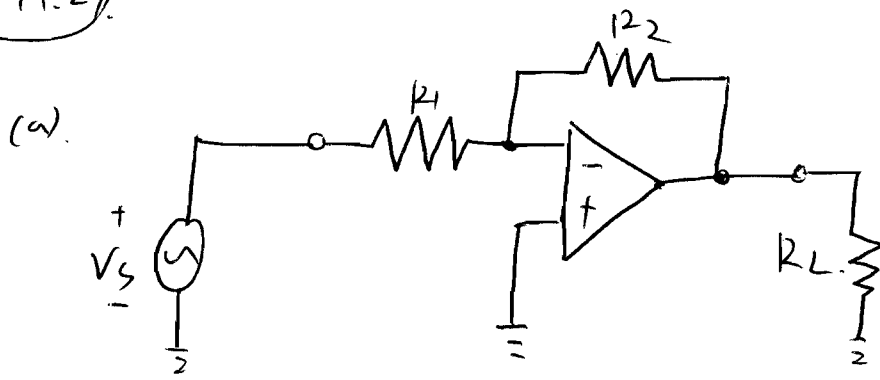

(a) inverting amplifier.


$$A_v = -\frac{R_2}{R_1} \Rightarrow R_{in} = R_1.$$

input power:  $P_{input} = \frac{V_s^2}{R_{in}} = \boxed{\frac{V_s^2}{R_1}}$

output power:  $P_o = \boxed{\frac{V_o^2}{R_L}}$

the power gain  $G$ :  $\frac{P_o}{P_{in}} = \frac{V_o^2/R_L}{V_s^2/R_1} = A_v^2 \frac{R_1}{R_L} = \boxed{\frac{R_2^2}{R_1 R_L}}$


(b)

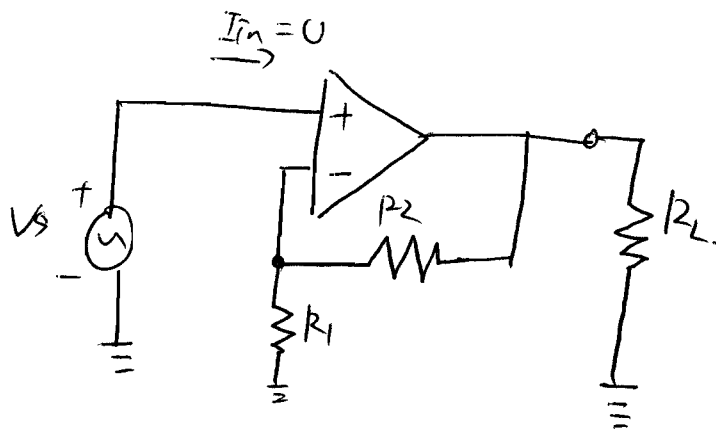



This is a noninverting amplifier.

$\boxed{I_{in} = 0}$ . Therefore  $\boxed{P_{in} = 0}$  and  $\boxed{G = \infty}$




P. 10.6.

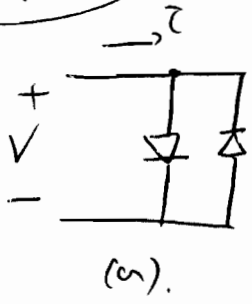

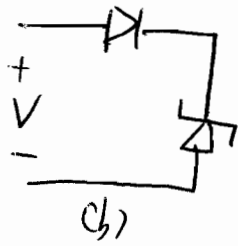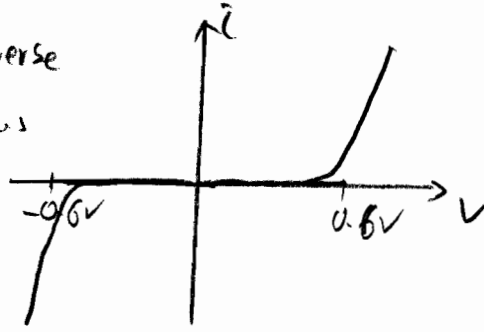
one diode in forward bias region.  
Another one is in reverse bias region as  $V_{bias}$  is sweeping



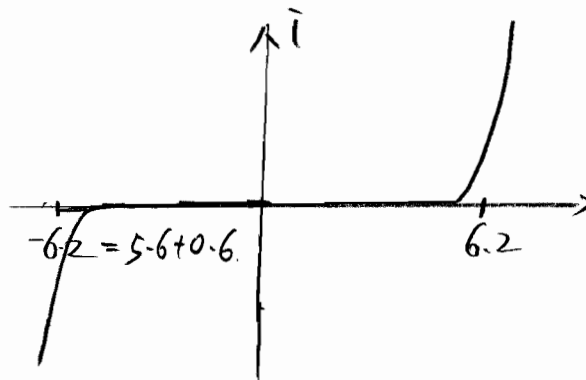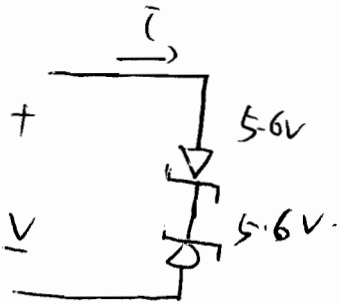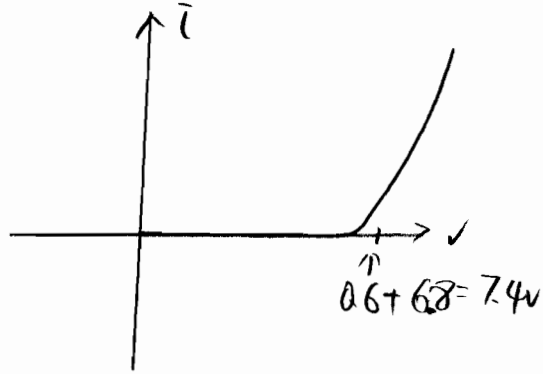
The Zener diode is operated as constant-voltage in reverse-breakdown region.




P10.36

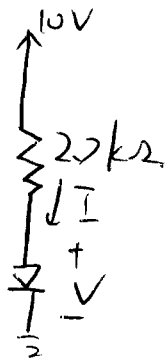

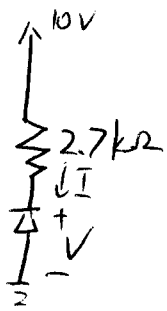
(a) The diode is on,  $V=0$  and  $I = \frac{10}{2700} = 3.70 \text{ mA}$ .



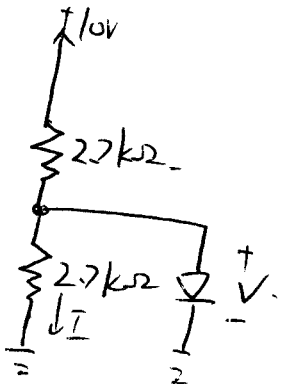(b) The diode is off,  $V=10\text{V}$  and  $I=0$ .





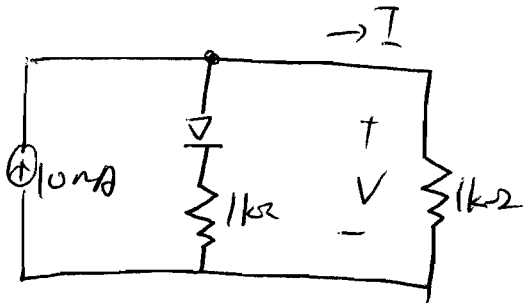
(c) The diode is on,  $V=0$  and  $I=0$ .



(d) The diode is on,  $I=5 \text{ mA}$  and  $V=5 \text{ V}$ .



P10.39

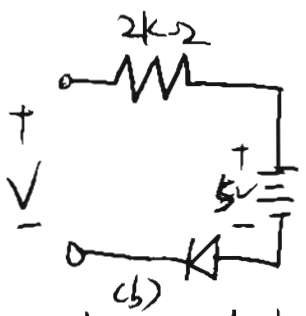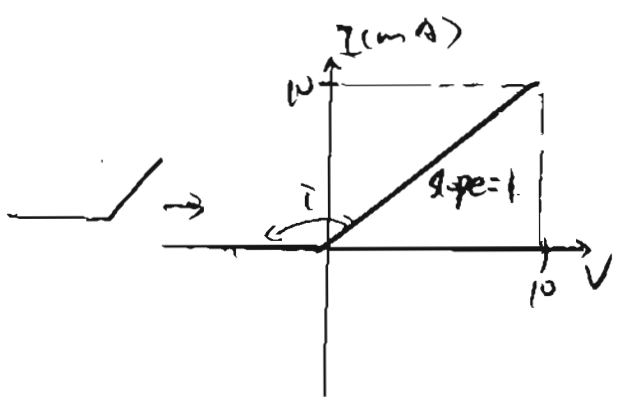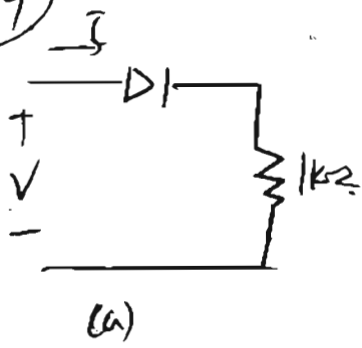

replace the diode with a voltage source and resistor.

