

EE 100/42 Spring 2009  
Solutions to Homework 9

P 7.33

$$(a) F = AB + (\bar{C} + A)\bar{D} = \overline{(\bar{A} + \bar{B})(C\bar{A} + D)}$$

$$(b) F = A(\bar{B} + C) + D = \overline{(\bar{A} + \overline{BC})\bar{D}}$$

$$(c) F = \bar{A}\bar{B}C + A(B + C) = \overline{(\bar{A} + B + \bar{C})(\bar{A} + \bar{B}\bar{C})}$$

$$(d) F = (A + B + C)(A + \bar{B} + C)(\bar{A} + B + \bar{C}) = \overline{\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C}}$$

$$(e) F = ABC + \bar{A}\bar{B}C + \bar{A}B\bar{C} = \overline{(\bar{A} + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})(A + \bar{B} + C)}$$

P 7.43

$$I = \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC = \sum m(3, 6, 7)$$

$$I = (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)(\bar{A} + B + C)(\bar{A} + B + \bar{C}) = \prod M(0, 1, 2, 4, 5)$$

P 7.44

$$J = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C} + ABC = \sum m(1, 3, 5, 6, 7)$$


$$J = (A + B + C)(A + \bar{B} + C)(\bar{A} + B + C) = \prod M(0, 2, 4)$$

P 7.50

The truth table is as shown in the right, thus the product of sum expression is:

$$A \oplus B = (A + B)(\bar{A} + \bar{B}) = \overline{(\bar{A} + B)(A + \bar{B})}$$

The circuit is:

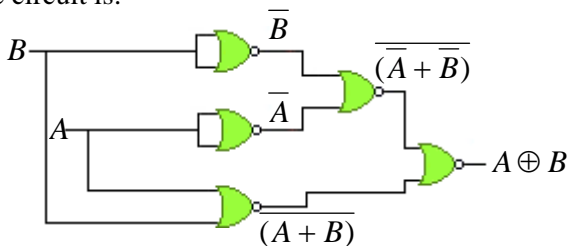

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

P 7.81

Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>
1	0	0
0	1	0
1	0	1
1	1	0
1	1	1
0	1	1
0	0	1
repeats		

The register returns to the initial state after seven shifts.

P 7.82

(a) With an OR gate, after the register reaches the 111 state, it remains in that state and never returns to the starting state.

Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>
1	0	0
0	1	0
1	0	1
1	1	0
1	1	1
1	1	1

(b) With an AND gate, after the register reaches the 000 state, it remains in that state and never returns to the starting state.

Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>
1	0	0
0	1	0
0	0	1
0	0	0
0	0	0

P 7.83

The period of the Q<sub>0</sub> waveform is double that of V<sub>in</sub>, and the period of Q<sub>1</sub> is twice that of Q<sub>0</sub>. Thus flip flops connected in this manner divide the frequency of an input signal by two and by four.

