

lecture 2 - class notes

Ex: Find voltage across & current (i) ①

through

the resistor.


note Units of

Resistance: ohms


Symbol:



Upper case

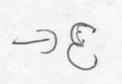

lower case

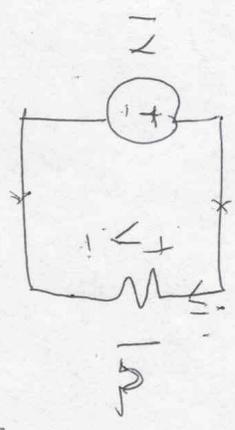

Sol:


$$V = 1 \text{ V}$$

$$V = iR \Rightarrow (1) = (i) (1 \Omega)$$

$$\Rightarrow i = 1 \text{ A}$$


(2)

Es 2: Find V & i :

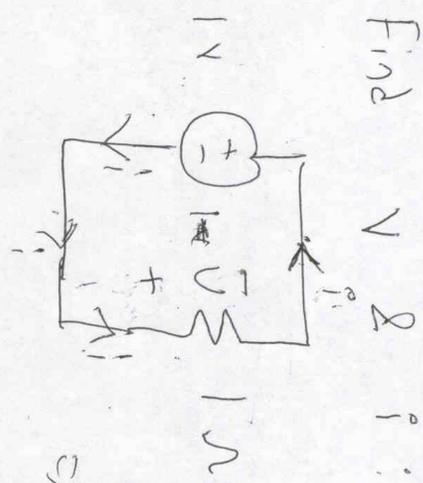



$$V = -1 \text{ V}$$

$$U = iR$$

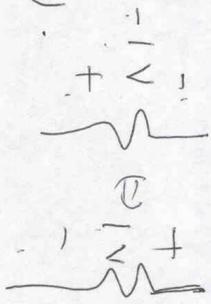


$$\Rightarrow (-1) = (i)(1 \Omega)$$
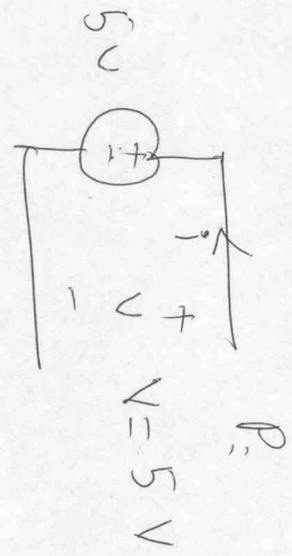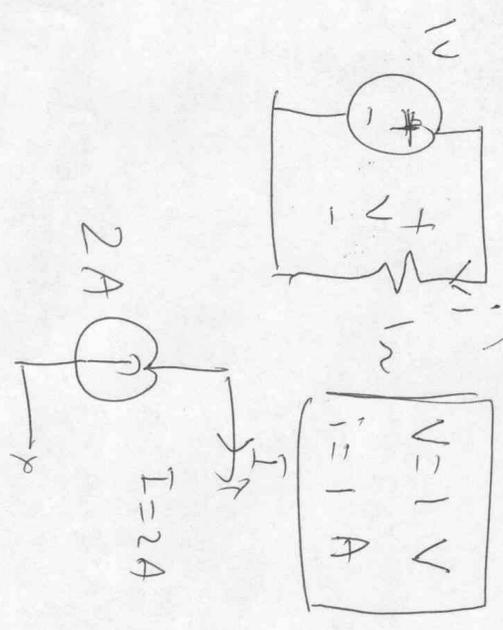
$$\Rightarrow \begin{bmatrix} i = -1 \text{ A} \end{bmatrix}$$




$$V = 5 \text{ V}$$

(1-26)

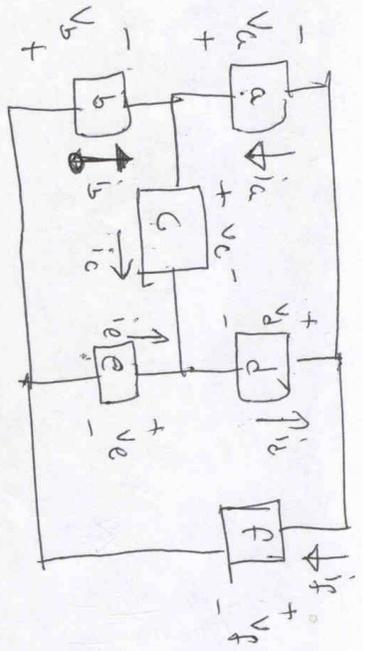

Element	Voltage (V)	Current (A)
a	-18	-51
b	-18	-45
c	20	-6
d	16	-14
e	36	31
f		

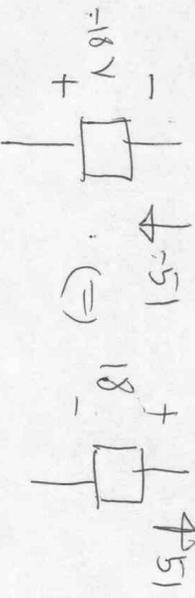

(iii) Find if the circuit is valid (3)


i.e. Is $P_{absorbed} = P_{dissipated}$

Releasing



$$P_{a} = V_a i_a = (-18)(-51) = 918 \text{ W}$$

Absorbing
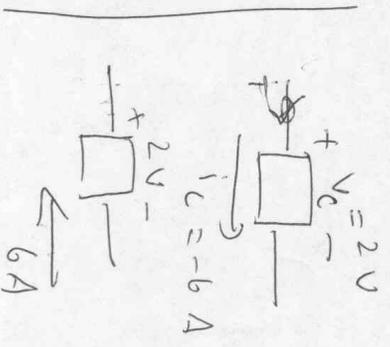
$$P_c = V_c i_c = (20)(-6) = -120 \text{ W}$$



~~18V~~

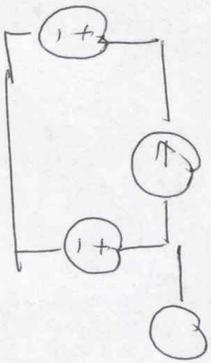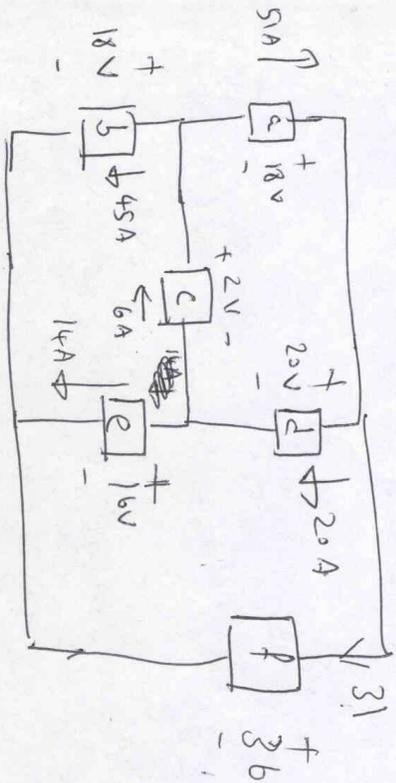

Receiving
 (a) $(18)(5) = 198 \text{ W}$
 (c) $(2)(6) = 12 \text{ W}$

Supplying
 (b) $(18)(45) = 810 \text{ W}$
 (d) $(20)(20) = 400 \text{ W}$
 (e) $(6)(14) = 224 \text{ W}$
 (f) $(31)(36) = 1116 \text{ W}$


(4)

skip 2.5 ← 700 READ IT! (5)


Eg 2.5 ← related to HW # 2.17
look at eq. 2.9



Kirchoff's laws

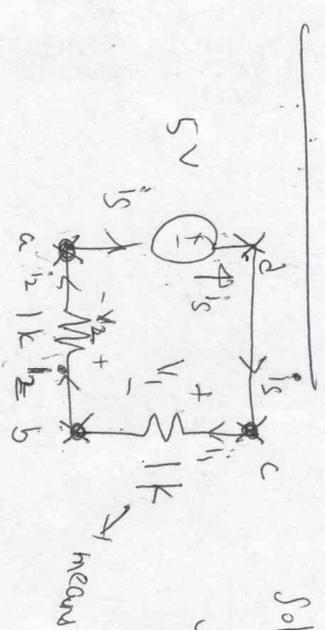

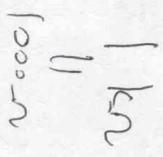Solving a circuit → we find every unknown voltage & current.




node ≡ a point in the circuit where two or more elements meet.

$$V_1 = (i_1) (1k\Omega)$$

$$V_2 = (i_2) (1k\Omega)$$


• Kirchoff's current law: Algebraic sum of currents at $\textcircled{6}$

(KCL) any node is zero.

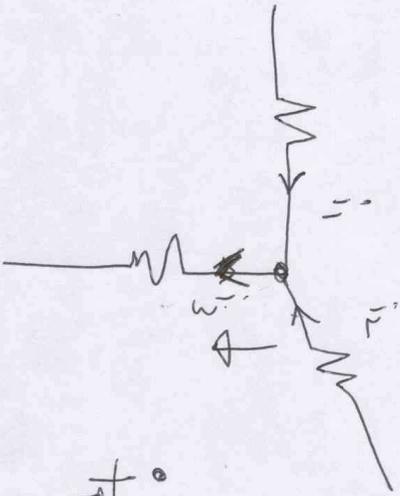

Current entering: +ve
↓
mean positive

Current leaving: -ve

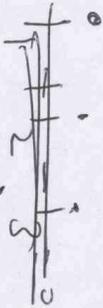

$$i_1 + i_2 + (-i_3) = 0$$

$$\Rightarrow \boxed{i_1 + i_2 = i_3}$$