
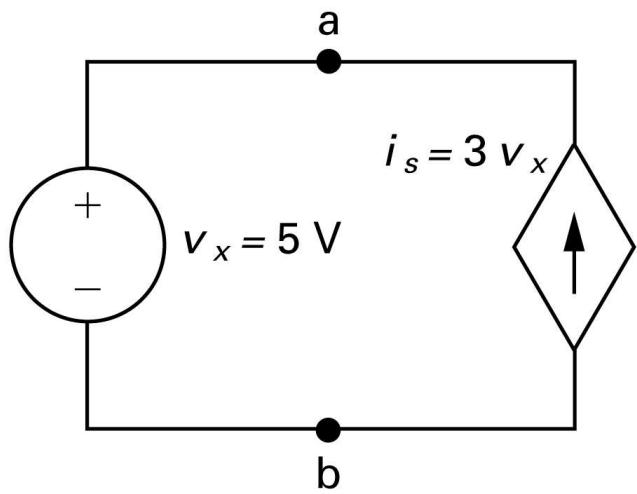



(a)

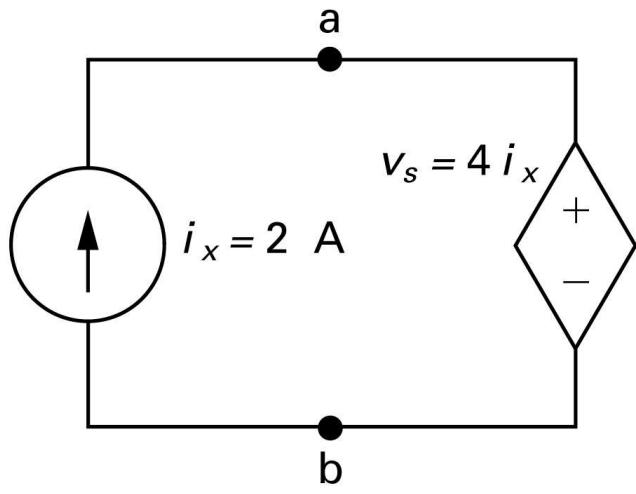

(b)



(c)

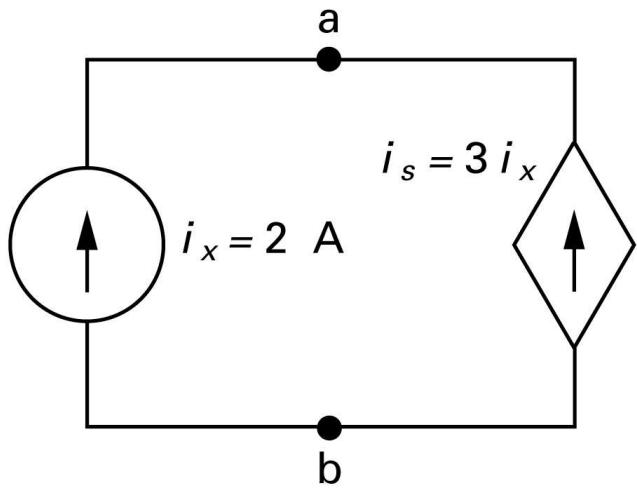

(d)

Figure 2.4 The circuits for Example 2.2.

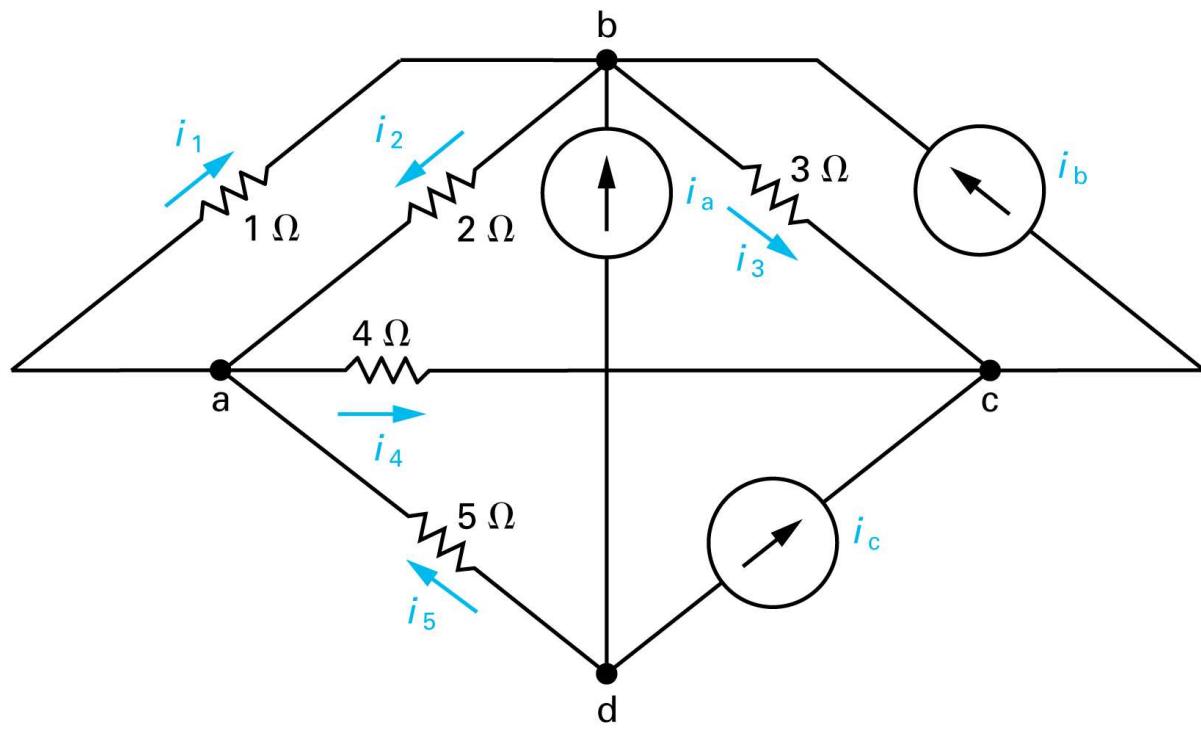


Figure 2.16 The circuit for Example 2.6

From: Nilsson/Riedel, Electric Circuits, 6e, July 2000 Prentice Hall, Inc.

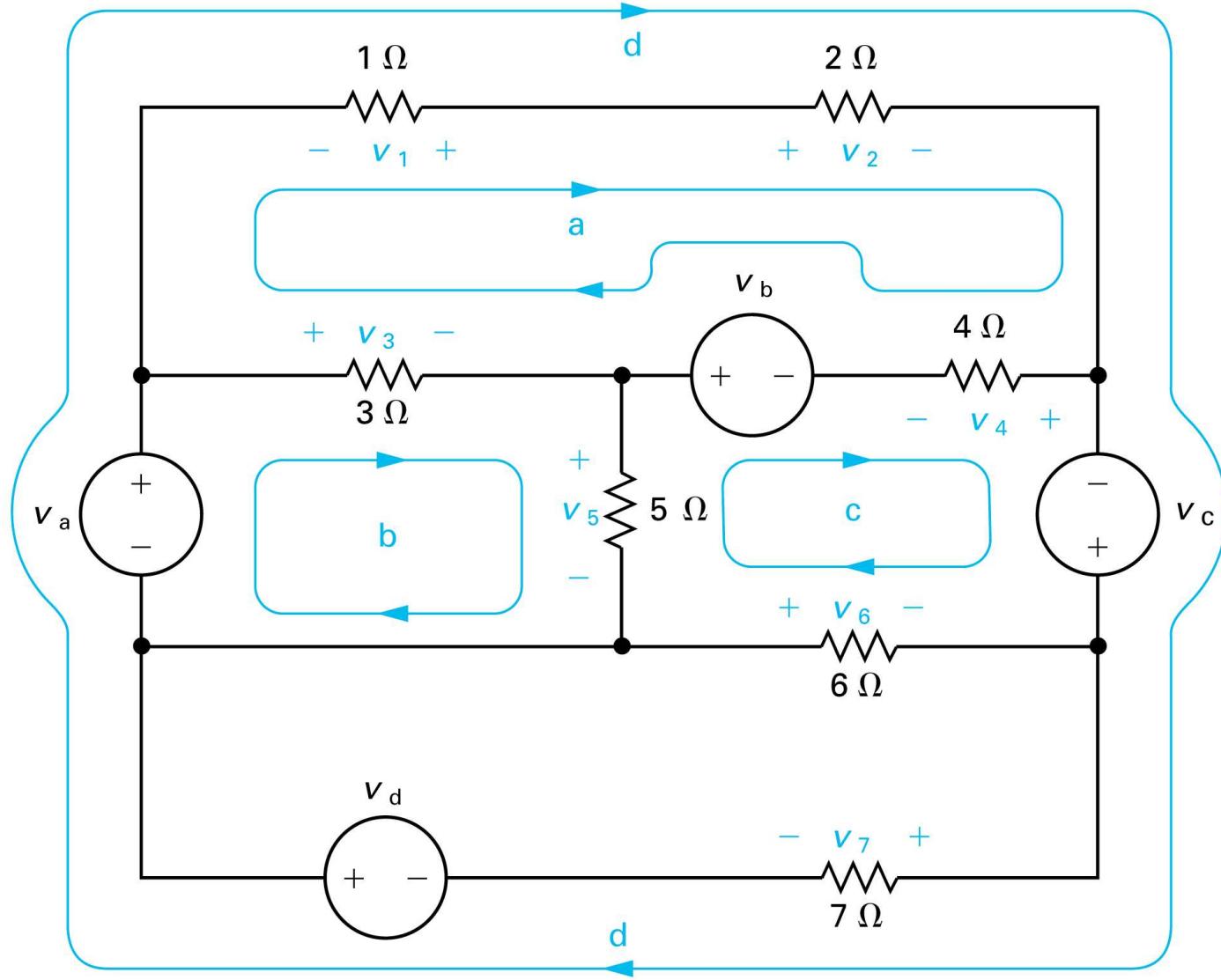


Figure 2.17 The circuit for Example 2.7

From: Nilsson/Riedel, Electric Circuits, 6e, July 2000 Prentice Hall, Inc.

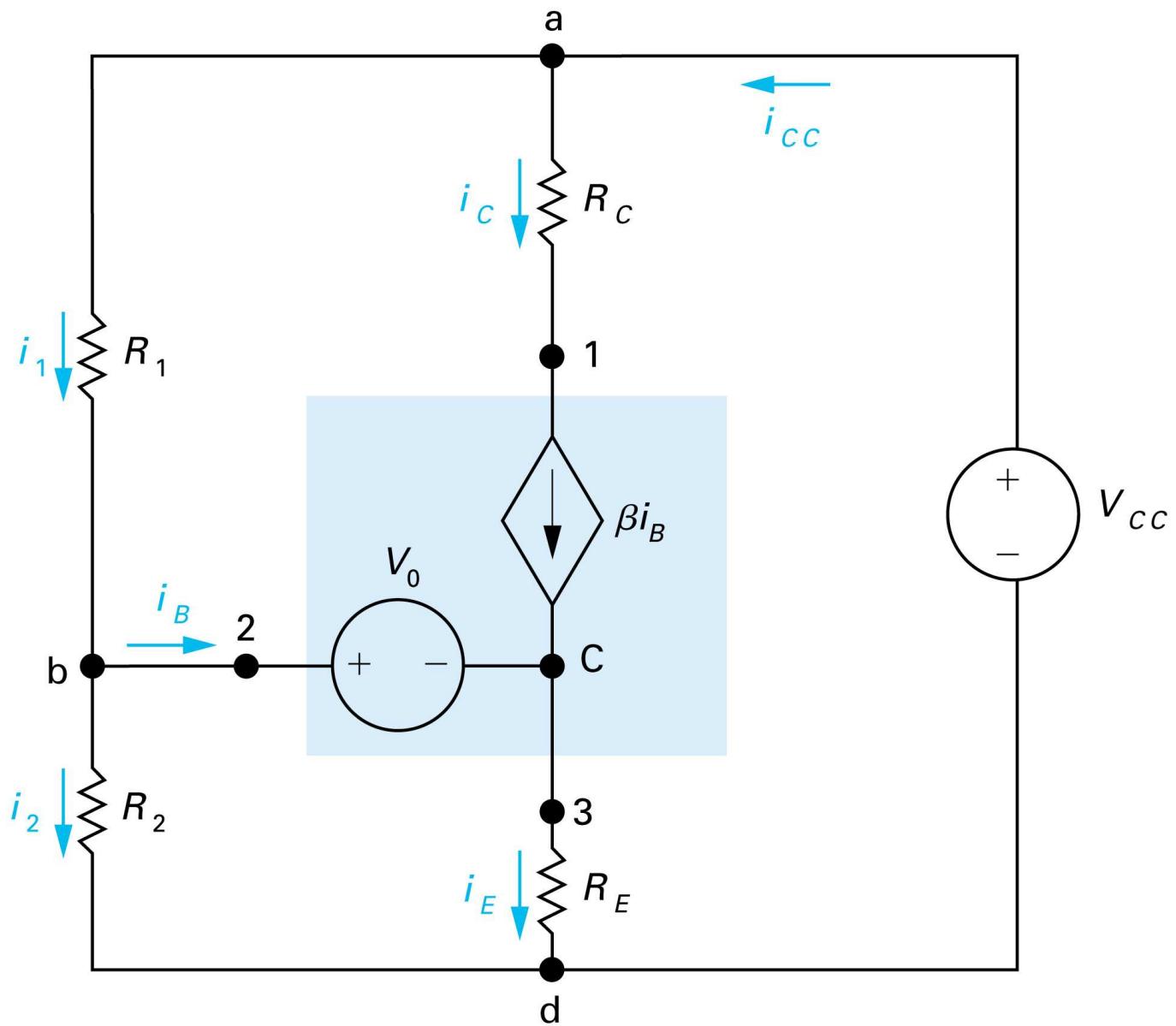


Figure 2.24 The circuit for Example 2.11