

Lecture 16 - 08/02/04

Administrivia: \* Grades coming up


Last date for grade corrections (excluding final) is 08/11/04.

\* Make up Finals - email Bart before 08/06 w/ valid reason

Regular Final: Thurs. 08/12/04 - 3-6 PM


ADP Quiz

In lab: Using 1N4148 Diode

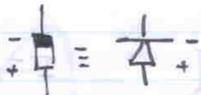

Do not reverse bias a diode too much

Recall

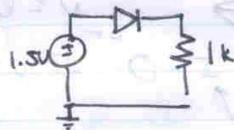

KVL:  $1.5 = v + v_R = v + IR$



$1.5 = v + 10^{-15} (e^{\frac{v}{V_T}} - 1) (1000)$

$T: 300 \rightarrow V = 0.712V$


Note:  $V_T = \frac{kT}{q}$  ← thermal voltage  $\approx .026V @$  room temp

Now: Offset diode model


Recall: Ideal Diode

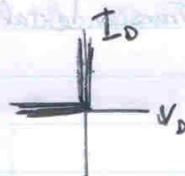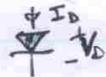

Offset Diode Model

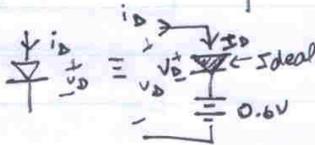

$I_D = I_D$   
 $v_D = V_D + 0.6$

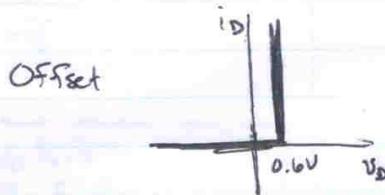




Ex.  $v_D = 0.1$

$v_D = 0.1 - 0.6 = -0.5$

So ideal diode is off

Ex. 9.4

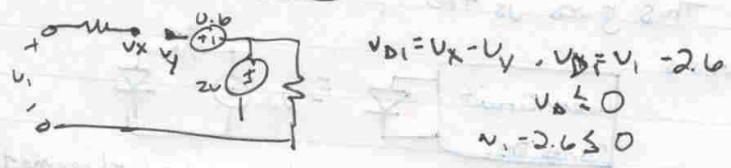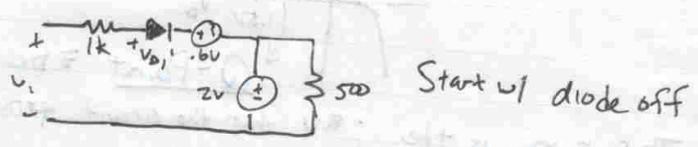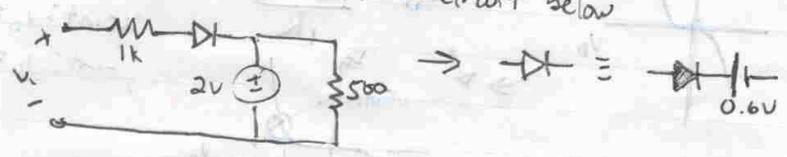
Using the offset diode model, determine  $V_i$ , for which diode first conducts in the circuit below



$v_{D1} = v_x - v_y$ ,  $v_{D1} = v_i - 2.6$   
 $v_{D1} \leq 0$   
 $v_i - 2.6 \leq 0$

What if  $v_i = 2.6V$ ?  $v_i \leq 2.6V$ , so  $v_i > 2.6V \Rightarrow$  Diode is


Diode can be either on or off

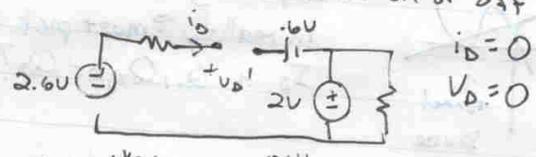


Load-line method



Graphical way to solve nonlinear circuits

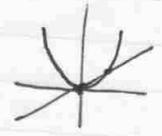Ex.  $y = x^2$   $y = x \rightarrow$  where do they meet?




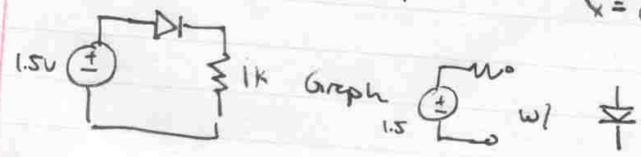Graph or set equal to each other  
 $x^2 = x \Rightarrow x^2 - x = 0$   
 $x = 0, 1$



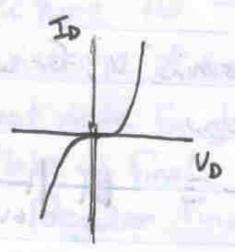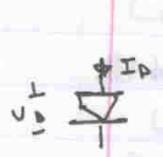

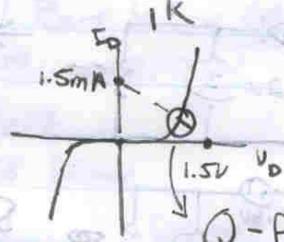KVL:  $1.5 = V_R + V_D$   
 $1.5 = I_D(1k) + V_D$   
 $I_D = \frac{1.5 - V_D}{1k}$




x-int:  $V_D = 1.5V$   
 y-int:  $I_D = 1.5mA$



Q-Point  $\equiv$  DC Point

This gives us the  $V$  &  $I$  that the circuit operates at

Limitations

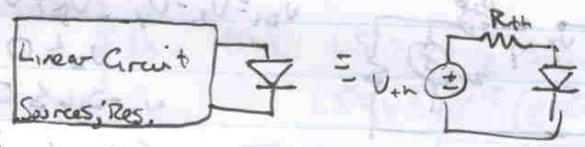


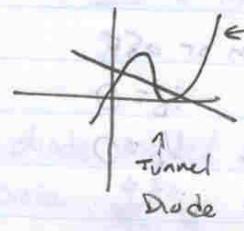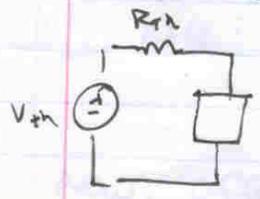If contains non-linear parts, can't use load-line method



3 Operating Pts  
 In reality  $\Rightarrow$  must pick 1 pt.  
 Is it  $Q_1, Q_2,$  or  $Q_3$ ?

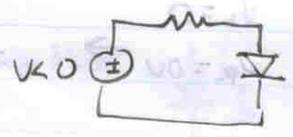Circuit will choose pt w/ greatest stability



$\leftarrow$  Very hard,  
 but we will approximate when  
 we learn small-signal analysis.