

Lecture 9 07/12/04

REVIEW

(1) Midterm \rightarrow Chap's 1-5

Skip: Mesh Analysis, all "Practical Perspectives"
No Δ -Y

(2) What does the midterm cover?

Midterm: 100 pts

\rightarrow You get x pts for writing name & SID
 $x \leq 5$

(1) Nodal Analysis \rightarrow solve circuit (only 2×2 system)
 \circ Just set up equations

(2) Thevenin/Norton

(3) Solve circuit \rightarrow any method

(Hard?) \rightarrow (4) Op-Amp \rightarrow Go through HW3 problems
 \leftarrow 5.17 or 5.18 are good practice!

Midterm is easier than HW

" " way ~~easy~~ ^{easier} than review

Cheat Sheet?

KCL, KVL, Ohm's Law, Power, Thevenin, Norton, Op-Amp


Steps to nodal analysis

①

②

Sample Problem

Find v_x and v_y

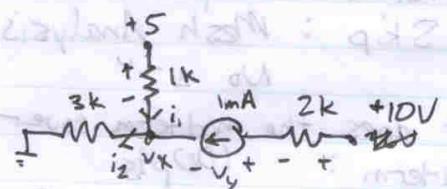


Sol'n: DO NODAL

- ① Define reference ✓
- ② Label node voltages ✓
- ③ Write KCL @ each unknown node
- ④ v_x $1mA + i_1 = i_2$

$$i_1 = \frac{5 - v_x}{1000} \quad i_2 = \frac{v_x}{3000}$$

$$.001 + \frac{5 - v_x}{1000} = \frac{v_x}{3000} \Rightarrow 3 + 15 - 3v_x = v_x$$

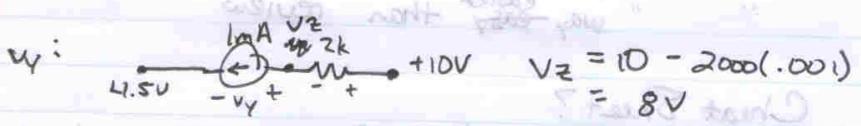
$$4v_x = 18 \Rightarrow \boxed{v_x = 4.5V}$$



$$v_y = v_z - 4.5 = 8 - 4.5$$


$$\boxed{v_y = 3.5V}$$

Redraw Circuit!

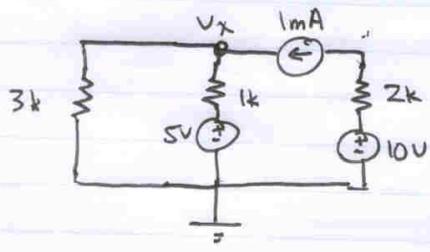

An easy problem:

3

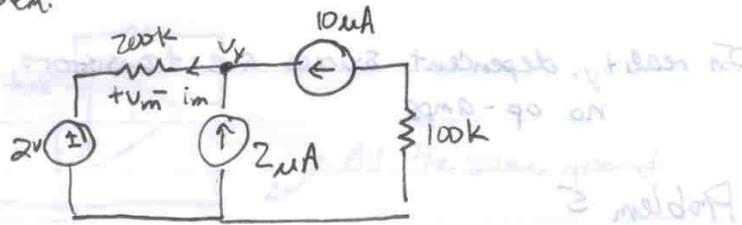

KVL around loop 1

$$2 - v_m - v_y = 0$$

KCL @ v_y $i_m = 10\mu A + 2\mu A = 12\mu A$

$$\begin{aligned} v_m &= -i_m R \\ &= -(12\mu A)(200k) \\ &= -(1.2 \times 10^{-5})(2 \times 10^5) \\ &= -2.4V \end{aligned}$$

$$2 - v_m - v_y = 0$$

$$v_y = 2 - (-2.4) \Rightarrow \boxed{v_y = 4.4V}$$

Review Problems

#9. How do you find V_{oc} ?

Is there any independent source?

$$\text{NO} \Rightarrow V_{oc} = 0$$

Thevenin Equivalent is only a resistor

Send in a test voltage to find the equivalent resistance

4

In reality, dependent sources are transistors,
no op-amps

Problem 5

$$V_{ab} = -5$$

$$i = g_m v_x = \frac{v_x}{\left(\frac{1}{g_m}\right)} \quad v_x = \frac{1}{g_m} i \quad \frac{1}{g_m} \triangleq R$$

Problem 6: Current source = 2mA


Can we do superposition?

Golden Rule: DO NOT KILL

DEPENDENT SOURCES

Using Superposition

Killing current source

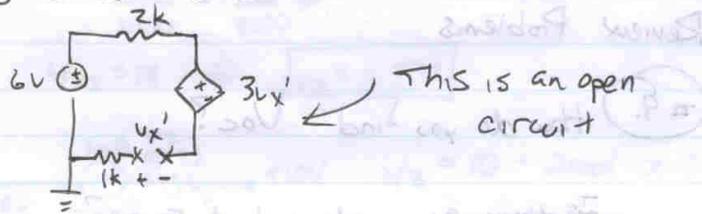


$$\ominus 6 - 0 - 3v_x' + v_x' \rightarrow v_x' = 3V$$

Then kill voltage, but return current source


Trick: Avoid superposition if you have several dependent sources

What if:

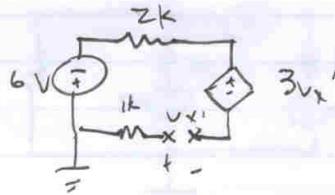


is there a current from voltage source to ground? No
→ Still not a complete loop

5

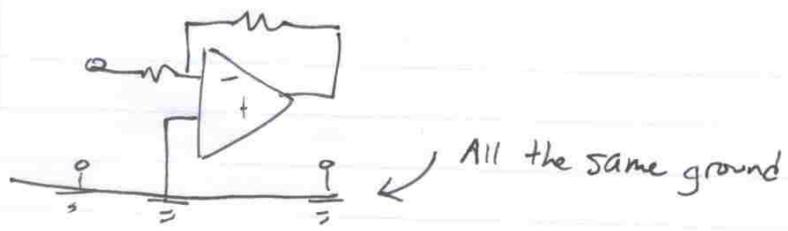

S.I.S from book

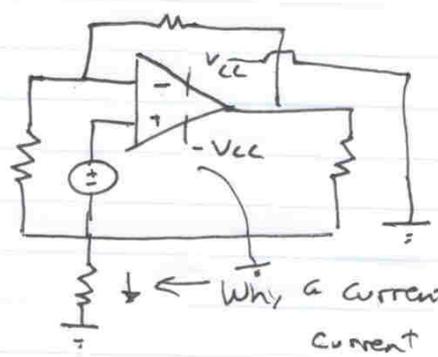

Because power supplies also grounded
- current travels back

Voltage polarity across a current source

