

UNIVERSITY OF CALIFORNIA, BERKELEY
Department of Electrical Engineering and Computer Sciences

EE 100/EE 42
Intro. To Electronics Engineering

Summer 2005
Bharath "Bart Simpson" Muthuswamy

FINAL
August 12th 2005
Time Allotted: 3 hours

NAME: _____, _____
(print) Last First

STUDENT ID#: _____

I WILL NOT CHEAT ON THIS EXAM. Signature: _____

Note(s):

- 1. You will receive [3 pts] for filling out the information above.**
- 2. MAKE SURE THE EXAM HAS 10 NUMBERED PAGES.**
- 3. This is a CLOSED BOOK exam. However, you may use THREE 8.5 x 11" of notes (both sides) and a calculator.**
- 4. SHOW YOUR WORK on this exam. MAKE YOUR METHODS CLEAR TO THE GRADER so you can receive partial credit.**
- 5. WRITE ANSWERS CLEARLY IN THE SPACES (lines or boxes) PROVIDED.**
- 6. Remember to specify units on answers whenever appropriate.**
- 7. If you are asked to setup equation(s) only, do NOT attempt to solve the equation(s).**

SCORE: This page: _____ / 3

1: _____ / 22

2: _____ / 25


3: _____ / 25

4: _____ / 25

TOTAL: _____ / 100

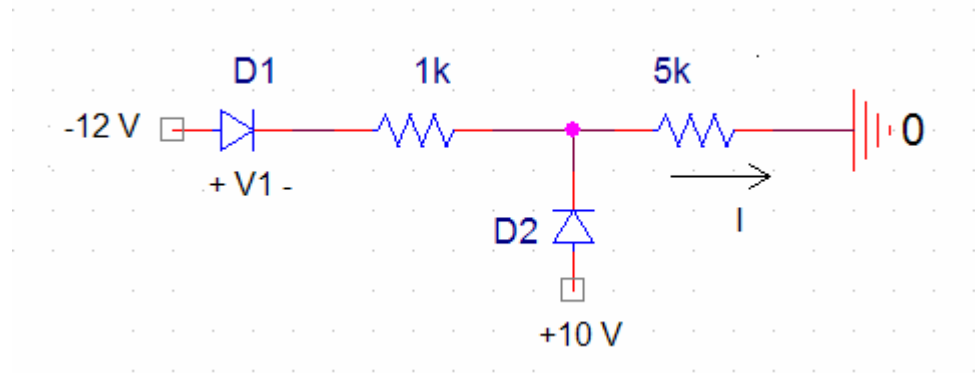Problem 1 Diodes (22 points)

In the circuit below, assume both diodes are ideal. Find I and V_1 .




$$I = \underline{\hspace{2cm}}$$
$$V_1 = \underline{\hspace{2cm}}$$

Problem 1 EXTRA WORKSPACE

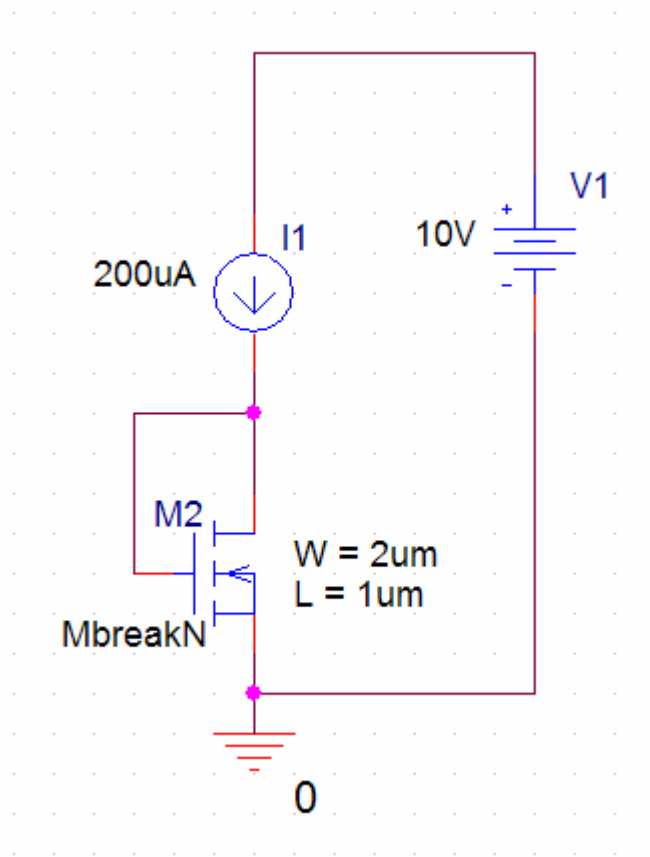Problem 2 NMOS FETs (25 points)

In the circuit below, which elements are absorbing and which elements are releasing power? Specify how much power an element is absorbing or releasing. Use $V_{T0} = 1\text{ V}$ and $K_P = 50\text{ }\mu\text{A}/\text{V}^2$ for the NMOS.



Power Absorbed or Delivered by Elements

NMOS: _____


Current Source: _____

Voltage Source: _____

Problem 2 EXTRA WORKSPACE

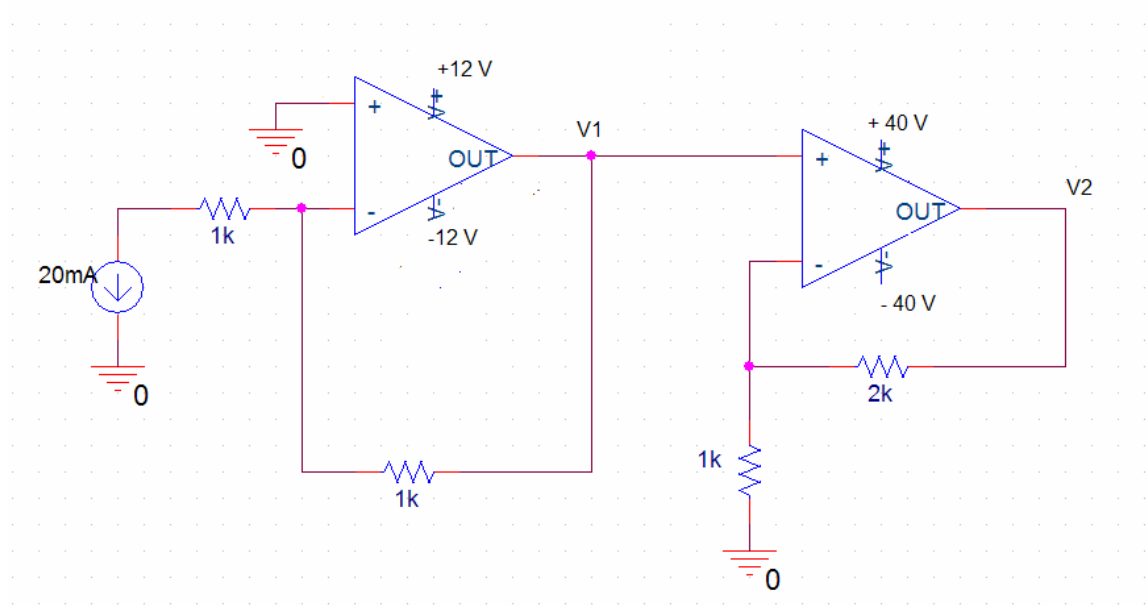PROBLEM 3 Cascaded Opamps (25 points)

In the circuit below, find V1 and V2. **DO NOT IGNORE THE EFFECTS OF THE OPAMP RAIL VOLTAGES!**




V1 = _____
V2 = _____


Problem 3 EXTRA WORKSPACE

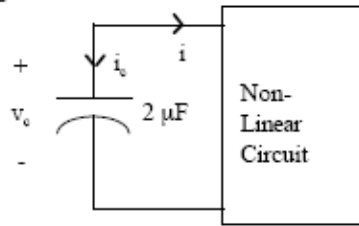PROBLEM 4 Nonlinear Circuit Analysis (25 points)

Suppose you are given the following circuit:



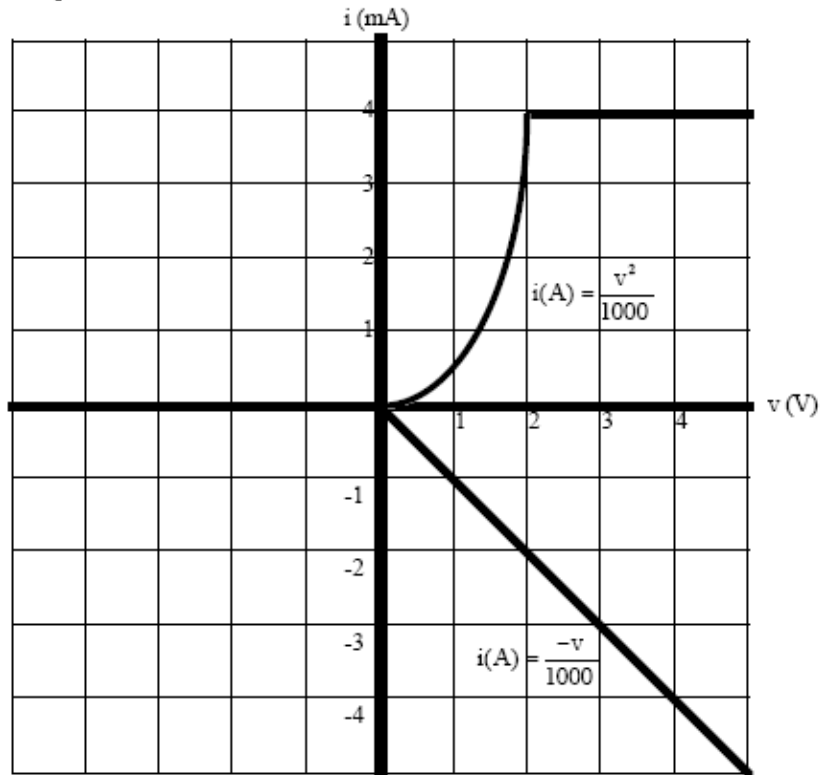The i - v relationship of the non-linear circuit is shown below:



(Note: the parabolic portion is not drawn to scale, but the equations are valid.)

- Sketch the dynamic route, label all equilibrium points, and describe them as stable or unstable.
- Given that $v_c(0) = 4\text{V}$ and $i_c(0) = -4\text{mA}$, how long (in milliseconds) does the current remain constant? If the current is never constant, then explain why.
- Using the same initial conditions, how long (in milliseconds) does it take for the voltage to reach 0.01V ?

T1 (for constant current) = _____
T2 (for voltage to reach 0.01 V) = _____

Problem 4 EXTRA WORKSPACE

EVEN MORE EXTRA WORKSPACE