
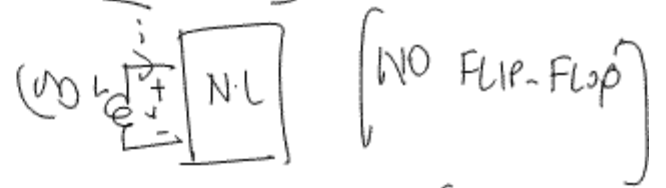
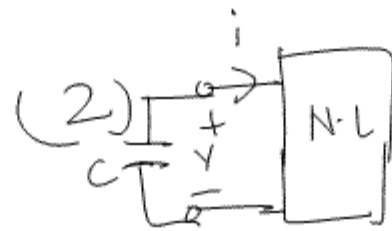


FINAL REVIEW SESSION

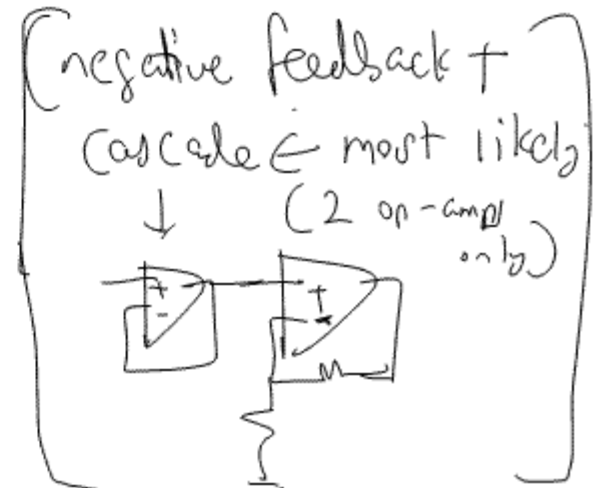Final \rightarrow 4 problems \Rightarrow (1) op-amps




(3) Diode problem (SIMPLE) (≤ 3 diodes)

(4) NMOS (NO PMOS) (VERY SIMPLE)

Ex 1: Op-amps cascade (N&R p. 5.45)

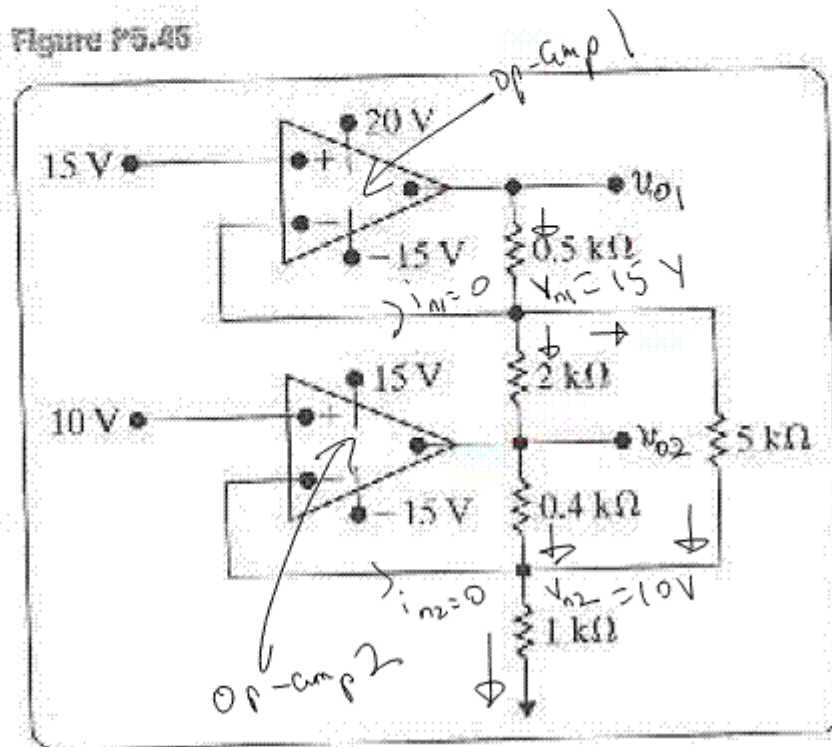5.45 The two op amps in the circuit in Fig. P5.45 are ideal. Calculate v_{o1} and v_{o2} .



Assume op-amp 1 does not rail;

$$V_{n1} = V_{p1} = 15 \text{ V}$$

Assume op-amp 2 does not rail;

$$V_{n2} = V_{p2} = 10 \text{ V}$$

Also: $i_{n1} = i_{n2} = 0 \text{ A}$

KCL @ V_{n1} : $\frac{V_{o1} - V_{n1}}{0.5 \text{ k}} = \frac{V_{n1} - V_{n2}}{5 \text{ k}} + \frac{V_{n1} - V_{o2}}{2 \text{ k}}$ — (1)

KCL @ V_{n2} : $\frac{V_{o2} - V_{n2}}{0.4 \text{ k}} + \frac{V_{n1} - V_{n2}}{5 \text{ k}} = \frac{V_{n2}}{1 \text{ k}}$

$$\Rightarrow \frac{V_{o2} - 10 \text{ V}}{0.4 \text{ k}} + \frac{15 - 10}{5 \text{ k}} = \frac{10}{1 \text{ k}}$$

$$\Rightarrow \frac{V_{o2} - 10}{0.4k} + 1 \text{ mA} = 10 \text{ mA}$$

$$\Rightarrow V_{o2} - 10 = (9 \text{ mA})(0.4k)$$

$$\Rightarrow \boxed{V_{o2} = 13.6 \text{ V}}$$

Substituting V_{o2} in (1):

$$\frac{V_{o1} - 15}{0.5k} = \frac{15 - 10}{5k} + \frac{15 - 13.6}{2k}$$


$$\Rightarrow \frac{V_{o1} - 15}{0.5k} = 1 \text{ mA} + 0.7 \text{ mA}$$

$$\Rightarrow V_{o1} = (0.5 \text{ V} + 0.35 \text{ V}) + 15 \text{ V}$$

$$\Rightarrow \boxed{V_{o1} = 15.85 \text{ V}}$$

For more problems (including nonlinear problems) go over previous exams (midterm(s) & final). Example
 EE109 Sp 05 MT II.

Ex:

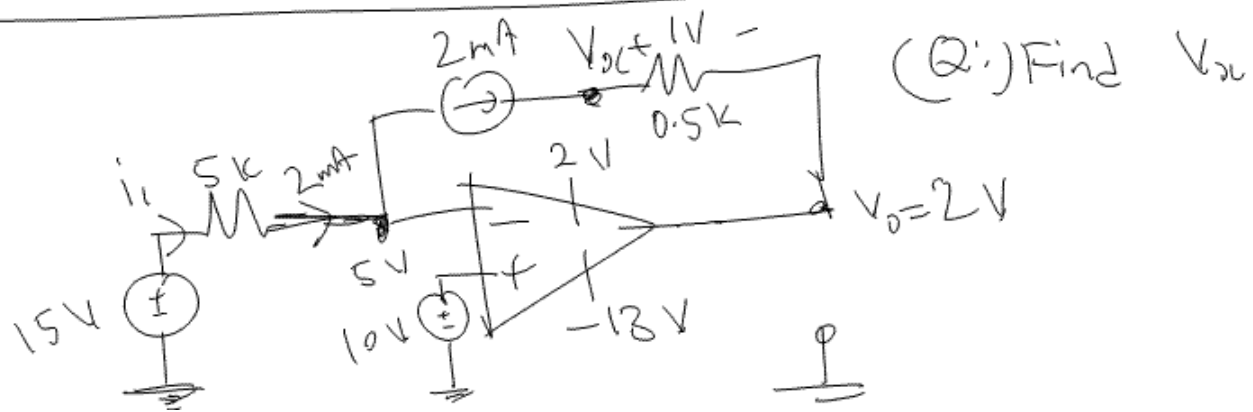

Notice! op-amp must rail because if $V_n = V_o = 10\text{ V}$

$$\Rightarrow i_1 = \frac{15 - 10}{5\text{ k}} = 1\text{ mA}, \text{ but}$$

this violates KCL at


$$V_n \quad (1\text{ mA} \neq 2\text{ mA})$$

$$\therefore V_n = 15\text{ V} - (2\text{ mA})(5\text{ k}) \\ = 5\text{ V}$$

$$\therefore V_o = A \left(\underset{10}{V_p} - \underset{5}{V_n} \right) \rightarrow +\infty, \text{ but op-amp rails} \\ \text{at } V_{dd} = 2\text{ V}$$

$$\therefore V_o = 2\text{ V} \Rightarrow \boxed{V_{pr} = 2\text{ V} + (1/2\text{ k})(2\text{ mA}) = 3\text{ V}}$$

Q:

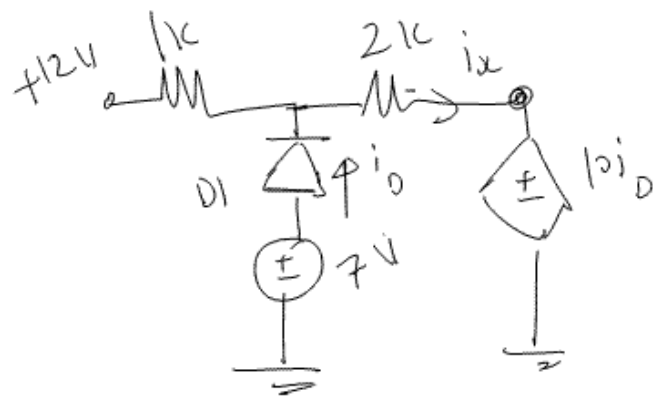

(Q:) Find i_x . Assume diode is ideal.


$$i_x = 4 \text{ mA}$$

(A:)

Assume $D1$ off:

(Verify: if $V_D < 0$)

$$i_D = 0$$

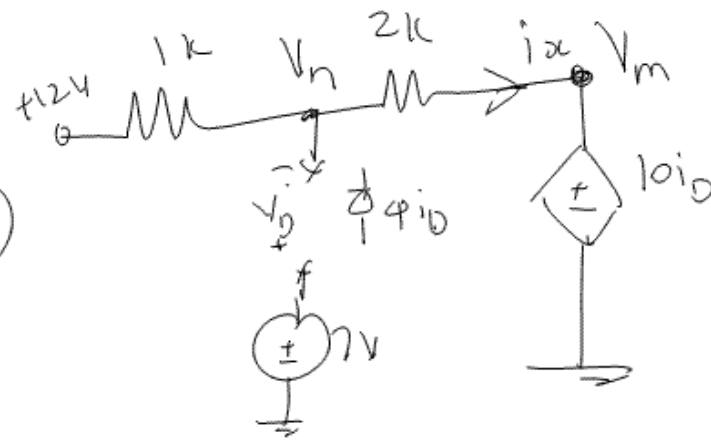


$$\Rightarrow i_x = \frac{12 - V_m}{3k} \quad \text{But } V_m = 0, \text{ since } i_D = 0 \Rightarrow 10i_D = 0$$

$$\therefore i_x = \underline{4 \text{ mA}}$$

$$\therefore V_n = 12 - (1k)(4 \text{ mA}) = 8 \text{ V}$$

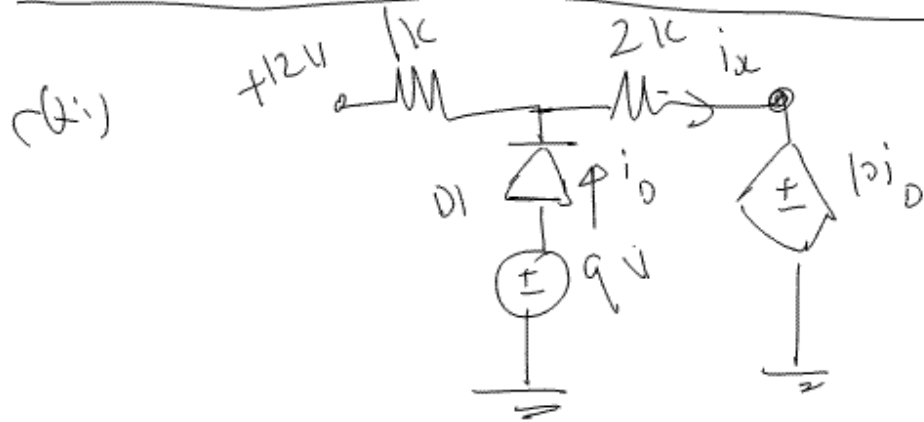
$$\therefore V_D = 7 - 8 = -1 < 0 \checkmark$$



Find i_x . (note 9V supply)

From previous problem, diode off will not work!

\therefore Assume diode is on.

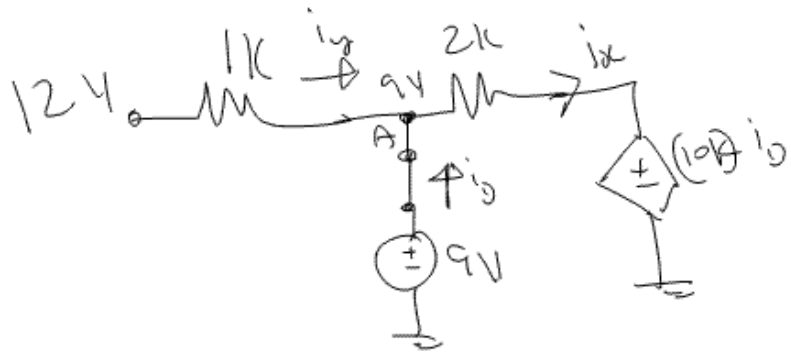

$$i_y = \frac{12 - 9}{1k} = 3 \text{ mA}$$

$$i_x = 3 \text{ mA} + i_b \quad (\text{KCL @ A}) \quad \text{--- (1)}$$

$$\text{But, } i_x = \frac{9 - (10k)i_b}{2k} \quad \text{--- (2)}$$

$$\text{Substitute (2) in (1) } \Rightarrow \frac{9 - (10k)i_b}{2k} = 3 \text{ mA} + i_b$$


$$\Rightarrow 9 - (10k)i_b = (3 \text{ mA})(2k) + i_b(2k)$$

$$\Rightarrow 9 - 6 = (12000)i_b$$

$$\Rightarrow i_b = \frac{3}{12000} = 0.25 \text{ mA}$$

$$\therefore i_x = 3 \text{ mA} + 0.25 \text{ mA} \quad (\text{From (1)}) \Rightarrow \boxed{i_x = 3.25 \text{ mA}}$$

Ex:

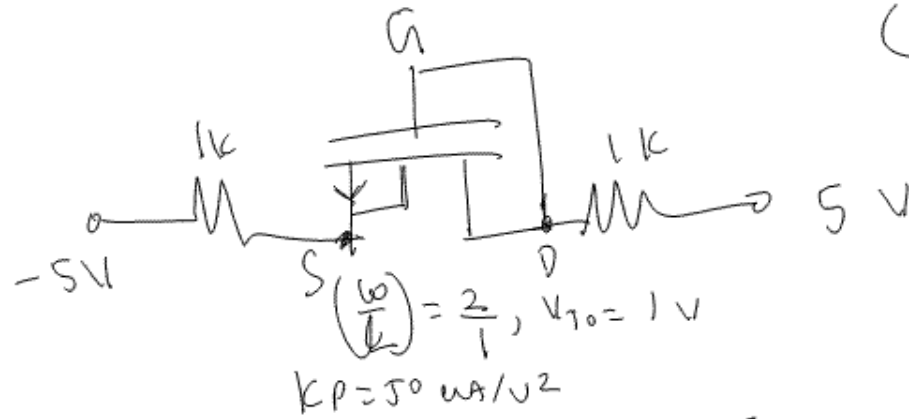

(Q:) Find V_{DS} for the transistor circuit.

Sol: (1) I identify G, D & S. ✓

(2) Educated guess of transistor mode [cutoff, triode, saturation]

Here, transistor is always saturated,

Since $V_G = V_D$, $V_{DS} \geq V_{GS} - V_{TO}$ ↙ saturation condition

$$\Rightarrow V_{GS} \geq V_{GS} - V_{TO} \quad \text{--- (1)}$$


① is always true, $V_{T0} > 0$

$$(3) \quad I_{DS} = \frac{1}{2} k_P \left(\frac{W}{L}\right) (V_{GS} - V_{T0})^2$$

$$= \left(\frac{1}{2}\right) \left(\frac{50 \mu A}{V^2}\right) \left(\frac{2}{1}\right) (V_{DS} - 1)^2$$

$$\boxed{I_{DS} = 50 \frac{\mu A}{V^2} (V_{DS} - 1)^2}$$

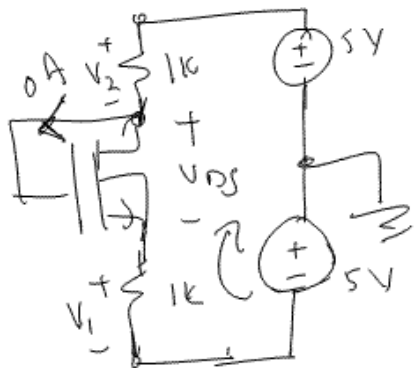One equation, two unknowns. one more equation,



KVL: $V_1 + V_{DS} + V_2 - 5 - 5 = 0$

$$\Rightarrow (I_{DS})(1k) + V_{DS} + (I_{DS})(1k) = 10V$$


$$\Rightarrow \boxed{I_{DS} = \frac{10 - V_{DS}}{2k}}$$


$$\therefore \frac{10 - V_{DS}}{2k} = (50 \times 10^{-6}) (V_{DS} - 1)^2$$

$$\Rightarrow \boxed{V_{DS} = 6.724 \text{ V}}$$
 ~~-14 V~~ 11 mOS

Check in PSpICE:
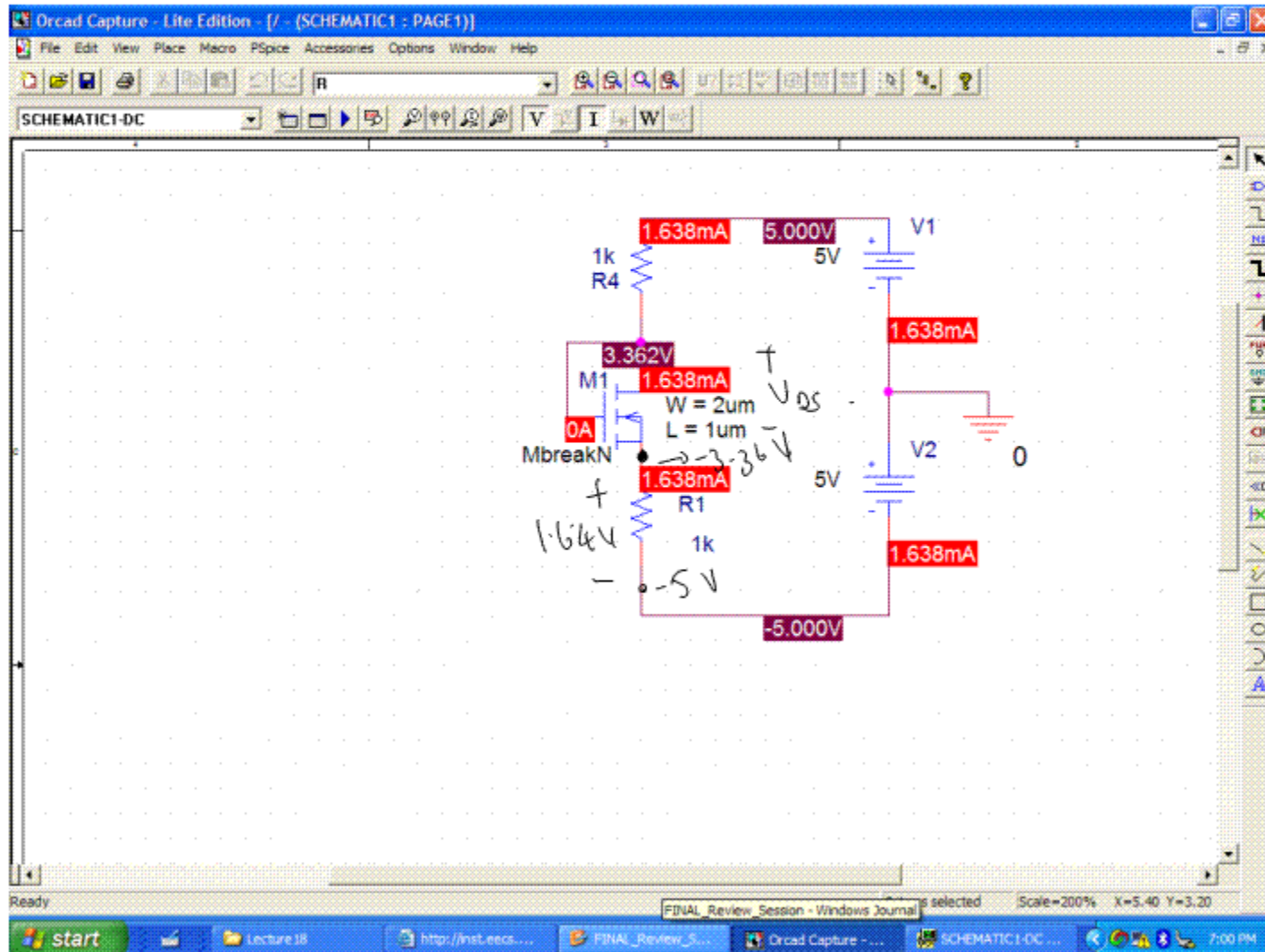
$$V_{DS} = 3.36 - (-3.36) = 6.72 \text{ V}$$



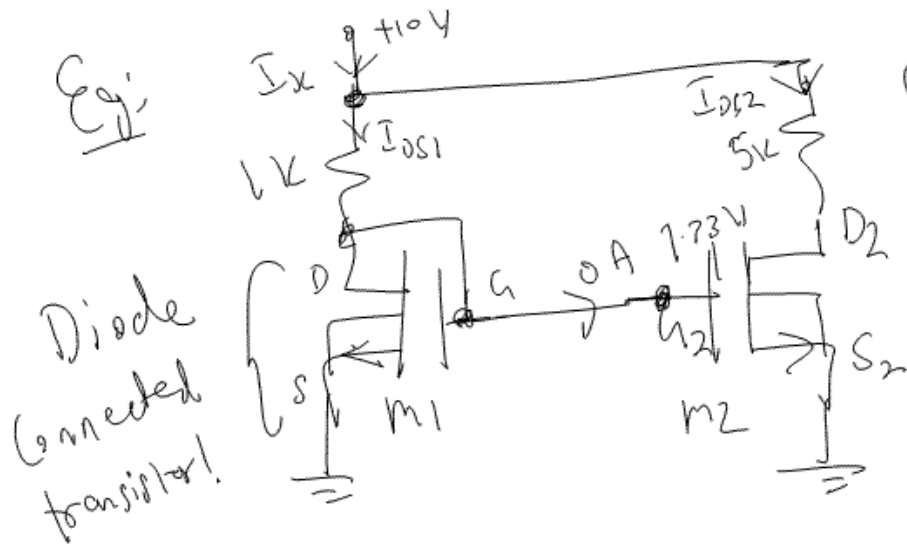

(Q:) Find I_{DC}

Assume $\left(\frac{W}{L}\right) = \left(\frac{2}{1}\right)$,

$k_p = 50 \frac{\mu A}{V^2}$, $V_{T0} = 1V$

for both m_1 & m_2

$$I_{DC} = I_{DS1} + I_{OS2} \text{ (KCU)}$$

I_{OS1} is easy to find as m_1 is saturated.

i.e.:


$$\frac{10 - V_{OS1}}{1k} = \frac{1}{2} (k_p) \left(\frac{W}{L}\right) \left(\underset{V_{OS1}}{V_{GS1}} - V_{T0} \right)^2$$

\Rightarrow solve for $V_{DS1} = 7.73 \text{ V}$, ~~-25 V~~

$$\therefore V_{DS1} = V_{D1} - V_{S1} = 7.73 \text{ V}$$

$$\Rightarrow \boxed{V_{D1} = V_G = 7.73 \text{ V}}$$

Now, solve for I_{DS2} :

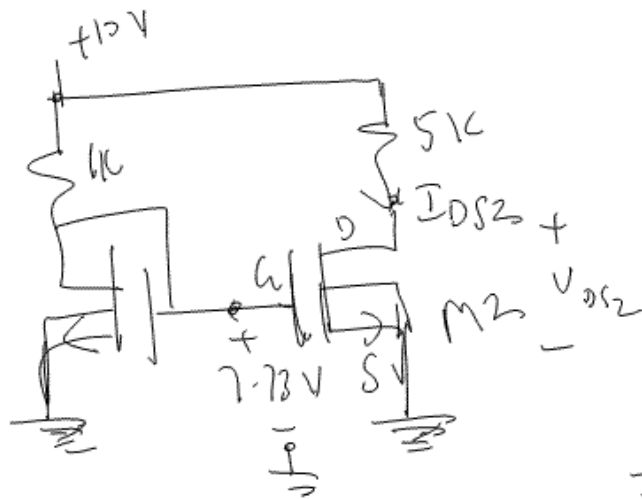

Check m_2 is saturated:

$$V_{DS2} = 5.32 \text{ V} \leftarrow \text{no!}$$

$$V_{GS2} - V_{TH} = 6.73 \text{ V}$$

$$\therefore V_{DS2} < V_{GS2} - V_{TH}$$

\Rightarrow M2 is triode

∴ Assomig m_2 in triode, $V_{DS2} = 10 - 7.3V$
 $= 2.7V$ ✓

∴ $I_{d2} = 3.72 \text{ mA}$

Verbs in PSPICE

