
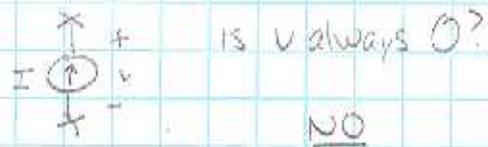



① Final Review 8/10/05

Overall Review & Tips

A) Nodal Analysis

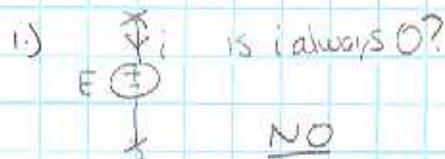


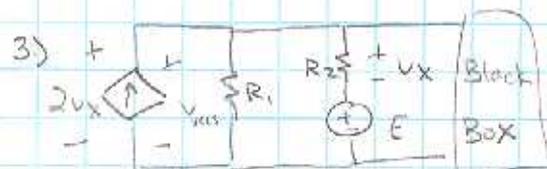2) $P = IV \Rightarrow P = I^2R$ or $P = V^2/R$
ONLY for resistors




$P_{\text{vccs}} = i \cdot V$
 $i = 2V_x$ $V_{\text{vccs}} \neq V_x$

$P \neq (2V_x) \cdot V_x$

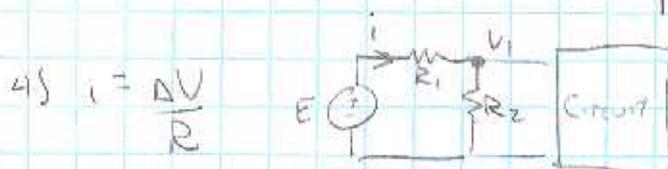

$i = \frac{E \cdot V_1}{R_1}$ NOT $i = \frac{E}{R_1}$

B) Op-Amps

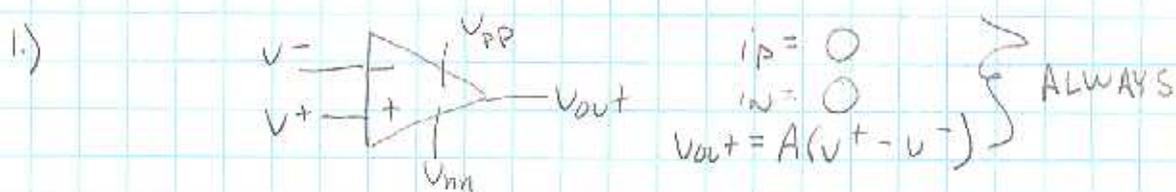

2) Op-Amps on the final may not be idle.

3) If ideal (linear region): $V^+ = V^- \neq A \rightarrow \infty$


4) If voltage/current source is either directly or indirectly connected to $V^- \rightarrow$ op-amp is inverting
 $\neq A_v < 0$

If connected to $V^+ \rightarrow$ non-inverting $\neq A_v > 0$


2

5) Op-Amps ALWAYS amplify. $\rightarrow |A_v| \geq 1$
 $0 < A_v < 1$ ← Never

6) Typical op-amps:

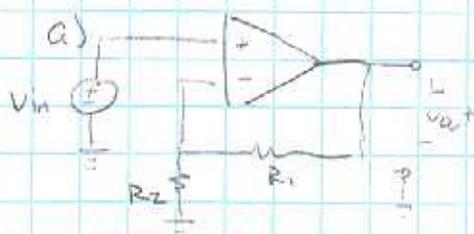


Non-Inverting
 $A_v = 1 + R_2/R_1$

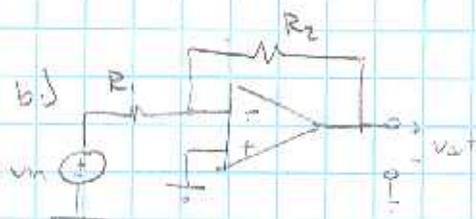

Inverting
 $A_v = -R_2/R_1$

Note: Equations do not hold in cascades

7) Cascade (like 4.18)

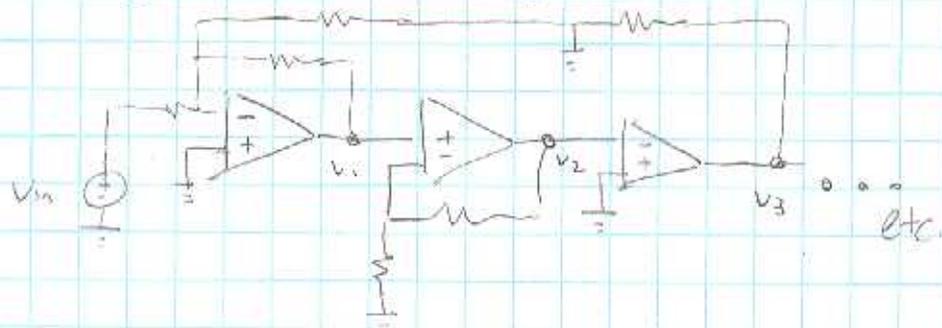

Let $A_1 = v_1/v_{in}$
 $A_2 = v_2/v_1$
 $A_3 = v_3/v_2$
... etc.
 $A_i = v_i/v_{i-1}$

a) $|A_i| \geq 1$ for all i

b) $A_{overall} = \frac{v_{out}}{v_{in}} = A_1 A_2 A_3 \dots$

8) For all diode problems:


a) Assume ideal $\Rightarrow v^+ = v^- \Rightarrow$ Calculate v_{out}

b) If $v_{out} > v_{upp}$, then set $v_{out} = v_{upp}$ & recalculate v^+ & v^-

c) " $v_{out} < v_{lwn}$ " " $v_{out} = v_{lwn}$ " " " " "

3


C) Diodes

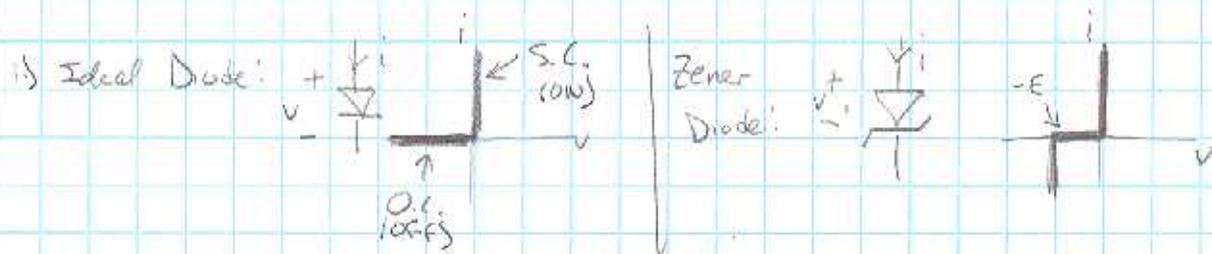

2) Method:

- Guess each diode as either on or off.
- ON = S.C. $\Rightarrow V_D = 0$; OFF = O.C. V_D is unknown \leftarrow calculate.
- Calculate V_D for all off diodes
- IF $V_D < 0 \rightarrow$ Open circuit region \rightarrow Assumption correct
- IF $V_D > 0 \rightarrow$ Short circuit region \rightarrow Assumption wrong



3) Good guesses:

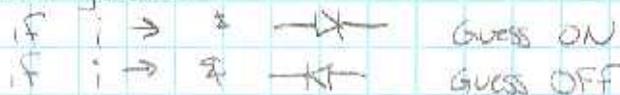

4) Zener Diodes in the breakdown region \rightarrow

Treat diode as voltage source.

D) Transistors

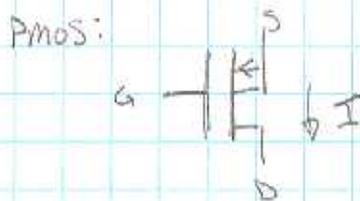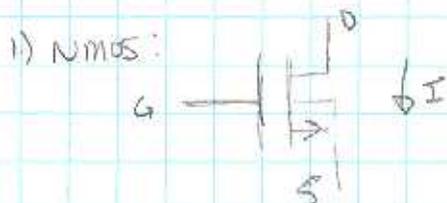

2) Operation Regions & Equations


- Cutoff: $i_D = 0$ for $V_{GS} \leq V_{to}$ (12.1)
- Triode: $i_D = K [2(V_{GS} - V_{to})V_{DS} - V_{DS}^2]$ for $V_{DS} < V_{GS} - V_{to}$ & $V_{GS} \geq V_{to}$ (12.2)
- Saturation: $i_D = K (V_{GS} - V_{to})^2$ for $V_{GS} \geq V_{to}$ & $V_{DS} \geq V_{GS} - V_{to}$ (12.3)

d) Boundary (Triode & Saturation) $\rightarrow V_{DS} = V_{GS} - V_{to}$


e) $K = \left(\frac{W}{L}\right) \frac{K_P}{2}$

4

E) Nonlinear Circuits

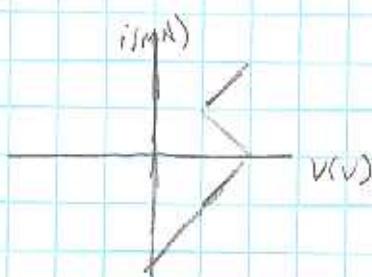

1) Equations & Equilibrium

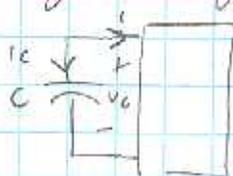

$$i = -C \frac{dv}{dt}$$

$$\frac{dv}{dt} = 0 \Rightarrow i = 0 \Rightarrow \text{Eq.}$$

$$i > 0 \Rightarrow v \downarrow$$

$$i < 0 \Rightarrow v \uparrow$$



$$v = -L \frac{di}{dt}$$

$$\frac{di}{dt} = 0 \Rightarrow v = 0 \Rightarrow \text{Eq.}$$

$$v > 0 \Rightarrow i \downarrow$$

$$v < 0 \Rightarrow i \uparrow$$

2.) Important! Look @ labels!

$$v_C = v, v_L = v, \underline{i_C = -i}, \underline{i_L = -i}$$

3) When finding v_f or i_f , extrapolate the lines forward to the proper equilibrium condition.

C \rightarrow $i = 0$ (x-axis) L \rightarrow $v = 0$ (y-axis)

Note: if in negative slope region, extrapolate backwards to eq.

4) For capacitors, i_f always = 0
For inductors, v_f always = 0

$$5) \text{ Slope} = \frac{\Delta i}{\Delta v} = \frac{1}{R}, \text{ so}$$

$$\tau_C = RC = \frac{\Delta v}{\Delta i} C = \frac{C}{\text{slope}}; \tau_L = \frac{L}{R} = \frac{\Delta i}{\Delta v} L = (\text{slope})^{-1} L$$

6) Always find $i_0, v_0, i_f, v_f, R, C \text{ (or } L), \tau, \tau$ to insert

$$x(t) = x_f + (x_0 - x_f) \exp\left[-\frac{(t-t_0)}{\tau}\right]$$

5

- 7) (i) If not @ eq pt & not heading to one, calculate a switching time.
(ii) If heading towards an eq pt., do not calculate a switching time (it will be ∞).


8.) Shapes of curves?

State of Region	What is x doing?	Draw
Negative	Increasing	
Negative	Decreasing	
Positive	Increasing	
Positive	Decreasing	

6

Problems

1) Op-Amps & AC Analysis

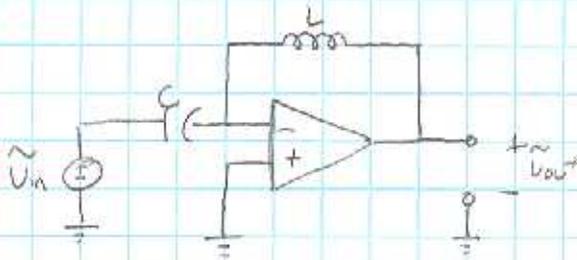

$$\begin{aligned} \tilde{V}_in &= \sin(\omega t) \\ \omega &= 1000 \text{ rad/sec} \\ L &= 1 \text{ mH} \\ C &= 1 \text{ mF} \end{aligned}$$

Use AC analysis to find V_{out}/V_{in} .


Solution: $Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$ $Z_L = j\omega L$

Nodal Analysis: $\textcircled{2} V^-$ $\frac{(V_{in} - 0)}{1/j\omega C} = (V_{in})(j\omega C) = \frac{0 - V_{out}}{j\omega L}$

$$\frac{V_{out}}{V_{in}} = -j^2 \omega^2 LC = -(-1)(1000 \text{ rad/s})^2 (1.001 \frac{\text{V}\cdot\text{s}}{\text{A}})(1.001 \frac{\text{A}\cdot\text{s}}{\text{V}})$$

$$\boxed{= 1}$$

2) Cascading Op-Amp

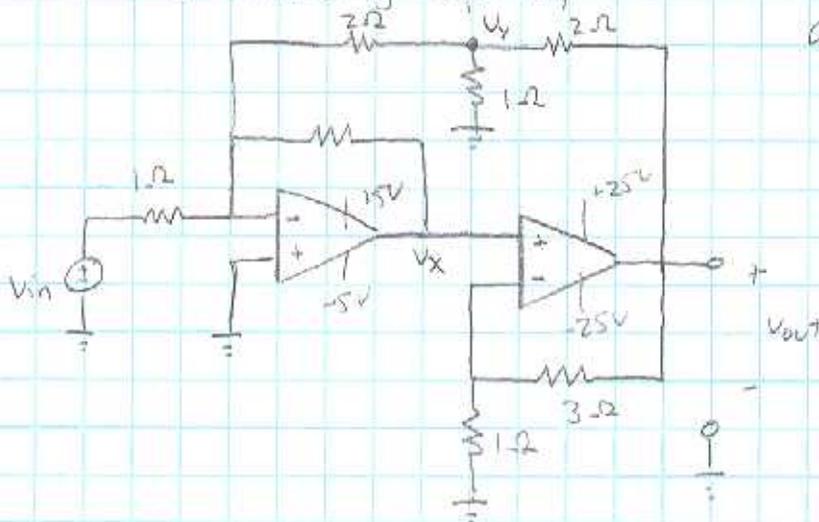

a.) Assume both op-amps are ideal & find V_{out}/V_{in}


b.) Find V_x/V_{in}

c.) $V_{in} = 3V$, Find V_{out}

d.) $V_{in} = -6V$, Find V_{out}

e.) $V_{in} = 30V$, Find V_{out}

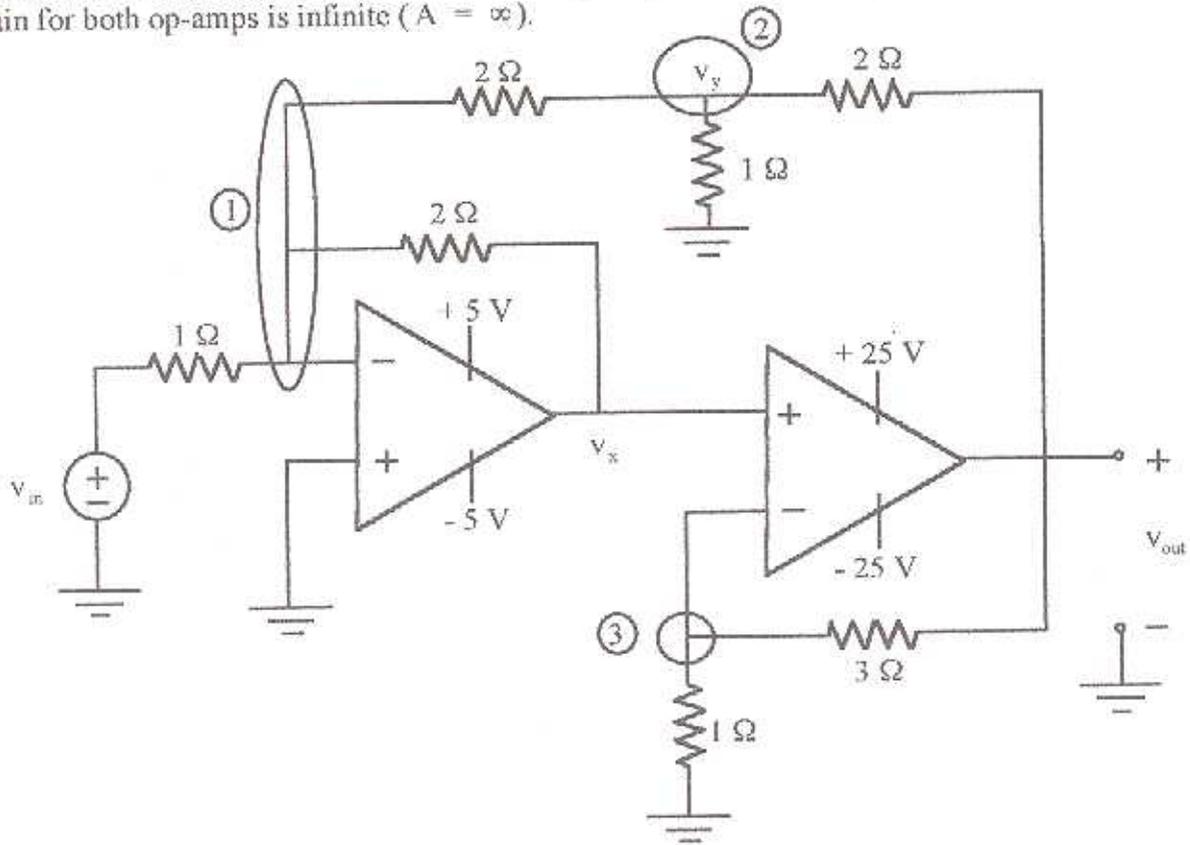7
 Consider the following dual op-amp circuit. Each op-amp has a separate power supply. Assume the open loop gain for both op-amps is infinite ($A = \infty$).



a.) Is the above circuit inverting or non-inverting? Answer this by inspection only. Explain your logic.

Soln: As shown in lecture the label "inverting" or "non-inverting" is dependent on where the input voltage is connected to the op-amp. v_{in} is connected to V_N of the first op-amp, making the first op-amp inverting. The output voltage of the first op-amp is the input of the second op-amp. v_x is connected to V_P of the second op-amp, making this op-amp non-inverting. Thus, overall the input voltage is inverted by the first op-amp and so the overall circuit is **INVERTING**.

b.) Assuming both op-amps are working in the linear region, find the overall closed loop gain: $\frac{V_{out}}{V_{in}}$.

(Hint: it may be useful to find the relationship between v_{out} and v_y or v_x .)

Soln: Since the op-amps are ideal we can assume that $V_P = V_N$.

Nodal analysis at node 3: $\frac{v_{out} - v_x}{3} = \frac{v_x}{1}$, so $v_{out} = 4v_x$.

Nodal analysis at node 2: $\frac{0 - v_y}{2} = \frac{v_y - v_{out}}{2} + \frac{v_y}{1}$, so $v_{out} = 4v_y$.

8

Node 1 is at 0 V because V_p is grounded. Nodal analysis at node 1: $\frac{v_{in} - 0}{1} = \frac{0 - v_x}{2} + \frac{0 - v_y}{2}$.

Substituting from what we got from nodes 2 and 3: $\frac{v_{in} - 0}{1} = \frac{-1}{2} \left(\frac{v_{out}}{4} \right) - \frac{1}{2} \left(\frac{v_{out}}{4} \right)$.

so: $\frac{v_{out}}{v_{in}} = -4$

c.) Using the same assumption, find the closed loop gain of the first op-amp: $\frac{v_x}{v_{in}}$

Soln: Use the node 1 analysis, replace v_y with v_{out} and then replace v_{out} with v_{in} .

$\frac{v_{in}}{1} = \frac{-v_x}{2} - \frac{v_{out}}{8}$, $v_{out} = -4v_{in}$, $\frac{v_{in}}{1} = \frac{-v_x}{2} + \frac{4v_{in}}{8}$.

Rearrange: $\frac{v_x}{v_{in}} = -1$

d.) If $v_{in} = 3$ V, find v_{out} .

Soln: Simple insert into our answers above, BUT WE MUST MAKE SURE TO CHECK FOR SATURATION. If $v_{in} = 3$ V, then $v_x = -3$ V (op-amp 1 not saturated), and $v_{out} = -12$ V (op-amp 2 not saturated).

So: $v_{out} = -12$ V

e.) If $v_{in} = -6$ V, find v_{out} .

Soln: If $v_{in} = -6$ V, then $v_x = +6$ V, but the op-amp is saturated, so $v_x = +5$ V. Op-amp 2 will not saturate.

$v_{out} = +20$ V

f.) If $v_{in} = 30$ V, find v_{out} .

Soln: If $v_{in} = 30$ V, then $v_x = -30$ V, but the op-amp is saturated, so $v_x = -5$ V. Op-amp 2 will not saturate.

$v_{out} = -20$ V


g.) What range of values of v_{in} will saturate the second op-amp? Explain how you came up with your answer.

Soln: A voltage greater than +6.25V or less than -6.25V would be required as a value of v_x to saturate the second op-amp. But because of the different power supplies attached to each op-amp, this can never occur. When the first op-amp saturates, the largest voltage it outputs has a magnitude of 5V. This means that the overall circuit cannot output more than +20V or less than -20V. In other words,

NO VALUES OF AN INPUT VOLTAGE WILL SATURATE THE SECOND OP-AMP.

9

3) Diodes (+ Op-Amp)

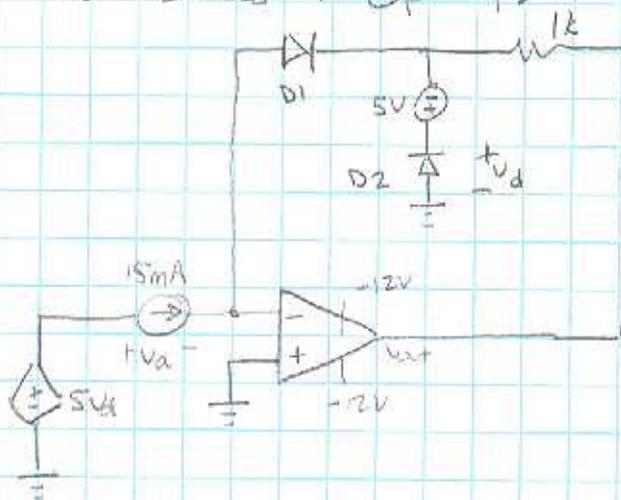


All diodes are ideal
Find v_a .

Solution: Guess state of diodes

D1 seems on * D2 seems off

Assume op-amp is ideal at first.

Redraw:

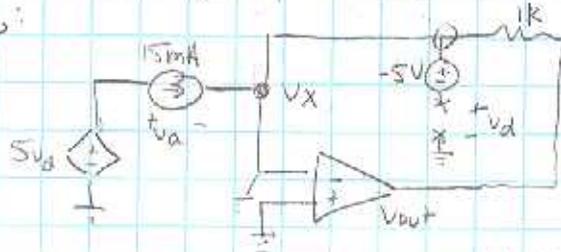

$$v_x = v^- = v^+ = 0$$

$$i_{1k} = 5\text{mA} \quad v_{1k} = 15\text{V}$$

$$v_{out} = 0 - 15\text{V} = -15\text{V}$$

Saturation

$$v_{out} = -12\text{V}$$


$$\frac{v^- - v_{out}}{1k} = 5\text{mA} \Rightarrow v^- + 12 = 15 \Rightarrow v^- = 3\text{V}$$

$$v^- = v_a - 5 \Rightarrow v_a = v^- + 5 = 8\text{V}$$

$$v_a = 5v_d - v_x = 5(3) - 3 = \boxed{37\text{V}}$$

10

4) Transistors

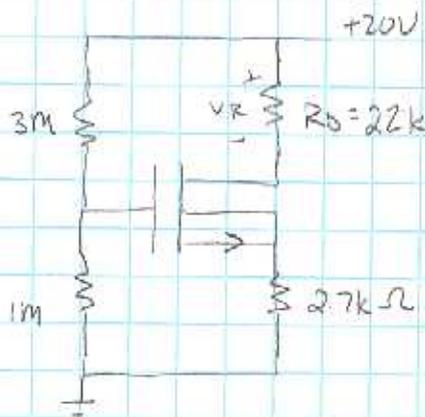

$$K_P = 50 \mu\text{A}/\text{V}^2$$

$$V_{to} = 2\text{V}$$

$$L = 10 \mu\text{m}$$

$$W = 40 \mu\text{m}$$

Find $i_{DS}, V_D, V_S, V_G, V_{GS}, V_{DS}, V_{DGS}$

Solution: Label NMOS:

$$V_G = 20\text{V} \cdot \frac{1\text{m}}{1\text{m} + 3\text{m}} \rightarrow \boxed{V_G = 5\text{V}} \quad V_{GS} = 5 - V_S$$

$$i_D = i_{DS} = V_S / 2.7\text{k}\Omega$$

$$K = \frac{W}{L} \left(\frac{K_P}{2} \right) = \left(\frac{400}{10} \right) \left(\frac{50 \times 10^{-6} \text{A}/\text{V}^2}{2} \right) = 0.001 \text{A}/\text{V}^2$$

$$i_D = K V_{GS}^2$$

$$V_{GS} = V_{GS} - V_{to} = 5 - V_S - 2 = 3 - V_S$$

$$\frac{V_S}{2.7\text{k}} = 0.001 (3 - V_S)^2$$

Solve $\Rightarrow V_S = 2.1149\text{V}$ or 4.2554V
if $V_S = 4.2554 \Rightarrow V_{GS} = 5 - V_S = 0.7446 \Rightarrow < V_{to} \Rightarrow$ WRONG

$$V_S = 2.1149\text{V} \Rightarrow V_{GS} = 2.8851\text{V} \geq V_{to} \Rightarrow \text{ON}$$

Saturation? is $V_{GS} \geq V_{GS} - V_{to}$?

$$V_{DS} = 2.8851 - 2 = 0.8851\text{V}$$

$$I_{DS} = \frac{V_S}{2.7\text{k}} = 783.2963 \mu\text{A} \rightarrow V_R = 17.2325\text{V}$$

$$V_D = 20 - 17.9824 = 2.7675\text{V}$$

$$V_{DS} = 0.6526$$

$0.6526 < 0.8851$
NOT IN SATURATION REGION
 \rightarrow TRIODE

11

$$i_D = K \left[2 (V_{GS} - V_{th}) V_{DS} - V_{DS}^2 \right]$$

$$V_{GS} - V_{th} = 3 - V_S, \quad V_{DS} = V_D - V_S = 20 - (22k) i_{DS} - V_S$$
$$V_{DS} = 20 - \frac{22 V_S}{2.7} - V_S = 20 - \frac{24.7 V_S}{2.7}$$

$$\frac{V_S}{2700} = 0.001 \left[2(3 - V_S) \left(20 - \frac{24.7 V_S}{2.7} \right) - \left(20 - \frac{24.7 V_S}{2.7} \right)^2 \right]$$

Solve: $V_S = 2.1046V$ or $V_S = 2.0345$

V_S	$V_{GS} - V_{th} = 3 - V_S$	$V_{DS} = 20 - 24.7 V_S / 2.7$	VALID?
2.1046	0.8954	0.7468	NO
2.0345	0.9655	1.3881	YES

So, in conclusion

$$V_G = 5V, \quad V_S = 2.0345V, \quad V_D = 3.4226V$$
$$V_{GS} = 2.9655V, \quad V_{DS} = 1.3881V, \quad V_{DGS} = 1.5774V$$

$$i_{DS} = 753.5735 \mu A$$

$$V_R = 16.5774V$$

Try again w/ $R_D = 2.7k\Omega$



→ Saturation Region, so

$$V_G = 5V, \quad V_S = 2.1149V, \quad V_D = 16.3185V$$
$$V_{GS} = 2.8851V, \quad V_{DS} = 14.2036V, \quad V_{DGS} = 11.3185V$$

$$i_{DS} = 783.2963 \mu A \quad V_R = 3.6815V$$

12

5) Non-linear Problem

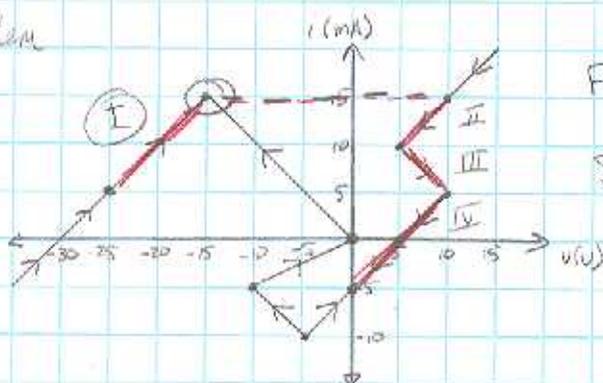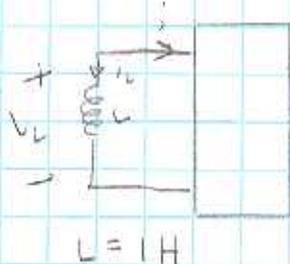

Find graph
 $v(t)$ & $i(t)$
 Start @ $v_0(0) = -25$

$$\frac{-v}{L} = \frac{di}{dt} \quad \frac{di}{dt} = 0 \rightarrow \text{Eq. } \textcircled{1} \quad v=0 \quad v > 0, i \downarrow ; v < 0, i \uparrow$$

Impasse Pt $\textcircled{2}$ $(-15V, 5mA) \rightarrow$ jumps to $(10V, 5mA)$

Region I: $v_0 = -25, v_{\infty} = 0 \quad R = 1000 \Omega \quad \tau = 0.001s$
 $i_0 = 30, i_{\infty} = 5 \quad L = 1H \quad t_0 = 0$
 $v(t) = -25 \exp[-1000t]$
 $i(t) = 30 - 25 \exp[-1000t]$ for $0 \leq t \leq t_1$
 $t_1 \textcircled{1} \quad v = -15V \quad t_1 = \ln(2/3)/1000$

Region II: $v_0 = 10, v_{\infty} = 0 \quad R = 1000 \Omega \quad \tau = 0.001s$
 $i_0 = 15, i_{\infty} = 5 \quad L = 1H \quad t_1 = \ln(10/5)/1000$
 $v(t) = 10 \exp[-1000(t-t_1)]$
 $i(t) = 5 + 10 \exp[-1000(t-t_1)]$ for $t_1 \leq t \leq t_2$
 $t_2 \textcircled{2} \quad v = 5 \quad t_2 = t_1 + \ln 2 / 1000 = \ln(10/3)/1000$

Region III: $v_0 = 5, v_{\infty} = 0 \quad R = 1000 \Omega \quad \tau = 0.001s$
 $i_0 = 10, i_{\infty} = 15 \quad L = 1H$
 $v(t) = 5 \exp[+1000(t-t_2)]$ for $t_2 \leq t \leq t_3$
 $i(t) = 15 - 5 \exp[+1000(t-t_2)]$
 $t_3 \textcircled{3} \quad v = 10 \quad t_3 = t_2 + \ln 2 / 1000 = \ln(20/5)/1000$

Region IV: $v_0 = 10, v_{\infty} = 0 \quad R = 1000 \Omega \quad \tau = 0.001s$
 $i_0 = 5, i_{\infty} = -5 \quad L = 1H$
 $v(t) = 10 \exp[-1000(t-t_3)]$
 $i(t) = -5 + 10 \exp[-1000(t-t_3)]$ for $t \geq t_3$

13

Plots of $v(t)$ & $i(t)$

