
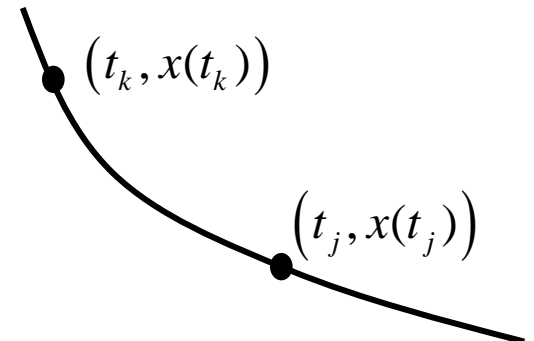


Elapsed Time Formula

$$t_k - t_j = \tau \ln \frac{x(t_j) - x(t_\infty)}{x(t_k) - x(t_\infty)}$$

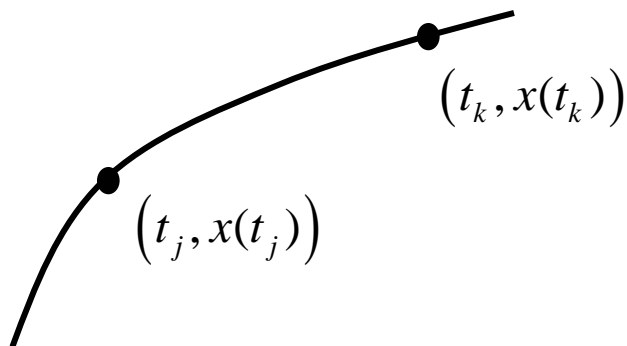$\left. \begin{array}{l} (t_j, x(t_j)) \\ (t_k, x(t_k)) \end{array} \right\}$ any point lying on an exponential waveform with positive or negative τ



1st-order Linear Time-Invariant Circuits Driven by DC Sources

State Equation

$$\dot{x} = -\frac{x}{\tau} + \frac{x(t_\infty)}{\tau}$$


τ = time constant

$x(t_\infty)$ = Equilibrium Point

$x(t_0)$ = Initial State at $t = t_0$

Solution:
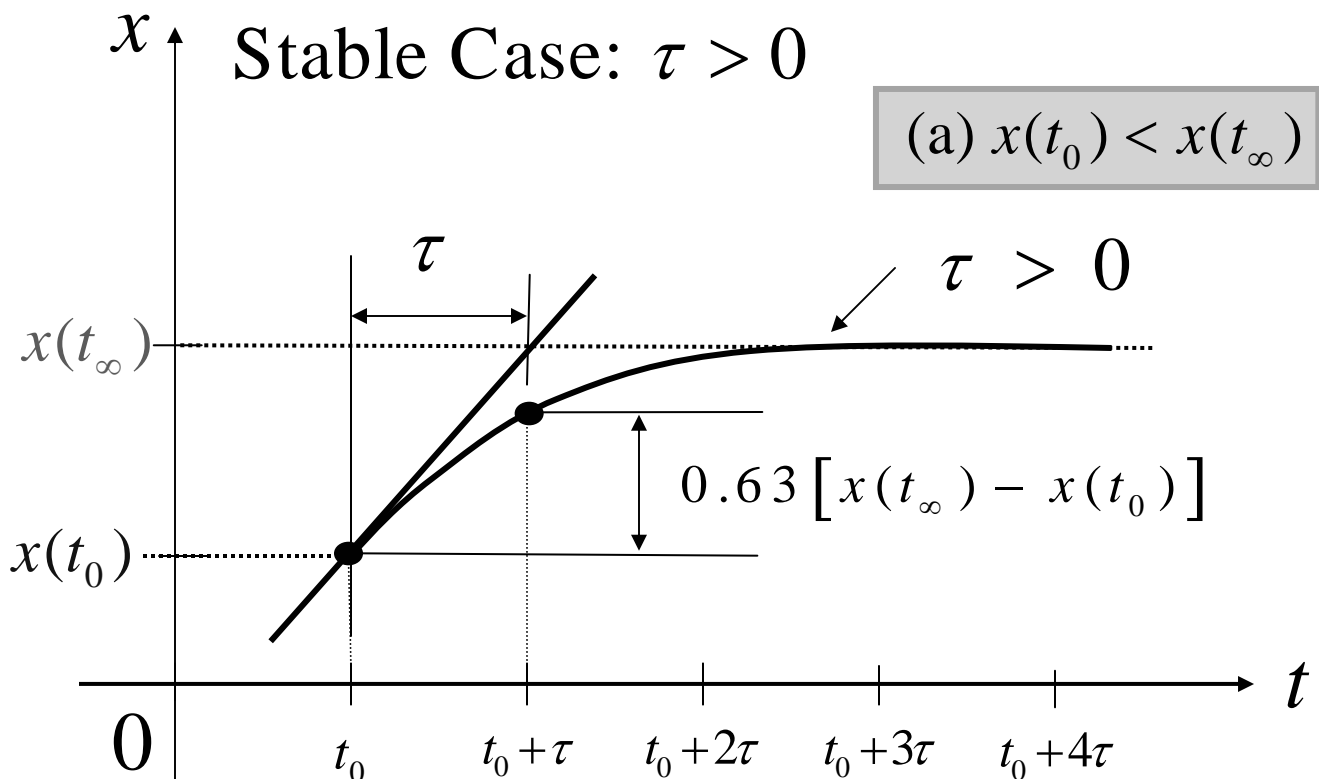
$$x(t) = x(t_\infty) + [x(t_0) - x(t_\infty)] e^{-\frac{(t-t_0)}{\tau}}$$



1st-order Linear Time-Invariant Circuits Driven by DC Sources

State Equation

$$\dot{x} = -\frac{x}{\tau} + \frac{x(t_\infty)}{\tau}$$


τ = time constant

$x(t_\infty)$ = Equilibrium Point

$x(t_0)$ = Initial State at $t = t_0$


Solution:
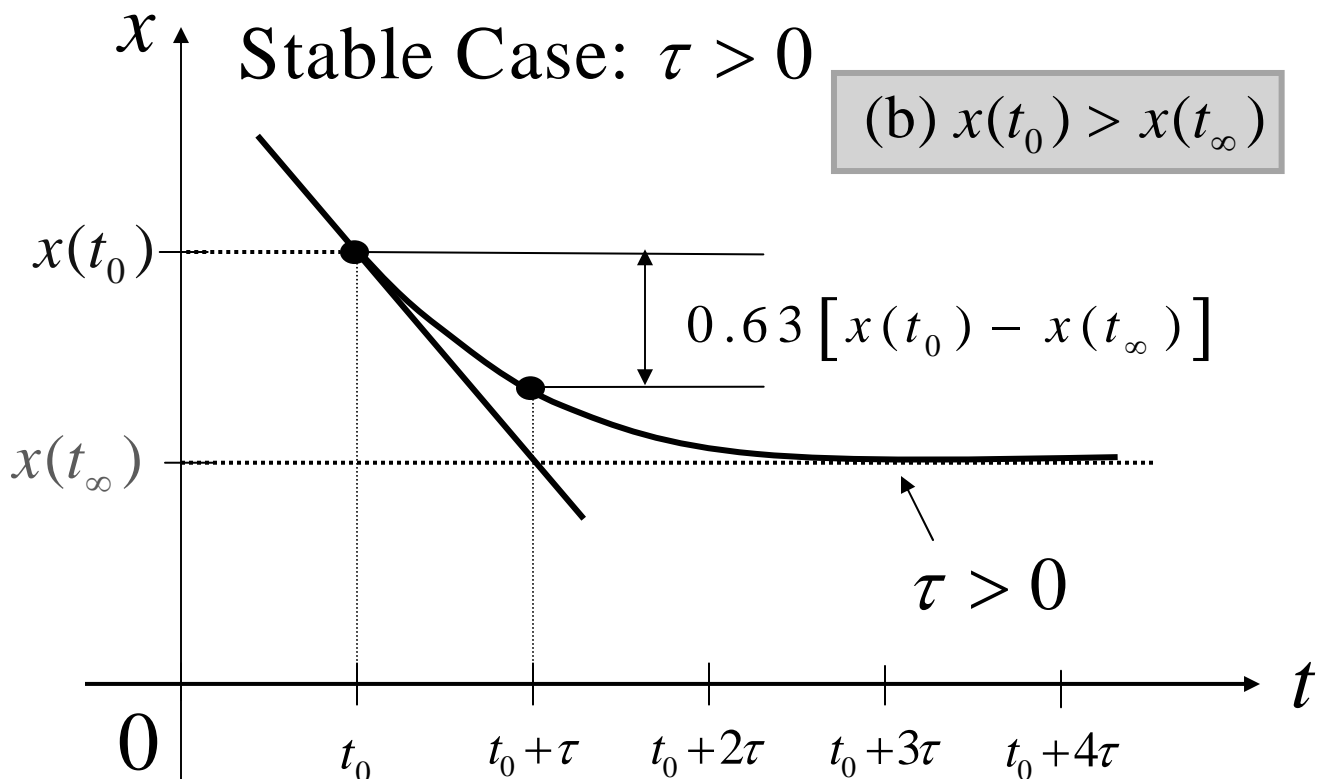
$$x(t) = x(t_\infty) + [x(t_0) - x(t_\infty)] e^{-\frac{(t-t_0)}{\tau}}$$




Unstable Case: $\tau < 0$


(a) $x(t_0) > x(t_\infty)$

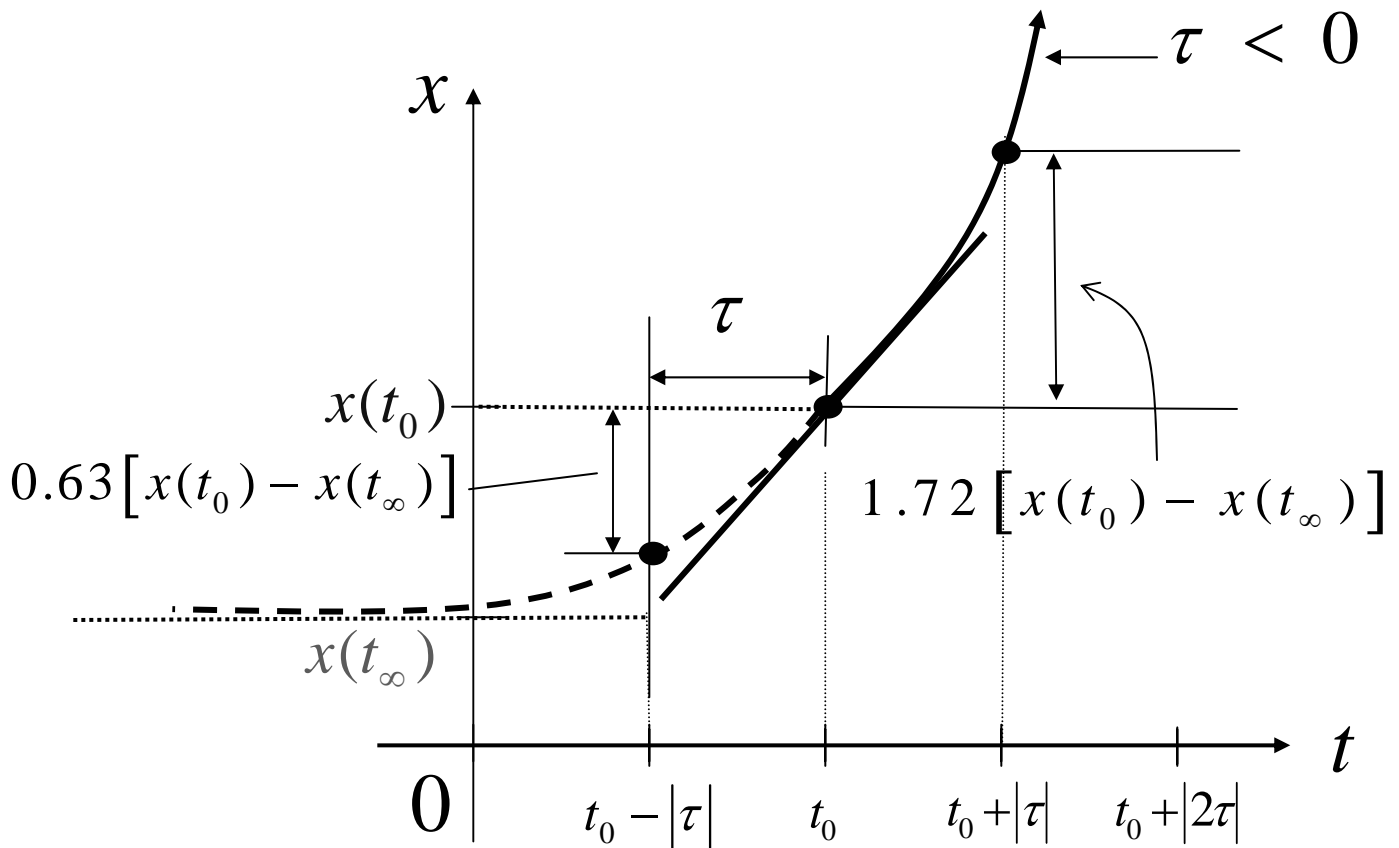

Unstable Case: $\tau < 0$

(b) $x(t_0) < x(t_\infty)$

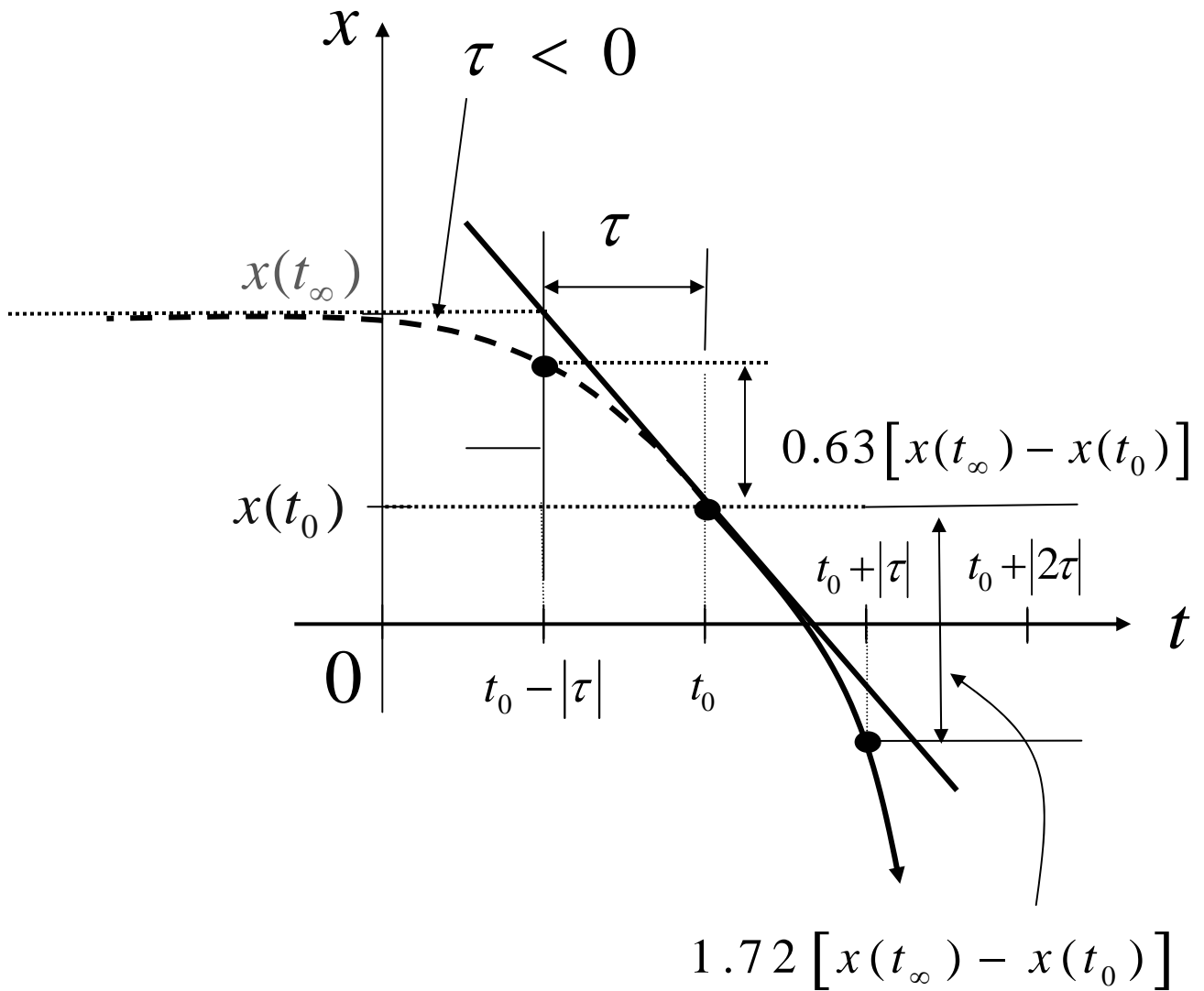

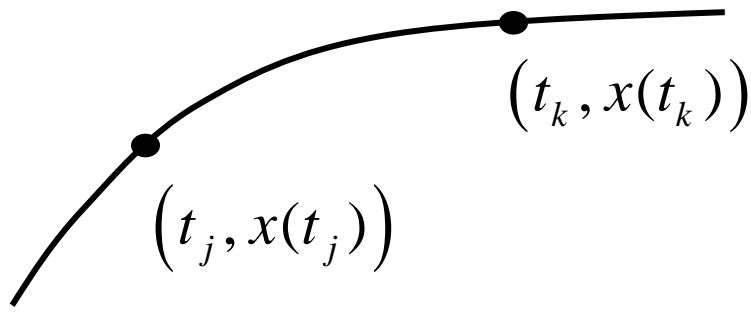

$$x(t_j) - x(t_\infty) = [x(t_0) - x(t_\infty)] e^{-\frac{(t_j - t_0)}{\tau}}$$

$$x(t_k) - x(t_\infty) = [x(t_0) - x(t_\infty)] e^{-\frac{(t_k - t_0)}{\tau}}$$


$$\frac{x(t_j) - x(t_\infty)}{x(t_k) - x(t_\infty)} = \frac{e^{-\frac{(t_j - t_0)}{\tau}}}{e^{-\frac{(t_k - t_0)}{\tau}}} = e^{\frac{(t_k - t_j)}{\tau}}$$

$$\ln \left[\frac{x(t_j) - x(t_\infty)}{x(t_k) - x(t_\infty)} \right] = \frac{(t_k - t_j)}{\tau}$$

\Rightarrow

$$t_k - t_j = \tau \ln \left[\frac{x(t_j) - x(t_\infty)}{x(t_k) - x(t_\infty)} \right]$$


Driving-Point Characteristic

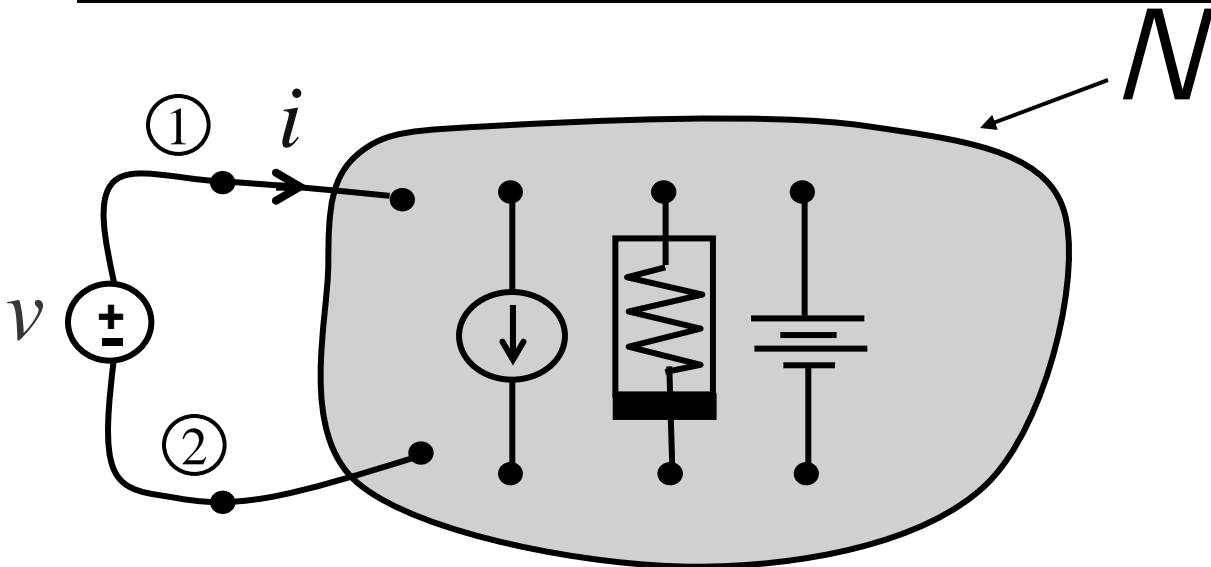


The 2 nodes { ① , ② } where the voltage source is connected are called **driving-point terminals**.

The i -vs.- v driving-point **characteristic** is the set of all (i,v) which simultaneously satisfy:

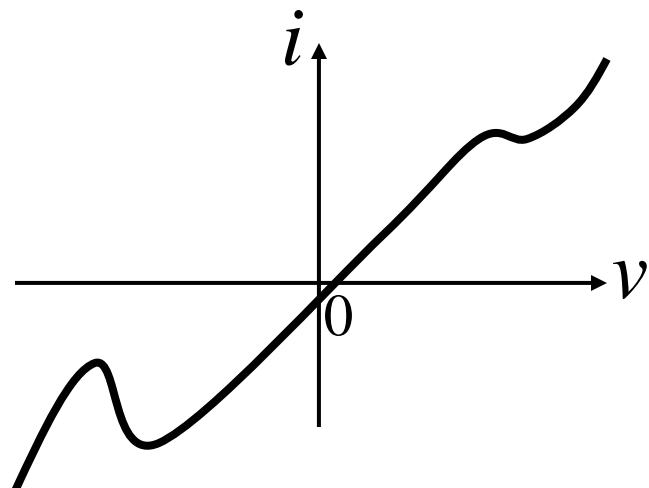1. KCL
2. KVL
3. Constitutive Relation of all elements inside N



Transfer Characteristic

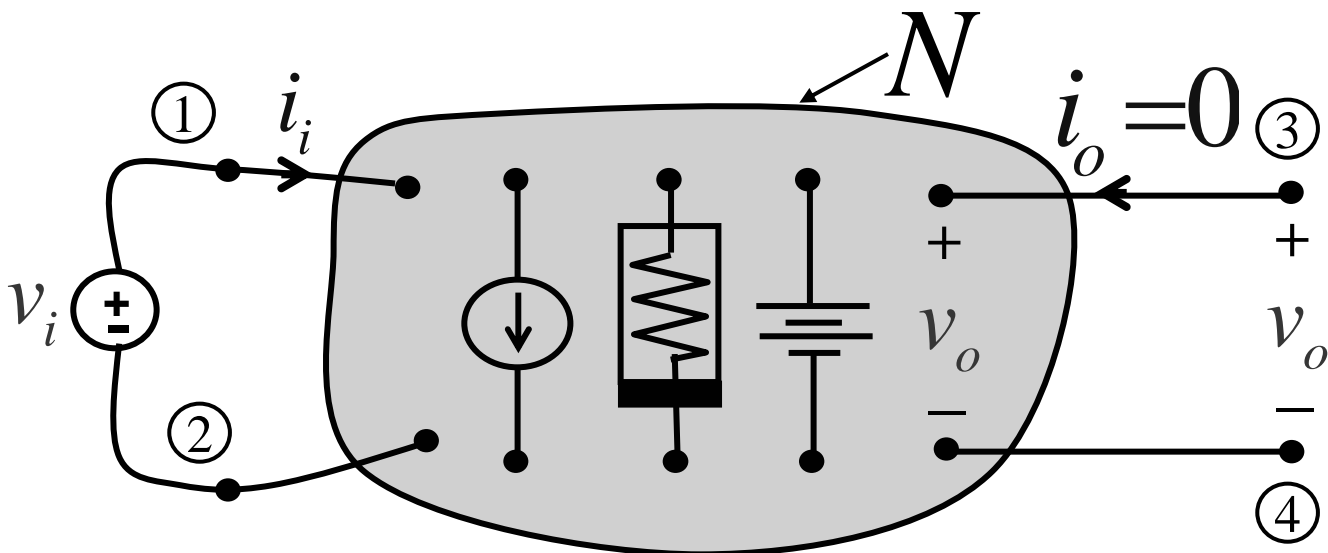


Nodes ① and ② are called driving-point terminals.



Remark:

The v_o -vs.- v_i **transfer characteristic** is the set of all (v_i, v_o) which simultaneously satisfy:

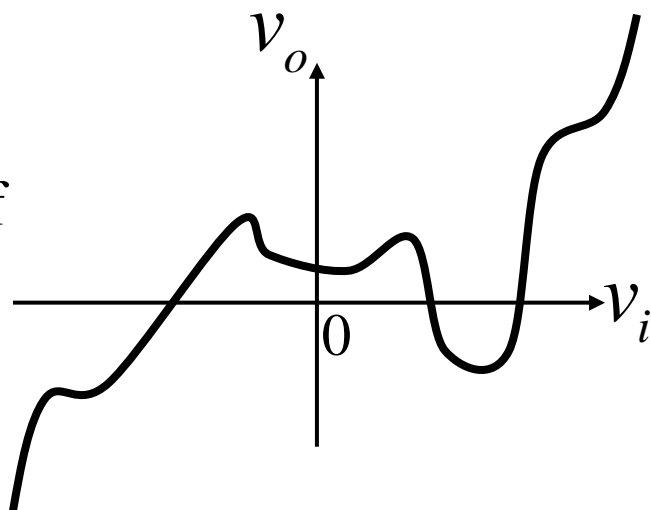1. KCL
2. KVL
3. $v - i$ characteristics of all elements inside N
4. $i_o = 0$
(no-loading condition)



TC (Transfer) Plot

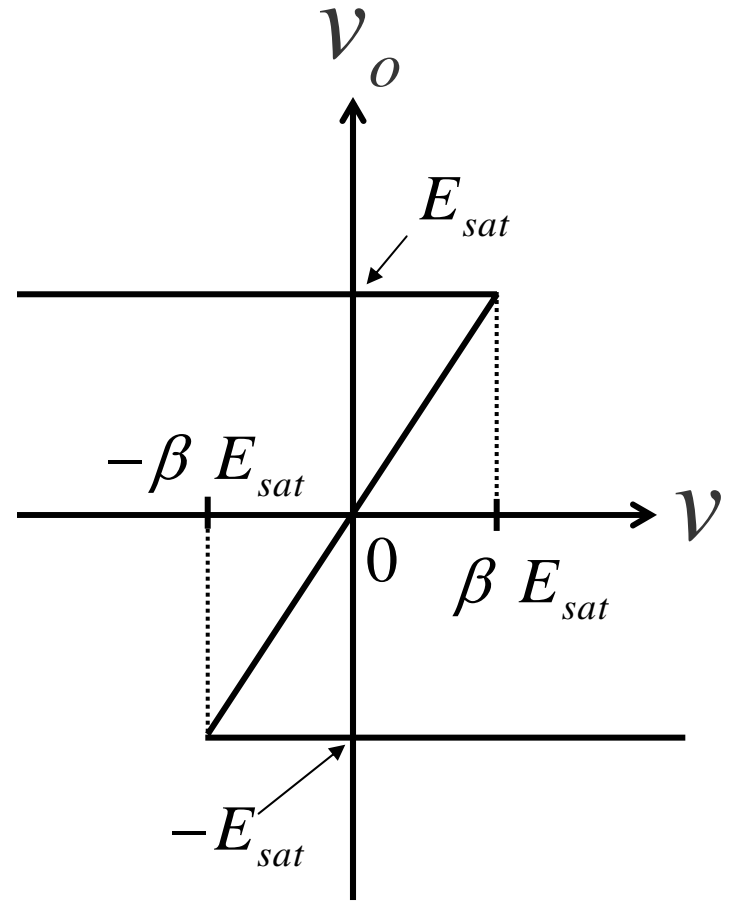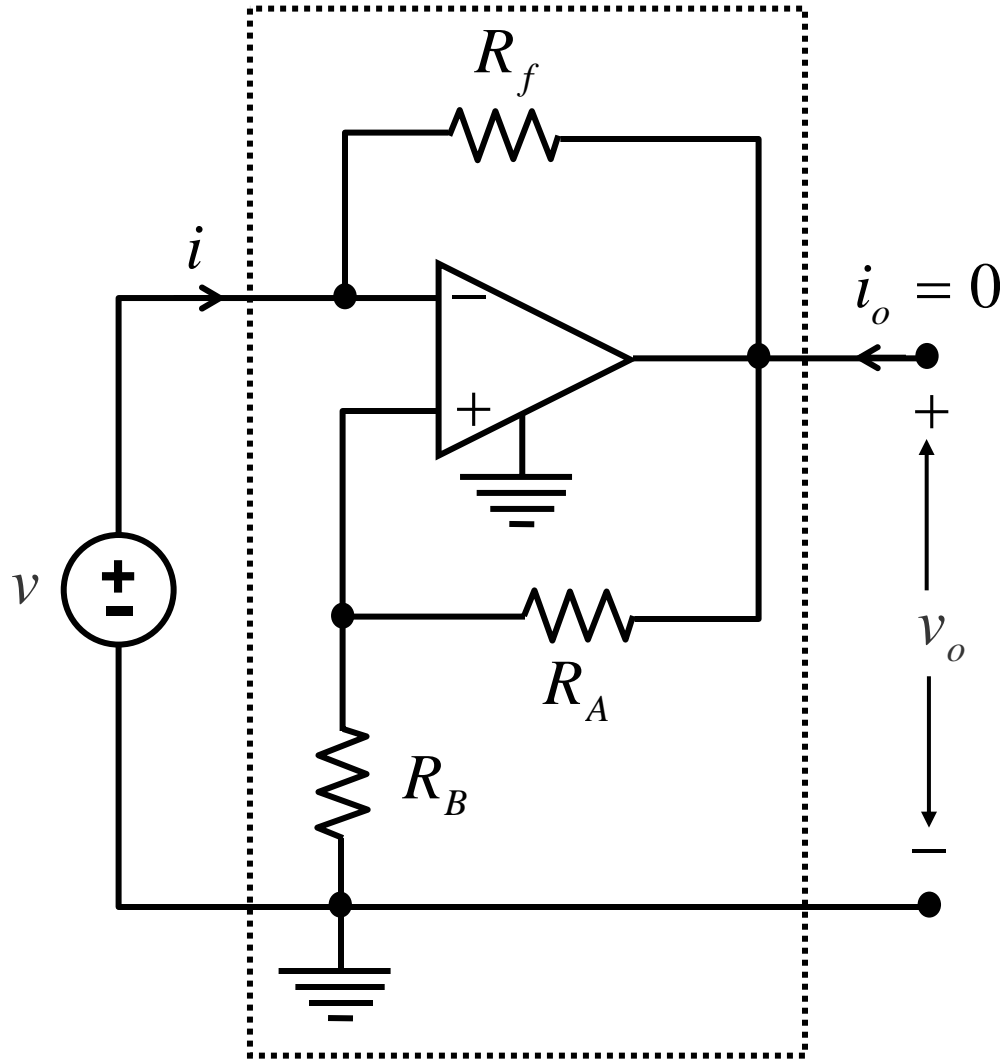

DP (Driving-Point) Plot

