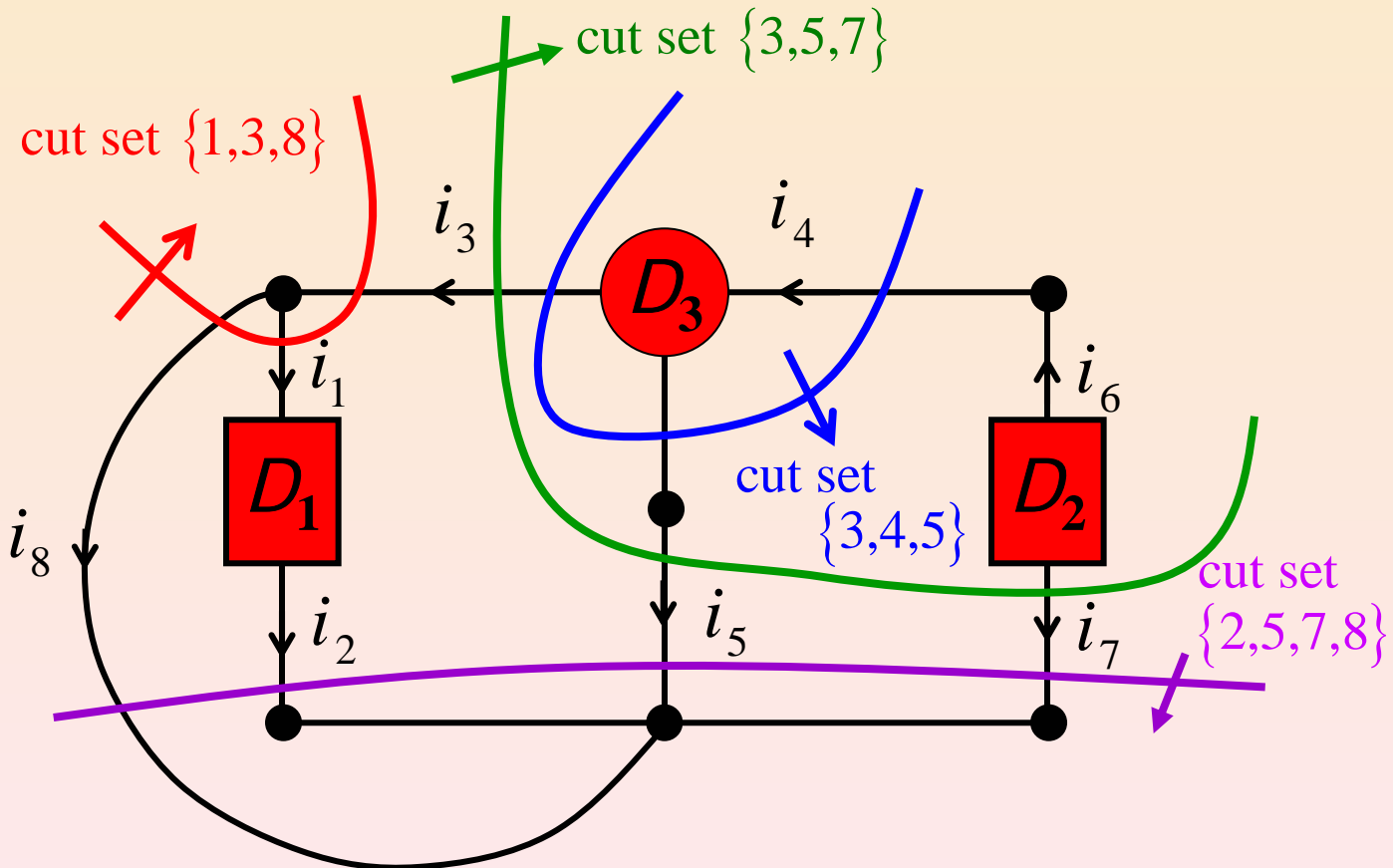


KCL

Before writing KCL on a cut set, we assign *arbitrarily* a positive reference direction by an arrowhead.



Some Examples of cut sets

KCL cut set equations

$$\{3,5,7\} \Rightarrow -i_3 - i_5 - i_7 = 0$$




$$\{1,3,8\} \Rightarrow i_3 - i_1 - i_8 = 0$$

$$\{2,5,7,8\} \Rightarrow i_2 + i_5 + i_7 + i_8 = 0$$



$$\{3,4,5\} \Rightarrow i_3 - i_4 + i_5 = 0$$

A Circuit with 3 different digraphs




1. Choose ③ as datum for D

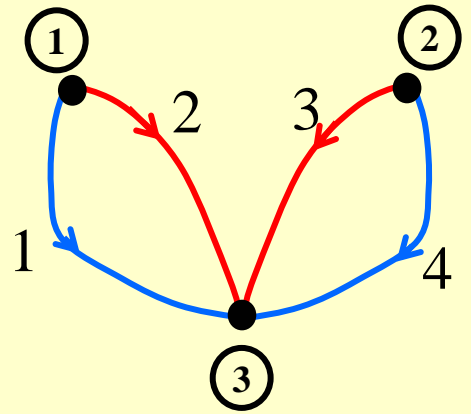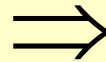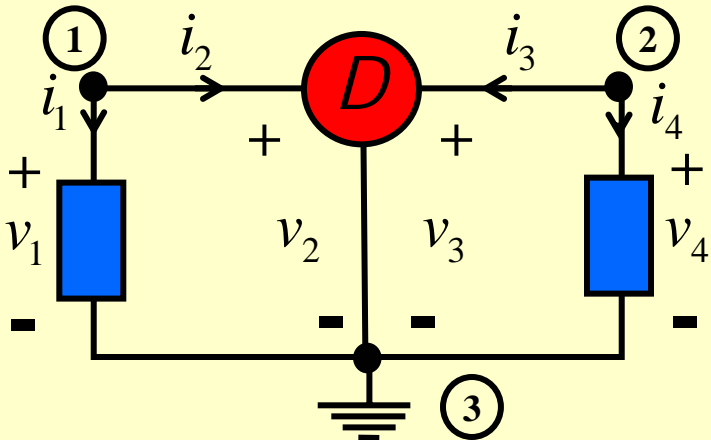




2. Choose ② as datum for D

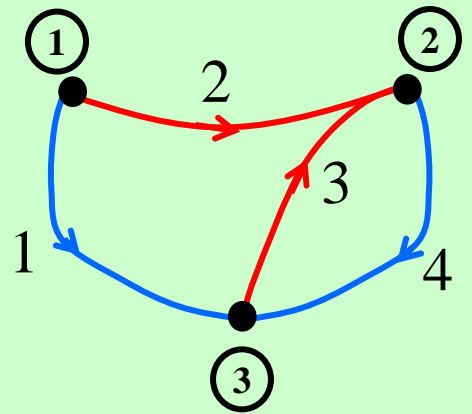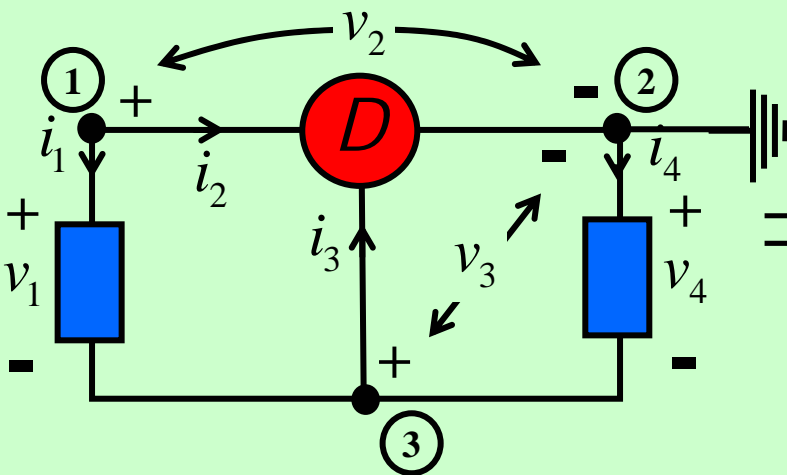

3. Choose ① as datum for D

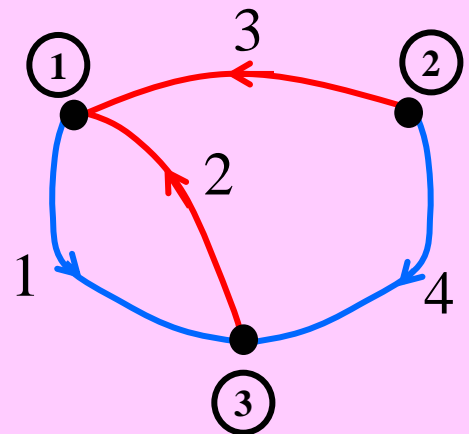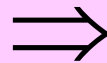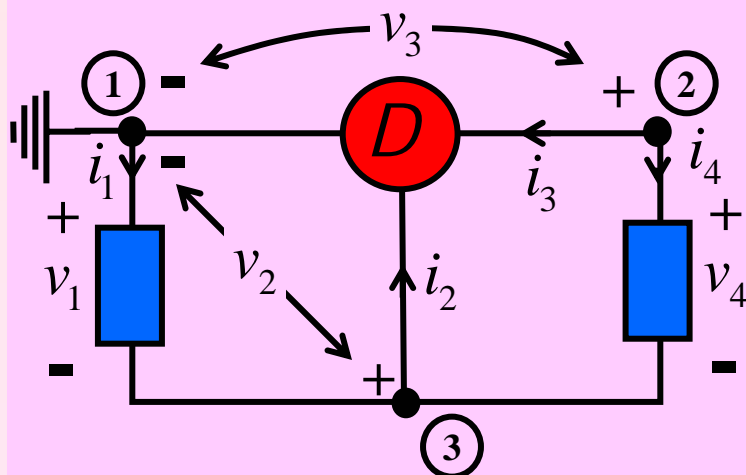

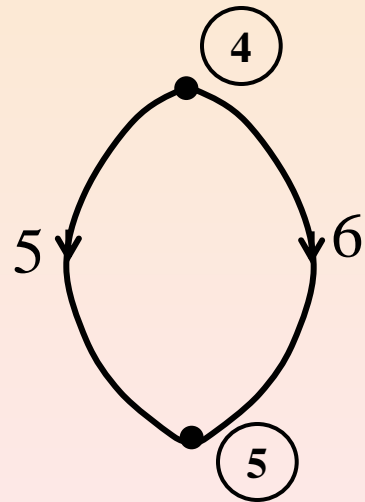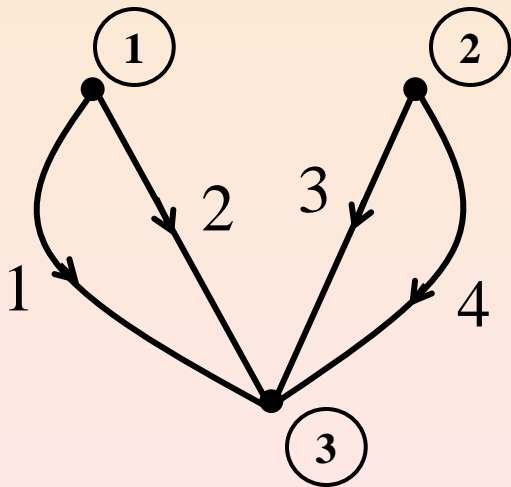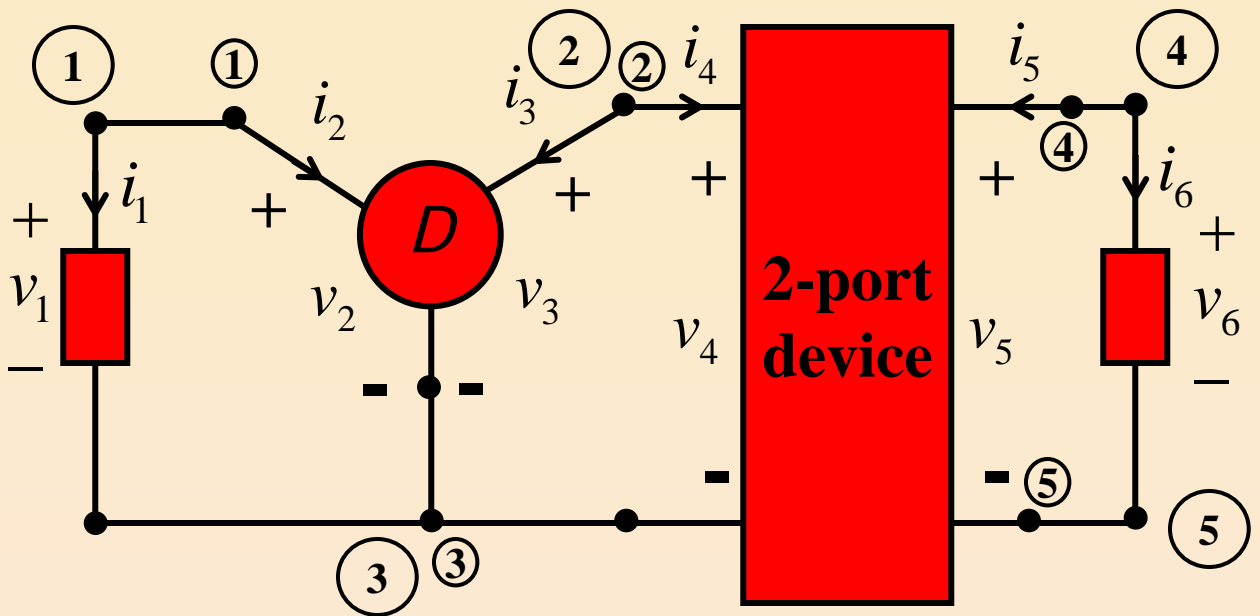- Circuits containing n -terminal devices can have many distinct digraphs, due to different (arbitrary) choices of the datum terminal for each n -terminal device.
- Although the KCL and KVL equations associated with 2 different digraphs of a given circuit are different, they contain the same information because each set of equations can be derived from the other.





disconnected digraph

$$\text{KCL at } \textcircled{2} : \quad i_3 + i_4 = 0$$



$$\text{KCL at } \textcircled{4} : \quad i_5 + i_6 = 0$$

$$\text{KVL around } \textcircled{2} - \textcircled{3} - \textcircled{2} : \quad v_4 - v_3 = 0$$

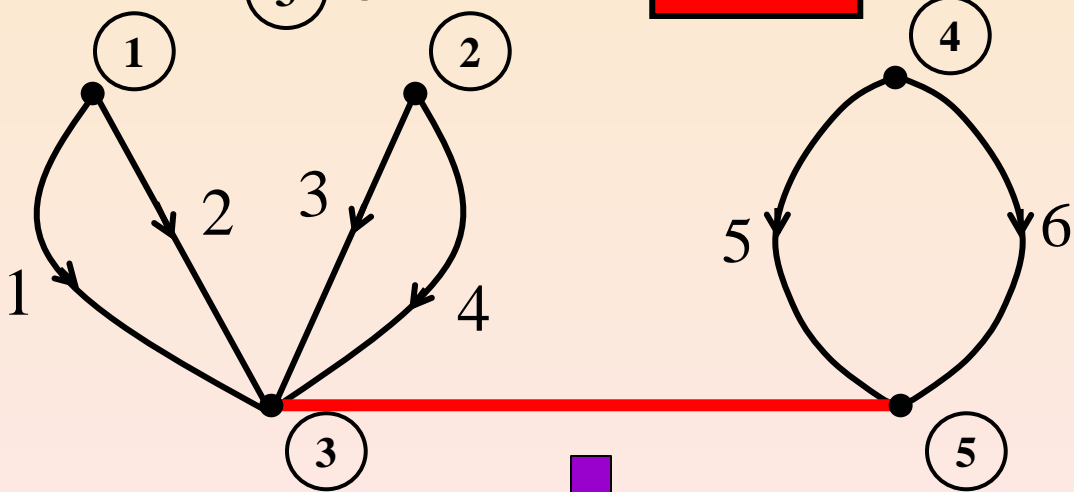
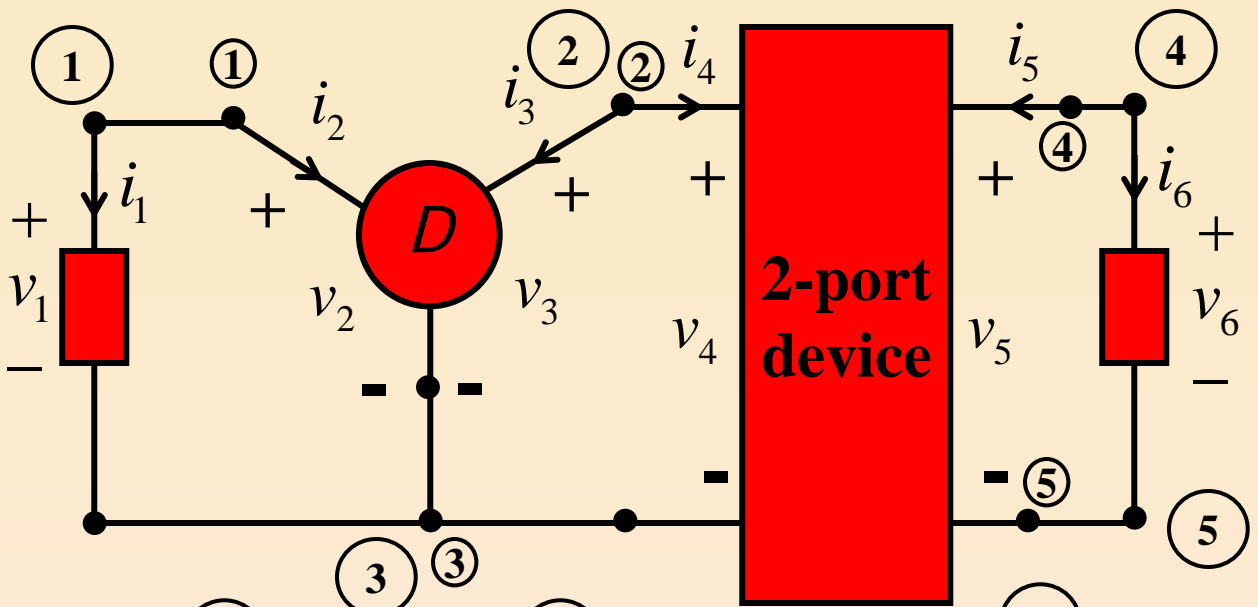
$$\text{KVL around } \textcircled{4} - \textcircled{5} - \textcircled{4} : \quad v_6 - v_5 = 0$$





HINGED DIGRAPH

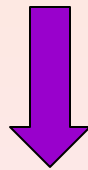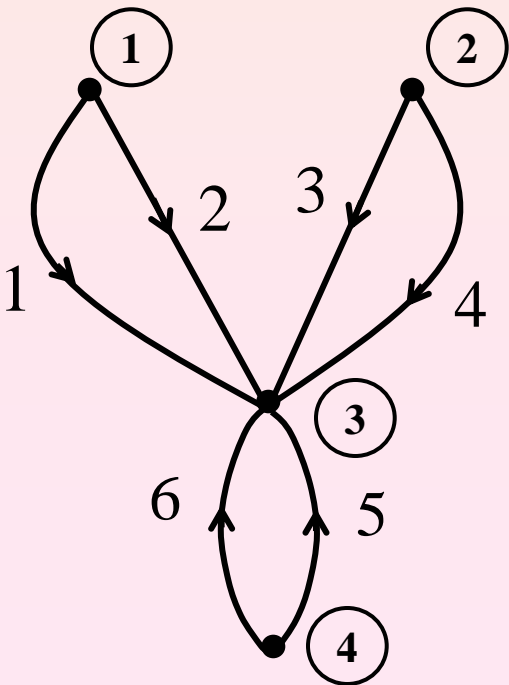

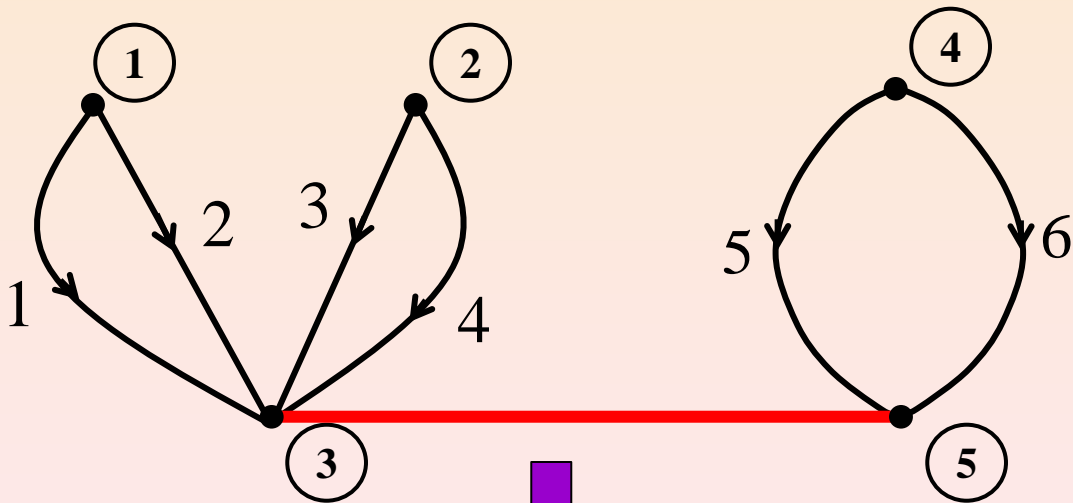
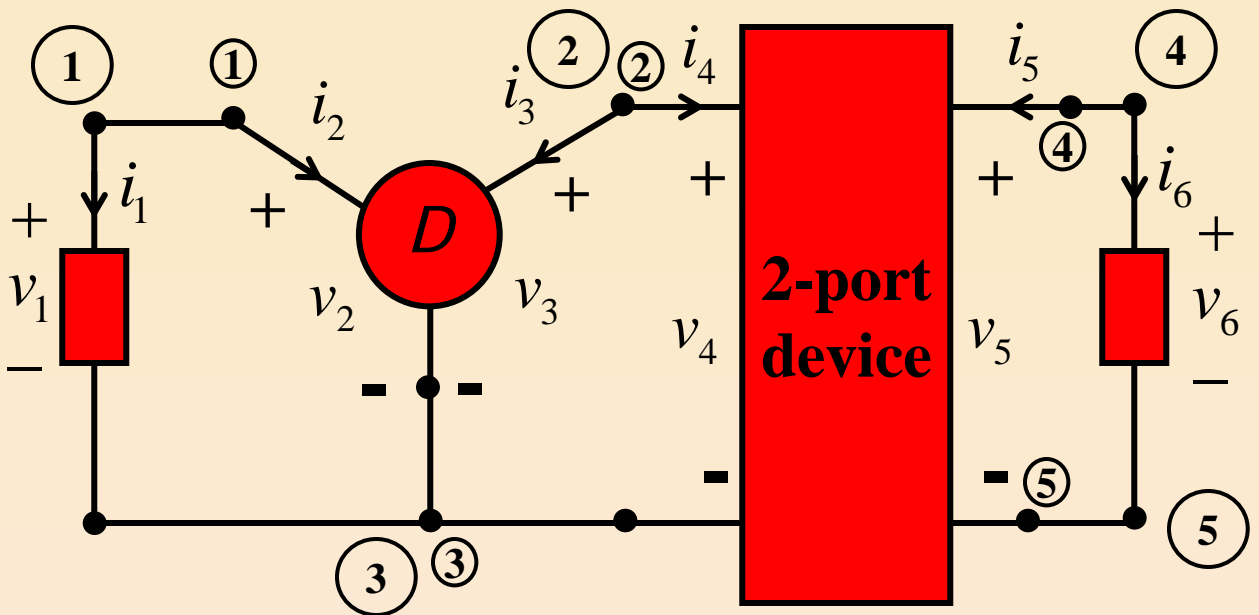
Since nodes (3) and (5) are now the same node, they can be combined into one node, and the redrawn digraph is called a **hinged** graph.



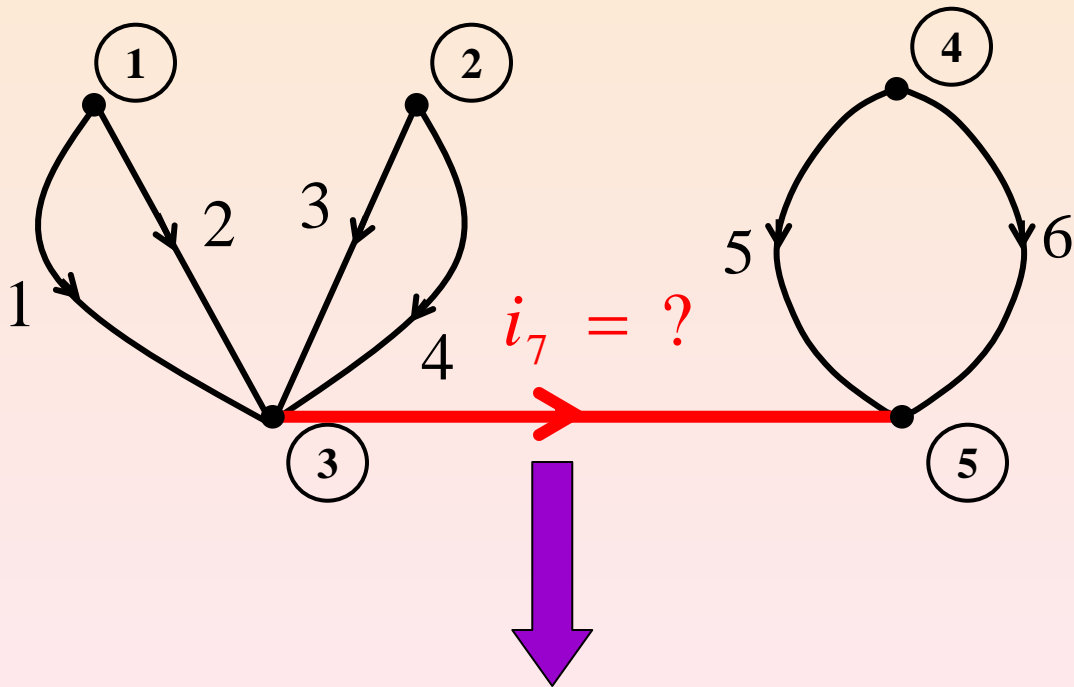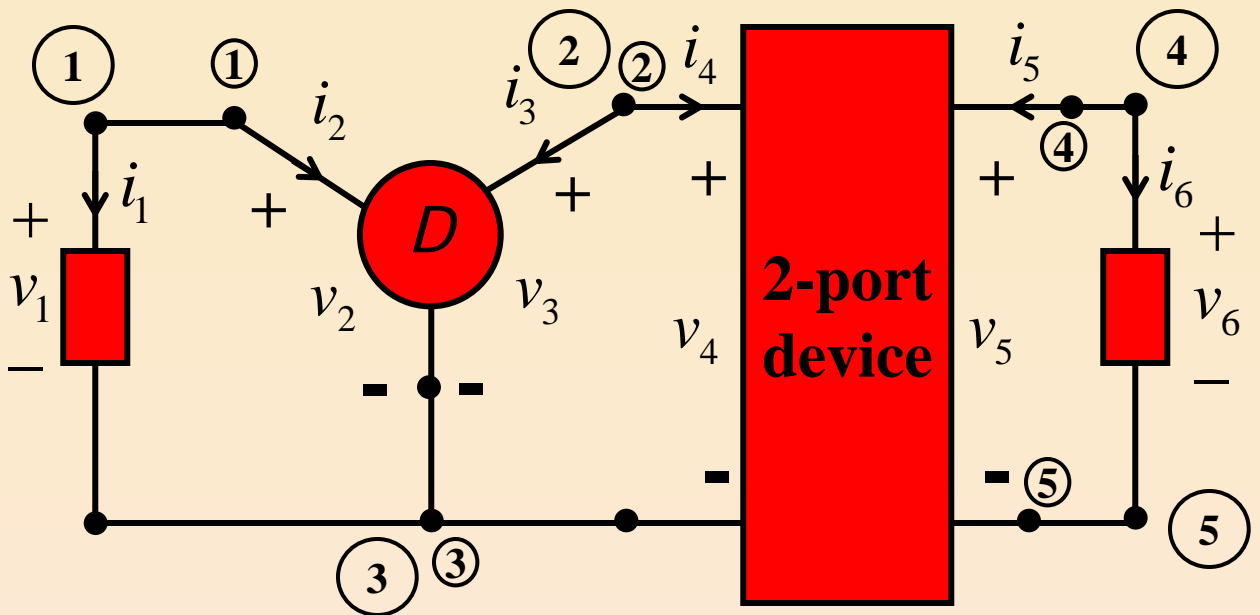Adding a wire connecting one node from each separate component does **not** change KVL or KCL equations.



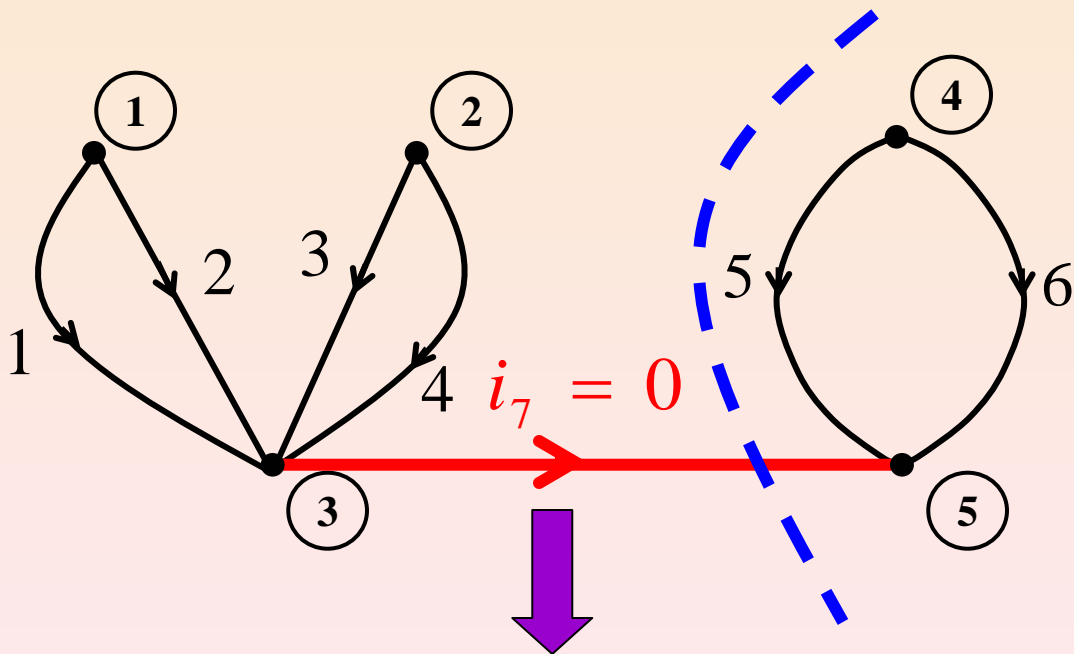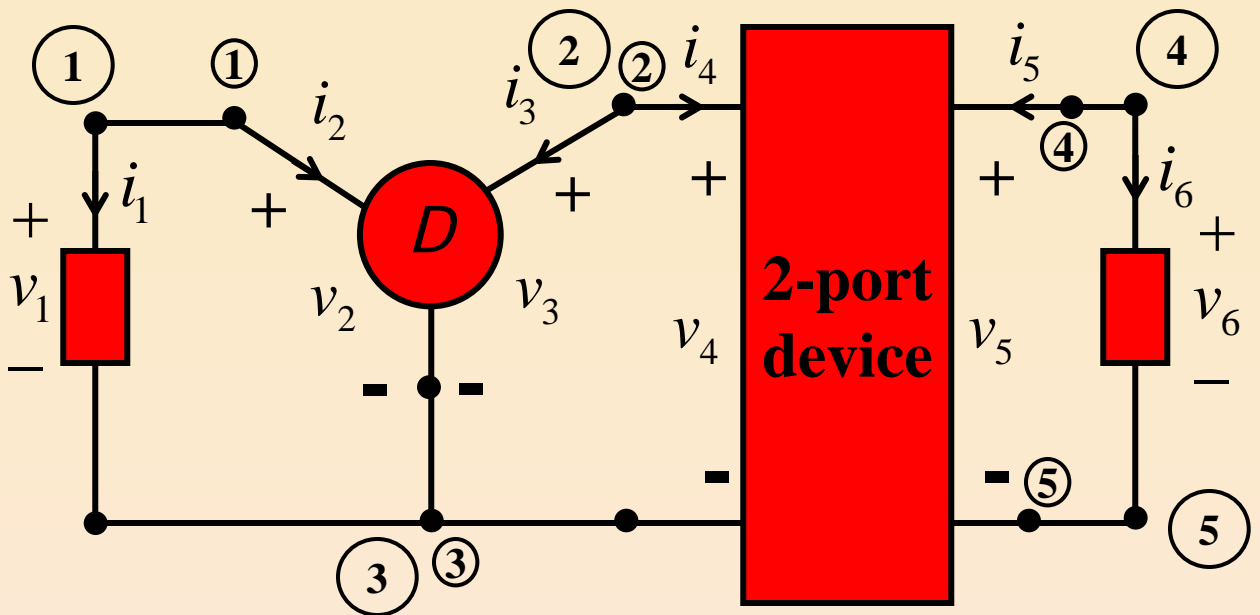
Adding a wire connecting one node from each separate component does **not** change KVL or KCL equations.




Adding a wire connecting one node from each separate component does **not** change KVL or KCL equations.

$$\{7\} \text{ is a cut set} \Rightarrow i_7 = 0$$

Associated Reference Convention :


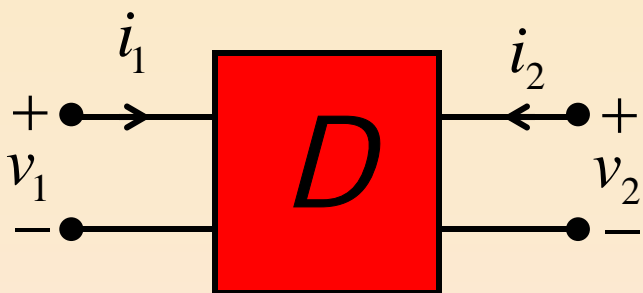



2-port Device

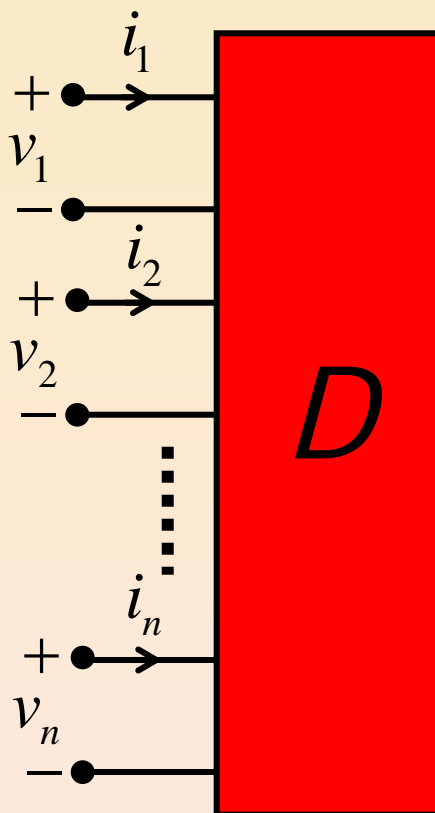

n -port Device


Device Graph

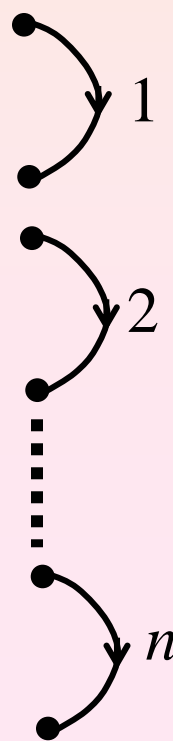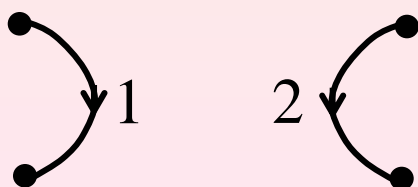

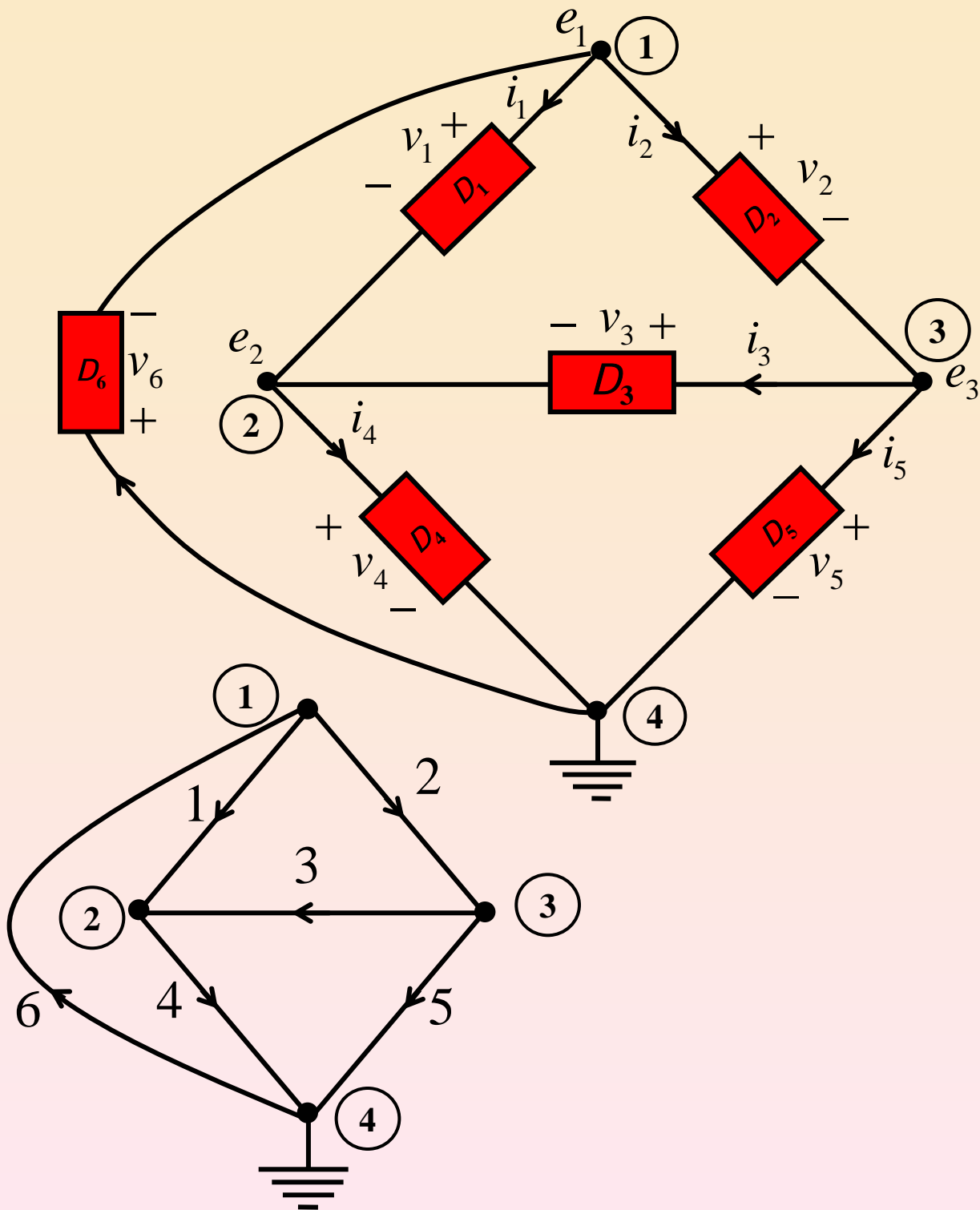

KCL at $\textcircled{1}$: $i_1 + i_2 - i_6 = 0$

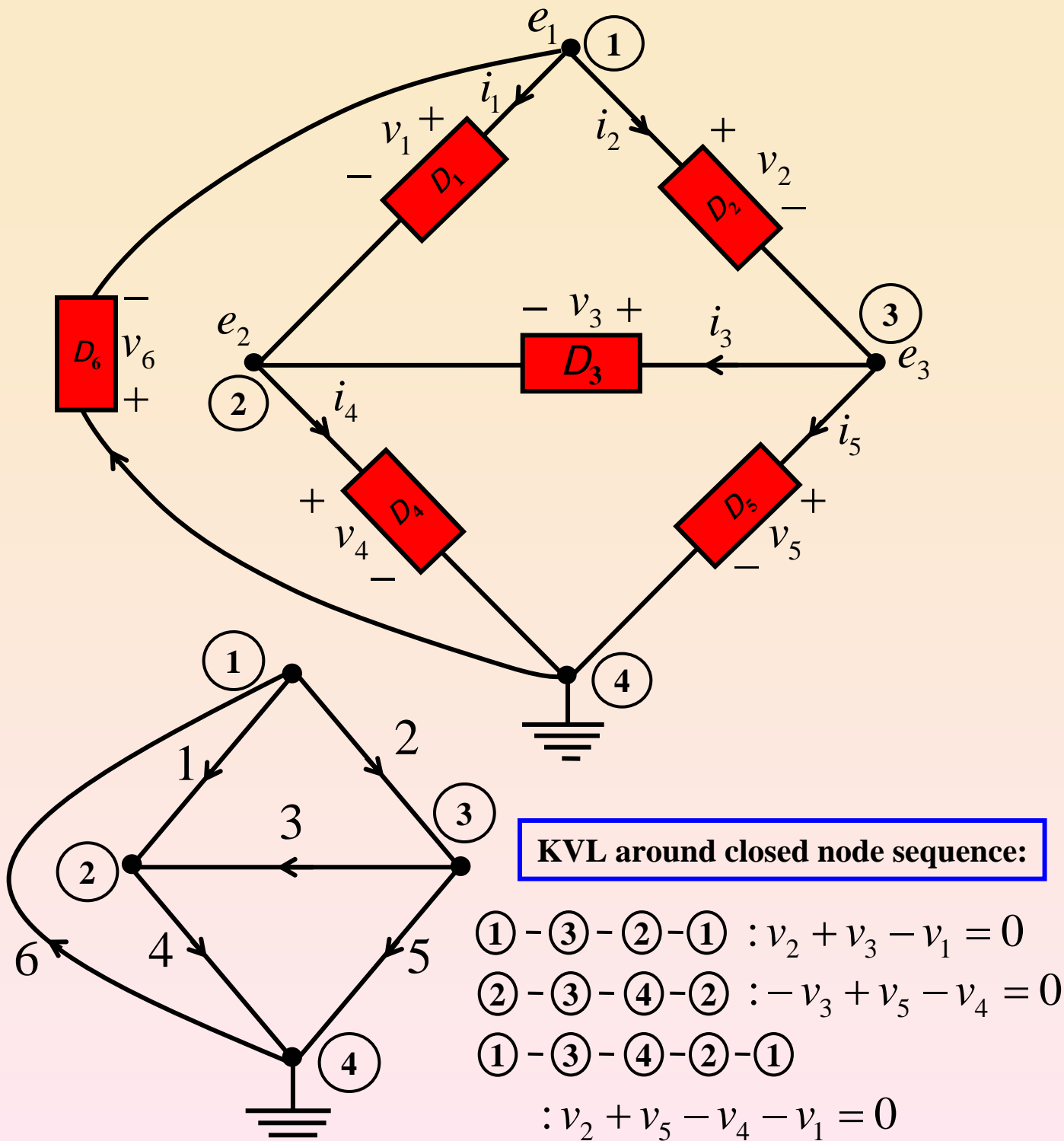KVL around $\textcircled{1}-\textcircled{3}-\textcircled{4}-\textcircled{2}-\textcircled{1}$:
 $v_2 + v_5 - v_4 - v_1 = 0$




These 3 KVL equations are **not** linearly-independent because the 3rd equation can be obtained by adding the first 2 equations:


$$\begin{aligned}
 & (v_2 + v_3 - v_1) + (-v_3 + v_5 - v_4) \\
 & = v_2 - v_1 + v_5 - v_4 = 0
 \end{aligned}$$

Associated Reference Convention :

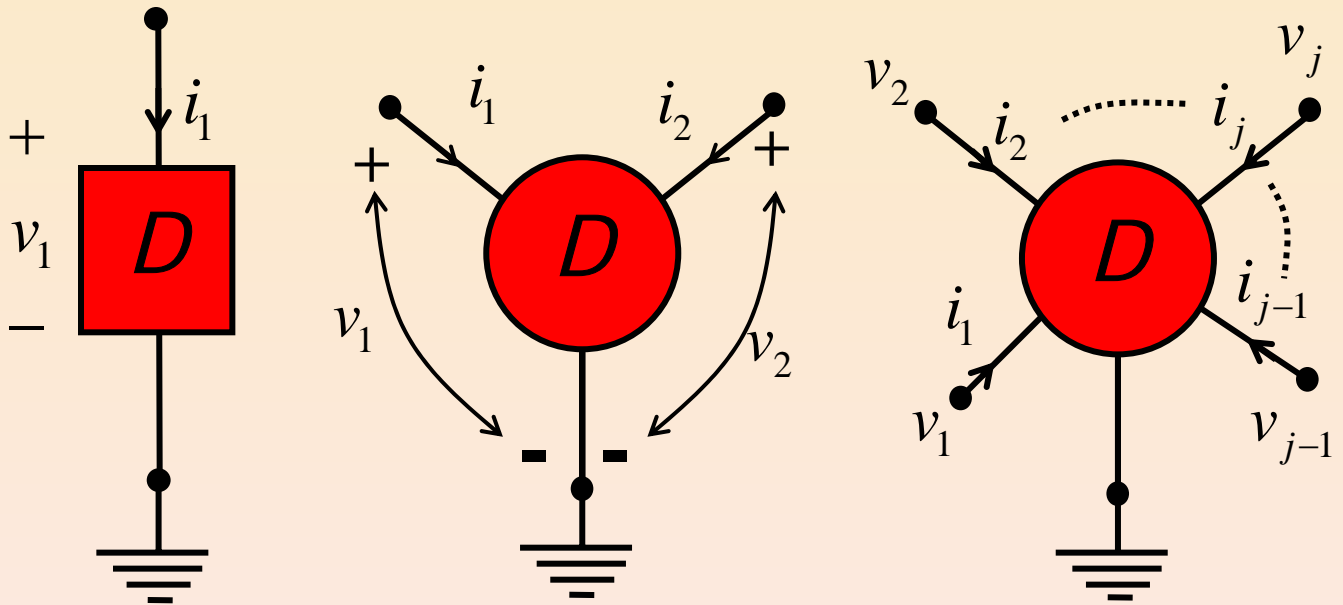
A current direction is chosen entering each positively-referenced terminal.




Device Graph : DIGRAPH (Directed Graph)

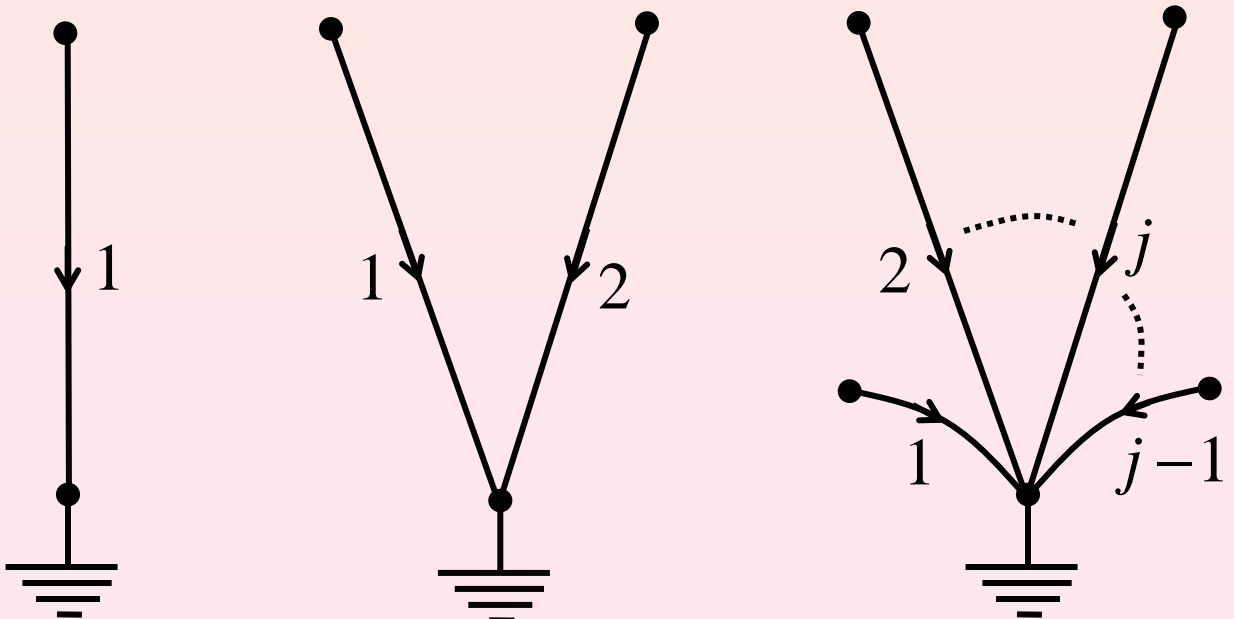

Circuit N

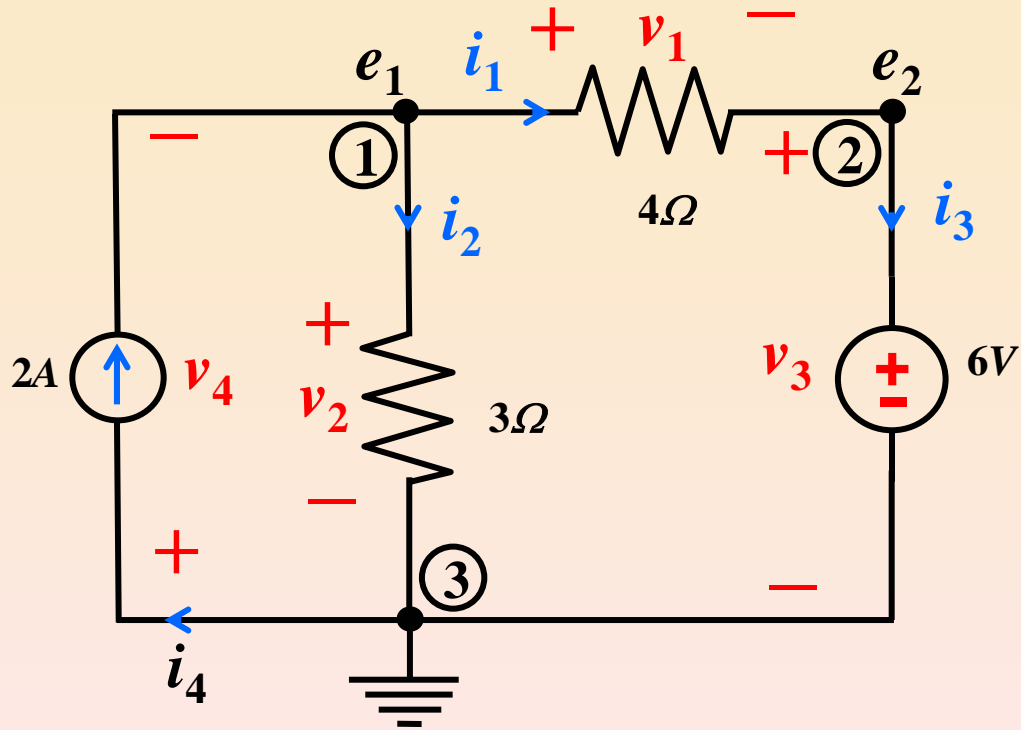

Digraph G

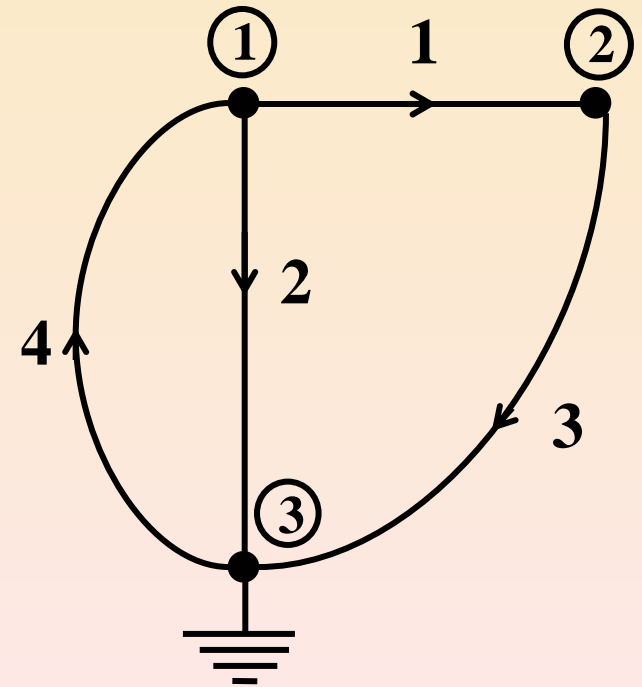

Reduced Incidence Matrix A

branch number

		1	2	3	4
node number	①	1	1	0	-1
	②	-1	0	1	0


KCL:

$$\underbrace{\begin{bmatrix} 1 & 1 & 0 & -1 \\ -1 & 0 & 1 & 0 \end{bmatrix}}_{\mathbf{A}} \underbrace{\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}}_{\mathbf{i}} = \underbrace{\begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}}_{\mathbf{0}} \Rightarrow \boxed{\begin{array}{l} i_1 + i_2 - i_4 = 0 \\ -i_1 + i_3 = 0 \end{array}}$$

KVL:

$$\underbrace{\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}}_{\mathbf{v}} = \underbrace{\begin{bmatrix} 1 & -1 \\ 1 & 0 \\ 0 & 1 \\ -1 & 0 \end{bmatrix}}_{\mathbf{A}^T} \underbrace{\begin{bmatrix} e_1 \\ e_2 \end{bmatrix}}_{\mathbf{e}} \Rightarrow \boxed{\begin{array}{l} v_1 = e_1 - e_2 \\ v_2 = e_1 \\ v_3 = e_2 \\ v_4 = -e_1 \end{array}}$$

Circuit N

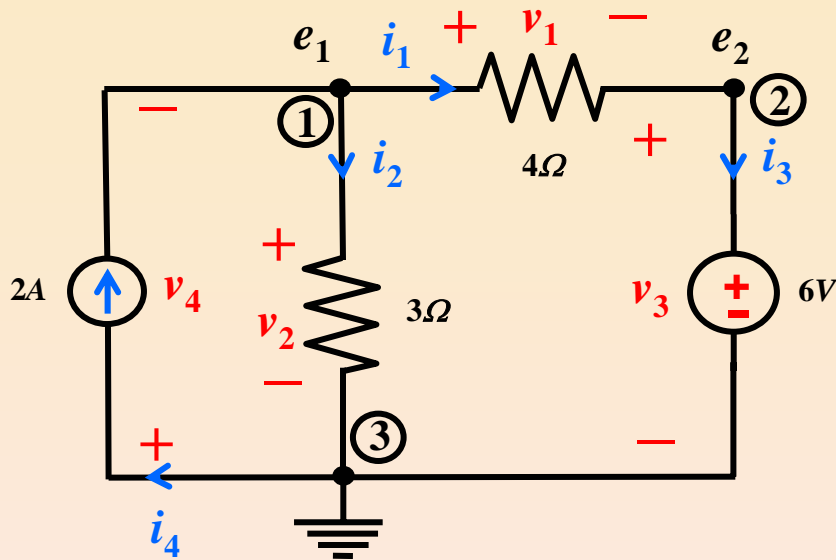

Circuit Variables

$$\mathbf{e} = \begin{bmatrix} e_1 \\ e_2 \end{bmatrix}, \quad \mathbf{v} = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}, \quad \mathbf{i} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}$$

Number of nodes: $n = 3$

Number of branches : $b = 4$

Number of circuit variables: $2b+(n-1) = (2 \times 4) + (3-1) = 10$

Number of Independent KCL Equations : $n-1 = 2$

Number of Independent KVL Equations: $b = 4$

Total number of independent KCL and KVL Equations : $b+(n-1) = 6$

We need “ b ” **additional** independent equations in order to obtain a system of $2b+(n-1)$ **independent equations** in $2b+(n-1)$ circuit variables.

The additional equations must come from the **constitutive relation** which relate the terminal voltages and currents of the circuit elements.

Let us rearrange all 10 independent equations as follow:


$$\begin{bmatrix}
 0 & 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 & -1 \\
 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 & 1 & 0 \\
 \hline
 -1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\
 -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\
 0 & -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\
 1 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\
 \hline
 0 & 0 & 1 & 0 & 0 & 0 & -4 & 0 & 0 & 0 \\
 0 & 0 & 0 & 1 & 0 & 0 & 0 & -3 & 0 & 0 \\
 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\
 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1
 \end{bmatrix}
 \begin{bmatrix}
 e_1 \\
 e_2 \\
 \hline
 v_1 \\
 v_2 \\
 v_3 \\
 v_4 \\
 \hline
 i_1 \\
 i_2 \\
 i_3 \\
 i_4
 \end{bmatrix}
 =
 \begin{bmatrix}
 0 \\
 0 \\
 \hline
 0 \\
 0 \\
 0 \\
 0 \\
 \hline
 0 \\
 0 \\
 6 \\
 2
 \end{bmatrix}$$

How Many Circuit Variables?


Answer:

$$\text{Total Number of Circuit Variables} = 2b + n - 1$$

Circuit N

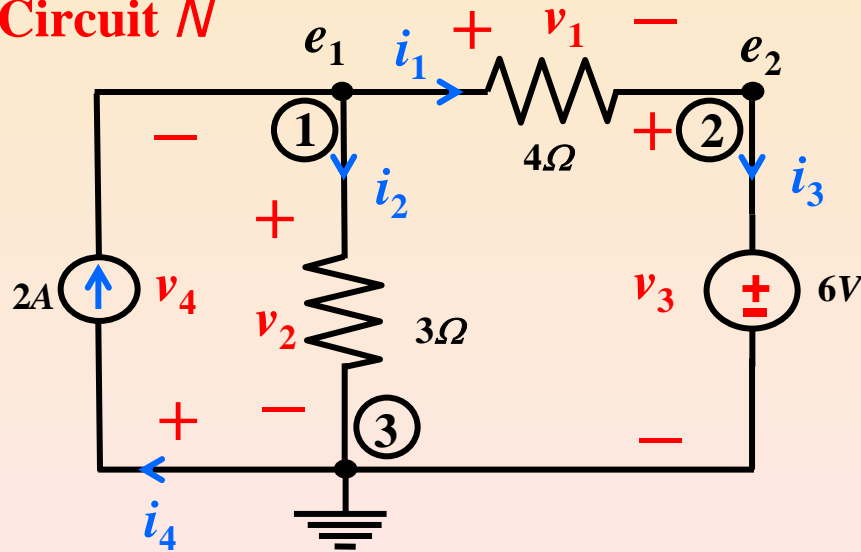

Digraph G

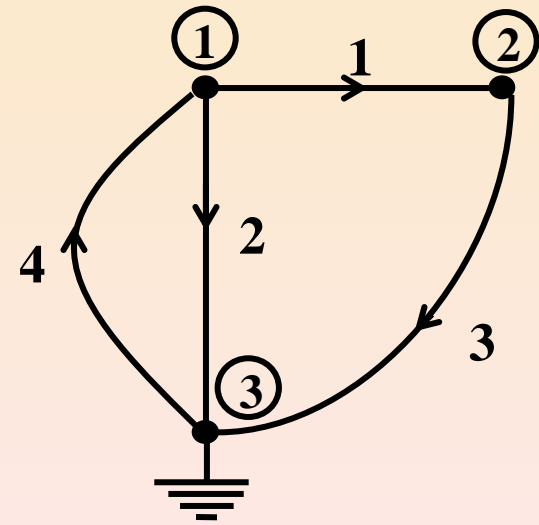

Number of Nodes: $n = 3$

$$\mathbf{e} = \begin{bmatrix} e_1 \\ e_2 \end{bmatrix}$$

node-to-datum voltages: $n-1 = 2$

Number of branches: $b = 4$

$$\mathbf{v} = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}$$


$$\mathbf{i} = \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}$$

branch voltages: $b = 4$


branch currents: $b = 4$

\therefore There are $\underbrace{(n-1) + b + b}_{2b + n - 1} = 10$ circuit variables; namely, $\{e_1, e_2, v_1, v_2, v_3, v_4, i_1, i_2, i_3, i_4\}$.

Circuit N

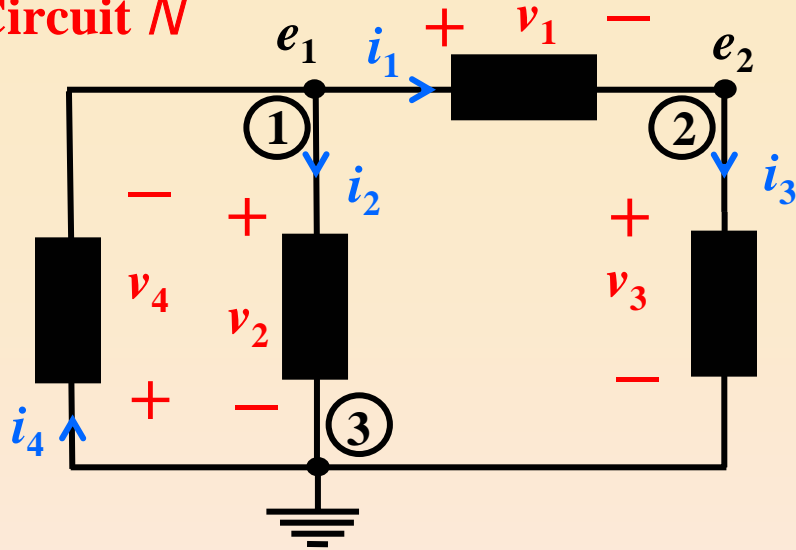

Digraph G

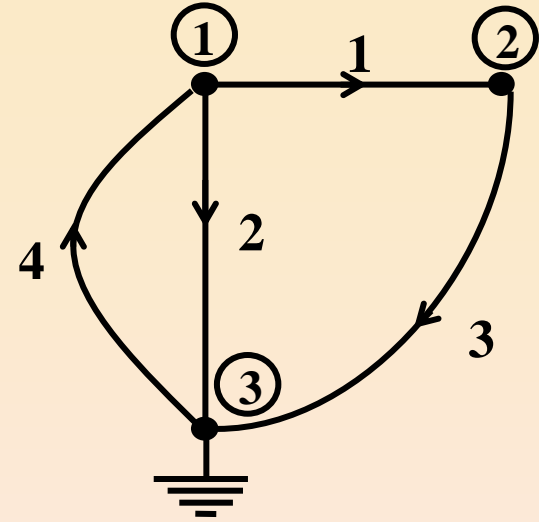

There are infinitely many sets of branch voltages (v_1, v_2, v_3, v_4) which satisfy KVL for G .
 2 Examples satisfying KVL:

KVL solution 1: $v_1 = -3V, v_2 = 2V, v_3 = 5V, v_4 = -2V$



KVL solution 2: $\hat{v}_1 = 2V, \hat{v}_2 = 4V, \hat{v}_3 = 2V, \hat{v}_4 = -4V$

There are infinitely many sets of branch currents (i_1, i_2, i_3, i_4) which satisfy KCL for G .
 2 Examples satisfying KCL:

KCL solution 1: $i_1 = 3A, i_2 = 2A, i_3 = 3A, i_4 = 5A$

KCL solution 2: $\hat{i}_1 = 6A, \hat{i}_2 = -4A, \hat{i}_3 = 6A, \hat{i}_4 = 2A$

NOTE: So far we have not specified what circuit elements are used in this circuit. This explains why the voltage and current solutions are **not** unique.

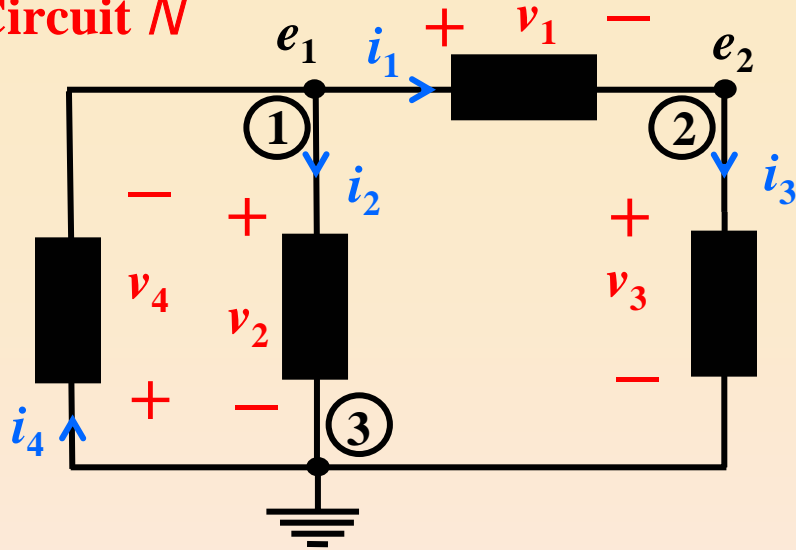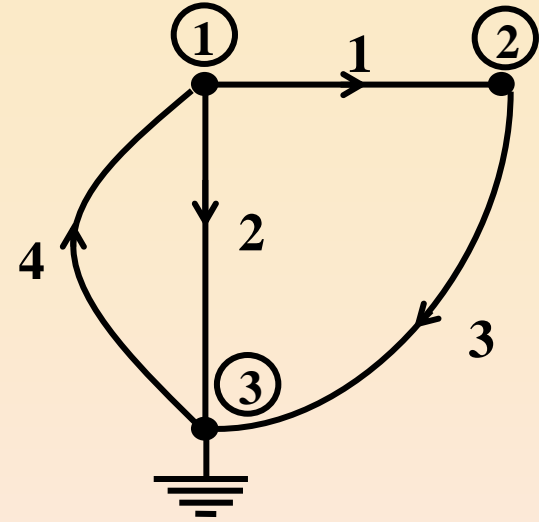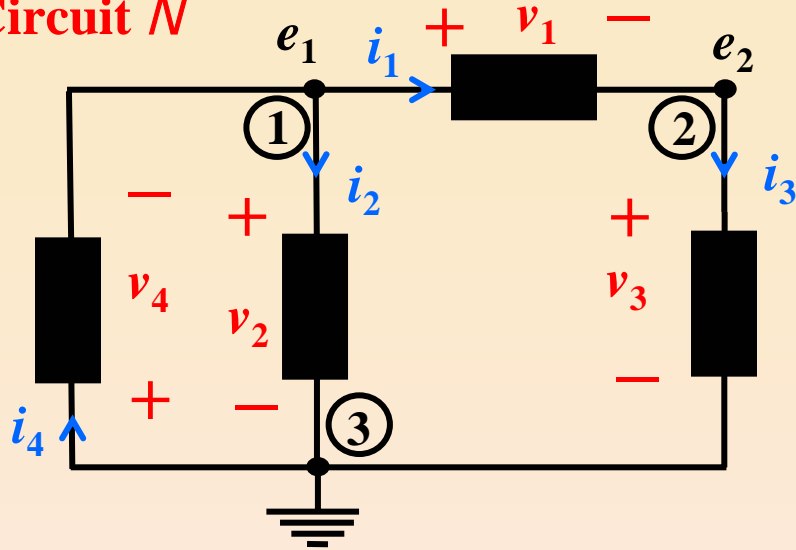
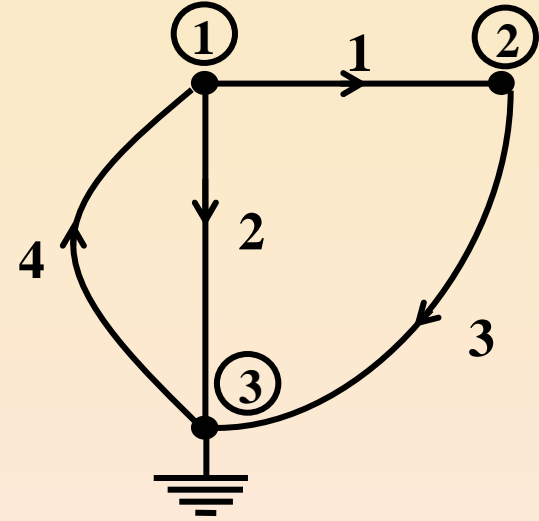
Circuit N **Digraph G** 

Example 1

KVL solution: Choose $v_1 = -3V, v_2 = 2V, v_3 = 5V, v_4 = -2V$

KCL solution: Choose $i_1 = 3A, i_2 = 2A, i_3 = 3A, i_4 = 5A$

$$\begin{aligned}
 \sum_{j=1}^4 v_j i_j &= (-3)(3) + (2)(2) + (5)(3) + (-2)(5) \\
 &= -9 + 4 + 15 - 10 \\
 &= 0
 \end{aligned}$$

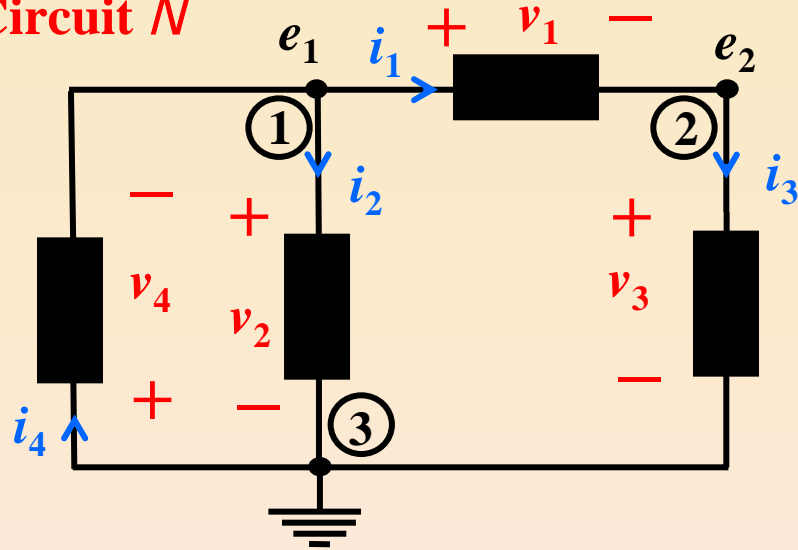
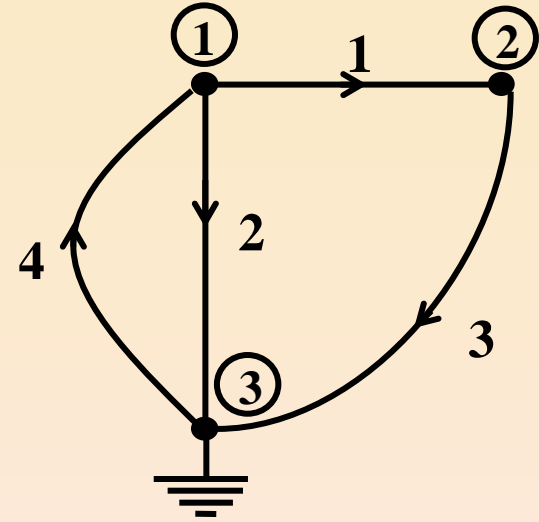
Circuit N **Digraph G** 

Example 2

KVL solution: Choose $\hat{v}_1 = 2V, \hat{v}_2 = 4V, \hat{v}_3 = 2V, \hat{v}_4 = -4V$

KCL solution: Choose $i_1 = 3A, i_2 = 2A, i_3 = 3A, i_4 = 5A$

$$\begin{aligned} \sum_{j=1}^4 \hat{v}_j i_j &= (2)(3) + (4)(2) + (2)(3) + (-4)(5) \\ &= 6 + 8 + 6 - 20 \\ &= 0 \end{aligned}$$

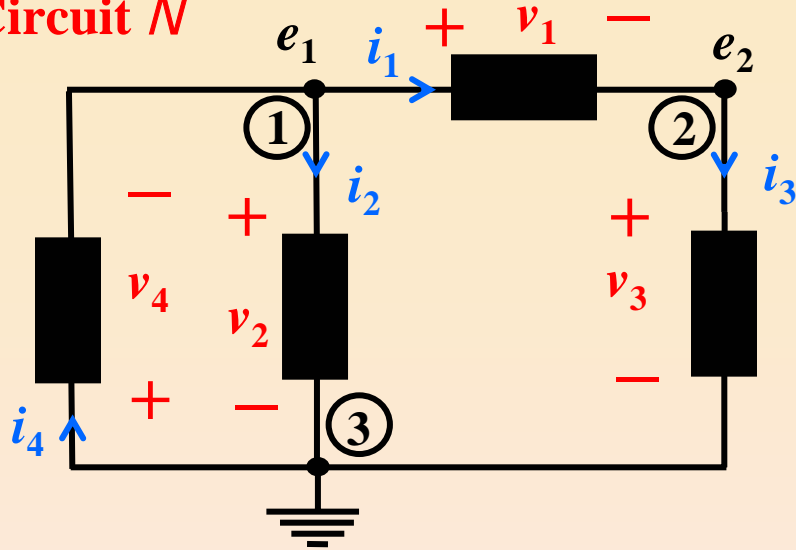
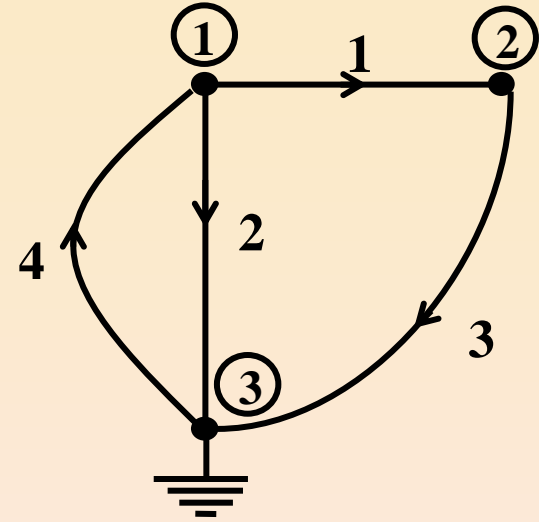
Circuit N **Digraph G** 

Example 3

KVL solution: Choose $v_1 = -3V, v_2 = 2V, v_3 = 5V, v_4 = -2V$

KCL solution: Choose $\hat{i}_1 = 6A, \hat{i}_2 = -4A, \hat{i}_3 = 6A, \hat{i}_4 = 2A$

$$\begin{aligned} \sum_{j=1}^4 v_j \hat{i}_j &= (-3)(6) + (2)(-4) + (5)(6) + (-2)(2) \\ &= -18 - 8 + 30 - 4 \\ &= 0 \end{aligned}$$



Circuit N **Digraph G** 

Example 4

KVL solution: Choose $\hat{v}_1 = 2V, \hat{v}_2 = 4V, \hat{v}_3 = 2V, \hat{v}_4 = -4V$

KCL solution: Choose $\hat{i}_1 = 6A, \hat{i}_2 = -4A, \hat{i}_3 = 6A, \hat{i}_4 = 2A$
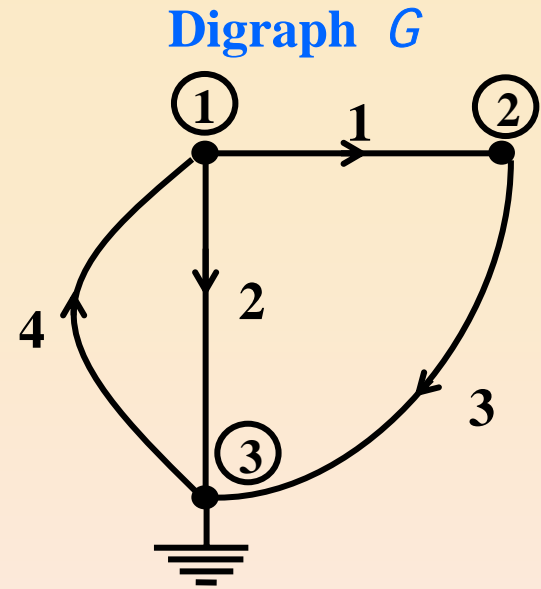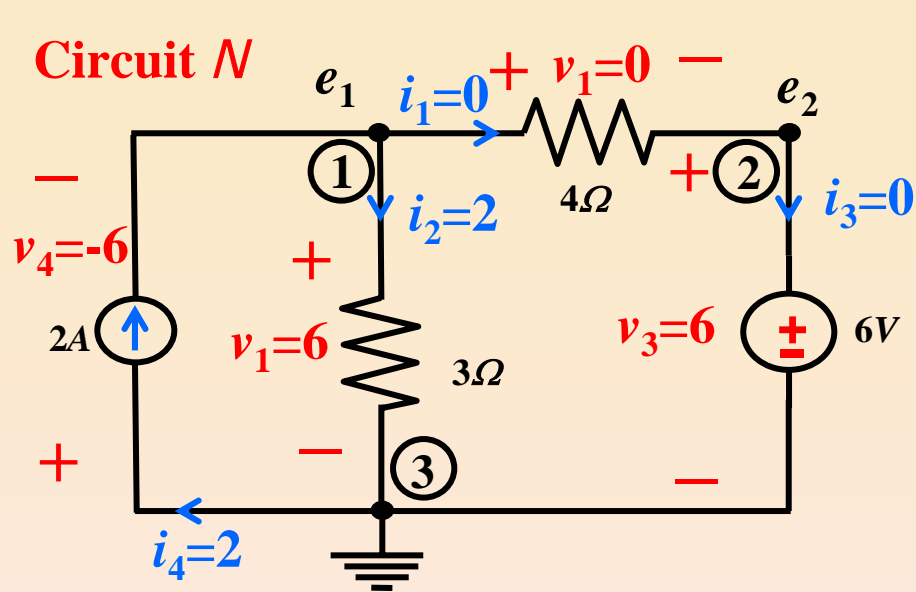
$$\begin{aligned} \sum_{j=1}^4 \hat{v}_j \hat{i}_j &= (2)(6) + (4)(-4) + (2)(6) + (-4)(2) \\ &= 12 - 16 + 12 - 8 \\ &= 0 \end{aligned}$$



Solution :

$$e_1 = 6V, e_2 = 6V$$

$$v_1 = 0V, v_2 = 6V, v_3 = 6V, v_4 = -6V$$

$$i_1 = 0A, i_2 = 2A, i_3 = 0A, i_4 = 2A$$

Verifying the solution satisfying Tellegen's Theorem:

$$\sum_{j=1}^4 v_j i_j = (v_1 i_1) + (v_2 i_2) + (v_3 i_3) + (v_4 i_4)$$

$$= (0)(0) + (6)(2) + (6)(0) + (-6)(2)$$

$$= 0 + 12 + 0 - 12$$

$$= 0$$

How to write An Independent System of KCL and KVL Equations

Let N be any connected circuit and let the **digraph** G associated with N contain “ n ” nodes and “ b ” branches. Choose an arbitrary datum node and define the associated **node-to-datum voltage** vector \mathbf{e} , the **branch voltage vector** \mathbf{v} , and the **branch current vector** \mathbf{i} . Then we have the following system of **independent** KCL and KVL equations.

($n-1$) Independent KCL Equations :

$$\mathbf{A} \mathbf{i} = \mathbf{0}$$

b Independent KVL Equations :

$$\mathbf{v} = \mathbf{A}^T \mathbf{e}$$

Element Constitutive Relations

Element 1: Resistor

Described by Ohm's Law : $v_1 = 4 i_1$

Element 2: Resistor

Described by Ohm's Law : $v_2 = 3 i_2$

Element 3: Voltage source

Described by : $v_3 = 6$

Element 4: Current source

Described by : $i_4 = 2$

Rearranging these equations so that circuit variables appear on the left-hand side, we obtain

Observe we

have obtained

4 additional

independent

equations.

Element
Equations

$$v_1 - 4 i_1 = 0$$

$$v_2 - 3 i_2 = 0$$

$$v_3 = 6$$

$$i_4 = 2$$


Equations obtained from the element constitutive relations are guaranteed to be **independent** because different elements involved different circuit variables.

We can always recast **any** system of **linear** constitutive equations into the following standard matrix form

$$\underbrace{\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}}_{\mathbf{H}_v} \underbrace{\begin{bmatrix} -4 & 0 & 0 & 0 \\ 0 & -3 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}}_{\mathbf{H}_i} \underbrace{\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ \hline i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}}_{\begin{bmatrix} \mathbf{v} \\ \mathbf{i} \end{bmatrix} \text{ independent source vector}} = \underbrace{\begin{bmatrix} 0 \\ 0 \\ 6 \\ 2 \end{bmatrix}}_{\mathbf{u}}$$


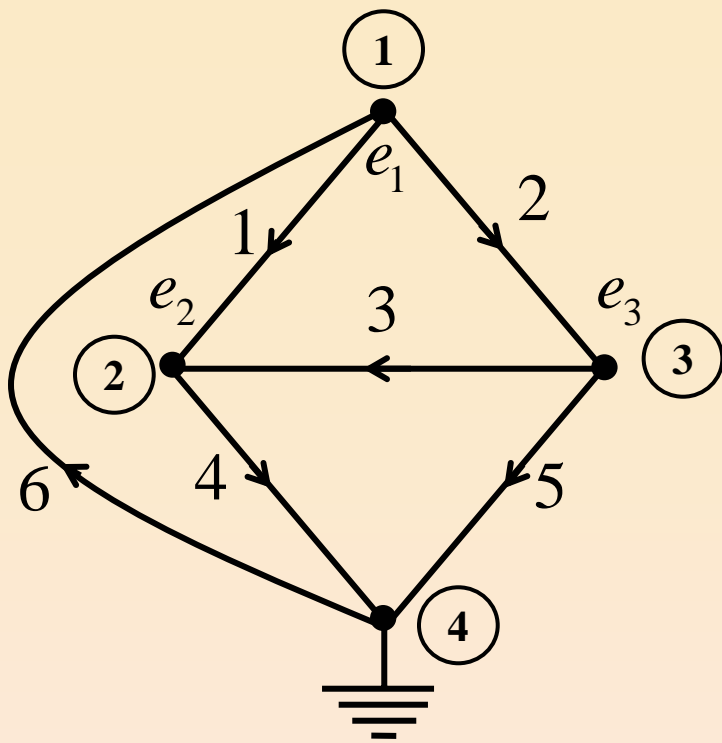
$$\boxed{\mathbf{H}_v \mathbf{v} + \mathbf{H}_i \mathbf{i} = \mathbf{u}}$$




KCL Equations:

$$\textcircled{1} \quad i_1 + i_2 - i_6 = 0$$

$$\textcircled{2} \quad -i_1 - i_3 + i_4 = 0$$

$$\textcircled{3} \quad -i_2 + i_3 + i_5 = 0$$

$$\mathbf{A} \mathbf{i} = \mathbf{0} \quad \Rightarrow \quad \begin{array}{c} \text{node} \\ \text{no.} \end{array} \begin{array}{c} \text{Branch no.} \\ 1 \quad 2 \quad 3 \quad 4 \quad 5 \quad 6 \end{array} \begin{array}{c} \textcircled{1} \\ \textcircled{2} \\ \textcircled{3} \end{array} \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

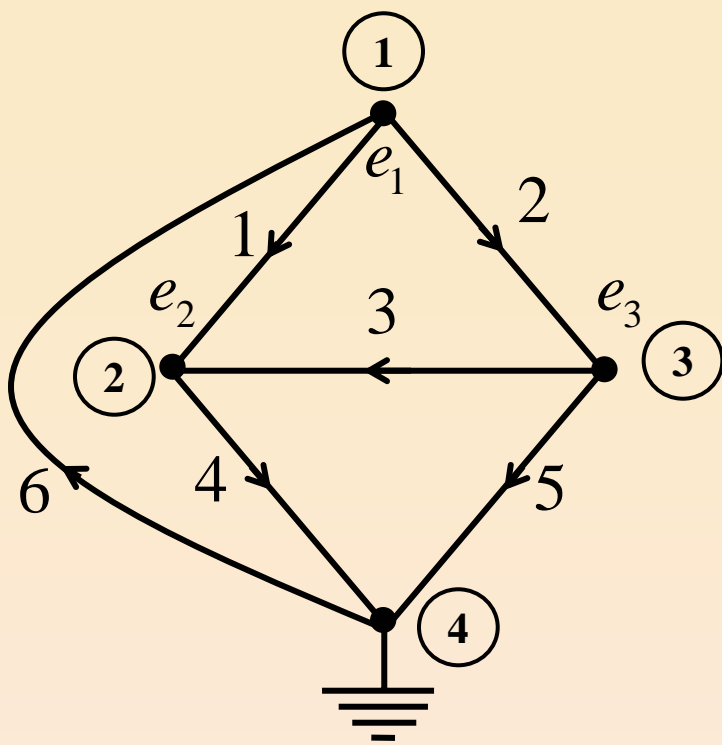

KCL Equations:

$$\textcircled{1} \quad i_1 + i_2 - i_6 = 0$$

$$\textcircled{2} \quad -i_1 - i_3 + i_4 = 0$$

$$\textcircled{3} \quad -i_2 + i_3 + i_5 = 0$$


$$\mathbf{A} \mathbf{i} = \mathbf{0} \quad \Rightarrow$$

node no.	1	2	3	4	5	6
$\textcircled{1}$	1	1	0	0	0	-1
$\textcircled{2}$	-1	0	-1	1	0	0
$\textcircled{3}$	0	-1	1	0	1	0

$$\underbrace{\hspace{15em}}_{\mathbf{A}} \underbrace{\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}}_{\mathbf{i}} = \underbrace{\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}}_{\mathbf{0}}$$

\mathbf{A} is called the **reduced Incidence Matrix** of the digraph G relative to datum node $\textcircled{4}$.

KCL Node Equations:

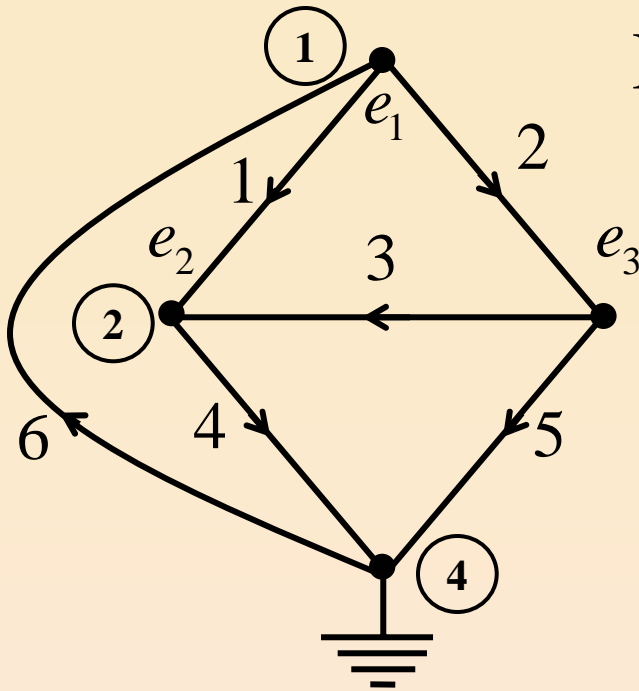

node No.

$$\textcircled{1} \quad i_1 + i_2 - i_6 = 0$$

$$\textcircled{2} \quad -i_1 - i_3 + i_4 = 0$$

$$\textcircled{3} \quad -i_2 + i_3 + i_5 = 0$$

$$\textcircled{4} \quad -i_4 - i_5 + i_6 = 0$$

These 4 equations are linearly-dependent.

Matrix Formulation:

node no.	Branch no.					
	1	2	3	4	5	6
$\textcircled{1}$	1	1	0	0	0	-1
$\textcircled{2}$	-1	0	-1	1	0	0
$\textcircled{3}$	0	-1	1	0	1	0
$\textcircled{4}$	0	0	0	-1	-1	1


$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

INCIDENCE MATRIX

$\longrightarrow \mathbf{A}_a$

$\mathbf{i} = \mathbf{0}$
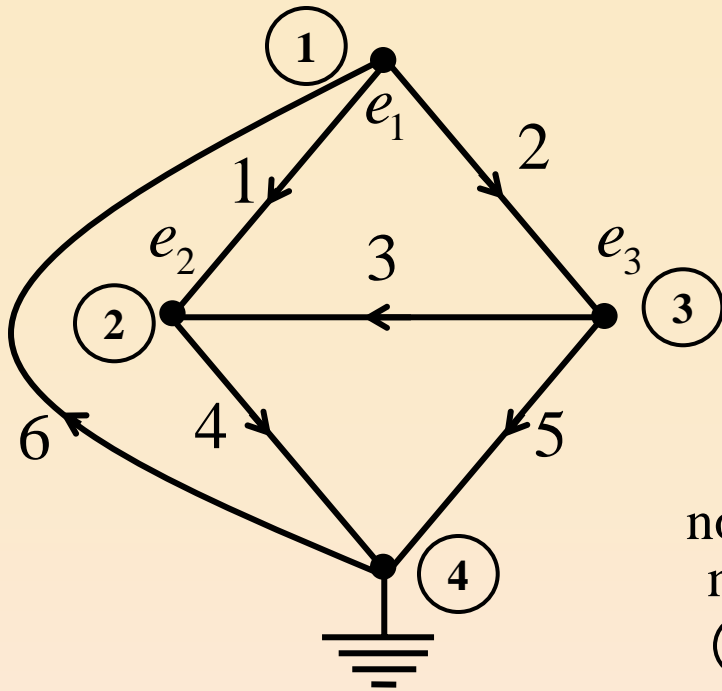
$$a_{jk} = \begin{cases} 1 & \text{if branch } k \text{ leaves node } \textcircled{j} \\ -1 & \text{if branch } k \text{ enters node } \textcircled{j} \\ 0 & \text{if branch } k \text{ is not connected to node } \textcircled{j} \end{cases}$$



KCL Equations:

$$\textcircled{1} \quad i_1 + i_2 - i_6 = 0$$

$$\textcircled{2} \quad -i_1 - i_3 + i_4 = 0$$

$$\textcircled{3} \quad -i_2 + i_3 + i_5 = 0$$

node Branch no.

no. 1 2 3 4 5 6

$$\begin{matrix} \textcircled{1} \\ \textcircled{2} \\ \textcircled{3} \end{matrix} \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\mathbf{A} \mathbf{i} = \mathbf{0} \Rightarrow$$

$$\underbrace{\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix}}_{\mathbf{v}} = \underbrace{\begin{bmatrix} 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & -1 & 1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & 0 & 0 \end{bmatrix}}_{\mathbf{A}^T} \underbrace{\begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix}}_{\mathbf{e}}$$

KVL Equations:

$$\Leftrightarrow \begin{cases} v_1 = e_1 - e_2 \\ v_2 = e_1 - e_3 \\ v_3 = e_3 - e_2 \\ v_4 = e_2 \\ v_5 = e_3 \\ v_6 = -e_1 \end{cases}$$

↓

$$\text{KVL: } \boxed{\mathbf{v} = \mathbf{A}^T \mathbf{e}}$$

Since v_j is present only in the j th equation, these k equations are **linearly - independent**.

Theorem

$$\mathbf{A} \mathbf{i} = \mathbf{0}$$

gives the **maximum possible** number of **linearly-independent KCL equations** for a connected circuit.

Reduced Incidence Matrix

Let G be a connected **digraph** with “ n ” nodes and “ b ” branches. Let \mathbf{A}_a be the **Incidence Matrix** of G . The $(n-1) \times b$ matrix \mathbf{A} obtained by deleting any one row of \mathbf{A}_a is called a **Reduced-Incidence Matrix** of G .

Observation : The 4 KCL node equations are *not* linearly independent.

Adding the left side of the 4 KCL node equations, we obtain:

$$\underbrace{(i_1 + i_2 - i_6)}_{\textcircled{1}} + \underbrace{(-i_1 - i_3 + i_4)}_{\textcircled{2}} + \underbrace{(-i_2 + i_3 + i_5)}_{\textcircled{3}} + \underbrace{(-i_4 - i_5 + i_6)}_{\textcircled{4}} \equiv 0$$

This means we can derive any one of these 4 equations from the other 3.

Example: Derive KCL equations at node $\textcircled{4}$:

Adding the first 3 node equations gives:

$$\underbrace{(i_1 + i_2 - i_6)}_{\textcircled{1}} + \underbrace{(-i_1 - i_3 + i_4)}_{\textcircled{2}} + \underbrace{(-i_2 + i_3 + i_5)}_{\textcircled{3}} = \underbrace{i_4 + i_5 - i_6}_{\textcircled{4}}$$

Reduced Incidence Matrix

A

Let G be a connected **digraph** with “ n ” nodes and “ b ” branches, the **reduced incidence matrix** \mathbf{A} relative to **datum node** \textcircled{n} is an $(n-1) \times b$ matrix whose coefficients a_{jk} are obtained from the $(n-1)$ KCL equations written at the $n-1$ non-datum nodes:

$$a_{jk} = \begin{cases} 1 & \text{if branch } k \text{ leaves node } \textcircled{j} \\ -1 & \text{if branch } k \text{ enters node } \textcircled{j} \\ 0 & \text{if branch } k \text{ is not connected to node } \textcircled{j} \end{cases}$$

By applying the various versions of KCL, we can write many different KCL equations for each circuit. However, these equations are usually **not** linearly independent in the sense that each equation can be derived by a linear combination of the others.

How can we write a maximum set of **linearly-independent** KCL equations?

Simplest Method to write linearly-Independent KCL Equations.


Given a connected circuit with “ n ” nodes, choose an arbitrary node as **datum**. Write a KCL equation at each of the remaining $(n-1)$ nodes.

Relationship between \mathbf{A} and \mathbf{A}_a

Let \mathbf{A}_a be the $n \times b$ **Incidence matrix** of a connected digraph G with “ n ” nodes and “ b ” branches.

By deleting any row corresponding to node \textcircled{m} from \mathbf{A}_a , we obtain the **reduced incidence matrix** \mathbf{A} of G relative to the datum node \textcircled{m} .

Choose ④ as datum node for digraph G

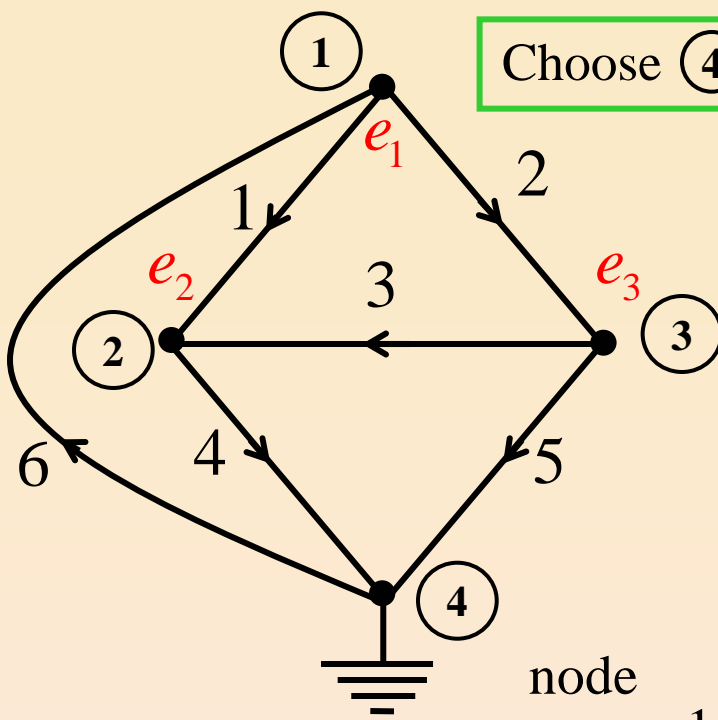

KCL Equations:

- ① $i_1 + i_2 - i_6 = 0$
- ② $-i_1 - i_3 + i_4 = 0$
- ③ $-i_2 + i_3 + i_5 = 0$

Independent KCL Equations

$$\mathbf{A} \mathbf{i} = \mathbf{0}$$

node no.	1	2	3	4	5	6		
①	1	1	0	0	0	-1	$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = \underbrace{\begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}}_{\mathbf{0}}$	
②	-1	0	-1	1	0	0		
③	0	-1	1	0	1	0		

$\underbrace{\hspace{10em}}_{\mathbf{A}}$


$\underbrace{\hspace{10em}}_{\mathbf{i}}$

Independent KVL Equations

$$\underbrace{\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix}}_{\mathbf{v}} = \underbrace{\begin{bmatrix} 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & -1 & 1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & 0 & 0 \end{bmatrix}}_{\mathbf{A}^T} \underbrace{\begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix}}_{\mathbf{e}}$$

$$\Rightarrow \begin{cases} v_1 = e_1 - e_2 \\ v_2 = e_1 - e_3 \\ v_3 = -e_2 + e_3 \\ v_4 = e_2 \\ v_5 = e_3 \\ v_6 = -e_1 \end{cases}$$

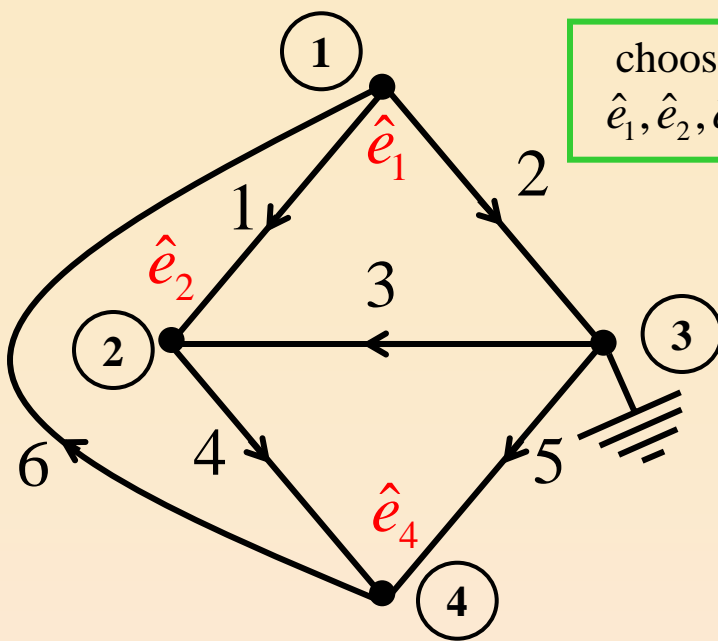choose ③ as datum and let $\hat{e}_1, \hat{e}_2, \hat{e}_4$ be new **node-to-datum** voltages.



KCL Equations:

$$\begin{aligned} \textcircled{1} \quad & i_1 + i_2 - i_6 = 0 \\ \textcircled{2} \quad & -i_1 - i_3 + i_4 = 0 \\ \textcircled{4} \quad & -i_4 - i_5 + i_6 = 0 \end{aligned}$$

Independent KCL Equations

$$\hat{\mathbf{A}} \mathbf{i} = \mathbf{0}$$

$$\begin{array}{c} \text{node} \\ \text{no.} \end{array} \begin{array}{c} \text{Branch no.} \\ 1 \quad 2 \quad 3 \quad 4 \quad 5 \quad 6 \end{array} \underbrace{\begin{bmatrix} \textcircled{1} & 1 & 1 & 0 & 0 & 0 & -1 \\ \textcircled{2} & -1 & 0 & -1 & 1 & 0 & 0 \\ \textcircled{4} & 0 & 0 & 0 & -1 & -1 & 1 \end{bmatrix}}_{\hat{\mathbf{A}}} \underbrace{\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}}_{\mathbf{i}} = \underbrace{\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}}_{\mathbf{0}}$$

Independent KVL Equations

$$\underbrace{\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix}}_{\mathbf{v}} = \underbrace{\begin{bmatrix} 1 & -1 & 0 \\ 1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 1 & -1 \\ 0 & 0 & -1 \\ -1 & 0 & 1 \end{bmatrix}}_{\hat{\mathbf{A}}^T} \underbrace{\begin{bmatrix} \hat{e}_1 \\ \hat{e}_2 \\ \hat{e}_4 \end{bmatrix}}_{\hat{\mathbf{e}}}$$

$$\begin{aligned} v_1 &= \hat{e}_1 - \hat{e}_2 \\ v_2 &= \hat{e}_1 \\ v_3 &= -\hat{e}_2 \\ v_4 &= \hat{e}_2 - \hat{e}_4 \\ v_5 &= -\hat{e}_4 \\ v_6 &= -\hat{e}_1 + \hat{e}_4 \end{aligned}$$

We can always recast **any** system of **linear** constitutive equations into the following standard matrix form

$$\underbrace{\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}}_{\mathbf{H}_v} \underbrace{\begin{bmatrix} -4 & 0 & 0 & 0 \\ 0 & -3 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}}_{\mathbf{H}_i} \underbrace{\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ \hline i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix}}_{\begin{bmatrix} \mathbf{v} \\ \mathbf{i} \end{bmatrix} \text{ independent source vector}} = \underbrace{\begin{bmatrix} 0 \\ 0 \\ 6 \\ 2 \end{bmatrix}}_{\mathbf{u}}$$



$$\boxed{\mathbf{H}_v \mathbf{v} + \mathbf{H}_i \mathbf{i} = \mathbf{u}}$$

$$\begin{array}{l}
 \text{KCL} \\
 \text{KVL} \\
 \text{Element} \\
 \text{Constitutive} \\
 \text{Relation}
 \end{array}
 \left\{
 \begin{array}{l}
 i_1 + i_2 - i_4 = 0 \\
 -i_1 + i_3 = 0 \\
 v_1 = e_1 - e_2 \\
 v_2 = e_1 \\
 v_3 = e_2 \\
 v_4 = -e_1 \\
 v_1 = 4i_1 \\
 v_2 = 3i_2 \\
 v_3 = 6 \\
 i_4 = 2
 \end{array}
 \right.
 \begin{array}{l}
 (1) \\
 (2) \\
 (3) \\
 (4) \\
 (5) \\
 (6) \\
 (7) \\
 (8) \\
 (9) \\
 (10)
 \end{array}
 \left.
 \vphantom{\begin{array}{l}
 \text{KCL} \\
 \text{KVL} \\
 \text{Element} \\
 \text{Constitutive} \\
 \text{Relation}
 \end{array}}
 \right\}
 \begin{array}{l}
 \mathbf{10} \\
 \mathbf{independent} \\
 \mathbf{linear} \\
 \mathbf{equations} \\
 \mathbf{involving} \\
 \mathbf{10} \\
 \mathbf{variables}
 \end{array}$$

We can always find the solution using **Cramer's rule**.

For simple circuits, we can often find the solution by *as hoc* elimination and substitution of variables:

$$\text{EXAMPLE : (5) and (9)} \quad \Rightarrow \quad e_2 = 6 \quad (11)$$

$$(1) \text{ and (10)} \quad \Rightarrow \quad i_1 + i_2 = 2 \quad (12)$$

$$(3), (7) \text{ and (11)} \quad \Rightarrow \quad i_1 = \frac{1}{4}(e_1 - 6) \quad (13)$$

$$(4) \text{ and (8)} \quad \Rightarrow \quad i_2 = \frac{1}{3}e_1 \quad (14)$$

Substituting (10), (11), (12), and (13) into (1), we obtain

$$\begin{aligned} \frac{1}{4}(e_1 - 6) + \frac{1}{3}e_1 - 2 &= 0 \\ \Rightarrow e_1 &= 6 \end{aligned} \quad (15)$$

Complete Solution:

$$e_1 = 6V, e_2 = 6V$$

$$v_1 = 0V, v_2 = 6V, v_3 = 6V, v_4 = -6V$$

$$i_1 = 0A, i_2 = 2A, i_3 = 0A, i_4 = 2A$$

Verification of solution via Tellegen's Theorem

$$\begin{aligned} \sum_{j=1}^4 v_j i_j &= (v_1 i_1) + (v_2 i_2) + (v_3 i_3) + (v_4 i_4) \\ &= (0)(0) + (6)(2) + (6)(0) + (-6)(2) \stackrel{?}{=} 0 \end{aligned}$$

Tellegen's Theorem

Let G be a diagraph with " b " branches.

Let (v_1, v_2, \dots, v_b) be **any** set of b **voltages** of G which satisfy KVL.

Let (i_1, i_2, \dots, i_b) be **any** set of b **currents** of G which satisfy KCL.

Then

$$\sum_{j=1}^b v_j i_j = 0$$

Proof: suppose


$$\mathbf{v} = \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_b \end{bmatrix} \text{ satisfies KVL for } G, \quad \mathbf{i} = \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_b \end{bmatrix} \text{ satisfies KCL for } G$$


$$\text{Then } \sum_{j=1}^b v_j i_j = \mathbf{v}^T \mathbf{i} = \underbrace{(\mathbf{A}^T \mathbf{e})^T}_{\text{KVL}} \mathbf{i} = \mathbf{e}^T \underbrace{(\mathbf{A} \mathbf{i})}_{\text{KCL}} = 0$$

where $\mathbf{e} = [e_1, e_2, \dots, e_{n-1}]^T$ is **any** node-to-datum voltage. ■

Warning: By definition of a diagraph, each branch voltage v_j

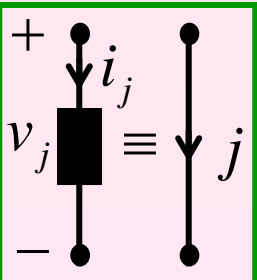and branch current i_j associated with branch j must follow the **Associated reference convention**: i_j flows from the positive terminal to the negative terminal.



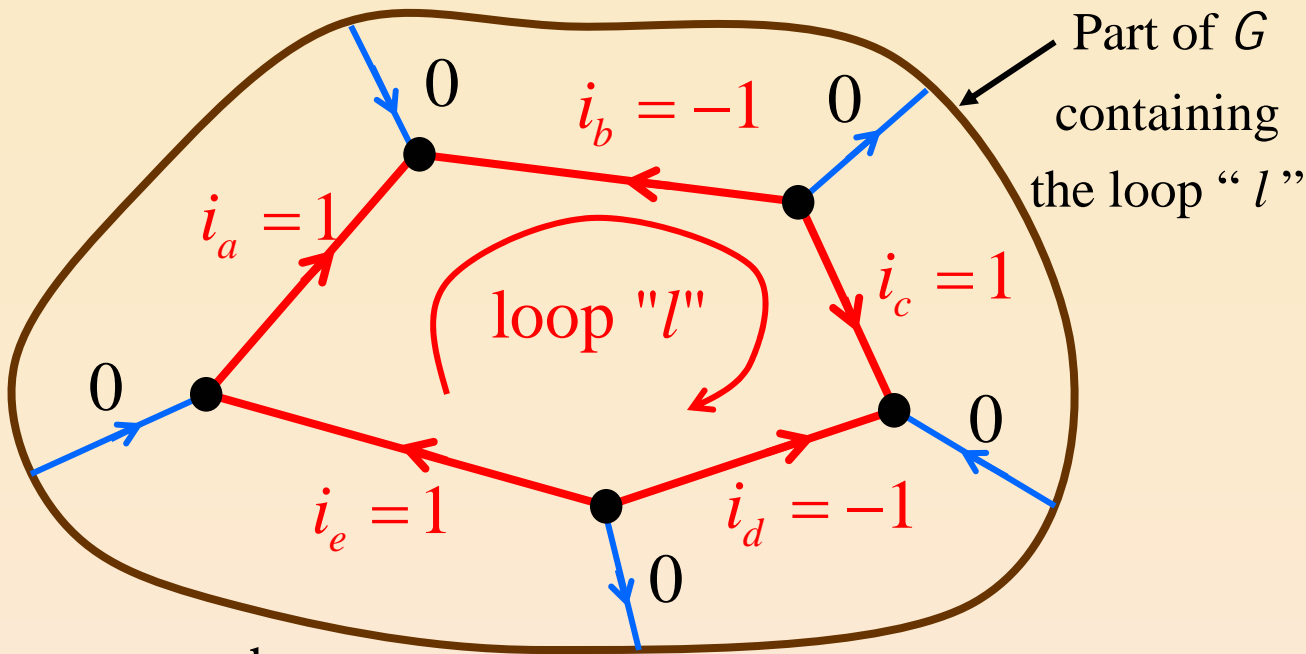

Suppose we choose:

This choice
of
 $\{i_1, i_2, \dots, i_b\}$
Satisfies
KCL

$i_j = 0$, if i_j is **not** in loop "l"
 $= 1$, if i_j is in loop "l" and flows in
 the same direction as loop "l"
 $= -1$, if i_j is in loop "l" and flows in
opposite direction as loop "l"

$$\therefore \sum_{j=1}^b v_j i_j = 0 \quad (\text{because } v_j \text{ chosen earlier satisfies Tellegen's theorem})$$

$$0 = \sum_{j=1}^b v_j i_j = \underbrace{\sum_{b_j \text{ belonging to loop "l"}} v_j i_j}_{\text{equals 0 because } i_j = 0} + \underbrace{\sum_{b_j \text{ not belonging to loop "l"}} v_j i_j}_{\text{equals 0 because } i_j = 0}$$

$$\Rightarrow \sum_{b_j \text{ belonging to loop "l"}} v_j i_j = 0 \Rightarrow \text{KVL} \quad \blacksquare$$

Relationship Between Kirchhoff's Laws and Tellegen's Theorem

1. **KCL** and **KVL** \longrightarrow **Tellegen's Theorem**
2. **KVL** and **Tellegen's Theorem** \longrightarrow **KCL**
3. **Tellegen's Theorem** and **KCL** \longrightarrow **KVL**

KVL and Tellegen's Theorem \longrightarrow KCL

Proof.

Let \mathbf{v} satisfy KVL for G :

$$\mathbf{v} = \mathbf{A}^T \mathbf{e} \quad (1)$$

Let \mathbf{v} and \mathbf{i} satisfy Tellegen's Theorem:

$$\mathbf{v}^T \mathbf{i} = 0 \quad (2)$$

Substitute (1) for \mathbf{v} in (2):

$$\left(\mathbf{A}^T \mathbf{e} \right)^T \mathbf{i} = 0 \quad (3)$$

$$\mathbf{e}^T (\mathbf{A} \mathbf{i}) = 0 \quad (4)$$

Since (4) is true for any node-to-datum voltages $\mathbf{e} \neq \mathbf{0}$,

(4) can be true only if

$$\boxed{\mathbf{A} \mathbf{i} = \mathbf{0}} \quad \Rightarrow \quad \mathbf{KCL} \quad \blacksquare$$

Tellegen's Theorem and KCL \longrightarrow KVL

Proof.

Let G be any connected digraph with b branches $\{1, 2, \dots, b\}$.

Let $\{i_1, i_2, \dots, i_b\}$ be any set of branch currents satisfying KCL.

Choose *any* subset $\{b_a, b_b, \dots, b_n\}$ of the b branches which form a **closed loop** “ l ”. Let $\{v_1, v_2, \dots, v_b\}$ be *any* set of branch voltages which, together with $\{i_1, i_2, \dots, i_b\}$ satisfy Tellegen's Theorem.

Our goal is to prove that the subset of these voltages which belong to the above closed loop “ l ” must satisfy KVL around the loop.

Applying Tellegen's Theorem to Circuits Containing $(n+1)$ -terminal devices

Let N be any circuit containing $(n+1)$ -terminal devices.


Step 1. Assign a datum to each device. Assign “ n ” terminal-to-datum voltages for each $(n+1)$ -terminal device, following **associated reference convention**.

Step 2. Draw the digraph G of N .


Step 3. Apply Tellegen's theorem to G .

Remarks

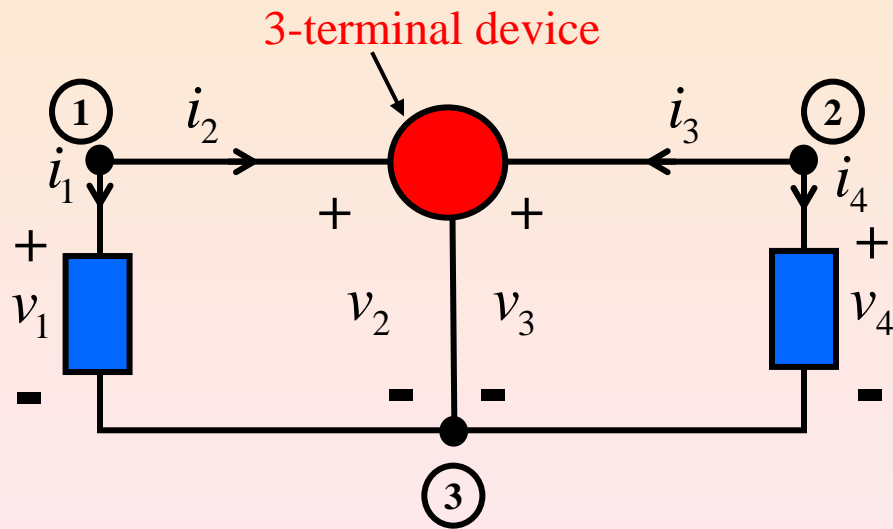Tellegen's theorem can be applied directly to a circuit provided we use Associated Reference convention for all device terminal currents and voltages.



circuit N


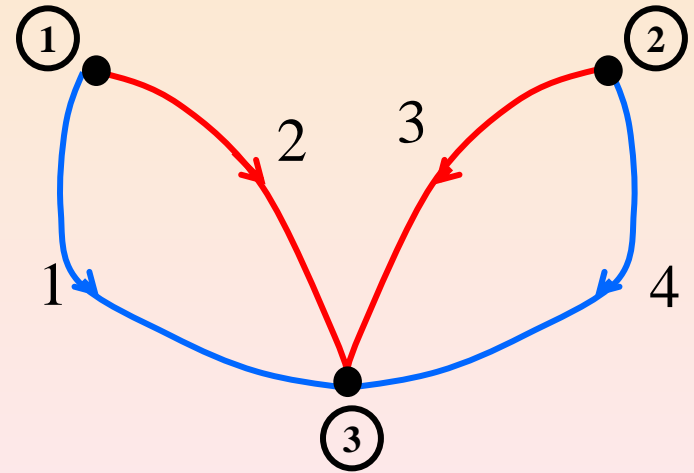


digraph G

$$\sum_{j=1}^4 v_j i_j = v_1 i_1 + v_2 i_2 + v_3 i_3 + v_4 i_4 = 0$$

(choose ③ as datum node for the 3-terminal device)

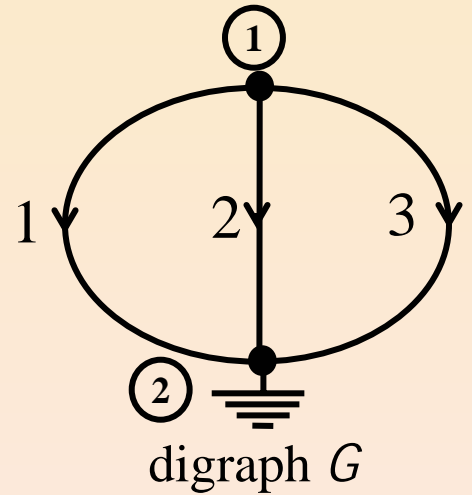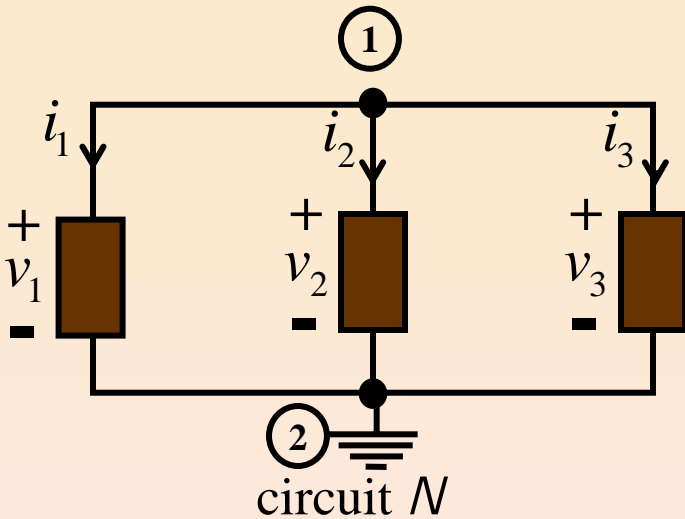Voltage and Current Solutions are Orthogonal!




Reduced Incidence Matrix

$$\mathbf{A} = [1 \quad 1 \quad 1]$$



$$\text{KCL} : \mathbf{A} \mathbf{i} = \mathbf{0}$$
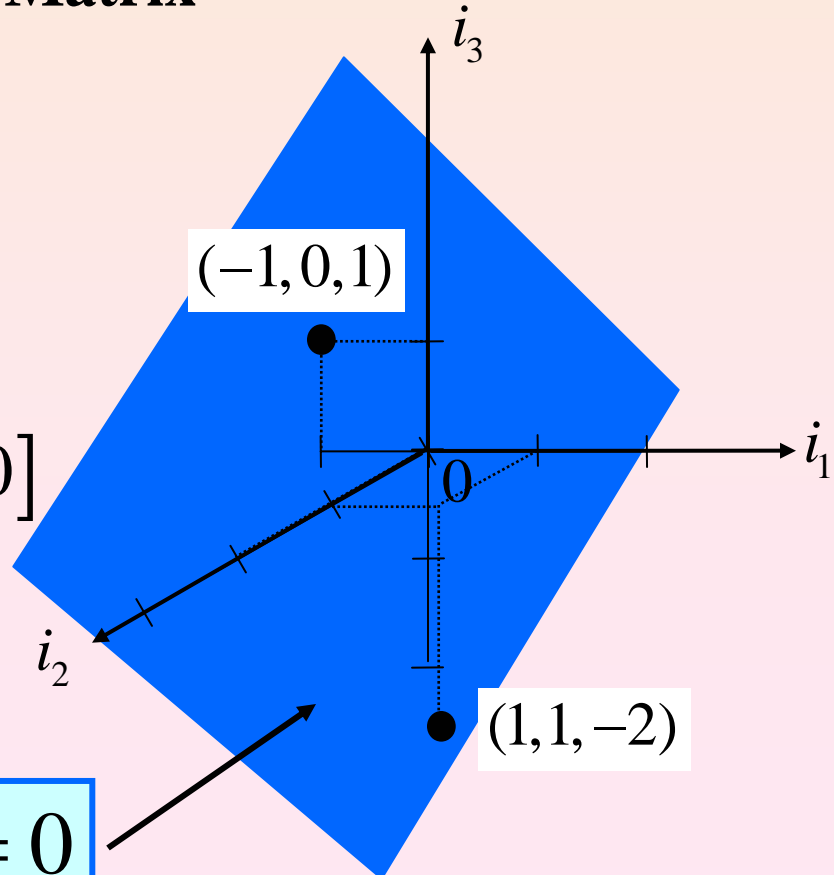
$$\underbrace{\begin{bmatrix} 1 & 1 & 1 \end{bmatrix}}_{\mathbf{A}} \underbrace{\begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix}}_{\mathbf{i}} = \begin{bmatrix} 0 \end{bmatrix}$$



$$i_1 + i_2 + i_3 = 0$$

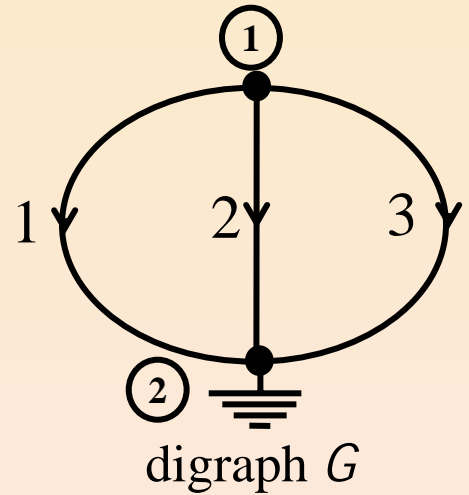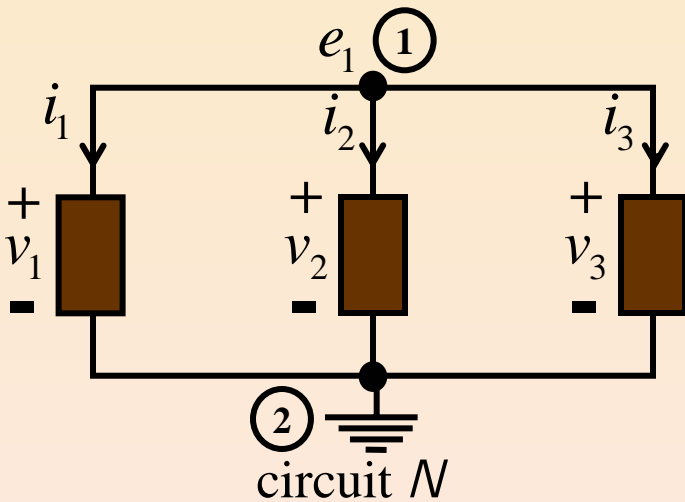Voltage and Current Solutions are Orthogonal!




Reduced Incidence Matrix

$$\mathbf{A} = \begin{bmatrix} 1 & 1 & 1 \end{bmatrix}$$

$$\text{KVL} : \mathbf{v} = \mathbf{A}^T \mathbf{e}$$
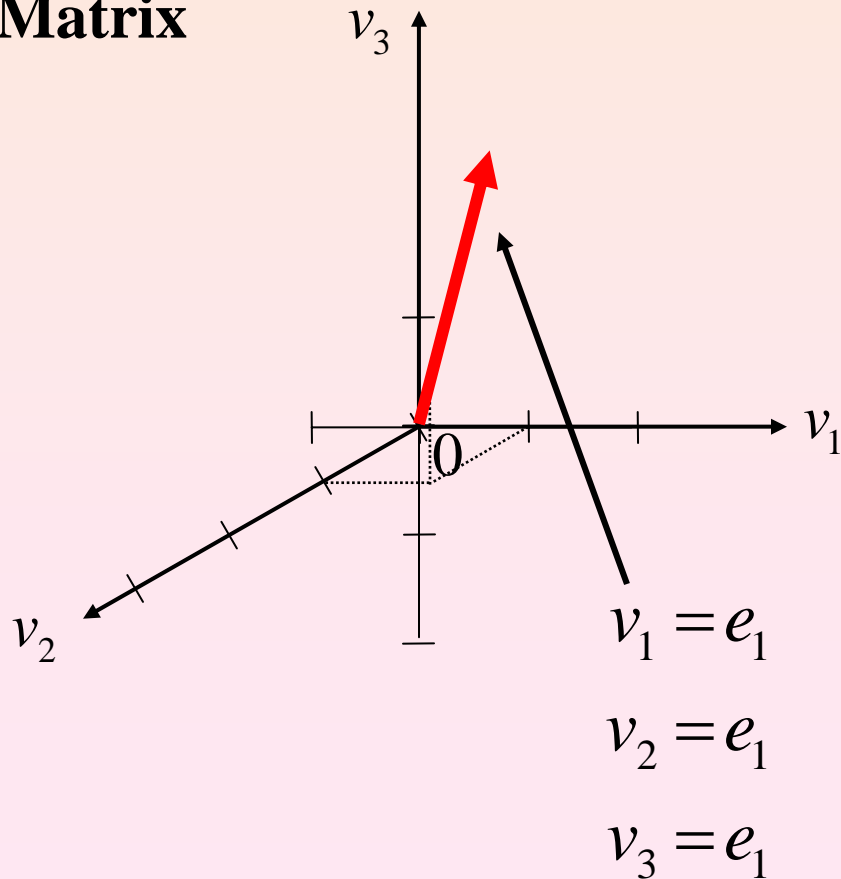
$$\underbrace{\begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}}_{\mathbf{v}} = \underbrace{\begin{bmatrix} 1 \\ 1 \\ 1 \end{bmatrix}}_{\mathbf{A}^T} \underbrace{\begin{bmatrix} \mathbf{e}_1 \end{bmatrix}}_{\mathbf{e}}$$



Geometrical Interpretation of Tellegen's Theorem

$$\text{KCL} : i_1 + i_2 + i_3 = 0$$

$$\text{KVL} : v_1 = v_2 = v_3$$

$$\begin{aligned} \sum_{j=1}^3 v_j i_j &= v_1 i_1 + v_2 i_2 + v_3 i_3 \\ &= e_1 i_1 + e_1 i_2 + e_1 i_3 \\ &= e_1 (i_1 + i_2 + i_3) = 0 \end{aligned}$$

All voltage solutions
(v_1, v_2, v_3) falling on
this line satisfy KVL.

$$i_1 + i_2 + i_3 = 0$$

All current solutions
(i_1, i_2, i_3) falling on this
plane satisfy KVL.

i_2, v_2

