


The solution of **differential equation**


$$\frac{dx}{dt} = -\frac{x}{\tau} + \frac{x(t_{\infty})}{\tau}$$

with a given **initial condition** $x(t_0)$ at

$t = t_0$ is a time function $\hat{x}(t)$ (waveform)

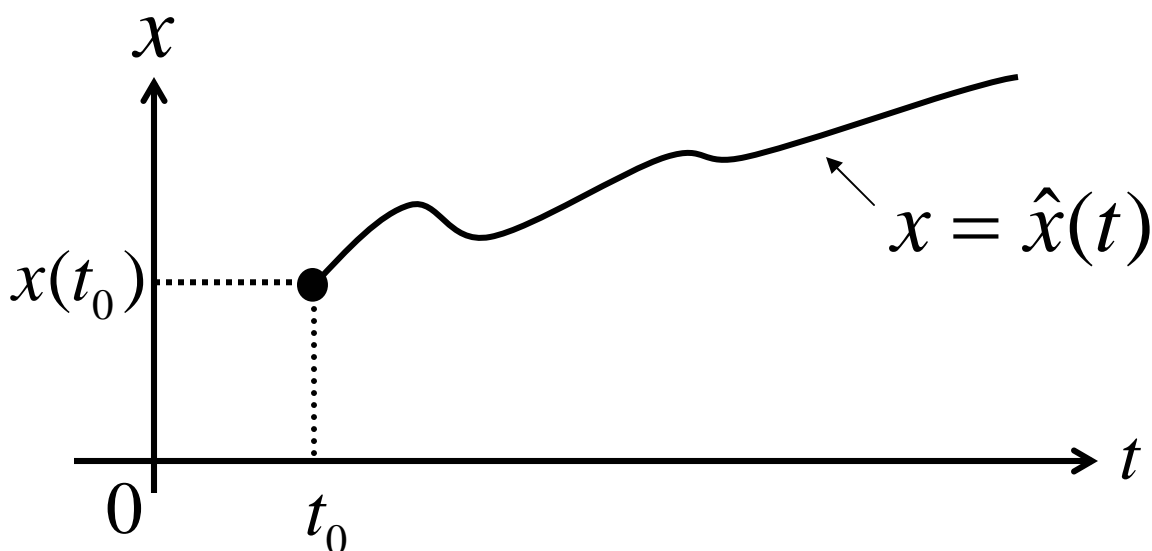which satisfies both the differential equation and the initial condition.



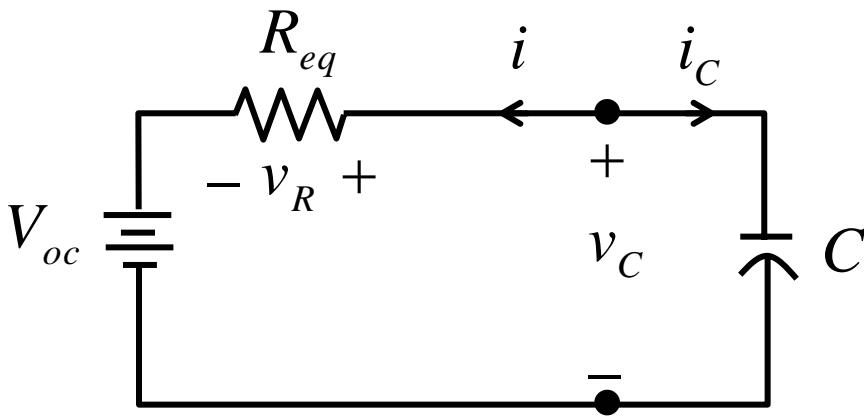

$$\text{KCL} \Rightarrow i = -i_C$$

$$\text{KVL} \Rightarrow v_R = v_C - V_{oc}$$


$$\text{Ohms law} \Rightarrow i = \frac{v_R}{R_{eq}} = \frac{v_C - V_{oc}}{R_{eq}}$$

$$\begin{aligned} \text{capacitor law} \Rightarrow i_c &= C \frac{dv_C}{dt} \\ &= -i \\ &= -\frac{(v_C - V_{oc})}{R_{eq}} \end{aligned}$$


$$\frac{dv_C}{dt} = -\frac{v_C}{R_{eq}C} + \frac{V_{oc}}{R_{eq}C}$$

$$\text{define } x \triangleq v_C, \quad x(t_\infty) \triangleq V_{oc}, \quad \tau \triangleq R_{eq}C$$
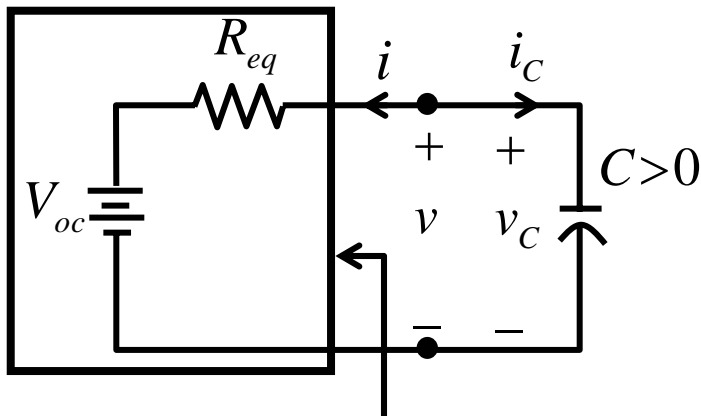
$$\frac{dx}{dt} = -\frac{x}{\tau} + \frac{x(t_\infty)}{\tau}$$




Thevenin Equivalent circuit N

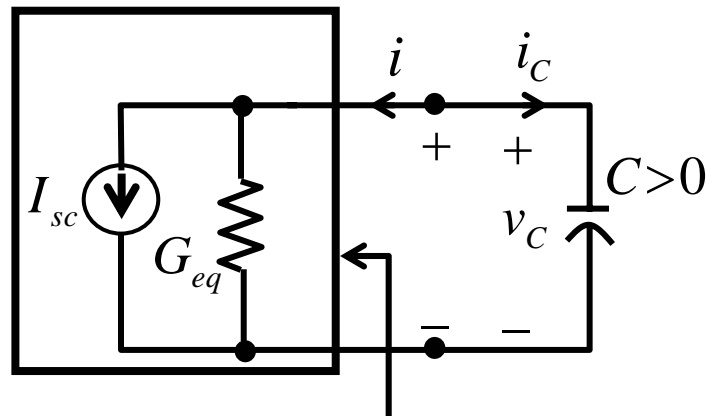

Norton Equivalent circuit N

DP (Driving-Point)
Plot of N

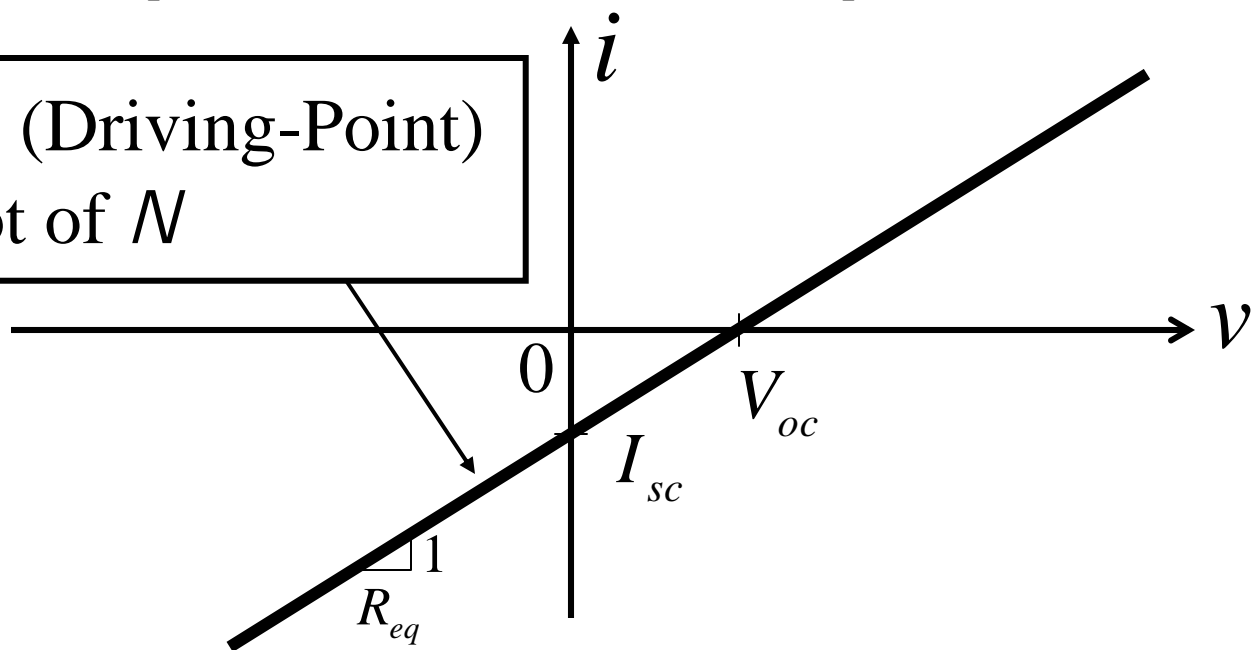


$$i(t) = -i_C(t) = -C \frac{dv_C}{dt} = -C \frac{dv}{dt}$$

$C > 0 \Rightarrow$

$$\left. \frac{dv(t)}{dt} \right|_{t=t_k} > 0 \quad \text{iff} \quad \left. i(t) \right|_{t=t_k} < 0$$


$$\left. \frac{dv(t)}{dt} \right|_{t=t_k} < 0 \quad \text{iff} \quad \left. i(t) \right|_{t=t_k} > 0$$

$$\left. \frac{dv(t)}{dt} \right|_{t=t_k} = 0 \quad \text{iff} \quad \left. i(t) \right|_{t=t_k} = 0$$

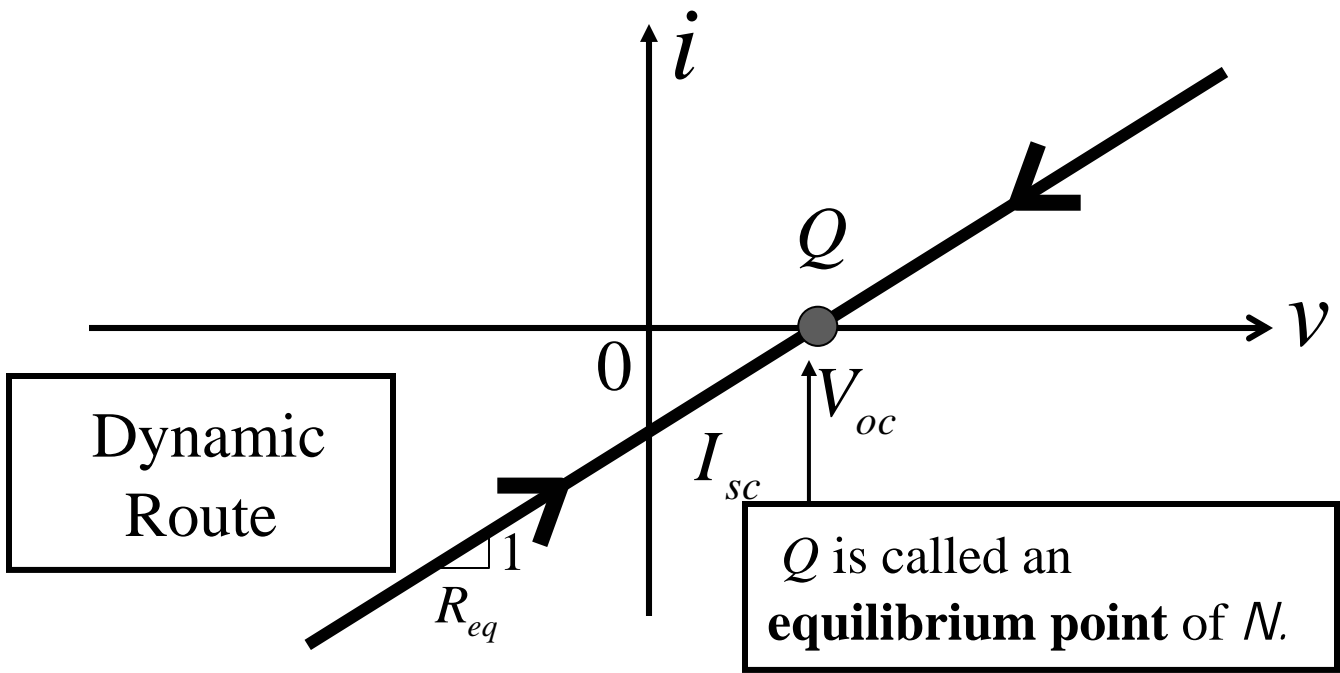

Thevenin's Theorem

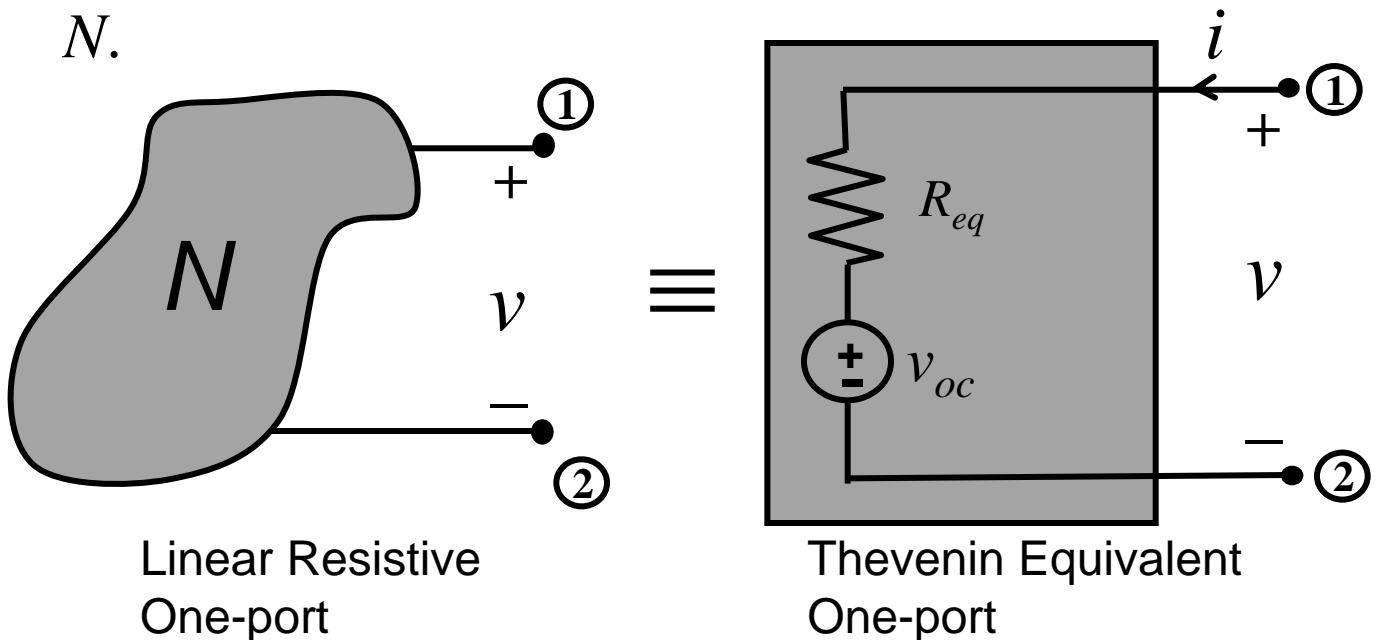We can substitute the 2-terminal box N with an equivalent one-port called the **Thevenin Equivalent Circuit** made of a **linear resistance** R_{eq} , called the Thevenin **equivalent resistance**, **in series** with an independent voltage source v_{oc} , called the Thevenin **open-circuit voltage**, without affecting the solutions inside *any* external circuit N_{ext} connected across N .



Norton's Theorem

We can substitute the 2-terminal box N with an **equivalent** one-port called the **Norton Equivalent Circuit** made of a **linear conductance** G_{eq} , called the Norton **equivalent conductance**, in **parallel** with an independent current source i_{sc} , called the Norton **short-circuit current**, without affecting the solutions inside *any* external circuit Next connected across

