

# Chapters 2, 4 and 5 from Reader


---

- **OUTLINE**
  - Diode Current and Equation
  - Some Interesting Circuit Applications
  - Load Line Analysis
  - Solar Cells, Detectors, Zener Diodes
  - Circuit Analysis with Diodes
  - Half-wave Rectifier
  - Clamps and Voltage Doublers using Capacitors
  - MOSFETs
  - Transistor small signal amplifier circuits
- **Reading**
  - Reader: Chapter 2, Chapter 4 and 5
 
# I-V Characteristics


---

In forward bias (+ on p-side) we have almost unlimited flow (very low resistance). Qualitatively, the I-V characteristics must look like:




In reverse bias (+ on n-side) almost no current can flow. Qualitatively, the I-V characteristics must look like:

 The current is close to zero for any negative bias




# Diode Physical Behavior and Equation


Schematic Device

 

Symbol

 

Qualitative I-V characteristics:

 

Quantitative I-V characteristics:

$$I = I_0(e^{qV/kT} - 1)$$

In which  $kT/q$  is 0.026V and  $I_0$  is a constant depending on diode area. Typical values:  $10^{-12}$  to  $10^{-16}$  A. Interestingly, the graph of this equation looks just like the figure to the left.

**A non-ideality factor  $n$  times  $kT/q$  is often included.**

# The pn Junction I vs. V Equation

---

## I-V characteristic of PN junctions

In EECS 105, 130, and other courses you will learn why the I vs. V relationship for PN junctions is of the form


$$I = I_0(e^{qV/kT} - 1)$$

where  $I_0$  is a constant proportional to junction area and depending on doping in P and N regions,  $q$  = electronic charge =  $1.6 \times 10^{-19}$ ,  $k$  is Boltzman constant, and  $T$  is absolute temperature.  
 $kT/q = 0.026V$  at  $300^\circ K$ , a typical value for  $I_0$  is  $10^{-12} - 10^{-15} A$


We note that in forward bias,  $I$  increases **exponentially** and is in the  $\mu A$ - $mA$  range for voltages typically in the range of  $0.6$ - $0.8V$ . In reverse bias, the current is essentially zero.
 
# Diode Ideal (Perfect Rectifier) Model

The equation  $I = I_0 \exp\left(\frac{qV}{kT} - 1\right)$  is graphed below for  $I_0 = 10^{-15}$  A




 The characteristic is described as a “rectifier” – that is, a device that permits current to pass in only one direction. (The hydraulic analog is a “check valve”.) Hence the symbol:




 
## Simple “Perfect Rectifier” Model

If we can ignore the small forward-bias voltage drop of a diode, a simple effective model is the “perfect rectifier,” whose I-V characteristic is given below:




# Diode Large-Signal Model (0.7 V Drop)

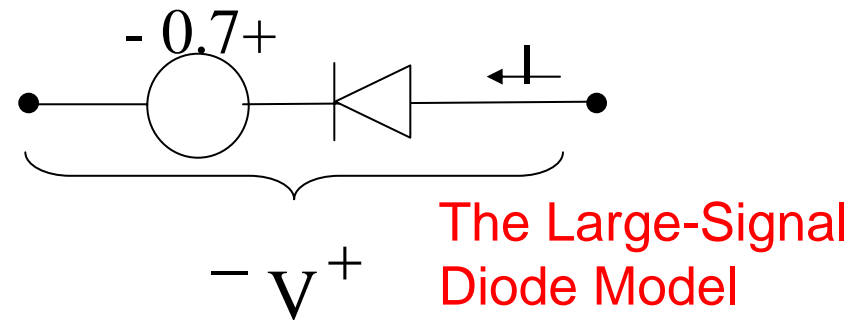 


 
## Improved "Large-Signal Diode" Model:

If we choose not to ignore the small forward-bias voltage drop of a diode, it is a very good approximation to regard the voltage drop in forward bias as a constant, about 0.7V. the "Large signal model" results.



  
# Rectifier Circuit

Assume the ideal  
(perfect rectifier)  
model.






“rectified” version of  
input waveform

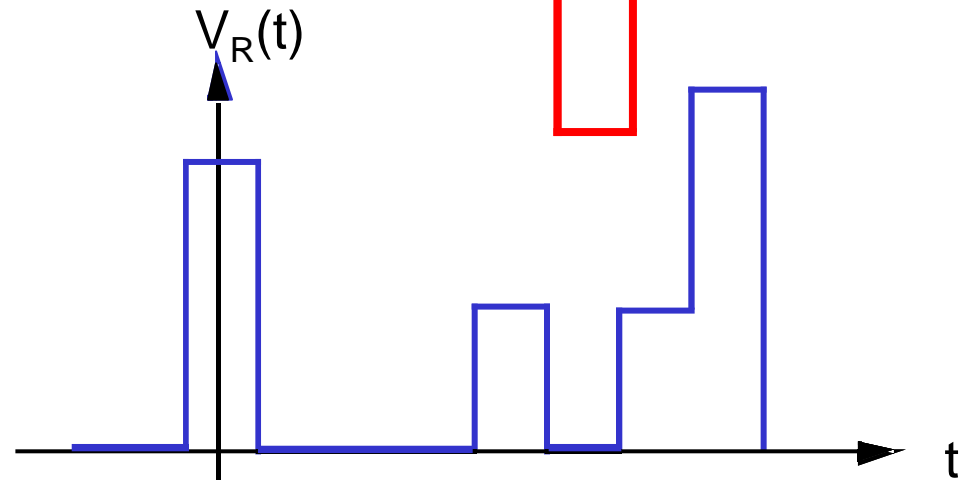
   
# Peak Detector Circuit

Assume the ideal (perfect rectifier) model.




**Key Point:**  
The capacitor charges due to one way current behavior of the diode.



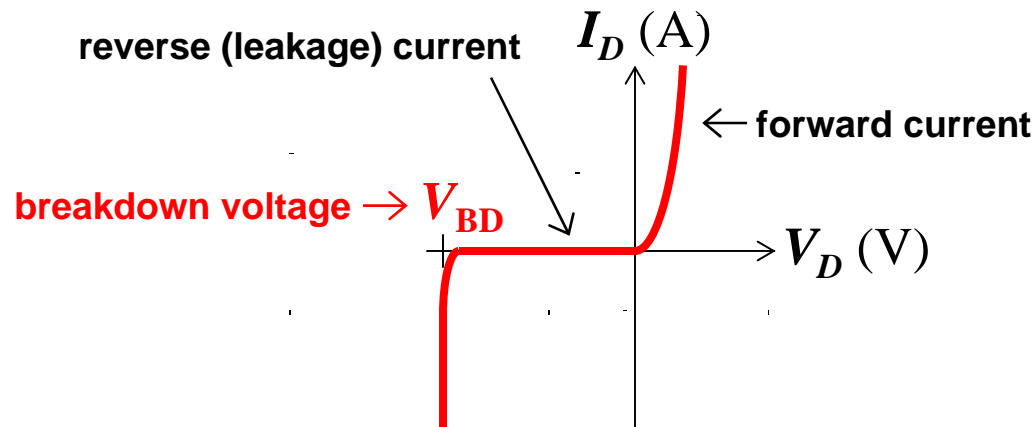
# pn-Junction Reverse Breakdown

- As the reverse bias voltage increases, the peak electric field in the depletion region increases. When the electric field exceeds a critical value ( $E_{crit} \cong 2 \times 10^5$  V/cm), the reverse current shows a dramatic increase:



 
# Zener Diode

A **Zener diode** is designed to operate in the breakdown mode.




Example:

 

# Load Line Analysis Method

 
1. Graph the  $I$ - $V$  relationships for the non-linear element and for the rest of the circuit
2. The operating point of the circuit is found from the intersection of these two curves.



The  $I$ - $V$  characteristic of all of the circuit except the non-linear element is called the load line
 
# Solar cell: Example of simple PN junction

- What is a solar cell?
  - Device that converts sunlight into electricity
- How does it work?
  - In simple configuration, it is a diode made of PN junction
  - Incident light is absorbed by material
  - Creates electron-hole pairs that transport through the material through
    - Diffusion (concentration gradient)
    - Drift (due to electric field)




**PN Junction Diode**
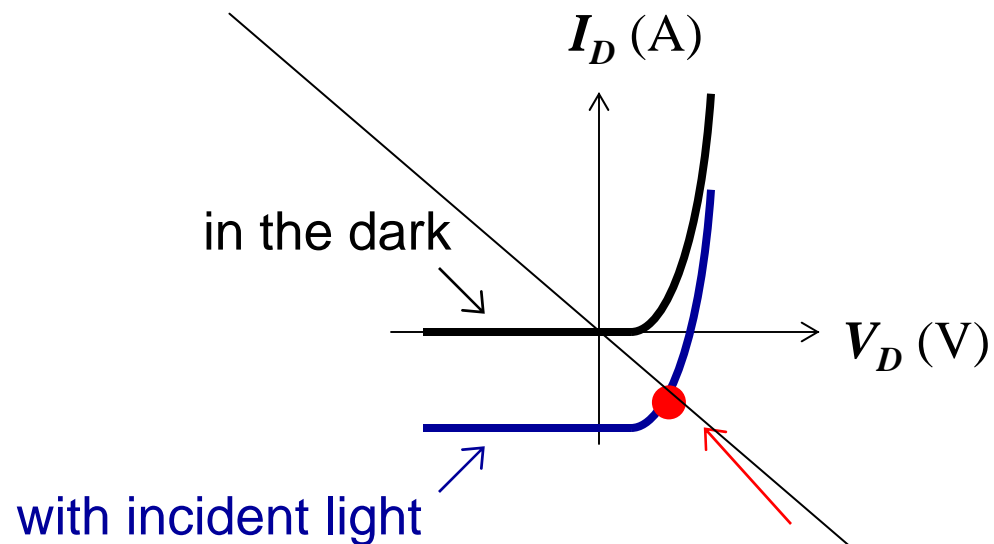
# Photovoltaic (Solar) Cell

---

$$I_D = I_S (e^{qV_D/kT} - 1) - I_{optical}$$



**Operating point**  
**The load line a simple resistor.**

# I-V characteristics of the device

- I-V characteristics of a PN junction is given by


$$I = I_s \left[ \exp\left(\frac{eV}{kT}\right) - 1 \right] - I_L$$

where  $I_s$  is the saturation intensity depending on band gap and doping of the material and  $I_L$  is the photocurrent generated due to light

- Efficiency is defined as

$$\eta = \frac{I_m \cdot V_m}{\text{Light Intensity}} = \frac{FF * V_{oc} * I_{sc}}{\text{Light Intensity}}$$

FF is the Fill Factor

 


$V_{oc}$  - Open circuit voltage

$I_{sc}$  - Short circuit current

$I_{mp}$ ,  $V_{mp}$  - Current and voltage at maximum power


## Example 2: Photodiode

 


- An intrinsic region is placed between the p-type and n-type regions

- $W_j \cong W_{i\text{-region}}$ , so that most of the electron-hole pairs are generated in the depletion region

 → faster response time  
(~10 GHz operation)




# Photodetector Circuit Using Load Line

 

As light shines on the photodiode, carriers are generated by absorption. These excess carriers are swept by the electric field at the junction creating drift current, which is same direction as the reverse bias current and hence negative current. The current is proportional to light intensity and hence can provide a direct measurement of light intensity → photodetector.

 operating points under different light conditions.




- What happens when  $R_{th}$  is too large?
- Why use  $V_{th}$ ?




# Ideal Diode Model of PN Diode


## Circuit symbol

 

## I-V characteristic

 


## Switch model

 


- An ideal diode passes current only in one direction.
  - An **ideal diode** has the following properties:
    - when  $I_D > 0$ ,  $V_D = 0$
    - when  $V_D < 0$ ,  $I_D = 0$
- } Diode behaves like a switch:
- closed in forward bias mode
  - open in reverse bias mode

# Large-Signal Diode Model


## Circuit symbol

 

## I-V characteristic

 

## Switch model

 

For a Si pn diode,  $V_{Don} \cong 0.7 \text{ V}$

RULE 1: When  $I_D > 0$ ,  $V_D = V_{Don}$

RULE 2: When  $V_D < V_{Don}$ ,  $I_D = 0$



Diode behaves like a voltage source in series with a switch:

- closed in forward bias mode
- open in reverse bias mode
  
# Diode: Large Signal Model

- Use piece-wise linear model

"Practical" diode model  
ideal with offset



# How to Analyze Circuits with Diodes

---


**A diode has only two states:**

- **forward biased:**  $I_D > 0$ ,  $V_D = 0$  V (or 0.7 V)
- **reverse biased:**  $I_D = 0$ ,  $V_D < 0$  V (or 0.7 V)

Procedure:

1. Guess the state(s) of the diode(s)
2. Check to see if KCL and KVL are obeyed.
3. If KCL and KVL are not obeyed, refine your guess
4. Repeat steps 1-3 until KCL and KVL are obeyed.

Example:

 

If  $v_s(t) > 0$  V, diode is forward biased  
(else KVL is disobeyed – try it)


If  $v_s(t) < 0$  V, diode is reverse biased  
(else KVL is disobeyed – try it)

# Diode Logic: AND Gate


- Diodes can be used to perform logic functions:
 
## AND gate

output voltage is high only if  
both A and B are high



 
Inputs **A** and **B** vary between 0 Volts (“low”) and  $V_{CC}$  (“high”) Between what voltage levels does **C** vary?


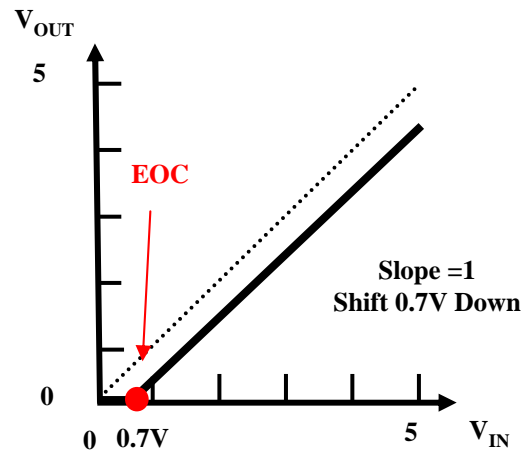
# Diode Logic: OR Gate


- Diodes can be used to perform logic functions:

Inputs **A** and **B** vary between 0 Volts (“low”) and  $V_{CC}$  (“high”) Between what voltage levels does **C** vary?


 
## OR gate

output voltage is high if either (or both) A and B are high



# Diode Logic: Incompatibility and Decay


- Diode Only Gates are Basically Incompatible:

## AND gate

output voltage is high only if both A and B are high

 
## OR gate

output voltage is high if either (or both) A and B are high




# Device Isolation using pn Junctions

---

 

 No current flows if voltages are applied between n-type regions, because two pn junctions are “back-to-back”



=> n-type regions **isolated** in p-type substrate and vice versa



# Why are pn Junctions Important for ICs?


---

- The basic building block in digital ICs is the MOS transistor, whose structure contains reverse-biased diodes.
  - pn junctions are important for electrical isolation of transistors located next to each other at the surface of a Si wafer.
  - The junction capacitance of these diodes can limit the performance (operating speed) of digital circuits

 
# Power Conversion Circuits

---

- Converting AC to DC
- Potential applications: Charging a battery



# Rectifier Equivalent circuit

 


$V > 0.6V$ , diode = short circuit

$$\rightarrow V_o = V_I - 0.6$$



$V < 0.6V$ , diode = open circuit

$$\rightarrow V_o = 0$$

 


# Half-wave Rectifier Circuits

- Adding a capacitor: what does it do?

 
 


# Half-Wave Rectifier

---

 


# Level Shift Circuit

  

Once the capacitor is charged by the negative most voltage the rest of the signal is shifted up by that amount.

# Voltage Doubler Circuit

---

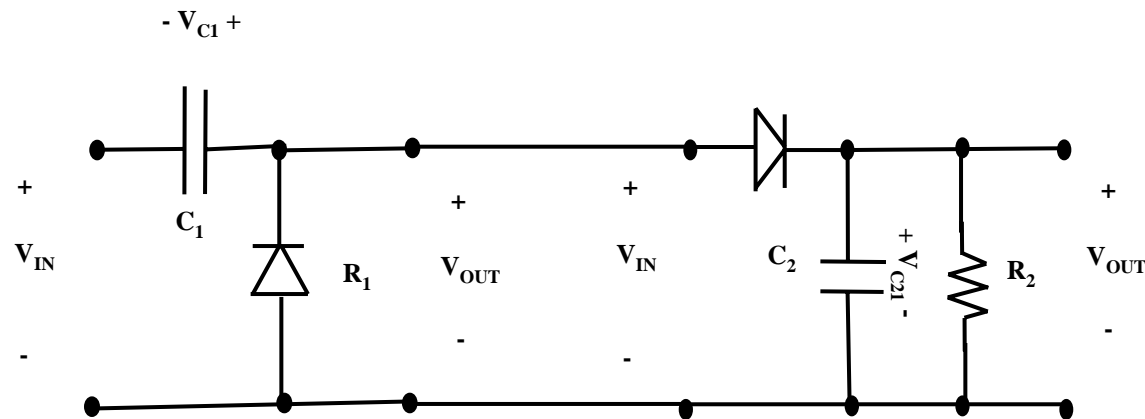

Level Shift

Peak Detect

The final output is the peak to peak voltage of the input.

# MOSFETs: Detailed outline

---

- OUTLINE
  - The MOSFET as a controlled resistor
  - Pinch-off and current saturation
  - MOSFET  $I_D$  vs.  $V_{GS}$  characteristic
  - NMOS and PMOS I-V characteristics
  - Load-line analysis; Q operating point; Bias circuits
  - Small-signal equivalent circuits
  - Common source amplifier
  - Source follower
  - Common gate amplifier
  - Gain
- Reading
  - Reader: Chapters 4 and 5




# MOSFET Terminals

---

- The voltage applied to the GATE terminal determines whether current can flow between the SOURCE & DRAIN terminals.
  - For an n-channel MOSFET, the SOURCE is biased at a *lower* potential (often 0 V) than the DRAIN  
(Electrons flow from SOURCE to DRAIN when  $V_G > V_T$ )
  - For a p-channel MOSFET, the SOURCE is biased at a *higher* potential (often the supply voltage  $V_{DD}$ ) than the DRAIN  
(Holes flow from SOURCE to DRAIN when  $V_G < V_T$ )
- The BODY terminal is usually connected to a fixed potential.
  - For an n-channel MOSFET, the BODY is connected to 0 V
  - For a p-channel MOSFET, the BODY is connected to  $V_{DD}$

# MOSFET Structure

 

- In the absence of gate voltage, no current can flow between S and D.
- Above a certain gate to source voltage  $V_t$  (the “threshold”), electrons are induced at the surface beneath the oxide. (Think of it as a capacitor.)
- These electrons can carry current between S and D if a voltage is applied.

# MOSFET

- Symbol and subscript convention
  - Upper case for both (e.g.  $V_D$ ) = DC signal (often as bias)
  - Lower case for both (e.g.  $v_d$ ) = AC signal (often small signal)
  - Lower symbol and upper sub (e.g.  $v_{D}$ ) = total signal =  $V_D + v_d$

- **NMOS**: Three regions of operation

- $V_{DS}$  and  $V_{GS}$  normally **positive** values
- $V_{GS} < V_t$ : cut off mode,  $I_{DS} = 0$  for any  $V_{DS}$
- $V_{GS} > V_t$ : transistor is turned on

- $V_{DS} < V_{GS} - V_t$ : Triode Region

$$i_D = K \left[ 2(v_{GS} - V_t)v_{DS} - v_{DS}^2 \right]$$

- $V_{DS} > V_{GS} - V_t$ : Saturation Region

$$i_D = K \left[ 2(v_{GS} - V_t)^2 \right]$$

- Boundary  $v_{GS} - V_t = v_{DS}$

$$K = \frac{W}{L} \frac{KP}{2}$$

# MOSFET

- PMOS: Three regions of operation (interchange > and < from NMOS)

- $V_{DS}$  and  $V_{GS}$  Normally **negative** values

- $V_{GS} > V_t$ : cut off mode,  $I_{DS} = 0$  for any  $V_{DS}$

- $V_{GS} < V_t$ : transistor is turned on

- $V_{DS} > V_{GS} - V_t$ : Triode Region  $i_D = K \left[ 2(v_{GS} - V_t)v_{DS} - v_{DS}^2 \right]$

- $V_{DS} < V_{GS} - V_t$ : Saturation Region  $i_D = K \left[ 2(v_{GS} - V_t)^2 \right]$


- Boundary  $v_{GS} - V_t = v_{DS}$

$$K = \frac{W}{L} \frac{KP}{2}$$

# MOSFET Operating Regions

---

## NMOS

 


## PMOS



 
# Bias Circuits

- Use load line to find Quiescent operating point.
- Remember no current flow through the gate.



Fixed-plus Self-Bias CKT

 


# MOSFET Circuit

---

- First look at DC case to find Q point
  - Use load line technique
  - All capacitors are open circuit
  - From Q-point, get  $g_m$  and  $r_d$  for small signal AC model
- AC Small signal analysis
  - DC source is AC ground (because there is no AC signal variation).
  - All capacitors are short circuit (unless otherwise specified).

# Common Source Amplifier

---

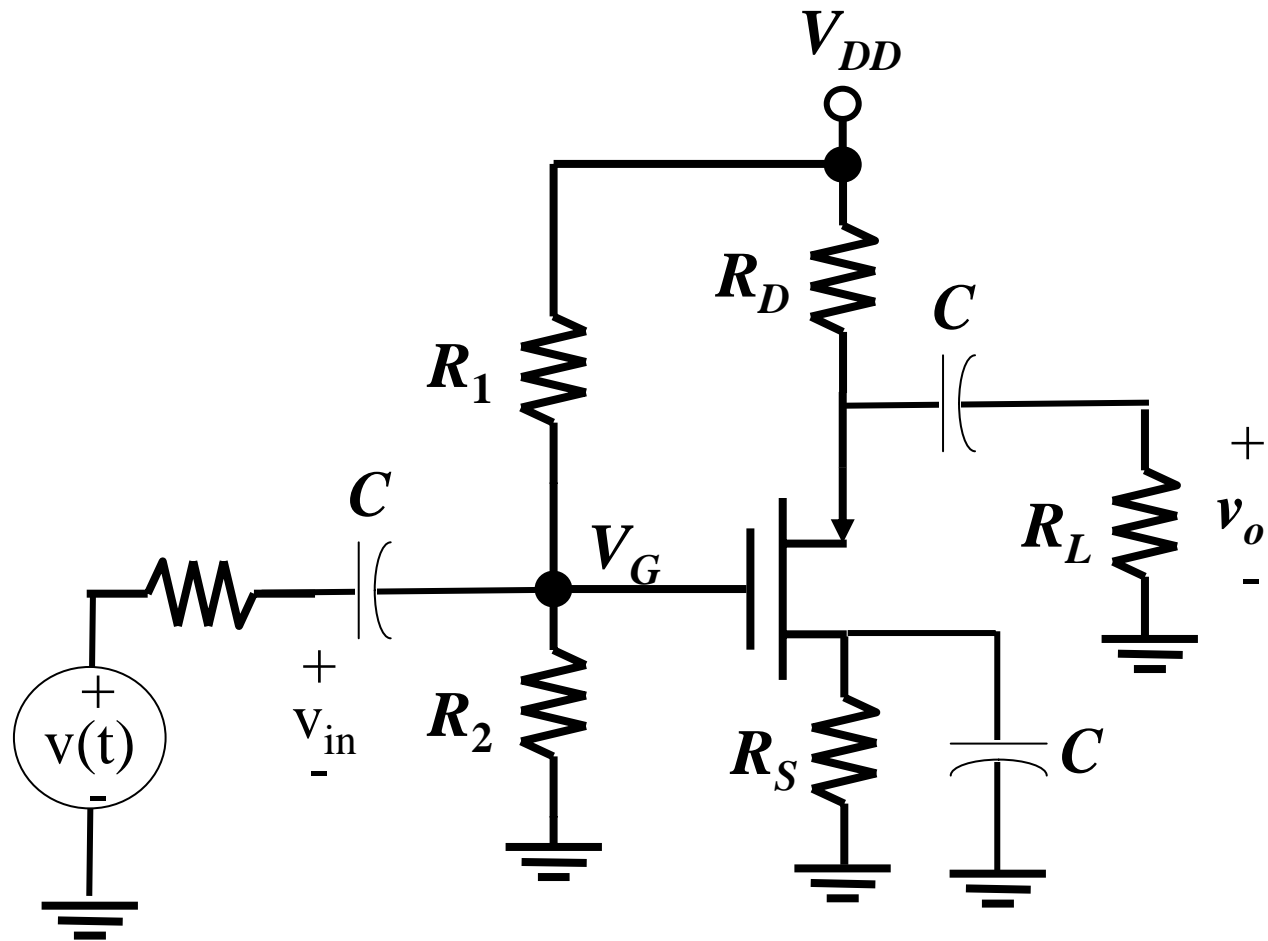




## Step 1: find Q point


$$V_G = V_{DD} \frac{R_2}{R_1 + R_2}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{DD} = I_D (R_D + R_S) + V_{DS}$$

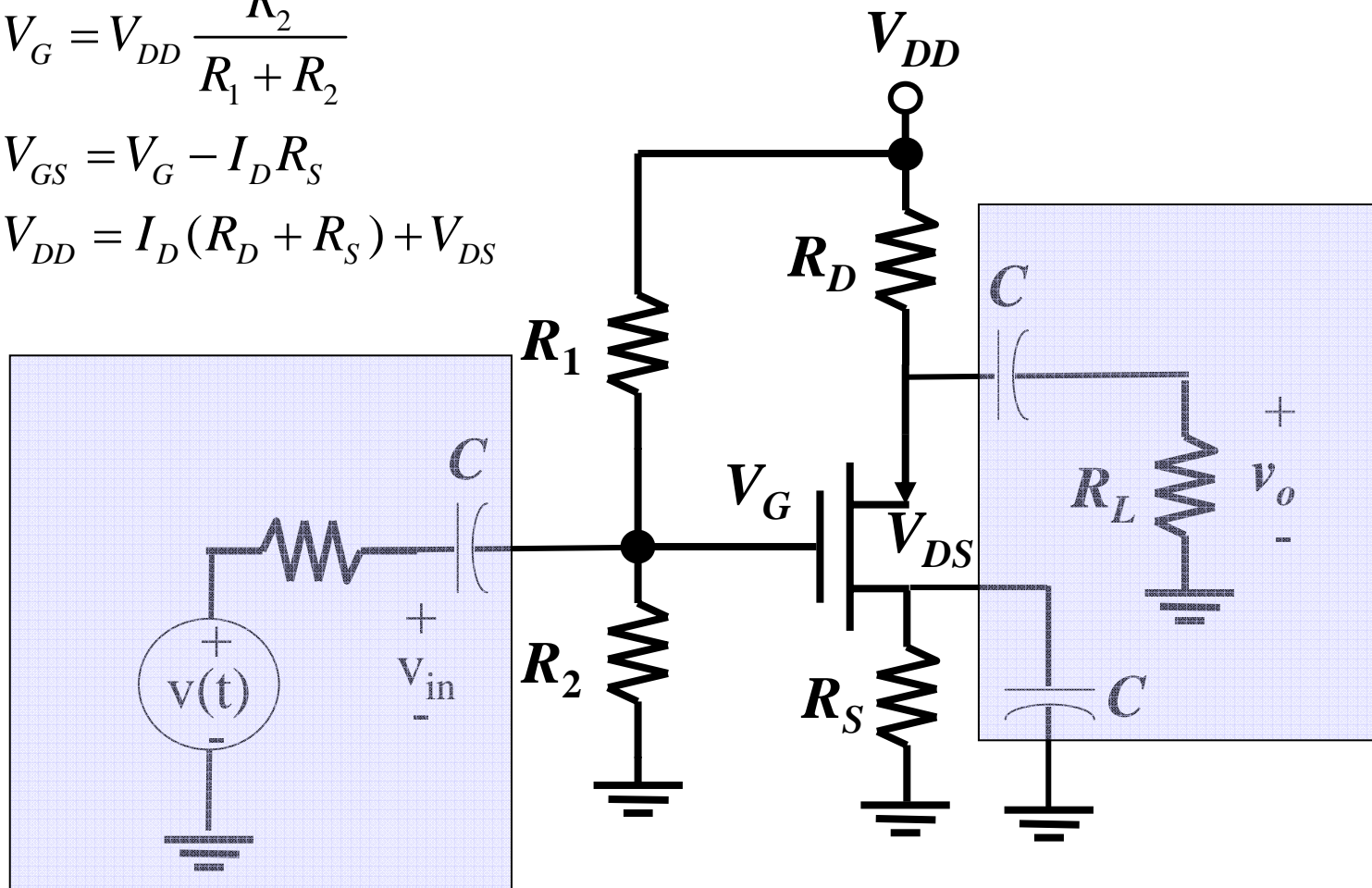

# Load line

 


$$I_D = \frac{V_{DD} - V_{DS}}{R_D + R_S}$$

$$I_D = \frac{V_G - V_{GS}}{R_S}$$

$\Downarrow$   
 $g_m$

From load lines, we get  $I_D \rightarrow$  and hence  $g_m$  and  $r_d$

# Small Signal Model

 

$$v_g = v_{in}, v_s = 0 \rightarrow v_{gs} = v_{in}$$

$$v_o = \frac{R_L R_D}{R_L + R_D} (-g_m v_{gs})$$

$$A_v = \frac{v_o}{v_{in}} = -g_m \frac{R_L R_D}{R_L + R_D}$$

$$R_{in} = \frac{v_{in}}{i_{in}} = \frac{R_1 R_2}{R_1 + R_2}$$

For output impedance  $R_{out}$ :

1. Turn off all independent sources.


2. Take away load impedance  $R_L$

$$v_{in} = 0, v_{gs} = 0, g_m v_{gs} = 0$$

$$R_{out} = \frac{r_d R_D}{r_d + R_D}$$

# Source Follower

---

 


## Step 1: find Q point


$$V_G = V_{DD} \frac{R_2}{R_1 + R_2}$$

$$V_{GS} = V_G - I_D R_S$$

$$V_{DD} = I_D R_S + V_{DS}$$

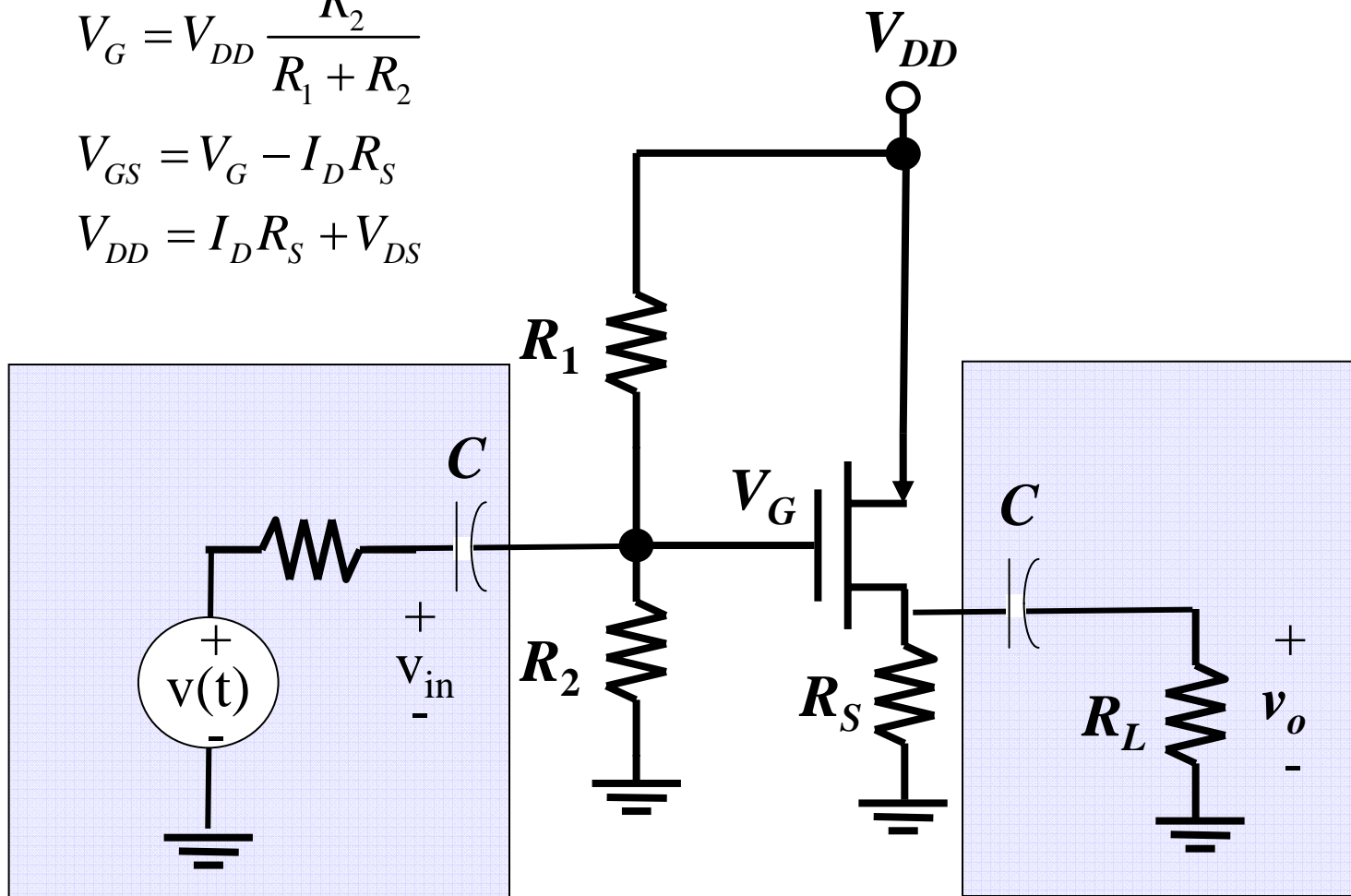


# Load line

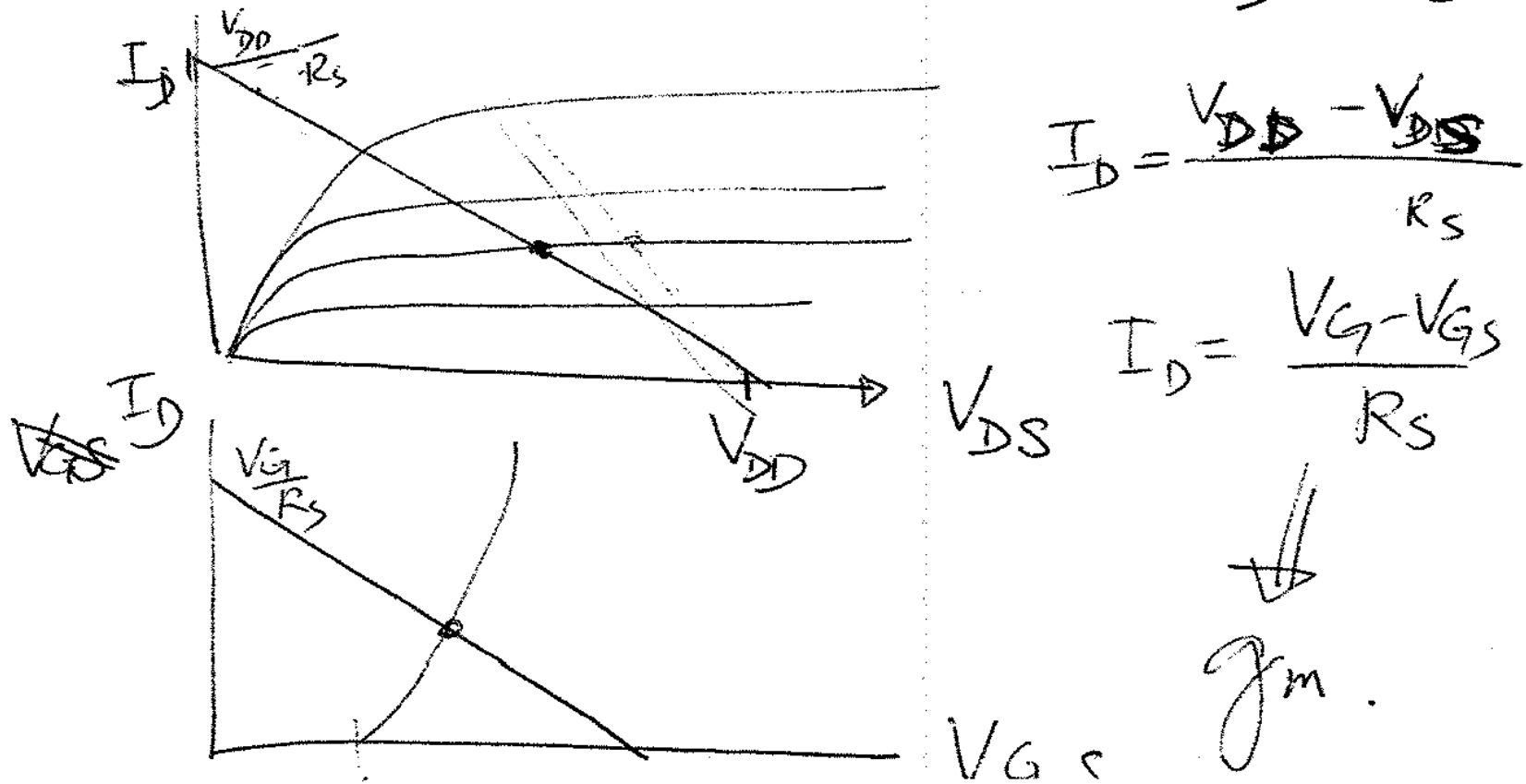

From load lines, we get  $I_D \rightarrow$  and hence  $g_m$  and  $r_d$

# Small Signal Model

 

$$R_L' = \frac{1}{r_d^{-1} + R_s^{-1} + R_L^{-1}}$$

$$v_{gs} = v_{in} - v_o$$

$$v_o = g_m v_{gs} R_L'$$

$$v_{in} = v_{gs} (1 + g_m R_L')$$

$$A_v = \frac{v_o}{v_{in}} = \frac{g_m R_L'}{1 + g_m R_L'}$$

$$R_{in} = \frac{v_{in}}{i_{in}} = \frac{R_1 R_2}{R_1 + R_2}$$

For output impedance  $R_{out}$ :

1. Turn off all independent sources.
2. Take away  $R_L$
3. Add  $V_x$  and find  $i_x$


$$v_x = v_s, v_g = 0, v_{gs} = -v_x$$

$$R_s' = \frac{r_d R_s}{r_d + R_s}, i_x = \frac{v_x}{R_s'} - g_m (-v_x) = v_x (R_s'^{-1} + g_m)$$

$$R_{out} = \frac{1}{g_m + r_d^{-1} + R_s^{-1}}$$

# Common Gate Amplifier

---

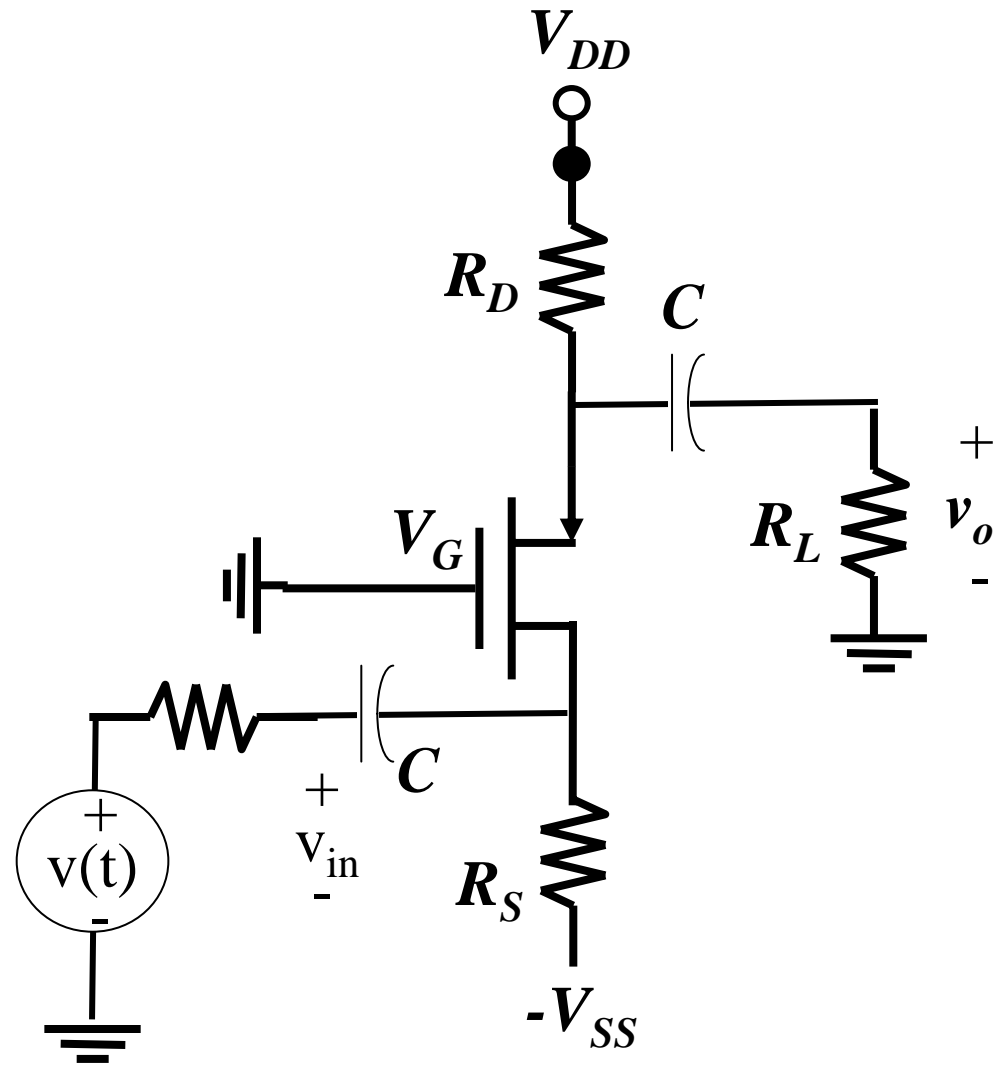



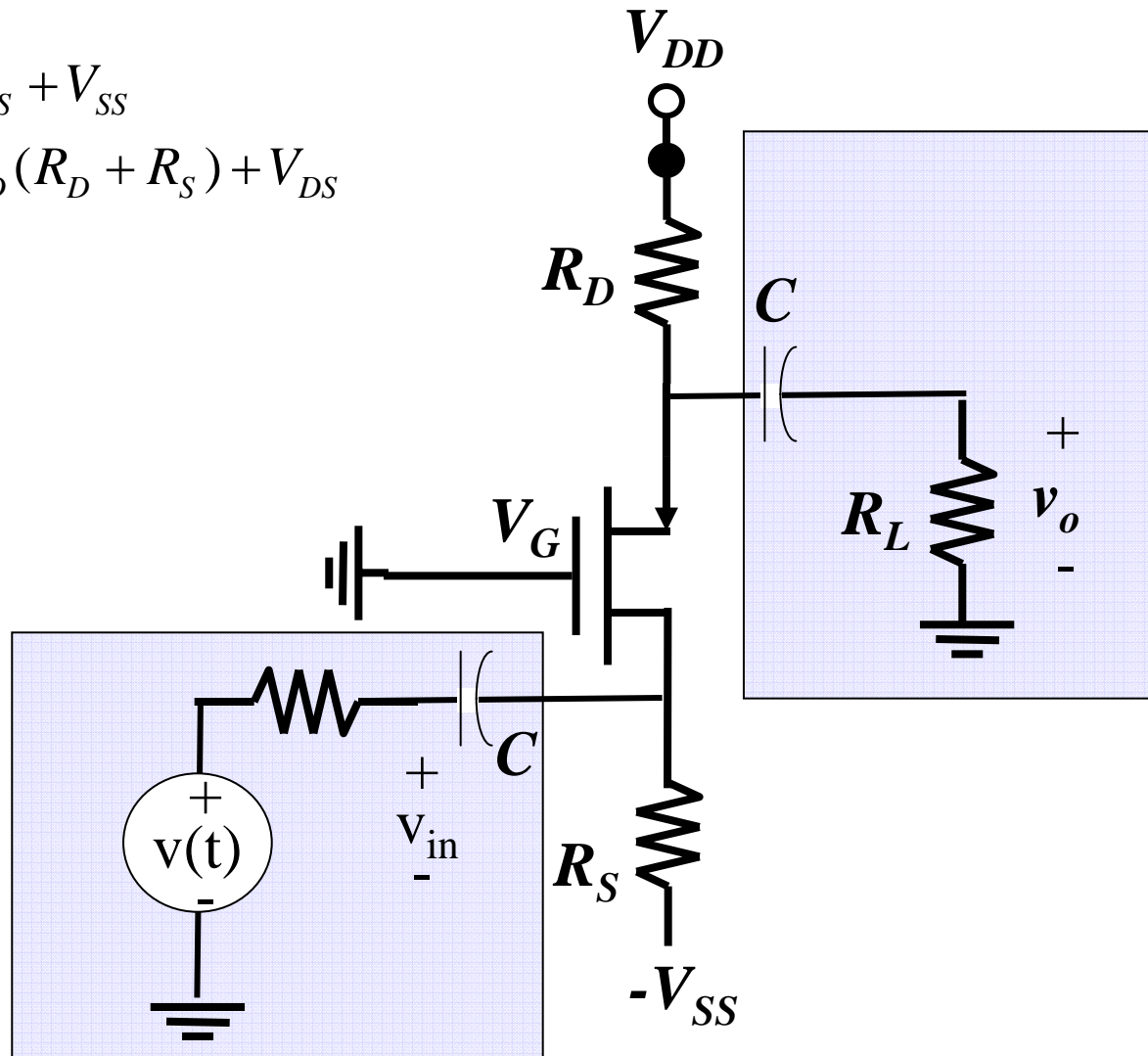
## Step 1: find Q point

$$V_{GS} = 0 - I_D R_S + V_{SS}$$

$$V_{DD} + V_{SS} = I_D (R_D + R_S) + V_{DS}$$




## Load line

---

The only difference in all three circuits are the intercepts at the axes.

Again from load lines, we get  $I_D \rightarrow$  and hence  $g_m$  and  $r_d$

# Small Signal Model

 

$$R_L' = \frac{1}{R_L^{-1} + R_D^{-1}}$$

$$v_{gs} = -v_{in}$$

$$v_o = -g_m v_{gs} R_L'$$

$$A_v = \frac{v_o}{v_{in}} = g_m R_L'$$

$$i_{in} = -\left(g_m v_{gs} + \frac{v_{gs}}{R_s}\right)$$

$$R_{in} = \frac{v_{in}}{i_{in}} = \frac{1}{g_m + R_s^{-1}}$$

For output impedance  $R_{out}$ :

1. Turn off all independent sources.
2. Take away  $R_L$
3. Add  $V_x$  and find  $i_x$

$$R' = \frac{R R_s}{R + R_s}$$

$$i_x = \frac{v_x}{R_D} + g_m v_{gs}$$

$$v_{gs} = -g_m v_{gs} R', \text{ but } g_m R' \neq 1 \therefore v_{gs} = 0$$

$$R_{out} = R_D$$

# MOSFET Digital Circuits – Introduction

---

- Analog: signal amplitude is continuous with time.
- Digital: signal amplitude is represented by a restricted set of discrete numbers.
  - Binary: only two values are allowed to represent the signal: High or low (i.e. logic 1 or 0).
- Digital word:
  - Each binary digit is called a bit
  - A series of bits form a word
    - Byte is a word consisting of 8-bits
- Advantages of digital signal
  - Digital signal is more resilient to noise → can more easily differentiate high (1) and low (0)
- Transmission
  - Parallel transmission over a bus containing  $n$  wires.
    - Faster but short distance (internal to a computer or chip)
  - Serial transmission (transmit bits sequentially)
    - Longer distance

# Analog vs. Digital Signals

---

- **Most** (but not all) **observables are analog**

*think of analog vs. digital watches*

**but the most convenient way to represent & transmit information electronically is to use digital signals**

*think of telephony*


→ Analog-to-digital (A/D) & digital-to-analog (D/A) conversion is essential (and nothing new)

*think of a piano keyboard*

# Analog Signal Example: Microphone Voltage

Voltage with normal piano key stroke


50 microvolt 440 Hz signal

 

t in milliseconds


Voltage with soft pedal applied

25 microvolt 440 Hz signal

 

t in milliseconds

50 microvolt 220 Hz signal

 

t in milliseconds

← Analog signal representing piano key A, below middle C (220 Hz)

# Digital Signal Representations

---

**Binary numbers can be used to represent any quantity.**

We generally have to agree on some sort of “code”, and the dynamic range of the signal in order to know the form and the number of binary digits (“bits”) required.

**Example 1:** Voltage signal with maximum value 2 Volts

- Binary two (**10**) could represent a 2 Volt signal.
- To encode the signal to an accuracy of 1 part in 64 (1.5% precision), 6 binary digits (“bits”) are needed

**Example 2:** Sine wave signal of known frequency and maximum amplitude  $50 \mu\text{V}$ ;  $1 \mu\text{V}$  “resolution” needed.

# Decimal Numbers: Base 10

---

Digits: 0, 1, 2, 3, 4, 5, 6, 7, 8, 9

Example:

$$3271 = (3 \times 10^3) + (2 \times 10^2) + (7 \times 10^1) + (1 \times 10^0)$$

This is a four-digit number. The left hand most number (3 in this example) is often referred as the most significant number and the right most the least significant number (1 in this example).



# Numbers: positional notation

---

- Number Base  $B \Rightarrow B$  symbols per digit:
  - Base 10 (Decimal): 0, 1, 2, 3, 4, 5, 6, 7, 8, 9
  - Base 2 (Binary): 0, 1
- Number representation:
  - $d_{31}d_{30} \dots d_1d_0$  is a 32 digit number
  - value =  $d_{31} \times B^{31} + d_{30} \times B^{30} + \dots + d_1 \times B^1 + d_0 \times B^0$
- Binary: 0,1 (In binary digits called “bits”)
  - $11010 = 1 \times 2^4 + 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 0 \times 2^0$
  - $= 16 + 8 + 2$
  - $= 26$
  - Here 5 digit binary # turns into a 2 digit decimal #

# Hexadecimal Numbers: Base 16

---

- Hexadecimal:  
0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F  
– Normal digits + 6 more from the alphabet
- Conversion: Binary  $\Leftrightarrow$  Hex
  - 1 hex digit represents 16 decimal values
  - 4 binary digits represent 16 decimal values
  - $\Rightarrow$  1 hex digit replaces 4 binary digits

# Digital Signal Representations

---

**Binary numbers can be used to represent any quantity.**

We generally have to agree on some sort of “code”, and the dynamic range of the signal in order to know the form and the number of binary digits (“bits”) required.

**Example 1:** Voltage signal with maximum value 2 V and minimum of 0 V.

- Binary two (**10**) could represent a 2 Volt signal.
- To encode the signal to an accuracy of 1 part in 64 (1.5% precision), 6 binary digits (“bits”) are needed

**Example 2:** Sine wave signal of known frequency and maximum amplitude 50  $\mu\text{V}$ ; 1  $\mu\text{V}$  “resolution” needed.

# Resolution

---

- The size of the smallest element that can be separated from neighboring elements. The term is used to describe imaging systems, the frequency separation achieved by spectrometers, and so on.

# Decimal-Binary Conversion

---

- Decimal to Binary
  - Repeated Division By 2
    - Consider the number 2671.
  - Subtraction – if you know your  $2^N$  values by heart.

- Binary to Decimal conversion

$$\begin{aligned}110001_2 &= 1 \times 2^5 + 1 \times 2^4 + 0 \times 2^3 + 0 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 \\ &= 32_{10} + 16_{10} + 1_{10} \\ &= 49_{10} \\ &= 4 \times 10^1 + 9 \times 10^0\end{aligned}$$

## Example 2 (continued)

---

Possible digital representation for the sine wave signal:

Analog representation: Amplitude in $\mu\text{V}$	Digital representation: Binary number
1	000001
2	000010
3	000011
4	000100
5	000101
8	001000
16	010000
32	100000
<b>50</b>	<b>110010</b>
63	111111

# Binary Representation

---

- N bit can represent  $2^N$  values: typically from 0 to  $2^N-1$ 
  - 3-bit word can represent 8 values: e.g. 0, 1, 2, 3, 4, 5, 6, 7
- Conversion
  - Integer to binary
  - Fraction to binary ( $13.5_{10}=1101.1_2$  and  $0.392_{10}=0.011001_2$ )
- Octal and hexadecimal

- 
- Logic gates
    - Combine several logic variable inputs to produce a logic variable output
  - Memory
    - Memoryless: output at a given instant depends the input values of that instant.
    - Momory: output depends on previous and present input values.



# Boolean algebras

---

- Algebraic structures
  - "capture the essence" of the logical operations AND, OR and NOT
  - corresponding set for theoretic operations intersection, union and complement
  - named after George Boole, an English mathematician at University College Cork, who first defined them as part of a system of logic in the mid 19th century.
  - Boolean algebra was an attempt to use algebraic techniques to deal with expressions in the propositional calculus.
  - Today, Boolean algebras find many applications in electronic design. They were first applied to switching by Claude Shannon in the 20th century.

## Boolean algebras

---

- The operators of Boolean algebra may be represented in various ways. Often they are simply written as AND, OR and NOT.
- In describing circuits, NAND (NOT AND), NOR (NOT OR) and XOR (eXclusive OR) may also be used.
- Mathematicians often use  $+$  for OR and  $\cdot$  for AND (since in some ways those operations are analogous to addition and multiplication in other algebraic structures) and represent NOT by a line drawn above the expression being negated.

# Boolean Algebra

---

- NOT operation (inverter)

$$A \cdot \bar{A} = 0$$

- AND operation

$$A + \bar{A} = 1$$

$$A \cdot A = A$$

$$A \cdot 1 = A$$

$$A \cdot 0 = 0$$

$$A \cdot B = B \cdot A$$

- OR operation

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

$$A + A = A$$

$$A + 1 = 1$$


$$A + 0 = A$$

$$A + B = B + A$$

$$(A + B) + C = A + (B + C)$$

# Graphic Representation

---

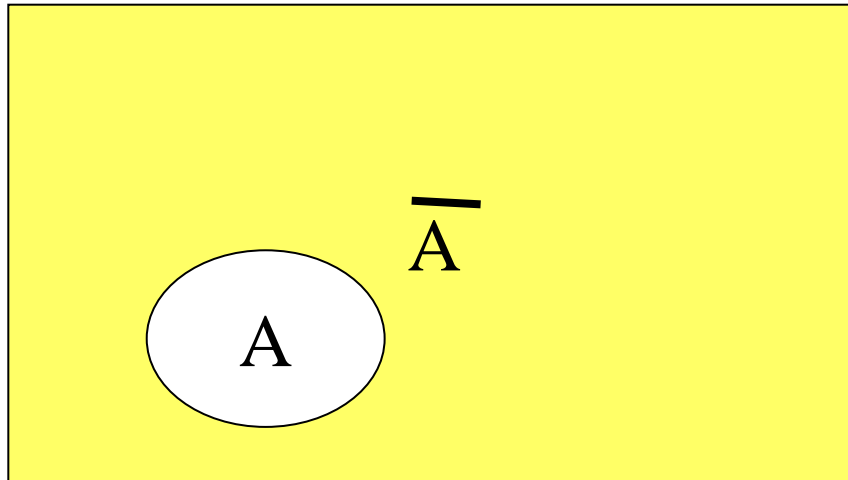

$$A \cdot \bar{A} = 0$$

$$A + \bar{A} = 1$$


Full square = complete set = 1

Yellow part = NOT(A) =  $\bar{A}$

White circle = A

# Graphic Representation

---

 

$$A \oplus B = A\bar{B} + \bar{A}B = (A + B) \cdot (\bar{A} + \bar{B}) = \overline{A \cdot B} + \overline{\overline{A + B}}$$

Exclusive OR = yellow and blue part –  
intersection/overlap part

= exactly when only one of the input is true

# Boolean Algebra

---

- Distributive Property

$$A \cdot (B + C) = A \cdot B + A \cdot C$$

$$(A + B) \cdot C = (A + B) \cdot (A + C)$$

- De Morgan's laws

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

- An excellent web site to visit
  - [http://en.wikipedia.org/wiki/Boolean\\_algebra](http://en.wikipedia.org/wiki/Boolean_algebra)




## Examples

---

$$F = A \cdot \bar{B} \cdot C + A \cdot B \cdot C + (C+D) \cdot (\bar{D}+E)$$

$$F = C \cdot (A + \bar{D} + E) + D \cdot E$$

# Logic Functions, Symbols, & Notation

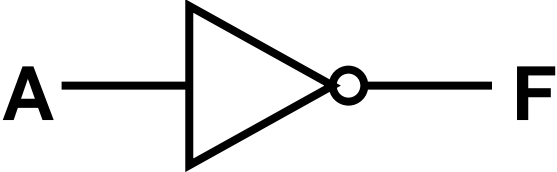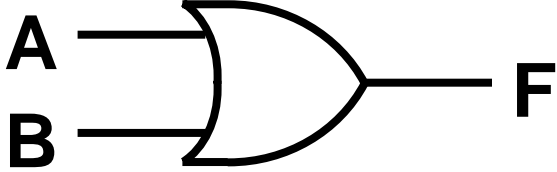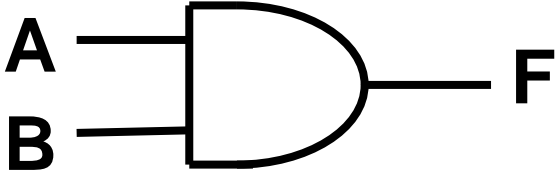
<u>NAME</u>	<u>SYMBOL</u>	<u>NOTATION</u>	<u>TRUTH TABLE</u>															
"NOT"		$F = \bar{A}$	<table border="1"><thead><tr><th>A</th><th>F</th></tr></thead><tbody><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></tbody></table>	A	F	0	1	1	0									
A	F																	
0	1																	
1	0																	
"OR"		$F = A+B$	<table border="1"><thead><tr><th>A</th><th>B</th><th>F</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></tbody></table>	A	B	F	0	0	0	0	1	1	1	0	1	1	1	1
A	B	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
"AND"		$F = A \cdot B$	<table border="1"><thead><tr><th>A</th><th>B</th><th>F</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></tbody></table>	A	B	F	0	0	0	0	1	0	1	0	0	1	1	1
A	B	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																



## Logic Functions, Symbols, & Notation 2

---


**“NOR”**

 

$$F = \overline{A+B}$$

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0


**“NAND”**

 

$$F = \overline{A \cdot B}$$

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

**“XOR”**  
(exclusive OR)

 


$$F = A \oplus B$$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0



 
## Circuit Realization

---

$$A \oplus B = A\bar{B} + \bar{A}B = (A + B) \cdot (\bar{A} + \bar{B}) = \overline{A \cdot B + \bar{A} + \bar{B}}$$




# Logic Functions, Symbols, & Notation
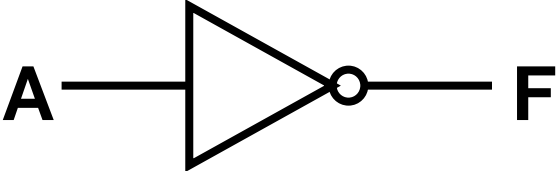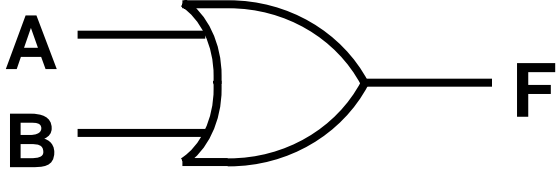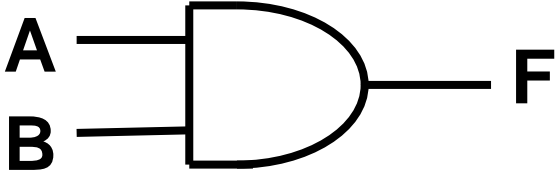
<u>NAME</u>	<u>SYMBOL</u>	<u>NOTATION</u>	<u>TRUTH TABLE</u>															
"NOT"		$F = \bar{A}$	<table border="1"> <thead> <tr> <th>A</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	F	0	1	1	0									
A	F																	
0	1																	
1	0																	
"OR"		$F = A+B$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	A	B	F	0	0	0	0	1	1	1	0	1	1	1	1
A	B	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
"AND"		$F = A \cdot B$	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>F</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	A	B	F	0	0	0	0	1	0	1	0	0	1	1	1
A	B	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																

## Logic Functions, Symbols, & Notation 2

---


**“NOR”**

 

$$F = \overline{A+B}$$

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0


**“NAND”**

 

$$F = \overline{A \cdot B}$$

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

**“XOR”**  
(exclusive OR)

 

$$F = A \oplus B$$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0


## Fan in/Fan out

---


- Complex digital operations are formed with a variety of gates interconnected to yield the desired logic function.
- Sometimes a number of inputs are connected to one gate input and output of a gate may be connected to a number of gates.
- Fan-in: the maximum number of logic gates that can be connected at the input of a gate **without altering its performance**.
- Fan-out: the maximum number of logic gates that can be connected to the output of a gate **without altering its performance**.
- Typical fan-in and fan-out numbers are 3.

# Inverter = NOT Gate


---

 


Ideal Transfer Characteristics

 

# Terminology for a Logic Circuit

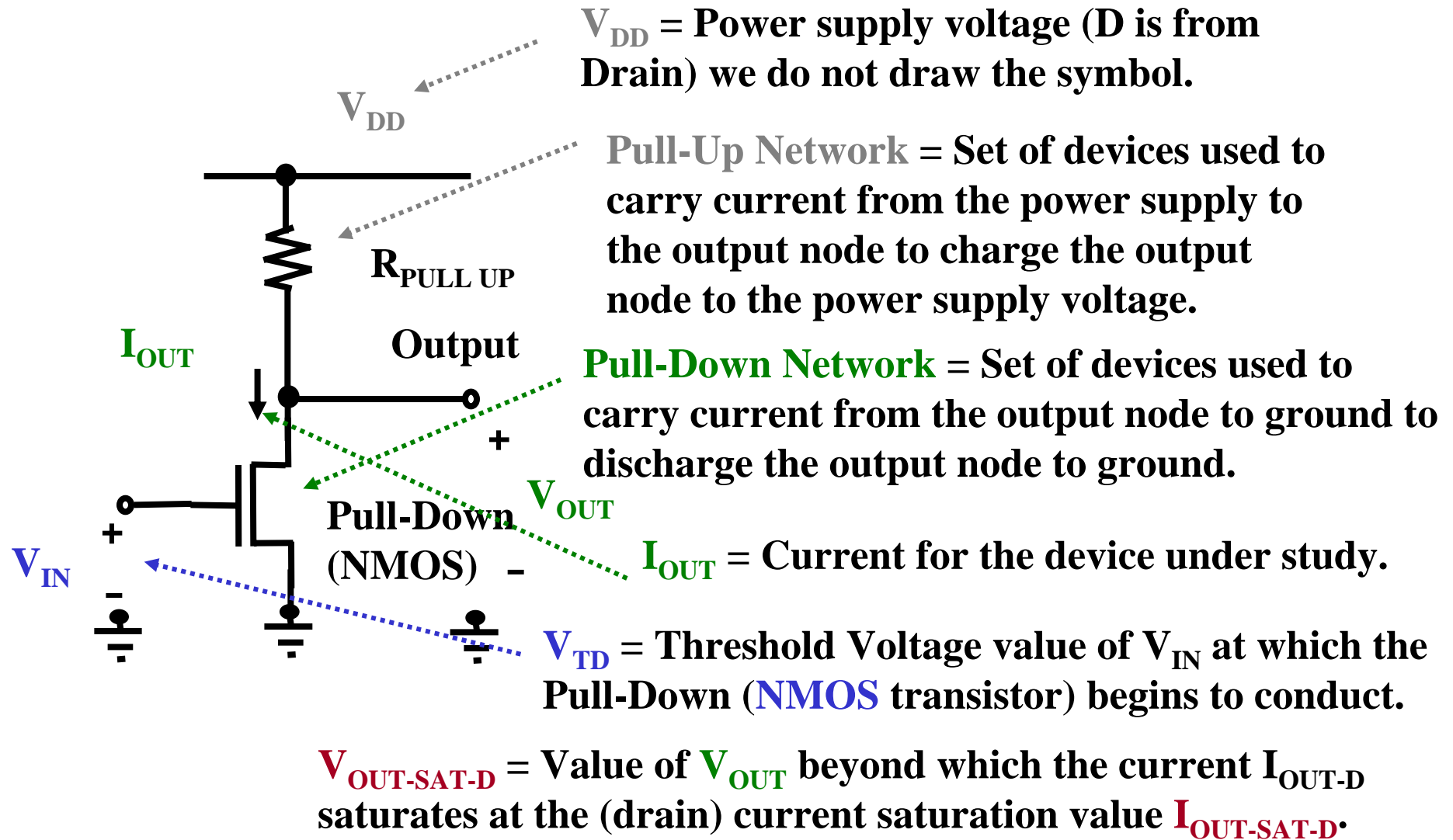

# Thevenin Model For Pull-Up Device

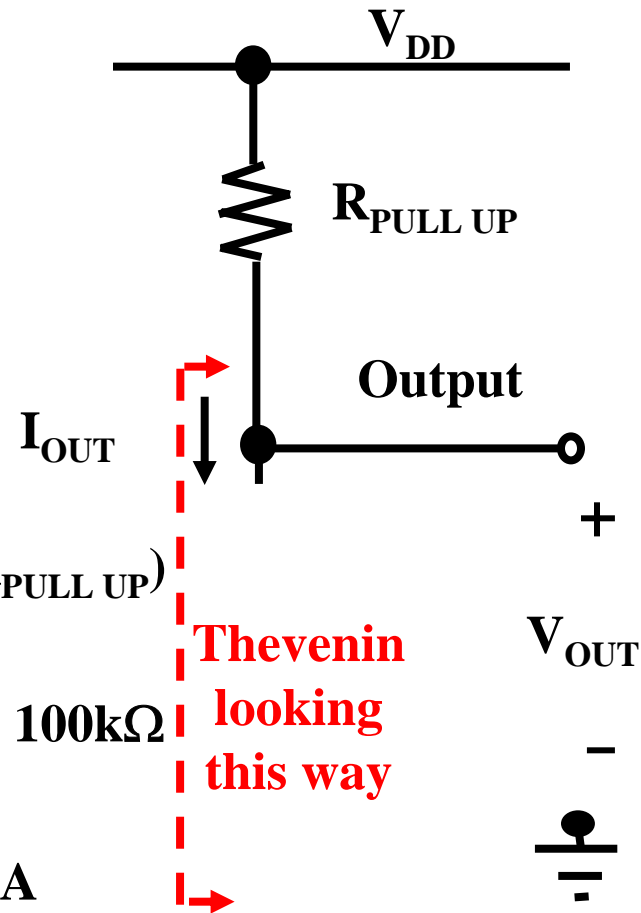

$$V_{THEVENIN} = V_{DD}$$

$$I_{OUT\ SHORT\ CIRCUIT} = (V_{DD}/R_{PULL\ UP})$$

**Example:**

$$V_{DD} = 5V \text{ and } R_{PULL\ UP} = 100k\Omega$$


$$V_{THEVENIN} = 5V$$

$$I_{OUT\ SHORT\ CIRCUIT} = 50\ \mu A$$



 
# Load Line For Pull-Up Device

$I_{OUT}$  vs.  $V_{OUT}$   
For the Pull-Up Resistor and  $V_{DD}$




# NMOS Resistor Pull-Up

Circuit:

 

Voltage-Transfer Characteristic

 


# Disadvantages of NMOS Logic Gates

---

- Large values of  $R_D$  are required in order to
  - achieve a low value of  $V_{OL}$
  - keep power consumption low
- Large resistors are needed, but these take up a lot of space.
  - One solution is to replace the resistor with an NMOSFET that is always on.


# The CMOS Inverter: Intuitive Perspective

## CIRCUIT

 

Low static power consumption, since one MOSFET is always off in steady state


## SWITCH MODELS

 

$$V_{IN} = V_{DD}$$

$$V_{IN} = 0\text{ V}$$


 
# CMOS Inverter Voltage Transfer Characteristic



# CMOS Inverter Load-Line Analysis



$$V_{IN} = V_{DD} + V_{GSp}$$

$$V_{OUT} = V_{DD} + V_{DSp}$$

  



# CMOS Inverter Load-Line Analysis: Region A

$$V_{IN} \leq V_{Tn}$$

  

# CMOS Inverter Load-Line Analysis: Region B



$$V_{DD}/2 > V_{IN} > V_{Tn}$$

  




# CMOS Inverter Load-Line Analysis: Region D

$$V_{DD} - |V_{Tp}| > V_{IN} > V_{DD}/2$$

  

# CMOS Inverter Load-Line Analysis: Region E

$$V_{IN} > V_{DD} - |V_{Tp}|$$

 


# Features of CMOS Digital Circuits



---

- The output is always connected to  $V_{DD}$  or **GND** in steady state
  - Full logic swing; **large noise margins**
  - Logic levels are not dependent upon the relative sizes of the devices (“**ratioless**”)
- There is no direct path between  $V_{DD}$  and **GND** in steady state
  - **no static power dissipation**
 
# The CMOS Inverter: Current Flow during Switching


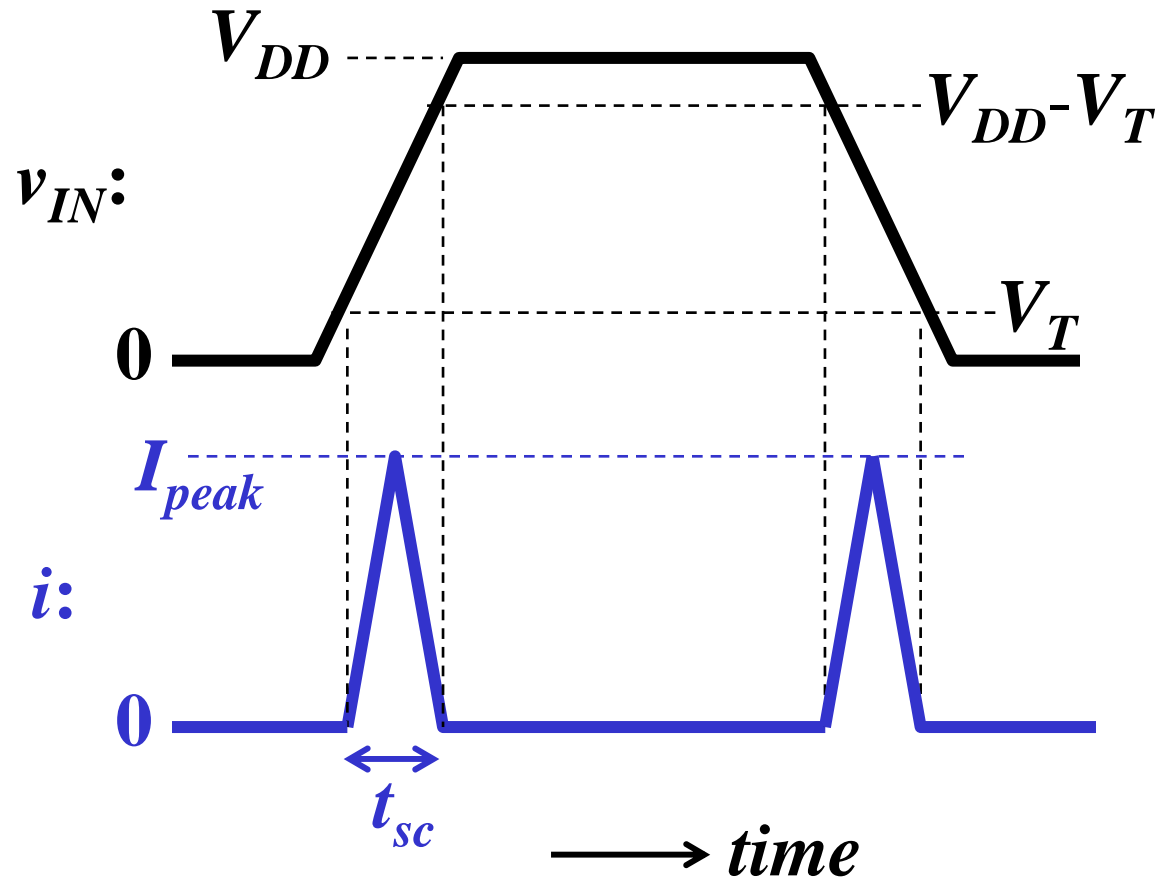 
# Power Dissipation due to Direct-Path Current




Energy consumed per switching period:  $E_{dp} = t_{sc} V_{DD} I_{peak}$
 
# NMOS NAND Gate

---

- Output is low only if both inputs are high




Truth Table

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

# NMOS NOR Gate

- Output is low if either input is high

 


Truth Table


A	B	F
0	0	1
0	1	0
1	0	0
1	1	0
 
# N-Channel MOSFET Operation

An NMOSFET is a closed switch when the input is high



$Y = X$  if A and B

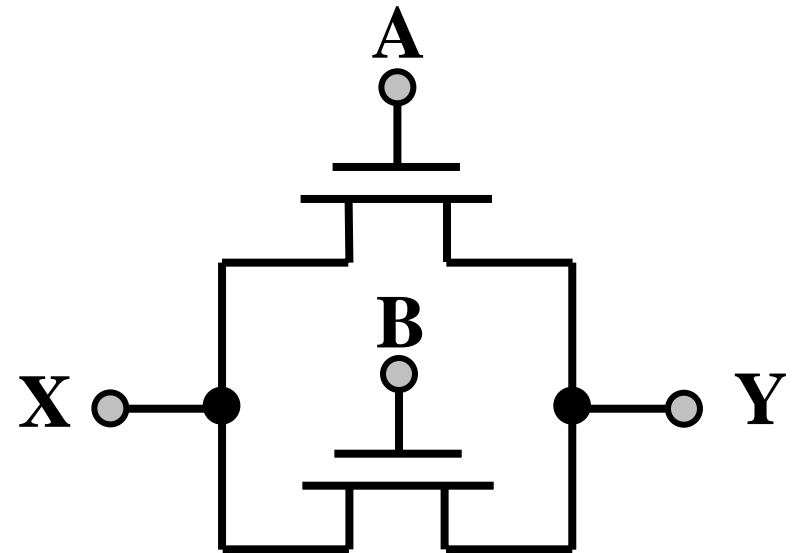


$Y = X$  if A or B

NMOSFETs pass a “strong” 0 but a “weak” 1



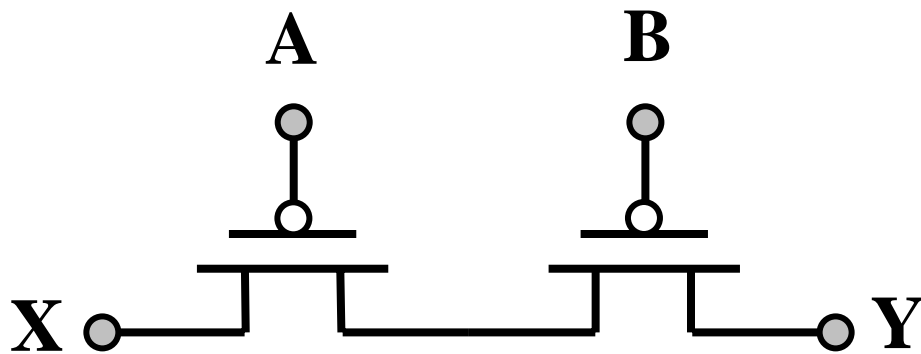
# P-Channel MOSFET Operation

A PMOSFET is a closed switch when the input is low


 
$$Y = X \text{ if } \bar{A} \text{ and } \bar{B} \\ = (\overline{A + B})$$




$$Y = X \text{ if } \bar{A} \text{ or } \bar{B} \\ = (\overline{A\bar{B}})$$

PMOSFETs pass a “strong” 1 but a “weak” 0

 
# Pull-Down and Pull-Up Devices

- In CMOS logic gates, **NMOSFETs** are used to connect the output to **GND**, whereas **PMOSFETs** are used to connect the output to  $V_{DD}$ .
  - An NMOSFET functions as a **pull-down device** when it is turned on (gate voltage =  $V_{DD}$ )
  - A PMOSFET functions as a **pull-up device** when it is turned on (gate voltage = **GND**)




# CMOS NAND Gate

---

 

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0


# CMOS NOR Gate

 

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

# CMOS Pass Gate

---

 

$$Y = X \text{ if } A$$