


EE100 Su08 Lecture #2 (June 25th 2008)

- For today:
 - Bart: slight change in office hours:
 - Check website
 - Student accounts
 - Handed out in class. If you are in EE100, pick up account from TA in lab. If you are in EE42, pick up account forms in my office hours.
 - Remote access
 - Reading for this week and next: Chapters 1, 2, 3 (except 3.7) and 4
 - Questions and/or comments on previous material?
 - **New material: wrap up chapters 1 and 2**
 - MultiSim demo


Sign Convention for Power

Passive sign convention

$$p = vi$$

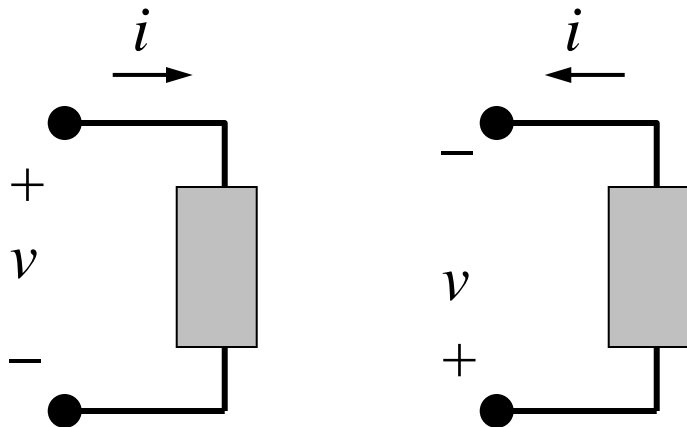

$$p = -vi$$

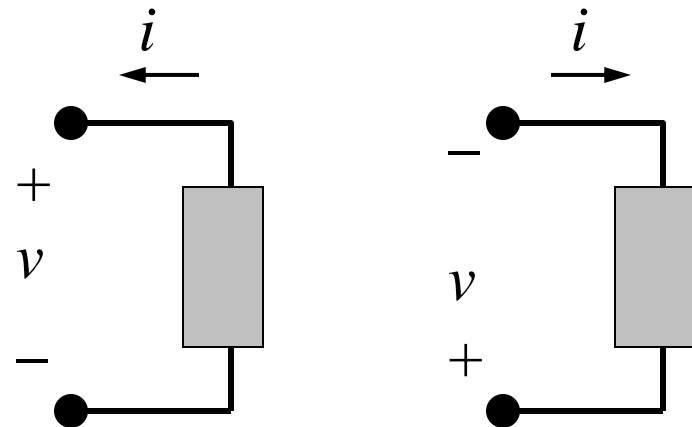


- If $p > 0$, power is being delivered to the box.
- If $p < 0$, power is being extracted from the box.

Power

If an element is absorbing power (*i.e.* if $p > 0$), positive charge is flowing from higher potential to lower potential.

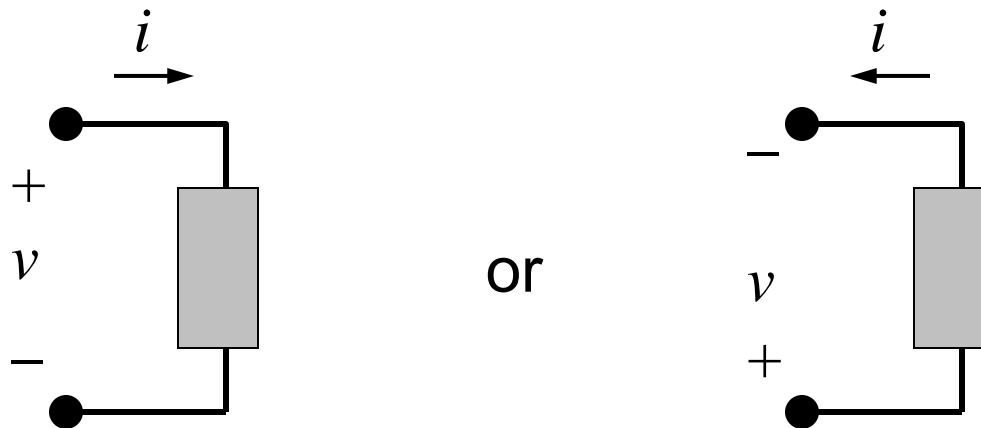$p = vi$ if the “passive sign convention” is used:




How can a circuit element absorb power?

By converting electrical energy into heat (resistors in toasters), light (light bulbs), or acoustic energy (speakers); by storing energy (charging a battery).

Power Calculation Example

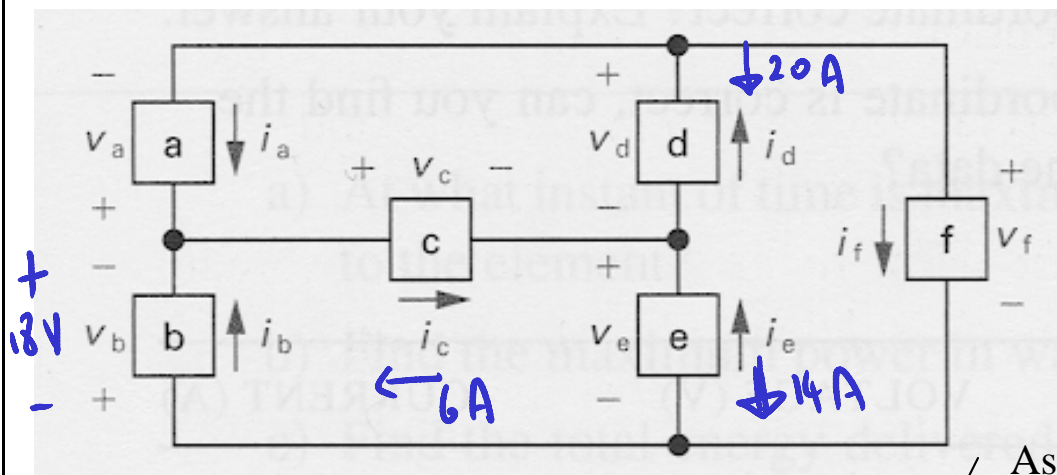Find the power **absorbed** by each element:




Conservation of energy
 → total power delivered
 equals
 total power absorbed

Aside: For electronics these are unrealistically large currents – milliamperes or smaller is more typical

ELEMENT	VOLTAGE (V)	CURRENT (A)
a	-18	-51
b	-18	45
c	2	-6
d	20	-20
e	16	-14
f	36	31

<u>v_i (W)</u>	<u>p (W)</u>
918	-918 W
-810	-810 W
-12	-12 W
-400	400 W
-224	224 W
1116	1116 W
	0 W??

Power calculations

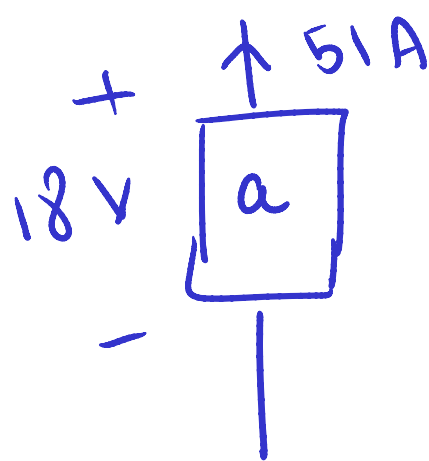

$$\begin{aligned} P &= -vi \\ &= -(18)(51) \\ &= \underline{\underline{-918 \text{ W}}} \end{aligned}$$

power associated with device "a"

∴ Power absorbed by device "a" is -918 W

Circuit Elements

- 5 ideal basic circuit elements:
 - voltage source
 - current source

} **active elements**, capable of generating electric energy

 - resistor
 - inductor
 - capacitor

} **passive elements**, incapable of generating electric energy
- Many practical systems can be modeled with just sources and resistors
- The basic analytical techniques for solving circuits with inductors and capacitors are similar to those for resistive circuits

Electrical Sources

- An ***electrical source*** is a device that is capable of converting non-electric energy to electric energy and *vice versa*.

Examples:


- battery: chemical \longleftrightarrow electric
- dynamo (generator/motor): mechanical \longleftrightarrow electric
(Ex. gasoline-powered generator, Bonneville dam)

→ Electrical sources can either deliver or absorb power


Ideal Voltage Source

- Circuit element that maintains a prescribed voltage across its terminals, **regardless of the current flowing in those terminals.**
 - Voltage is known, but current is determined by the circuit to which the source is connected.
- The voltage can be either **independent** or **dependent** on a voltage or current elsewhere in the circuit, and can be constant or time-varying.


Device symbols:

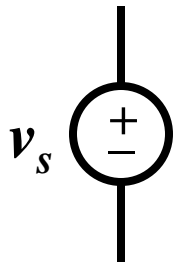

independent

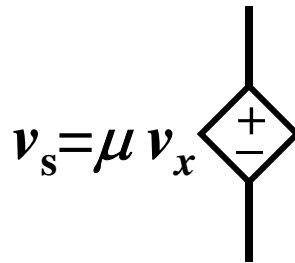

voltage-controlled

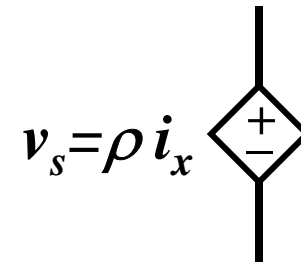


current-controlled


Ideal Current Source

- Circuit element that maintains a prescribed current through its terminals, **regardless of the voltage across those terminals.**
 - Current is known, but voltage is determined by the circuit to which the source is connected.
- The current can be either **independent or dependent** on a voltage or current elsewhere in the circuit, and can be constant or time-varying.


Device symbols:

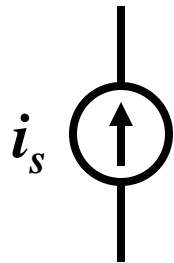

independent

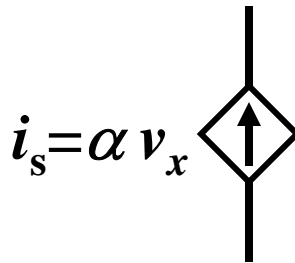

voltage-controlled

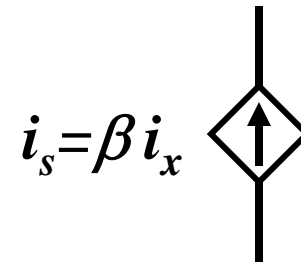

current-controlled

Electrical Resistance

- **Resistance:** the ratio of voltage drop and current. The circuit element used to model this behavior is the **resistor**.


Circuit symbol:



Units: Volts per Ampere \equiv ohms (Ω)

- The current flowing in the resistor is proportional to the voltage across the resistor:

$$v = i R \quad (\text{Ohm's Law})$$

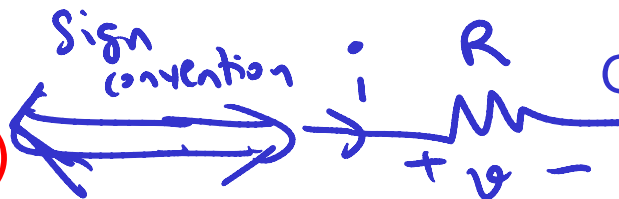

Georg Simon Ohm
1789-1854



where v = voltage (V), i = current (A), and R = resistance (Ω)

Note: $p = vi = i^2 R = v^2 / R$

Electrical Conductance

- **Conductance** is the reciprocal of resistance.


Symbol: G

Units: siemens (S) or mhos (\mathcal{U})

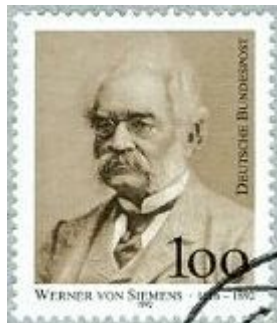Example:

$$\rightarrow \mathcal{U} = \frac{1}{8}$$

Consider an 8Ω resistor. *What is its conductance?*




Werner von Siemens
1816-1892



Short Circuit and Open Circuit


- Short circuit

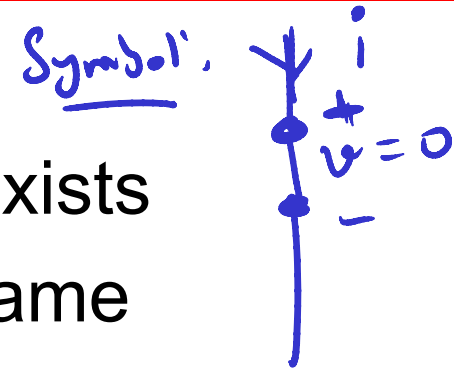- $R = 0 \rightarrow$ no voltage difference exists
- all points on the wire are at the same potential.
- Current can flow, as determined by the circuit




- Open circuit

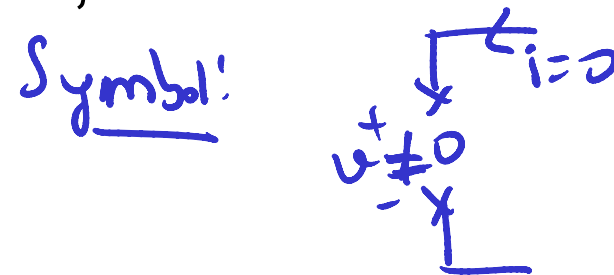- $R = \infty \rightarrow$ no current flows
- Voltage difference can exist, as determined by the circuit



(Q.) Why are short-circuits "bad"?

Ex.

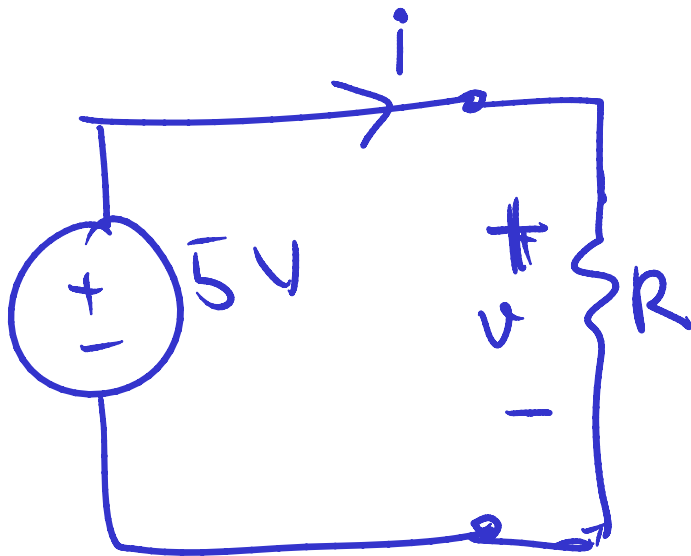

$$i = \frac{v}{R} = \frac{5}{R} \quad (\text{KVL})$$

or
Kirchoff's
Voltage
law

As $R \rightarrow 0$, $i \rightarrow \infty$

oops, battery
doesn't like it

Example: Power Absorbed by a Resistor


$$p = vi = (iR)i = i^2R$$

$$p = vi = v(v/R) = v^2/R$$


Note that $p > 0$ always, for a resistor \rightarrow a resistor dissipates electric energy

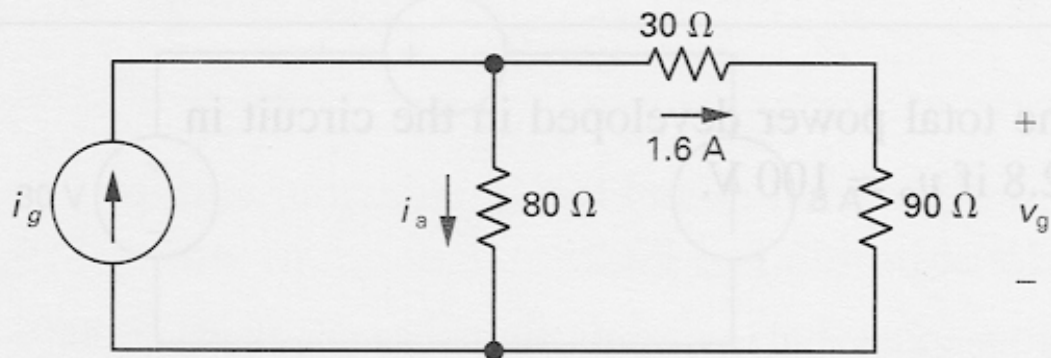Example:

- Calculate the voltage v_g and current i_a .
- Determine the power dissipated in the 80Ω resistor.




Example solution

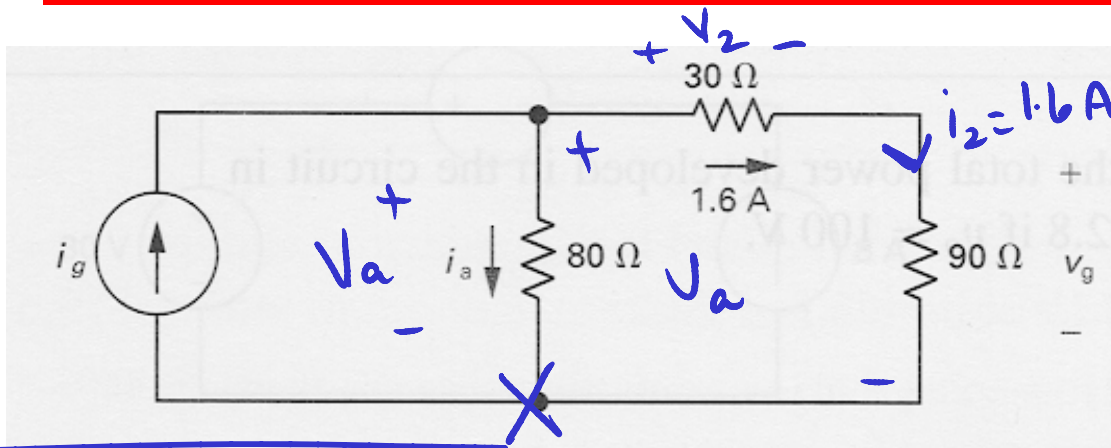

KCL: $i_2 = 1.6 \text{ A}$

$\therefore v_g = i_2 \cdot 90$ (Ohm's law)
 $= \underline{\underline{144 \text{ V}}}$

Note:

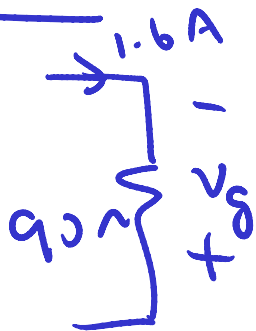

$v_g = - (1.6)(90)$

$i_a = \frac{v_a}{80}$ (Ohm's law)

KVL: $v_a = v_2 + v_g$ $\left[\begin{array}{l} +v_a - v_2 - v_g = 0 \\ -v_a + v_2 + v_g = 0 \end{array} \right]$

$= (1.6)(30) + 144 = \underline{\underline{192 \text{ V}}}$

$\therefore i_a = \frac{192}{80} = \underline{\underline{2.4 \text{ A}}}$. $P = v_a i_a = (192)(2.4) \text{ W}$

Summary


- **Current** = rate of charge flow $i = dq/dt$
- **Voltage** = energy per unit charge created by charge separation
- **Power** = energy per unit time
- **Ideal Basic Circuit Elements**
 - two-terminal component that cannot be sub-divided
 - described mathematically in terms of its terminal voltage and current
 - An **ideal voltage source** maintains a prescribed voltage regardless of the current in the device.
 - An **ideal current source** maintains a prescribed current regardless of the voltage across the device.
 - A **resistor** constrains its voltage and current to be proportional to each other: $v = iR$ (Ohm's law)

Summary (cont'd)

- ***Passive sign convention***
 - For a passive device, the reference direction for current through the element is in the direction of the reference voltage drop across the element



Current vs. Voltage (I - V) Characteristic

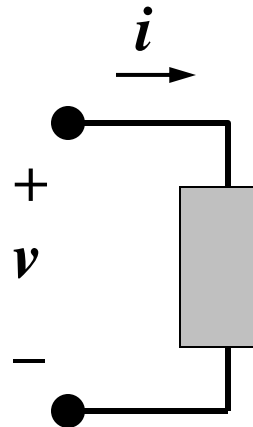- Voltage sources, current sources, and resistors can be described by plotting the current (i) as a function of the voltage (v)



Passive? Active?

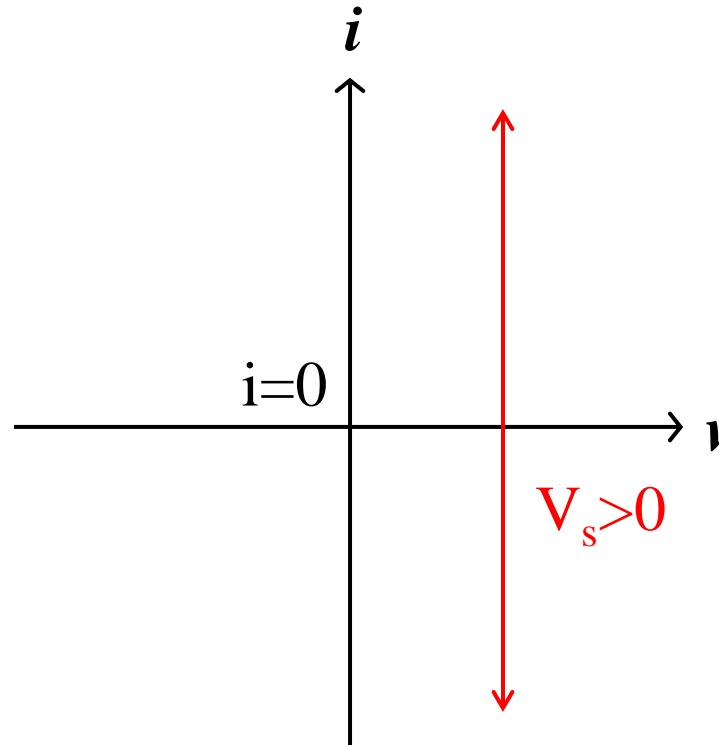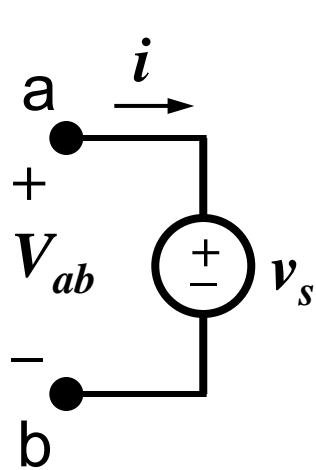
I-V Characteristic of Ideal Voltage Source



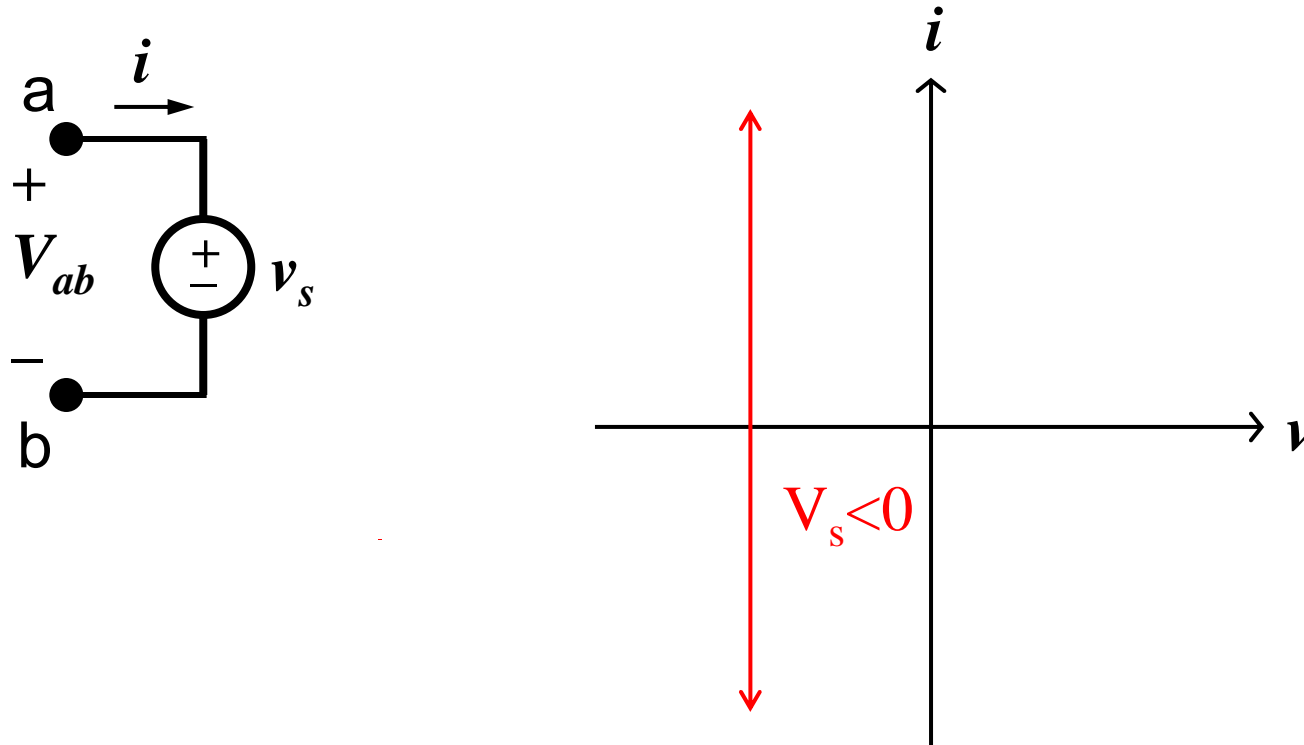1. Plot the I - V characteristic for $v_s > 0$. For what values of i does the source absorb power? For what values of i does the source release power?

$V_s > 0 \rightarrow i < 0$ release power; $i > 0$ absorb power


I-V Characteristic of Ideal Voltage Source



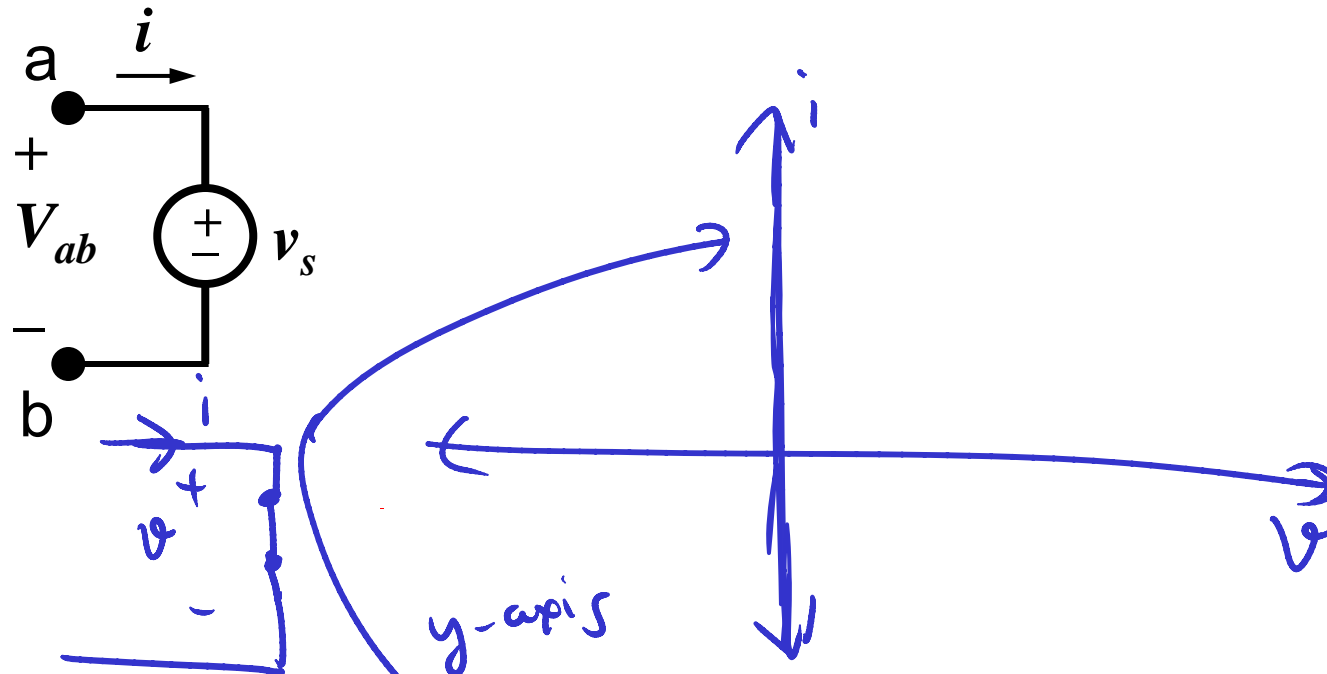2. Plot the I - V characteristic for $v_s < 0$. For what values of i does the source absorb power? For what values of i does the source release power?



$V_s < 0 \rightarrow i > 0$ release power; $i < 0$ absorb power

I-V Characteristic of Ideal Voltage Source



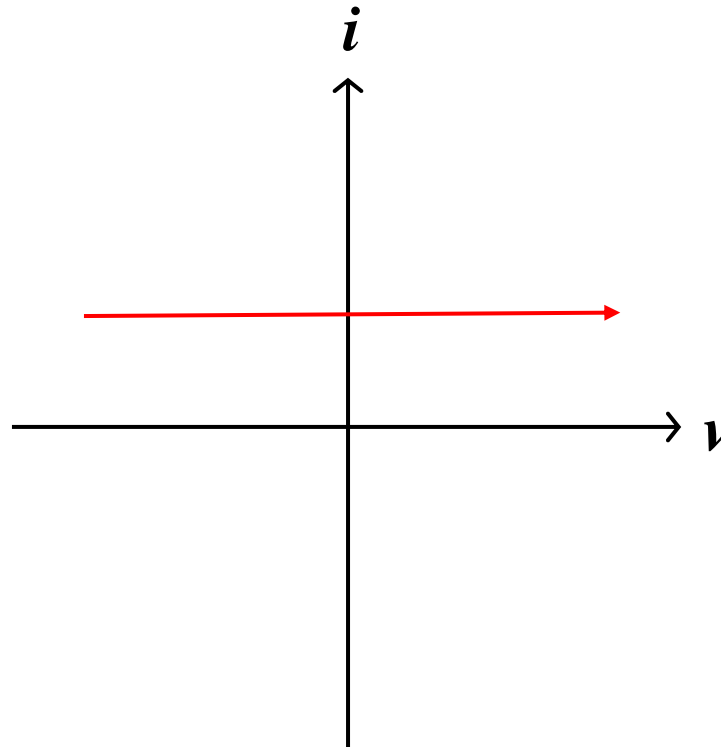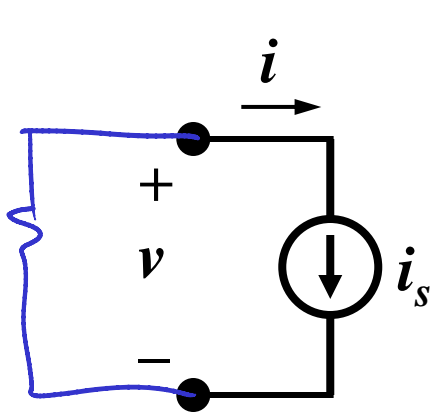3. What is the I-V characteristic for an ideal wire?

I - V Characteristic of Ideal Current Source



1. Plot the I - V characteristic for $i_s > 0$. For what values of v does the source absorb power? For what values of v does the source release power?

$V > 0$ absorb power; $V < 0$ release power


Short Circuit and Open Circuit

Wire (“short circuit”):


- $R = 0 \rightarrow$ no voltage difference exists
(all points on the wire are at the same potential)
- Current can flow, as determined by the circuit

Air (“open circuit”):


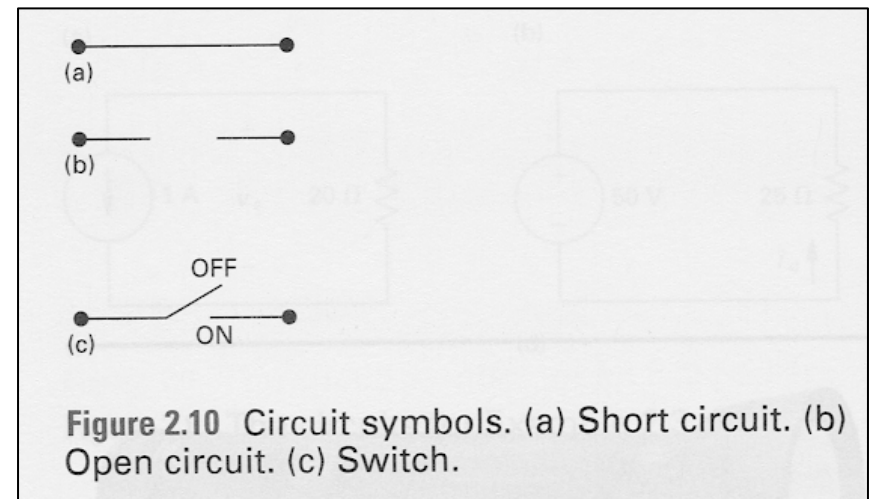
- $R \rightarrow \infty \rightarrow$ no current flows
- Voltage difference can exist,
as determined by the circuit



I-V Characteristic of Ideal Resistor

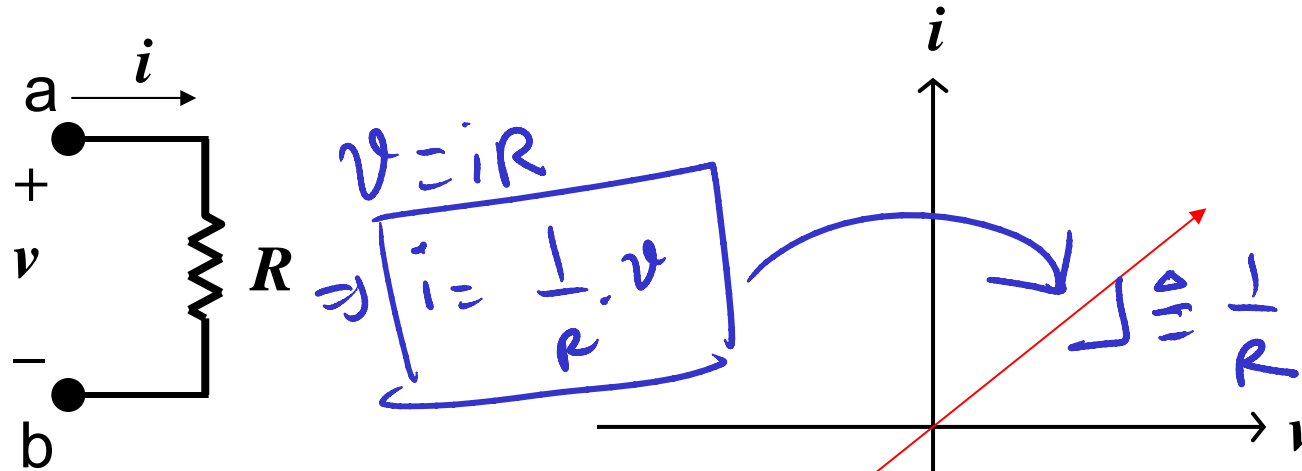

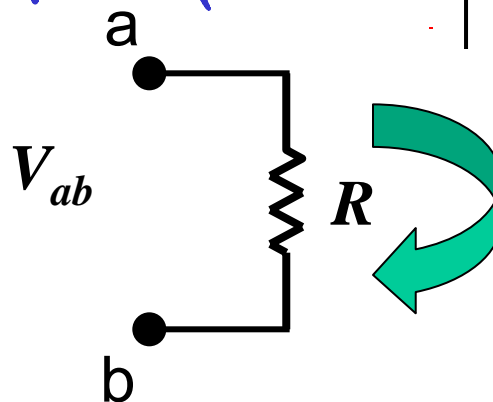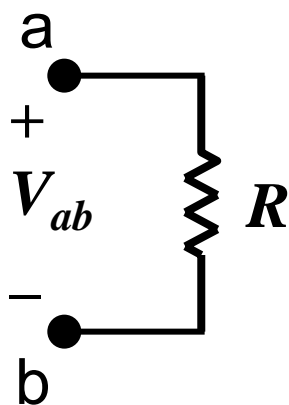1. Plot the I-V characteristic for $R = 1 \text{ k}\Omega$. What is the slope? slope $\cong \frac{1}{R} = \frac{1}{1000}$




Construction of a Circuit Model



- The electrical behavior of each physical component is of primary interest.
- We need to account for undesired as well as desired electrical effects.
- Simplifying assumptions should be made wherever reasonable.

Terminology: Nodes and Branches

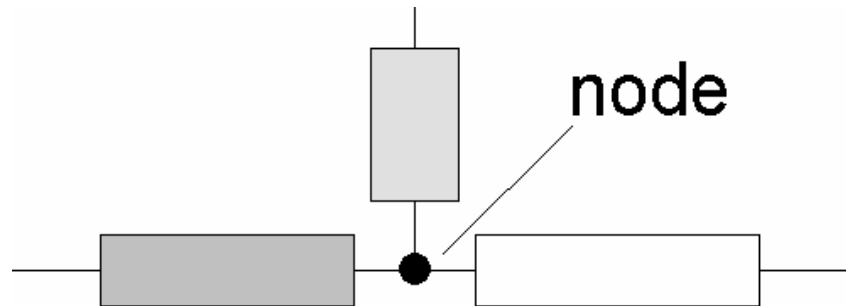Node: A point where two or more circuit elements are connected




Branch: A path that connects two nodes

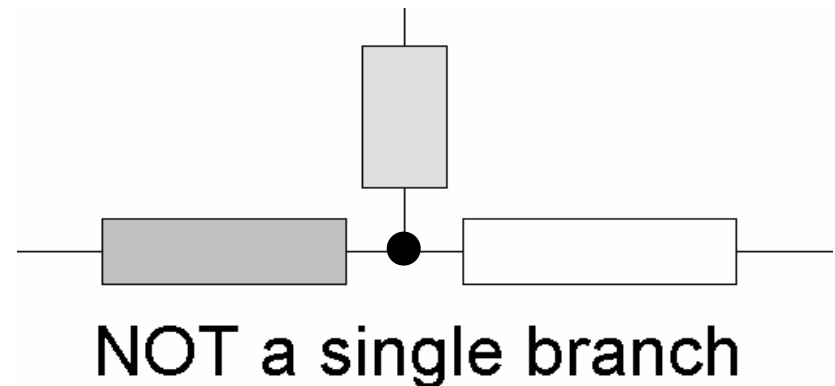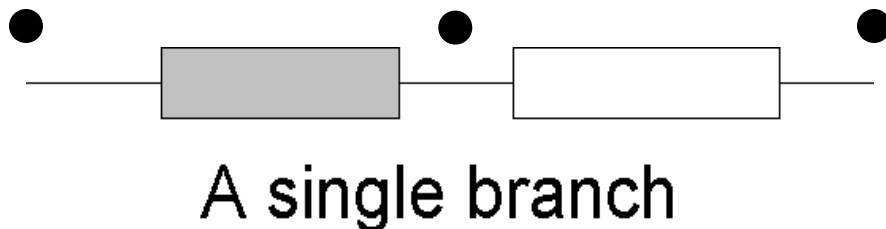

Circuit Nodes and Loops

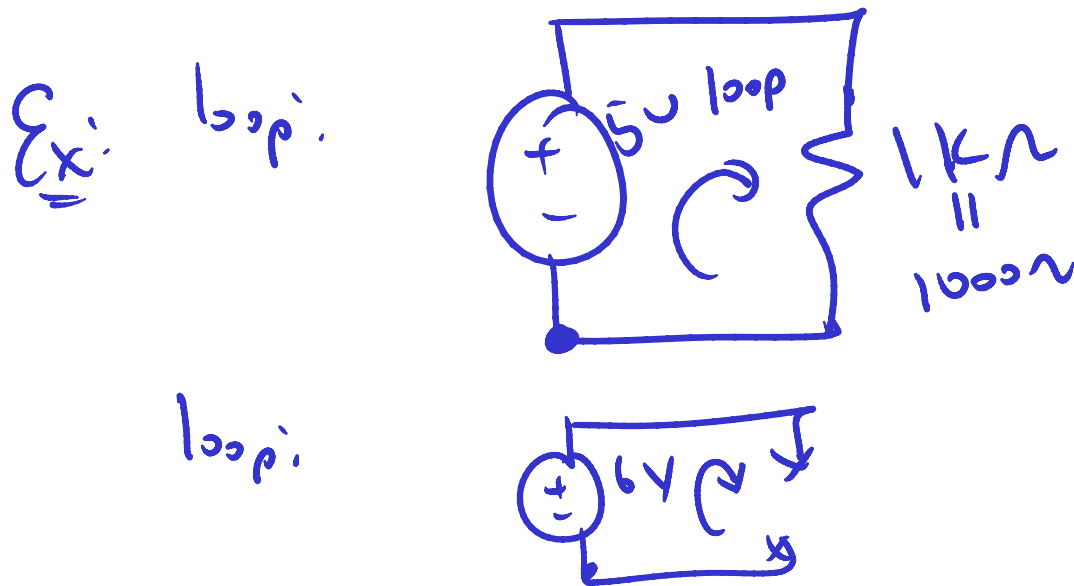- A **node** is a point where two or more circuit elements are connected.
- A **loop** is formed by tracing a ~~closed~~ path in a circuit through selected basic circuit elements without passing through any intermediate node more than once.





Kirchhoff's Laws

- Kirchhoff's Current Law (KCL):

- The algebraic sum of all the **currents** entering any **node** in a circuit equals zero.

- Kirchhoff's Voltage Law (KVL):

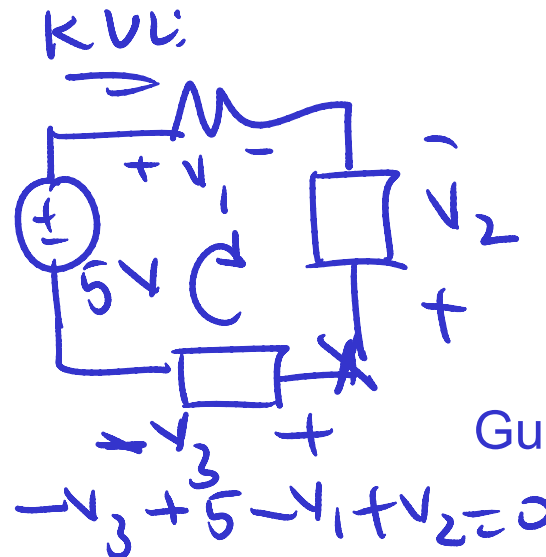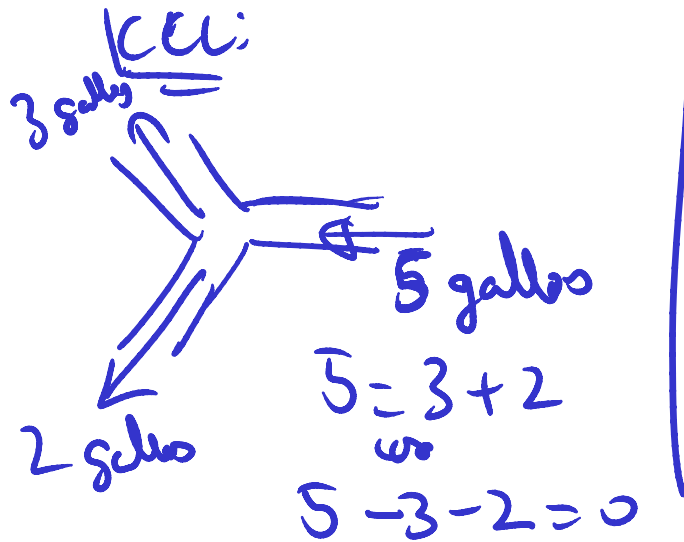- The algebraic sum of all the **voltages** around any **loop** in a circuit equals zero.




Gustav Robert Kirchhoff
1824-1887


Notation: Node and Branch Voltages

- Use one node as the reference (the “common” or “ground” node) – label it with a symbol
- The voltage drop from node x to the reference node is called the **node voltage** v_x .
- The voltage across a circuit element is defined as the difference between the node voltages at its terminals

Example:

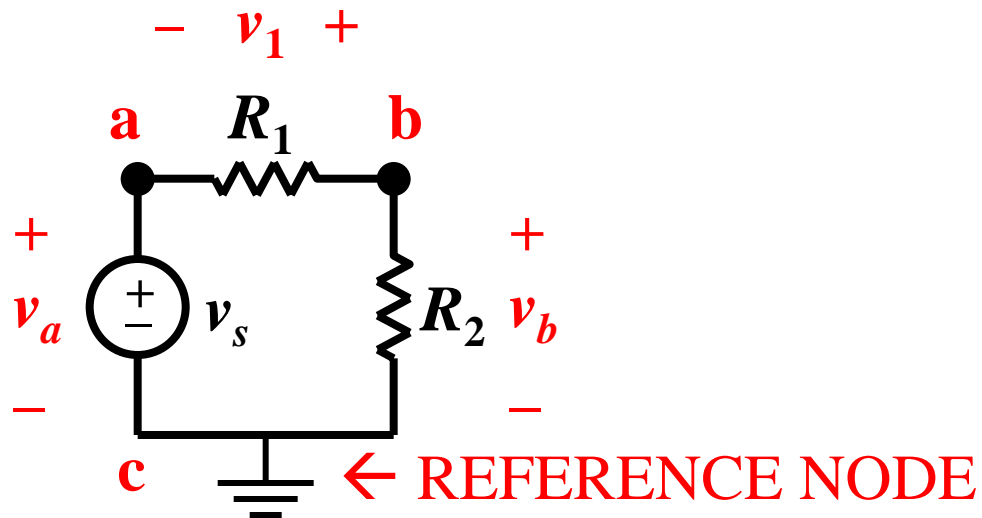

Concrete example

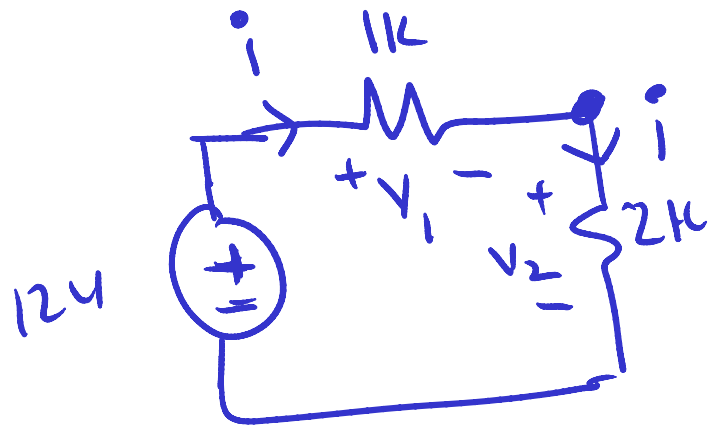

Ohm's law:

$$V_1 = (i)(1k)$$
$$V_2 = (i)(2k)$$

KVL:

$$12 = V_1 + V_2$$

$$= (i)(1k) + (i)(2k)$$

$$\therefore V_1 = (1k)(i) = 4V$$


$$V_2 = (2k)(i) = 8V$$

$$\Rightarrow 12 = (i)(3k)$$


$$\Rightarrow i = \frac{12}{3k} = 4 \times 10^{-3} A$$
$$= \underline{\underline{4mA}}$$

Concept of reference node

Support:

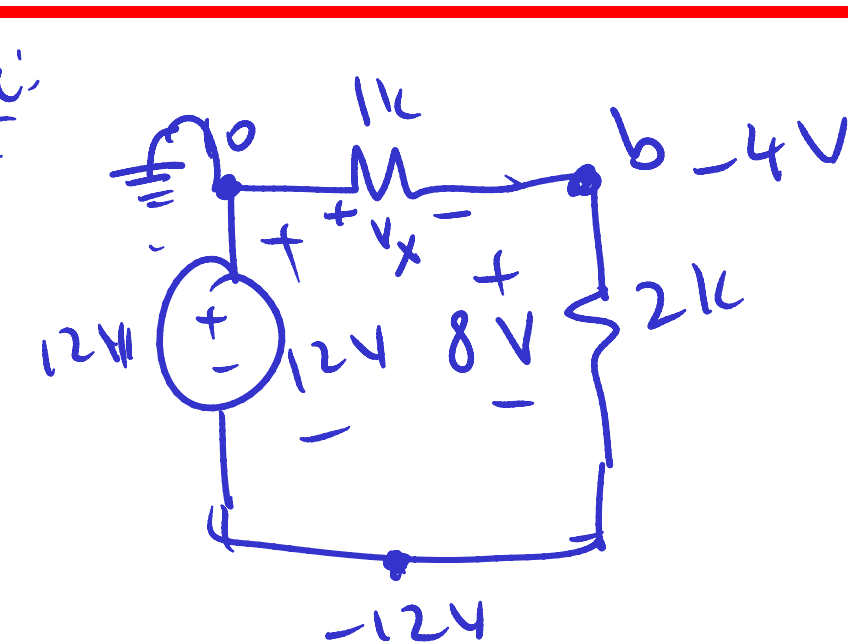

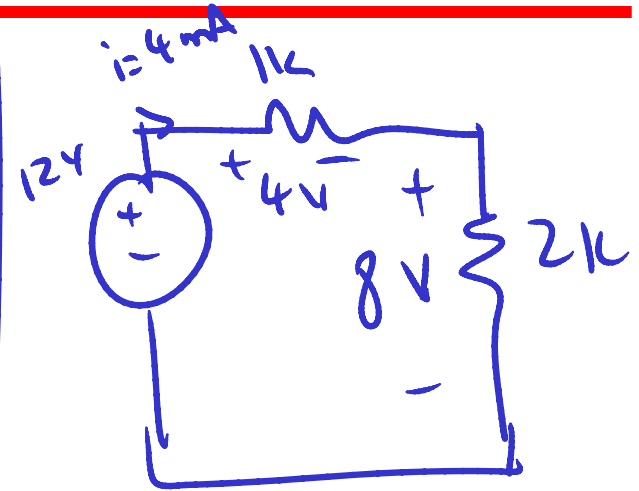
$$V_x = 0 - (-4) = \underline{\underline{4V}}$$



Notice: potential drops (voltage) across elements is same!

Using Kirchhoff's Current Law (KCL)

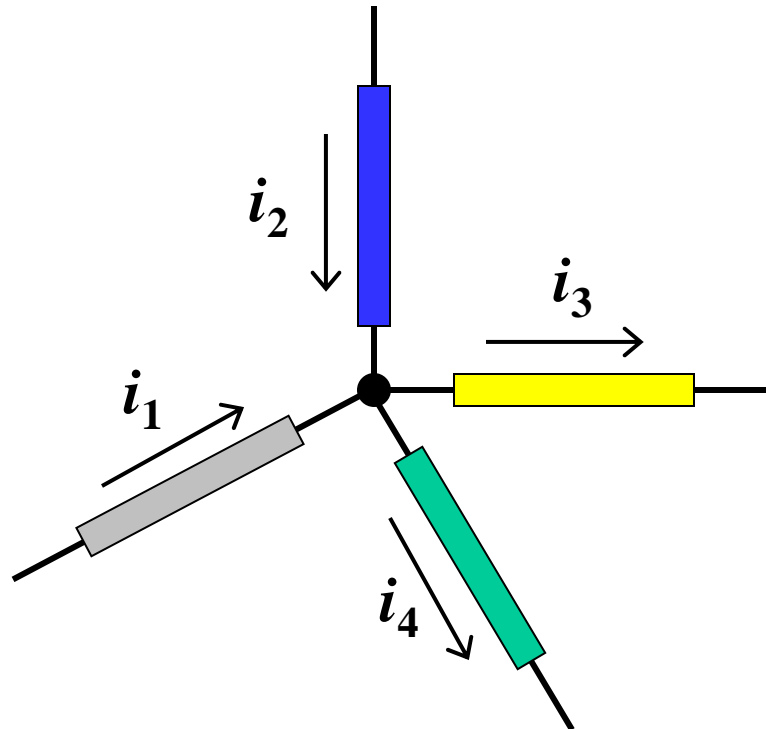
Consider a node connecting several branches:



- Use **reference directions** to determine whether currents are “entering” or “leaving” the node – **with no concern about actual current directions**

Formulations of Kirchhoff's Current Law

(Charge stored in node is zero.)

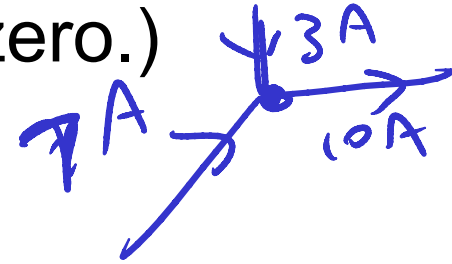

Formulation 1:

Sum of currents entering node
= sum of currents leaving node

$$7 + 3 = 10$$

Formulation 2:

Algebraic sum of currents entering node = 0

- Currents leaving are included with a minus sign.

$$7 + 3 - 10 = 0$$

Formulation 3:


Algebraic sum of currents leaving node = 0

- Currents entering are included with a minus sign.

$$10 - 7 - 3 = 0$$

A Major Implication of KCL

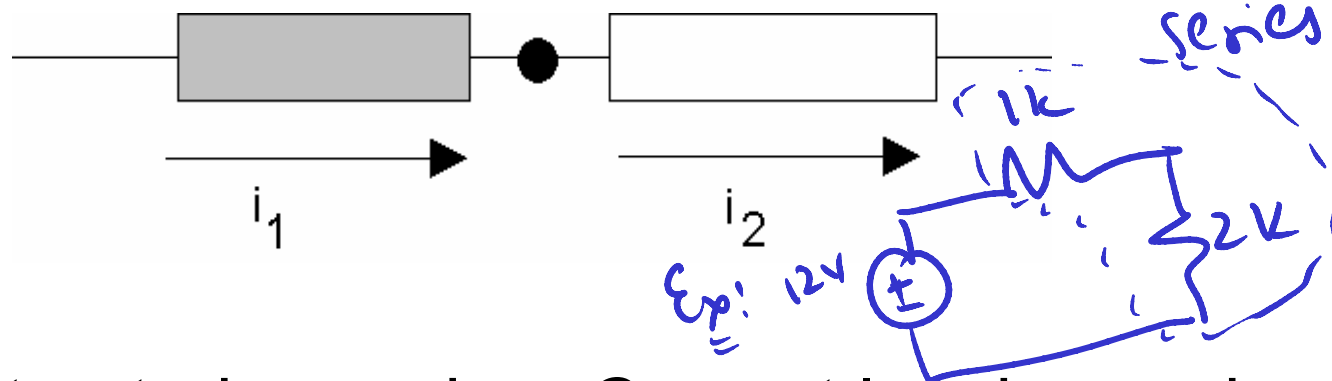
- KCL tells us that **all of the elements in a single branch carry the same current.**
- We say these elements are connected ***in series***.



Current entering node = Current leaving node

$$i_1 = i_2$$

KCL Example

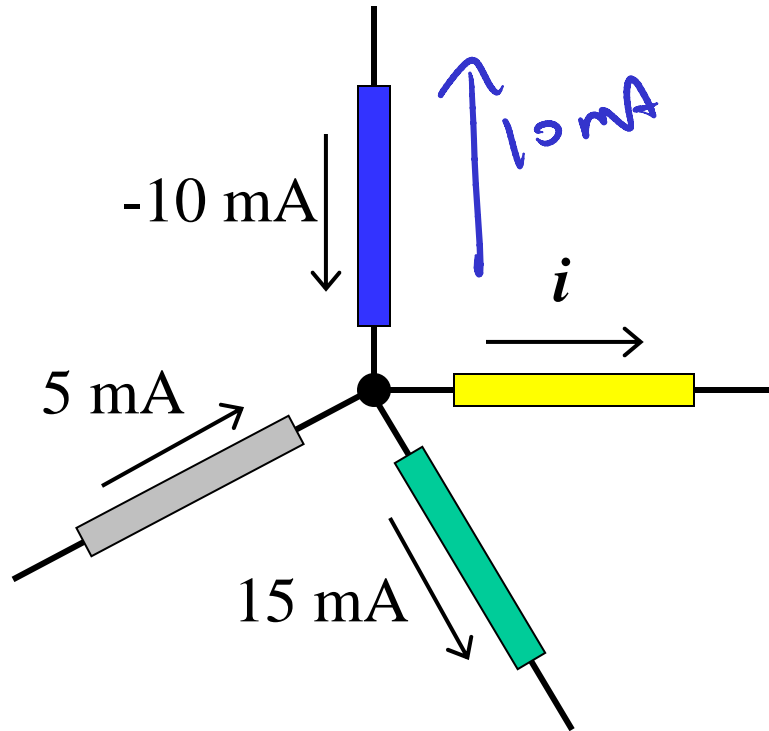

Currents entering the node:

5 mA

Currents leaving the node:

$i, 10 \text{ mA}, 15 \text{ mA}$

3 formulations of KCL:

- 1.
- 2.
- 3.

Do this yourself 😊