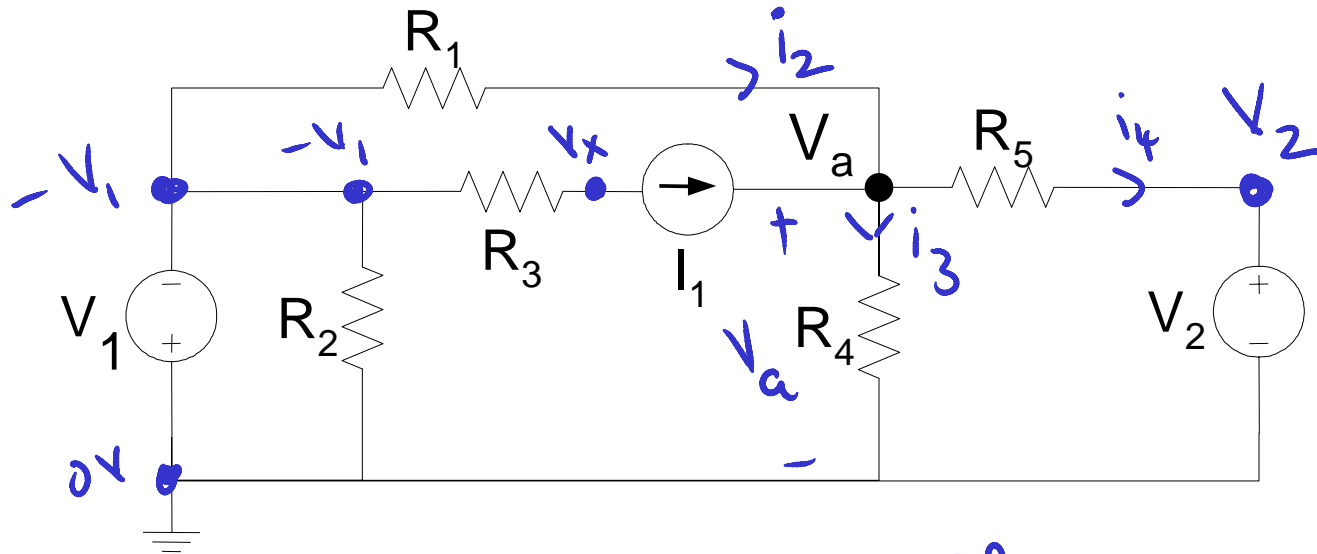


# EE100Su08 Lecture #5 (July 2<sup>nd</sup> 2008)

---

- Outline
  - Questions?
  - Lab notes:
    - Labs 2 and 3 have been shortened
    - Monday lab: go to your **SECOND** lab section next week.
  - Node-Voltage Analysis: wrap up
  - Mesh analysis: read it, **OPTIONAL**
  - Superposition
  - Thevenin's Theorem

## Nodal Analysis: Example #2



### Challenges:


- Determine number of nodes needed
- Deal with different types of sources

If you are systematic,  
not challenging 😊.

$$\textcircled{V_a}: \quad \bar{I}_1 + i_2 = i_3 + i_4 \Rightarrow \bar{I}_1 + \frac{-V_1 - V_a}{R_1} = \frac{V_a}{R_4} + \frac{V_a - V_2}{R_5}$$
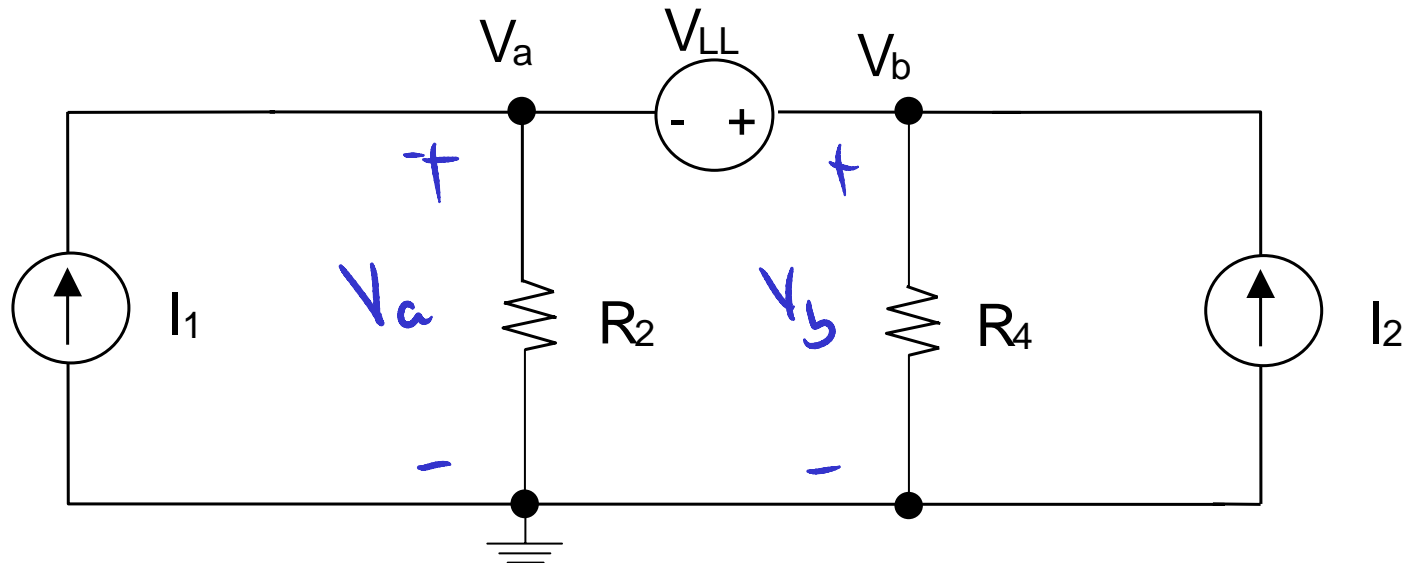
# Nodal Analysis w/ “Floating Voltage Source”


A “floating” voltage source is one for which neither side is connected to the reference node, e.g.  $V_{LL}$  in the circuit below:



Problem: We cannot write KCL at nodes a or b because there is no way to express the current through the voltage source in terms of  $V_a$ - $V_b$ .

Solution: Define a “supernode” – that chunk of the circuit containing nodes a and b. Express KCL for this supernode. Incorporate voltage source constraint into KCL equation.

# Nodal Analysis: Example #3

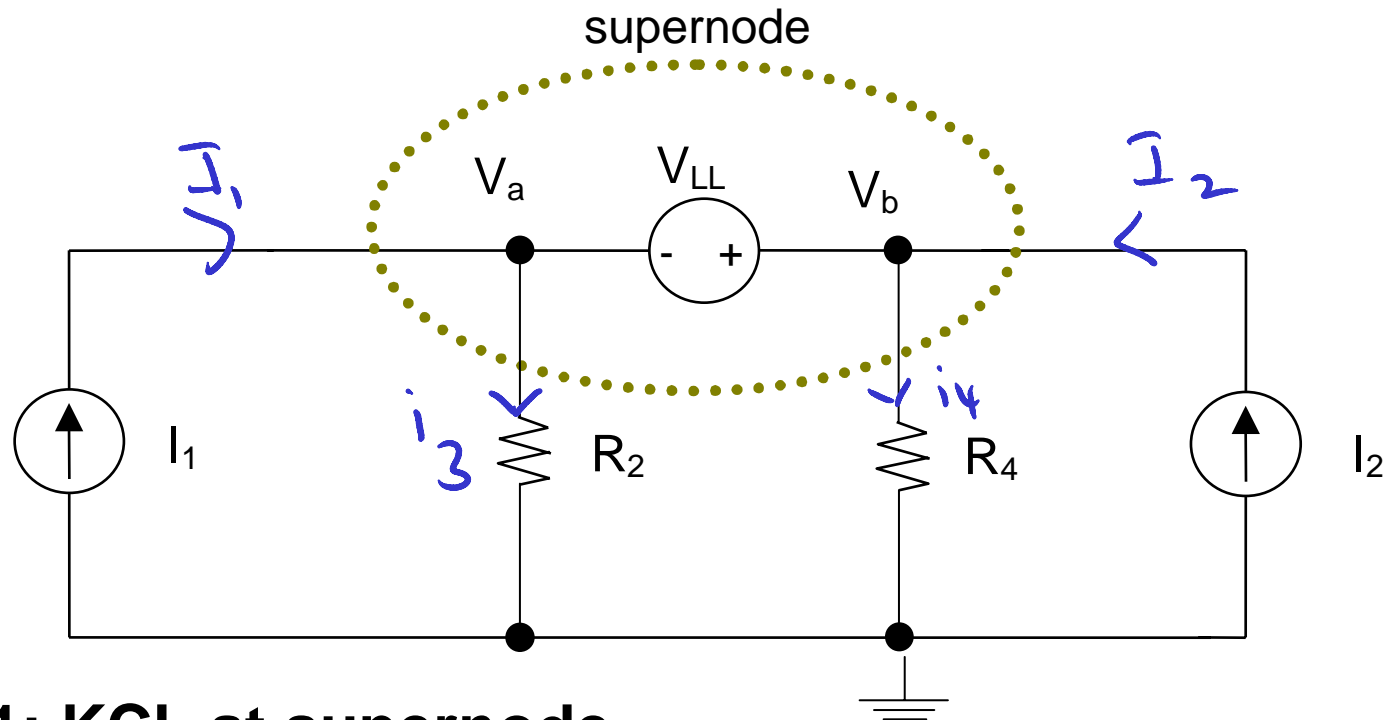

**Eq'n 1: KCL at supernode**

$$I_1 + I_2 = i_3 + i_4 \Rightarrow I_1 + I_2 = \frac{V_a}{R_2} + \frac{V_b}{R_4}$$

**Substitute property of voltage source:**

$$V_b - V_a = V_{LL}$$

# Superposition

---

A ***linear circuit*** is one constructed only of linear elements (linear resistors, and linear capacitors and inductors, linear dependent sources) and independent sources. Linear means I-V characteristic of elements/sources are straight lines when plotted

## Principle of Superposition:

- In any linear circuit containing multiple independent sources, the current or voltage at any point in the network may be calculated as the algebraic sum of the individual contributions of each source acting alone.

# Superposition

---

## Procedure:

1. Determine contribution due to **one** independent source
  - Set all other sources to 0: Replace independent voltage source by short circuit, independent current source by open circuit
2. Repeat for each independent source
3. Sum individual contributions to obtain desired voltage or current


## Open Circuit and Short Circuit

---

- Open circuit  $\rightarrow i=0$  ; Cut off the branch
- Short circuit  $\rightarrow v=0$  ; replace the element by wire
- Turn off an independent voltage source means
  - $V=0$
  - Replace by wire
  - Short circuit
- Turn off an independent current source means
  - $i=0$
  - Cut off the branch
  - open circuit

# Superposition Example

- Find  $V_o$

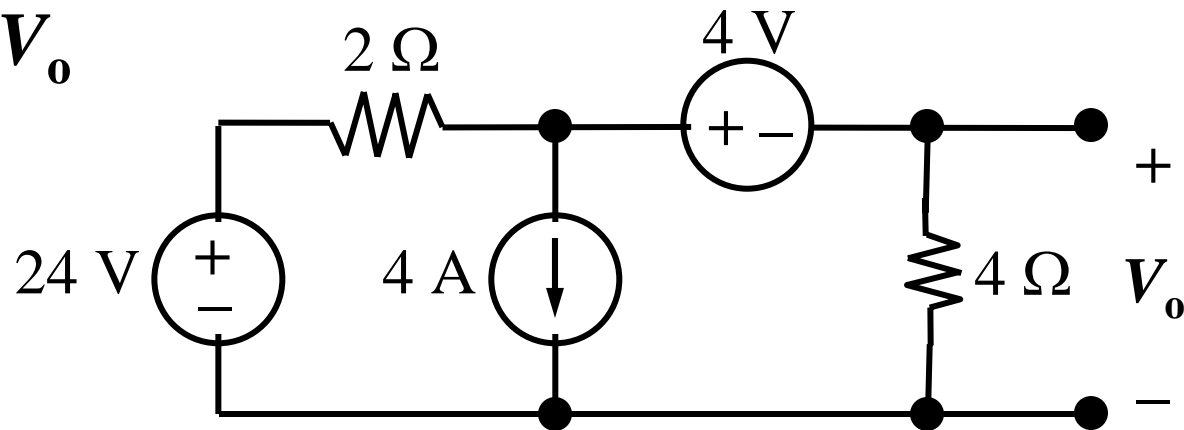

Handwritten analysis for the first superposition case (24V source active, others inactive):

$$V_{o1} = \left( \frac{4}{4+2} \right) 24 = \frac{4}{6} \cdot 24 = 16 \text{ V}$$

$\Rightarrow V_{o1} = 16 \text{ V}$

Handwritten analysis for the second superposition case (4A source active, others inactive):



$$V_{o2} = -i_1 \cdot 4$$

$$i_1 = \frac{2}{4+2} \cdot 4 = \frac{8}{6} = \frac{4}{3} \text{ A}$$

$V_{o2} = -\frac{16}{3} \text{ V}$



# Superposition example (contd.)

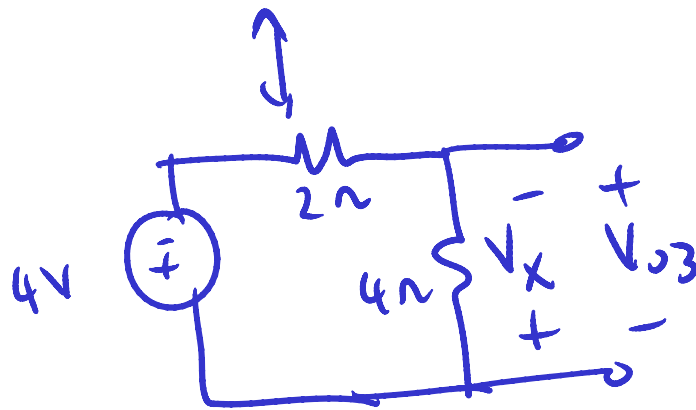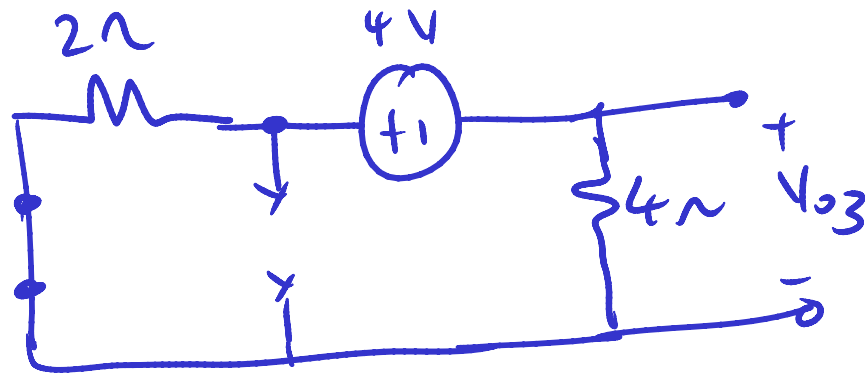

$$V_x = \left( \frac{4}{4+2} \right) 4$$

[Voltage Divider]

$$V_{o3} = -V_x = -\frac{4}{6} \cdot 4 = -\frac{16}{6} \text{ V} \\ = -\frac{8}{3} \text{ V}$$

## Superposition example (contd.)

---

$$V_o = V_{o1} + V_{o2} + V_{o3}$$

$$= 16 - \frac{16}{3} - \frac{8}{3} = 16 - \frac{24}{3} = \underline{\underline{8 \text{ V}}}$$

# Equivalent Circuit Concept

---


- A network of voltage sources, current sources, and resistors can be replaced by an **equivalent circuit** which has identical terminal properties ( $I$ - $V$  characteristics) without affecting the operation of the rest of the circuit.



$$i_A(v_A) = i_B(v_B)$$
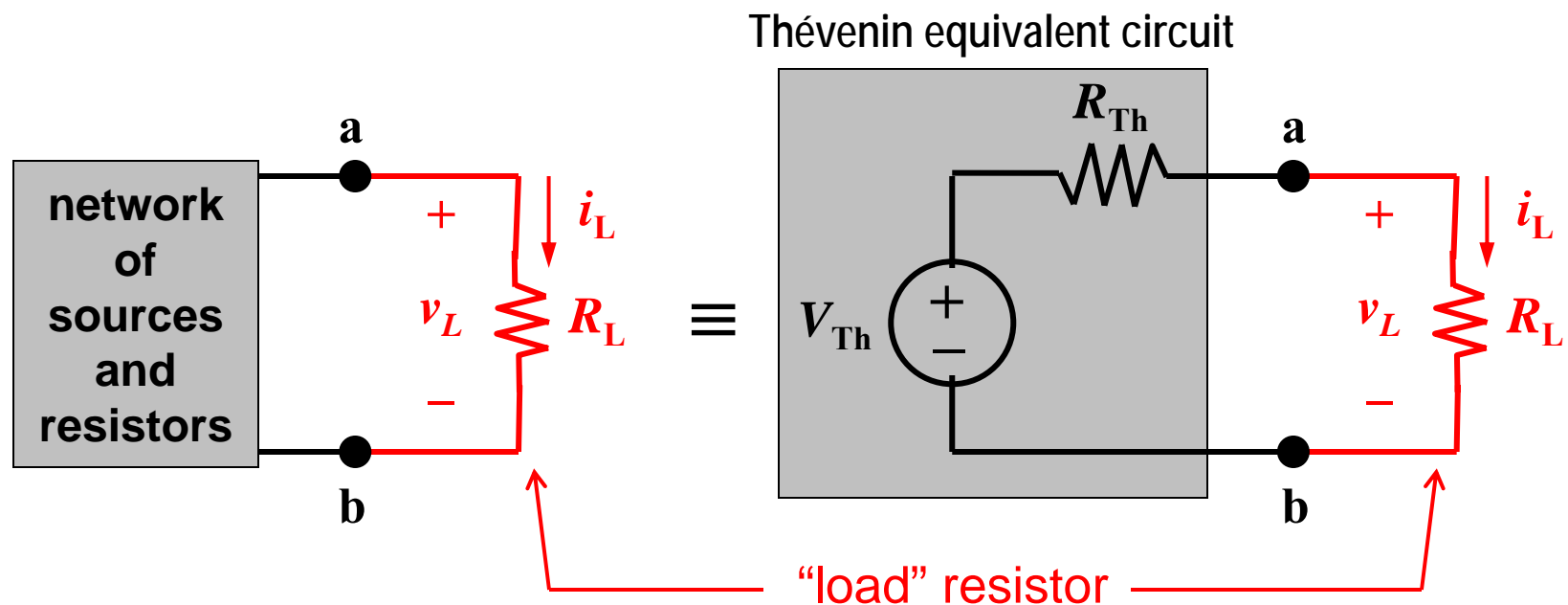
# Thévenin Equivalent Circuit



- Any\* *linear* 2-terminal (1-port) network of indep. voltage sources, indep. current sources, and linear resistors can be replaced by an equivalent circuit consisting of **an independent voltage source in series with a resistor** without affecting the operation of the rest of the circuit.



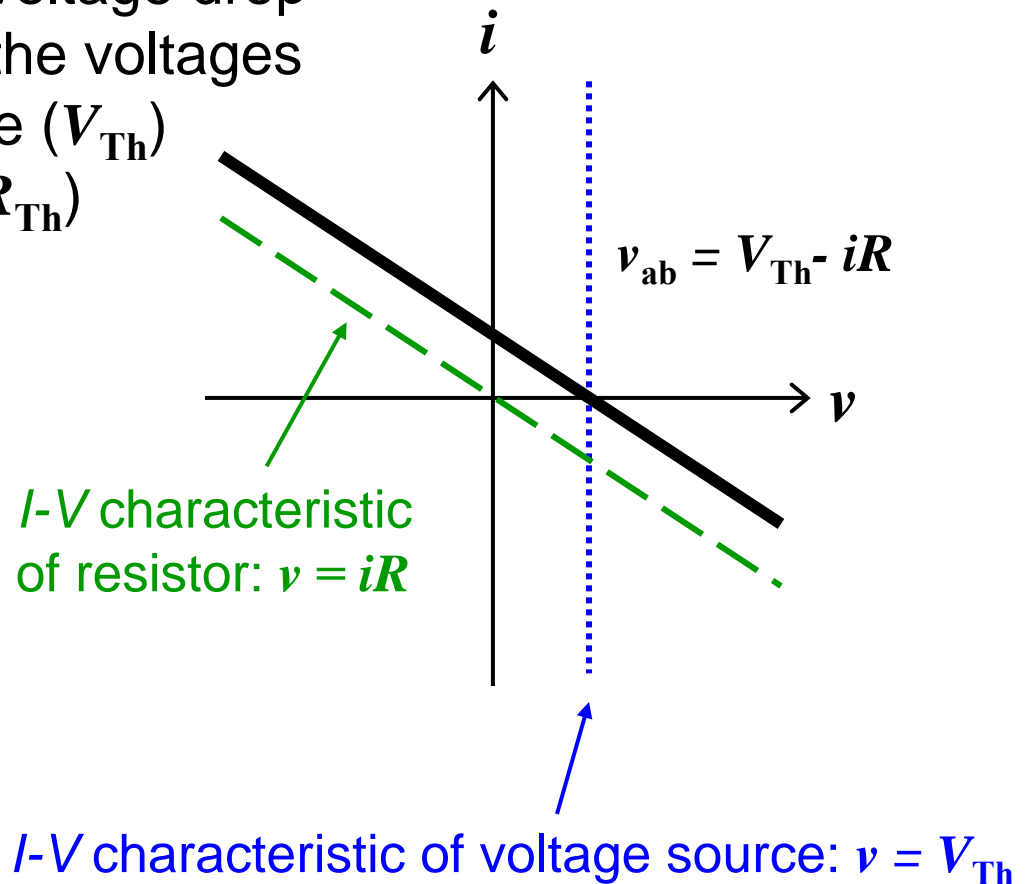
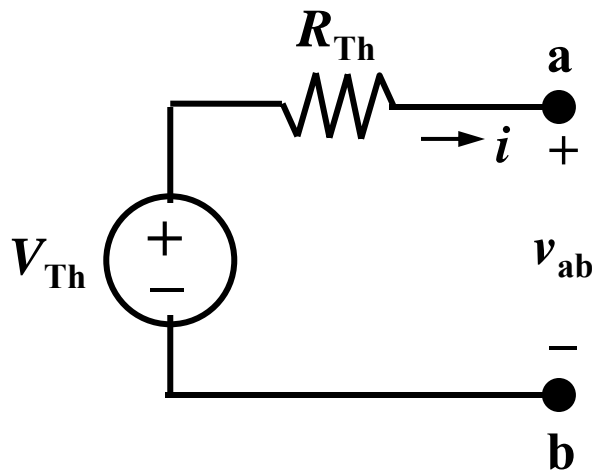
# I-V Characteristic of Thévenin Equivalent

- The *I-V* characteristic for the series combination of elements is obtained by adding their voltage drops:

For a given current  $i$ , the voltage drop  $v_{ab}$  is equal to the sum of the voltages dropped across the source ( $V_{Th}$ ) and across the resistor ( $iR_{Th}$ )



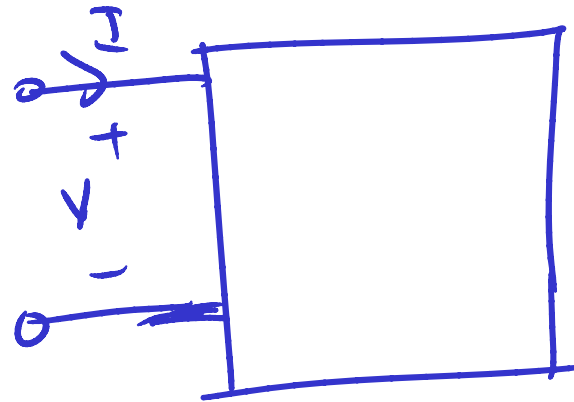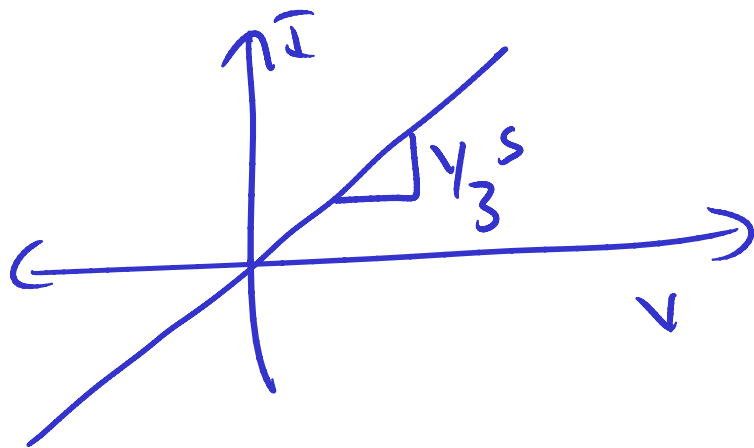
# Intuitive ideas behind Thevenin's theorem



$R_{eq} = 3 \Omega$ . We do not know what is (are) the actual resistance (resistances) inside the box!



ex:  $R_{eq} = 6 \parallel 6 \Omega, 2 + 1 \Omega, 0.5 + 2.5 \Omega \dots$
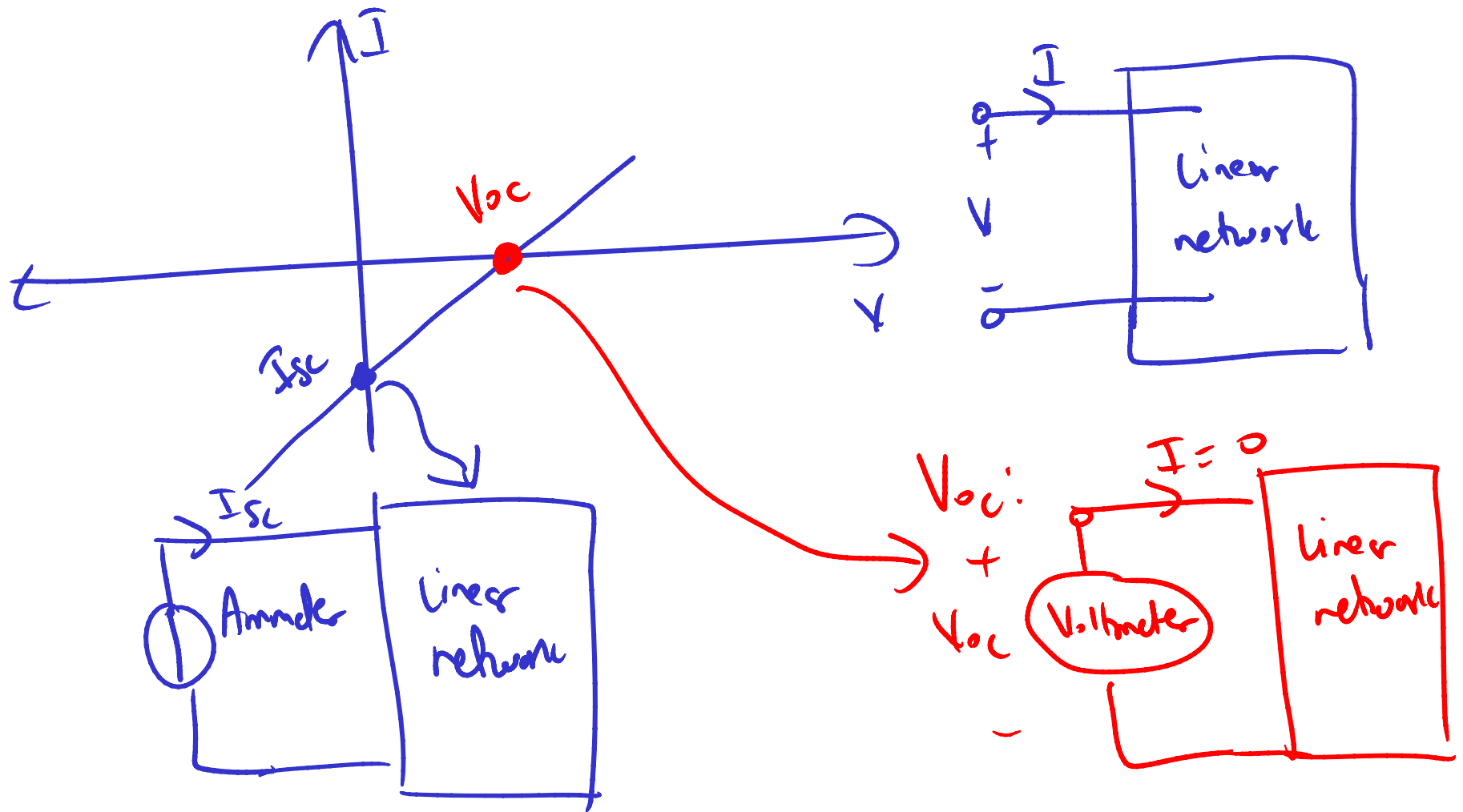
# Intuitive ideas behind Thevenin's theorem (contd.)


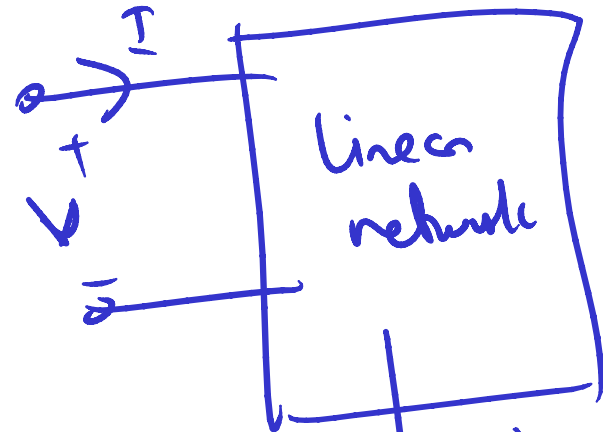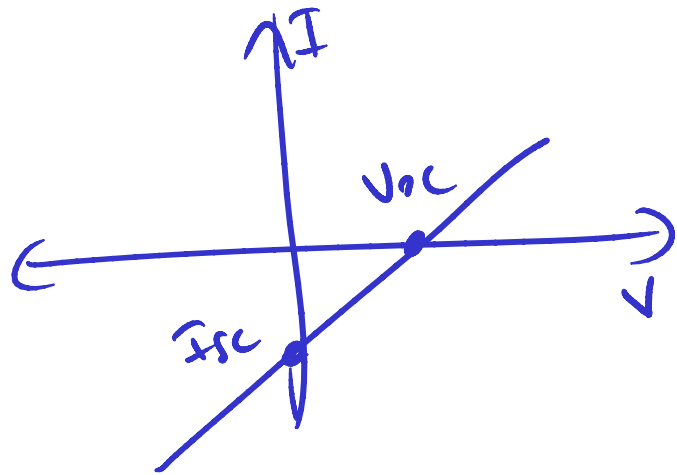
# Intuitive ideas behind Thevenin's theorem (contd.)


Now, I have  $V_{oc}$  &  $I_{sc} \Rightarrow R_{Thevenin} = R_m \triangleq \frac{-V_{oc}}{I_{sc}} \triangleq \frac{1}{\text{slope}}$




Replace  
Linear  
network  
with  
Thevenin equivalent



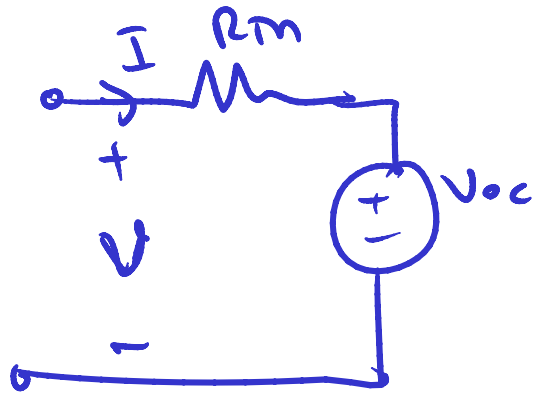
# Intuitive ideas behind Thevenin's theorem (contd.)



$$\tilde{V}_{oc} = V_{oc} \checkmark$$

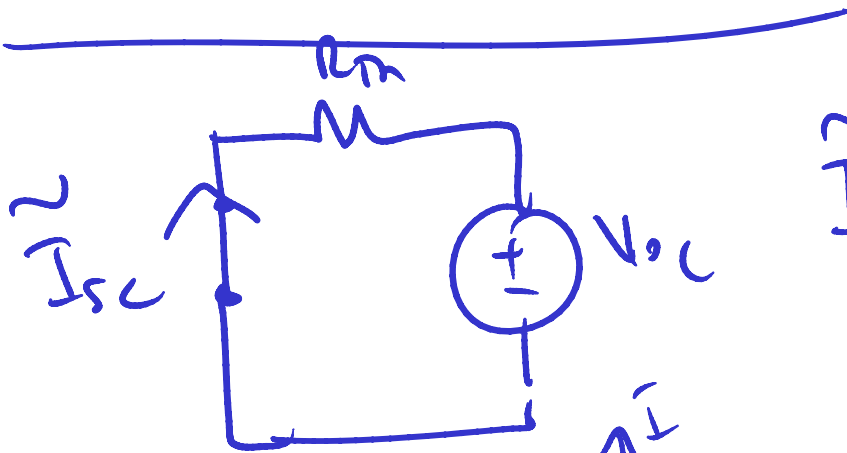
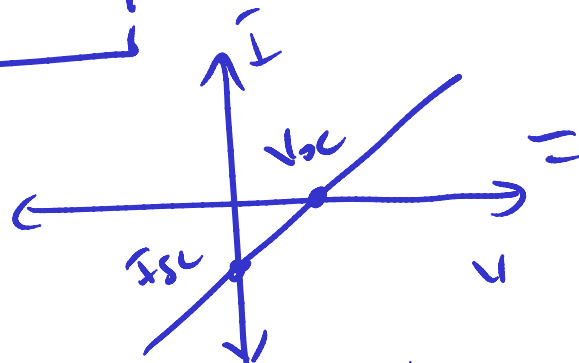
$$\tilde{I}_{sc} = -\frac{V_{oc}}{R_{Th}}$$




$$I_{sc} \checkmark$$

# Thévenin Equivalent Example

Find the Thevenin equivalent with respect to the terminals a,b:

(p. 4.64)

HW #2  
problem

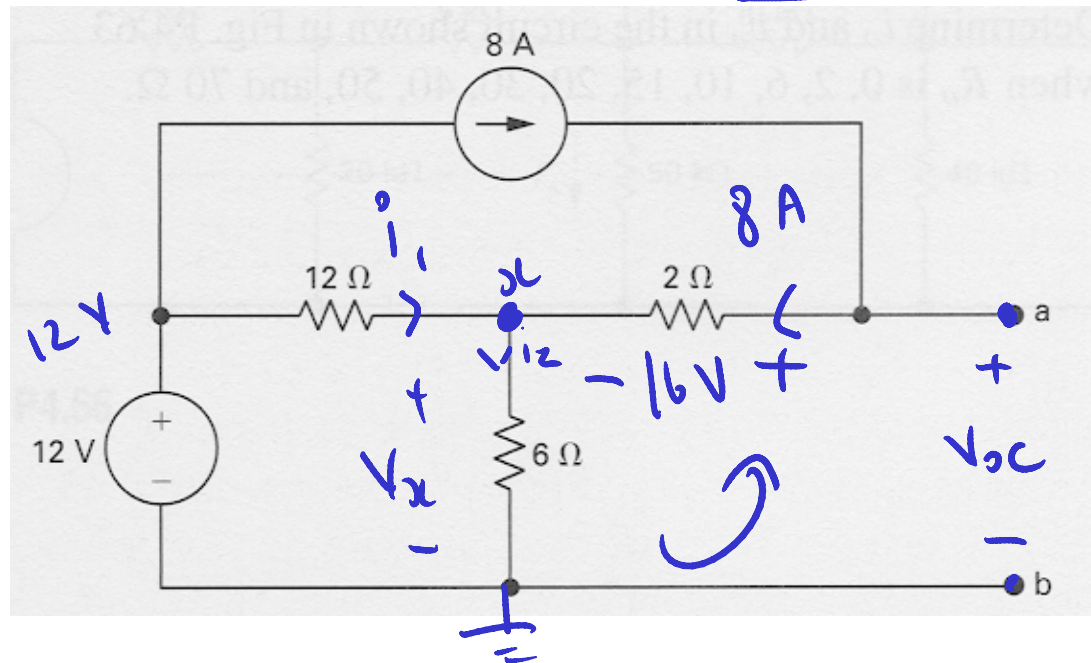

Goal: Find  $V_{oc}$  &  $I_{sc}$

Step 1: Finding  $V_{oc}$ :

$$V_x = V_{oc} - 16$$

Node eqn @  $x$ :  $i_1 + 8A = i_2 \Rightarrow \frac{12 - V_x}{12} + 8 = \frac{V_x}{6}$


# Thévenin Equivalent Example (contd.)

$$\Rightarrow 12 - V_x + 9b = 2V_x$$


$$\Rightarrow V_x = \frac{108}{3} = \underline{\underline{36\text{ V}}}$$

$$\therefore V_{oc} = V_x + 16 = \underline{\underline{52\text{ V}}}$$


$I_{sc}$ :

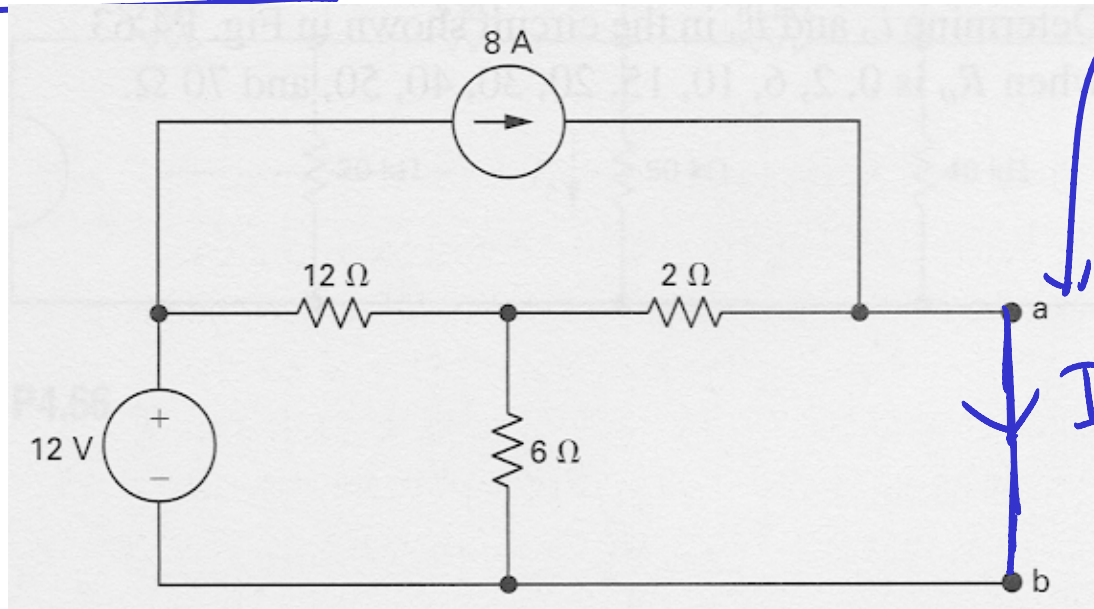

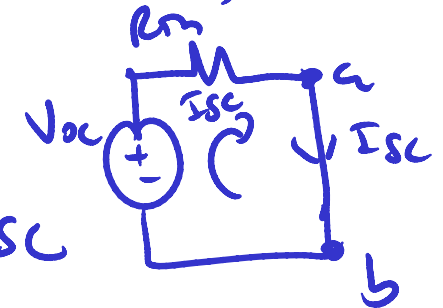Direction of  $I_{sc}$  is from a to b, because



## Aside: Prelab 1, question 3

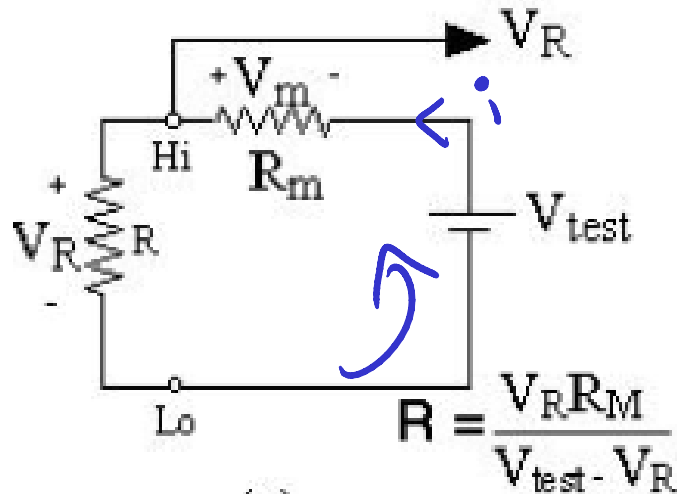

(Q:) Prove:  $R = \frac{V_R R_M}{V_{\text{test}} - V_R}$

KVL:  $V_{\text{test}} + V_m - V_R = 0$


$$\begin{array}{l}
 +V_m - \\
 \text{---} \\
 R_m \\
 \\
 V_m = -iR_m
 \end{array}
 \quad \Bigg| \quad
 \begin{array}{l}
 +V_R \\
 \text{---} \\
 R \\
 - \\
 V_R = iR
 \end{array}$$

$$\Rightarrow V_{\text{test}} + (-iR_m) - V_R = 0$$

$$\Rightarrow i = \frac{V_{\text{test}} - V_R}{R_m}$$



$$\therefore R = V_R / i$$

# Thévenin Equivalent Example (contd.)

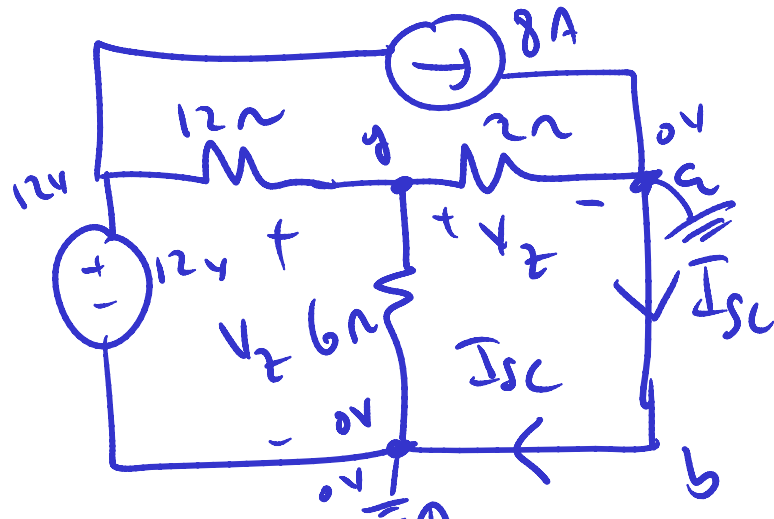


$$I_{sc} = 9 \text{ A (??)}$$
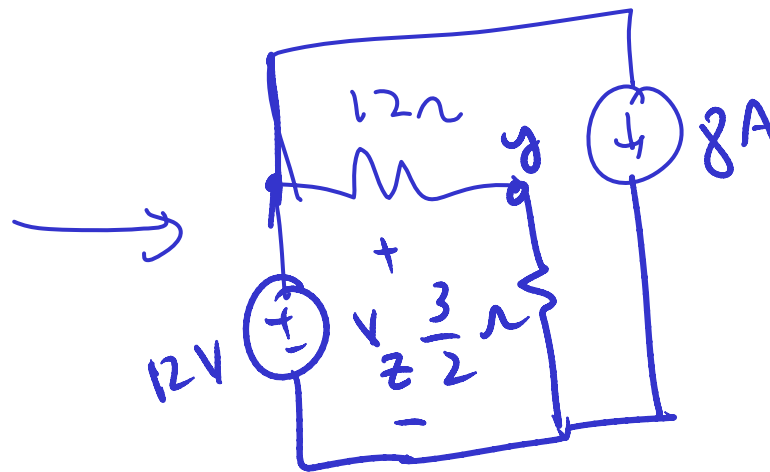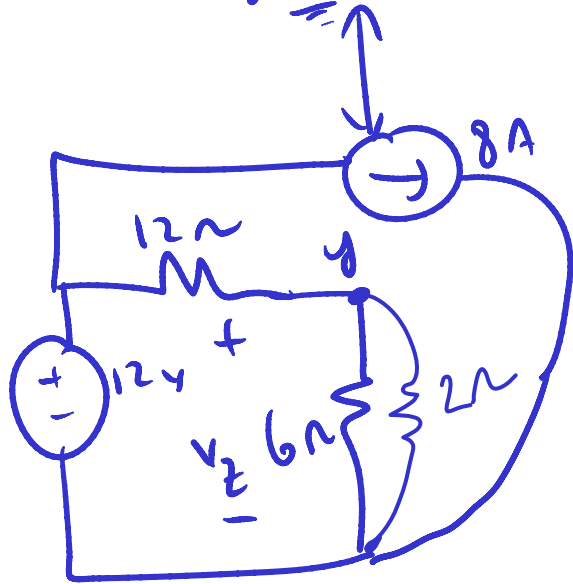
$$V_z = \left( \frac{\frac{3}{2}}{3\frac{1}{2} + 12} \right) 12 \text{ V} = \frac{36}{27} = \underline{\underline{\frac{4}{3} \text{ V}}}$$



# Thévenin Equivalent Example (contd.)

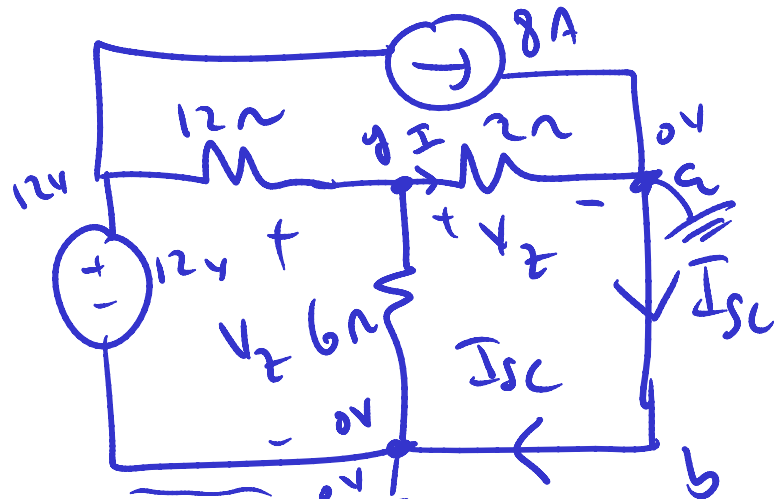

$$V_z = \frac{4}{3} \text{ V}$$



$$I = \frac{V_z}{2} = \frac{2}{3} \text{ A}$$

$$I_{sc} = 8 + 2 \frac{1}{3} = \underline{\underline{\frac{26}{3} \text{ A}}}$$




$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{52}{\frac{26}{3}} = \frac{52 \cdot 3}{26} = \underline{\underline{6 \Omega}}$$

# Thévenin Equivalent Example (contd.)

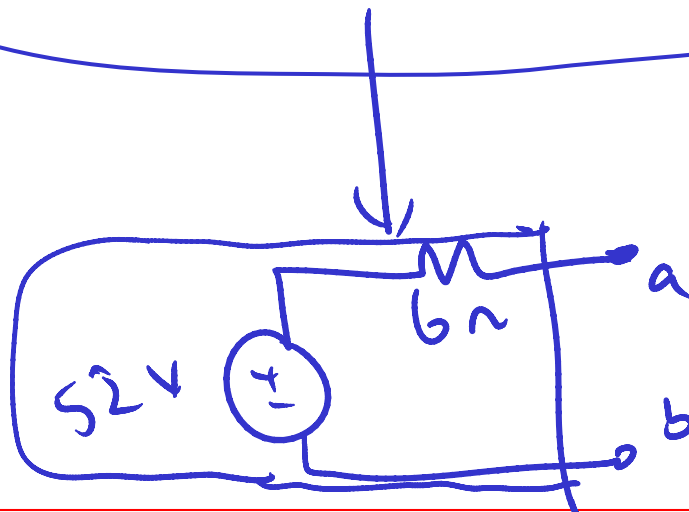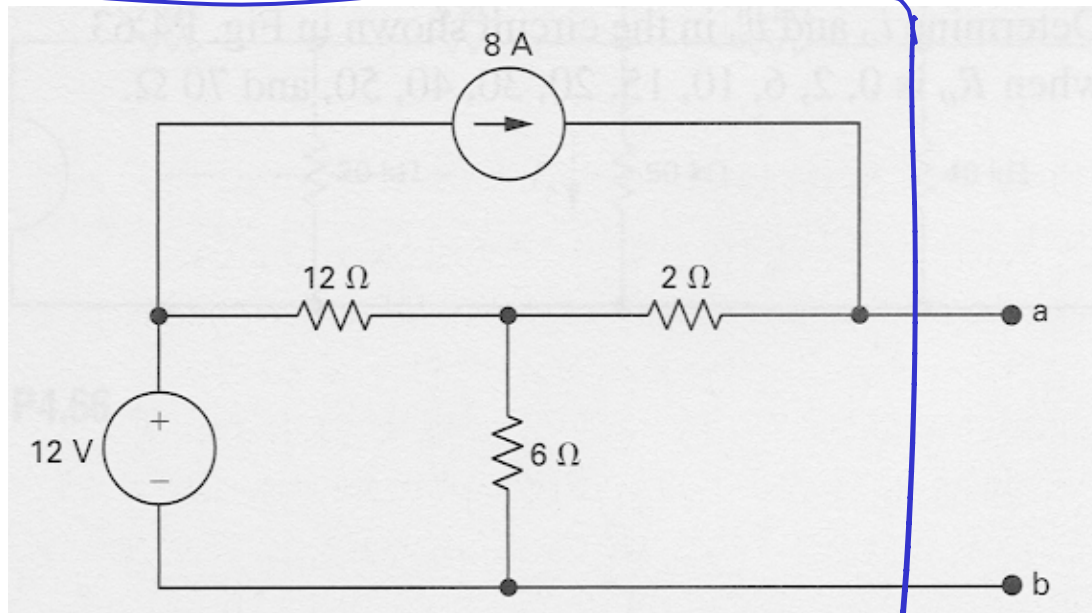

# $R_{Th}$ Calculation Example #1

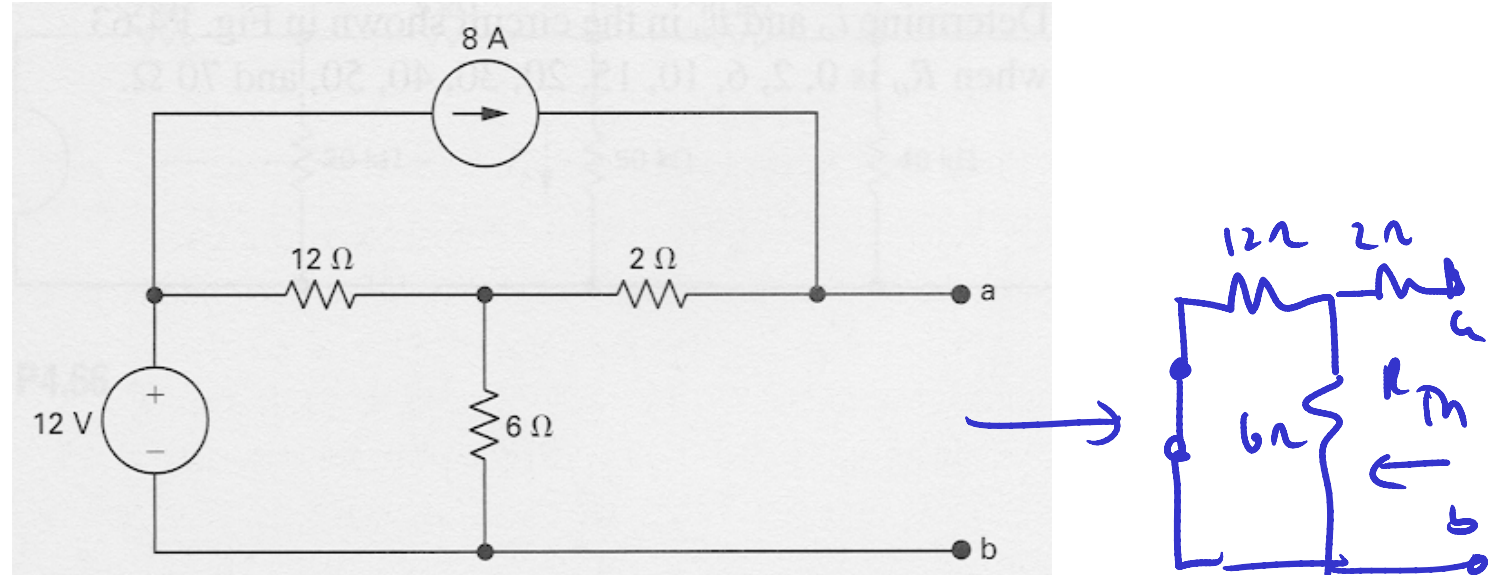

**Set all independent sources to 0:**

