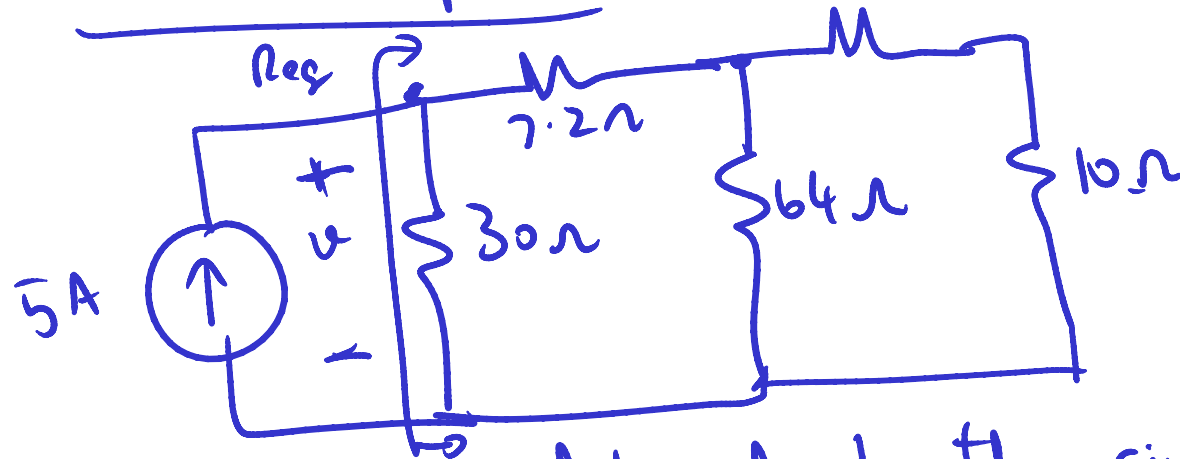


EE100Su08 Lecture #4 (June 30th 2008)

- Outline
 - Questions?
 - Lab notes:
 - Finish lab 1, will shorten lab 2 and others
 - **Dependent Sources Example**
 - Node-Voltage Analysis
 - Concept
 - Examples
 - Node voltage method with dependent sources

Review

(1) DP3.1 on p. 62



(Q.) Find v , power delivered to the circuit by the source & power dissipated in the 10Ω resistor.

Sol. Combine resistors into one equivalent resistance across the 5A source \Rightarrow we can find v .

$$R_{eq} = \left[(6 + 10) \parallel 64 \right] + 7.2 \parallel 30 = \left[(16 \parallel 64) + 7.2 \right] \parallel 30$$

DP 3.1 (cont d.)

$$= \left[\left(\frac{16 \cdot 64}{80} \right) + 7.2 \right] \parallel 130$$


$$= (12.8 + 7.2) \parallel 130$$

$$= 20 \parallel 130 = \frac{20 \cdot 130}{50} = 12 \Omega$$


$$P_{5A} = -vi = -(60)(5) = -300 \text{ W}$$

\therefore Power delivered by the 5A source = 300 W
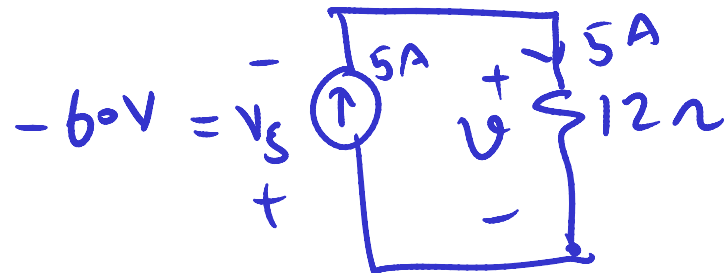
$$\begin{aligned} \therefore \text{KVL: } -V_s - V &= 0 \\ \Rightarrow V_s &= -V \end{aligned}$$




$$\begin{aligned} \therefore V &= (5A)(12\Omega) \\ &= 60V \end{aligned}$$

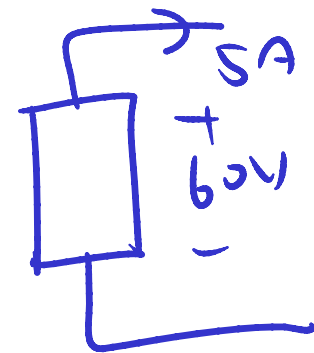

DP 3-1 (contd.)

Going back:

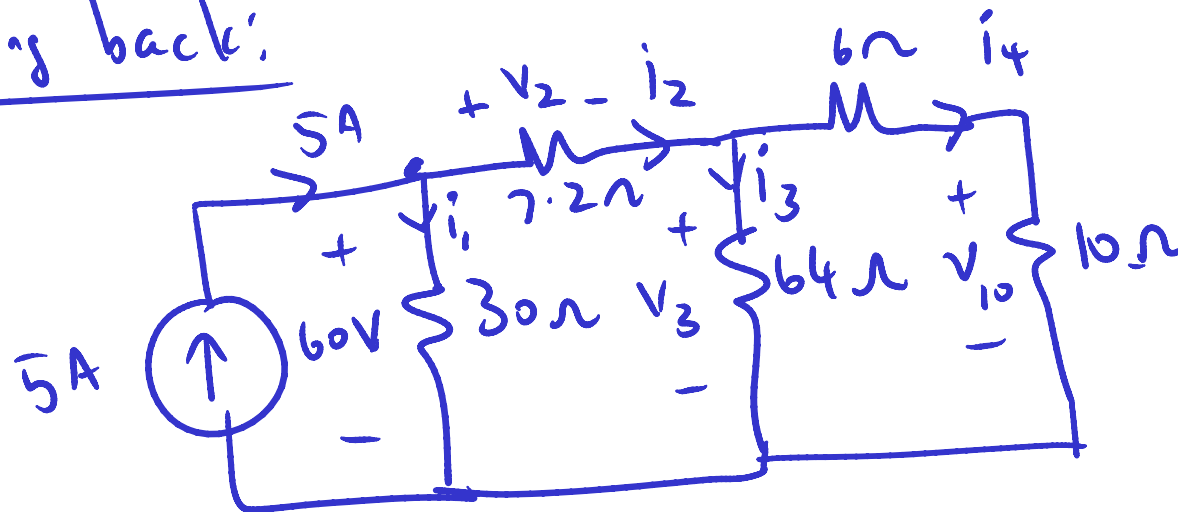

$$i_1 = \frac{60V}{30\Omega} = 2A \quad \therefore i_2 = 3A \text{ (by KCL)}$$


$$V_2 = (3)(7.2) = 21.6V \Rightarrow V_3 = 60 - 21.6 \text{ (KVL)} \\ = \underline{\underline{38.4V}}$$

$$i_3 = \frac{38.4}{64} = 0.6A \Rightarrow i_4 = 2.4A \text{ (by KCL)} \Rightarrow P_{10\Omega} = V_{10} i_4$$

DP3.1 (contd.)

$$\therefore P_{10\Omega} = v_i = i^2 R = (2.4)^2 (10) = (5.76)(10) = 57.6 \text{ W}$$


Ex: P2-30 on p. 53

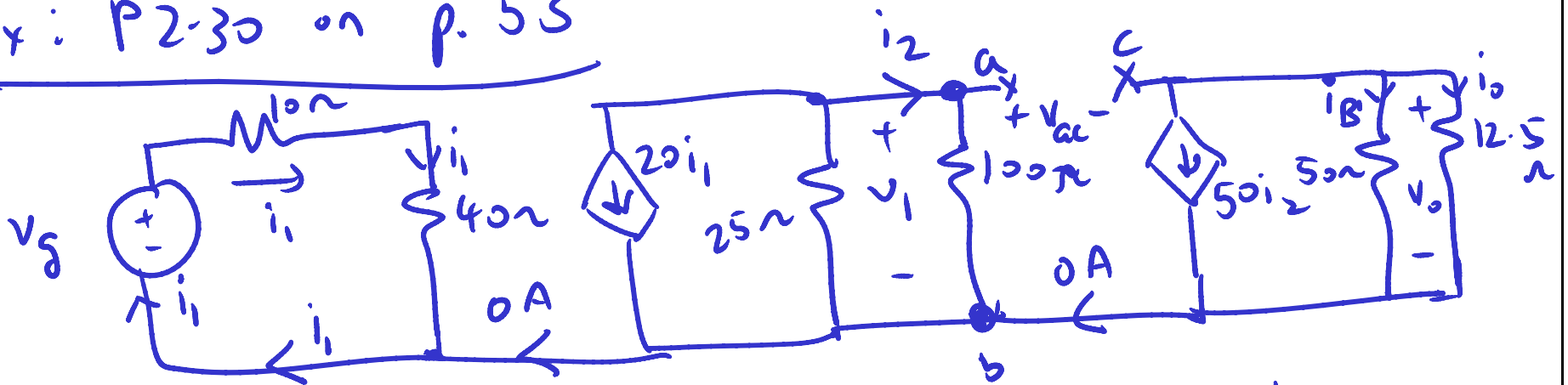

(Q:) Find v_1 & v_s if $v_o = 250 \text{ mV} = 0.25 \text{ V} = \frac{1}{4} \text{ V}$

Notice: $V_{ac} = v_1 - v_o$

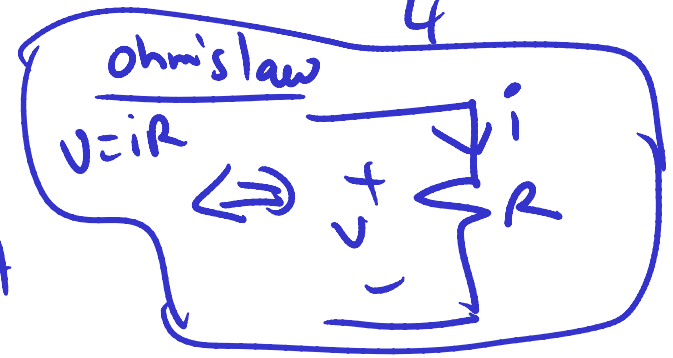
Also: $i_o = \frac{v_o}{12.5} = \frac{0.25}{12.5} = \underline{\underline{20 \text{ mA}}}$



P 2.30 (contd.)

$$i_B = \frac{V_o}{50} = \frac{0.25}{50} = \underline{\underline{5 \text{ mA}}}$$


KCL @ node "c": $50i_2 + i_B + i_o = 0$

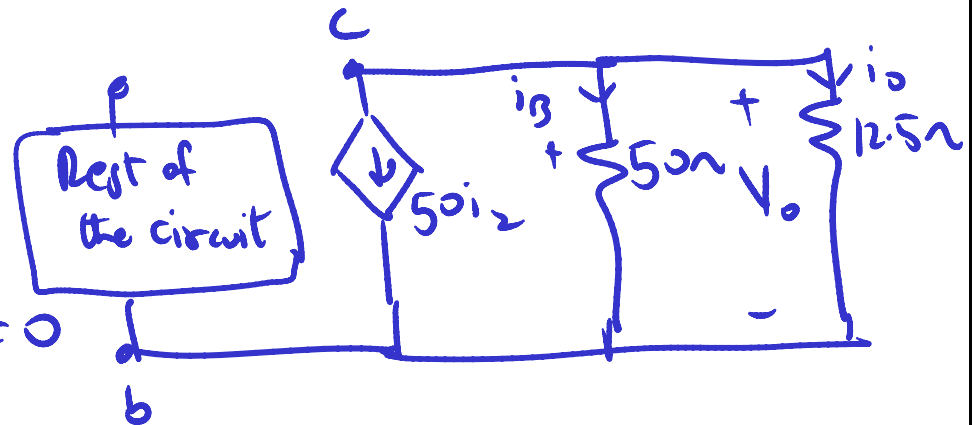

$$\Rightarrow 50i_2 = -25 \text{ mA}$$



$\Rightarrow i_2 = -\frac{1}{2} \text{ mA} \Rightarrow$ Use same strategy to
find i_1 & consequently V_g .

Note on sign conventions

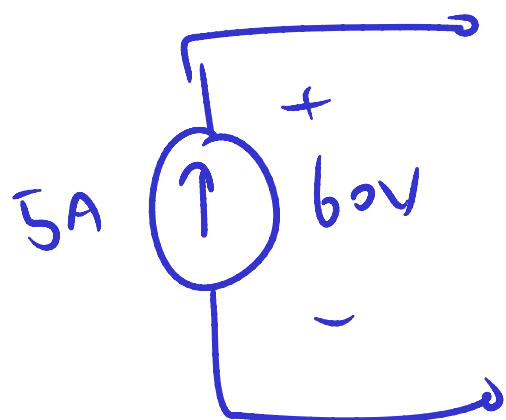

$$P_{5A} = -vi$$


$$= -(60)(5) = -300W$$

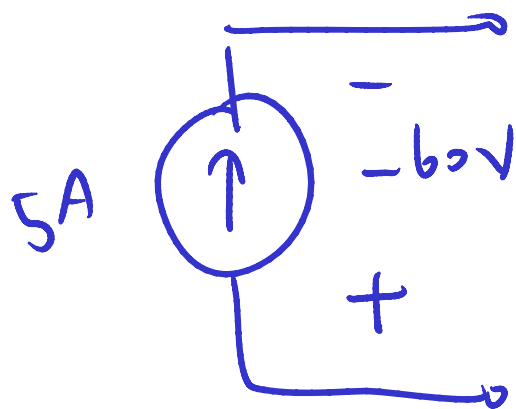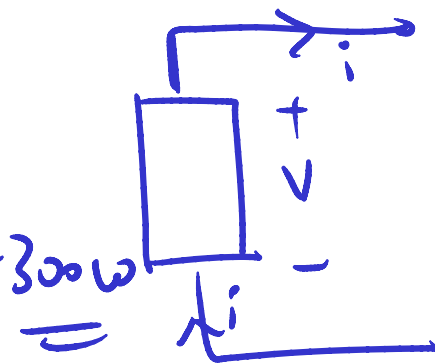

$$P_{5A} = +vi$$

$$= +(-60)(5)$$

$$= \underline{\underline{-300W}}$$

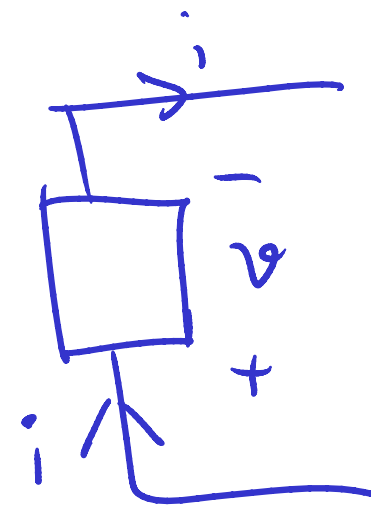


Node-Voltage Circuit Analysis Method

- (1) Sections 4.1 thro' 4.4
- (2) Rook has a good intuitive explanation of why nodal analysis works \Rightarrow uses concept of essential nodes.
- (3) I will use a different approach to explain nodal analysis.

Node-Voltage Circuit Analysis Method

- 1. Choose a reference node (“ground”)**
Look for the one with the most connections!
- 2. Define unknown node voltages**
those which are not fixed by voltage sources
- 3. Write KCL at each unknown node**, expressing current in terms of the node voltages (using the I - V relationships of branch elements)
Special cases: floating voltage sources
- 4. Solve the set of independent equations**
 N equations for N unknown node voltages

Nodal Analysis: Example #1

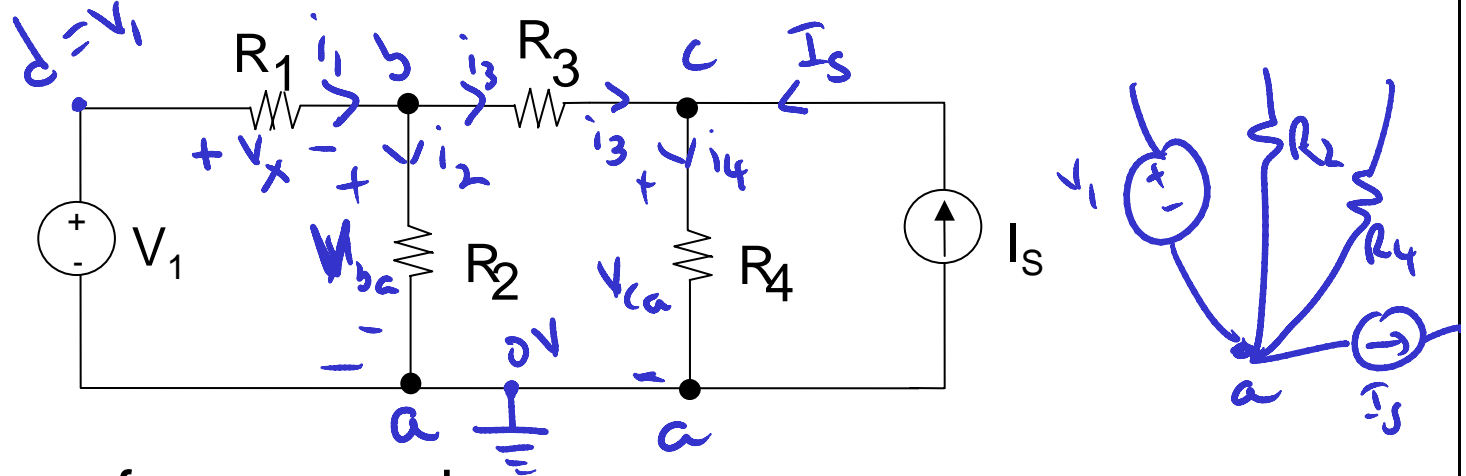

1. Choose a reference node.
2. Define the node voltages (except reference node and the one set by the voltage source).

3. Apply KCL at the nodes with unknown voltage.


KCL @ node "b": $i_1 = i_2 + i_3$

KCL @ node "c": $i_3 + I_s = i_4$

4. Solve for unknown node voltages.

4(a) $i_1 = \frac{v_x}{R_1} = \frac{v_1 - v_b}{R_1}$

Nodal Analysis: Example #1

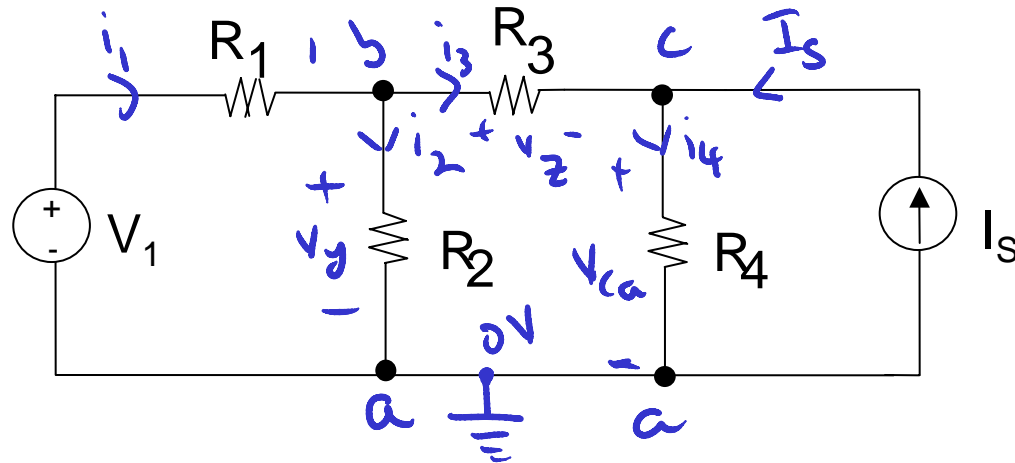

$$i_2 = \frac{V_b}{R_2} = \frac{V_b}{R_2}, \quad i_3 = \frac{V_b - V_c}{R_3}$$

$$i_4 = \frac{V_c}{R_4}$$


Step (9) b: $i_1 = i_2 + i_3 \Rightarrow \frac{V_1 - V_b}{R_1} = \frac{V_b}{R_2} + \frac{V_b - V_c}{R_3}$

$i_3 + I_s = i_4 \Rightarrow \frac{V_b - V_c}{R_3} + I_s = \frac{V_c}{R_4}$

Node analysis example. DP4.1 on p. 99



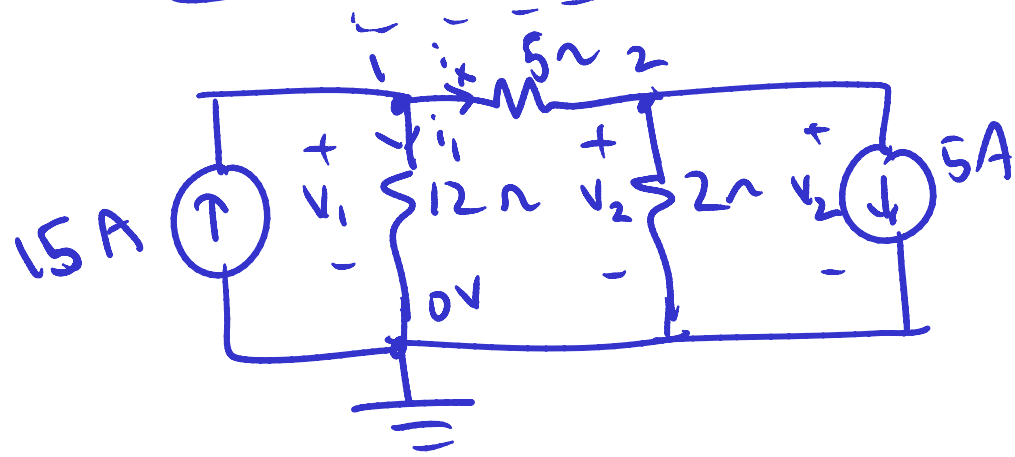(Q.) Use node-voltage method to find v_1 & v_2 .



Nodal analysis:

(1) Assign ground

(2) Nodal analysis @ ①:

$$15 = \frac{v_1}{12} + \frac{v_1 - v_2}{5} \quad \text{--- (1)}$$

$$\frac{v_1 - v_2}{5} = \frac{v_2}{2} + 5 \quad \text{--- (2)}$$

Nodal analysis @ ②:

DP4.1 on p. 99 (contd.)

$$(1) \times 60 \Rightarrow 900 = 5v_1 + 12(v_1 - v_2)$$

$$(2) \times 10 \Rightarrow 2(v_1 - v_2) = 5v_2 + 50.$$

$$\Rightarrow 900 = 17v_1 - 12v_2$$

$$50 = 2v_1 - 7v_2$$

solve

\Rightarrow

$$v_1 = 60V, v_2 = 10V$$


Check: $17 \cdot 60 - 12 \cdot 10 = 1020 - 120 = 900 \checkmark$

$$2 \cdot 60 - 7 \cdot 10 = 120 - 70 = 50 \checkmark$$

Section 4.3: Node-voltage method & Dependent sources

Nothing special, just need a "constraint equation" for the dependent source.

DP 4.3 on p. 101

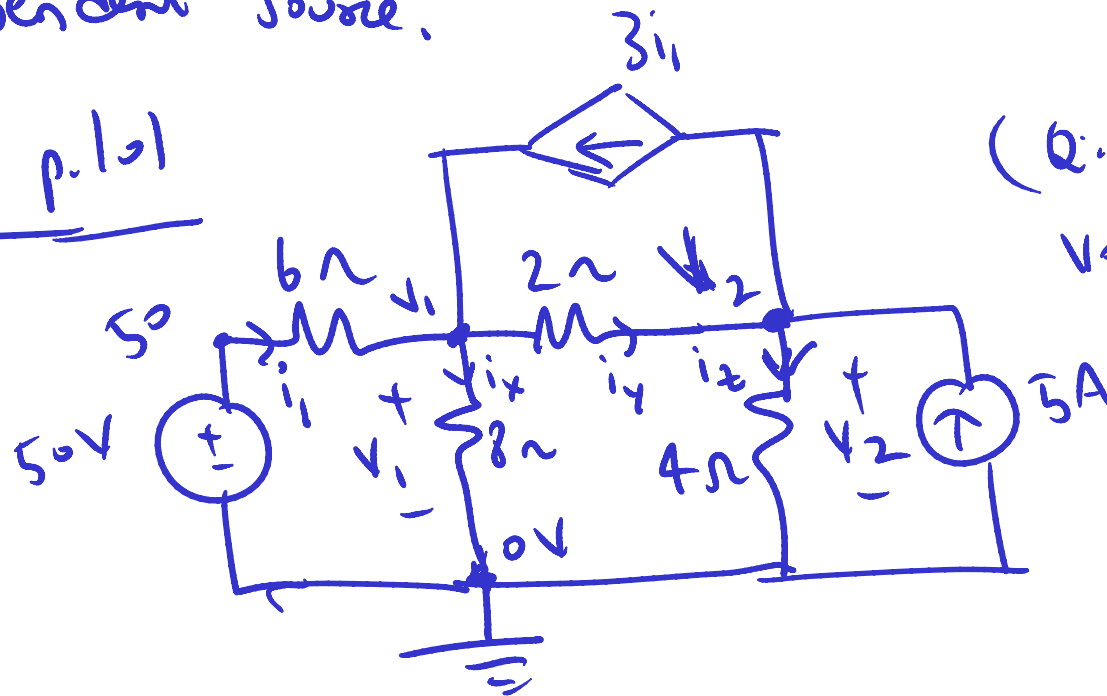

(Q:) Use node voltage to find the power associated with each source.
constraint eqn.

Node analysis: @ v_1 : $i_1 + 3i_1 = i_x + i_y$, $i_1 = \frac{50 - v_1}{6}$

$i_x = \frac{v_1}{8}$, $i_y = \frac{v_1 - v_2}{2}$, @ v_2 : $i_y + 5 = i_z + 3i_1$, $i_z = v_2/4$