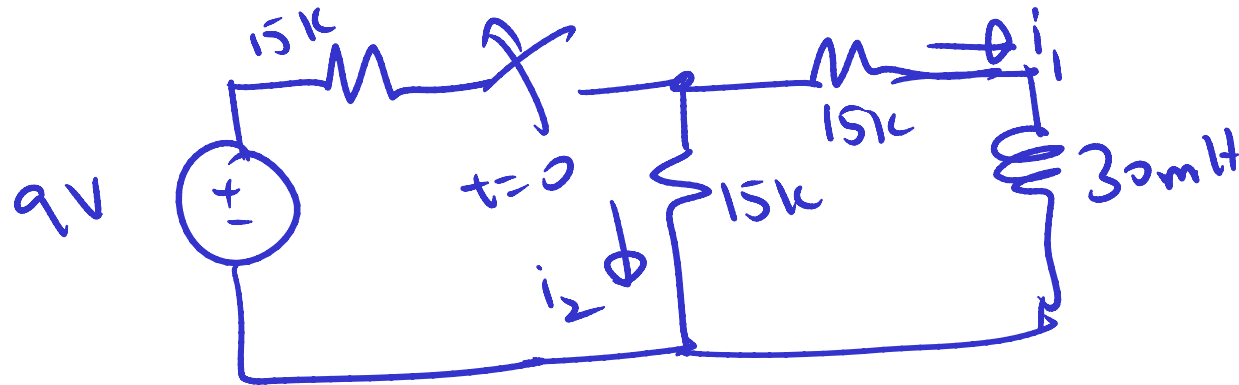


EE100Su08 Lecture #8 (July 11th 2008)

- Outline
 - HW #1s will be returned on Monday
 - Questions?
 - Wrap up problem 7.2
 - Midterm review
 - TA review session: tomorrow (Saturday, 07/12 from 2 – 4 in 105 North Gate).
 - Start operational amplifiers*

Problem 7.2 on p. 265



Notes:

$$v = L \frac{di}{dt}$$

(a) Find $i_1(0^-)$, $i_2(0^-)$

(b) Find $i_1(0^+)$, $i_2(0^+)$


⋮
⋮
⋮

⇒ (1) Steady state, inductor is a short circuit

(2) Inductor maintains current across discontinuities

$$(3) \tau = L/R$$


Problem 7.2 on p. 265

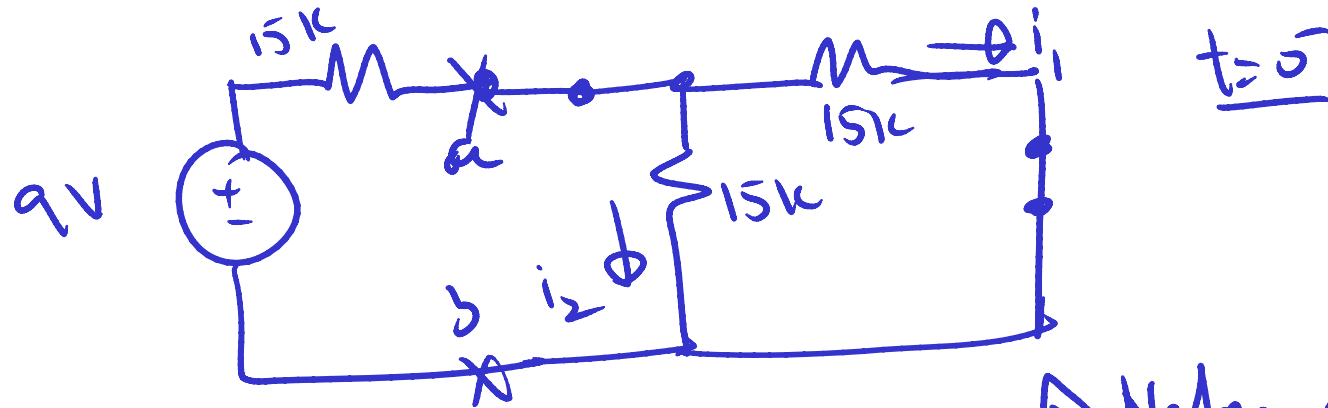


(as Find $i_1(0^-), i_2(0^-)$)

$$i_1(0^-) = i_2(0^-) = \frac{1}{5} \text{ mA}$$

Norton at ab

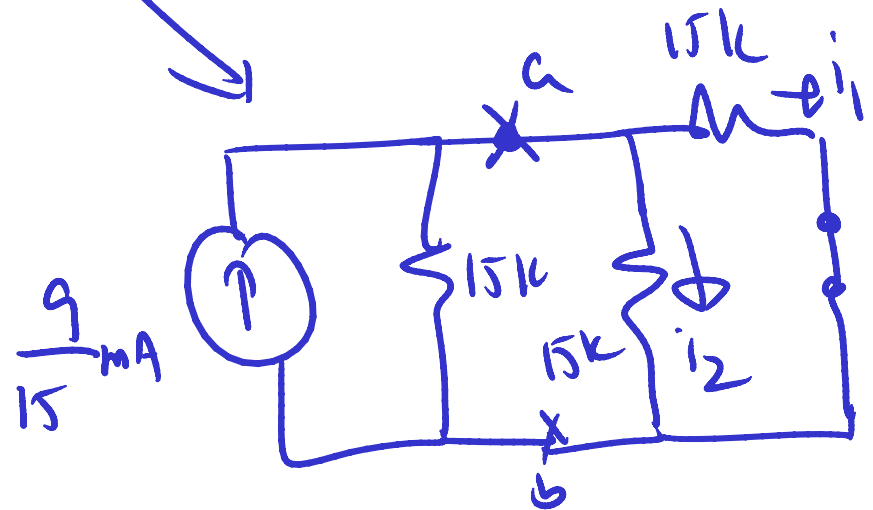

Problem 7.2 on p. 265

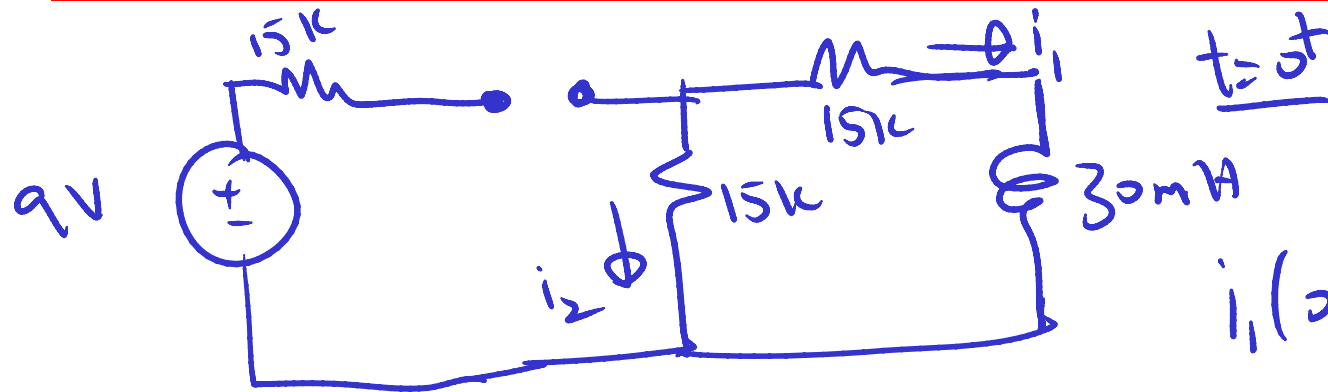

$$i_1(0^+) = i_1(0^-)$$

(b) Find $i_1(0^+)$, $i_2(0^+)$


$$= \underline{\underline{0.2 \text{ mA}}}$$

Notice: $i_2(0^+) = -i_1(0^+)$

$$= \underline{\underline{-0.2 \text{ mA}}}$$

(c) $i_1(t) = i_{1\text{find}} + (i_{1\text{initial}} - i_{1\text{find}}) e^{-t/\tau}$, $\tau = L/R$

Problem 7.2 on p. 265

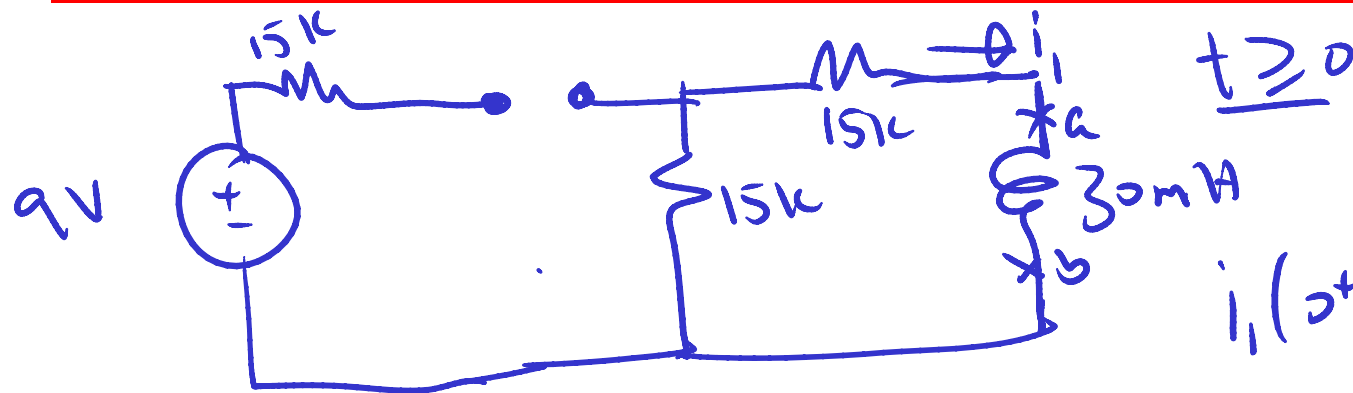

$t \geq 0$

$$i_l(0^+) = i_l(0^-)$$


$$= \underline{\underline{0.2 \text{ mA}}}$$

$$(c) \quad i_l(t) = i_{l, \text{final}} + (i_{l, \text{initial}} - i_{l, \text{final}}) e^{-t/\tau}, \quad \tau = L/R$$


$$i_{l, \text{initial}} = i_l(0^+) = i_l(0^-) = 0.2 \text{ mA}$$

$$i_{l, \text{final}} = i_l(t \rightarrow \infty) = 0$$

$$\therefore i_l(t) = 0.2 e^{-t/\tau} \text{ mA}, \quad \tau = \frac{L}{R_{\text{eq}}} = \frac{30 \text{ mH}}{30 \text{ k}\Omega} = \underline{\underline{1 \mu\text{s}}}$$

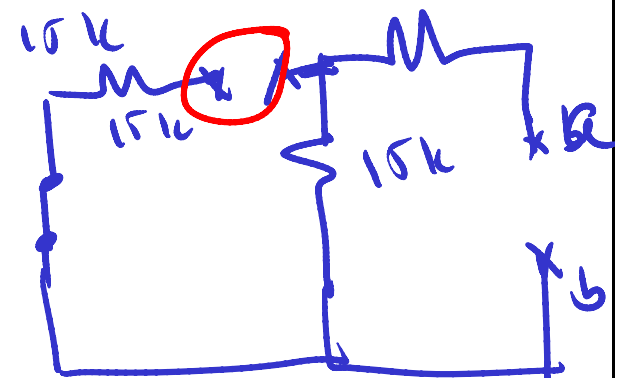

Problem 7.2 on p. 265

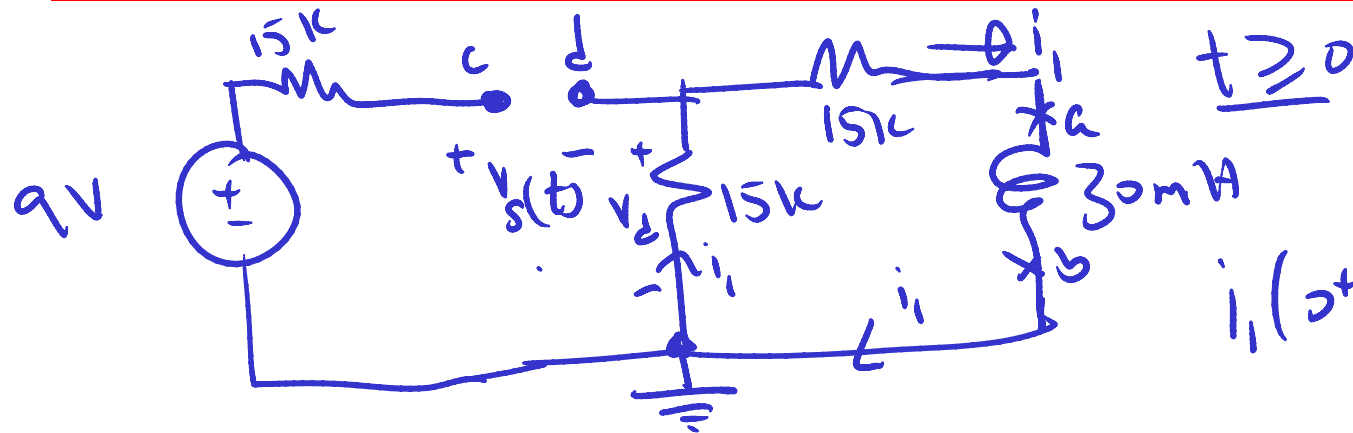


$$i_1(0^+) = i_1(0^-)$$

(a) Find $v_s(t)$ [voltage across the switch] for $t \geq 0$ $= 0.2 \text{ mA}$


$$v_s(t) = v_{sf} + (v_{si} - v_{sf}) e^{-t/\tau} \quad \tau = L/R_{Th}$$

$$v_{si} = v_{ci} - v_{di} = 9 = [-i_1(0^+)(15k)]$$

$$= 9 + 3 = \underline{\underline{12V}}$$

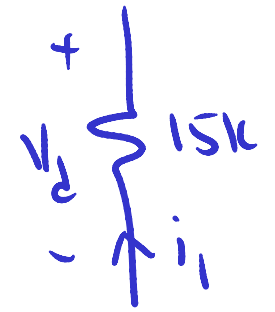

Problem 7.2 on p. 265

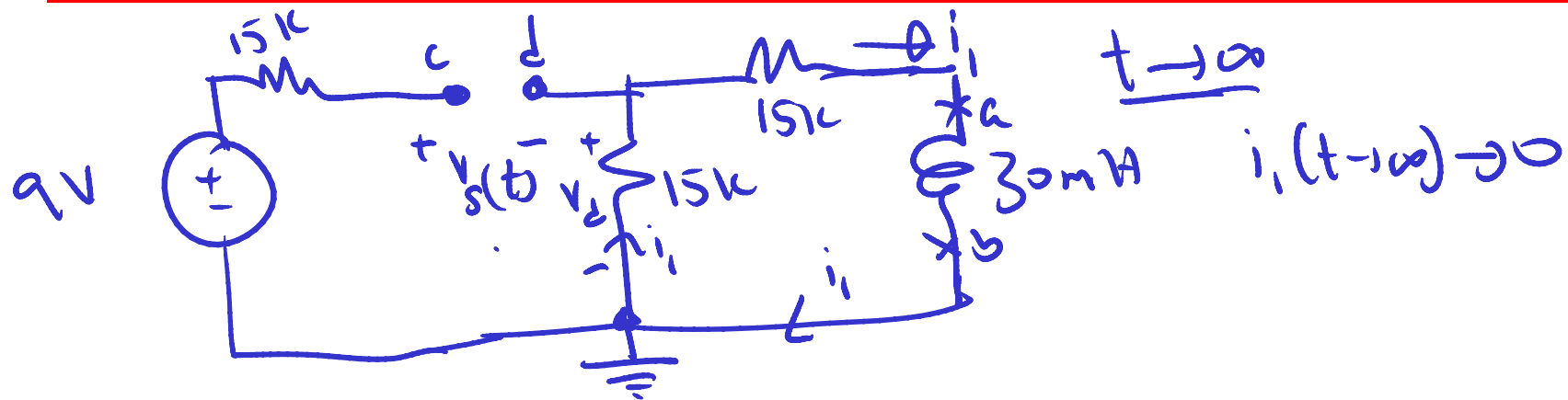


(a) Find $v_s(t)$ [voltage across the switch] for $t \geq 0$?

$$v_s(t) = v_{sf} + (v_{si} - v_{sf}) e^{-t/\tau} \quad \tau = L/R_{Th}$$

$$v_{sf} = v_s(t \rightarrow \infty) = v_c(t \rightarrow \infty) - v_d(t \rightarrow \infty) = 9 - 0 = 9$$




Problem 7.2 on p. 265

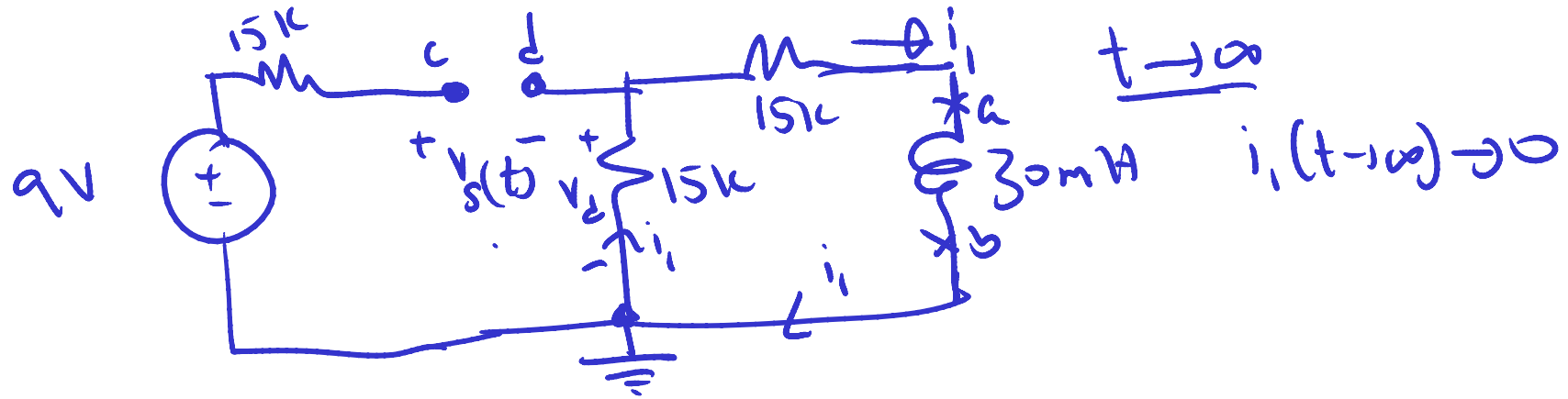


(a) Find $V_s(t)$ [voltage across the switch] for $t \geq 0$?

$$V_s(t) = 9 + (12 - 9)e^{-t/1\mu s} = 9 + 3e^{-\frac{t}{1\mu s}} \quad t \geq 0$$

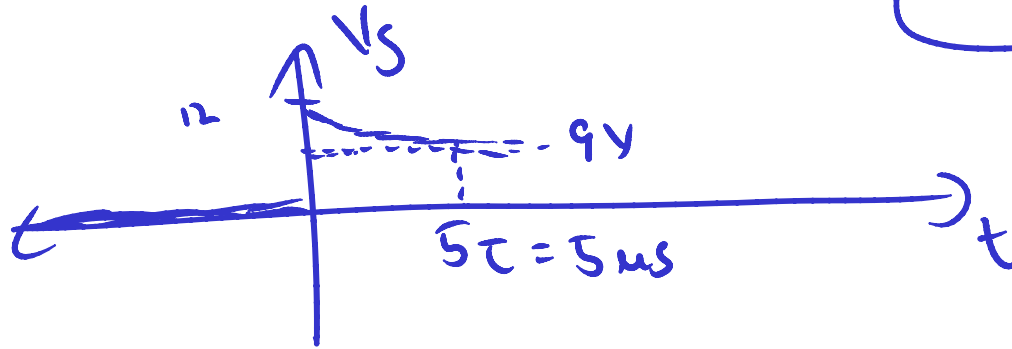


Problem 7.33 on p. 220

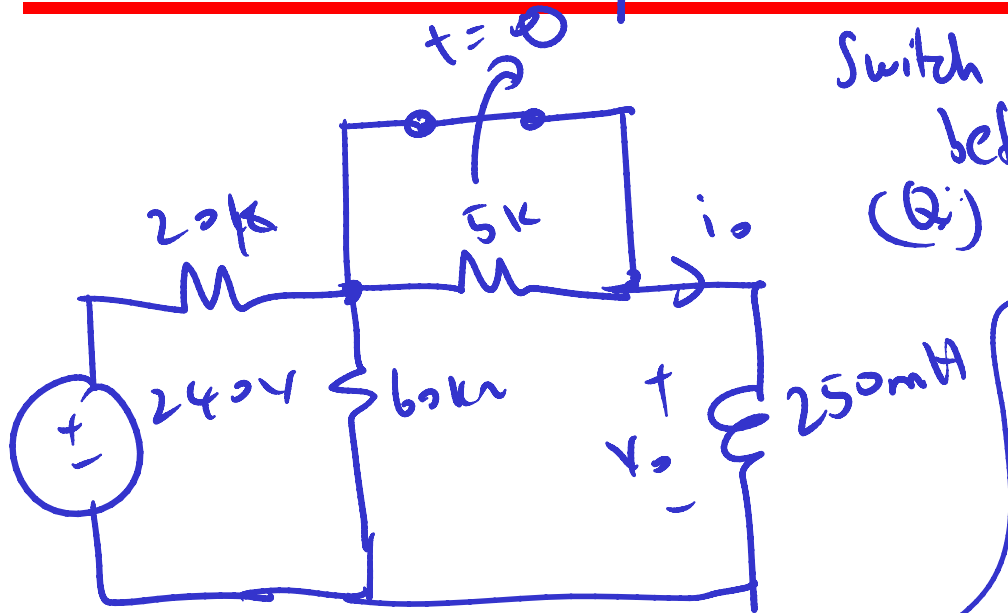


Switch closed for a long time before opening @ $t=0$

(Q) find $i_o(t)$, $v_o(t)$, $t \geq 0$.

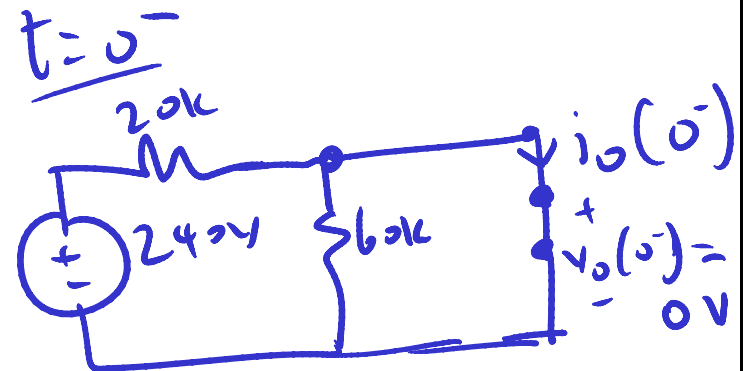

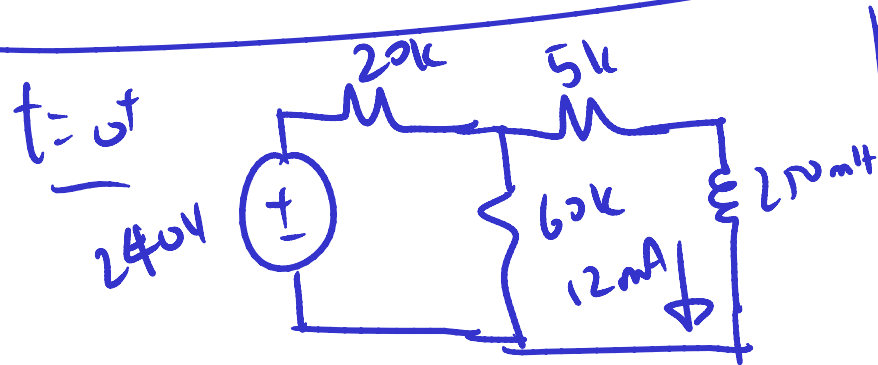
$$i_o(0^-) = 12 \text{ mA} = \frac{24 \text{ V}}{2 \text{ k}}$$




$$i_o(t=0^+) = 12 \text{ mA} = i_{o \text{ initial}}$$

Problem 7.33 on p. 220

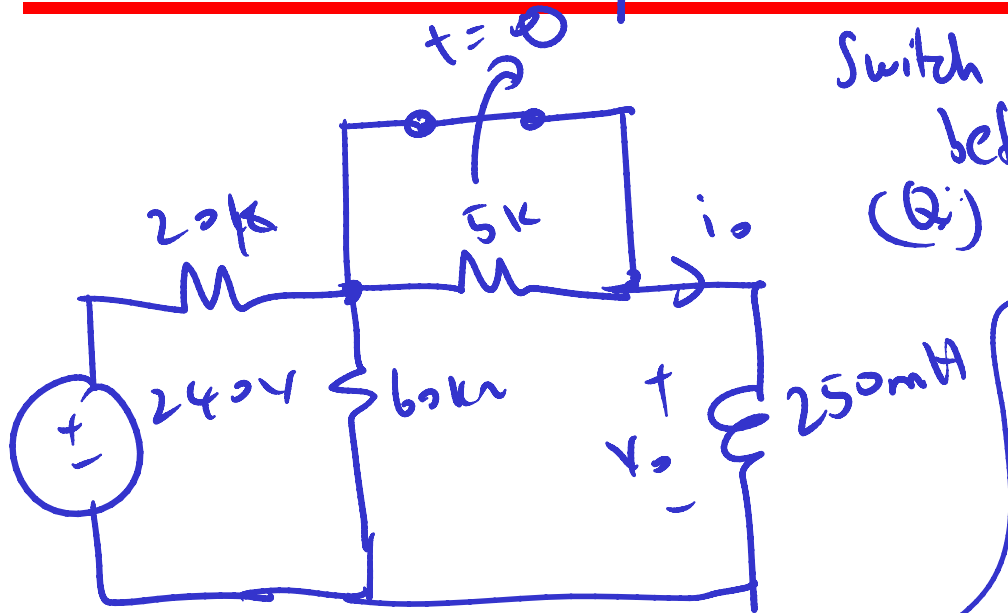


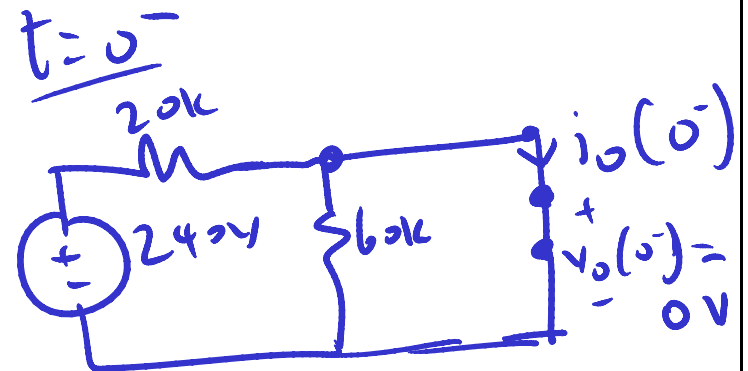Switch closed for a long time before opening @ $t=0$
 (Q) find $i_o(t)$, $v_o(t)$, $t \geq 0$.




$$i_o(0^-) = 12 \text{ mA} = \frac{24 \text{ V}}{2 \text{ k}} = i_o(0^+)$$

$$\tau = \frac{L}{R_m}, \quad R_m = (20 \text{ k} \parallel 60 \text{ k}) + 5 \text{ k} = 20 \text{ k} \text{??}$$

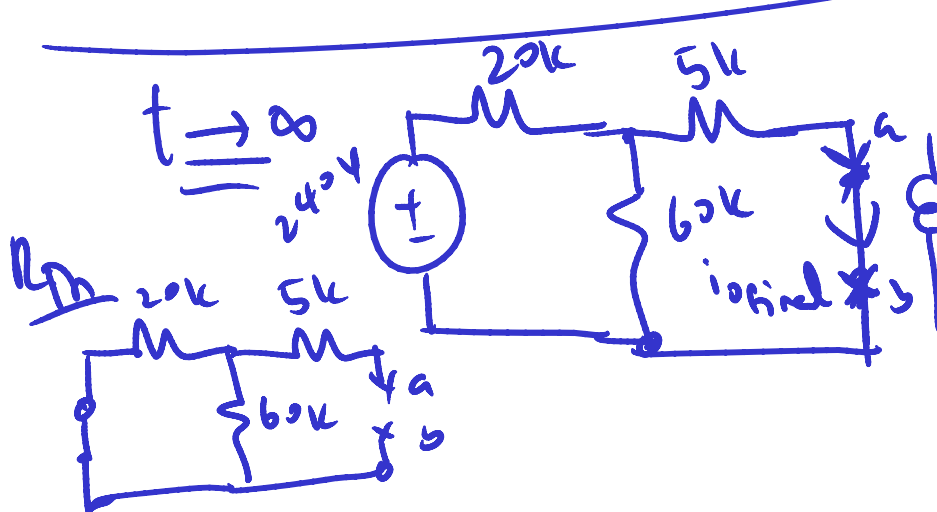


Problem 7.33 on p. 220

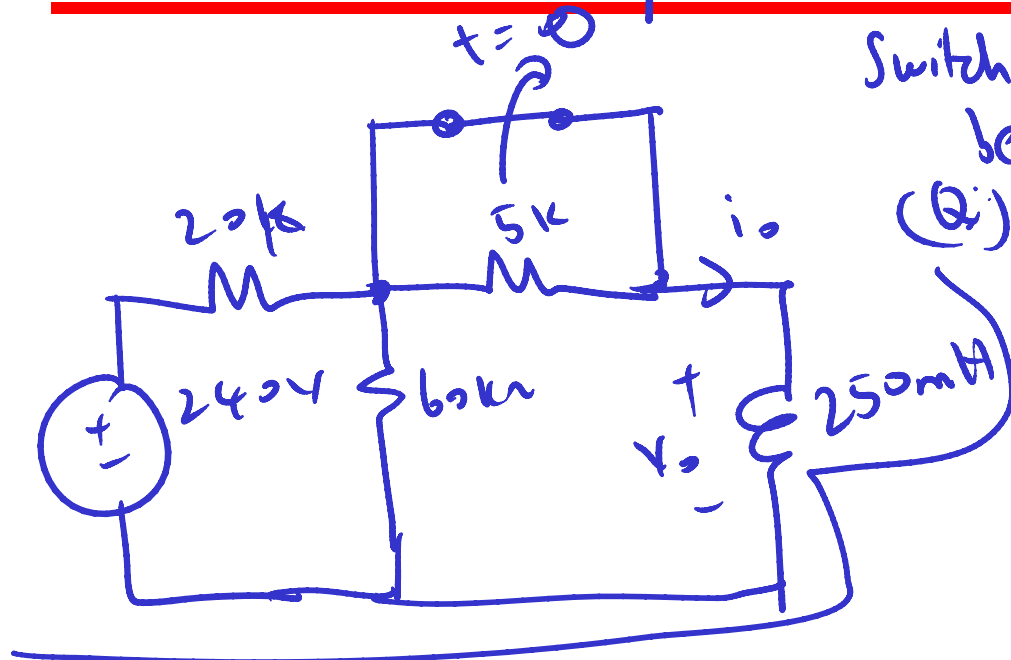

Switch closed for a long time before opening @ $t=0$

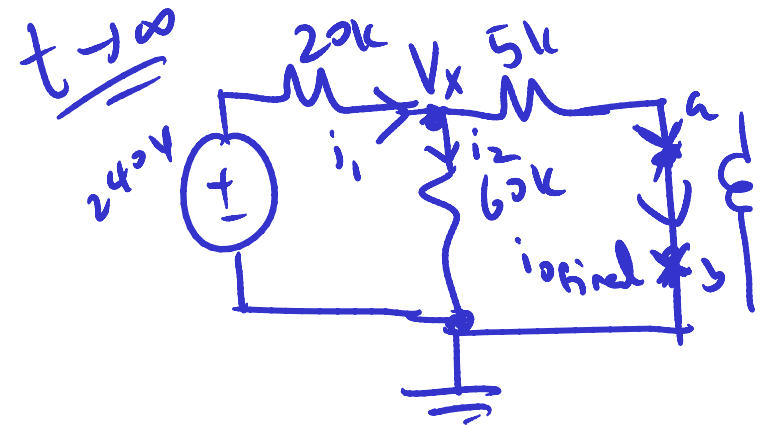(Q:) find $i_o(t)$, $v_o(t)$, $t \geq 0$.



$$i_{o \text{ final}} = \frac{V_x}{5k}$$

$$= \underline{\underline{9 \text{ mA}}}$$


Node @ V_x :

$$\frac{240 - V_x}{20k} = \frac{V_x}{60k} + \frac{V_x}{5k}$$

$$\Rightarrow (240 - V_x) \cdot 3 = V_x + 12V_x$$

$$\Rightarrow 3 \cdot 240 = 16V_x \Rightarrow V_x = \frac{240 \cdot 3}{16} = \underline{\underline{45V}}$$

Problem 7.33 on p. 220

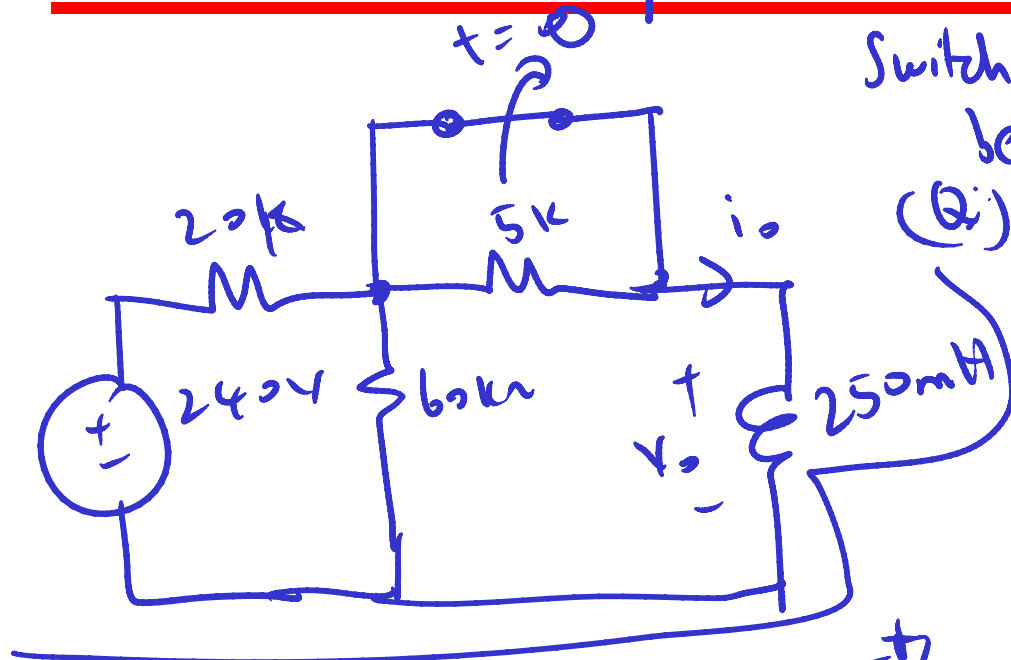

Switch closed for a long time before opening @ $t=0$

(Q) find $i_o(t)$, $v_o(t)$, $t \geq 0$.

$$i_{o \text{ initial}} = 12 \text{ mA}$$

$$i_{o \text{ final}} = 9 \text{ mA}$$


$$\tau = \frac{L}{R_{\text{th}}} = \frac{250 \text{ mH}}{2 \text{ k}} = 12.5 \text{ } \underline{\underline{\mu\text{s}}}$$

$$\therefore i_o(t) = i_{o \text{ final}} + (i_{o \text{ initial}} - i_{o \text{ final}}) e^{-t/\tau}$$

$$i_o(t) = 9 + 3 e^{-t/12.5 \mu\text{s}} \text{ mA}$$

$$v_o = L \frac{di_o}{dt} = L \left(3 e^{-t/12.5 \mu\text{s}} \times \frac{-1}{12.5 \mu\text{s}} \right) \times 10^{-3} \text{ volt}$$

Midterm Review (1) Power:

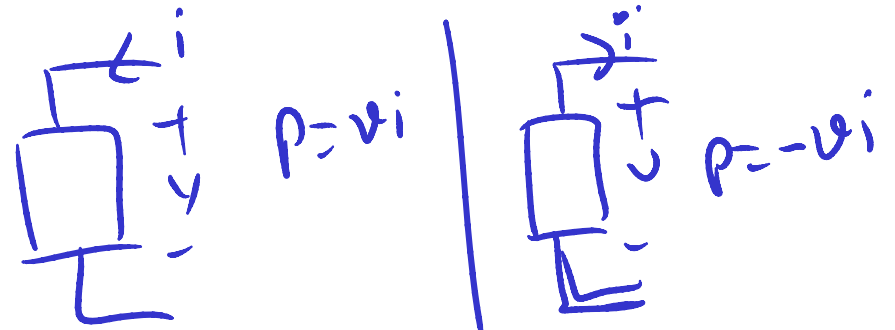


(2) KCL; KVL; $i = f(v)$ (i-v relationships)

(3) Nodal, Thevenin; Norton, Superposition, source transformations, maximum power transfer.

(4) AC/DC

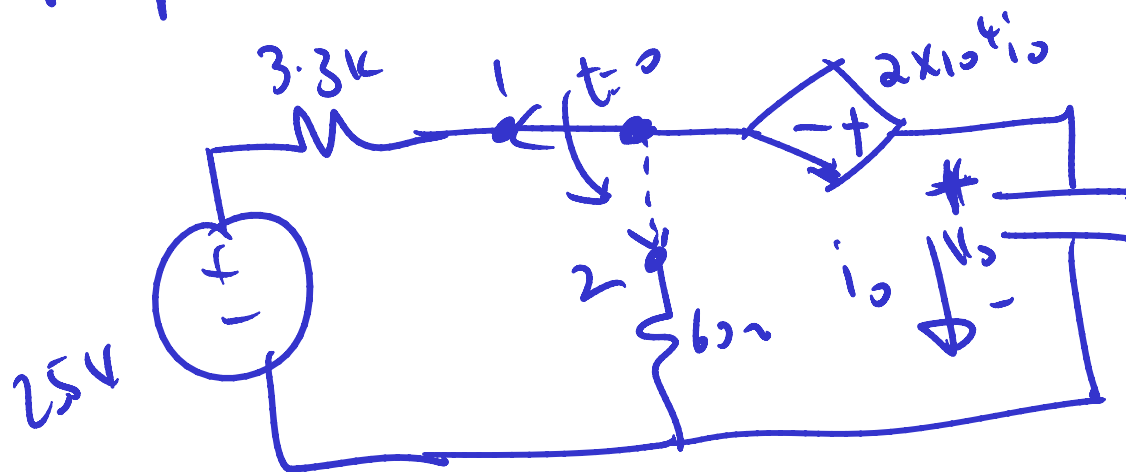Problem 7.27 on p. 269


Switch is in position 1 for a long time before moving to position 2 @ $t=0$. Find $i_o(t) \forall t \geq 0^+$



$$i_o = C \frac{dv_o}{dt}$$

$$v_o(t) = v_{of} + (v_{oi} - v_{of}) e^{-t/\tau}$$


$$v_{oi} = v_o(0^+) = v_o(0^-) = 25V$$

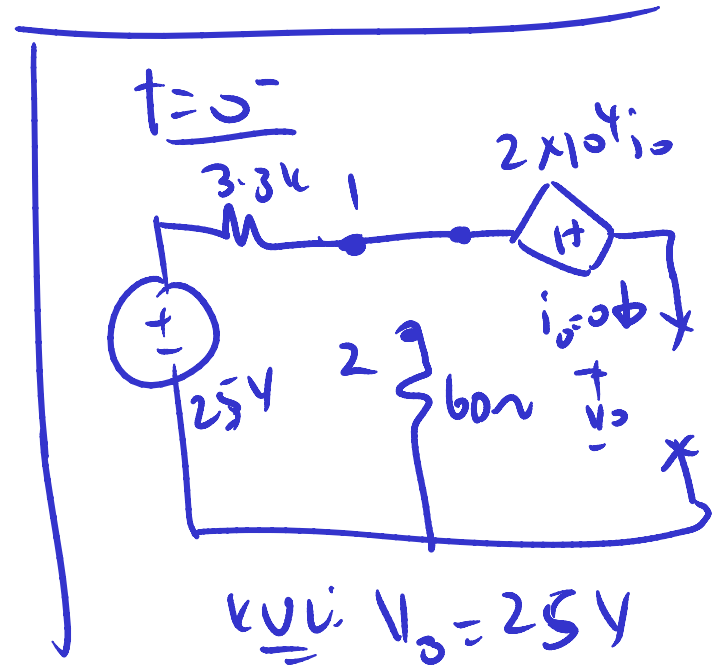

KVL: $v_o = 25V$


Problem 7.27 on p. 269

Switch is in position 1 for a long time before moving to position 2 @ $t=0$. Find $i_o(t) \forall t \geq 0^+$

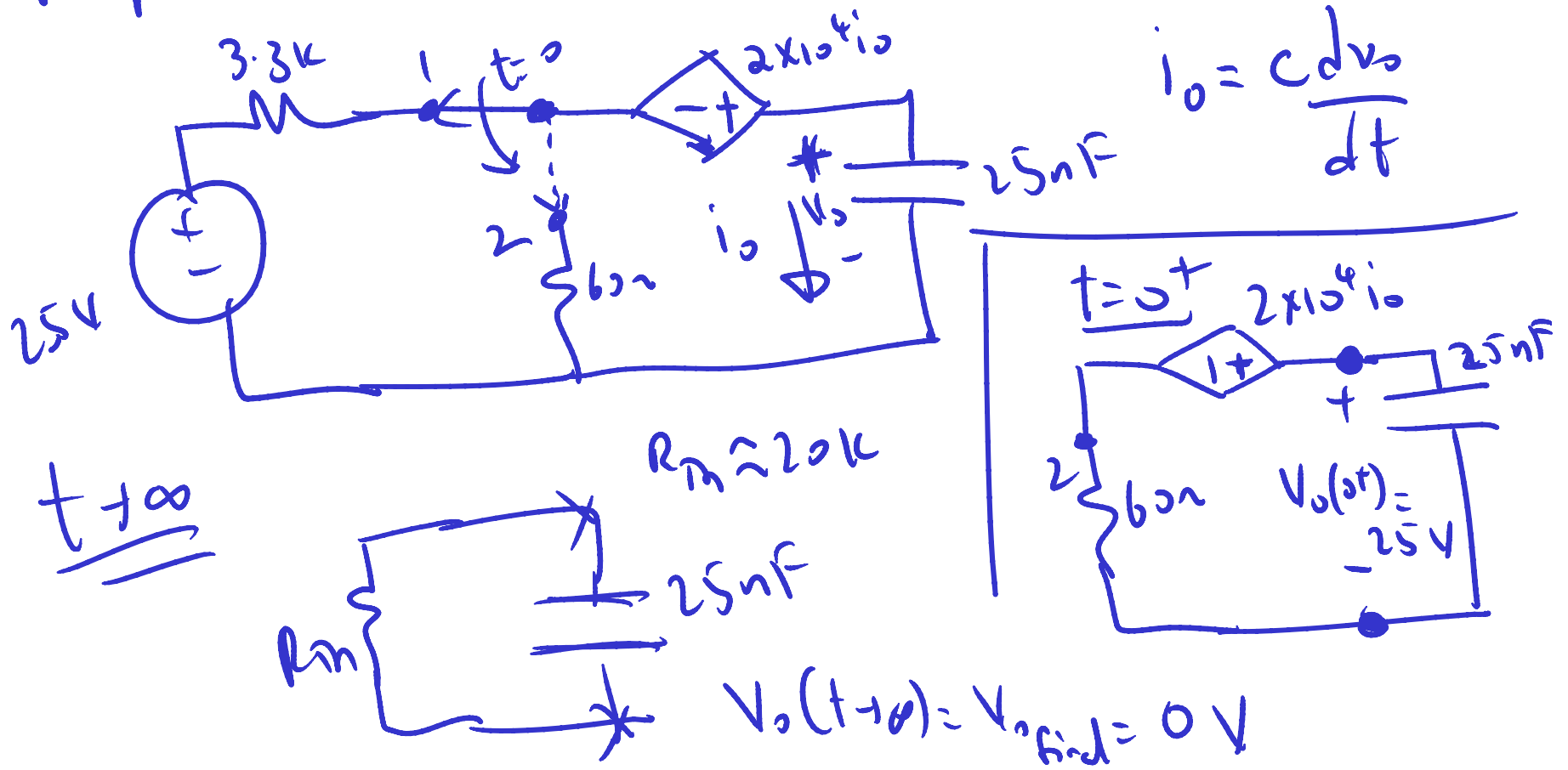

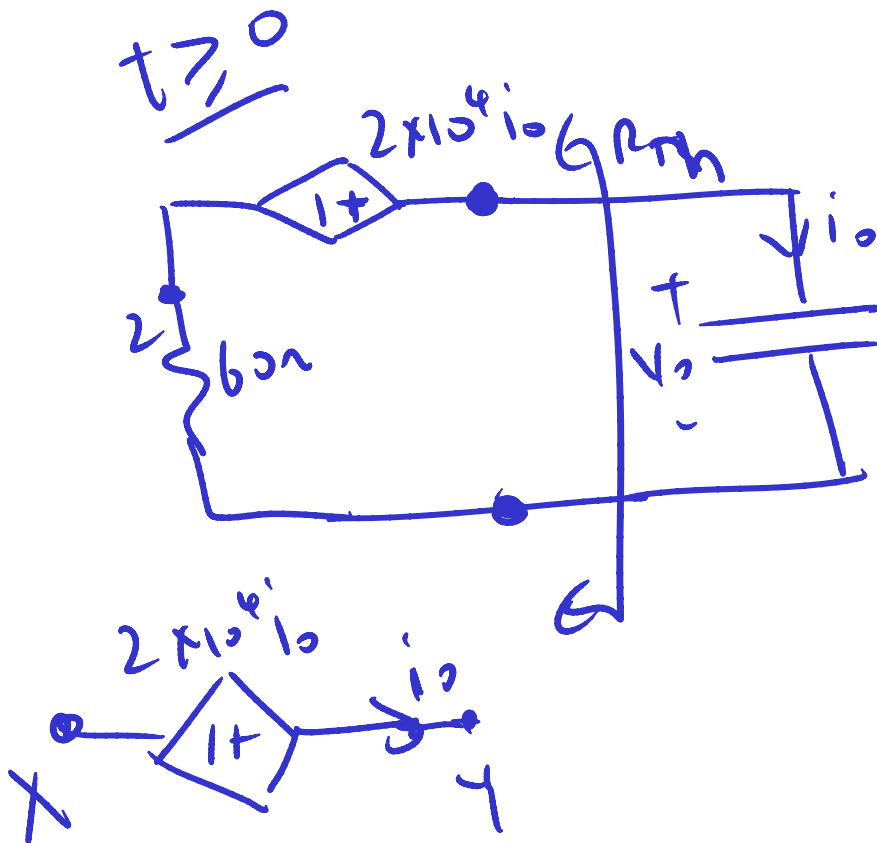Problem 7.27 on p. 269

Switch is in position 1 for a long time before moving to position 2 @ $t=0$. Find $i_o(t) \forall t \geq 0^+$




$$\begin{aligned}
 i_o &= C \frac{dv_o}{dt} \\
 &= C \frac{d}{dt} \left[v_{of} + (V_{oi} - v_{of}) e^{-t/\tau} \right] \\
 &= C \frac{d}{dt} \left[25 e^{-t/\tau} \right] \\
 &= \left(C \cdot 25 e^{-t/\tau} \cdot -\frac{1}{\tau} \right)
 \end{aligned}$$

$v_o = 1/2$

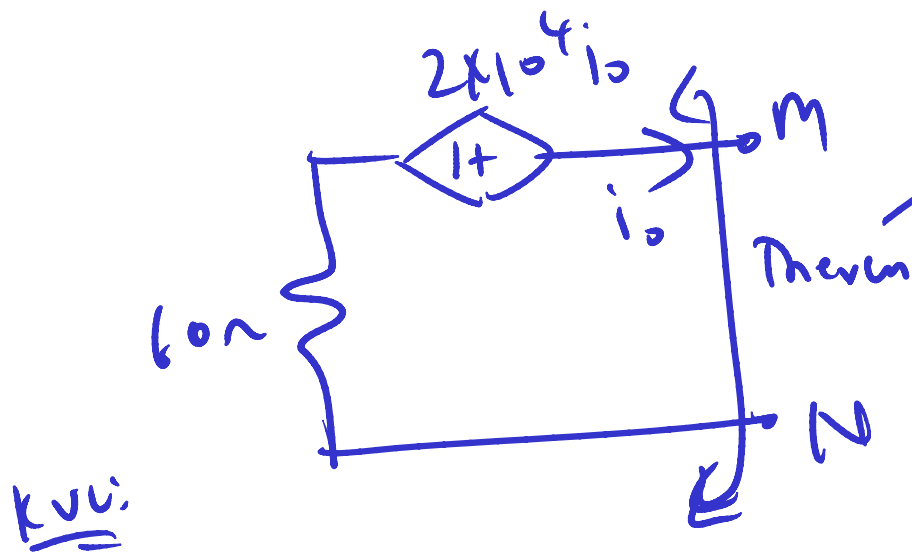
Problem 7.27 on p. 269

Switch is in position 1 for a long time before moving to position 2 @ $t=0$. Find $i_o(t) \forall t \geq 0^+$



$$V_T - (2 \times 10^4 i_o) - V_{60} = 0$$

$$\Rightarrow V_T - (2 \times 10^4 (-i_T)) - (60 i_T) = 0 \Rightarrow V_T = 60 i_T - 2 \times 10^4 i_T$$

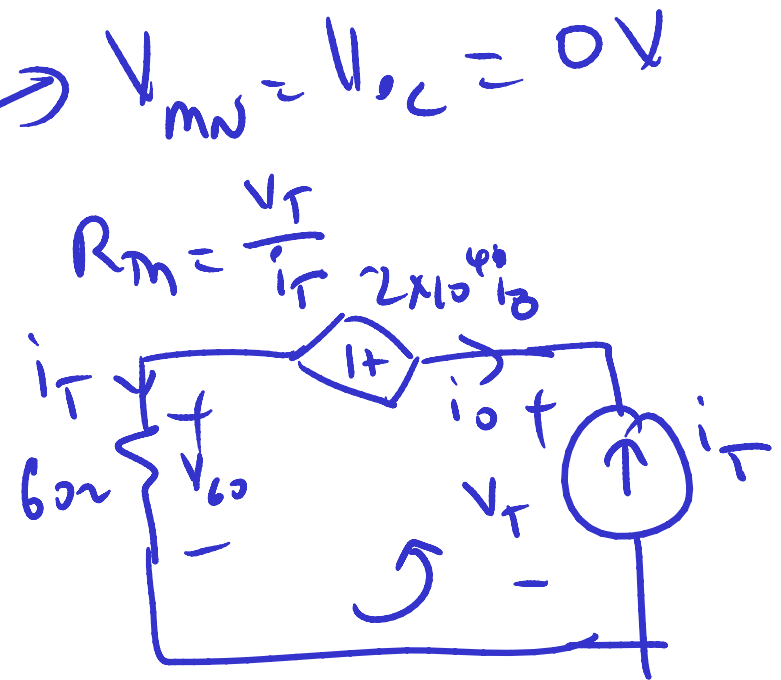

Problem 7.27 on p. 269

Switch is in position 1 for a long time before moving to position 2 @ $t=0$. Find $i_o(t) \forall t \geq 0^+$


$$\therefore R_{Th} = \frac{V_T}{i_T} \approx \underline{\underline{-20,000 \Omega}}$$

$\Rightarrow V_o \rightarrow \infty, i_o \rightarrow \infty$) next week,
 application to
 the feedback

KVL:

$$V_T - (2 \times 10^4 i_o) - V_{60} = 0$$

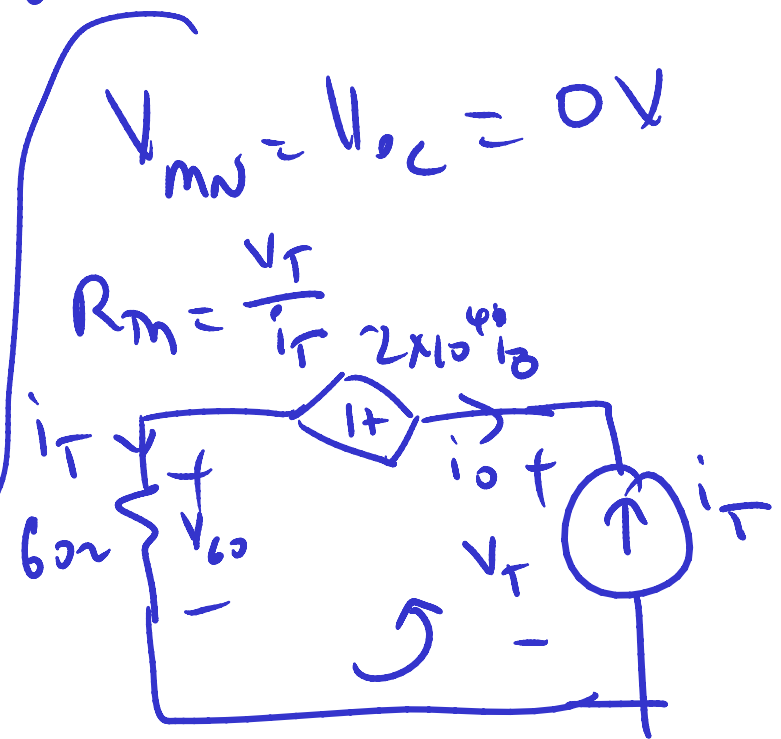
$$\Rightarrow V_T - (2 \times 10^4 (-i_T)) - (60 i_T) = 0 \Rightarrow V_T = 60 i_T - 2 \times 10^4 i_T$$




Digital Signals

We compute with pulses.

We send beautiful pulses in:

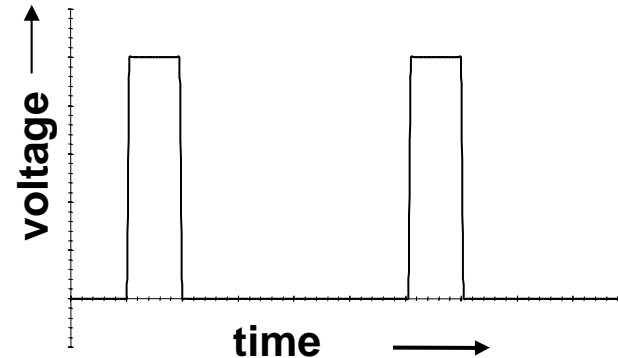

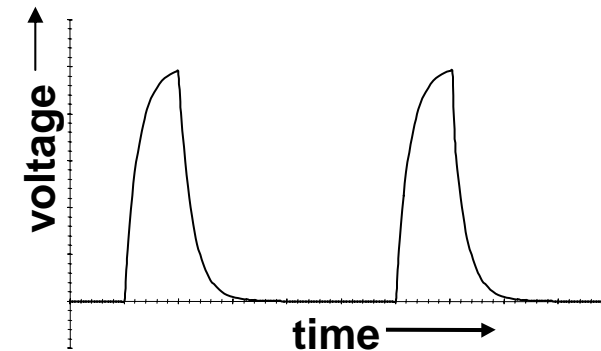But we receive lousy-looking pulses at the output:



Capacitor charging effects are responsible!

- Every node in a real circuit has capacitance; it's the charging of these capacitances that limits circuit performance (speed)