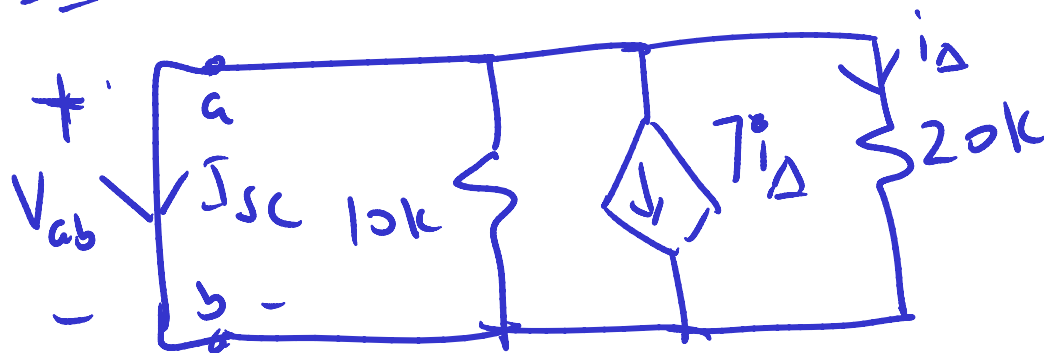


EE100Su08 Lecture #7 (July 9th 2008)


- Outline
 - Questions?
 - Finish Chapter #7
 - RC circuit: total response to a step input
 - RL circuit: total response to a step input
 - Application of Thevenin's Theorem to RC/RL circuits

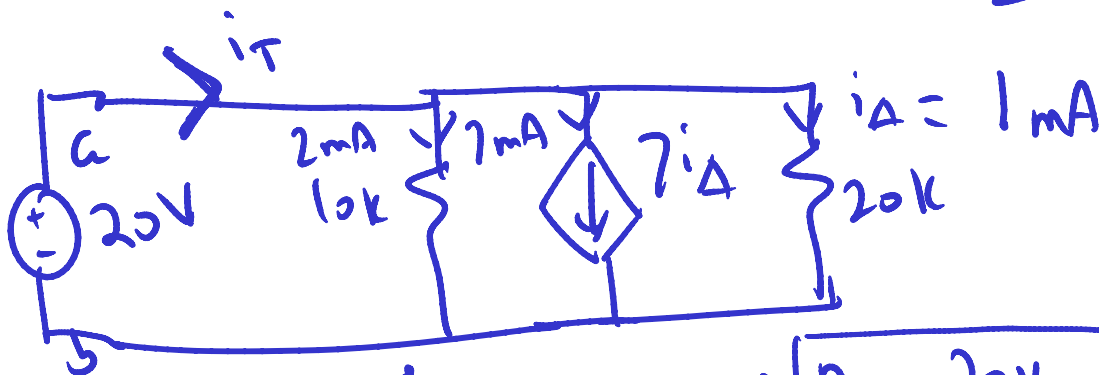Question: Thevenin equivalent for a circuit with only dependent sources (and resistors)

Ex:




$I_{sc} = ? \quad V_{ab} = 0 \Rightarrow i_D = \frac{V_{ab}}{20k} = 0$




$\therefore i_T = 10 \text{ mA} \Rightarrow R_m = \frac{20 \text{ V}}{10 \text{ mA}} = 2 \text{ k}$

(and resistors)

Find Thevenin equivalent at ab.

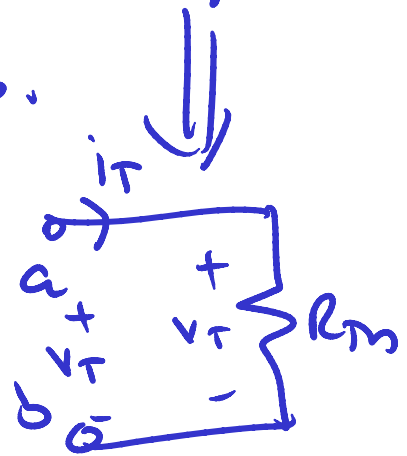

$R_m = \frac{V_T}{i_T}$

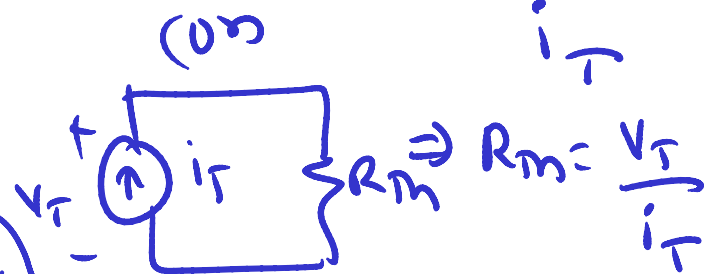

$R_m = \frac{V_T}{i_T}$

Summary

Capacitor

$$i = C \frac{dv}{dt}; w = \frac{1}{2} C v^2$$

v cannot change instantaneously

i can change instantaneously

Do not short-circuit a charged capacitor (-> infinite current!)

$$n \text{ cap.'s in series: } \frac{1}{C_{eq}} = \sum_{i=1}^n \frac{1}{C_i}$$

$$n \text{ cap.'s in parallel: } C_{eq} = \sum_{i=1}^n C_i$$

In steady state (not time-varying), a capacitor behaves like an open circuit.

Inductor

$$v = L \frac{di}{dt}; w = \frac{1}{2} L i^2$$

i cannot change instantaneously

v can change instantaneously

Do not open-circuit an inductor with current (-> infinite voltage!)



$$n \text{ ind.'s in series: } L_{eq} = \sum_{i=1}^n L_i$$

$$n \text{ ind.'s in parallel: } \frac{1}{L_{eq}} = \sum_{i=1}^n \frac{1}{L_i}$$

In steady state, an inductor behaves like a short circuit.

First-Order Circuits

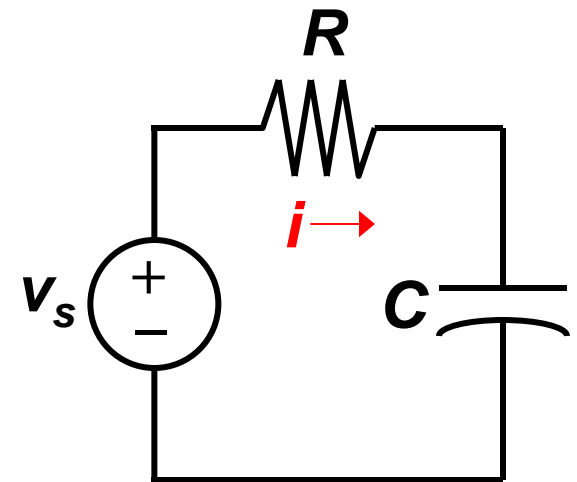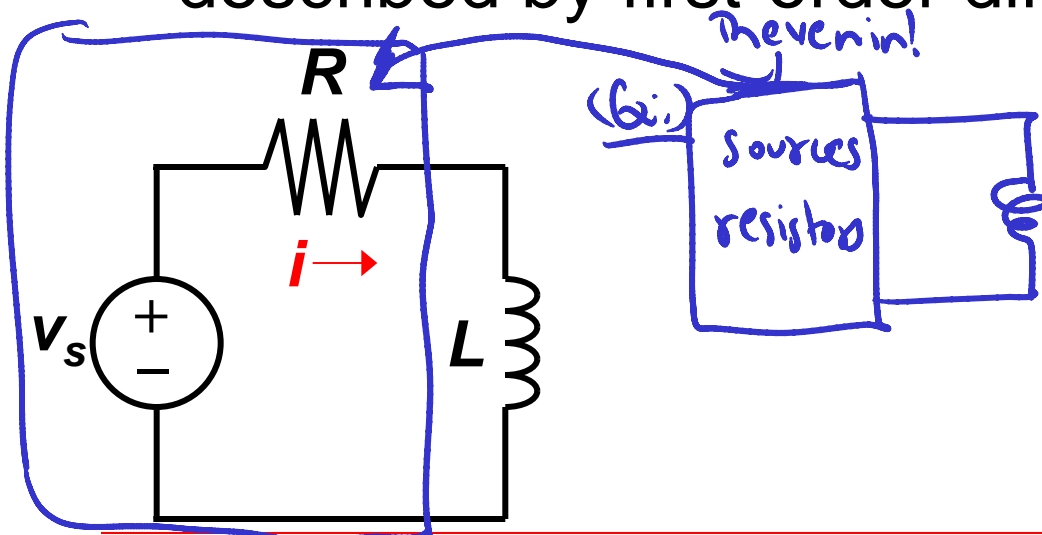- A circuit that contains only sources, resistors and an inductor is called an **RL circuit**.
- A circuit that contains only sources, resistors and a capacitor is called an **RC circuit**.
- RL and RC circuits are called first-order circuits because their voltages and currents are described by first-order differential equations.




Response of a Circuit

- ***Transient response*** of an RL or RC circuit is
 - Behavior when voltage or current source are **suddenly** applied to or removed from the circuit due to switching.
 - Temporary behavior
- ***Steady-state response (aka. forced response)***
 - Response that persists long after transient has decayed
- ***Natural response*** of an RL or RC circuit is
 - Behavior (*i.e.*, current and voltage) when stored energy in the inductor or capacitor is released to the resistive part of the network (containing no independent sources).


Natural Response Summary

RL Circuit

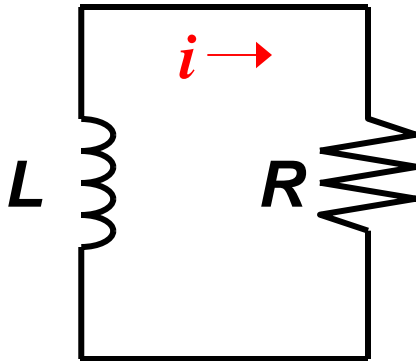


- Inductor current cannot change instantaneously
- In steady state, an inductor behaves like a short circuit.

RC Circuit

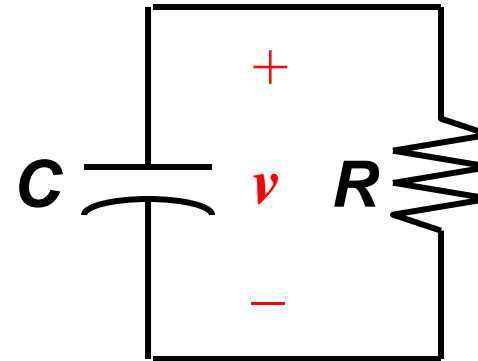

- Capacitor voltage cannot change instantaneously
- In steady state, a capacitor behaves like an open circuit


First Order Circuits

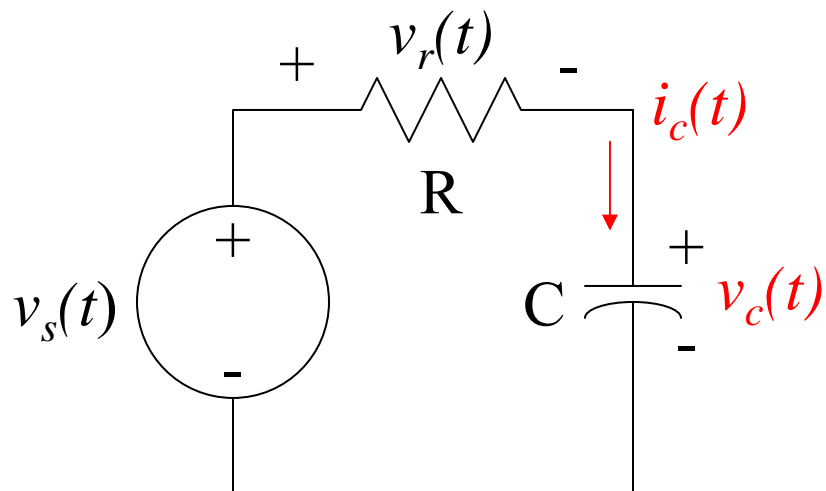

KVL around the loop:

$$v_r(t) + v_c(t) = v_s(t)$$
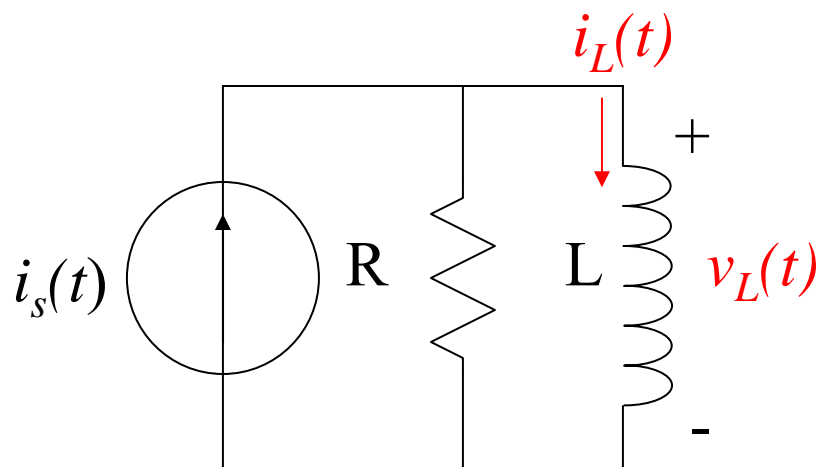
$$RC \frac{dv_c(t)}{dt} + v_c(t) = v_s(t)$$




KCL at the node:

$$\frac{v(t)}{R} + \frac{1}{L} \int_{-\infty}^t v(x) dx = i_s(t)$$

$$\frac{L}{R} \frac{di_L(t)}{dt} + i_L(t) = i_s(t)$$

Solution of RC circuit:

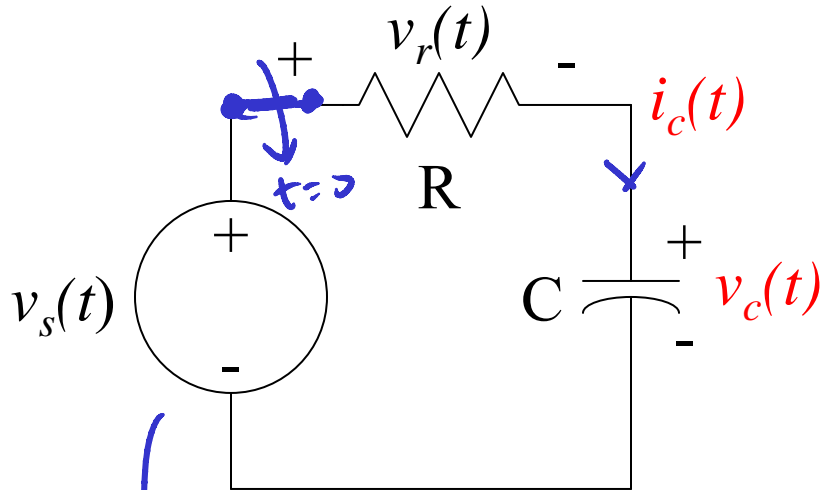


(Q:) Find $v_c(t)$, $t > 0$

$$v_c(0) = v_{\text{initial}}$$

KVL:
$$v_s = v_r + v_c$$


$$\Rightarrow v_s(t) = iR + v_c(t)$$
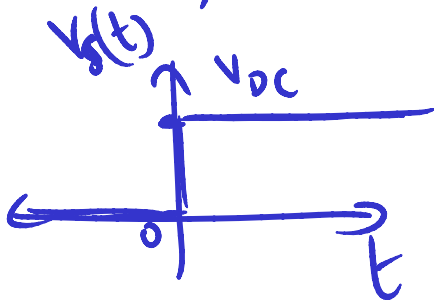
$$\Rightarrow v_s(t) = C \frac{dv_c(t)}{dt} + v_c(t)$$




$$\Rightarrow \boxed{v_s(t) = RC \frac{dv_c}{dt} + v_c} \quad v_c(0) = v_{\text{initial}}$$

Solution of RC circuit:

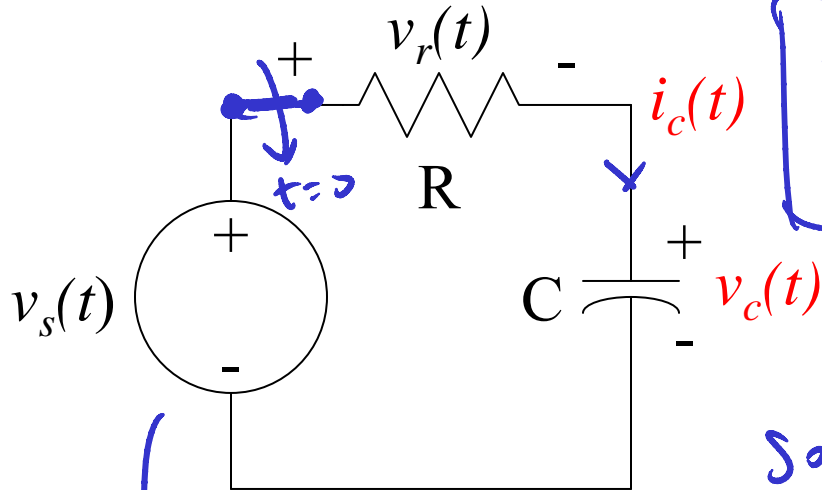

$$V_s(t) = RC \frac{dv_c}{dt} + v_c(t) \quad v_c(0) = v_{\text{initial}}$$

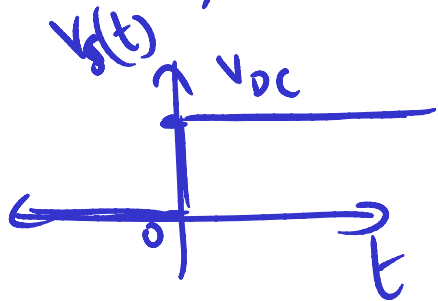lets try & guess the solution: suppose $v_s(t) = 0$




$$RC \frac{dv_c}{dt} = -v_c$$

$$\text{Try: } v_c(t) = v_0 e^{-t/RC} \quad [v_c(0) = v_0]$$

$$\Rightarrow \frac{dv_c}{dt} = v_0 e^{-t/RC} \cdot -\frac{1}{RC} = -\frac{v_0}{RC} e^{-t/RC}$$

Solution of RC circuit:

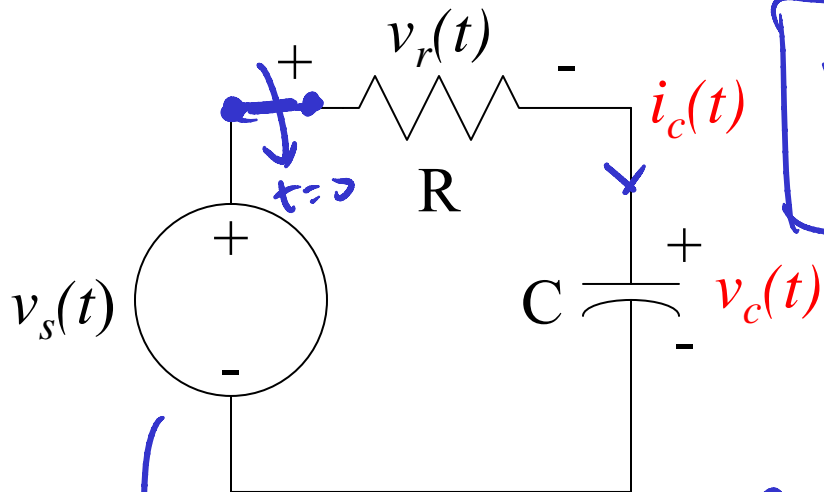

$$V_s(t) = RC \frac{dv_c}{dt} + v_c(t) \quad v_c(0) = v_{\text{initial}}$$


$$v_c(t) = A + B e^{-t/\tau} \quad \text{--- (1)}$$

Goal: Find A, B, τ


(1) must satisfy initial conditions

$$v_c(0) = v_{\text{initial}} = A + B$$

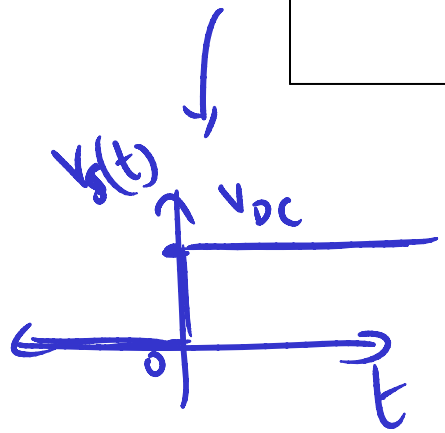(2) Consider $\lim_{t \rightarrow \infty} v_c(t) = A$




Solution of RC circuit:

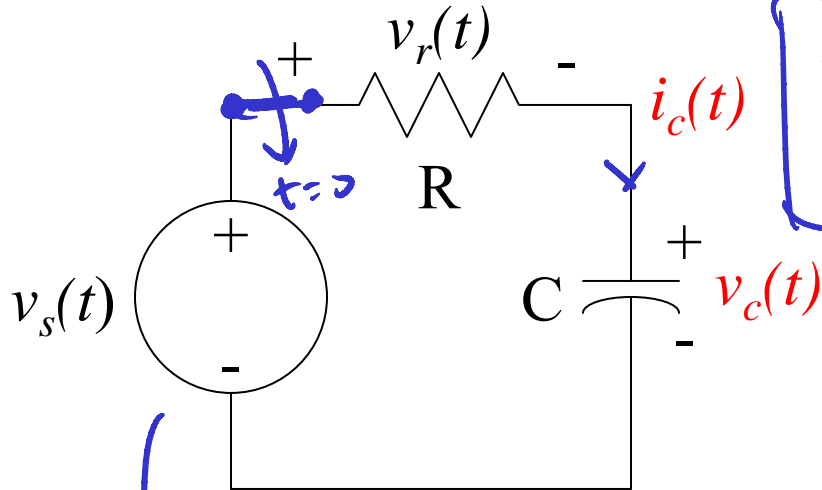

$$V_s(t) = RC \frac{dv_c}{dt} + v_c(t) \quad v_c(0) = v_{\text{initial}}$$
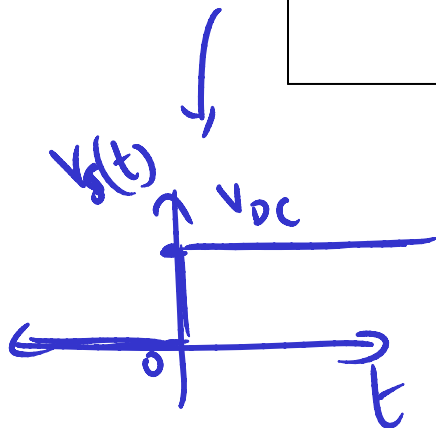
$$v_c(t) = A + B e^{-t/\tau} \quad \text{--- (1)}$$




$$v_c(0) \Rightarrow A + B = v_{\text{initial}} \text{ (specified)}$$

$v_c(t \rightarrow \infty) \Rightarrow$ (capacitor charges up to v_{oc} (constant))

$$\Rightarrow i(t \rightarrow \infty) = C \frac{dv_c}{dt} = C \frac{d(v_{oc})}{dt} = 0$$







Solution of RC circuit:

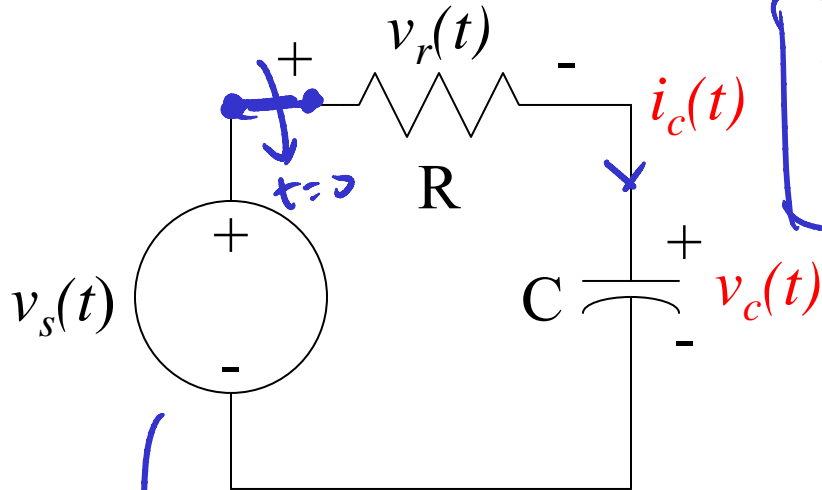


$$V_s(t) = RC \frac{dv_c}{dt} + v_c(t) \quad v_c(0) = v_{\text{initial}}$$
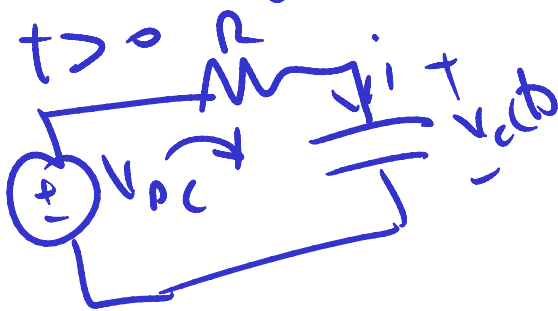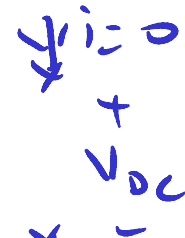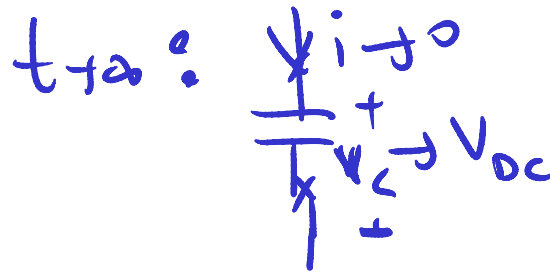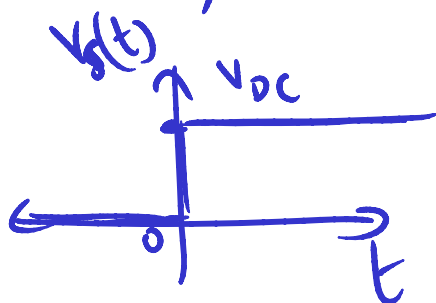
$$v_c(t) = A + B e^{-t/\tau} \quad \text{--- (1)}$$



\therefore As $t \rightarrow \infty$:

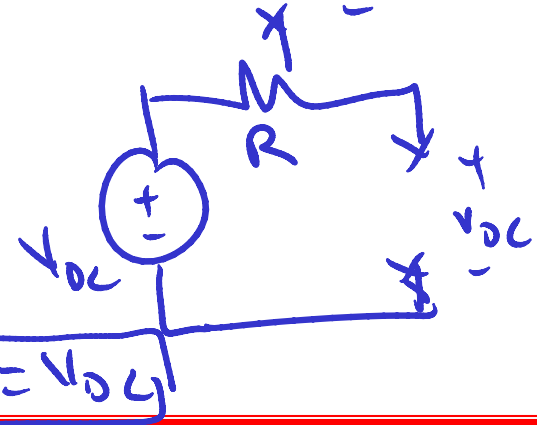$\therefore v_c(t \rightarrow \infty) = V_{OC}$
 \Rightarrow $A = V_{OC}$



$$V_c(t) = A + B e^{-t/\tau}$$

$$V_c(0) = A + B = V_{\text{initial}}$$


$$V_c(t \rightarrow \infty) = A = V_{\text{DC}}$$

$$\therefore B = V_{\text{initial}} - A$$

$$= V_{\text{initial}} - V_{\text{DC}} e^{-t/\tau}$$

$$\therefore V_c(t) = V_{\text{DC}} + (V_{\text{initial}} - V_{\text{DC}}) e^{-t/\tau}$$
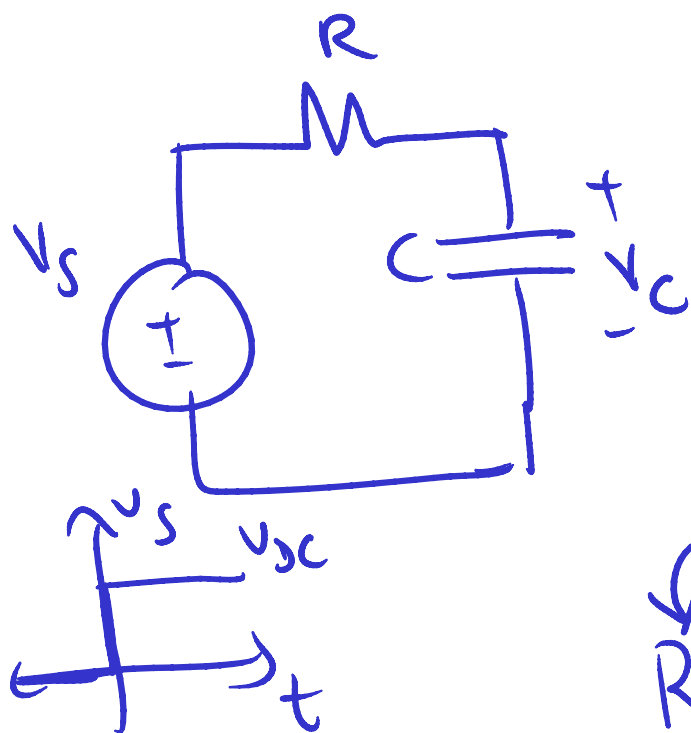
$$RC \frac{dv_c}{dt} + v_c = v_s = V_{\text{DC}} \quad (t \geq 0)$$



$$RC \frac{dv_c}{dt} + v_c = v_{DC},$$

$$v_c(t) = v_{DC} + (v_{initial} - v_{DC}) e^{-t/\alpha}$$

$$\Rightarrow RC \left[(v_{initial} - v_{DC}) e^{-t/\alpha} \cdot \left(-\frac{1}{\alpha}\right) \right] + \left[v_{DC} + (v_{initial} - v_{DC}) e^{-t/\alpha} \right] = v_{DC}$$

$$\Rightarrow \boxed{\alpha = RC}$$

$$\therefore \boxed{v_c(t) = v_{DC} + (v_{initial} - v_{DC}) e^{-\frac{t}{RC}} \quad t \geq 0}$$

$$\tau = RC$$

$$V_c(t) = V_{oc} + (V_{initial} - V_{oc}) e^{-\frac{t}{RC}} \quad t \geq 0$$

Note: (1) τ = seconds (time)

$$(2) RC = \frac{V}{i} \cdot \frac{q}{V}$$

$$\Rightarrow \tau = \left(\frac{V}{i} \right) \cdot \left(\frac{q}{V} \right) = \left(\frac{q}{dq/dt} \right) = \text{time!}$$

Significance: $\tau \triangleq$ Time constant $= \tau = RC$

$$\tau = RC$$

$$V_c(t) = V_{DC} + (V_{initial} - V_{DC}) e^{-\frac{t}{\tau}} \quad t \geq 0 \quad \text{volts}$$

Consider: $t = 5\tau$

$$\therefore V_c(t=5\tau) = V_{DC} + (V_{initial} - V_{DC}) e^{-5}$$

$\approx V_{DC}$

\Rightarrow 5 time constants, circuit has reached steady-state!

Some observations:

$$(1) \quad \tau = RC$$

$$\therefore V_c(t) = \underbrace{V_{oc}} + \underbrace{(V_{initial} - V_{oc}) e^{-\frac{t}{\tau}}}_{\text{volb}} \quad t \geq 0$$


⇓
①

⇓
②


Notice: ② is the transient response, ① is the steady-state response.

$$(2) \quad V_c = V_{dc} (1 - e^{-t/\tau}) + V_{initial} e^{-t/\tau} \quad (1)$$

Circuit:

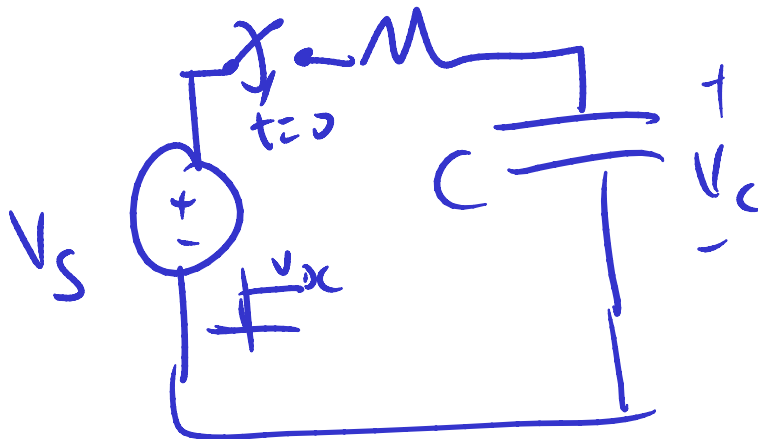

Suppose $V_{dc} = 0 \quad t \geq 0$

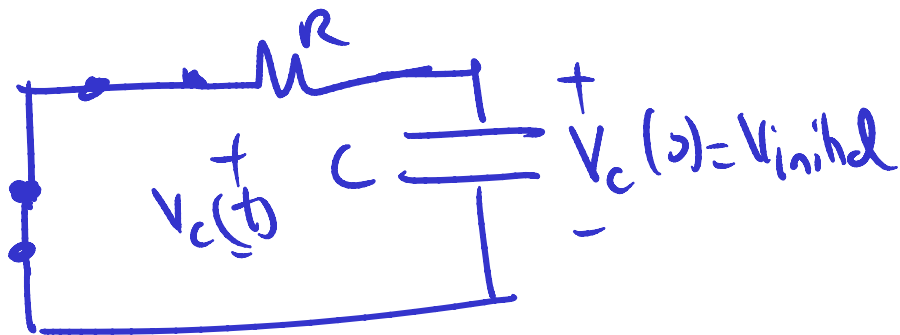


$$V_c(t) = V_{initial} e^{-t/\tau}$$

(From (1), $V_{dc} = 0$)

Observations (contd.)

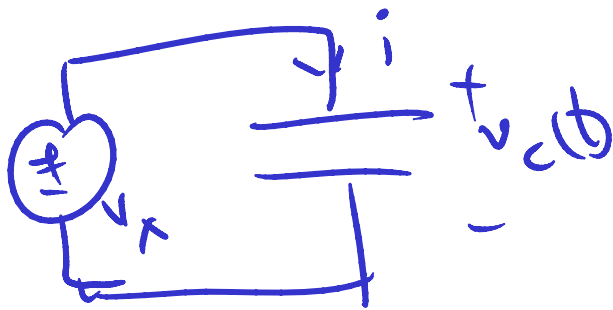(3) Can you physically change the voltage across a capacitor instantaneously?



$$i = C \frac{dv_c}{dt}$$


$$i = C \frac{\Delta v}{\Delta t}$$

$\Rightarrow i \rightarrow \infty$ / Bad idea

\Rightarrow Capacitors maintain voltage across its terminals across discontinuous

Observations (contd.)

(3)

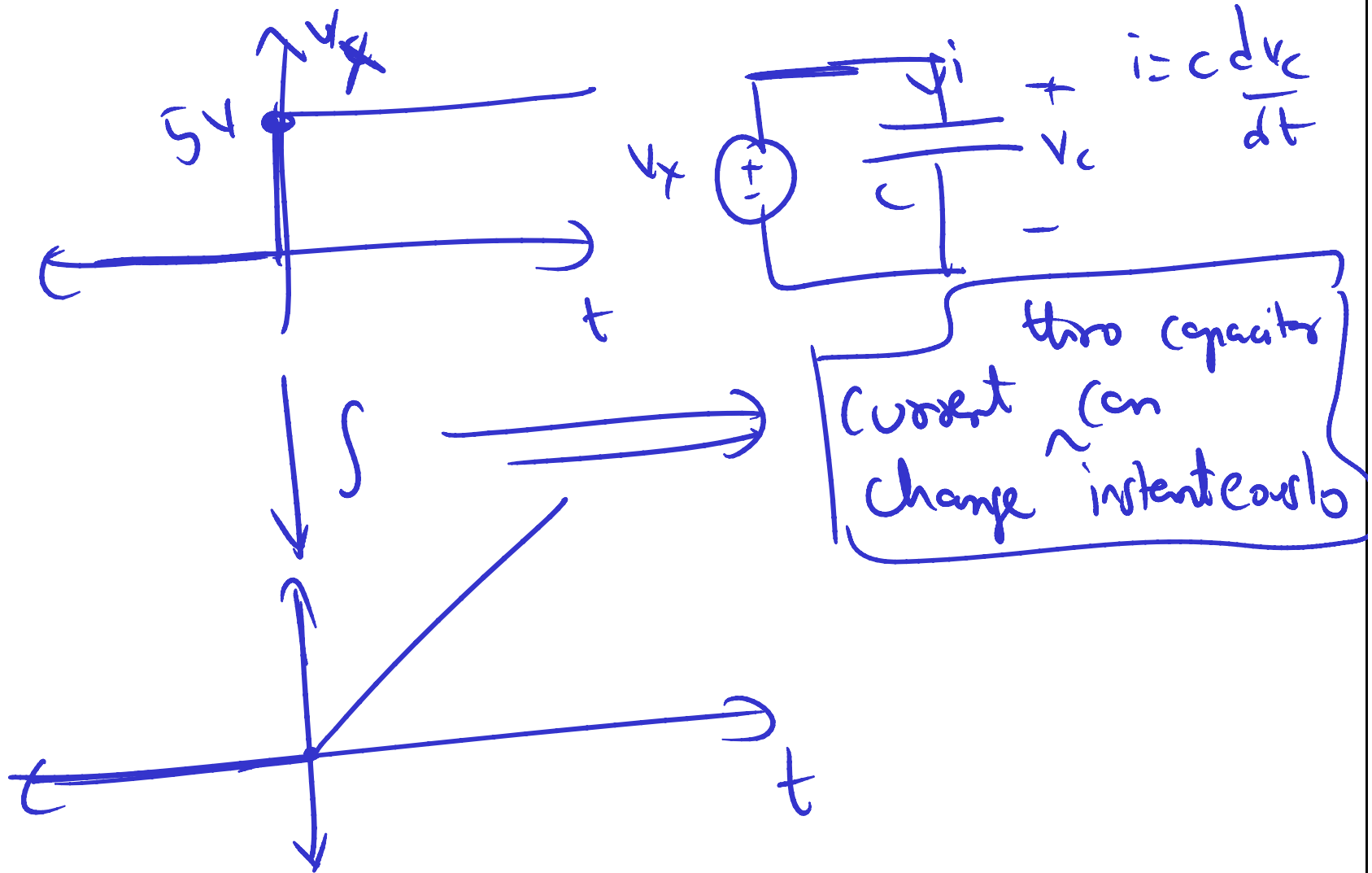

Procedure for Finding RC/RL Response

1. Identify the variable of interest

- For RL circuits, it is usually the inductor current $i_L(t)$
- For RC circuits, it is usually the capacitor voltage $v_c(t)$

2. Determine the initial value (at $t = t_0^-$ and t_0^+) of the variable

- Recall that $i_L(t)$ and $v_c(t)$ are continuous variables:

$$i_L(t_0^+) = i_L(t_0^-) \quad \text{and} \quad v_c(t_0^+) = v_c(t_0^-)$$

- Assuming that the circuit reached steady state before t_0 , use the fact that **an inductor behaves like a short circuit in steady state** or that **a capacitor behaves like an open circuit in steady state**

Procedure (cont'd)

3. Calculate the final value of the variable (its value as $t \rightarrow \infty$)

- Again, make use of the fact that **an inductor behaves like a short circuit in steady state ($t \rightarrow \infty$)** or that **a capacitor behaves like an open circuit in steady state ($t \rightarrow \infty$)**


4. Calculate the time constant for the circuit

$\tau = L/R$ for an RL circuit, where R is the Thévenin equivalent resistance “seen” by the inductor

$\tau = RC$ for an RC circuit where R is the Thévenin equivalent resistance “seen” by the capacitor

Natural Response of an RC Circuit

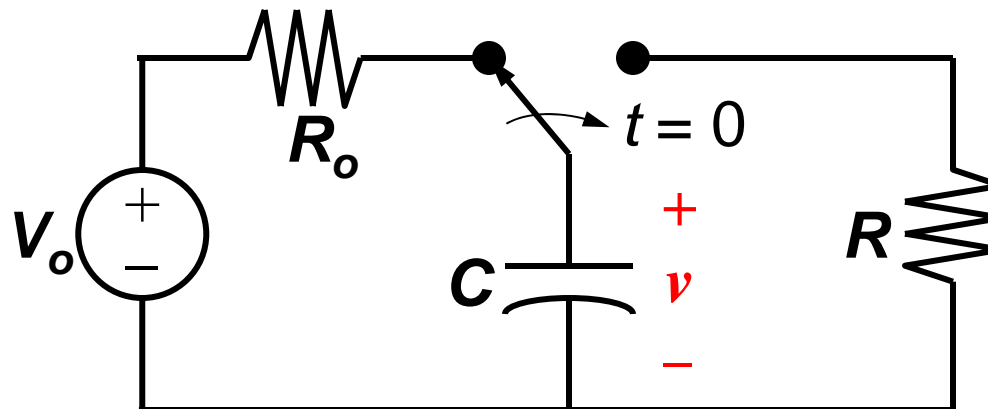- Consider the following circuit, for which the switch is closed for $t < 0$, and then opened at $t = 0$:



Notation:


0^- is used to denote the time just prior to switching

0^+ is used to denote the time immediately after switching

- The voltage on the capacitor at $t = 0^-$ is V_o

Solving for the Voltage ($t \geq 0$)


- For $t > 0$, the circuit reduces to

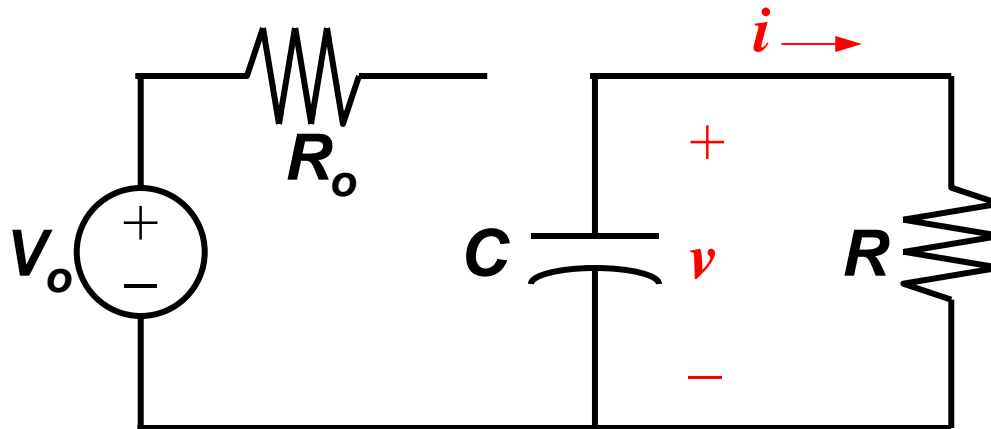

- Applying KCL to the RC circuit:

- Solution:
$$v(t) = v(0)e^{-t/RC}$$

Solving for the Current ($t > 0$)

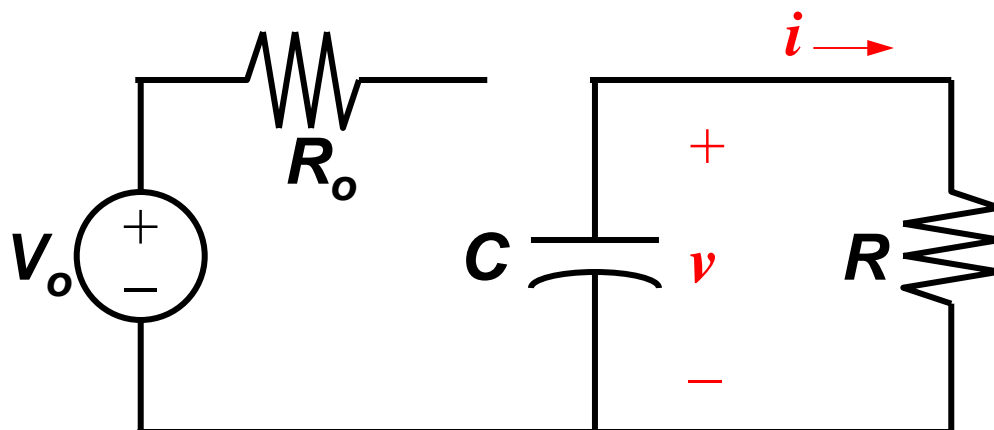


$$v(t) = V_o e^{-t/RC}$$

- Note that the current changes abruptly:
 $i(0^-) = 0$

$$\text{for } t > 0, i(t) = \frac{v}{R} = \frac{V_o}{R} e^{-t/RC}$$

$$\Rightarrow i(0^+) = \frac{V_o}{R}$$

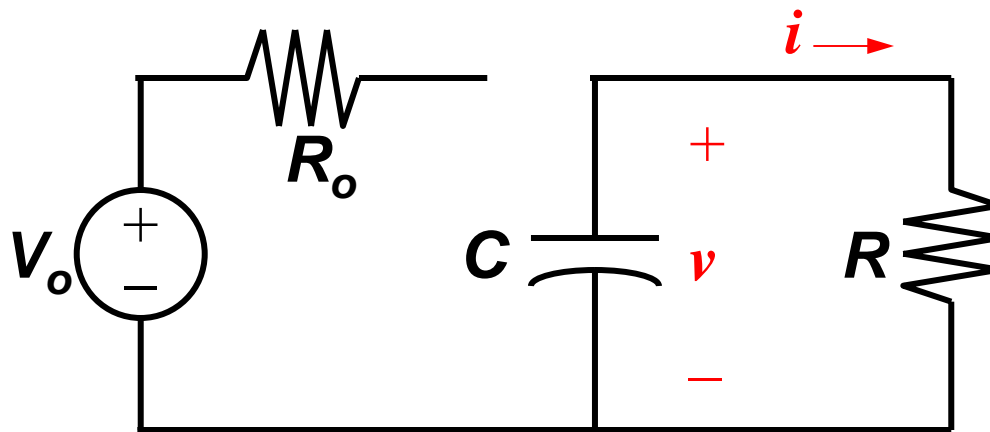Solving for Power and Energy Delivered ($t > 0$)



$$v(t) = V_o e^{-t/RC}$$


$$p = \frac{v^2}{R} = \frac{V_o^2}{R} e^{-2t/RC}$$

$$w = \int_0^t p(x) dx = \int_0^t \frac{V_o^2}{R} e^{-2x/RC} dx$$

$$= \frac{1}{2} C V_o^2 (1 - e^{-2t/RC})$$

Natural Response of an RL Circuit

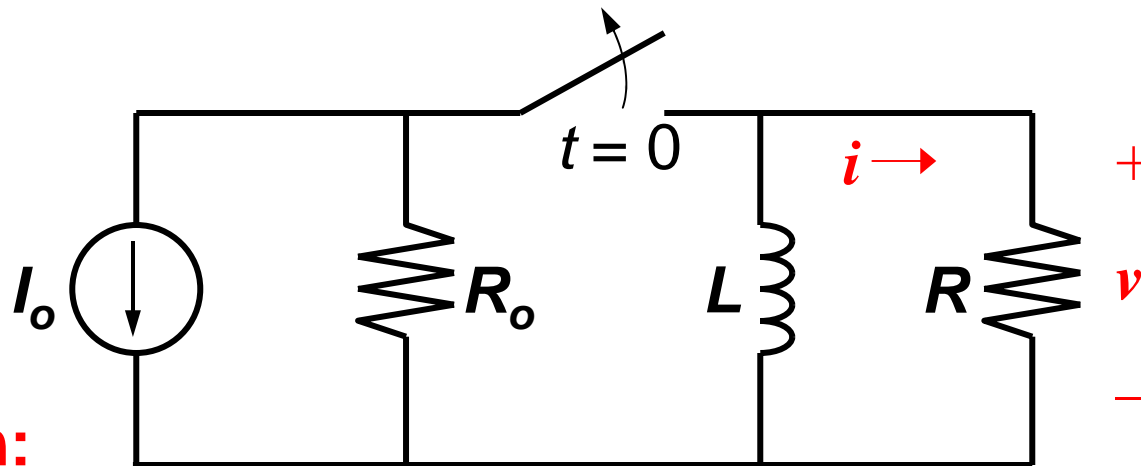- Consider the following circuit, for which the switch is closed for $t < 0$, and then opened at $t = 0$:



Notation:


0^- is used to denote the time just prior to switching

0^+ is used to denote the time immediately after switching

- $t < 0$ the entire system is at steady-state; and the inductor is \rightarrow like short circuit
- The current flowing in the inductor at $t = 0^-$ is I_o and V across is 0.


Solving for the Current ($t \geq 0$)

- For $t > 0$, the circuit reduces to

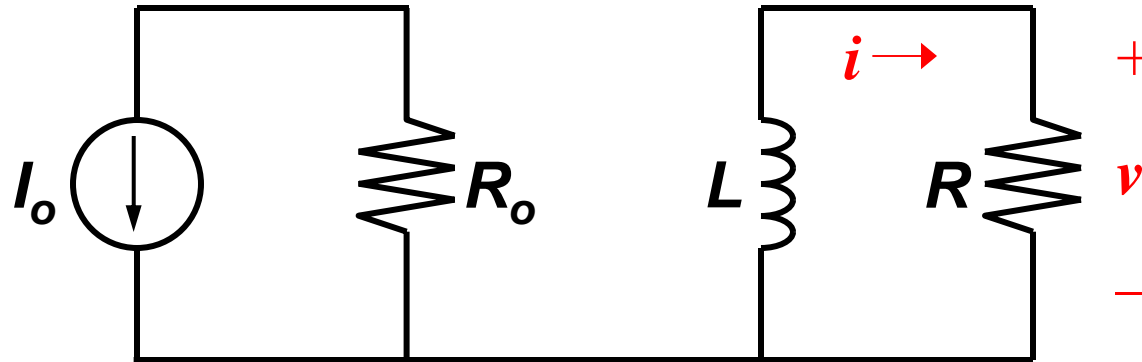

- Applying KVL to the LR circuit:
- $v(t) = i(t)R$
- At $t = 0^+$, $i = I_0$,
- At arbitrary $t > 0$, $i = i(t)$ and $v(t) = -L \frac{di(t)}{dt}$
- Solution: $i(t) = i(0)e^{-(R/L)t} = I_0 e^{-(R/L)t}$

Solving for the Voltage ($t > 0$)

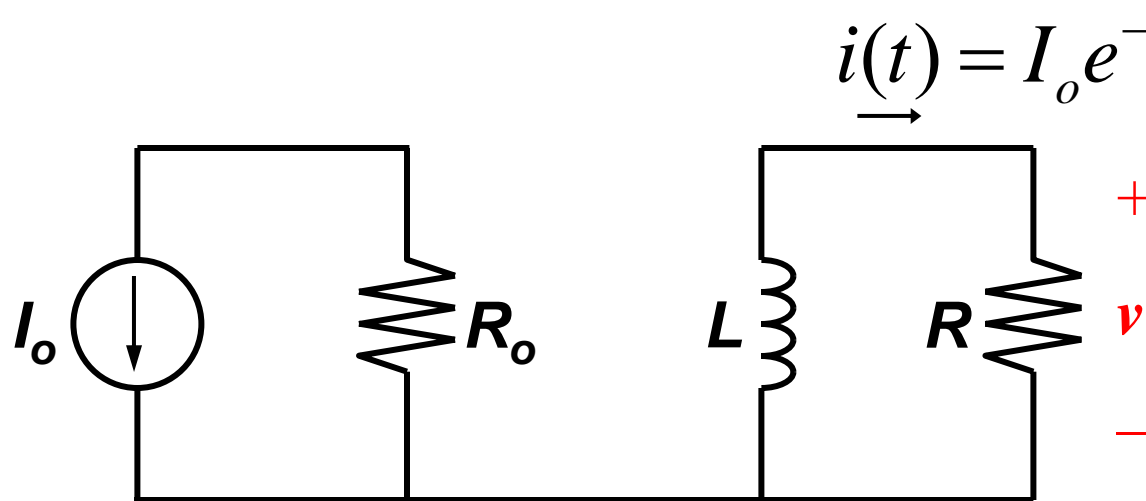


- Note that the **voltage** changes abruptly:
 $v(0^-) = 0$

$$\text{for } t > 0, \quad v(t) = iR = I_o R e^{-(R/L)t}$$

$$\Rightarrow v(0^+) = I_o R$$

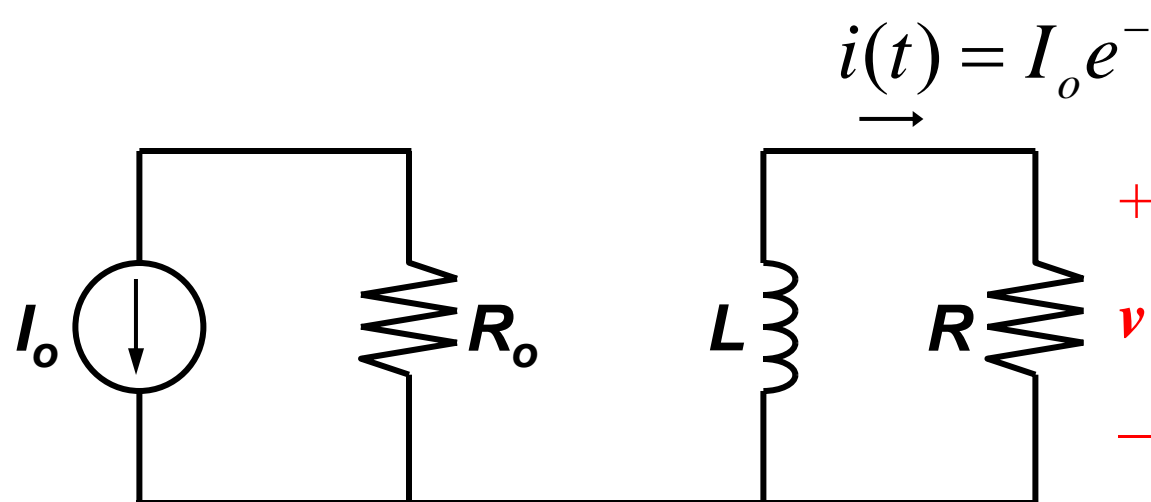Solving for Power and Energy Delivered ($t > 0$)




$$p = i^2 R = I_o^2 R e^{-2(R/L)t}$$

$$w = \int_0^t p(x) dx = \int_0^t I_o^2 R e^{-2(R/L)x} dx$$

$$= \frac{1}{2} L I_o^2 \left(1 - e^{-2(R/L)t} \right)$$

Natural Response Summary

RL Circuit

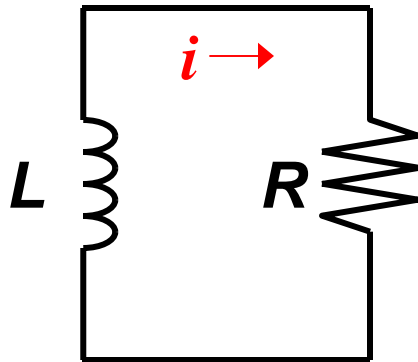


- **Inductor current** cannot change instantaneously

$$i(0^-) = i(0^+)$$

$$i(t) = i(0)e^{-t/\tau}$$

- time constant $\tau = \frac{L}{R}$

RC Circuit

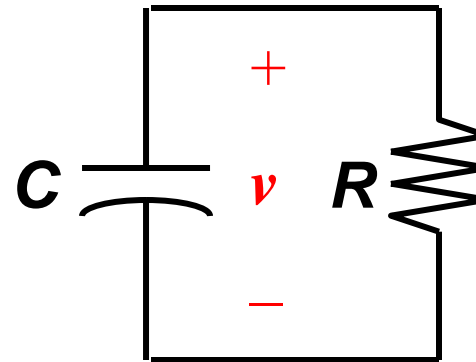


- **Capacitor voltage** cannot change instantaneously

$$v(0^-) = v(0^+)$$

$$v(t) = v(0)e^{-t/\tau}$$


- time constant $\tau = RC$

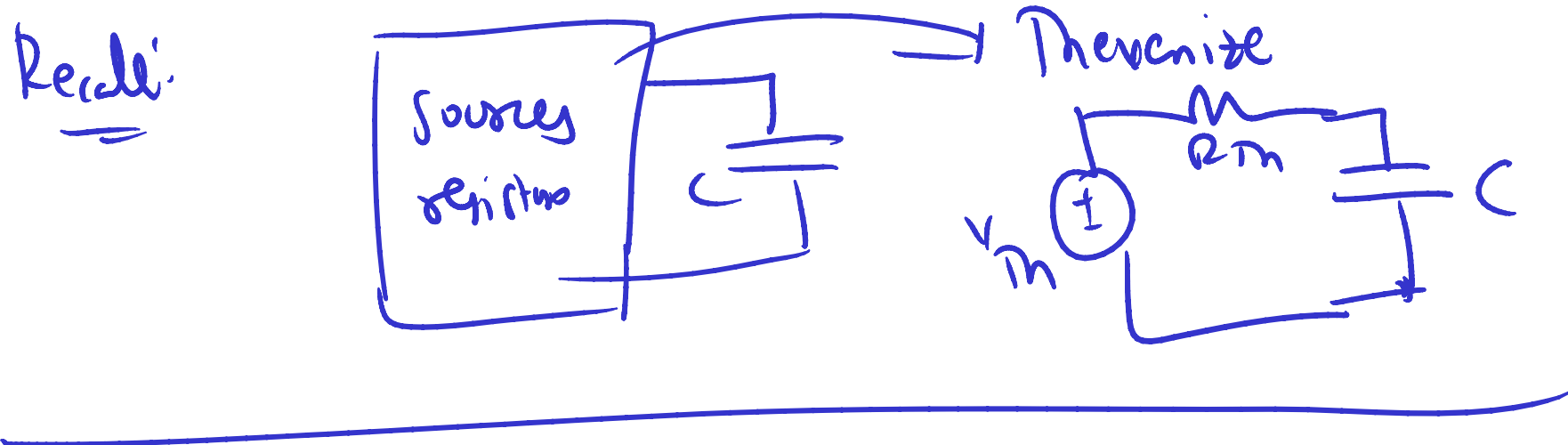Application of Thevenin's Theorem to RC/RL Circuits



Examples

D 7.3 on p. 240

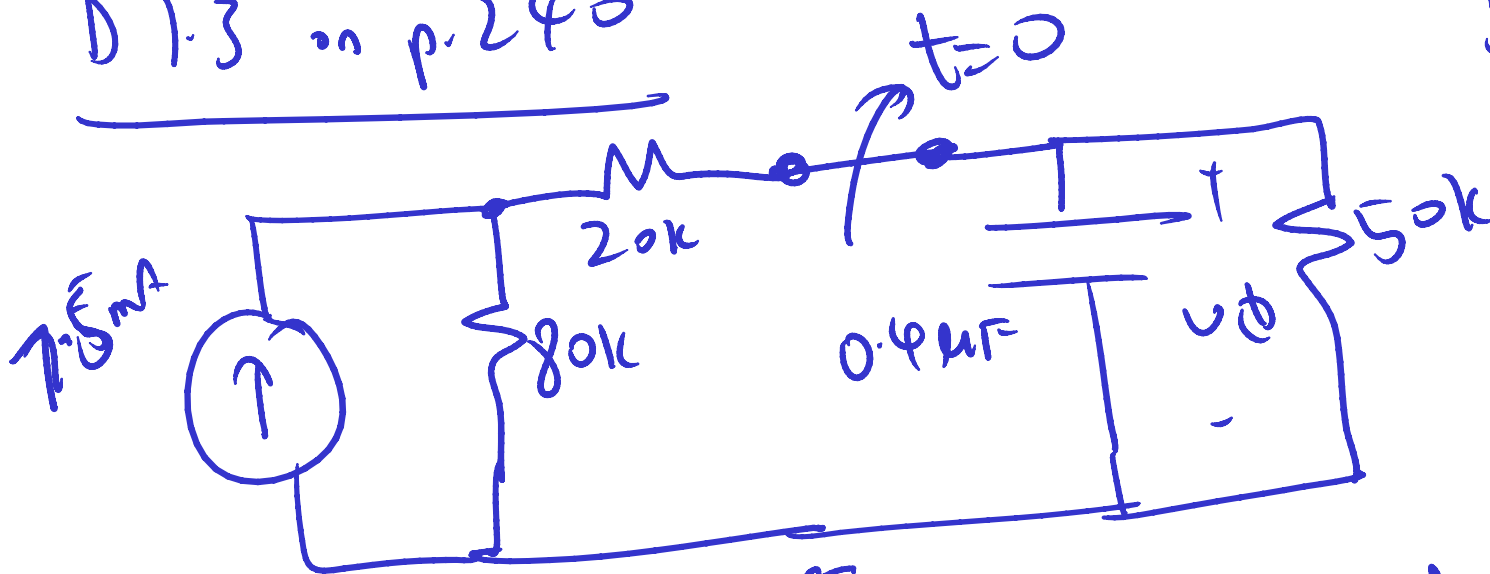


Switch closed for a long time and opens at $t=0$.

(1) Find $v(t=0^-)$
 $= v(t=0^+)$


Note: 0^- means at the infinitesimally small time instant before discontinuity

Examples

D 7.3 on p. 240

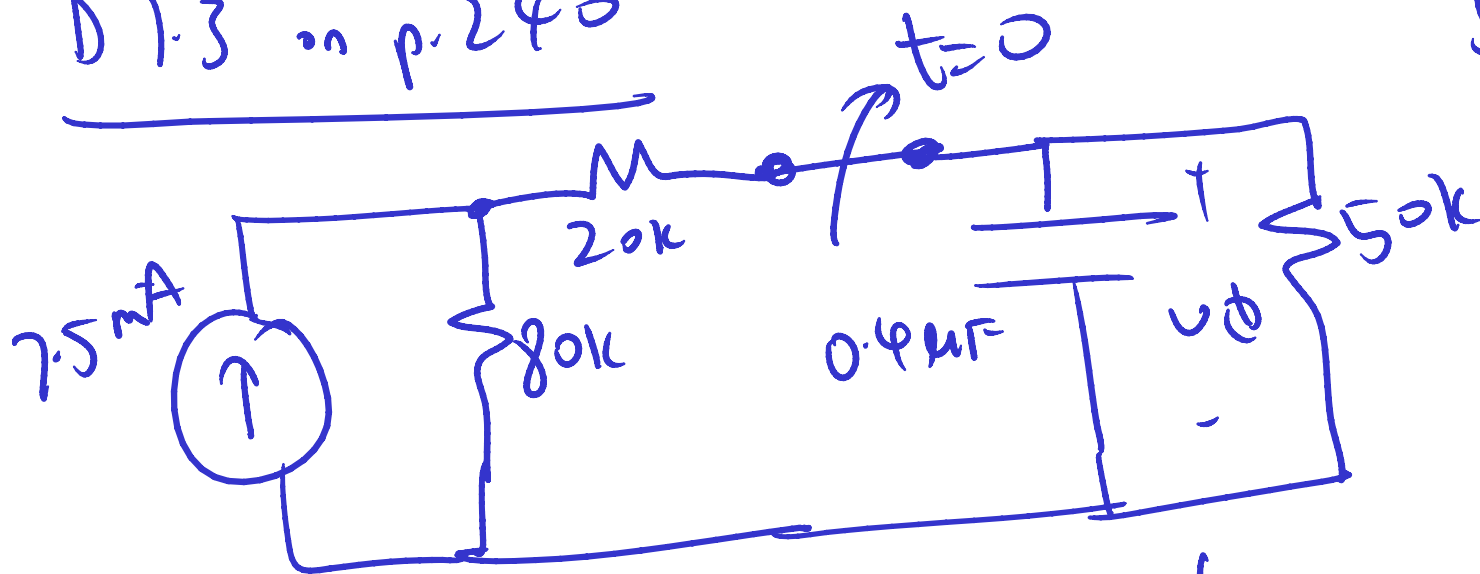

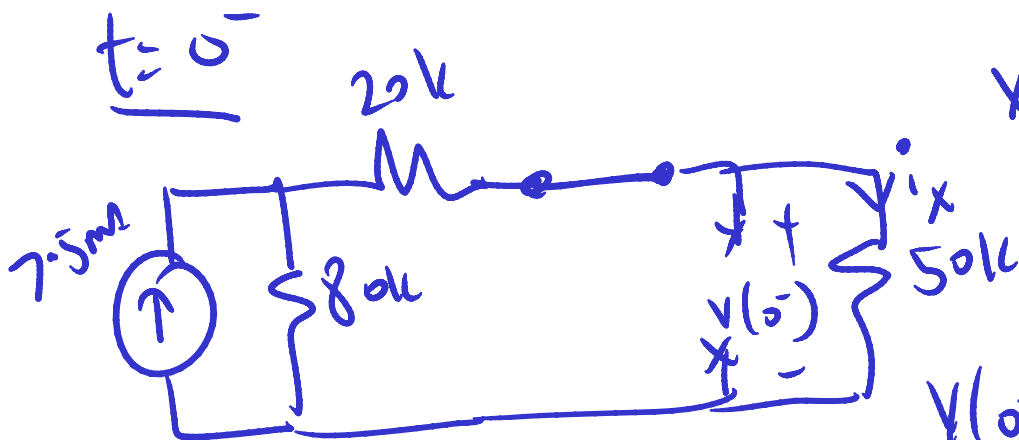Switch closed for a long time and opens at $t = 0$.



$$v(0^-) = \left(\frac{80k}{150k} \right) 7.5 \text{ mA} \cdot (50k)$$

$$\Rightarrow v(0^-) = 200 \text{ V}$$


$$v(0^-) = (i_x)(50k)$$

Example (contd.)

$$\therefore V(0^+) = V(0^-) = 200\text{V}$$



Because of continuity
of voltage across
(capacitor)

(b) Find τ , $t \geq 0$

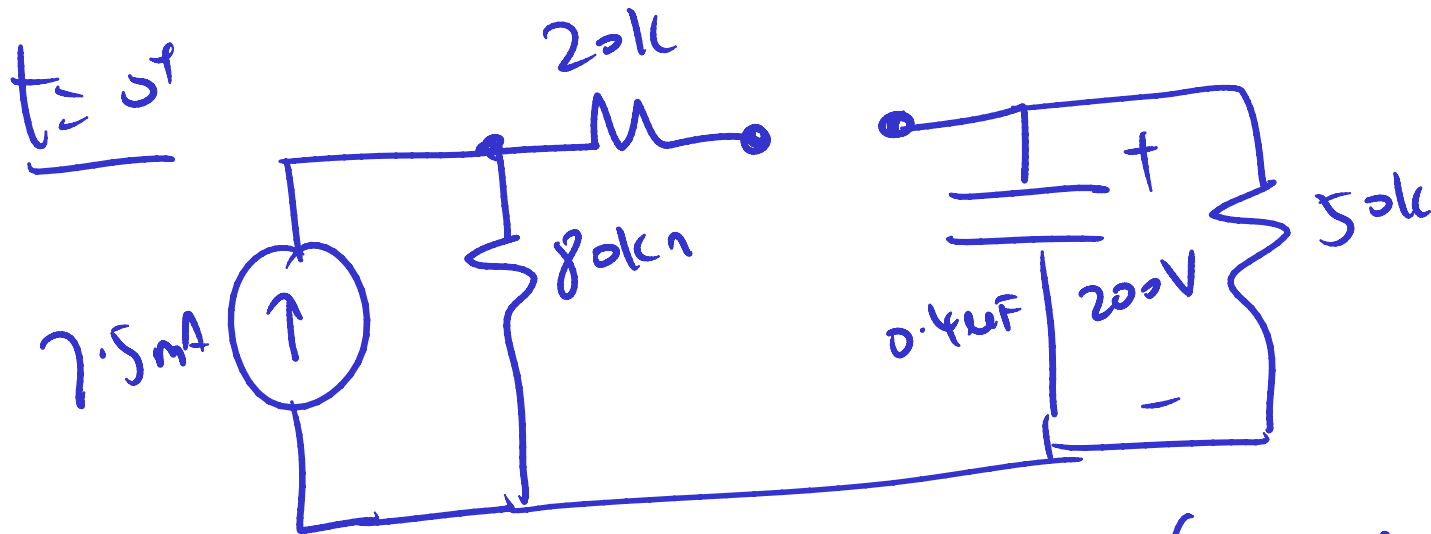


$$\tau = R_{Th} \cdot C = (50\text{k}) (0.4\mu\text{F}) = \underline{\underline{20\text{ms}}}$$

Example (contd.)

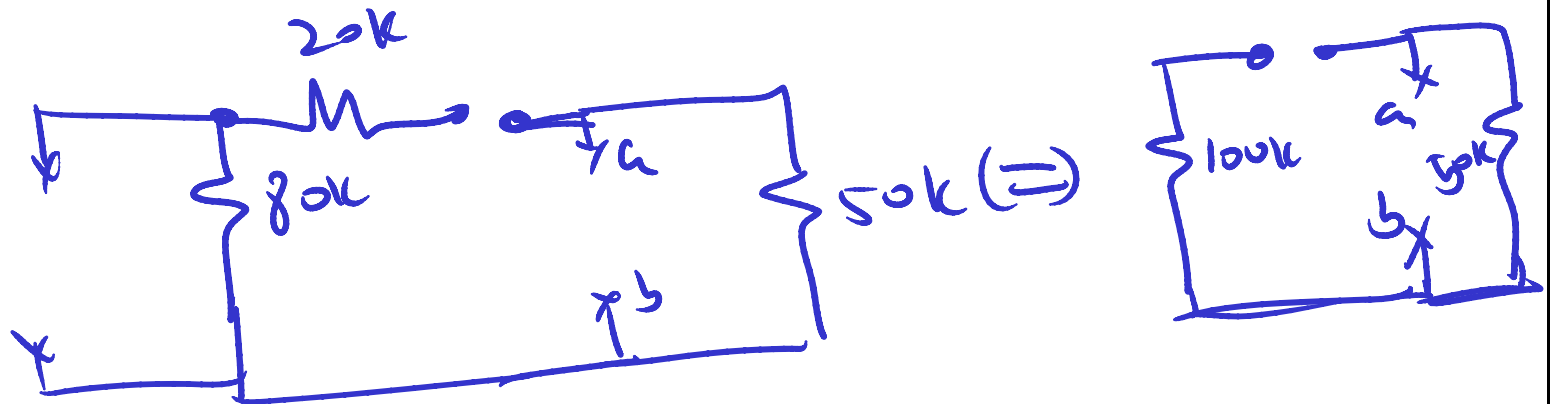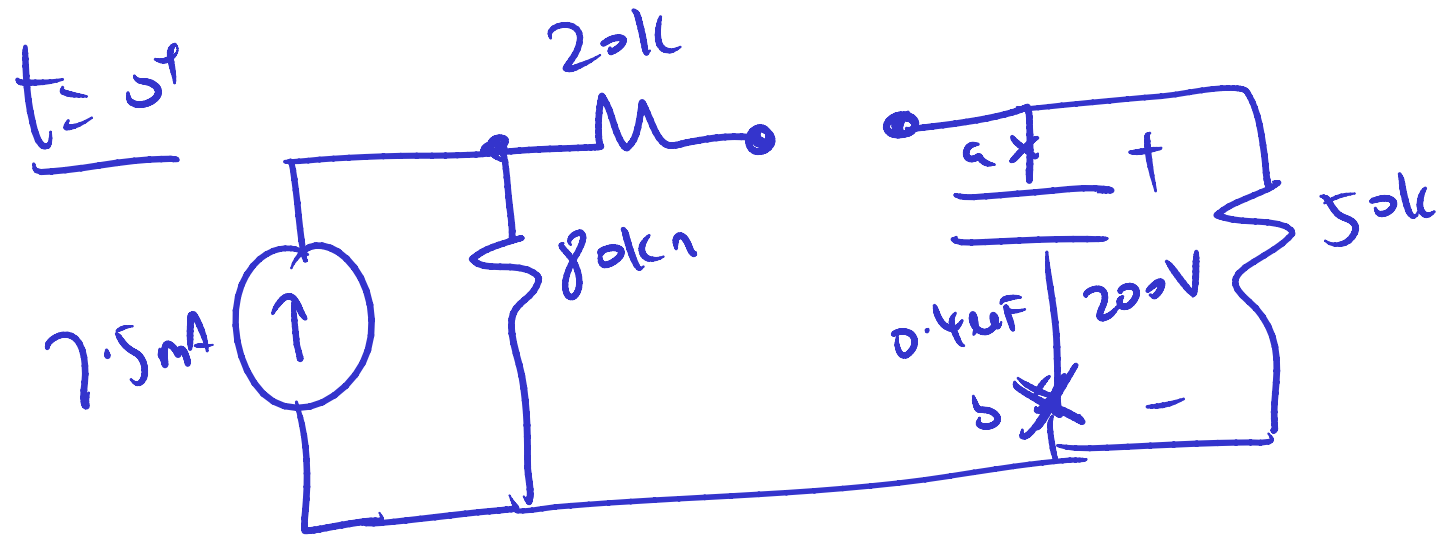


Example (contd.)

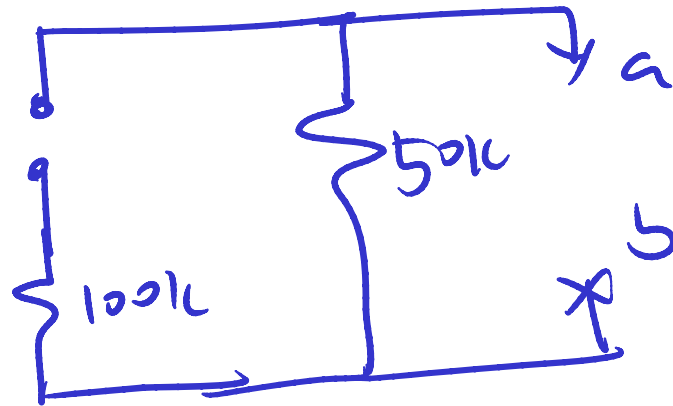

$$\Rightarrow R_{ab} = R_{in} = 50k$$

$$t \geq 0$$

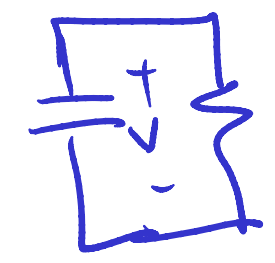


(C) Find $v(t)$ $t \geq 0$

$$v(t) = \cancel{V_{final}} + (V_{initial} - \cancel{V_{final}}) e^{-t/\tau}$$

$$v(t) = 200 e^{-t/20ms} \text{ Volt}$$

Example (contd.)

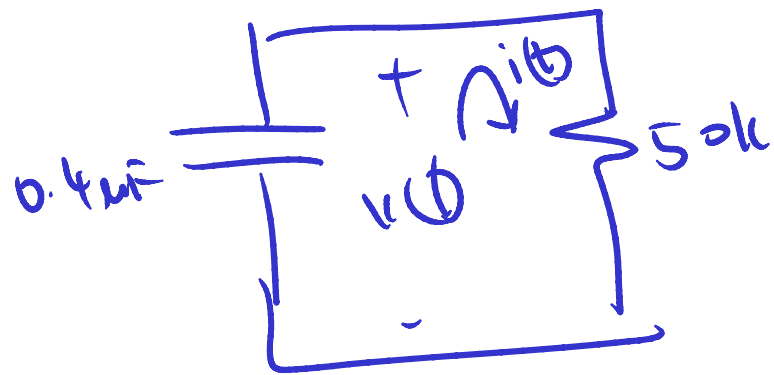

$$v(0) = 200\text{V}$$

$$E(0) = \frac{1}{2} C [v(0)]^2$$


* Find $i(t) = \frac{v(t)}{50\text{k}}$ (Ohm's law)

$$= \frac{1}{2} \cdot 0.4 \mu\text{F} \cdot 200 \cdot 200$$

$$\approx \underline{\underline{8 \text{ mJ}}}$$

Capacitor: $i = -C \frac{dv}{dt}$
 $= -C \frac{d(v_{\text{initial}} e^{-t/\tau})}{dt}$

Problem 7.2 on p. 265

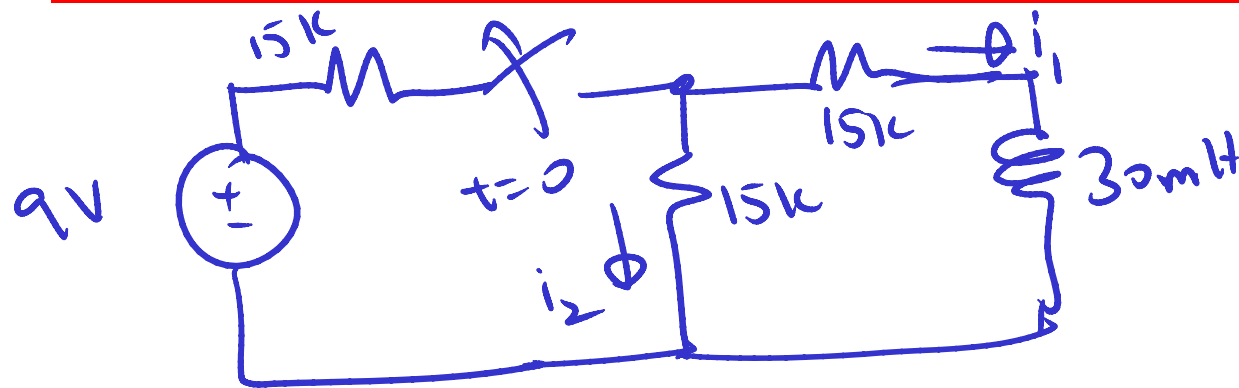

Notes:

$$v = L \frac{di}{dt}$$


(a) Find $i_1(0^-), i_2(0^-)$

(b) Find $i_1(0^+), i_2(0^+)$

- \Rightarrow (1) Steady state, inductor is a short circuit
- (2) Inductor maintains current across discontinuities

$$(3) \tau = L/R$$


Problem 7.2 on p. 265

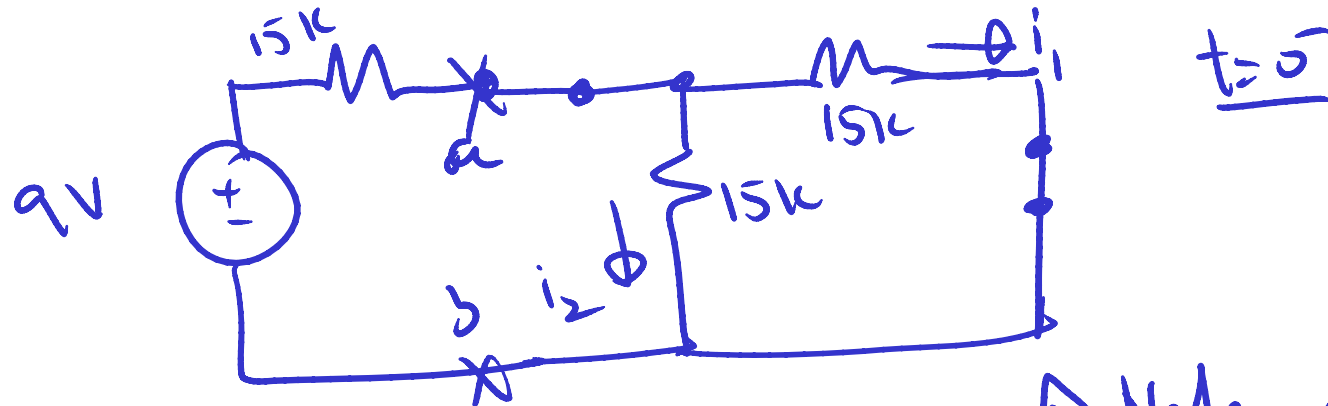


(as Find $i_1(0^-), i_2(0^-)$)

$$i_1(0^-) = i_2(0^-) = \frac{1}{5} \text{ mA}$$

Norton at ab

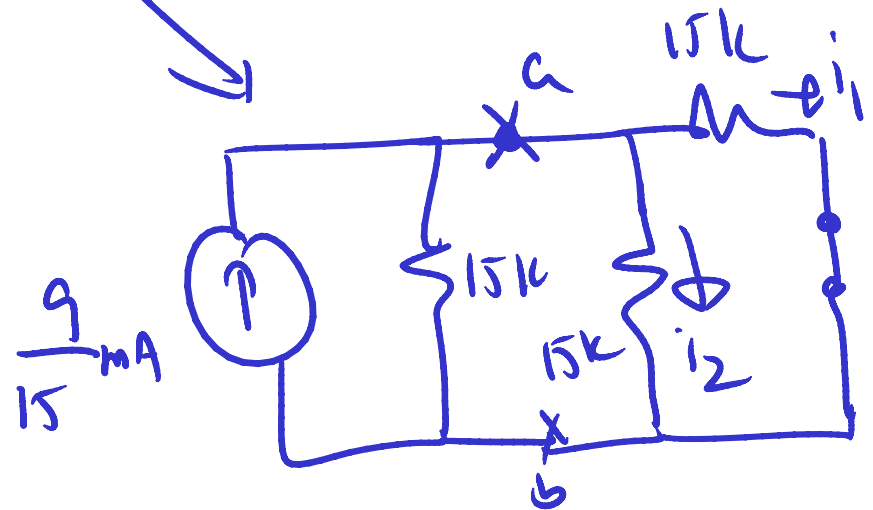

Problem 7.2 on p. 265

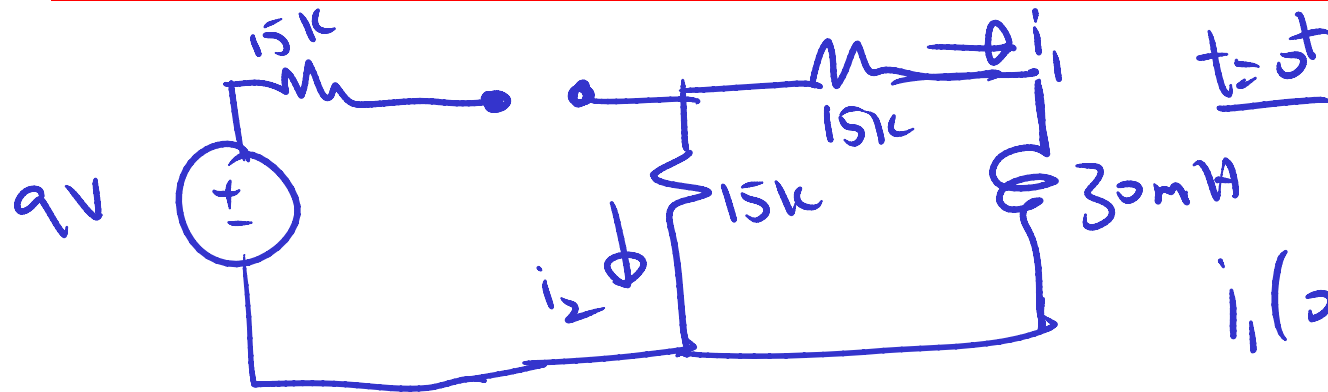

$$i_1(0^+) = i_1(0^-)$$

(b) Find $i_1(0^+)$, $i_2(0^+)$

$$= \underline{\underline{0.2 \text{ mA}}}$$

Notice: $i_2(0^+) = -i_1(0^+)$


$$= \underline{\underline{-0.2 \text{ mA}}}$$

(c) $i_1(t) = i_{1\text{find}} + (i_{1\text{initial}} - i_{1\text{find}}) e^{-t/\tau}$, $\tau = L/R$


Digital Signals

We compute with pulses.

We send beautiful pulses in:

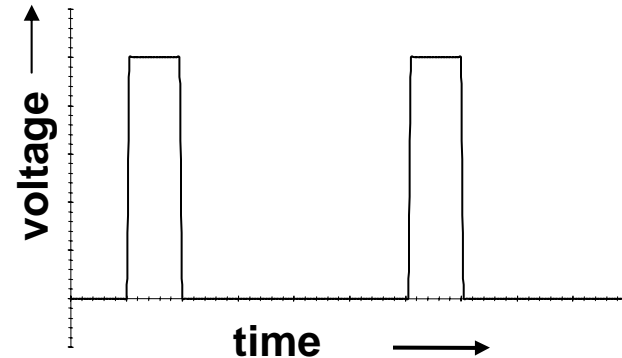

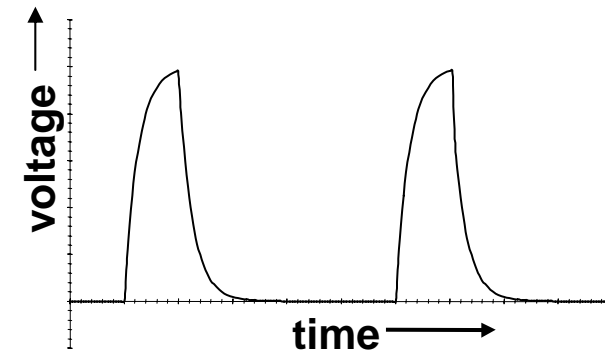But we receive lousy-looking pulses at the output:



Capacitor charging effects are responsible!

- Every node in a real circuit has capacitance; it's the charging of these capacitances that limits circuit performance (speed)