

EE100Su08 Lecture #9 (July 16th 2008)



- Outline
 - HW #1s and Midterm #1 returned today
 - Midterm #1 notes
 - HW #1 and Midterm #1 regrade deadline: Wednesday, July 23rd 2008, 5:00 pm PST. Procedure:
 - HW #1: Bart's office hours
 - Midterm #1: Attach a note to the FRONT of your test with your complaint and drop it in HW box
 - Questions?
 - This week: Operational Amplifiers (Op-Amps)
 - Op-Amp Model
 - Negative Feedback for Stability
 - Components around Op-Amp define the Circuit Function
 - Nonlinear circuits
 - Op-Amp from 2-Port Blocks

The Operational Amplifier

- The ***operational amplifier*** (“***op amp***”) is a basic building block used in analog circuits.
 - Its behavior is modeled using a dependent source.
 - When combined with resistors, capacitors, and inductors, it can perform various useful functions:
 - **amplification/scaling** of an input signal
 - **sign changing** (inversion) of an input signal
 - **addition** of multiple input signals
 - **subtraction** of one input signal from another
 - **integration** (over time) of an input signal
 - **differentiation** (with respect to time) of an input signal
 - **analog filtering**
 - **nonlinear functions** like exponential, log, sqrt, etc
 - Isolate input from output; allow cascading


Op Amp Terminals

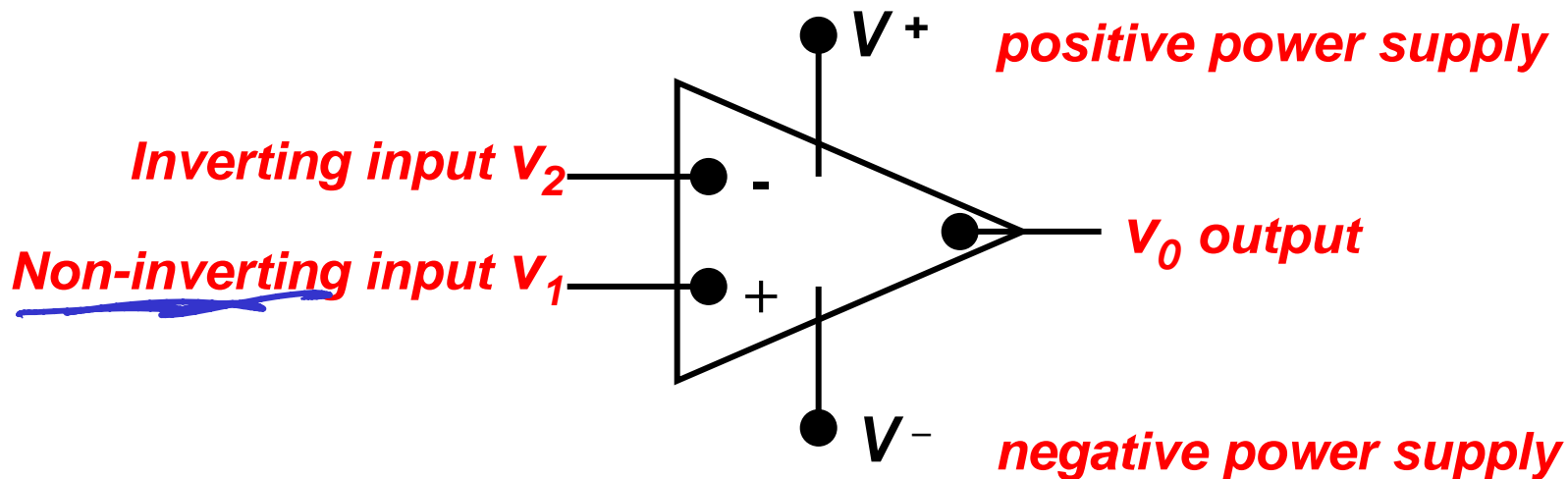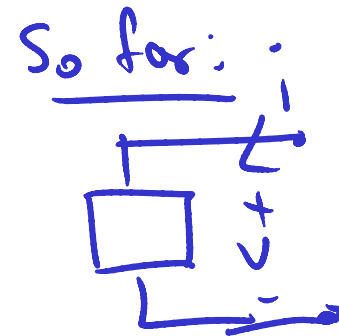- 3 signal terminals: 2 inputs and 1 output
- IC op amps have 2 additional terminals for DC power supplies
- Common-mode signal = $(v_1 + v_2)/2$
- Differential signal = $v_1 - v_2$




Op Amp "Notation" and Model

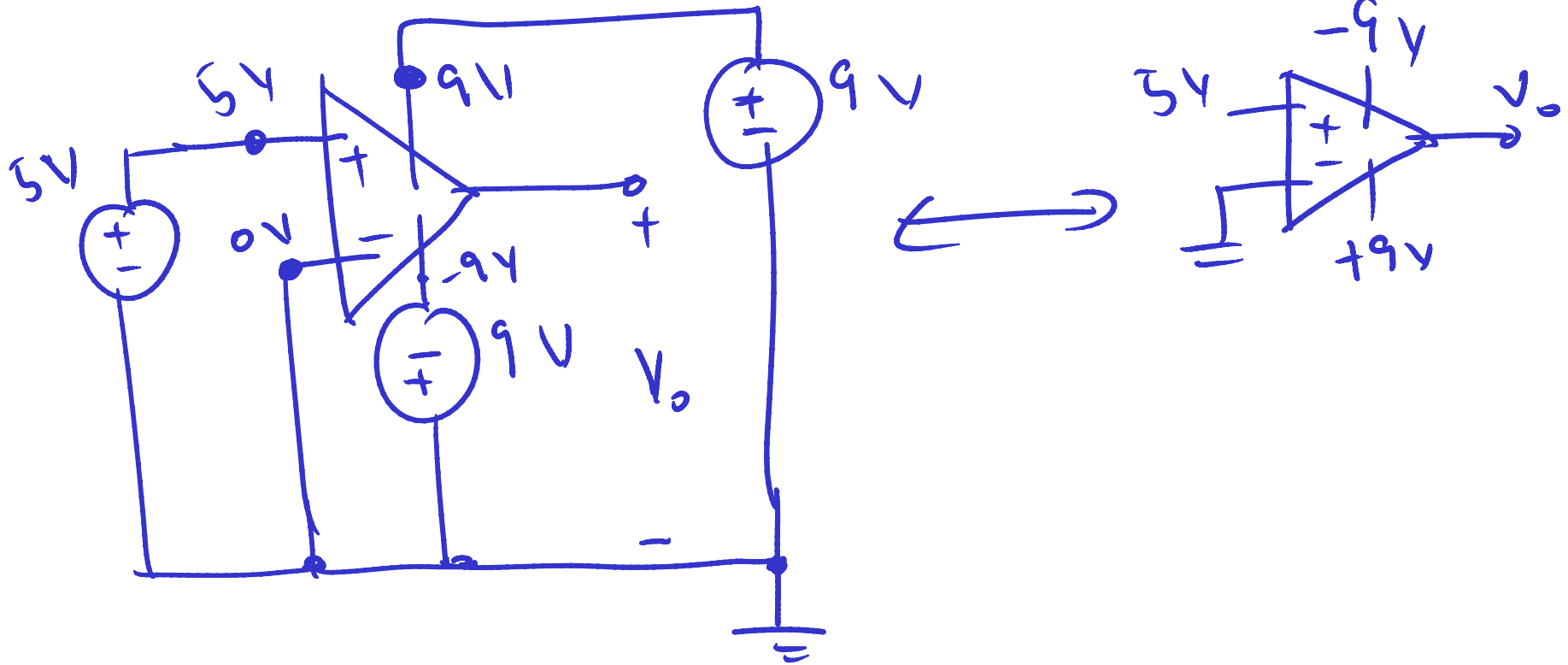Ref: (1) Chapter 5 of your book } Read all of it!
(2) Intro. to Nonlinear Circuit Analysis }



Op Amp "Notation" and Model

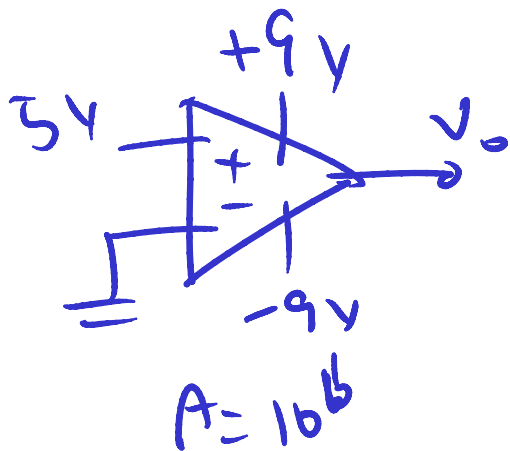

Assume op-amp is linear

$$V_o = A(v_p - v_n)$$

$$= 10^6 (5 - 0)$$

$$= 5 \text{ MV}$$


$$V_o = 5 \text{ mV} > 9 \text{ V} = V_{cc}$$

\Rightarrow op-amp is saturating at the positive

$$\Rightarrow \boxed{V_o = 9 \text{ V}}$$

op-amp is not in linear region

Model (p. 157 of book)

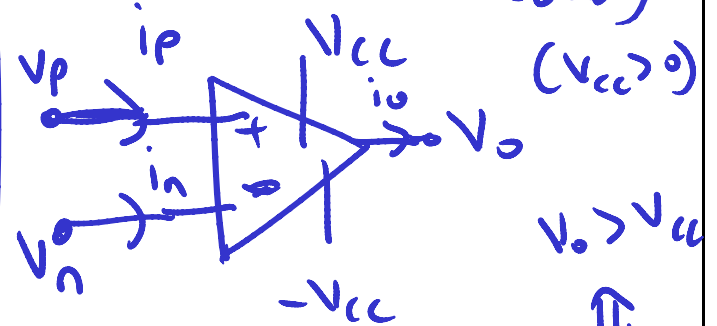

linear region

$$= V_{cc}$$

if $v_p > v_n$

$$\boxed{V_o = A(v_p - v_n) \text{ if } v_p \approx v_n}$$

$A \triangleq$ open-loop gain $\approx 10^6$ (HUGE)

$$= -V_{cc} \text{ if } v_p < v_n$$

Op Amp "Notation" and Model

Consider: $v_o = A(v_p - v_n) - \textcircled{1}$


For all practical circuits, $|v_d| \ll A$

ex: $A = 10^6$, $v_o \in [9V, -9V]$


$\therefore \textcircled{1} \Rightarrow v_p - v_n = \frac{v_o}{A}$

$\Rightarrow v_p - v_n \approx 0$

$\Rightarrow \boxed{v_p \approx v_n}$

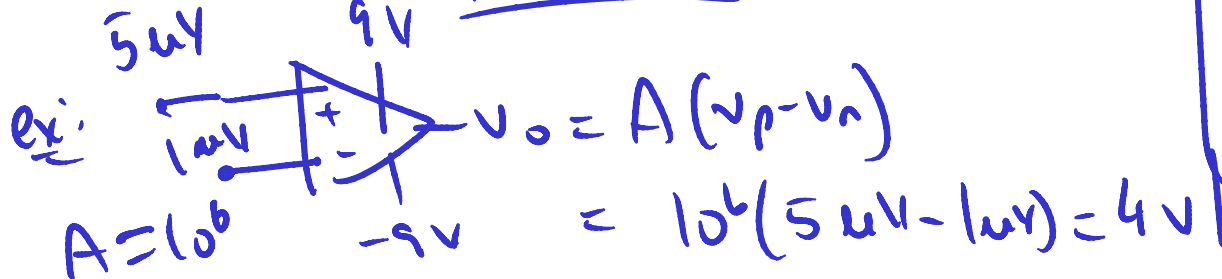

Model (p. 157 of book)

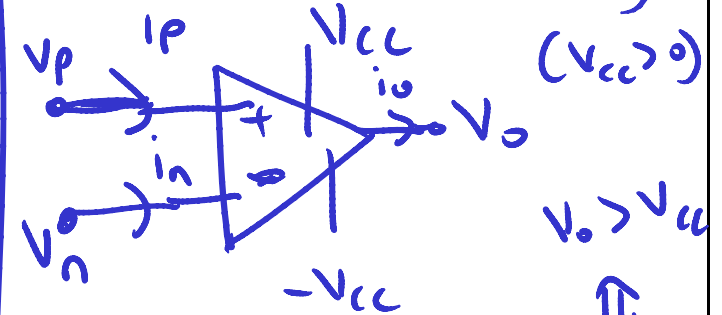

linear region $v_o = V_{cc}$ if $v_p > v_n$

$v_o = A(v_p - v_n)$ if $v_p \approx v_n$

$A \triangleq$ open-loop gain $\approx 10^6$ (HUGE)


$= -V_{cc}$ if $v_p < v_n$

Op Amp "Notation" and Model

positive

+ve rail!

Assume op-amp is in linear region

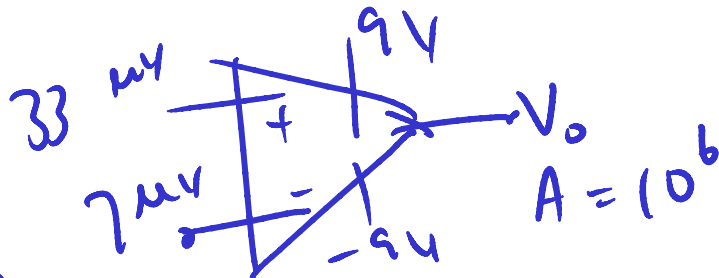

$$V_o = A(v_p - v_n)$$


$$= 10^6 (33 \mu\text{V} - 7 \mu\text{V})$$

$$\approx 10^6 (26 \mu\text{V})$$

$$= 26 \text{ V} > 9 \text{ V} = V_{cc}$$

$$\therefore \boxed{V_o = 9 \text{ V}}$$

Model (p. 157 of book)

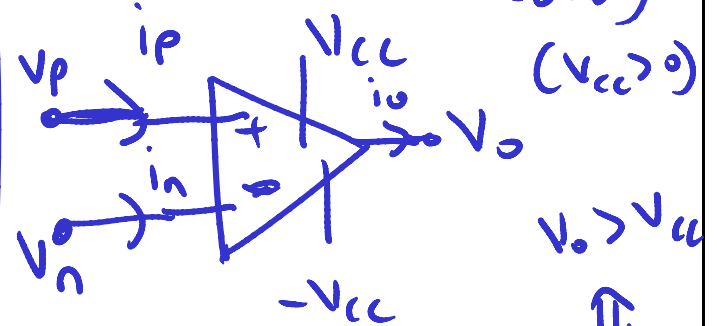

linear region

$$= V_{cc}$$


if $v_p > v_n$

$$\boxed{V_o = A(v_p - v_n) \text{ if } v_p \approx v_n}$$

$A \triangleq$ open-loop gain $\approx 10^6$ (HUGE)

$$= -V_{cc} \text{ if } v_p < v_n$$

Op Amp "Notation" and Model

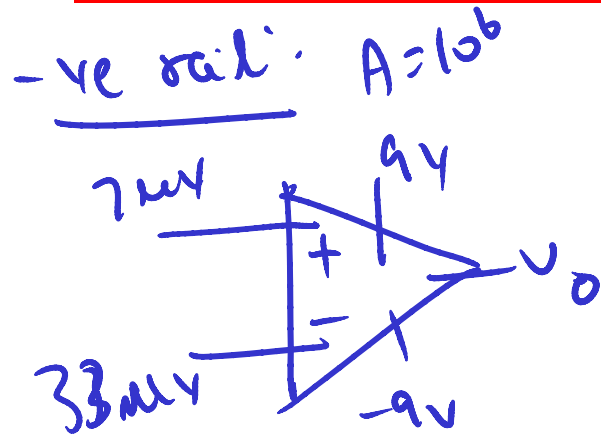


Assume op-amp is linear.

$$V_o = A(v_p - v_n)$$

$$= 10^6(7\mu\text{V} - 33\text{mV})$$


$$= -26\text{V} < -9\text{V}$$

$$\therefore \boxed{V_o = -9\text{V}}$$

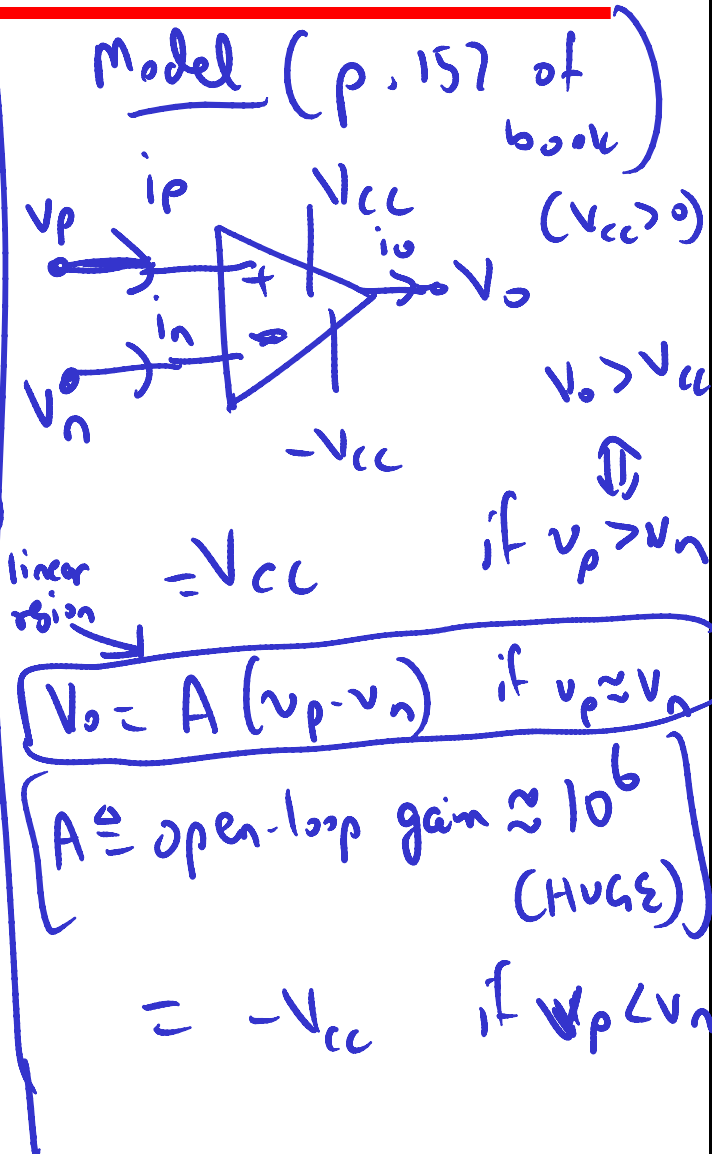

Op Amp "Notation" and Model

Op-amp model:

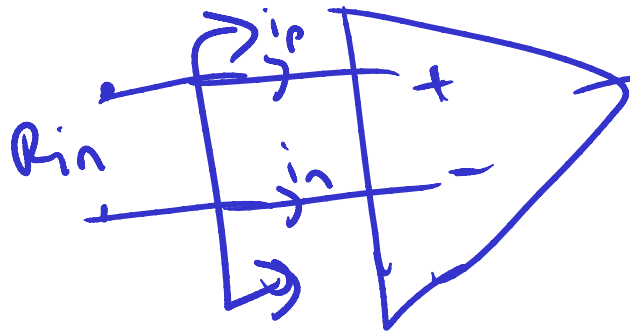


$i_p \approx i_n = 0$
 always true
 irrespective
 of op-amp
 region of
 operation

But, i_x , i_y & i_o
NEED NOT be zero!

(linear, +ve rail, -ve rail)

Model (p. 157 of book)

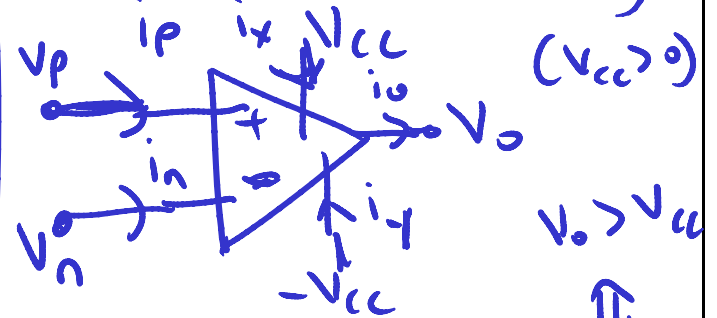

linear region

$= V_{cc}$

$v_o > V_{cc}$
 \Downarrow
 if $v_p > v_n$


$$v_o = A(v_p - v_n) \text{ if } v_p \approx v_n$$

$$A \triangleq \text{open-loop gain} \approx 10^6 \text{ (HUGE)}$$

$$= -V_{cc} \text{ if } v_p < v_n$$

Op Amp "Notation" and Model

Voltage Transfer Characteristics:

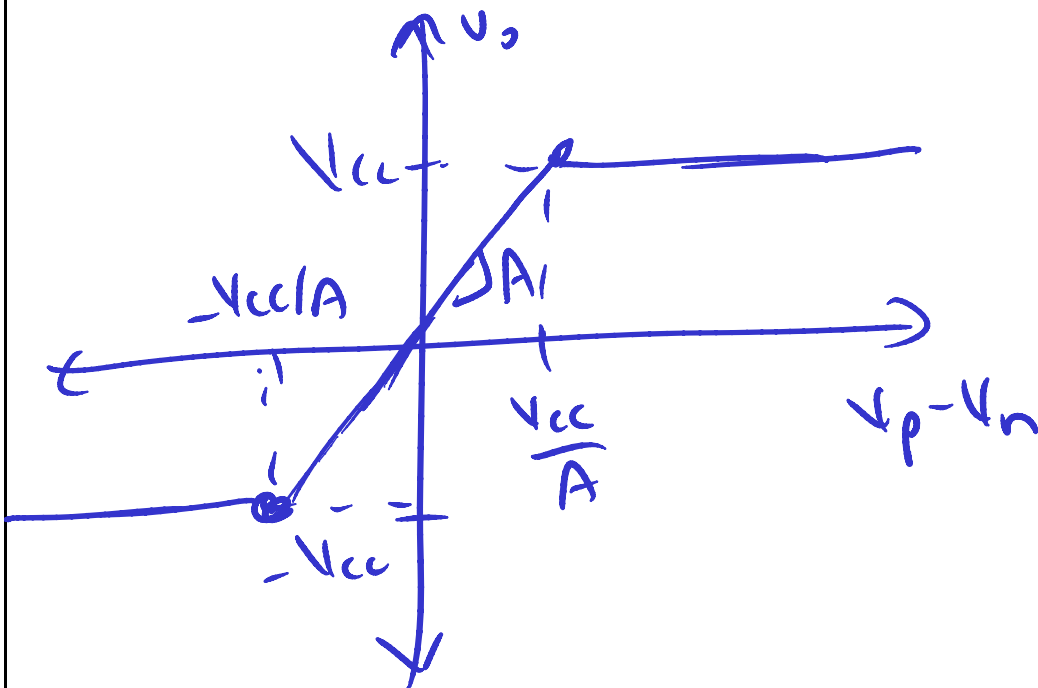


Book:

$$v_o = A(v_p - v_n) \text{ if}$$

$$-V_{cc} < A(v_p - v_n) < V_{cc}$$

Model (p. 157 of book)

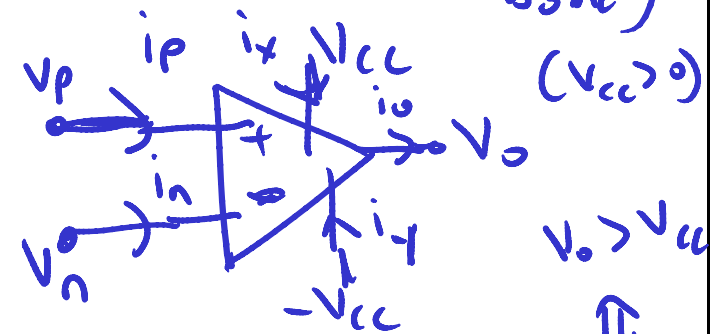

linear region

$$= V_{cc}$$

if $v_p > v_n$

$$v_o = A(v_p - v_n) \text{ if } v_p \approx v_n$$


$$A \triangleq \text{open-loop gain} \approx 10^6 \text{ (HUGE)}$$

$$\Rightarrow v_o = A(v_p - v_n) \text{ if}$$

$$-\frac{V_{cc}}{A} < v_p - v_n < \frac{V_{cc}}{A}$$

$$\frac{V_{cc}}{A}$$

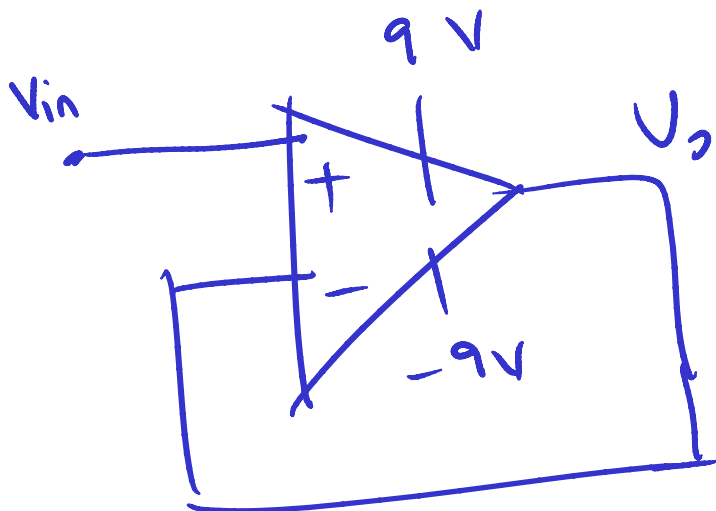Useful op-amp circuits (1) Voltage follower.



(Negative feedback)

Book:


$$V_o = \begin{cases} -V_{cc} \\ A(v_p - v_n) \\ V_{cc} \end{cases}$$

$$\begin{cases} A(v_p - v_n) < -V_{cc} \\ v_p \approx v_n \\ A(v_p - v_n) > V_{cc} \end{cases}$$


$A \rightarrow \infty$
↑
IDEALLY

$$\begin{cases} v_p < v_n \\ v_p = v_n \\ v_p > v_n \end{cases}$$

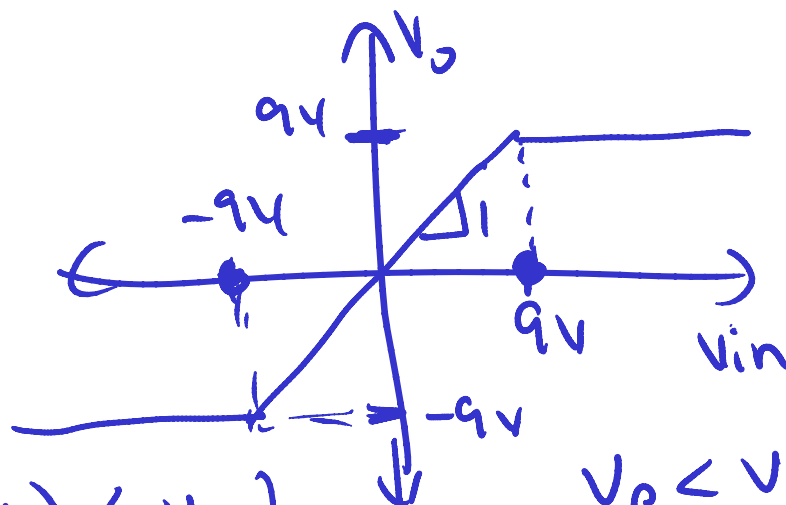(ii) Plot V_o vs V_{in}
[i.e., voltage transfer characteristics]



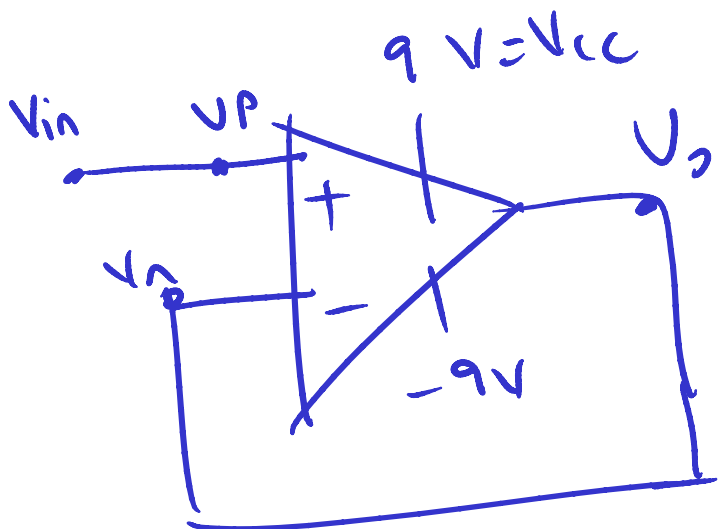Useful op-amp circuits (1) Voltage follower.




Assume opamp is in the real

$$\Rightarrow v_o = 9V \text{ if } v_p > v_n$$

$$\Rightarrow v_o = 9V \text{ if } v_{in} > v_o$$

$$\Rightarrow v_o = 9 \text{ if } v_{in} > 9$$

(Negative feedback)

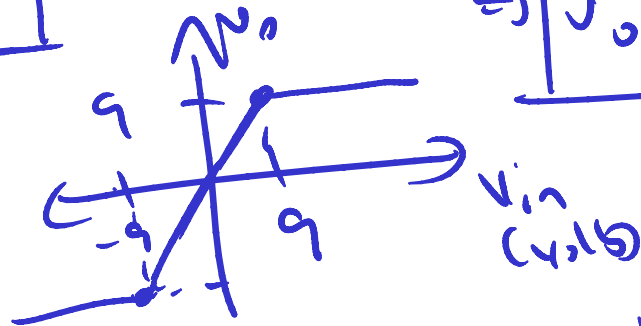


Book:

$$v_o = \begin{cases} -V_{cc} & A(v_p - v_n) < -V_{cc} \\ A(v_p - v_n) & -V_{cc} < v_o < V_{cc} \\ V_{cc} & A(v_p - v_n) > V_{cc} \end{cases}$$

$A \rightarrow \infty$
IDEALLY

\swarrow -ve rail $v_p < v_n$
 \rightarrow $v_p = v_n$
 \searrow +ve rail $v_p > v_n$

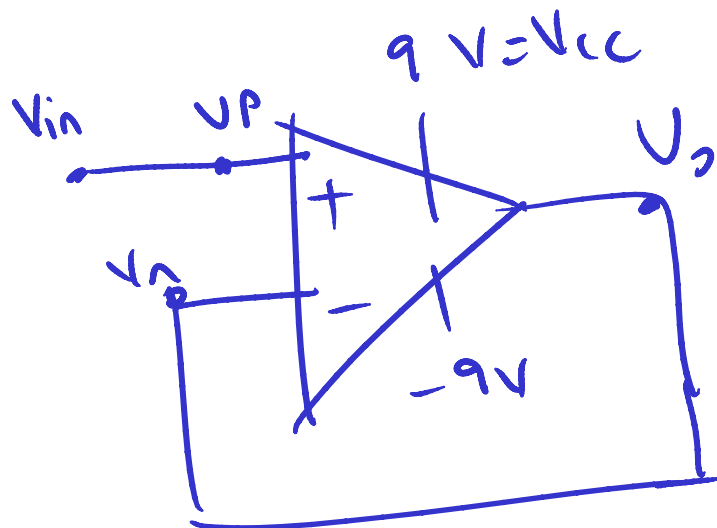Useful op-amp circuits (1) Voltage follower.




Linear region: $V_o = A(v_p - v_n)$

$$\Rightarrow v_p = v_n$$

$$\Rightarrow \boxed{V_{in} = V_o}$$

$$[-A < V_o < A]$$

(Negative feedback)

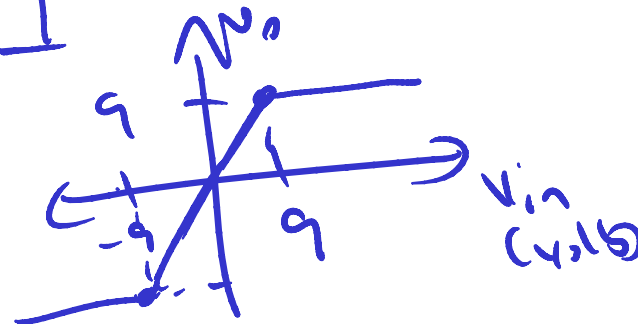

Book:


$$V_o = \begin{cases} -V_{cc} & A(v_p - v_n) < -V_{cc} \\ A(v_p - v_n) & -V_{cc} < V_o < V_{cc} \\ V_{cc} & A(v_p - v_n) > V_{cc} \end{cases}$$

$A \rightarrow \infty$
 \uparrow
IDEALLY

-ve rail $\rightarrow v_p < v_n$
 $v_p = v_n$
 +ve rail $\rightarrow v_p > v_n$



Useful op-amp circuits (1) Voltage follower.

(b:) How is this useful?

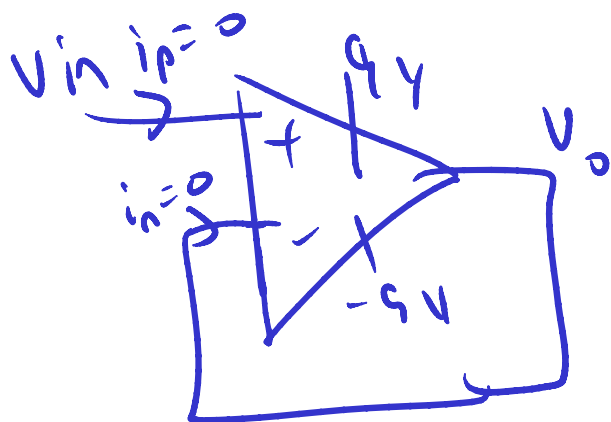


we could have
 ↓ done this!

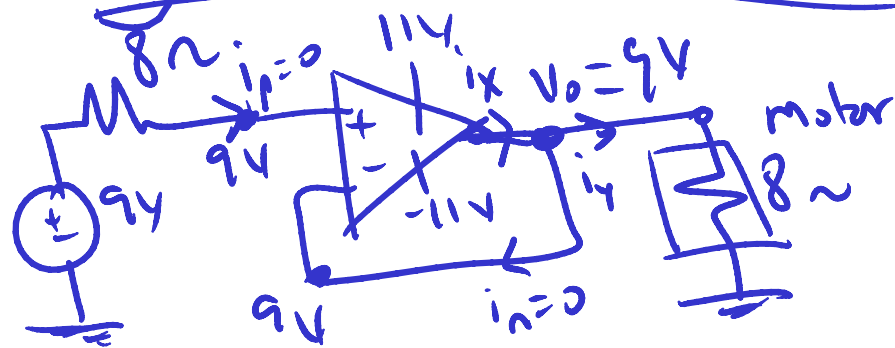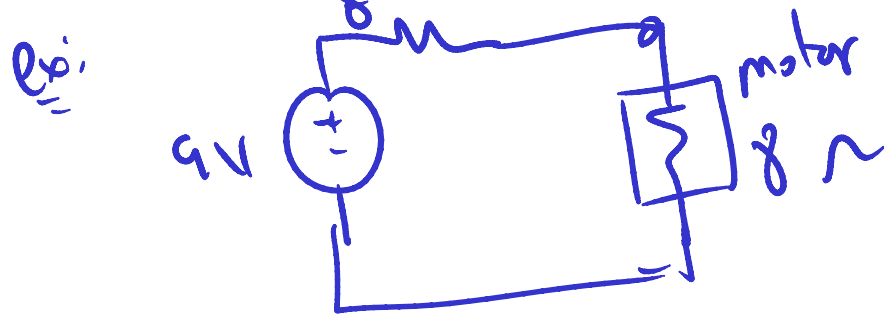Useful because it avoids
 "loading" the source



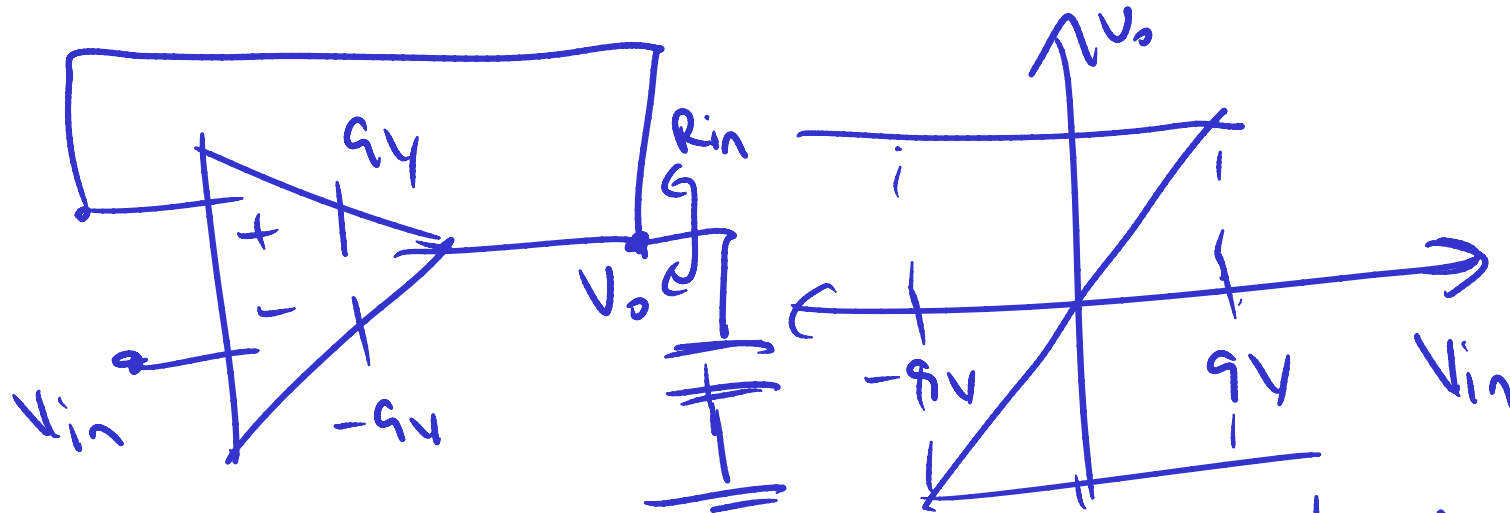Useful op-amp circuits (1) POSITIVE FEEDBACK



Assume op-amp is in the rail:

$V_o = 9V$ if $V_p > V_n$

$\Rightarrow V_o = 9V$ if $V_o > V_{in}$

$\Rightarrow V_o = 9V$ if $V_{in} < 9V$

Assume op-amp is in -ve rail:

$V_o = -9V$ if $V_p < V_n$

$V_o = -9V$ if $V_o < V_{in}$

$\Rightarrow V_o = -9V$ if $V_{in} > -9V$

Assume op-amp is saturated.

$V_o = V_{in}$ if $-9V < V_o < 9V$

Summing-Point Constraint

- Check if under negative feedback
 - Small v_i result in large v_o
 - Output v_o is connected to the inverting input to reduce v_i
 - Resulting in $v_i=0$
- Summing-point constraint
 - $v_1 = v_2$
 - $i_1 = i_2 = 0$
- Virtual short circuit
 - Not only voltage drop is 0 (which is short circuit), input current is 0
 - This is different from short circuit, hence called “virtual” short circuit.


Ideal Op-Amp Analysis Technique

Assumption 1: The **potential** between the op-amp input terminals, $v_{(+)} - v_{(-)}$, equals **zero**.

Assumption 2: The **currents** flowing into the op-amp's two input terminals both equal **zero**.

No Currents

No Potential Difference

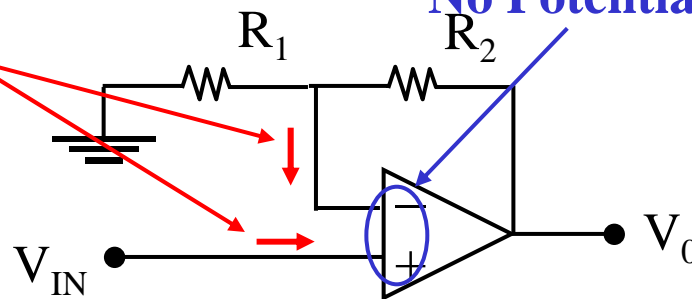


EXAMPLE

Ideal Op-Analysis: Non-Inverting Amplifier

Assumption 1: The **potential** between the op-amp input terminals, $v_{(+)} - v_{(-)}$, equals **zero**.

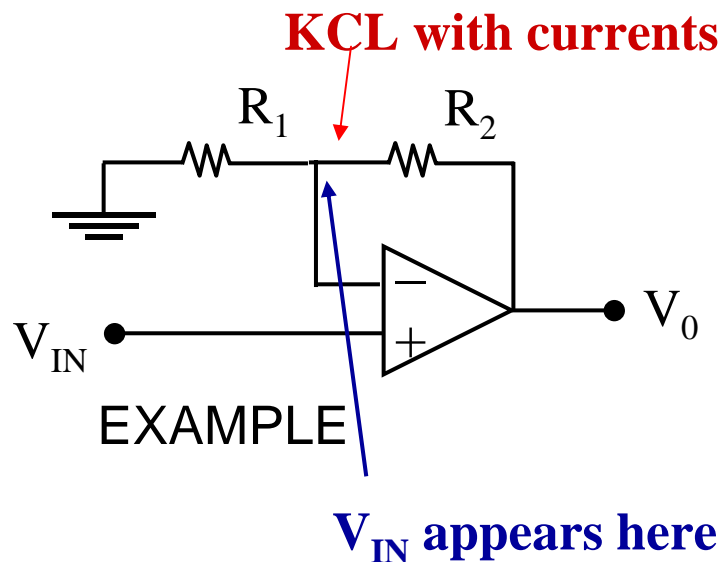Assumption 2: The **currents** flowing into the op-amp's two input terminals both equal **zero**.




$$\frac{v_{in}}{R_1} + \frac{v_{in} - v_{out}}{R_2} = 0$$
$$v_{out} = \frac{R_1 + R_2}{R_1} v_{in}$$

Non-inverting Amplifier

Non-Inverting Amplifier

- Ideal voltage amplifier

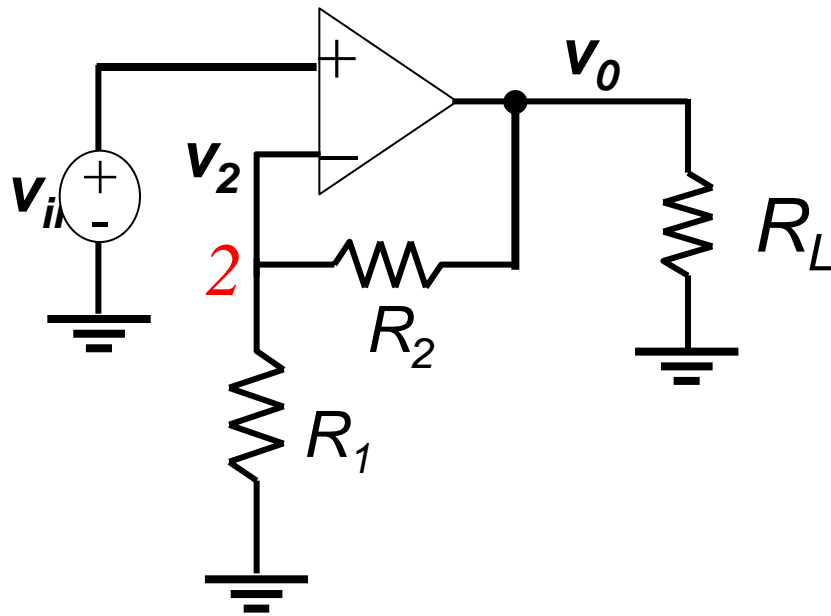

$$\text{Closed loop gain} = A_v = \frac{v_o}{v_{in}}$$

$$v_1 = v_2 = v_{in}, i_1 = i_2 = 0$$


Use KCL At Node 2.

$$i = \frac{(v_o - v_2)}{R_2} = \frac{(v_2 - 0)}{R_1}$$

$$A = \frac{v_o}{v_{in}} = \frac{(R_1 + R_2)}{R_1}$$

$$\text{Input impedance} = \frac{v_{in}}{i} \rightarrow \infty$$

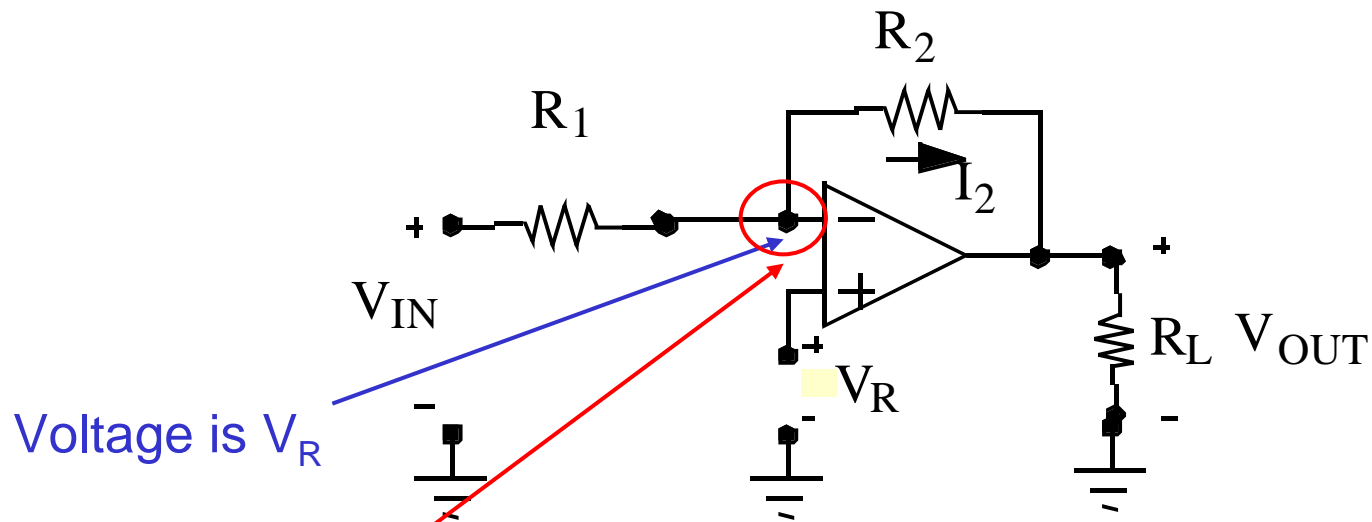Ideal Op-Amp Analysis: Inverting Amplifier



Voltage is V_R

Only two currents for KCL

$$\frac{V_R - V_{IN}}{R_1} + \frac{V_R - V_{OUT}}{R_2} = 0$$

$$V_{OUT} = V_R - \frac{R_2}{R_1} (V_{in} - V_R)$$

Inverting Amplifier with reference voltage

Inverting Amplifier

- Negative feedback → checked
- Use summing-point constraint

$$\text{Closed loop gain} = A_v = \frac{v_o}{v_{in}}$$


$$v_1 = v_2 = 0, i_1 = i_2 = 0$$

Use KCL At Node 2.

$$i = \frac{(v_{in} - v_2)}{R_1} = \frac{(v_{out} - v_2)}{R_2}$$


$$v_o = -\frac{R_2 v_o}{R_1}$$
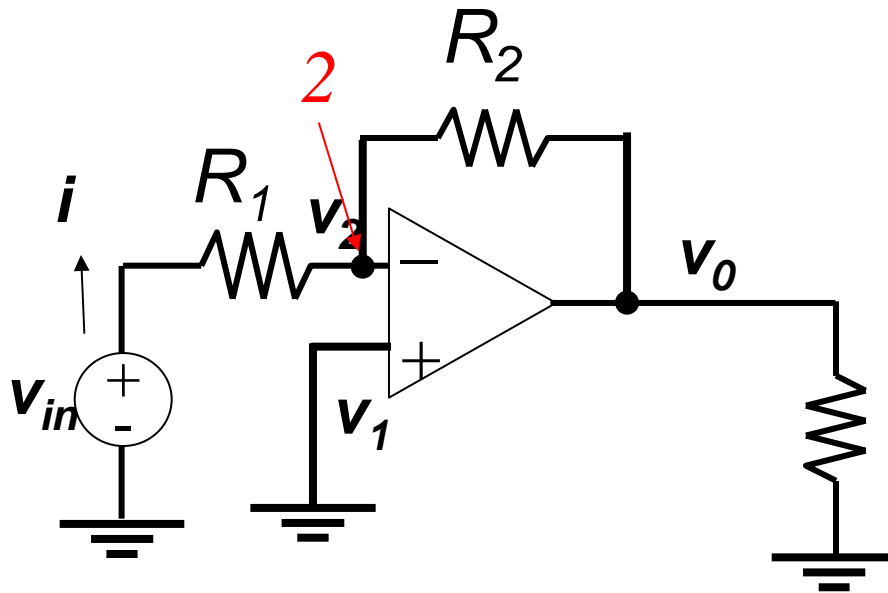
$$R_L \text{ Input impedance} = \frac{v_{in}}{i} = R_1$$



Ideal voltage source – independent of load resistor

Voltage Follower

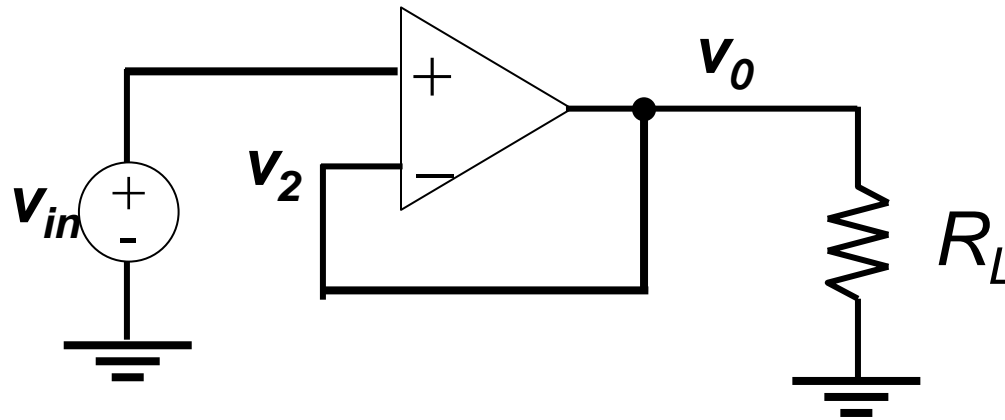

$$R_2 = 0$$


$$R_1 \rightarrow \infty$$

$$i = \frac{(v_o - v_2)}{R_2} = \frac{(v_2 - 0)}{R_1}$$

$$A = \frac{v_o}{v_{in}} = \frac{(R_1 + R_2)}{R_1} = 1 + \frac{R_2}{R_1} = 1$$

Op-amps in negative feedback:

Ex 5.3 on p. 176

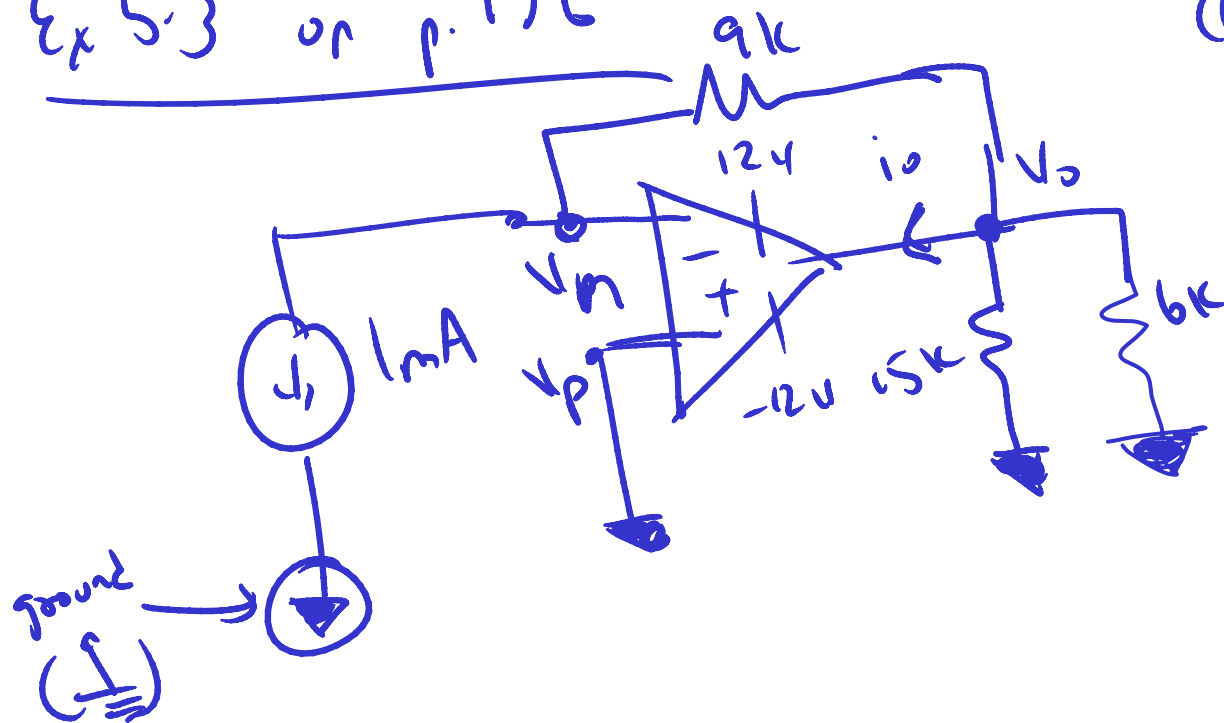

(6i) find i_o

Rule of thumb for
-ve feedback;

(1) Use summing
point constraint;

(i) Assume op-amp
is linear:

$$V_p = V_n \text{ \&}$$


check if

$$-V_{cc} < V_o < V_{cc}$$

Op-amps in negative feedback:

Ex 5.3 on p. 176

(6i) find i_o

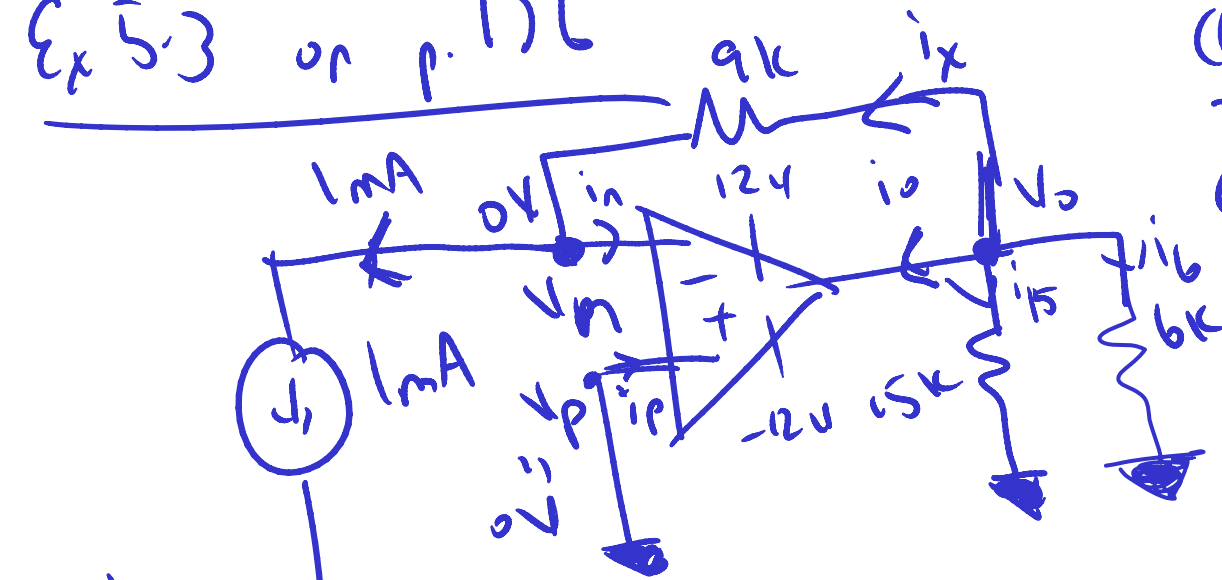

(1) Assume: $V_p = V_n = 0V$

$$i_n = i_p = 0$$

ground

 Notice:

$V_o \in (-12V, +12V)$

$$\Rightarrow V_p = V_n = 0V \checkmark$$

(2) KCL @ V_n :


$$1mA + i_n = i_x$$

$$\Rightarrow 1mA = \frac{V_o - V_n}{9k}$$

$$\Rightarrow \boxed{V_o = 9V}$$

Op-amps in negative feedback:

Ex 5.3 on p. 176

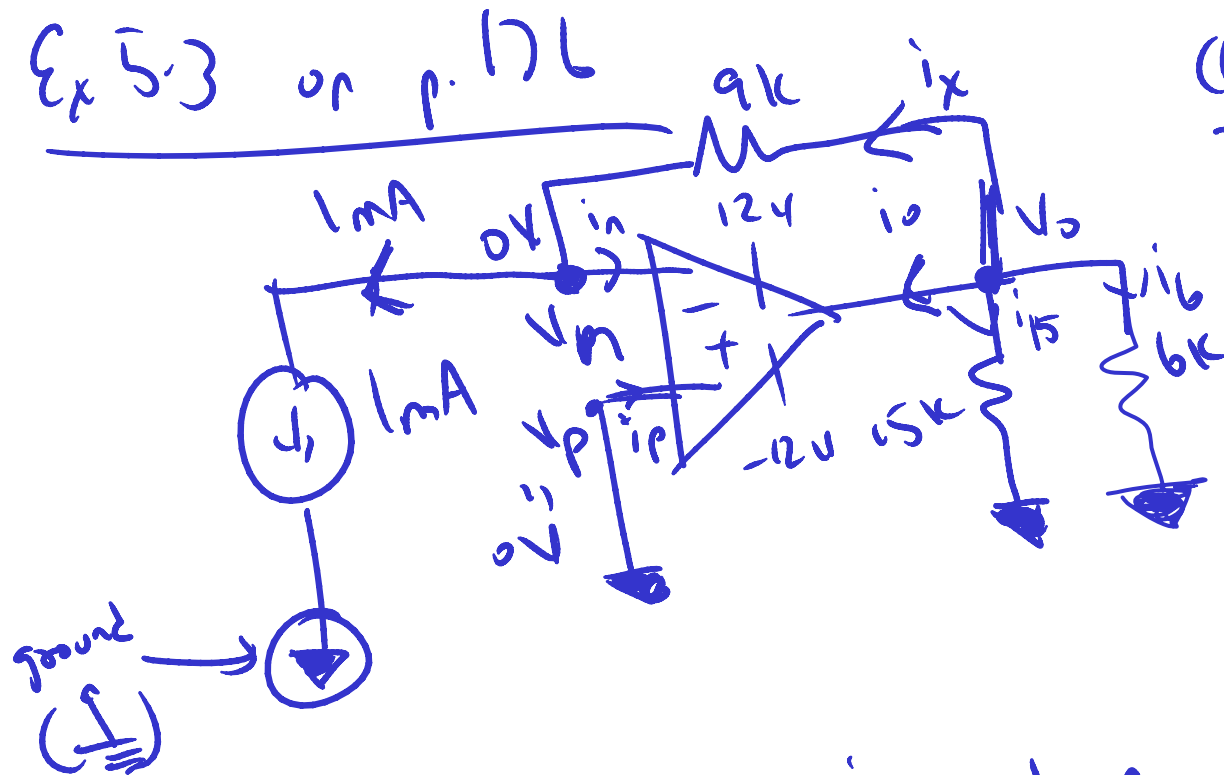

(6i) find i_o
KCL @ V_o :

$$i_o + i_x + i_{15} + i_6 = 0$$

$$\Rightarrow i_o + 1\text{mA} + \frac{V_o}{15\text{k}} + \frac{V_o}{6\text{k}} = 0$$


$$\Rightarrow i_o = -1\text{mA} - \frac{9}{15}\text{mA} - \frac{9}{6}\text{mA}$$

$$= -1\text{mA} - 0.6\text{mA} - 1.5\text{mA}$$

$$i_o = -3.1\text{mA}$$

Op-amps in negative feedback:

Mod. on Ex 5.3

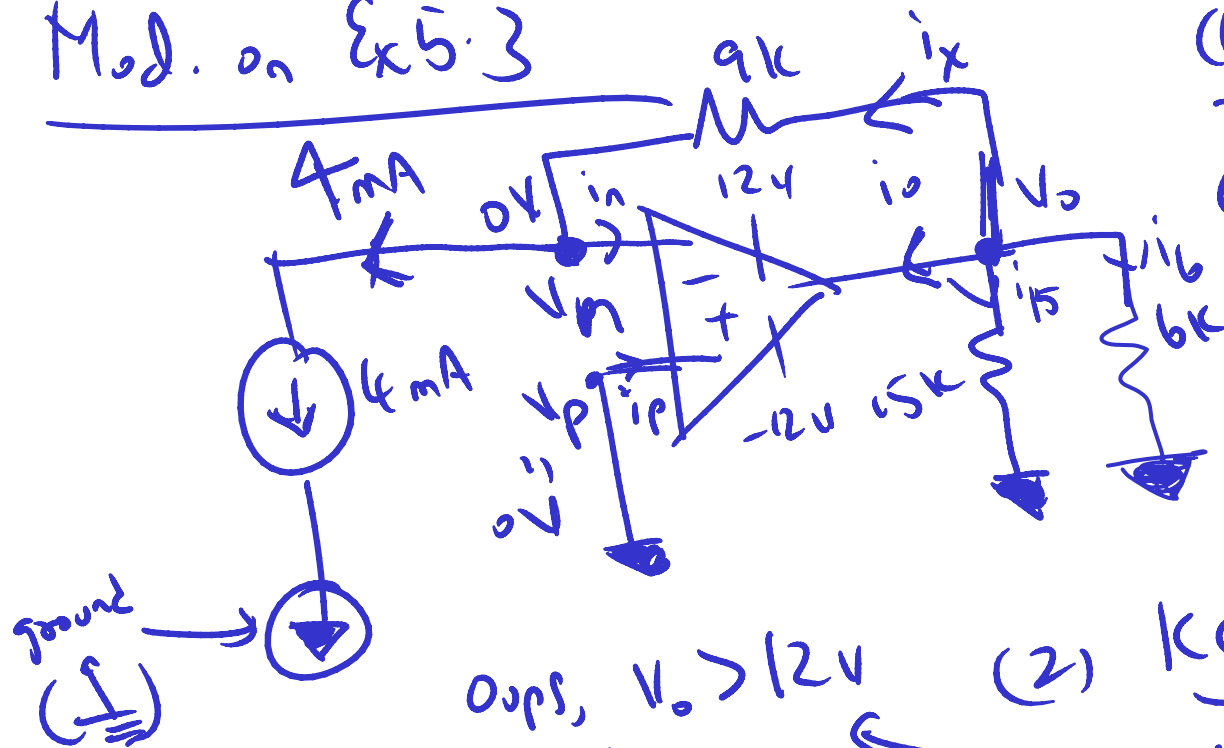

(6i) find i_o

(1) Assume: $V_p = V_n = 0V$

$$i_n = i_p = 0$$

Oops, $V_o > 12V$

\Rightarrow our assumption that $V_p = V_n = 0$ is wrong!

$$\Rightarrow \boxed{V_o = 12V}$$

(2) KCL @ V_n :


$$4mA + i_n = i_x$$

$$4mA = \frac{V_o - V_n}{9k}$$

$$\Rightarrow \boxed{V_o = 36V}$$

Op-amps in negative feedback:

Mod. on Ex 5.3

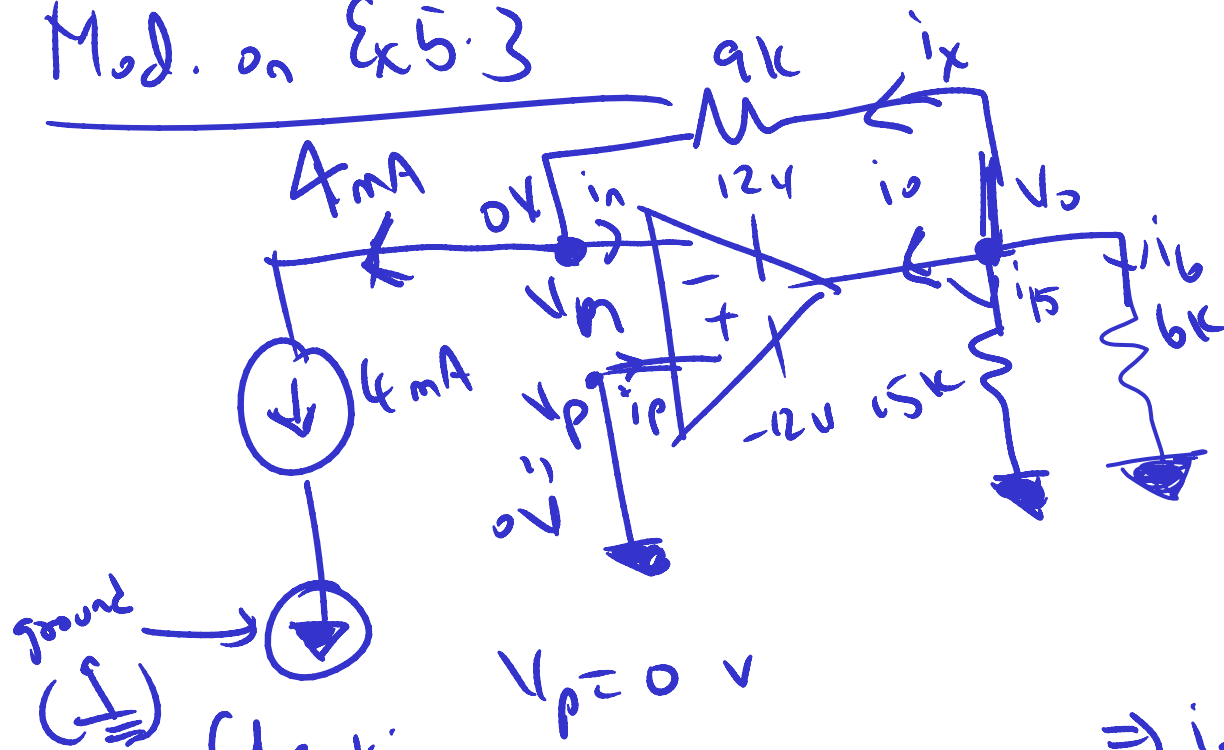

$$V_o = 12 \text{ V}$$

\therefore KCL @ v_o :

$$i_o + i_x + i_{15} + i_6 = 0$$

$$\Rightarrow i_o = -4 \text{ mA} - \frac{12}{15} \text{ mA} - \frac{12}{6} \text{ mA}$$

$$\Rightarrow i_o = -4 \text{ mA} - 0.8 \text{ mA} - 2 \text{ mA}$$

$$\boxed{i_o = -6.8 \text{ mA}}$$

Check:


$$V_p = 0 \text{ V}$$

$$i_x = \frac{V_o - V_n}{9 \text{ k}}$$

$$\Rightarrow (4 \text{ mA})(9 \text{ k}) = V_o - V_n \Rightarrow V_n = 12 - 36 = \underline{\underline{-24 \text{ V}}}$$

Op-amps in negative feedback:

Mod. on Ex 5.3

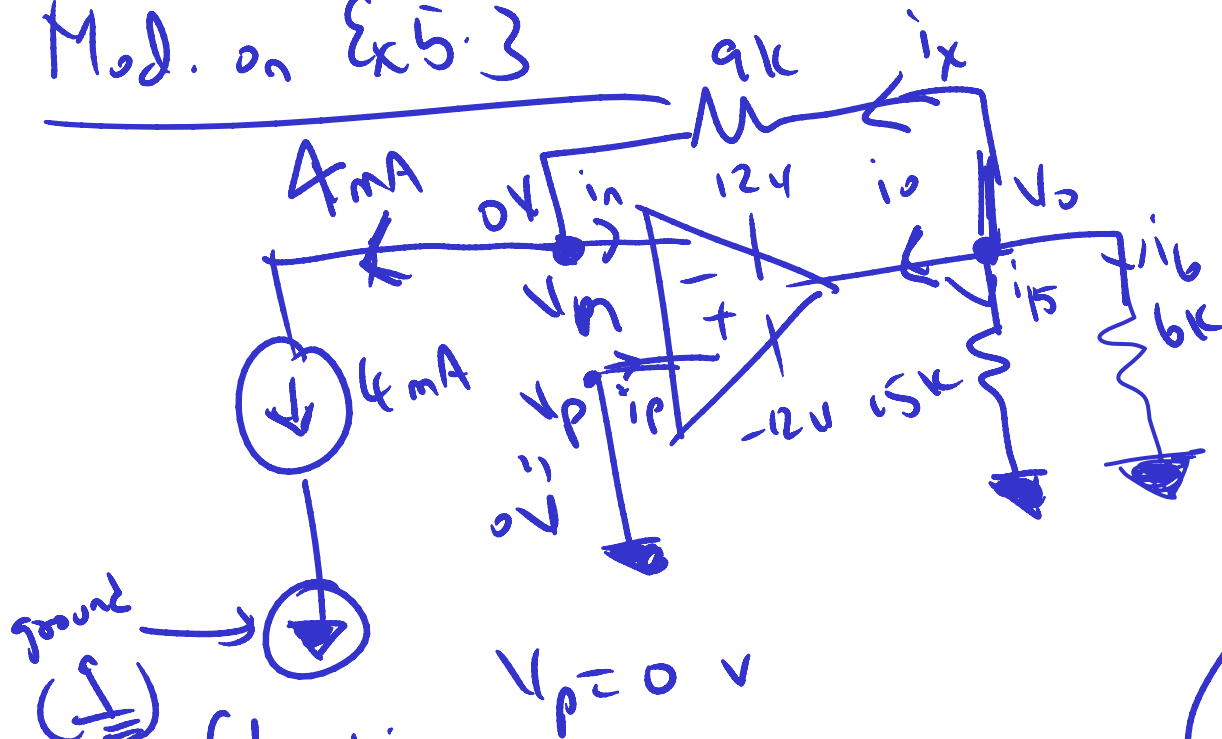

Check:

$$V_p = 0 \text{ V}$$


$$i_x = \frac{V_o - V_n}{9 \text{ k}}$$

$$\Rightarrow (4 \text{ mA})(9 \text{ k}) = V_o - V_n \Rightarrow V_n = 12 - 36 = \underline{\underline{-24 \text{ V}}}$$


open-loop gain

$$\begin{aligned} \therefore V_o &= A(V_p - V_n) \\ &= 10^6(0 - (-24)) \\ &= 10^6 \cdot 24 \\ &\downarrow \\ &\text{really big} \\ &\text{+ve} \\ &\text{number} \end{aligned}$$

Summing Amplifier

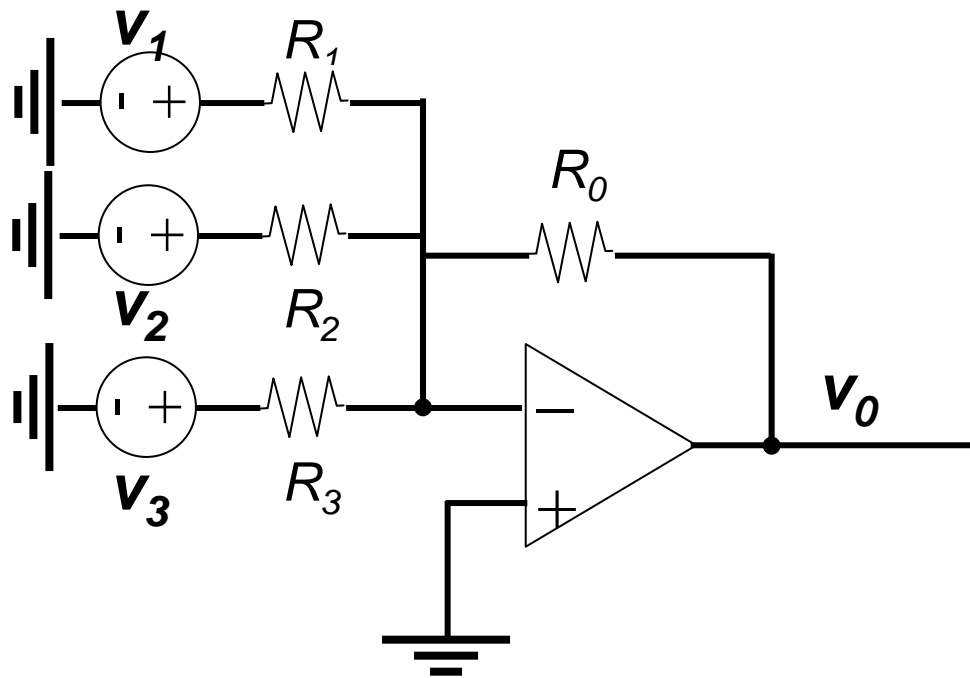


Difference Amplifier

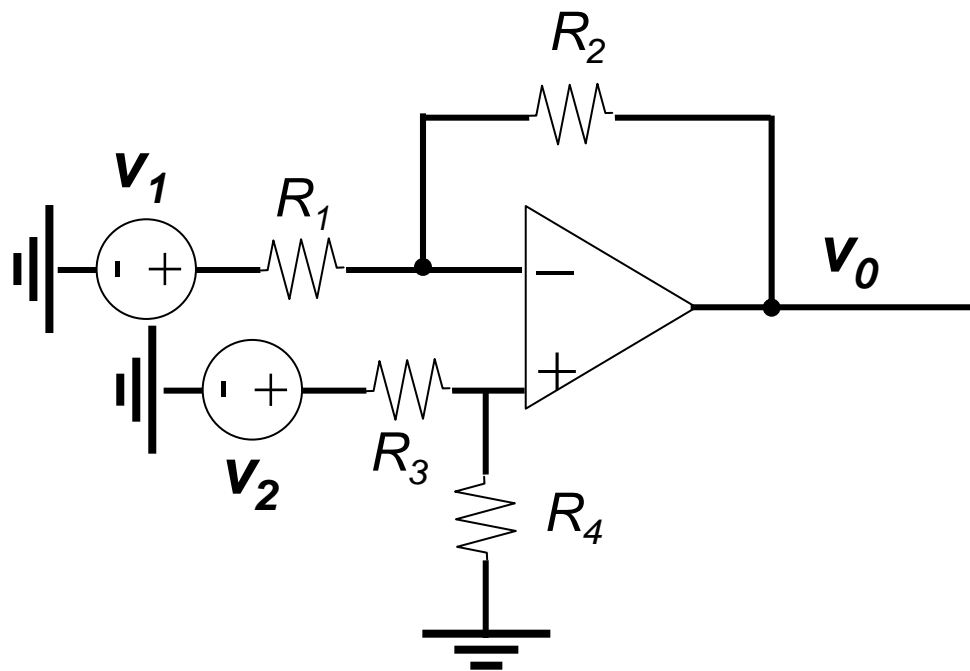


Integrator


- Want $v_o = K \int v_{in} dt$

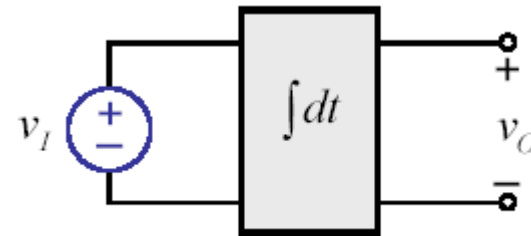

- What is the difference between:

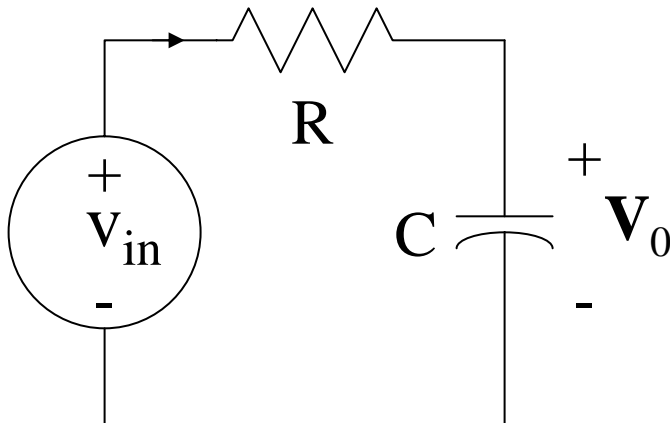



$$v_o \approx \frac{1}{RC} \int v_i dt$$

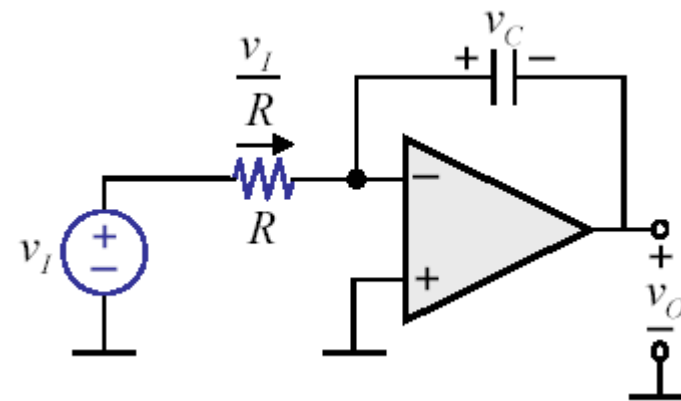

$$v_o = -\frac{1}{C} \int \frac{v_i}{R} dt$$


Differentiator

- Want

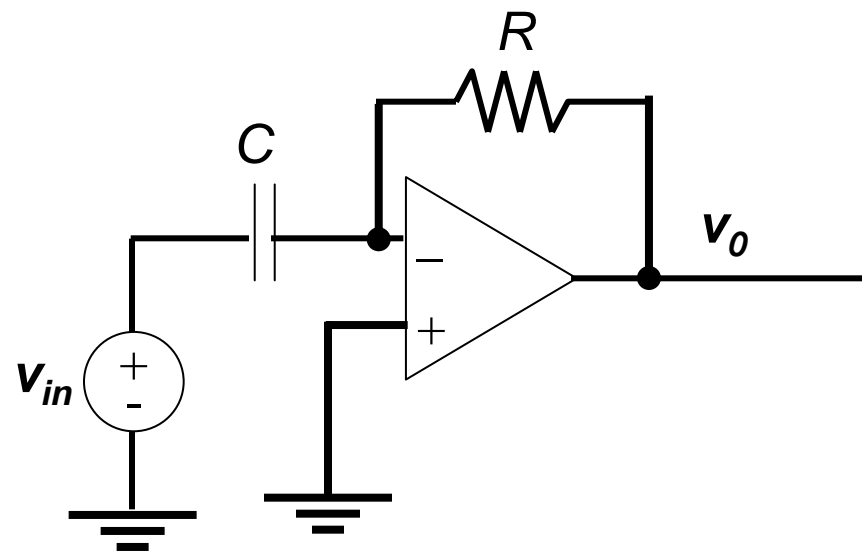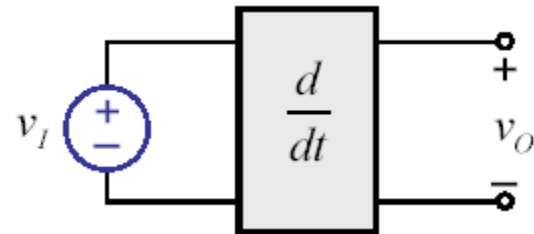

Nonlinear Opamp Circuits

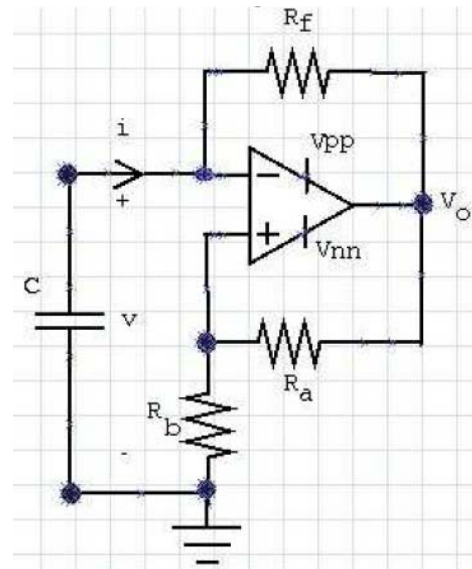- Start reading through online notes: “Introduction to nonlinear circuit analysis”.
- Outline:
 - Differences between positive and negative feedback.
 - Oscillator circuit.




High Quality Dependent Source In an Amplifier

AMPLIFIER SYMBOL


Differential Amplifier

$$V_0 = A(V_+ - V_-)$$

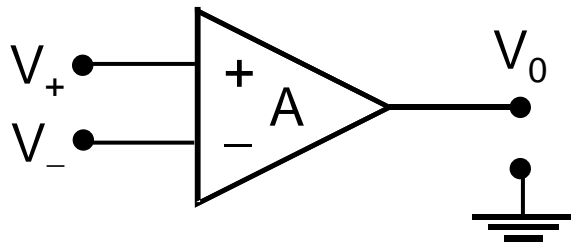

AMPLIFIER MODEL

Circuit Model *in linear region*

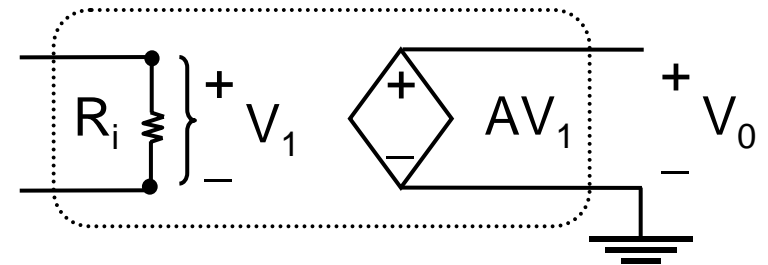

V_0 depends only on input ($V_+ - V_-$)

See the utility of this: this Model when used correctly mimics the behavior of an amplifier but omits the complication of the many many transistors and other components.

Model for Internal Operation

- A is differential gain or open loop gain
- Ideal op amp

$$A \rightarrow \infty$$

$$R_i \rightarrow \infty$$

$$R_o = 0$$


- Common mode gain = 0

$$v_{cm} = \frac{(v_1 + v_2)}{2}, v_d = v_1 - v_2$$

$$v_o = A_{cm} v_{cm} + A_d v_d$$

$$\text{Since } v_o = A(v_1 - v_2), A_{cm} = 0$$


- Circuit Model

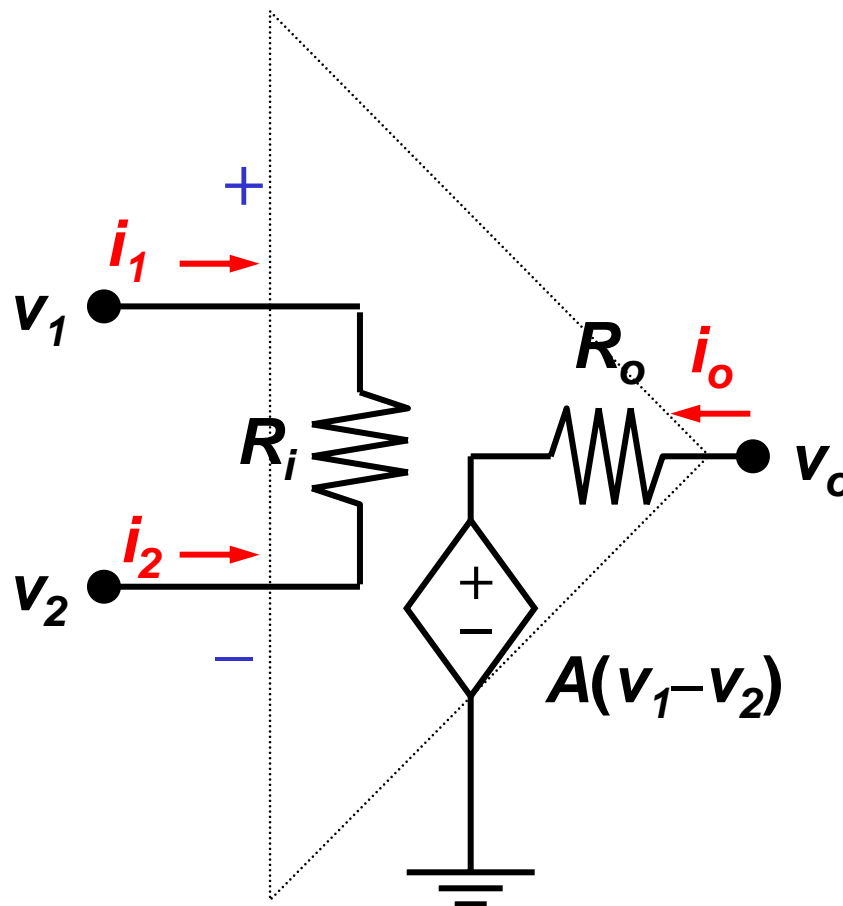

Model and Feedback


- Negative feedback
 - connecting the output port to the negative input (port 2)
- Positive feedback
 - connecting the output port to the positive input (port 1)
- Input impedance: R looking into the input terminals
- Output impedance: Impedance in series with the output terminals

- Circuit Model

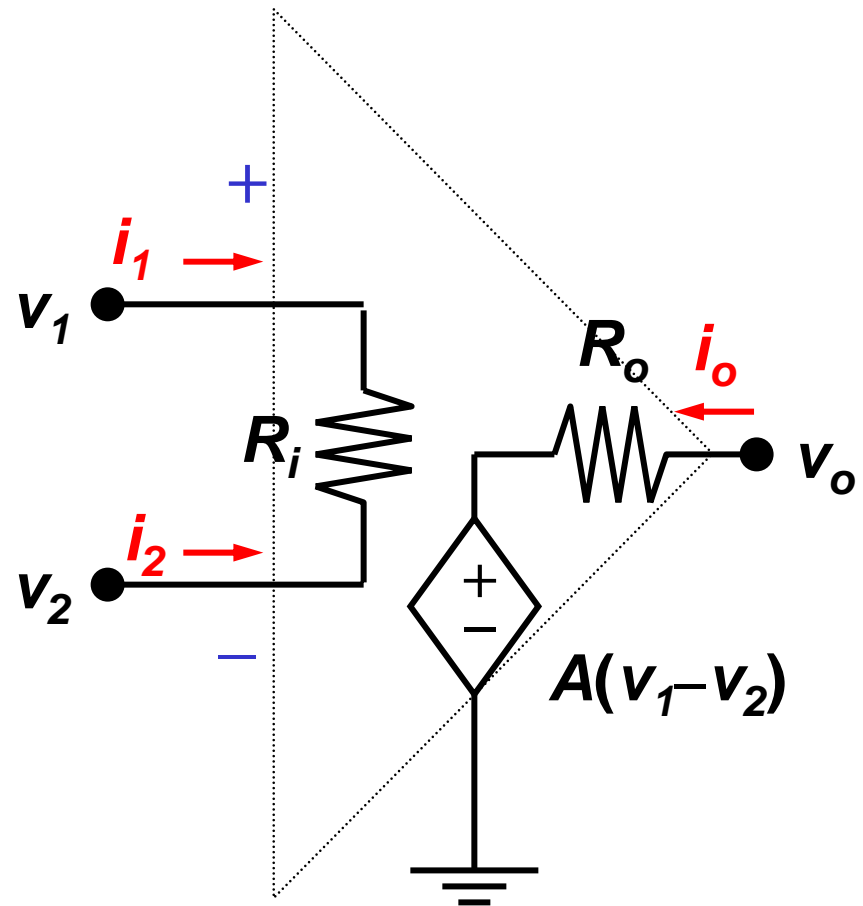

Op-Amp and Use of Feedback

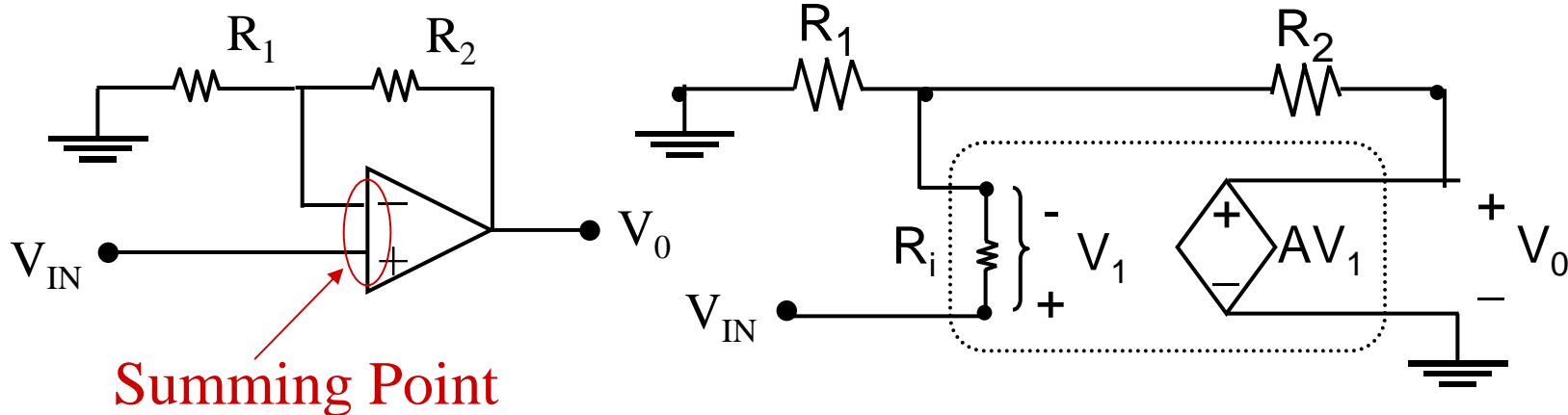A very high-gain differential amplifier can function in an extremely linear fashion as an operational amplifier by using negative feedback.



Circuit Model

Negative feedback \Rightarrow **Stabilizes** the output

Hambley Example pp. 644 for Power Steering

We can show that that for $A \rightarrow \infty$ and $R_i \rightarrow \infty$,


$$V_0 \cong V_{IN} \cdot \frac{R_1 + R_2}{R_1}$$

Stable, finite, and independent of the properties of the OP AMP !

Application: Digital-to-Analog Conversion

A DAC can be used to convert the digital representation of an audio signal into an analog voltage that is then used to drive speakers -- so that you can hear it!

“Weighted-adder D/A converter”

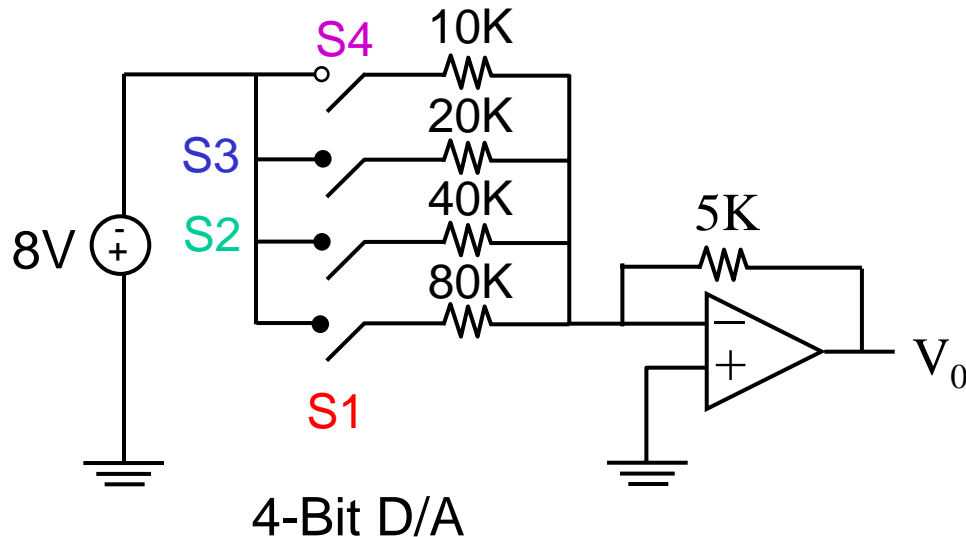

(Transistors are used as electronic switches)

S1 closed if LSB = 1
 S2 " if next bit = 1
 S3 " if " " = 1
 S4 " if MSB = 1

Binary number	Analog output (volts)
0 0 0 0	0
0 0 0 1	.5
0 0 1 0	1
0 0 1 1	1.5
0 1 0 0	2
0 1 0 1	2.5
0 1 1 0	3
0 1 1 1	3.5
1 0 0 0	4
1 0 0 1	4.5
1 0 1 0	5
1 0 1 1	5.5
1 1 0 0	6
1 1 0 1	6.5
1 1 1 0	7
1 1 1 1	7.5

↑ ↑
 MSB LSB

Characteristic of 4-Bit DAC

