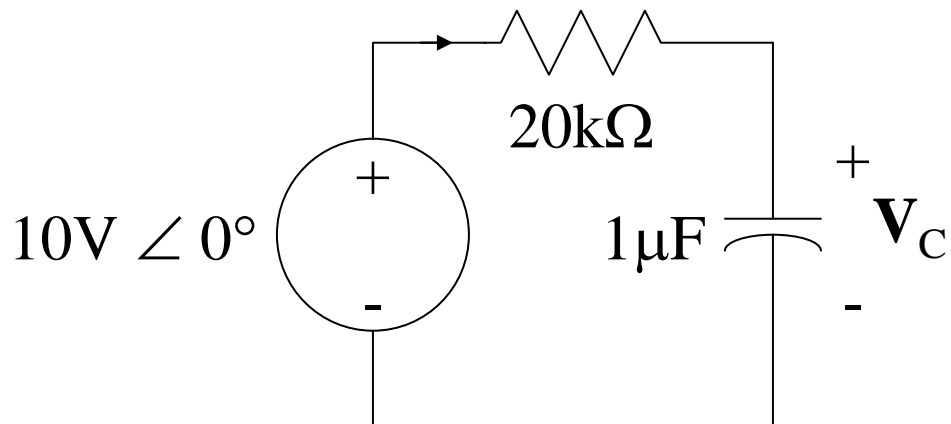


EE100Su08 Lecture #12 (July 23rd 2008)

- Outline
 - MultiSim licenses on Friday
 - HW #1, Midterm #1 regrade deadline: TODAY (5:00 pm PST).
 - QUESTIONS?
 - Circuit analysis using complex impedances:
Examples
 - Frequency Response and Bode plots
- Reading
 - Chapter 9 from your book (skip 9.10, 9.11 (duh)), Appendix E* (skip second-order resonance bode plots)
 - Chapter 1 from your reader (skip second-order resonance bode plots)

Example: Single Loop Circuit



$$f=60 \text{ Hz, } V_C=?$$

ω = 377 rad/sec


How do we find V_C ?

First compute impedances for resistor and capacitor:

$$\mathbf{Z}_R = R = 20\text{k}\Omega = 20\text{k}\Omega \angle 0^\circ$$

$$\mathbf{Z}_C = 1/j(2\pi f \times 1\mu\text{F}) = 2.65\text{k}\Omega \angle -90^\circ$$
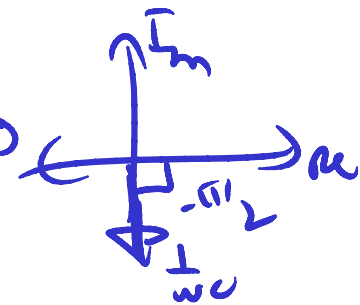
$$\frac{1}{j\omega C} = \frac{j}{j^2\omega C} = \frac{-j}{\omega C} = 0 + \frac{-j}{\omega C}$$



Circuit Analysis Using Complex Impedances

- Suitable for AC steady state.
- KVL

$$v_1(t) + v_2(t) + v_3(t) = 0$$

$$V_1 \cos(\omega t + \theta_1) + V_2 \cos(\omega t + \theta_2) + V_3 \cos(\omega t + \theta_3) = 0$$

$$\text{Re} \left[V_1 e^{j(\omega t + \theta_1)} + V_2 e^{j(\omega t + \theta_2)} + V_3 e^{j(\omega t + \theta_3)} \right] = 0$$


Phasor Form KVL

$$V_1 e^{j(\theta_1)} + V_2 e^{j(\theta_2)} + V_3 e^{j(\theta_3)} = 0$$

$$\mathbf{V}_1 + \mathbf{V}_2 + \mathbf{V}_3 = 0$$

- Phasor Form KCL $\mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 = 0$
- Use complex impedances for inductors and capacitors and follow same analysis as in chap 2.

Impedance Example


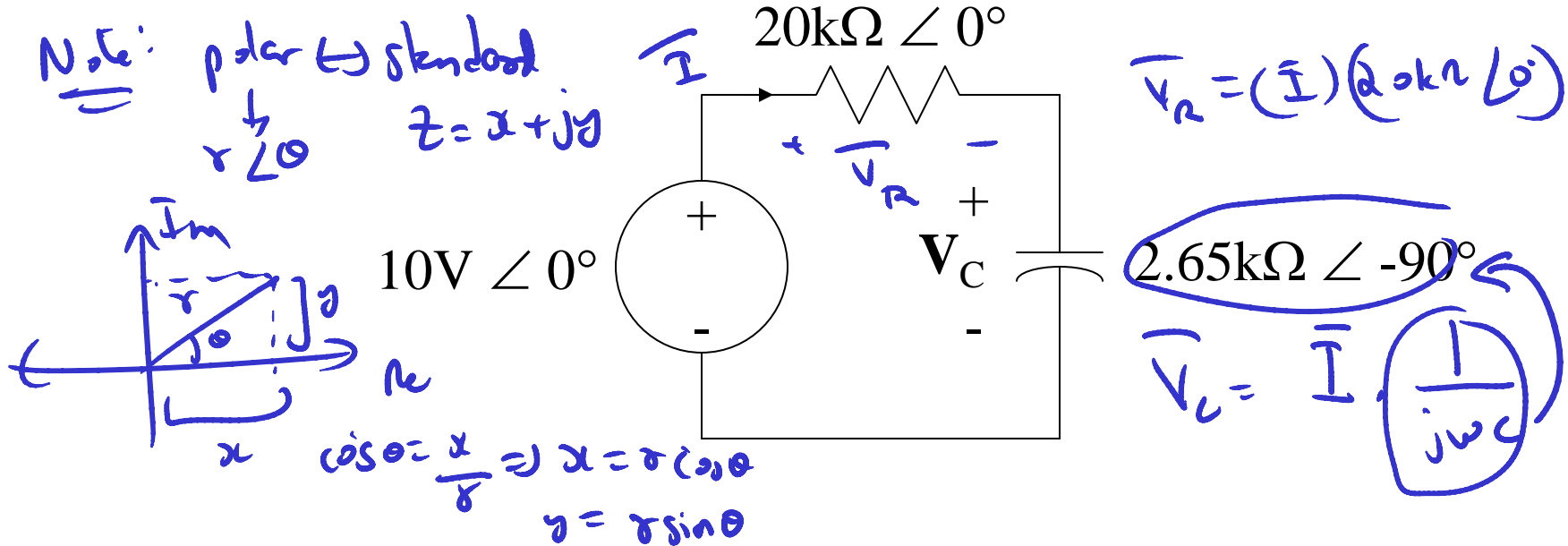


Now use the voltage divider to find V_C :

$$V_C = 10\text{V} \angle 0^\circ \left(\frac{2.65\text{k}\Omega \angle -90^\circ}{2.65\text{k}\Omega \angle -90^\circ + 20\text{k}\Omega \angle 0^\circ} \right)$$


$$V_C = 1.31\text{V} \angle -82.4^\circ$$

What happens when ω changes?

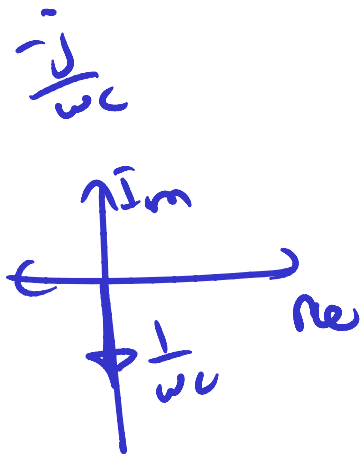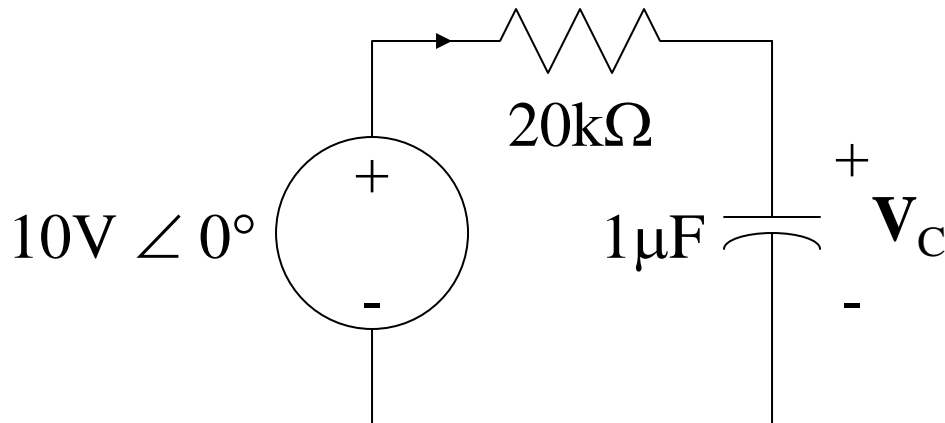

$\omega = 10$
 Find V_C

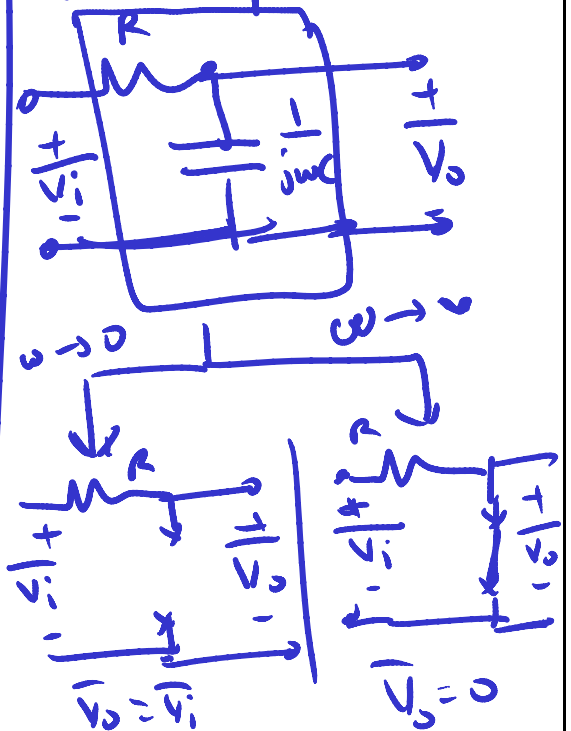
This circuit (recall your lab b) is a low-pass filter



Aside:




Steady-State AC Analysis

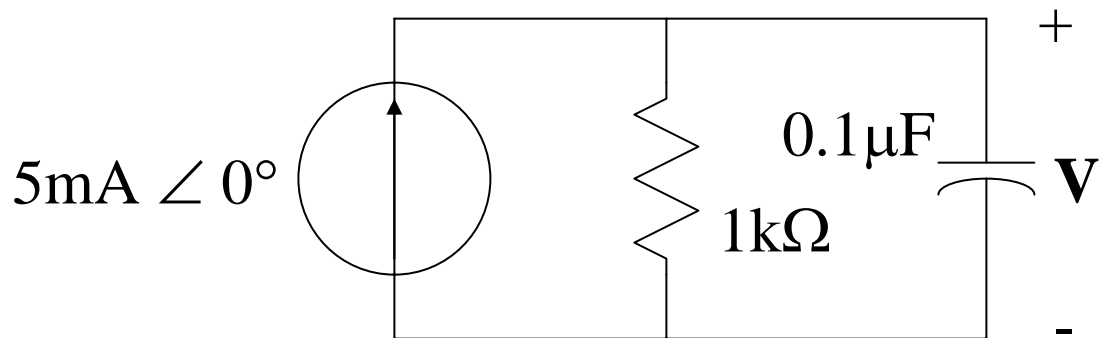


Find $v(t)$ for $\omega = 2\pi 3000$
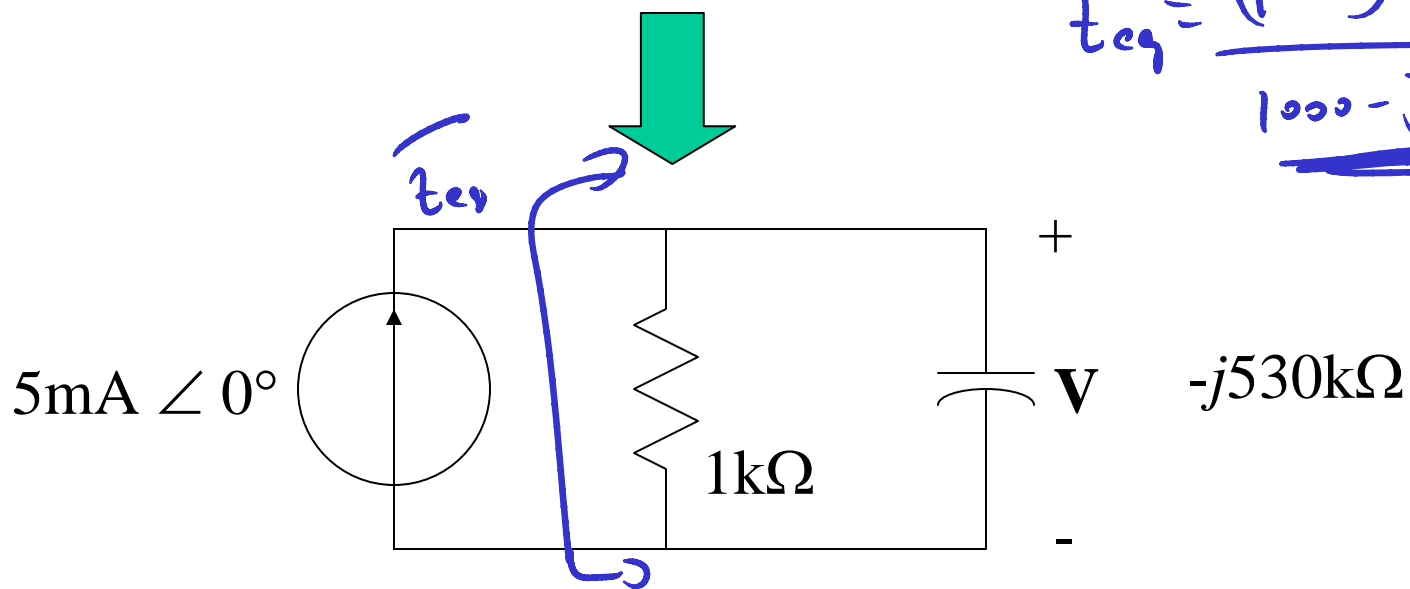
$$\bar{z}_{eq} = \frac{(1000)(-j530k\Omega)}{1000 - j530k\Omega}$$



Find the Equivalent Impedance

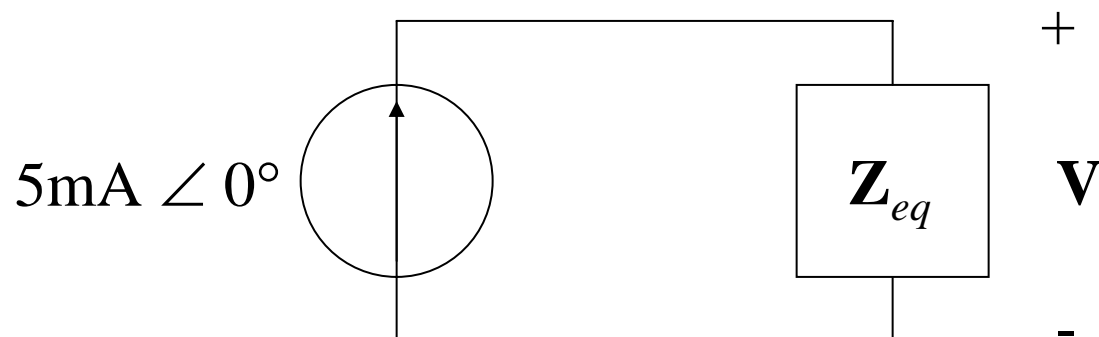

$$Z_{eq} = \frac{1000(-j530)k}{1000 - j530k} = \frac{10^3 \angle 0^\circ \times 530 \angle -90^\circ}{1132 \angle -27.9^\circ}$$


$$Z_{eq} = 468.2\Omega \angle -62.1^\circ$$

$$V = \mathbf{I}Z_{eq} = 5\text{mA} \angle 0^\circ \times 468.2\Omega \angle -62.1^\circ$$


$$V = 2.34\text{V} \angle -62.1^\circ$$

$$v(t) = 2.34\text{V} \cos(2\pi 3000t - 62.1^\circ)$$


Change the Frequency

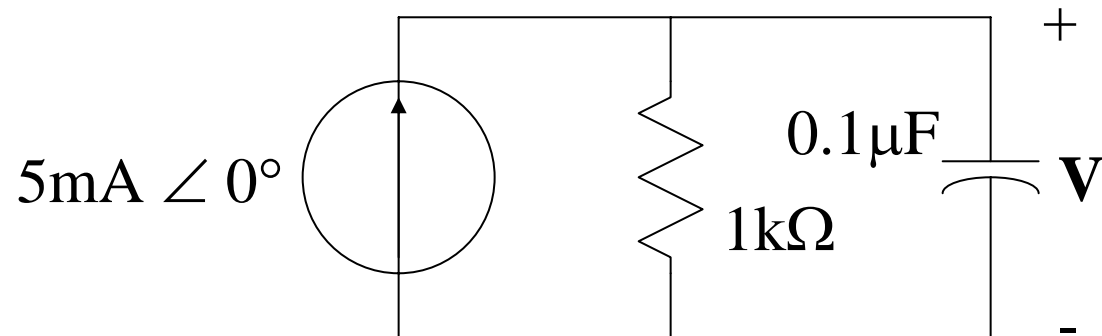

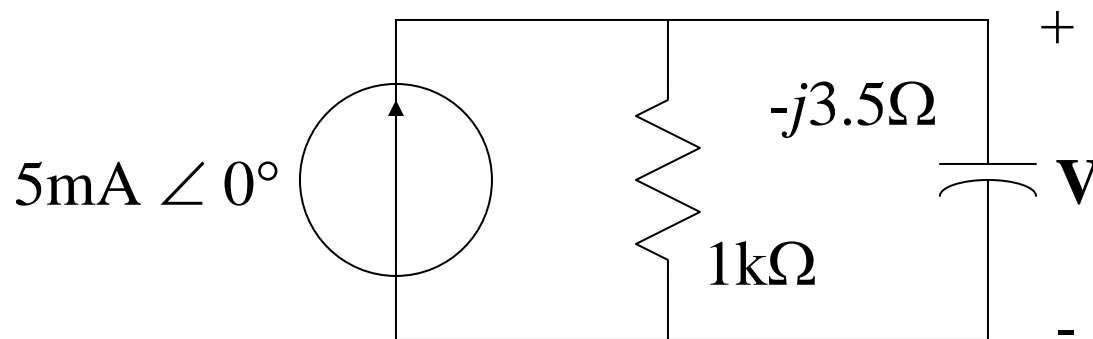Find $v(t)$ for $\omega = 2\pi \cdot 455000$



Find an Equivalent Impedance

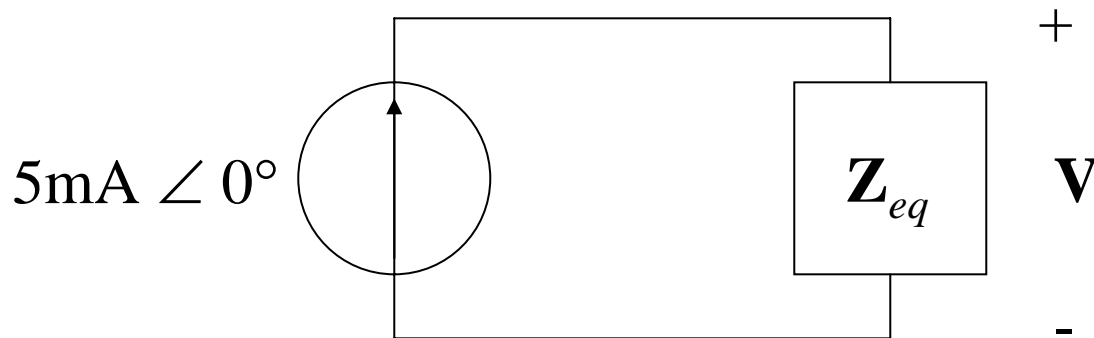

$$\mathbf{Z}_{eq} = \frac{1000(-j3.5)}{1000 - j3.5} = \frac{10^3 \angle 0^\circ \times 3.5 \angle -90^\circ}{1000 \angle -0.2^\circ}$$


$$\mathbf{Z}_{eq} = 3.5\Omega \angle -89.8^\circ$$

$$\mathbf{V} = \mathbf{I}\mathbf{Z}_{eq} = 5\text{mA} \angle 0^\circ \times 3.5\Omega \angle -89.8^\circ$$

$$\mathbf{V} = 17.5\text{mV} \angle -89.8^\circ$$



$$v(t) = 17.5\text{mV} \cos(2\pi 455000t - 89.8^\circ)$$

Series Impedance

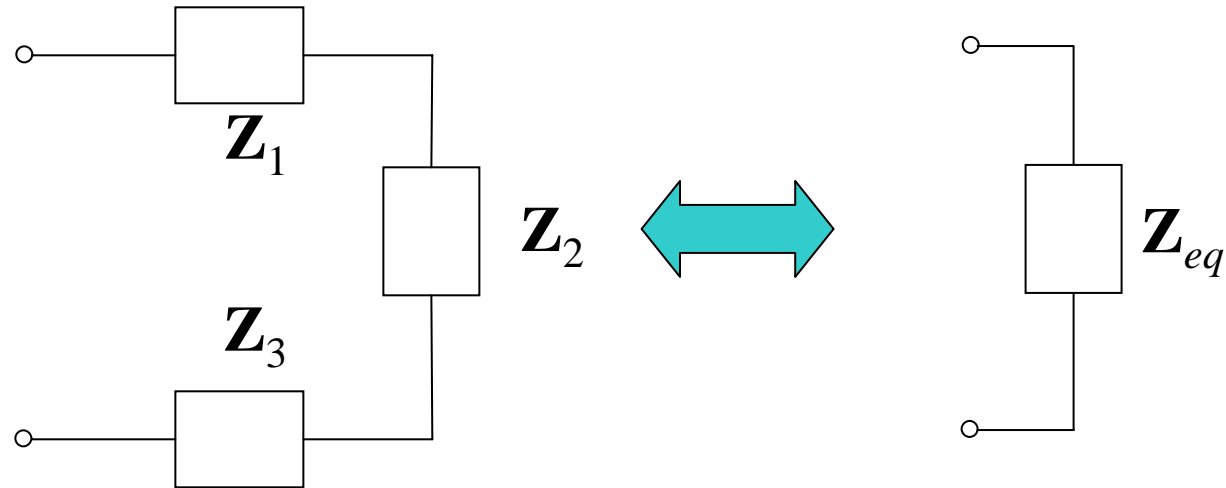


$$\mathbf{Z}_{eq} = \mathbf{Z}_1 + \mathbf{Z}_2 + \mathbf{Z}_3$$

For example:

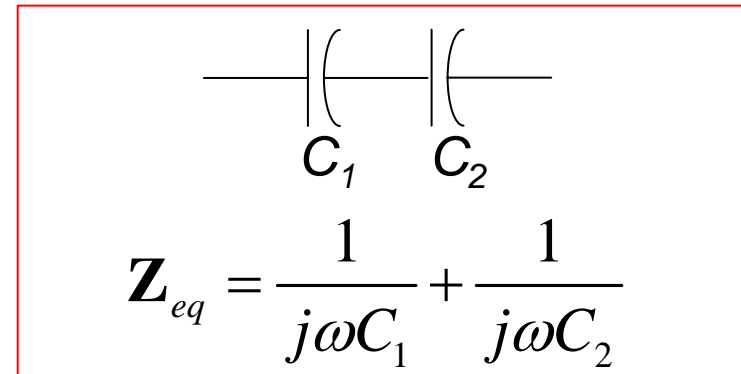
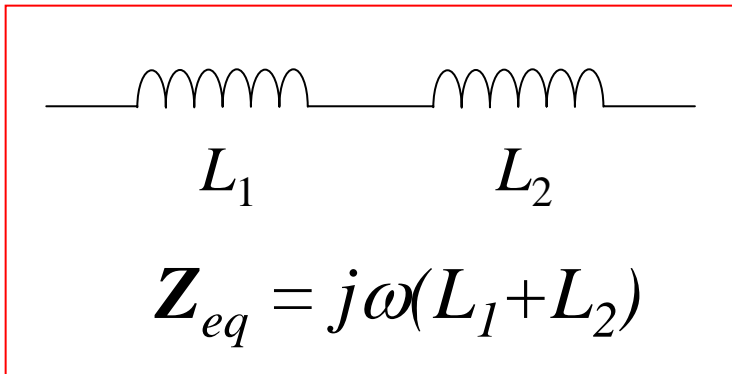


Parallel Impedance

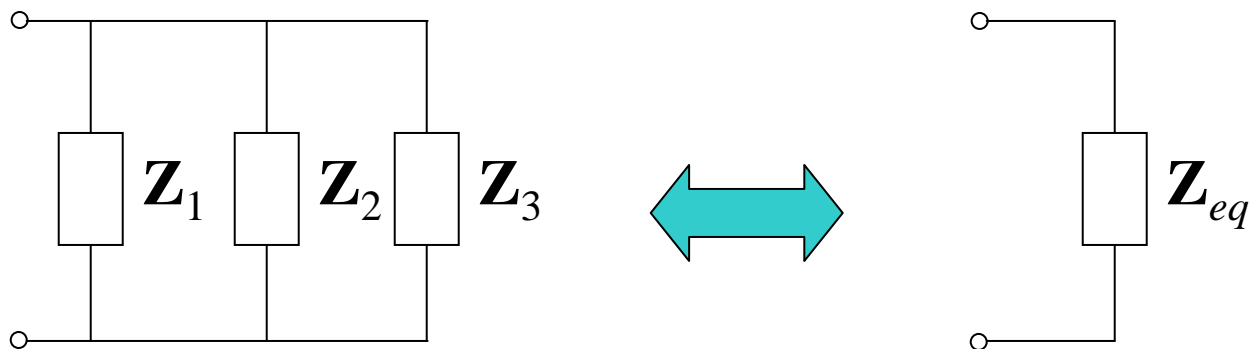


$$1/Z_{eq} = 1/Z_1 + 1/Z_2 + 1/Z_3$$

For example:

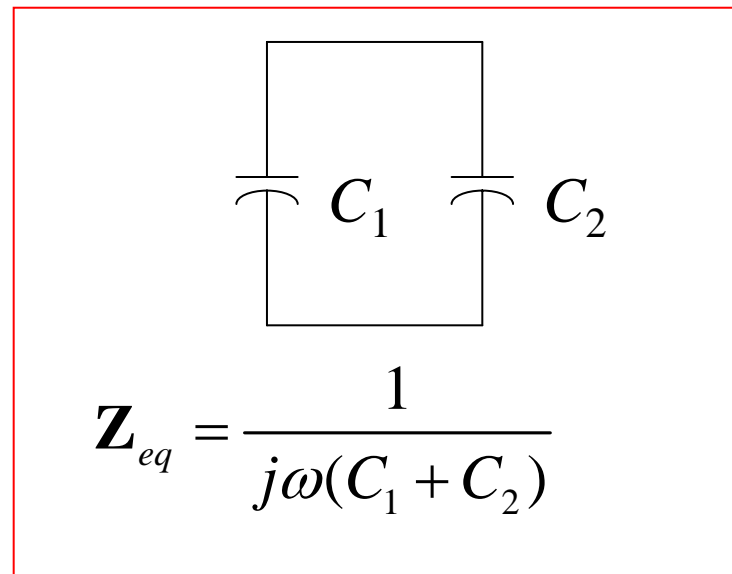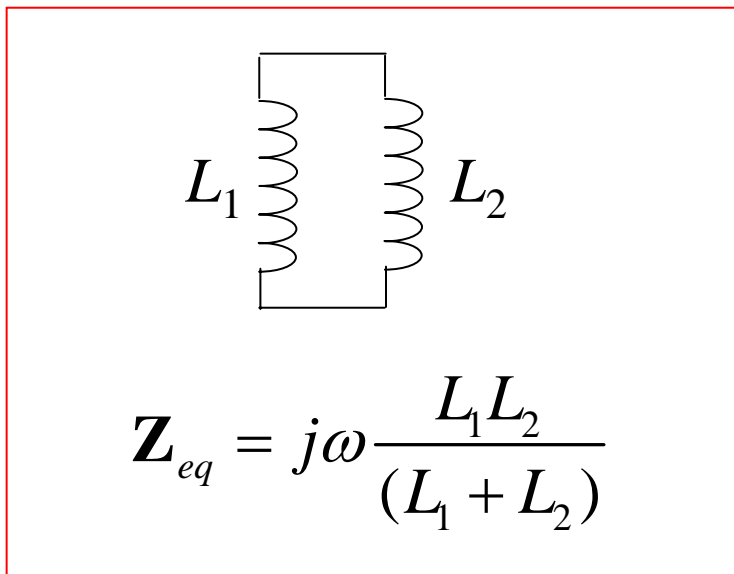

Steady-State AC Node-Voltage Analysis

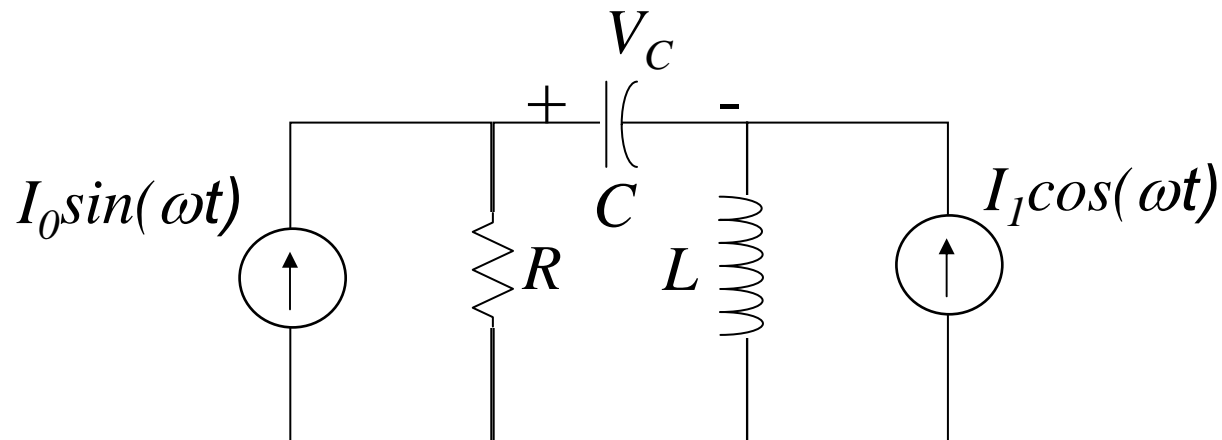

- Try using Thevenin equivalent circuit.
- What happens if the sources are at different frequencies?

A: Superposition, write final answer in time domain.

Resistor I-V relationship

$v_R = i_R R$ $\mathbf{V}_R = \mathbf{I}_R R$ where R is the resistance in ohms,
 $\mathbf{V}_R =$ phasor voltage, $\mathbf{I}_R =$ phasor current
(boldface indicates complex quantity)

Capacitor I-V relationship

$i_C = C dv_C/dt$ Phasor current $\mathbf{I}_C =$ phasor voltage $\mathbf{V}_C /$
capacitive impedance $\mathbf{Z}_C \rightarrow \mathbf{I}_C = \mathbf{V}_C / \mathbf{Z}_C$
where $\mathbf{Z}_C = 1/j\omega C$, $j = (-1)^{1/2}$ and boldface
indicates complex quantity


Inductor I-V relationship

$v_L = L di_L/dt$ Phasor voltage $\mathbf{V}_L =$ phasor current $\mathbf{I}_L /$
inductive impedance $\mathbf{Z}_L \rightarrow \mathbf{V}_L = \mathbf{I}_L \mathbf{Z}_L$
where $\mathbf{Z}_L = j\omega L$, $j = (-1)^{1/2}$ and boldface
indicates complex quantity

Summary of impedance relationships

R	C	L
$v_0(t) = V_0 \cos(\omega t)$	$v_0(t) = V_0 \cos(\omega t)$	$v_0(t) = V_0 \cos(\omega t)$
$\vec{V}_0 = V_0 \angle 0^\circ$	$\vec{V}_0 = V_0 \angle 0^\circ$	$\vec{V}_0 = V_0 \angle 0^\circ$
$i_0(t) = \frac{V_0}{R} \cos(\omega t)$	$i_0(t) = -\omega C V_0 \sin(\omega t)$	$i_0(t) = \frac{V_0}{\omega L} \sin(\omega t)$
$\vec{I}_0 = \frac{V_0}{R} \angle 0^\circ$	$\vec{I}_0 = \omega C V_0 \angle 90^\circ$	$\vec{I}_0 = \frac{V_0}{\omega L} \angle -90^\circ$

Thevenin Equivalent

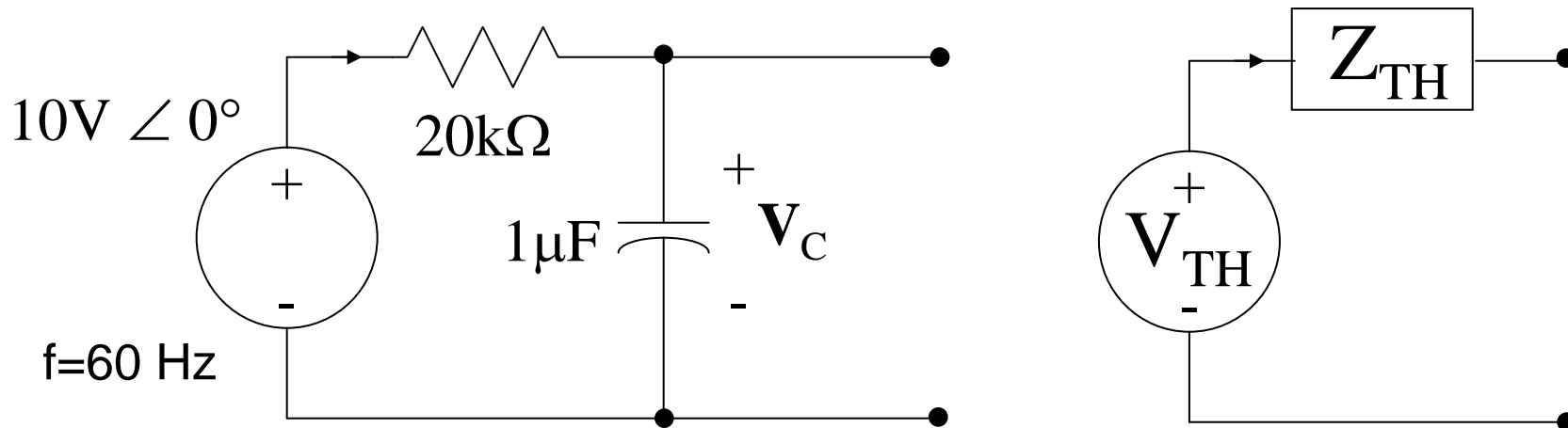

$$\mathbf{Z}_R = R = 20\text{k}\Omega = 20\text{k}\Omega \angle 0^\circ$$

$$\mathbf{Z}_C = 1/j(2\pi f \times 1\mu\text{F}) = 2.65\text{k}\Omega \angle -90^\circ$$

$$\mathbf{V}_{TH} = \mathbf{V}_{OC} = 10\text{V} \angle 0^\circ \left(\frac{2.65\text{k}\Omega \angle -90^\circ}{2.65\text{k}\Omega \angle -90^\circ + 20\text{k}\Omega \angle 0^\circ} \right) = 1.31 \angle -82.4$$

$$\mathbf{Z}_{TH} = \mathbf{Z}_R \parallel \mathbf{Z}_C = \left(\frac{20\text{k}\Omega \angle 0^\circ \cdot 2.65\text{k}\Omega \angle -90^\circ}{2.65\text{k}\Omega \angle -90^\circ + 20\text{k}\Omega \angle 0^\circ} \right) = 2.62 \angle -82.4$$

Bode Plots (Appendix E, Chapter 1 in Reader)

- OUTLINE
 - dB scale
 - Frequency Response for Characterization
 - Asymptotic Frequency Behavior
 - Log magnitude vs log frequency plot
 - Phase vs log frequency plot
 - Transfer function example

Bel and Decibel (dB)

- A **bel** (symbol **B**) is a unit of measure of ratios of power levels, i.e. relative power levels.
 - The name was coined in the early 20th century in honor of Alexander Graham Bell, a telecommunications pioneer.
 - The bel is a logarithmic measure. The number of bels for a given ratio of power levels is calculated by taking the logarithm, to the base 10, of the ratio.
 - one bel corresponds to a ratio of 10:1.
 - $B = \log_{10}(P_1/P_2)$ where P_1 and P_2 are power levels.
- The bel is too large for everyday use, so the **decibel (dB)**, equal to 0.1B, is more commonly used.
 - $1\text{dB} = 10 \log_{10}(P_1/P_2)$
- dB are used to measure
 - Electric power, Gain or loss of amplifiers, Insertion loss of filters.

$$1\text{ dB} = 10 \left[\log_{10} \left(\frac{P_1}{P_2} \right) \right] = 10 \cdot (1\text{ B}) \Rightarrow 0.1\text{ B} = 1\text{ dB}$$

Logarithmic Measure for Power

- To express a power in terms of decibels, one starts by choosing a reference power, $P_{\text{reference}}$, and writing

$$\text{Power } P \text{ in decibels} = 10 \log_{10}(P/P_{\text{reference}})$$

- Exercise:

- Express a power of 50 mW in decibels relative to 1 watt.
- $P \text{ (dB)} = 10 \log_{10}(50 \times 10^{-3}) = -13 \text{ dB}$

P in dB (P = 1 watt)

*$\Rightarrow P = (10^{0.1})$
(dB) = 0!*

- Exercise:

- Express a power of 50 mW in decibels relative to 1 mW.
- $P \text{ (dB)} = 10 \log_{10}(50) = 17 \text{ dB}$.

- dBm to express **absolute** values of power relative to a milliwatt.

- $\text{dBm} = 10 \log_{10}(\text{power in milliwatts} / 1 \text{ milliwatt})$
- $100 \text{ mW} = 20 \text{ dBm}$
- $10 \text{ mW} = 10 \text{ dBm}$

Logarithmic Measures for Voltage or Current

From the expression for power ratios in decibels, we can readily derive the corresponding expressions for voltage or current ratios.



Suppose that the voltage V (or current I) appears across (or flows in) a resistor whose resistance is R . The corresponding power dissipated, P , is V^2/R (or I^2R). We can similarly relate the reference voltage or current to the reference power, as

$$P_{\text{reference}} = (V_{\text{reference}})^2/R \text{ or } P_{\text{reference}} = (I_{\text{reference}})^2R.$$

Hence,

$$\begin{aligned} \text{Voltage, } V \text{ in decibels} &= 20\log_{10}(V/V_{\text{reference}}) \\ \text{Current, } I, \text{ in decibels} &= 20\log_{10}(I/I_{\text{reference}}) \end{aligned}$$

Logarithmic Measures for Voltage or Current

Note that the voltage and current expressions are just like the power expression except that they have **20** as the multiplier instead of **10** because power is proportional to the square of the voltage or current.

Exercise: How many decibels larger is the voltage of a 9-volt transistor battery than that of a 1.5-volt AA battery? Let $V_{\text{reference}} = 1.5$.

The ratio in decibels is

$$20 \log_{10}(9/1.5) = 20 \log_{10}(6) = 16 \text{ dB.}$$

Logarithmic Measures for Voltage or Current

The gain produced by an amplifier or the loss of a filter is often specified in decibels.

The input voltage (current, or power) is taken as the reference value of voltage (current, or power) in the decibel defining expression:

$$\text{Voltage gain in dB} = 20 \log_{10}(V_{\text{output}}/V_{\text{input}})$$

$$\text{Current gain in dB} = 20 \log_{10}(I_{\text{output}}/I_{\text{input}})$$

$$\text{Power gain in dB} = 10 \log_{10}(P_{\text{output}}/P_{\text{input}})$$


Example: The voltage gain of an amplifier whose input is 0.2 mV and whose output is 0.5 V is

$$20 \log_{10}(0.5/0.2 \times 10^{-3}) = 68 \text{ dB.}$$

Bode Plot

- Plot of magnitude of transfer function vs. frequency

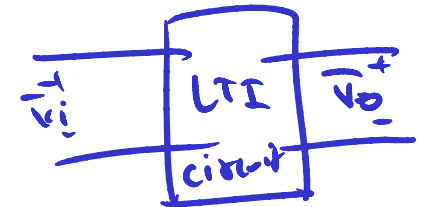- Both x and y scale are in log scale
- Y scale in dB




- Log Frequency Scale



- Decade \rightarrow Ratio of higher to lower frequency = 10

- Octave \rightarrow Ratio of higher to lower frequency = 2

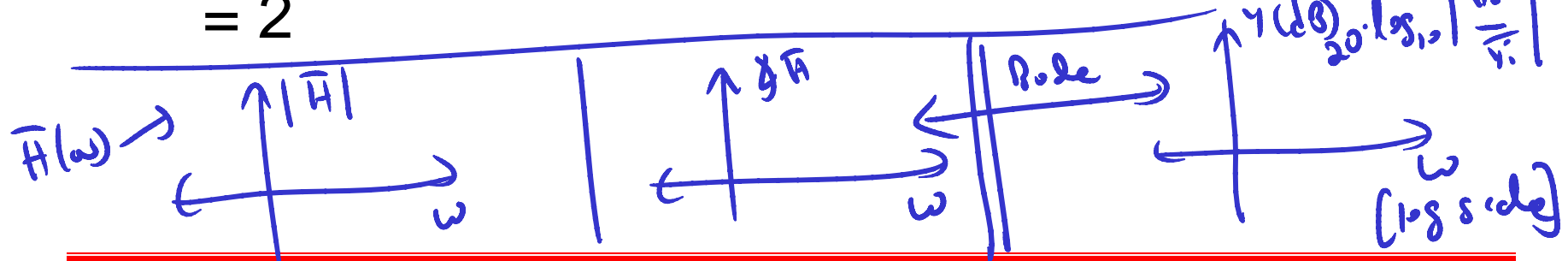Transfer function: $\bar{H}(w) = \frac{V_o}{V_i}$



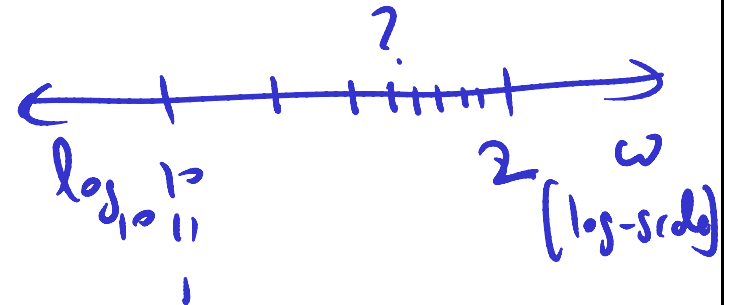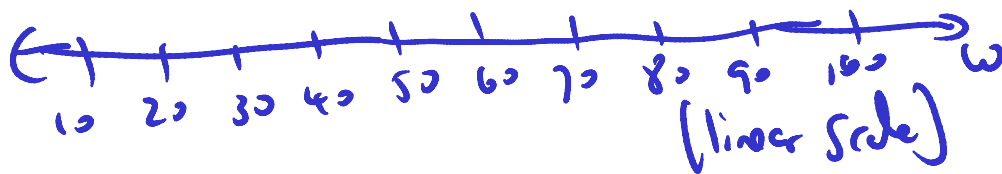Note: Converting linear scale \rightarrow log-scale Useful for x-axis of Bode plot



Note:


(1) $\log_a x \stackrel{?}{=} \frac{\ln_e x}{\ln_e a}$

encl. Part if incorrect

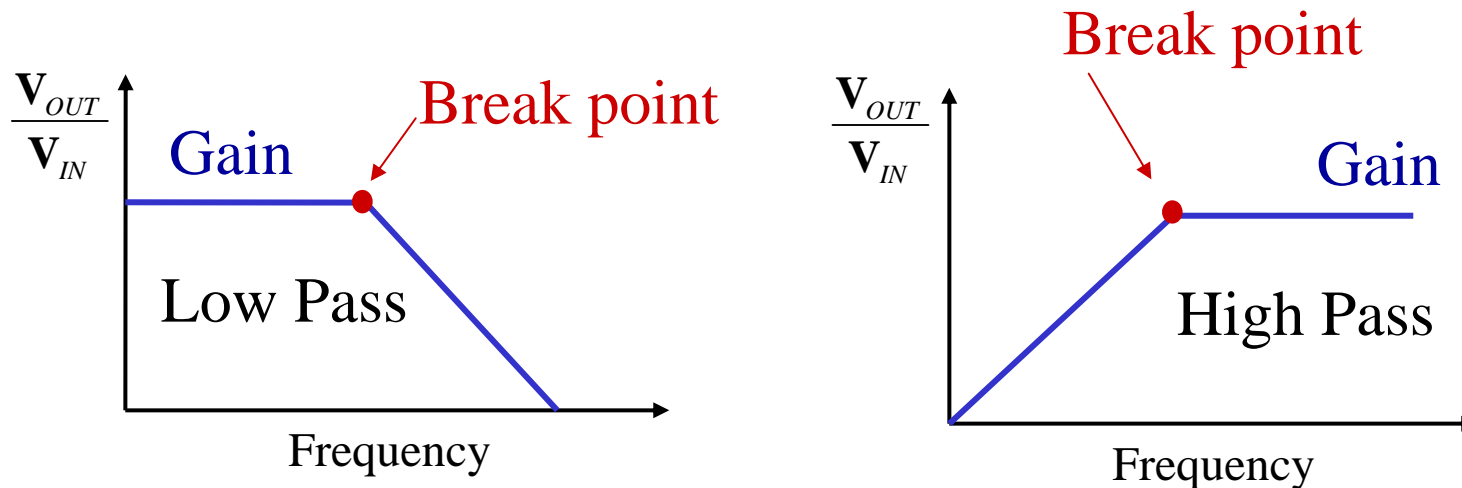(2) log is NONLINEAR!
 i.e., $\log(x_1 + x_2) \neq \log x_1 + \log x_2$
 $= \log(x_1 x_2)$



Frequency Response: Why?

- The shape of the frequency response of the complex ratio of phasors V_{OUT}/V_{IN} is a convenient means of classifying a circuit behavior and identifying key parameters.



FYI: These are log ratio vs log frequency plots

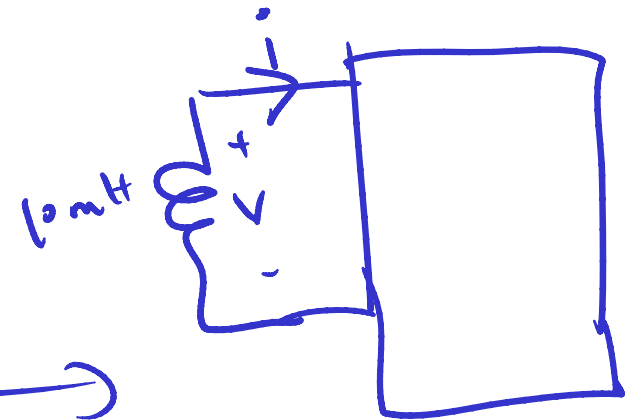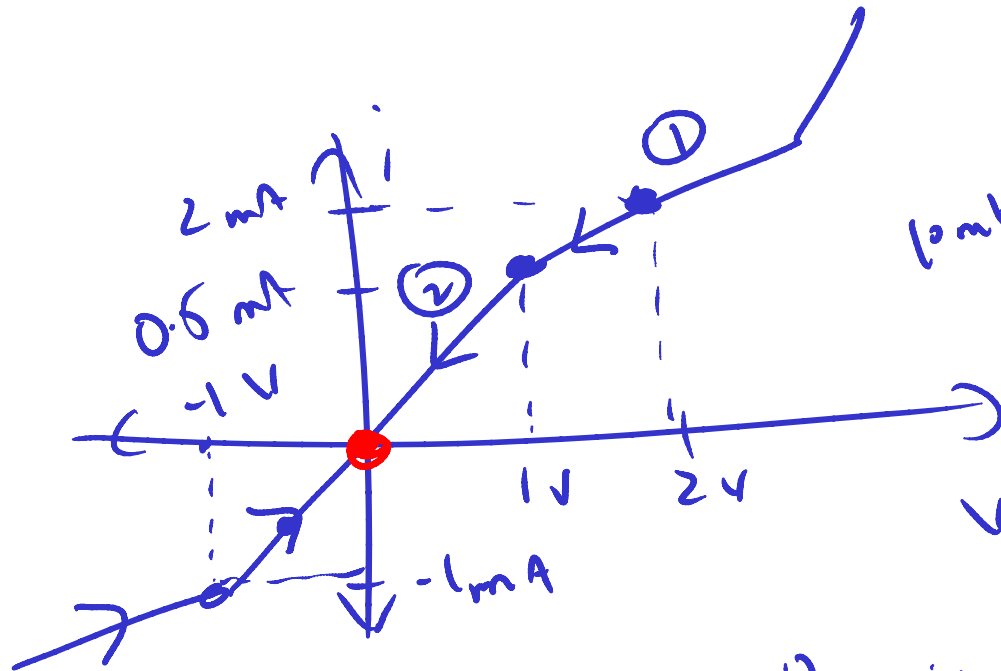HW question on nonlinear circuit analysis (1st order)



(Q.1) What happens,


$v(t) = 2V$?

$$V = -L \frac{di}{dt}$$



es. points: $i' = 0 \Rightarrow V = 0$
 [stable es. point]

Dynamic rate

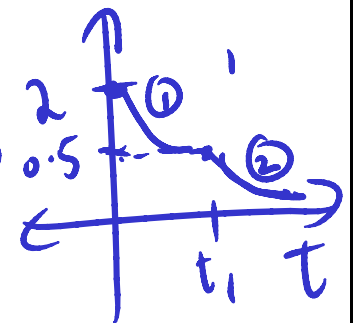$V > 0, \quad i' < 0$
 $V < 0, \quad i' > 0$



More interesting case

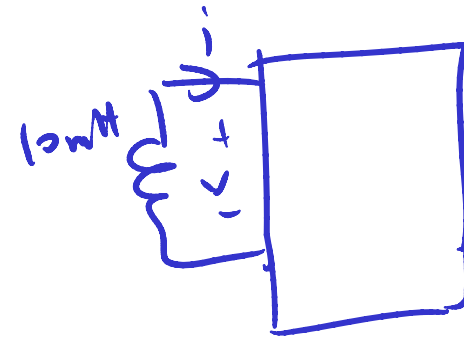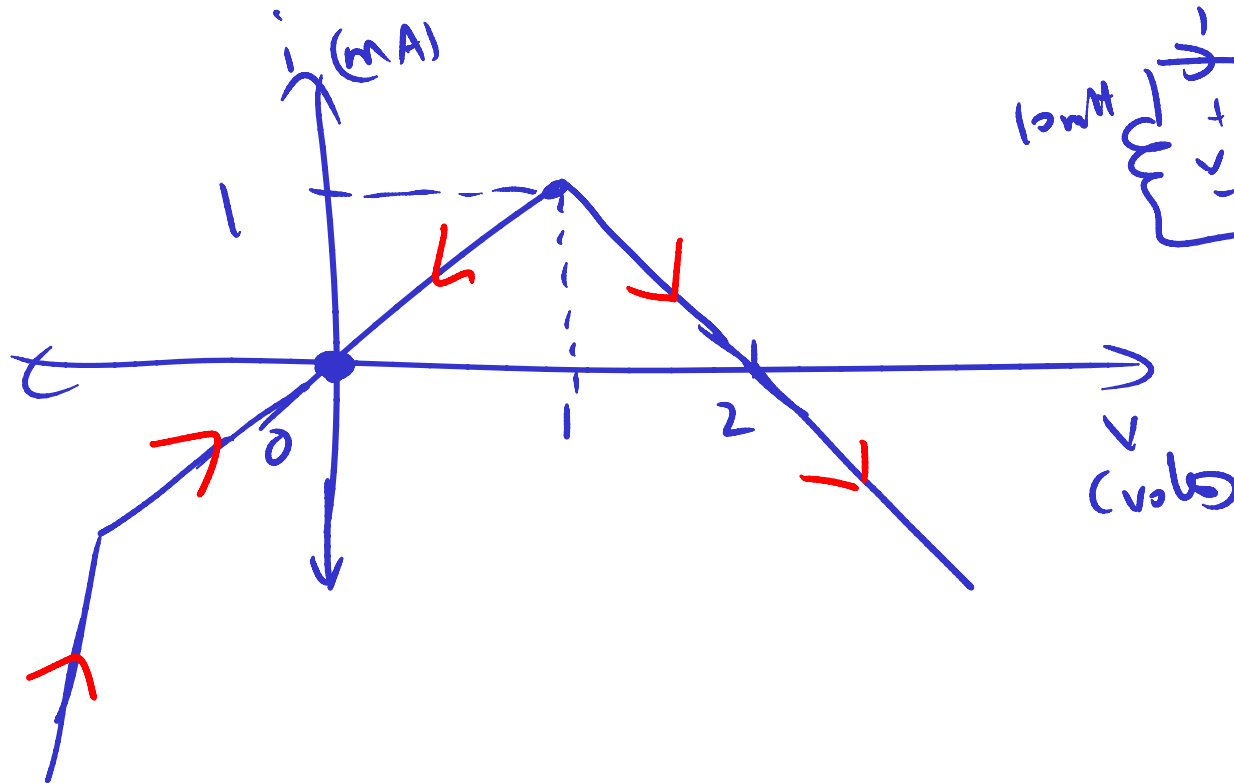

$$v = -L \frac{di}{dt}$$

eq. points: $i' = 0$
 $\Rightarrow v = 0$

Dynamic route & stability:

$v > 0$	$v < 0$
$i' < 0$	$i' > 0$