

EE100Su08 Lecture #13 (July 25th 2008)


- Outline

- MultiSim licenses: postponed to Monday, July 28th 2008
 - Apparently our license number is not working!
 - Thanks for coming to lecture today!
- HW #2: regrade deadline: Monday, 07/28, 5:00 pm PST.
- Midterm #1 regrades: I will finish em by office hours today.
- QUESTIONS?
- Strain Gauge and Project: Lab Lecture
 - **WARNING: BE REALLY CAREFUL AROUND THE STRAIN GAUGE SINCE THE APPARATUS “STICKS OUT” OF THE TABLE!**
- Frequency Response and Bode plots ← Monday
- Nonlinear circuits

- Reading

- Chapter 9 from your book (skip 9.10, 9.11 (duh)), Appendix E* (skip second-order resonance bode plots)
- Chapter 1 from your reader (skip second-order resonance bode plots)

Strain Gauge

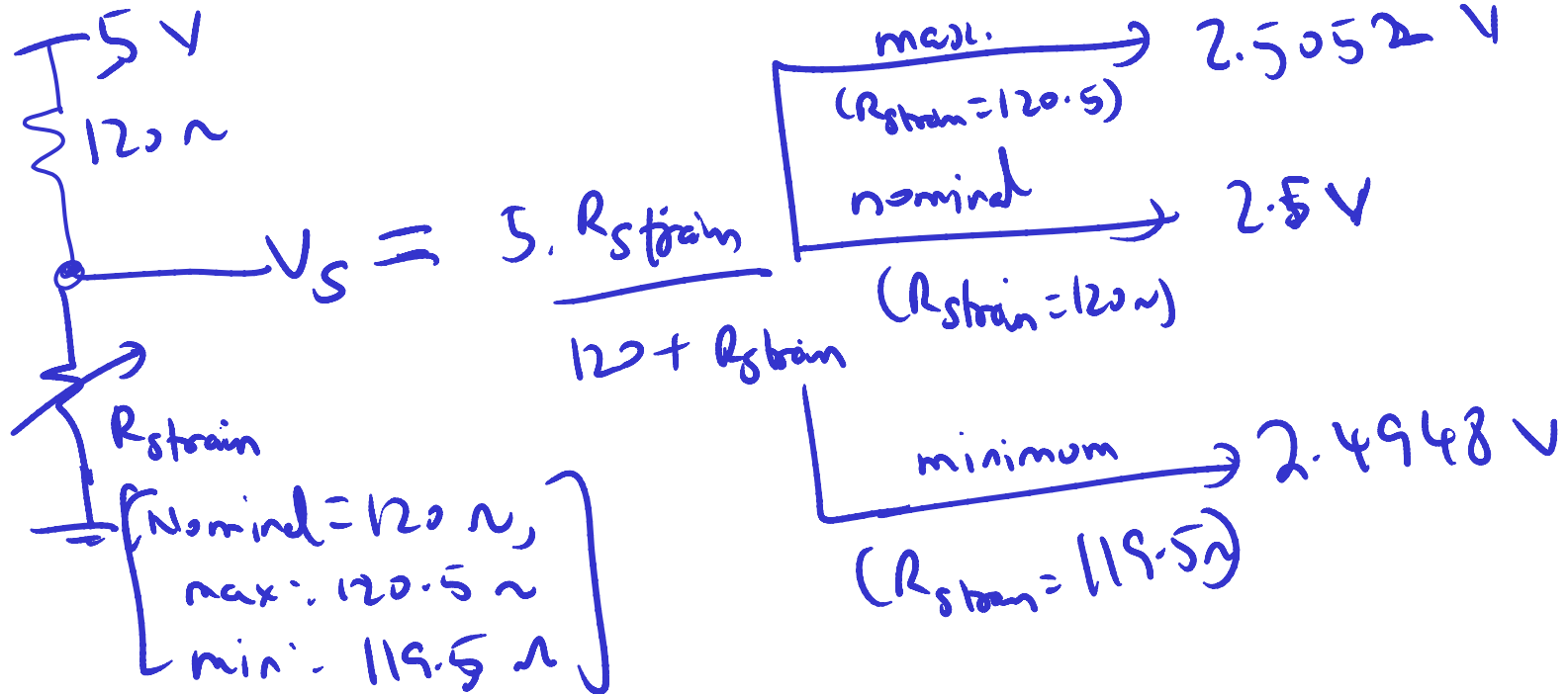


Voltage divider does not give a good dynamic range, but one possible interface:



The interface circuit consists of two operational amplifiers. The first op-amp is configured as a differential amplifier with inputs V_S and 2.5V. Its output is $V_x = V_S - 2.50V$. The second op-amp is configured as a gain stage with gain α , receiving V_x as input and producing an output αV_x .

Strain Gauge

Previous interface is not too "nice":

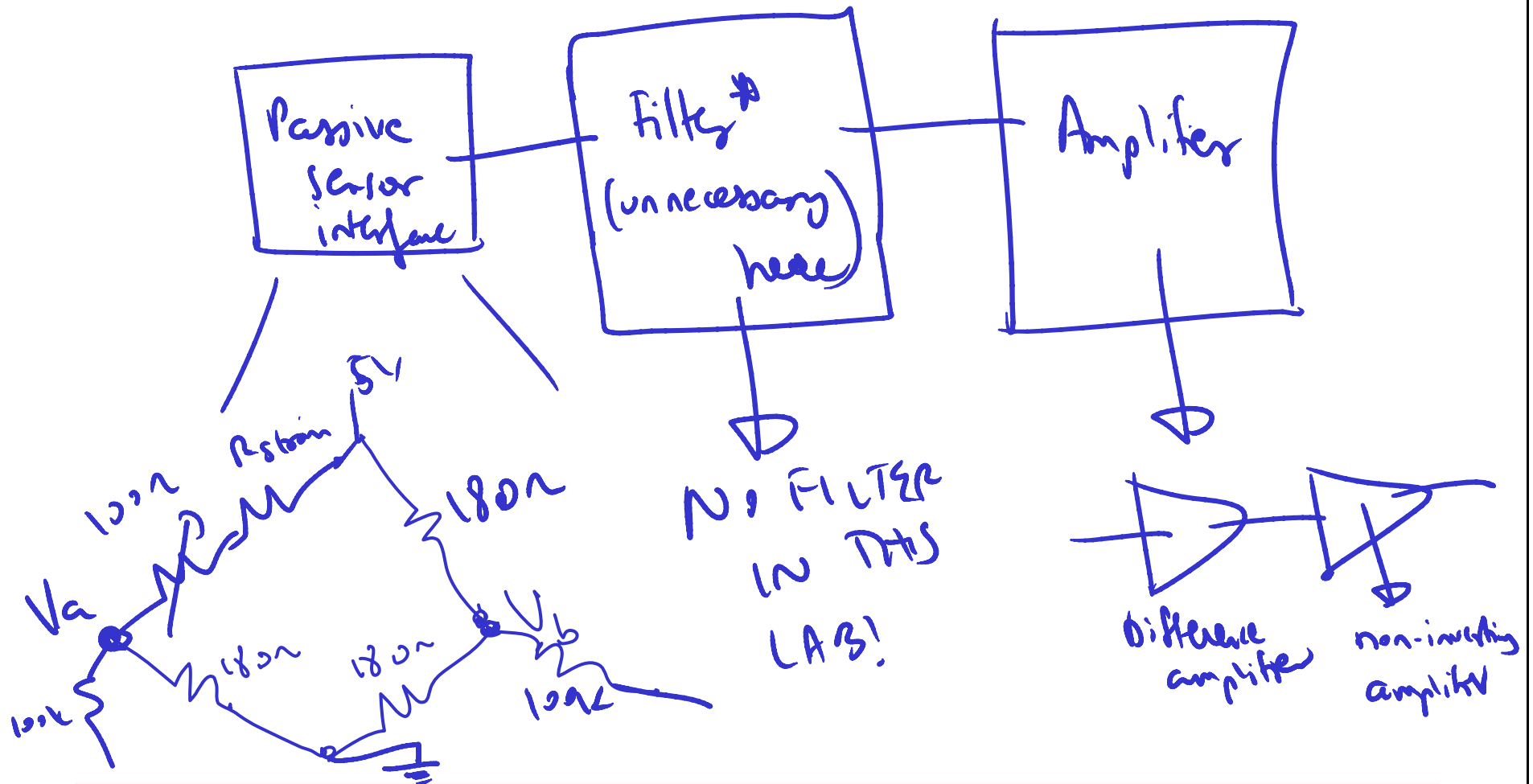

Nonlinear circuit example

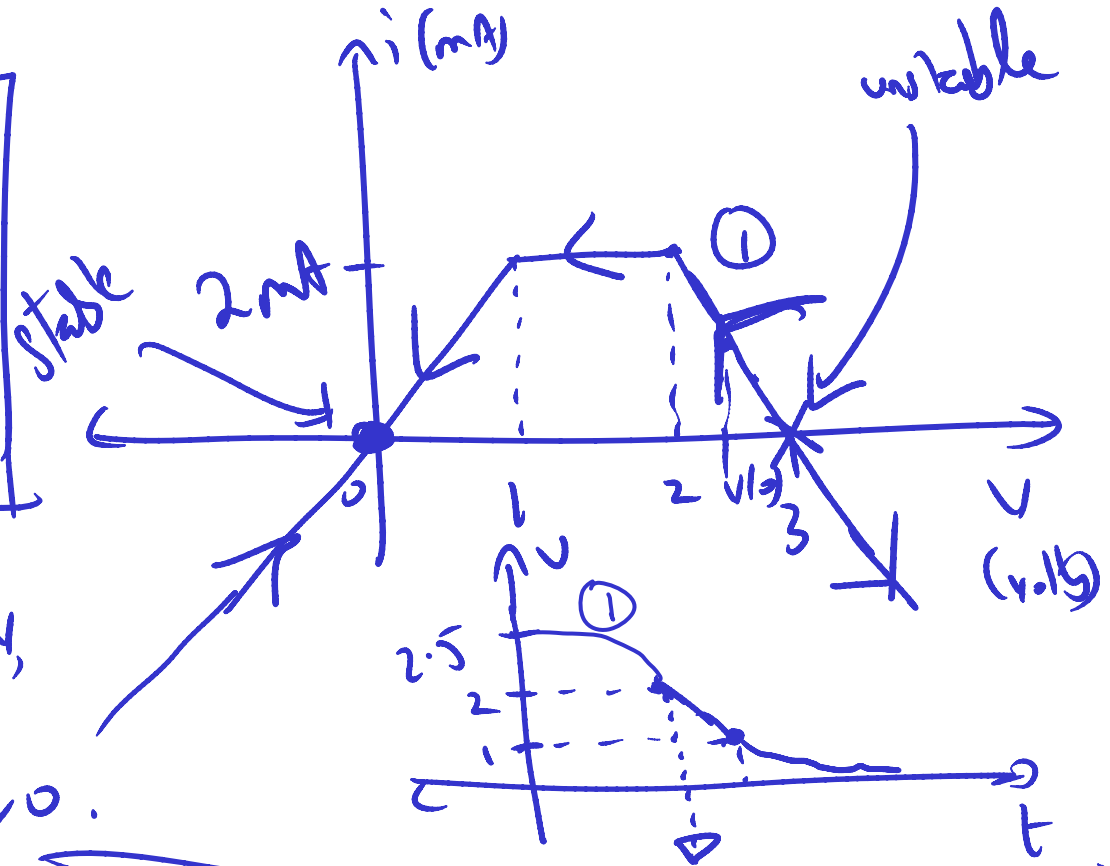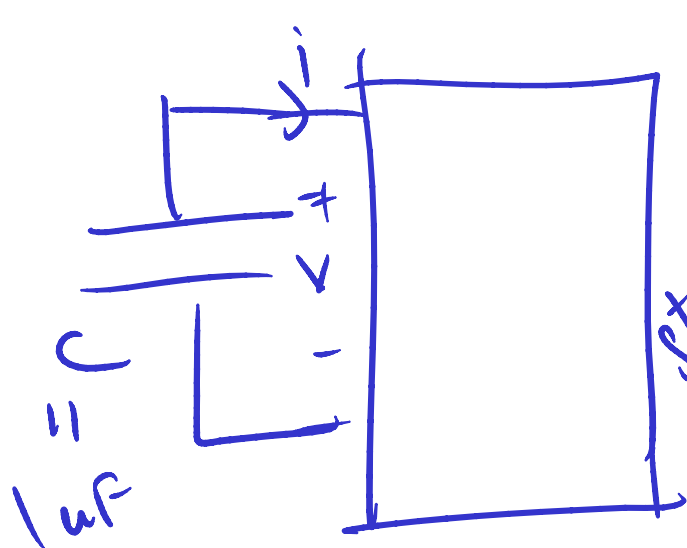



Suppose $v(0) = 2.5V$,
 sketch $v(t) \quad t \geq 0$.

(1) eq. points: $v' = 0 \Rightarrow \boxed{i = 0}$
 \Downarrow
 $\left[i = -C \frac{dv}{dt} \right]$
 \Downarrow
 x -axis intersections

(2) Dynamic route

$i > 0$	$i < 0$
$v' < 0$	$v' > 0$

Region ①

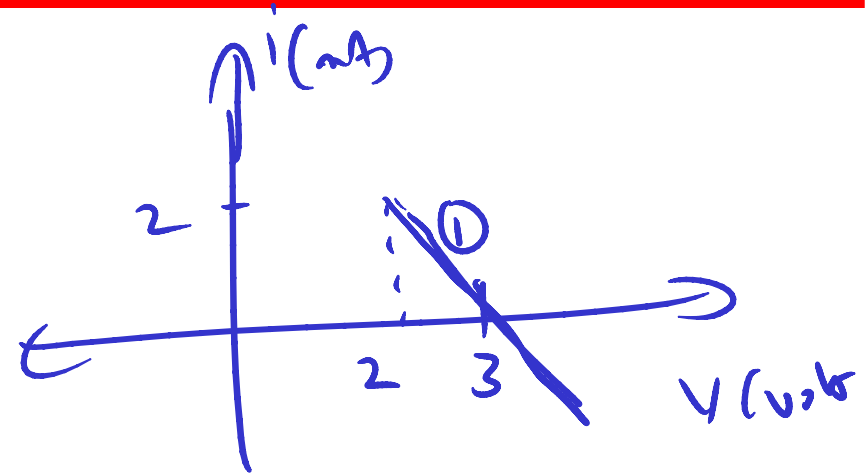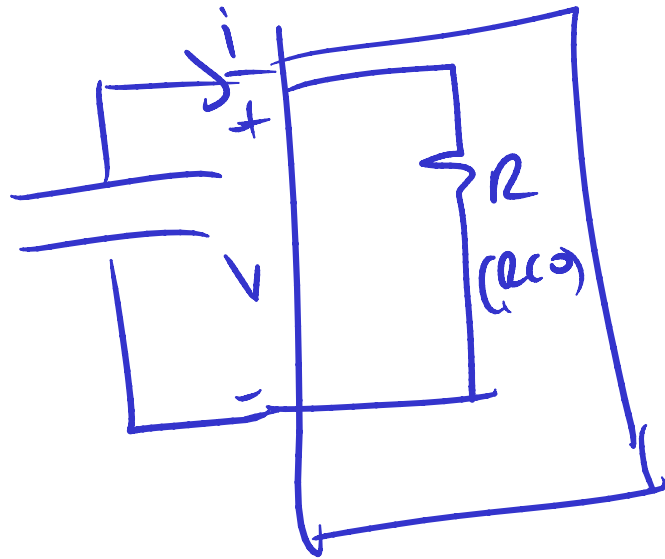



$$R_{\text{①}} = \frac{1}{\Delta} = \frac{1}{\frac{-2 \text{ mA}}{1}} = \underline{\underline{-500 \Omega}}$$

$$v(t) = A + B e^{-t/\tau}$$

$$= A + B e^{\frac{-t}{\tau_{\text{ROC}}}} = A + B e^{-\frac{t}{500 \mu\text{F}}}$$

(usually: $v_0(t) = v_f + (v_i - v_f) e^{-t/\tau}$) $v_0(t) = A + B e^{\frac{t}{0.5 \text{ ms}}}$ //

Region ①

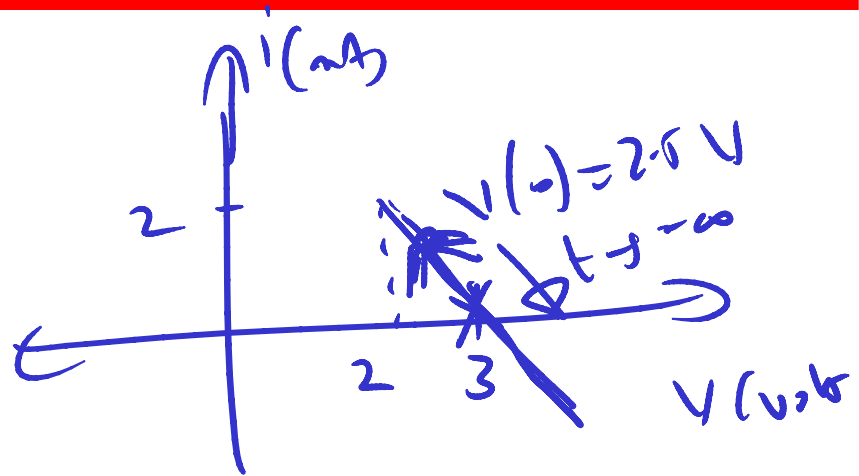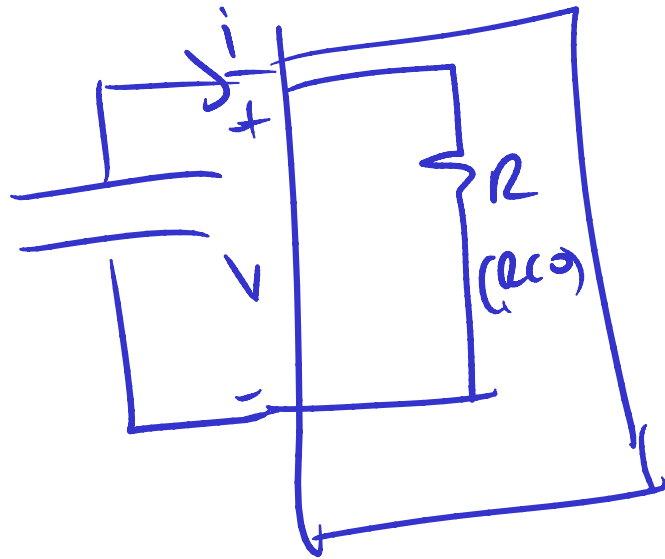


$$v(t) = A + \beta e^{-\frac{t}{0.5 \text{ ns}}} \quad v_0(0) = 2.5$$

$$v_0(t) = 3 - 0.5 e^{-\frac{t}{0.5 \text{ ns}}}$$

$$\Rightarrow A + \beta = 2.5 \Rightarrow \beta = -0.5$$

$$v_0(t \rightarrow -\infty) = A = 3$$

Example Circuit

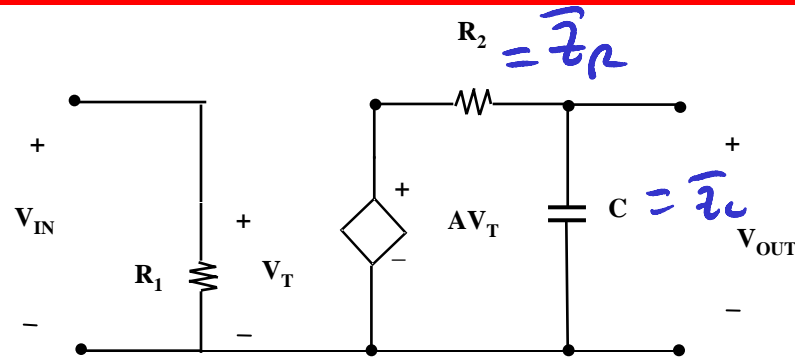

$$\overline{V_{out}} = \frac{\overline{Z_C}}{\overline{Z_R} + \overline{Z_C}} \cdot A \overline{V_T}$$

$$TransferFunction = \frac{V_{OUT}}{V_{IN}}$$

$$A = 100$$

$$R_1 = 100,000 \text{ Ohms}$$

$$\frac{V_{OUT}}{V_{IN}} = \frac{AZ_c}{Z_R + Z_c}$$


$$R_2 = 1000 \text{ Ohms}$$

$$C = 10 \text{ uF}$$

$$\overline{H} = \frac{V_{OUT}}{V_{IN}} = \frac{A(1/j\omega C)}{(R_2 + 1/j\omega C)} = \frac{A}{(1 + j\omega R_2 C)}$$

magnitude $\rightarrow 20 \log |H|$
 \downarrow phase $\rightarrow \omega$ (log scale)
 ω (log scale)

Example Circuit

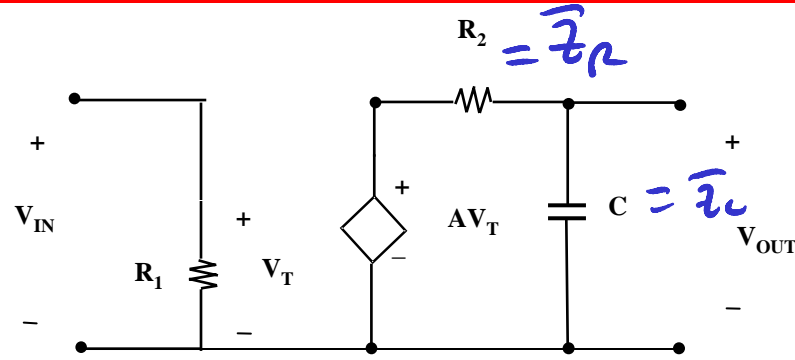

$$\overline{V_{out}} = \frac{\overline{z_0}}{\overline{z_R + z_0}} \cdot A \overline{V_{in}}$$

$$\overline{H} = \frac{A}{(1 + j\omega R_2 C)}$$

$$20 \log |\overline{H}| = 20 \log |A| = 20 \log \left(\frac{A}{\sqrt{1 + (\omega R_2 C)^2}} \right)$$

$$20 \log |\overline{H}| = 20 \log A - 20 \log \sqrt{1 + (\omega R_2 C)^2}$$

Sketch individually & subtract!

ω (log-scale)



$$A = 100$$

$$R_1 = 100,000 \text{ Ohms}$$

$$R_2 = 1000 \text{ Ohms}$$

$$C = 10 \text{ uF}$$

Example Circuit

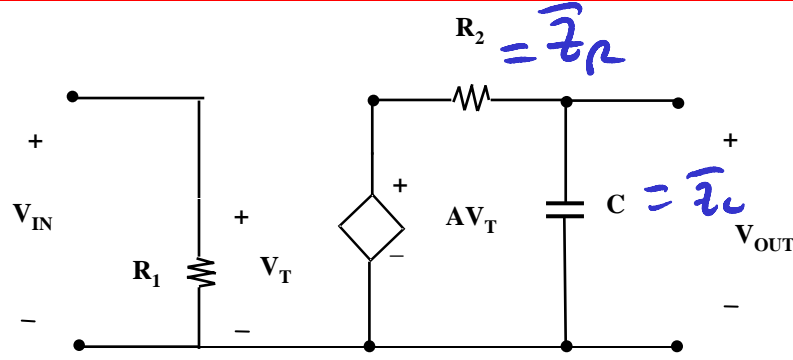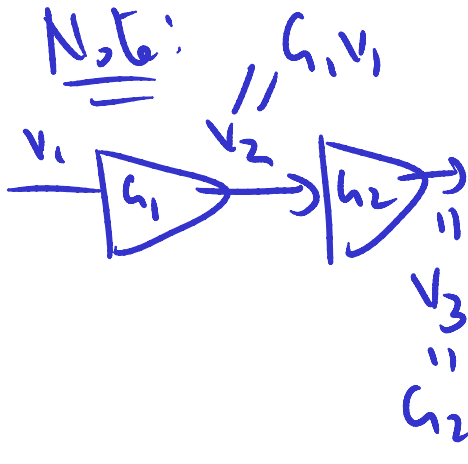


$$\bar{V}_{out} = \frac{\bar{z}_C}{\bar{z}_R + \bar{z}_C} \cdot A \bar{V}_T$$

$$\bar{H} = \frac{A}{(1 + j\omega R_2 C)}$$

- A = 100
- R₁ = 100,000 Ohms
- R₂ = 1000 Ohms
- C = 10 uF

Transfer fns:

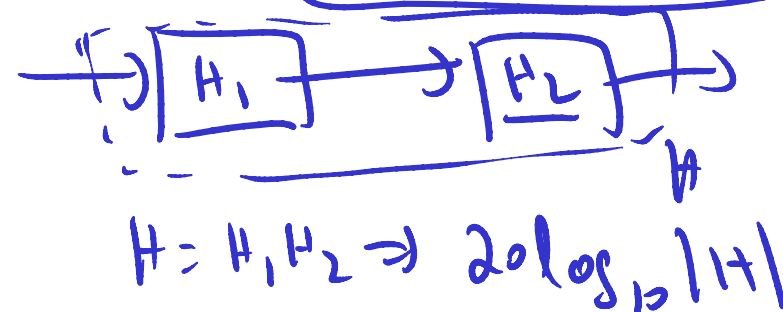


$$= 20 \log_{10} |H_1 H_2| = 20 \log_{10} |H_1| + 20 \log_{10} |H_2|$$


Break Point Values

- When dealing with resonant circuits it is convenient to refer to the frequency difference between points at which the power from the circuit is half that at the peak of resonance.
- Such frequencies are known as “half-power frequencies”, and the power output there referred to the peak power (at the resonant frequency) is
- $10\log_{10}(P_{\text{half-power}}/P_{\text{resonance}}) = 10\log_{10}(1/2) = -3 \text{ dB}.$

Example: Circuit in Slide #2 Magnitude

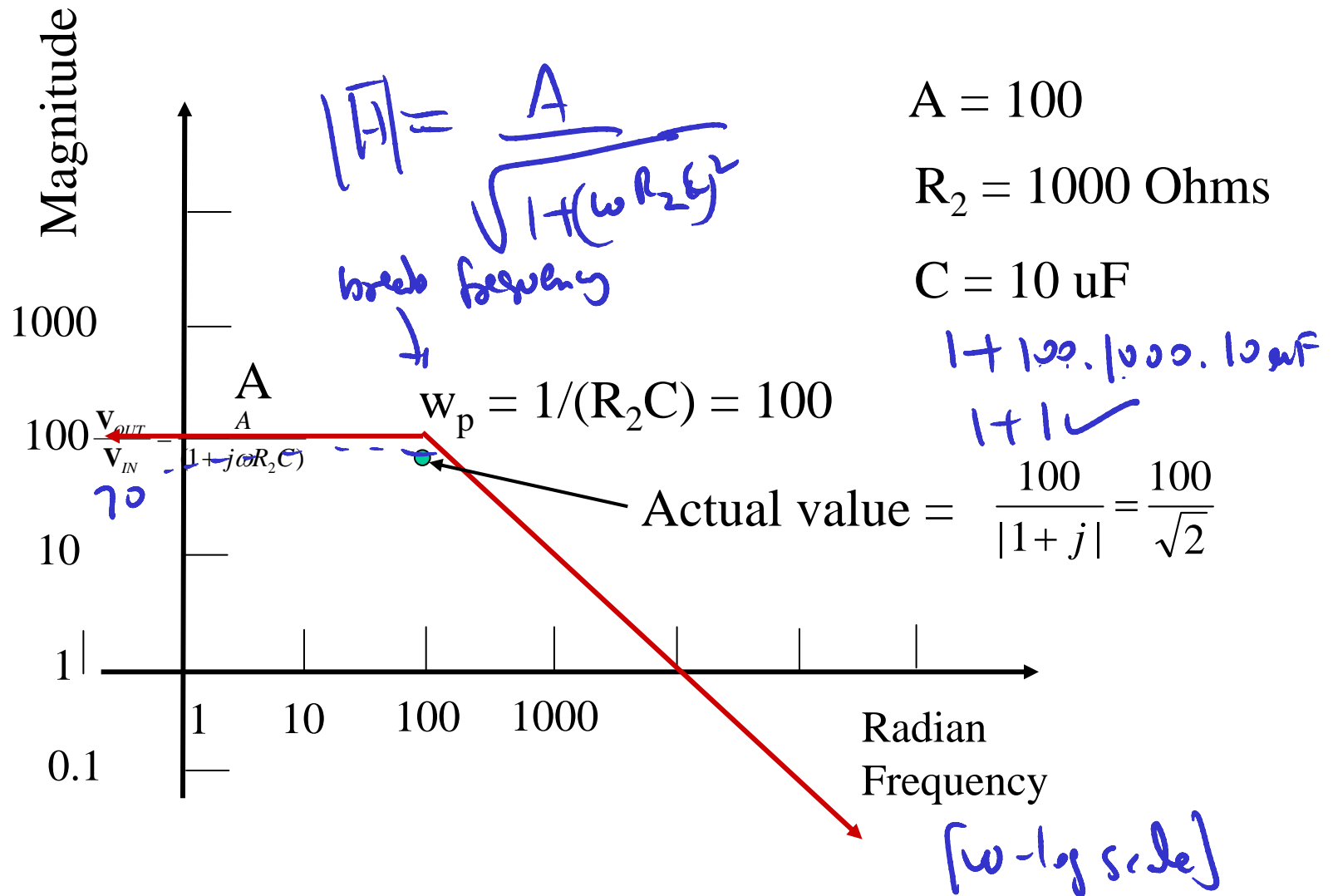

Bode Plot: Label as dB

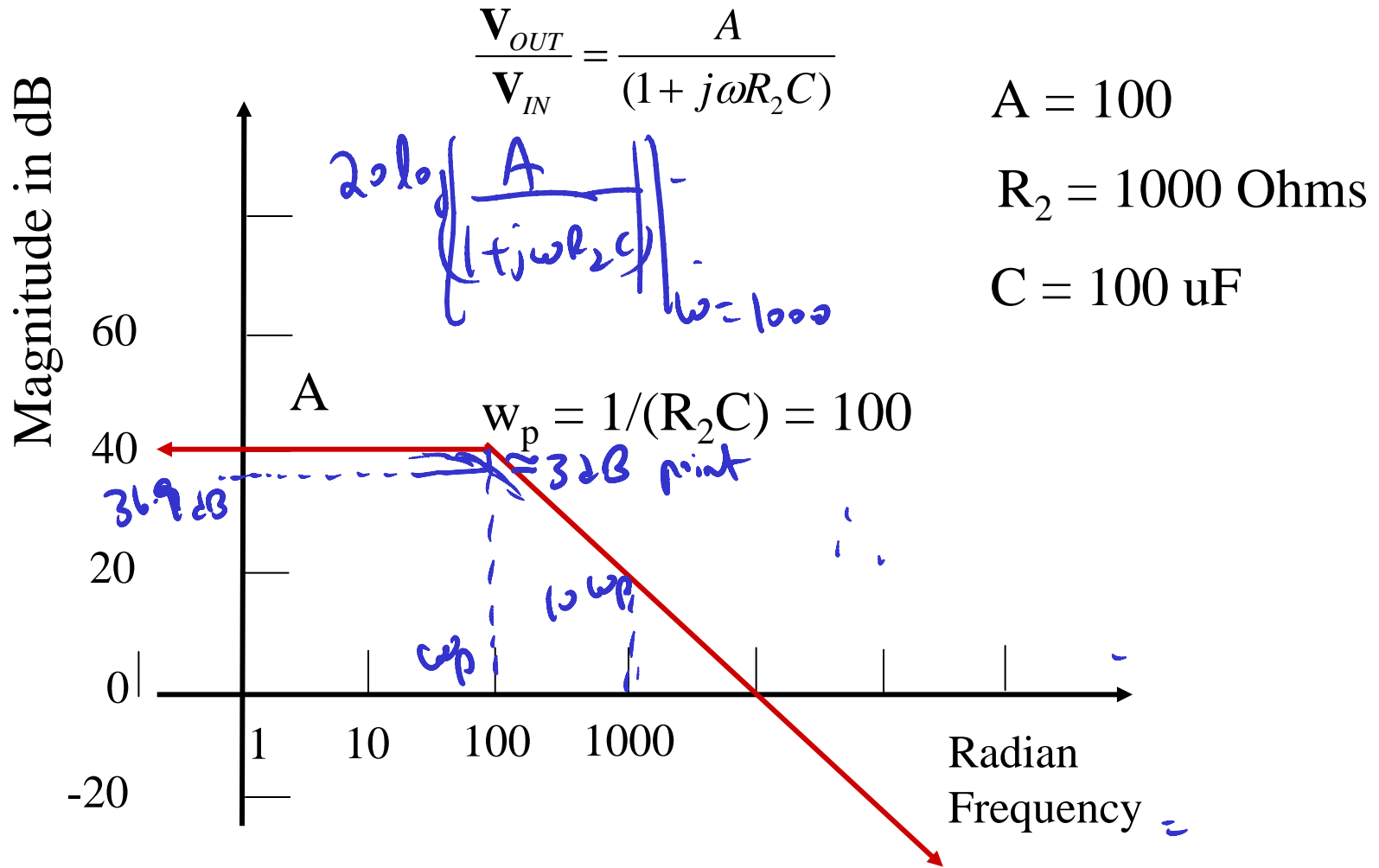

Note: Magnitude in dB = $20 \log_{10}(V_{OUT}/V_{IN})$