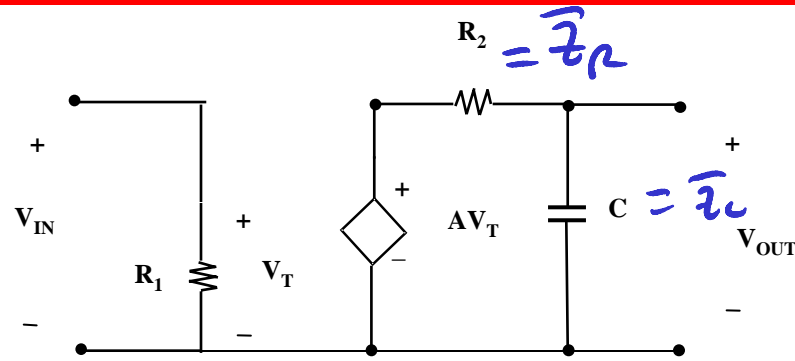


EE100Su08 Lecture #14 (July 28th 2008)

- Outline
 - MultiSim licenses: trying to get new licenses
 - HW #2: regrade deadline: Monday, 07/28, 5:00 pm PST.
 - Midterm #1 regrades: DONE!
 - QUESTIONS?
 - Bode plots
 - Diodes: Introduction
- Reading
 - Appendix E* (skip second-order resonance bode plots), Chapter 1 from your reader (skip second-order resonance bode plots)
 - Chapter 2 from your reader (Diode Circuits)

Example Circuit



$$\overline{V_{out}} = \frac{\overline{Z_C}}{\overline{Z_R} + \overline{Z_C}} \cdot A \overline{V_T}$$

$$\text{TransferFunction} = \frac{V_{OUT}}{V_{IN}}$$

$$A = 100$$

$$R_1 = 100,000 \text{ Ohms}$$

$$\frac{V_{OUT}}{V_{IN}} = \frac{AZ_c}{Z_R + Z_c}$$


$$R_2 = 1000 \text{ Ohms}$$

$$C = 10 \text{ uF}$$

$$\overline{H} = \frac{V_{OUT}}{V_{IN}} = \frac{A(1/j\omega C)}{(R_2 + 1/j\omega C)} = \frac{A}{(1 + j\omega R_2 C)}$$

magnitude $\rightarrow 20 \log |H|$
 ω (log scale) \rightarrow phase \rightarrow ω (log scale)

Example Circuit

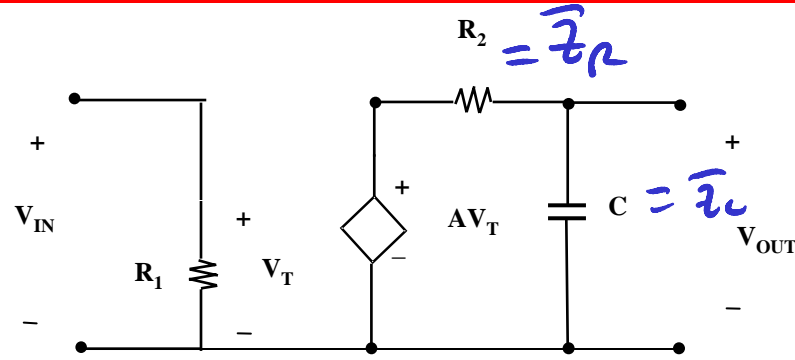

$$\bar{V}_{out} = \frac{\bar{z}_C}{\bar{z}_R + \bar{z}_C} \cdot A \bar{V}_T$$

$$\bar{H} = \frac{A}{(1 + j\omega R_2 C)}$$

$$20 \log |\bar{H}| = 20 \log |A| = 20 \log \left(\frac{A}{\sqrt{1 + (\omega R_2 C)^2}} \right)$$

$$20 \log |\bar{H}| = 20 \log A - 20 \log \sqrt{1 + (\omega R_2 C)^2}$$

Sketch individually & subtract!

ω (log-scale)



$$A = 100$$

$$R_1 = 100,000 \text{ Ohms}$$

$$R_2 = 1000 \text{ Ohms}$$

$$C = 10 \text{ uF}$$

Example Circuit

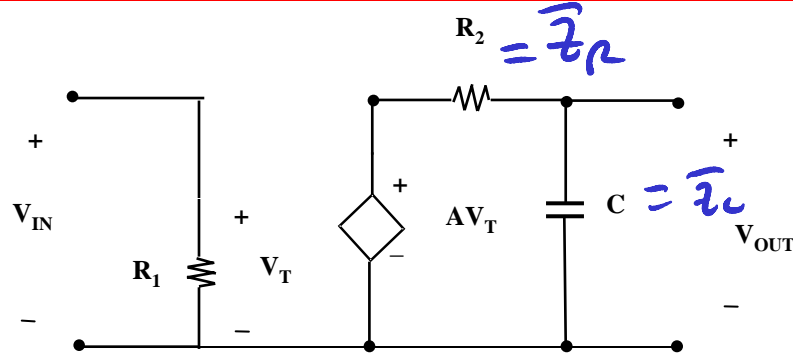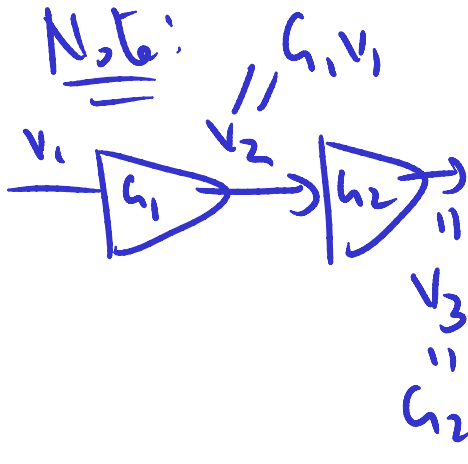


$$\bar{V}_{out} = \frac{\bar{z}_C}{\bar{z}_R + \bar{z}_C} \cdot A \bar{V}_T$$

$$\bar{H} = \frac{A}{(1 + j\omega R_2 C)}$$

- A = 100
- R₁ = 100,000 Ohms
- R₂ = 1000 Ohms
- C = 10 uF

Transfer fns:

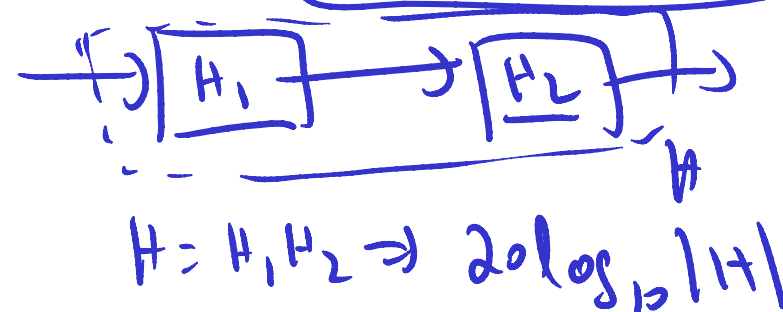

$$= 20 \log_{10} |H_1 H_2| = 20 \log_{10} |H_1| + 20 \log_{10} |H_2|$$

A Note on the form of transfer fns.


(1) Only responsible for: $\bar{H} = \frac{A}{(1+j\omega\alpha_1)(1+j\omega\alpha_2)\dots(1+j\omega\alpha_n)}$

(2) Not responsible for second-order transfer fns:

$$\bar{H} = \frac{A}{(\omega^2 + \alpha\omega + R)}$$

Roots are complex conjugate.

Bode Plot: Label as dB

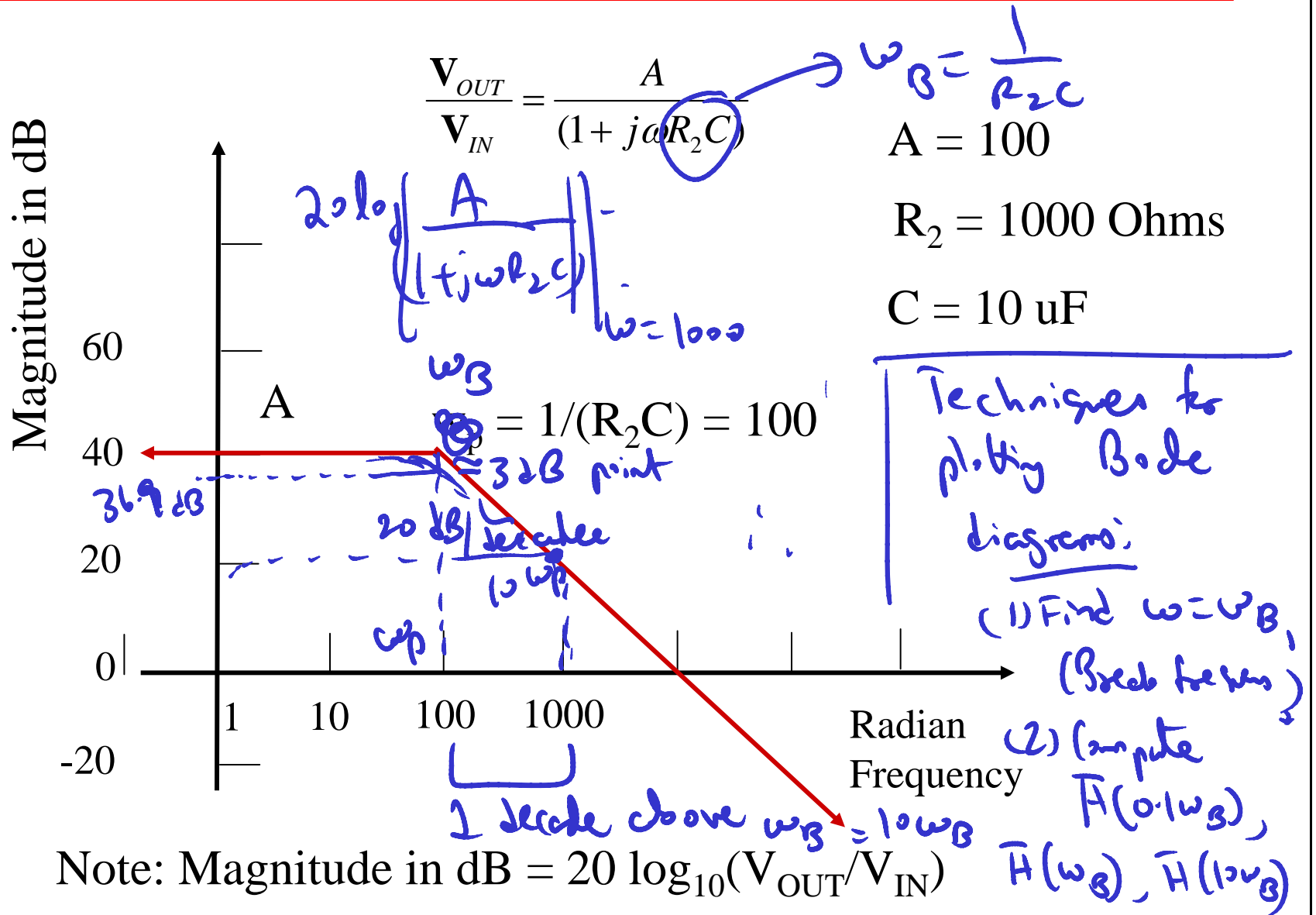

For the given t.f.

Consider: $\bar{H} = \frac{A}{1+j\omega R_2 C} = \frac{100}{(1+j\omega 100)}$


(1) $\bar{H}(0.1\omega_B) = \bar{H}\left(0.1 \frac{1}{100}\right) = \frac{100}{(1+j0.1 \cdot 100)} = \frac{100}{1+j1}$

[Recall: $\tau = R_2 C, \omega \approx \frac{1}{\tau} \approx 100$]

$\therefore 20 \log_{10} |\bar{H}(0.1\omega_B)| = 20 \log_{10} 100$
 $= 20 \cdot \frac{4}{2} = 40 \text{ dB}$

$\angle \bar{H}(0.1\omega_B) = \angle 100 = 0$

Example: Phase plot

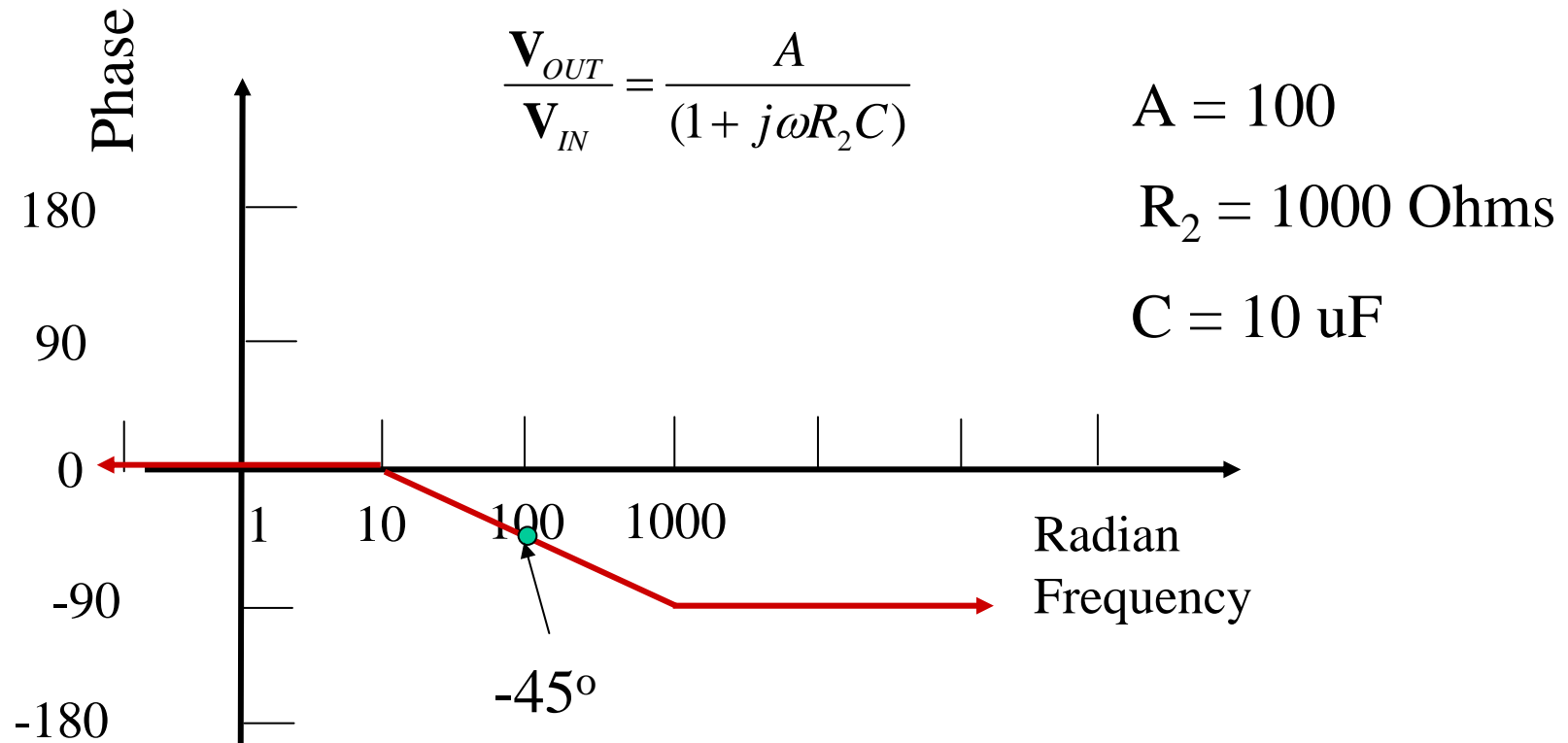

Actual value is

$$\text{Phase}\left\{\frac{100\angle 0}{|1+j|}\right\} = \text{Phase}\left\{\frac{100\angle 0}{\sqrt{2}\angle 45}\right\} = 0 - 45 = -45$$

Transfer Function

- Transfer function is a function of frequency
 - Complex quantity
 - Both magnitude and phase are function of frequency



$$\mathbf{H}(f) = \frac{\mathbf{V}_{out}}{\mathbf{V}_{in}} = \frac{V_{out}}{V_{in}} \angle (\theta_{out} - \theta_{in})$$

$$\mathbf{H}(f) = H(f) \angle \theta$$

Filters

- Circuit designed to retain a certain frequency range and discard others





Low-pass: pass low frequencies and reject high frequencies

High-pass: pass high frequencies and reject low frequencies

Band-pass: pass some particular range of frequencies, reject other frequencies outside that band

Notch: reject a range of frequencies and pass all other frequencies

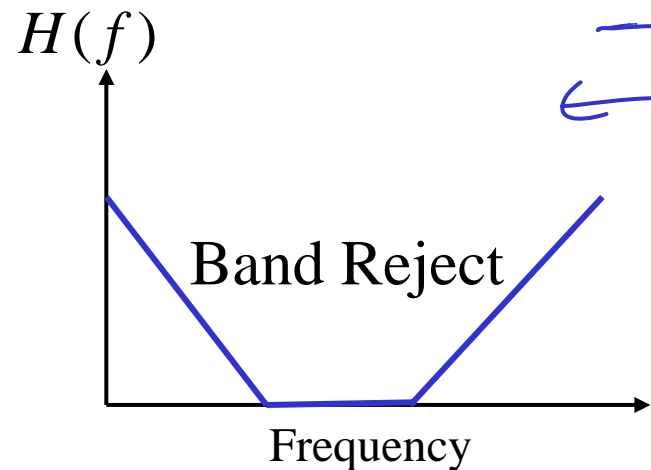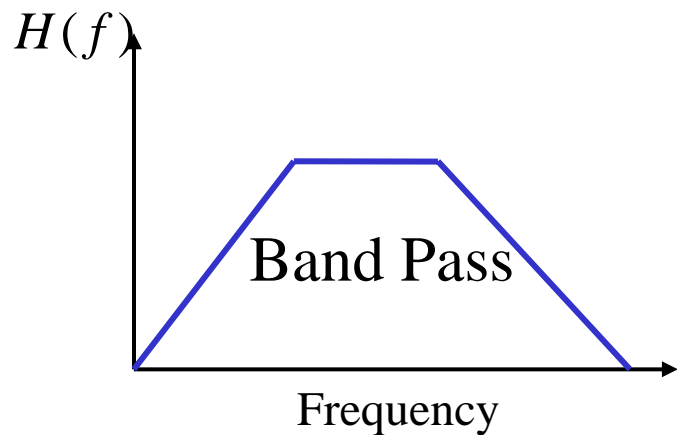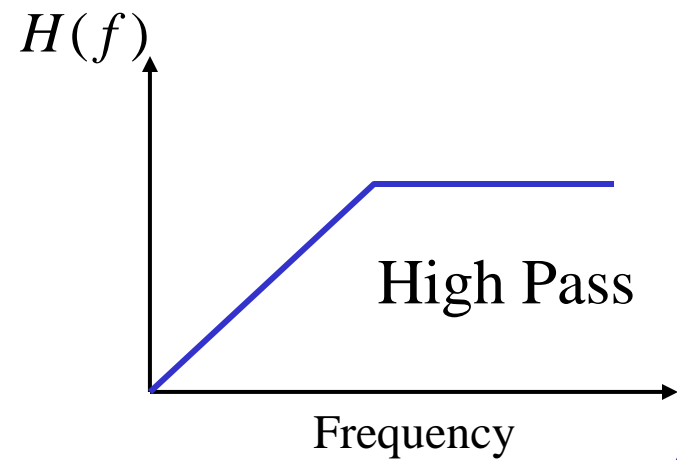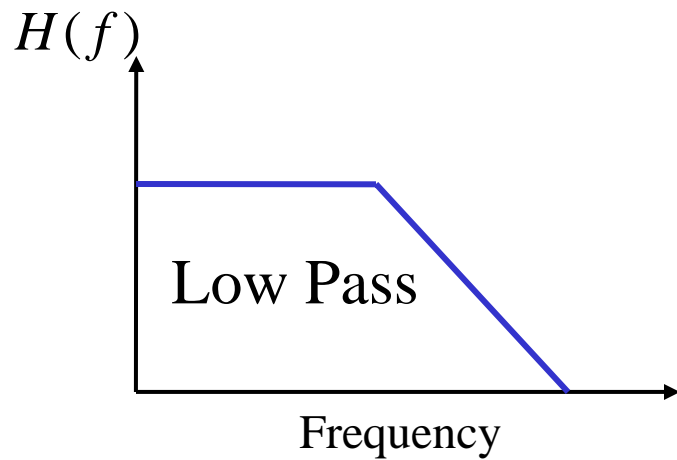Common Filter Transfer Function vs. Freq (Magnitude Plots shown)



Note:
↑
← →
ω
(log-scale)

First-Order Lowpass Filter

$$\mathbf{H}(f) = \frac{\mathbf{V}_c}{\mathbf{V}} = \frac{1/(j\omega C)}{1/(j\omega C) + R} = \frac{1}{1 + j\omega RC} = \frac{1}{\sqrt{1 + (\omega RC)^2}} \angle -\tan^{-1}(\omega RC)$$

$$\text{Let } \omega_B = \frac{1}{RC} \text{ and } f_B = \frac{1}{2\pi RC}$$


$$RC = 100$$

$$\mathbf{H}(f) = H(f) \angle \theta$$

$$H(f) = \frac{1}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}}, \theta = -\tan^{-1}\left(\frac{f}{f_B}\right)$$


$$H(f_B) = \frac{1}{\sqrt{2}} = 2^{-1/2}$$
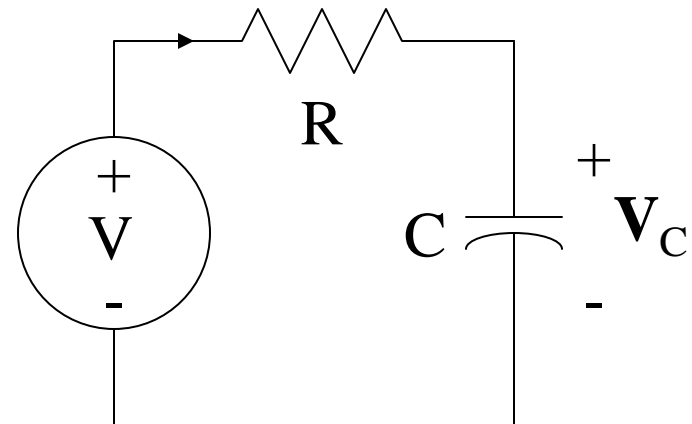
$$20 \log_{10} \frac{H(f_B)}{H(0)} = 20 \left(-\frac{1}{2}\right) \log_{10} 2 = -3 \text{ dB}$$



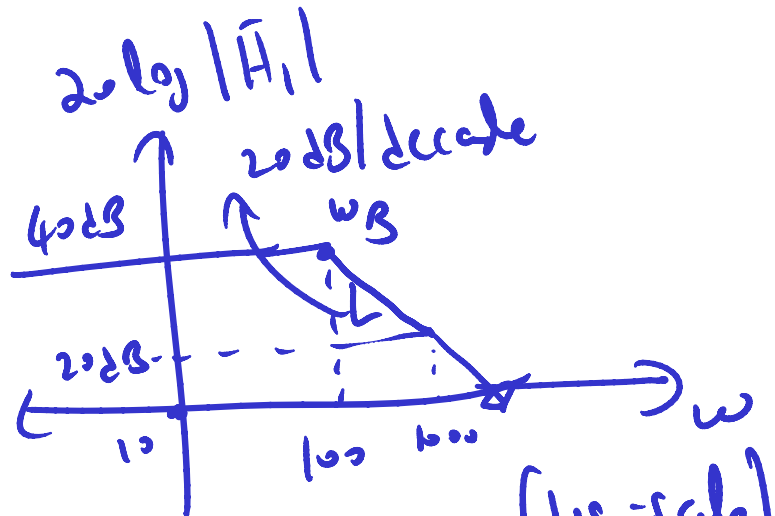
Question: What is the difference between the

Bode plots: $\bar{H}_1 = \frac{100}{1+j\omega R_2 C}$, $\bar{H}_2 = \frac{1}{1+j\omega R_2 C}$



$$R_2 C = \frac{1}{100} = 0.01$$
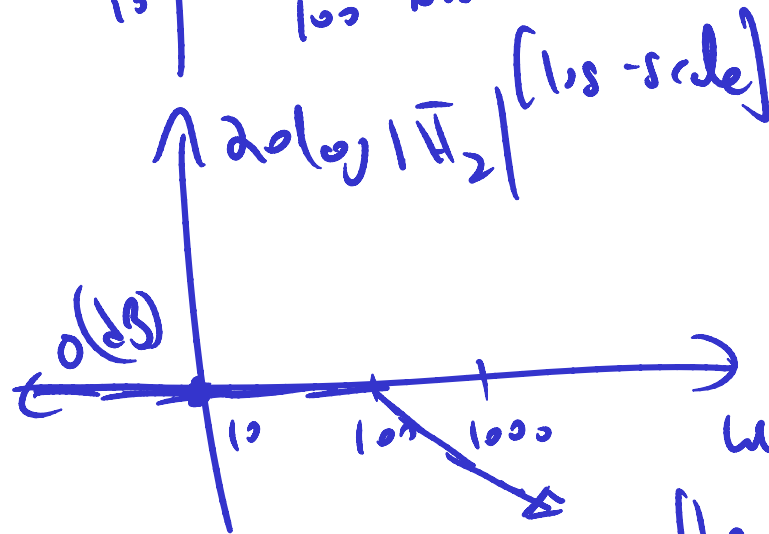
$$\omega_B = \frac{1}{R_2 C} = \frac{1}{0.01} = 100$$



$$\bar{H}_2(0.1\omega_B) = \frac{1}{1 + j \frac{0.1}{R_2 C} \cdot R_2 C}$$

$$= \frac{1}{1 + j0.1} \approx 1$$


$$\therefore 20 \log |\bar{H}_2(0.1\omega_B)| = 0$$

Question: What is the difference between the

Bode plots: $\bar{H}_1 = \frac{100}{1+j\omega R_2 C}$, $\bar{H}_2 = \frac{1}{1+j\omega R_2 C}$


$$R_2 C = \frac{1}{100} = 0.01$$
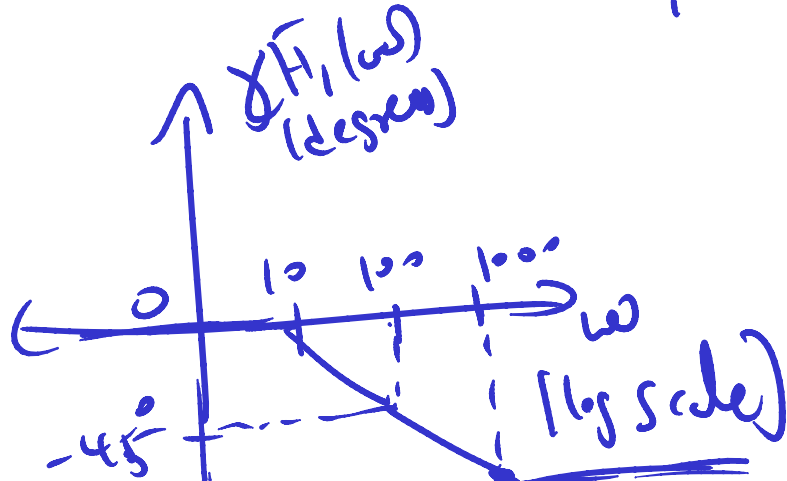
$$\omega_B = \frac{1}{R_2 C} = \frac{1}{0.01} = 100$$



$\angle \bar{H}_2(\omega)$ (degrees)

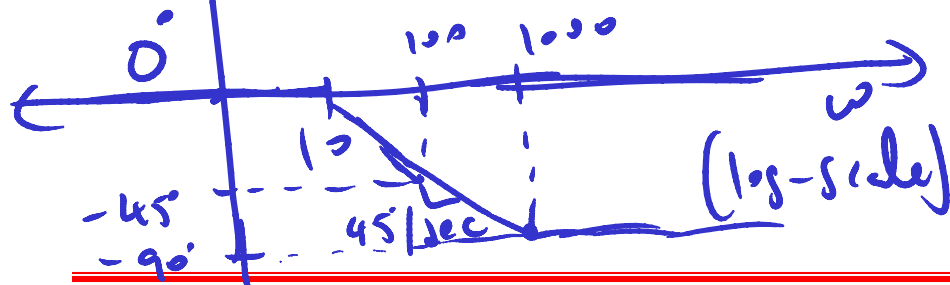
$$\bar{H}_2(0.1\omega_B) = \frac{1}{1 + j \frac{0.1}{R_2 C} \cdot R_2 C} \approx 1 \Rightarrow \angle = 0$$




$$\bar{H}_2(\omega_B) = \frac{1}{1 + j \frac{1}{R_2 C} \cdot R_2 C} = \frac{1}{1+j} \Rightarrow \angle \approx -45$$

Intuitively understand difference between Bode plot

of \bar{H}_1 & \bar{H}_2

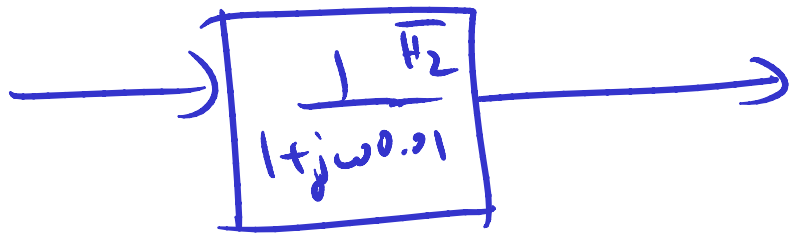

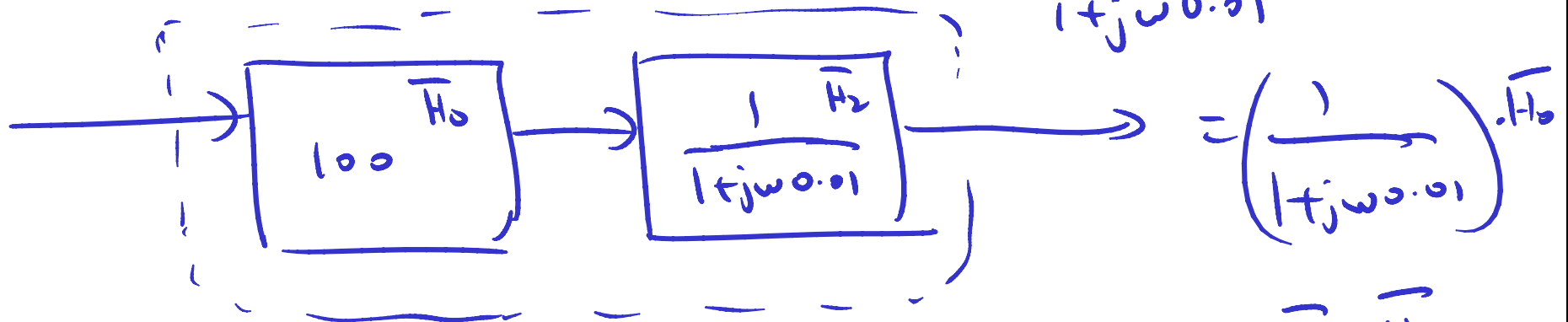
$$\bar{H}_1 = \frac{100}{1 + j\omega 0.01} = \bar{H}_2 \bar{H}_0$$



$$= \left(\frac{1}{1 + j\omega 0.01} \right) \cdot \bar{H}_0$$


$$= \bar{H}_0 \bar{H}_2$$

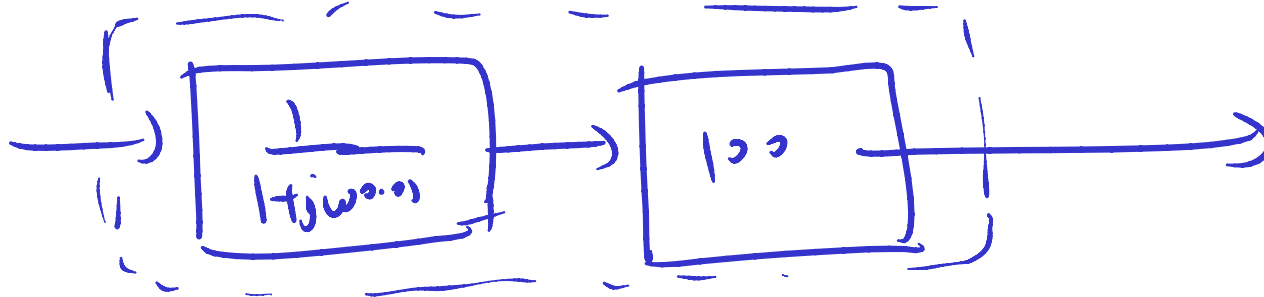

First-Order Highpass Filter


$$\mathbf{H}(f) = \frac{\mathbf{V}_R}{\mathbf{V}} = \frac{R}{1/(j\omega C) + R} = \frac{j\omega RC}{1 + j\omega RC} = \frac{(\omega RC)}{\sqrt{1 + (\omega RC)^2}} \angle \left[\frac{\pi}{2} - \tan^{-1}(\omega RC) \right]$$
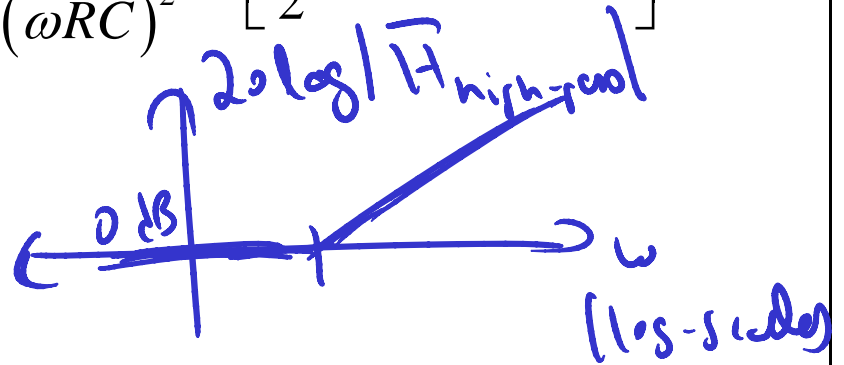
$$H(f) = \frac{\left(\frac{f}{f_B}\right)}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}}, \theta = \frac{\pi}{2} - \tan^{-1}\left(\frac{f}{f_B}\right)$$



$$H(f_B) = \frac{1}{\sqrt{2}} = 2^{-1/2}$$
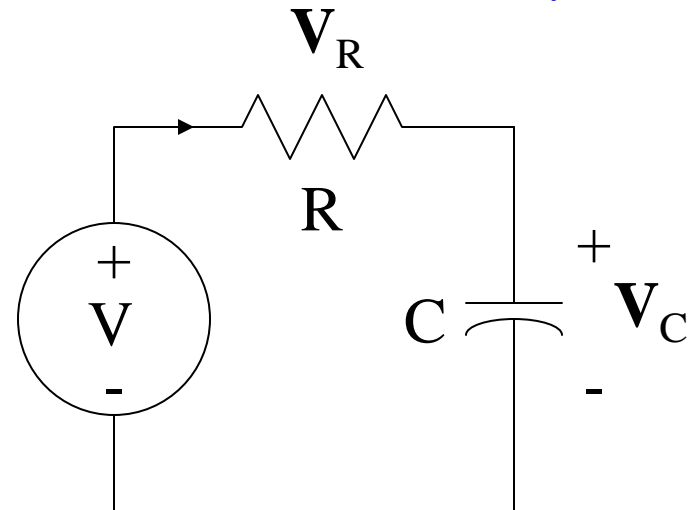
$$20 \log_{10} \frac{H(f_B)}{H(0)} = 20 \left(-\frac{1}{2}\right) \log_{10} 2 = -3 \text{ dB}$$




First-Order Lowpass Filter

$$\mathbf{H}(\mathbf{f}) = \frac{\mathbf{V}_R}{\mathbf{V}} = \frac{1}{\frac{j\omega L}{R} + 1} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} \angle -\tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$\text{Let } \omega_B = \frac{R}{L} \text{ and } f_B = \frac{R}{2\pi L}$$

$$\mathbf{H}(\mathbf{f}) = H(f) \angle \theta$$
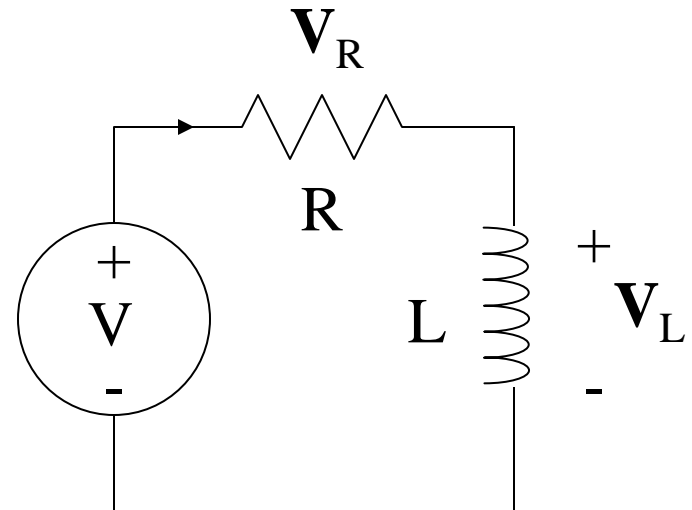
$$H(f) = \frac{1}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}}, \theta = -\tan^{-1}\left(\frac{f}{f_B}\right)$$




First-Order Highpass Filter

$$\mathbf{H}(f) = \frac{\mathbf{V}_L}{\mathbf{V}} = \frac{\frac{j\omega L}{R}}{\frac{j\omega L}{R} + 1} = \frac{\frac{\omega L}{R}}{\sqrt{1 + \left(\frac{\omega L}{R}\right)^2}} \angle \left[\frac{\pi}{2} - \tan^{-1} \left(\frac{\omega L}{R} \right) \right]$$


$$\text{Let } \omega_B = \frac{R}{L} \text{ and } f_B = \frac{R}{2\pi L}$$

$$\mathbf{H}(f) = H(f) \angle \theta$$
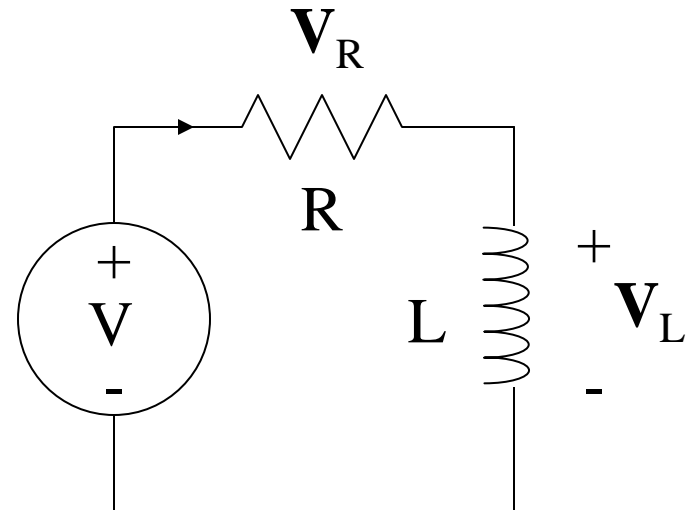
$$H(f) = \frac{\left(\frac{f}{f_B} \right)}{\sqrt{1 + \left(\frac{f}{f_B} \right)^2}}, \theta = \frac{\pi}{2} - \tan^{-1} \left(\frac{f}{f_B} \right)$$



First-Order Filter Circuits

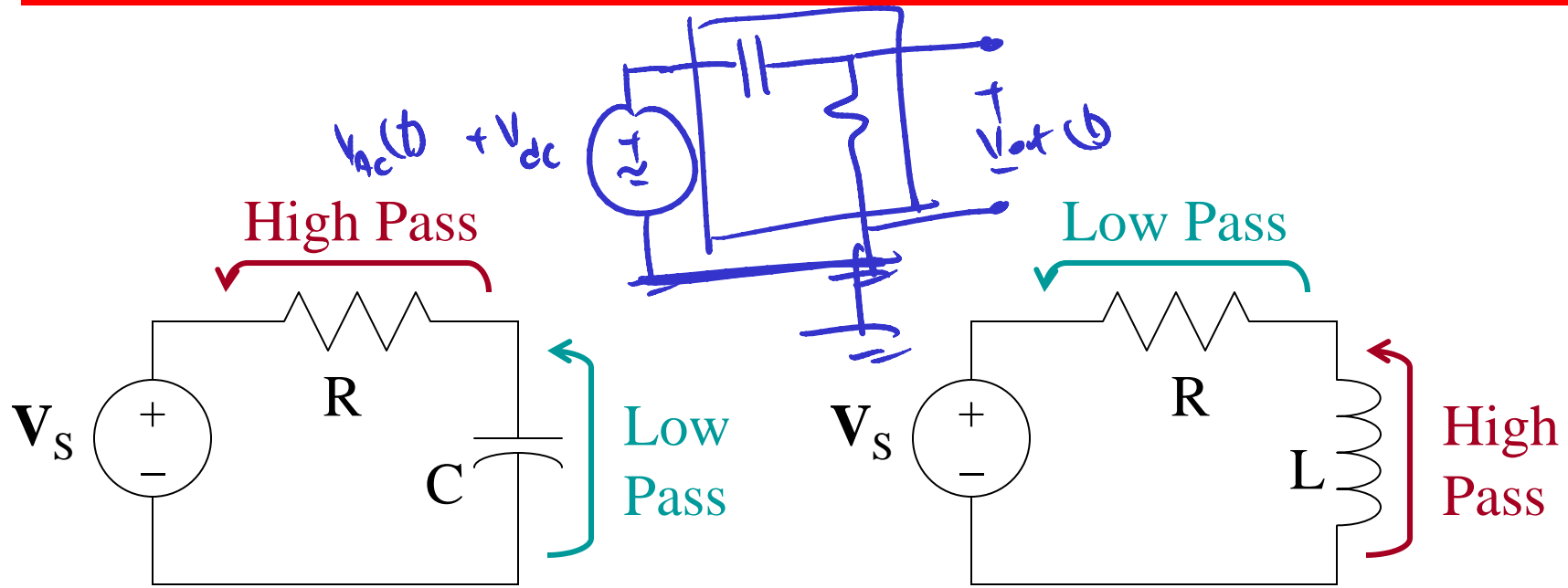


$$H_R = R / (R + 1/j\omega C)$$

$$H_R = R / (R + j\omega L)$$

$$H_C = (1/j\omega C) / (R + 1/j\omega C)$$

$$H_L = j\omega L / (R + j\omega L)$$

Recall / Summary of course material

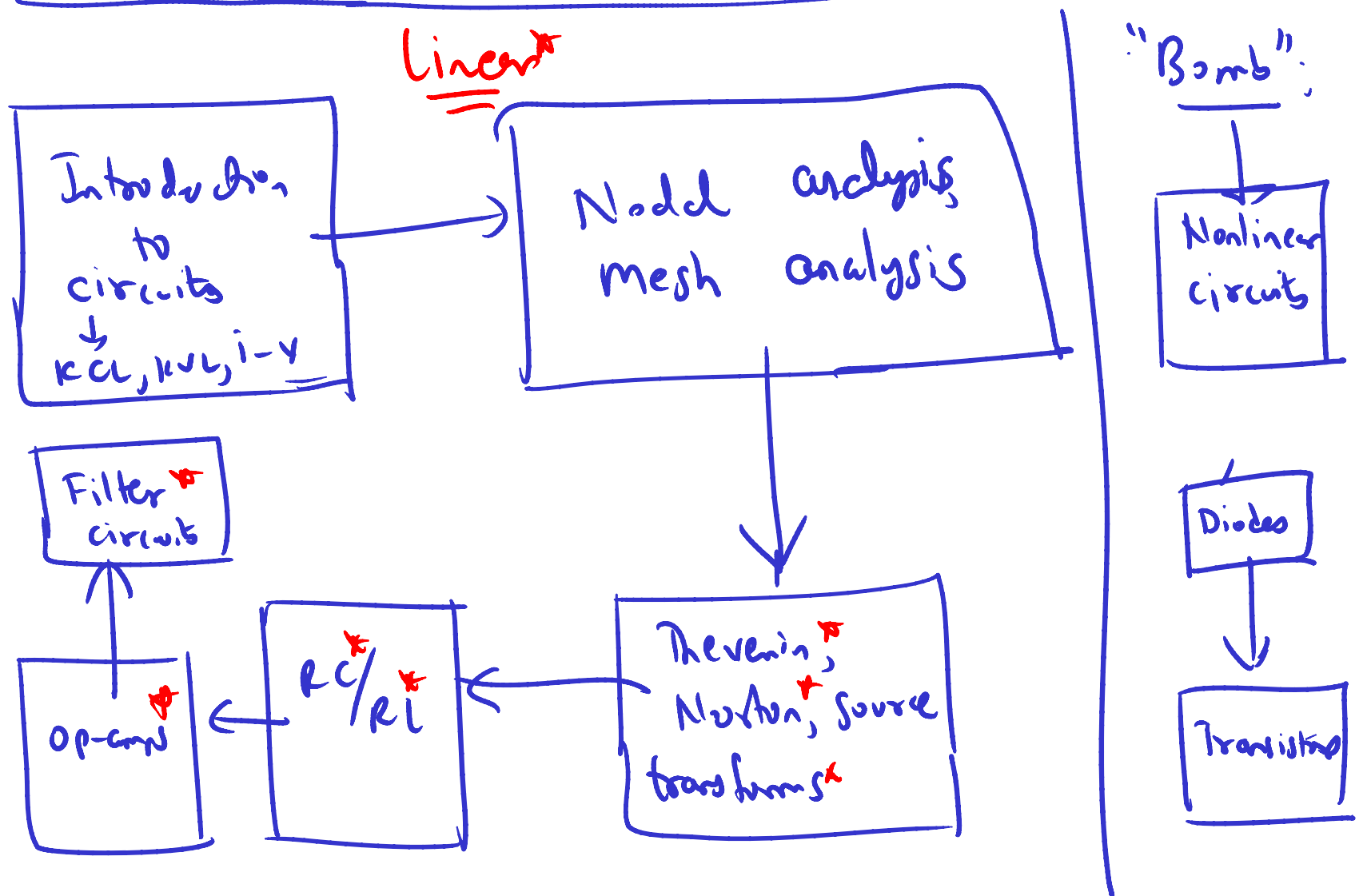


Diodes


- **OUTLINE**
 - Diode Model(s)
 - Circuit Analysis with Diodes
 - Diode Logic Gates
 - Load Line Analysis
 - Zener Diodes
 - Diode Peak Detector
- **Reading**
 - Reader: Chapter 2

Diode Physical Behavior and Equation

Schematic Device

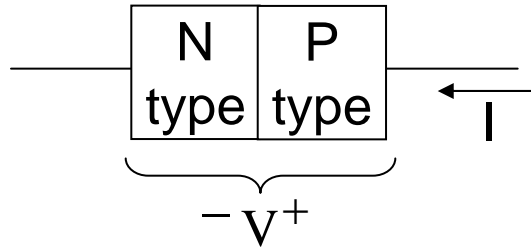


Symbol

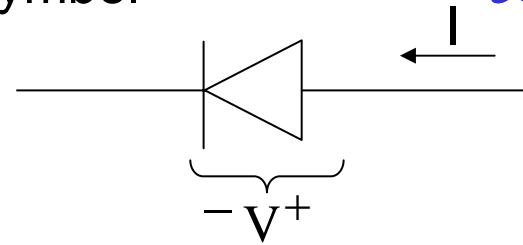

Ref: Howe & Sodini, Microelectronics: An Integrated Approach.

Qualitative I-V characteristics:

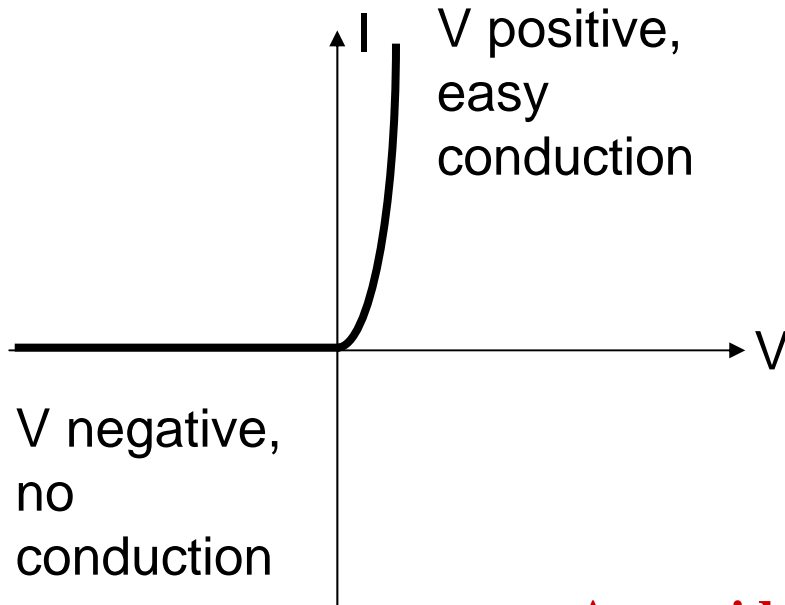

Quantitative I-V characteristics:


$$I = I_0(e^{qV/kT} - 1)$$

In which kT/q is 0.026V and I_0 is a constant depending on diode area. Typical values: 10^{-12} to 10^{-16} A. Interestingly, the graph of this equation looks just like the figure to the left.


A non-ideality factor n times kT/q is often included.

Diode Ideal (Perfect Rectifier) Model

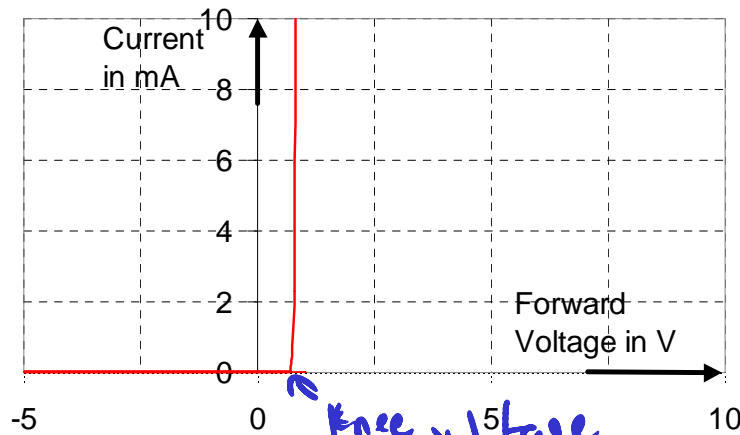The equation $I = I_0 \exp\left(\frac{qV}{kT} - 1\right)$ is graphed below for $I_0 = 10^{-15}$ A




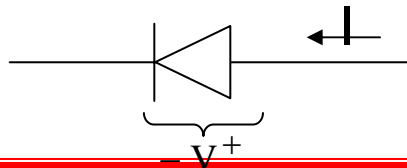The characteristic is described as a “rectifier” – that is, a device that permits current to pass in only one direction. (The hydraulic analog is a “check valve”.) Hence the symbol:




Simple “Perfect Rectifier” Model

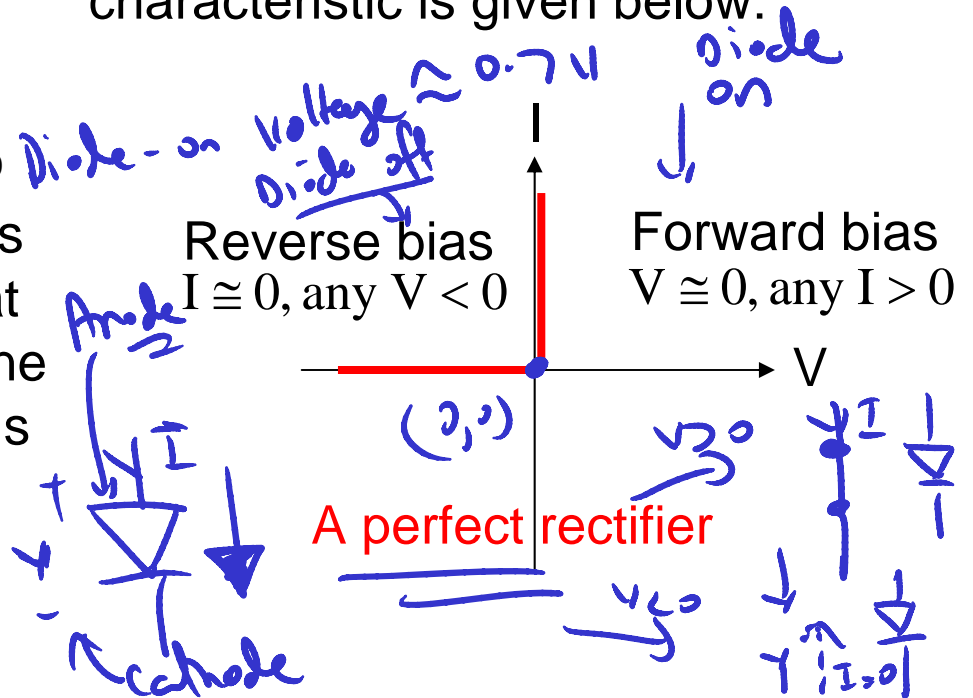If we can ignore the small forward-bias voltage drop of a diode, a simple effective model is the “perfect rectifier,” whose I-V characteristic is given below:




I-V Characteristics

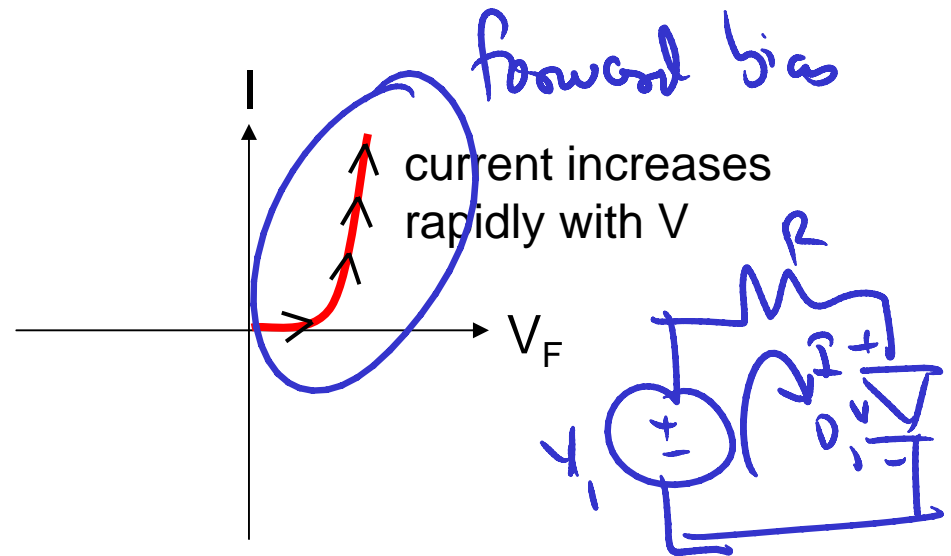In forward bias (+ on p-side) we have almost unlimited flow (very low resistance). Qualitatively, the I-V characteristics must look like:




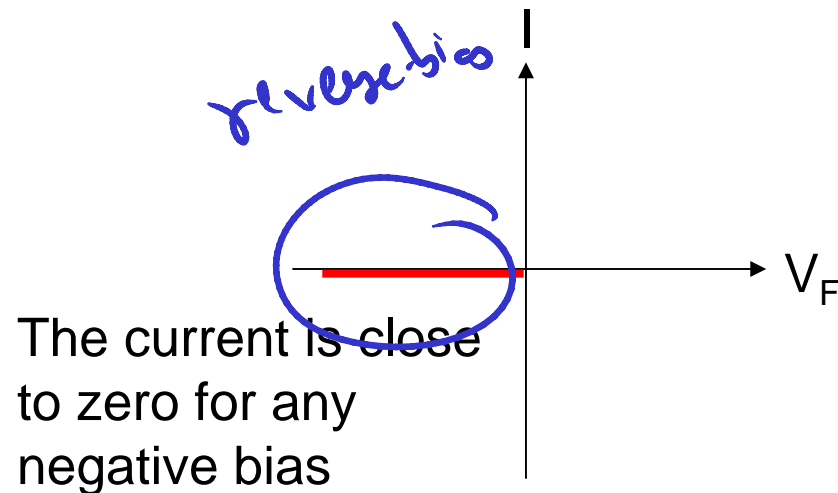In reverse bias (+ on n-side) almost no current can flow. Qualitatively, the I-V characteristics must look like:



pn-Junction Reverse Breakdown

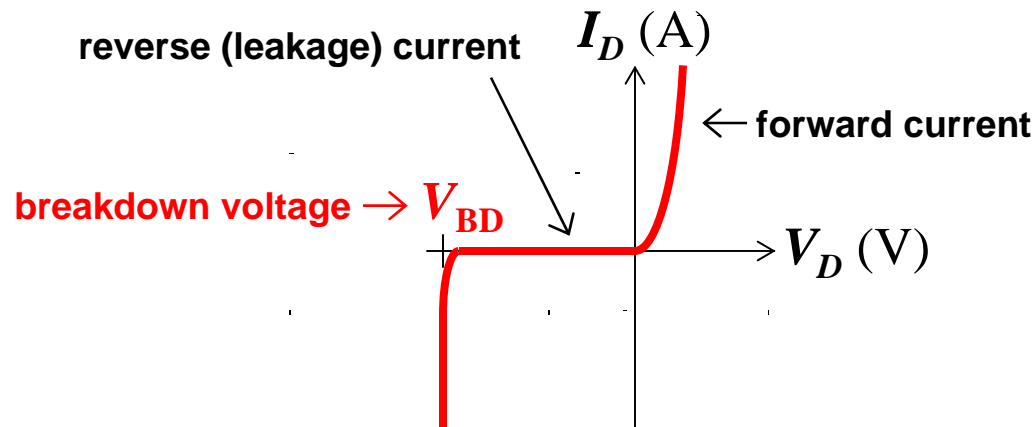- As the reverse bias voltage increases, the peak electric field in the depletion region increases. When the electric field exceeds a critical value ($E_{crit} \cong 2 \times 10^5$ V/cm), the reverse current shows a dramatic increase:



The pn Junction I vs. V Equation

I-V characteristic of PN junctions

In EECS 105, 130, and other courses you will learn why the I vs. V relationship for PN junctions is of the form


$$I = I_0(e^{qV/kT} - 1)$$

where I_0 is a constant proportional to junction area and depending on doping in P and N regions, q = electronic charge = 1.6×10^{-19} , k is Boltzman constant, and T is absolute temperature.
 $kT/q = 0.026V$ at $300^\circ K$, a typical value for I_0 is $10^{-12} - 10^{-15} A$


We note that in forward bias, I increases **exponentially** and is in the μA - mA range for voltages typically in the range of 0.6 - $0.8V$. In reverse bias, the current is essentially zero.

Ideal Diode Model of PN Diode


Circuit symbol

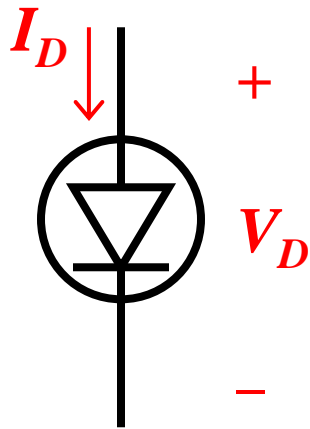

I-V characteristic


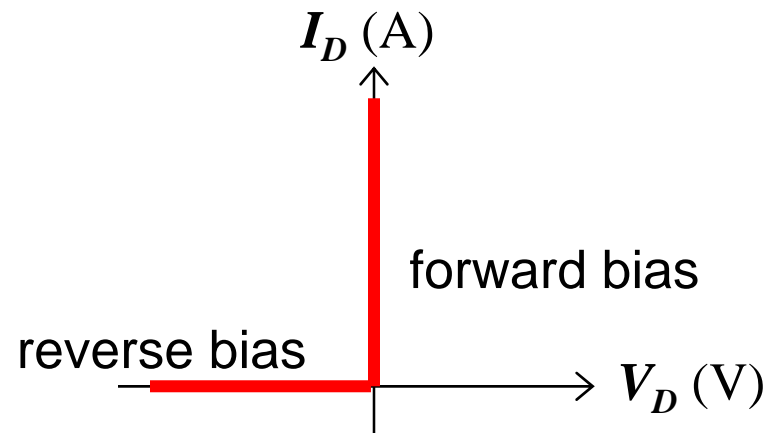


Switch model

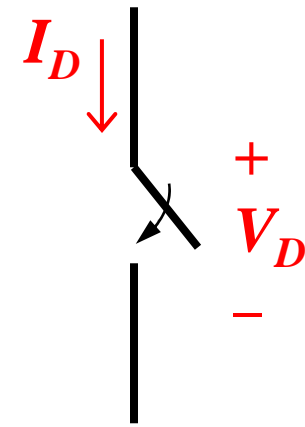


- An ideal diode passes current only in one direction.
 - An **ideal diode** has the following properties:
 - when $I_D > 0$, $V_D = 0$
 - when $V_D < 0$, $I_D = 0$
- Diode behaves like a switch:
- closed in forward bias mode
 - open in reverse bias mode

Diode Large-Signal Model (0.7 V Drop)

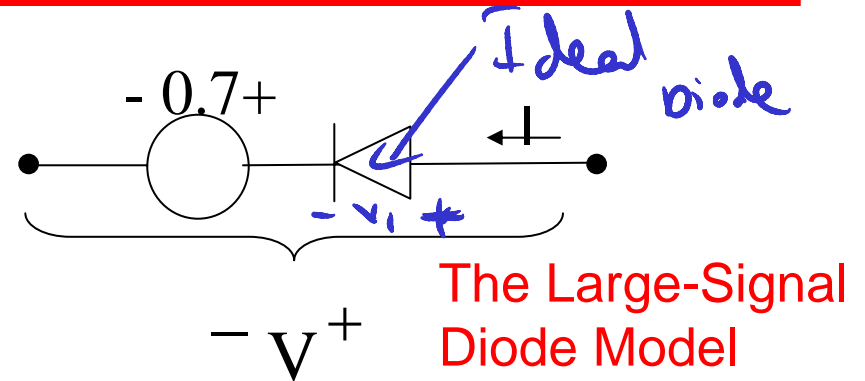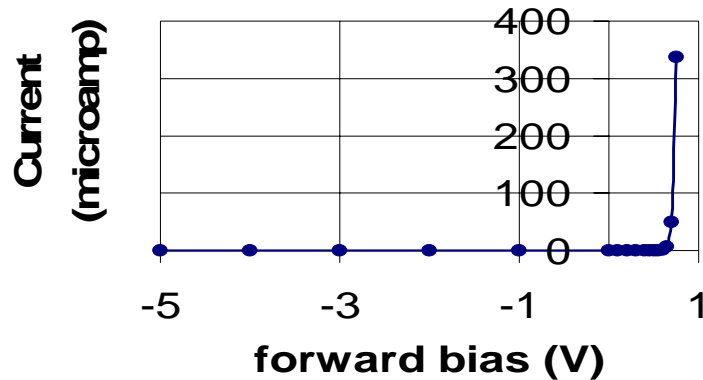


Improved “Large-Signal Diode” Model:

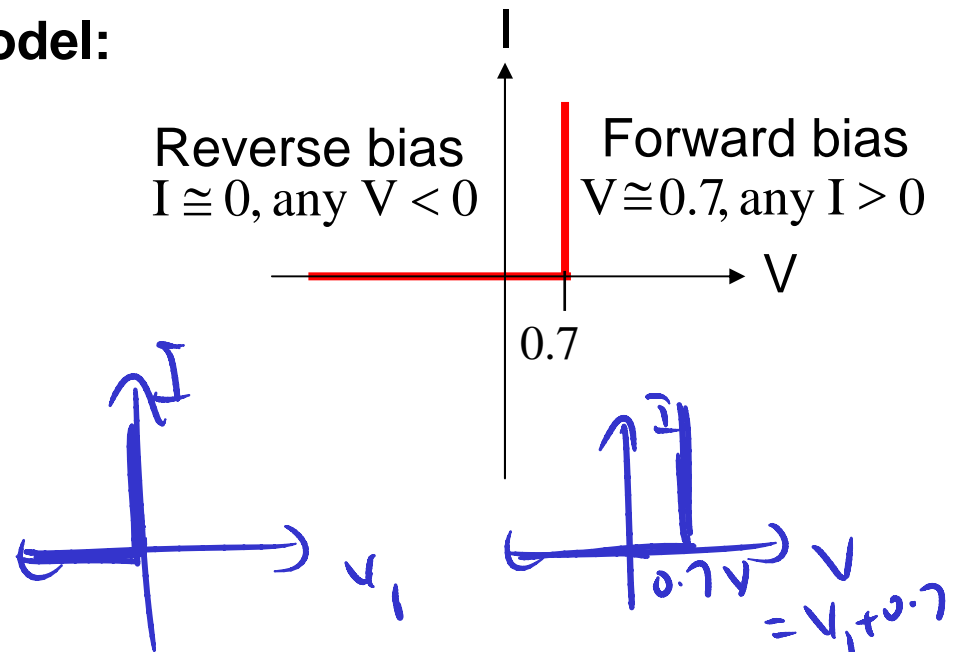If we choose not to ignore the small forward-bias voltage drop of a diode, it is a very good approximation to regard the voltage drop in forward bias as a constant, about 0.7V. the “Large signal model” results.




Large-Signal Diode Model


Circuit symbol

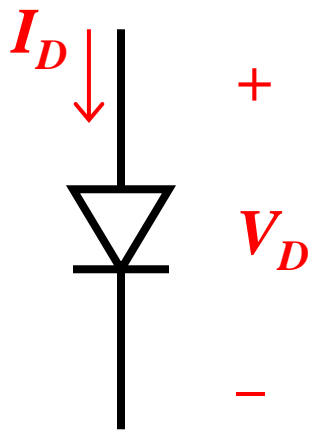

I-V characteristic

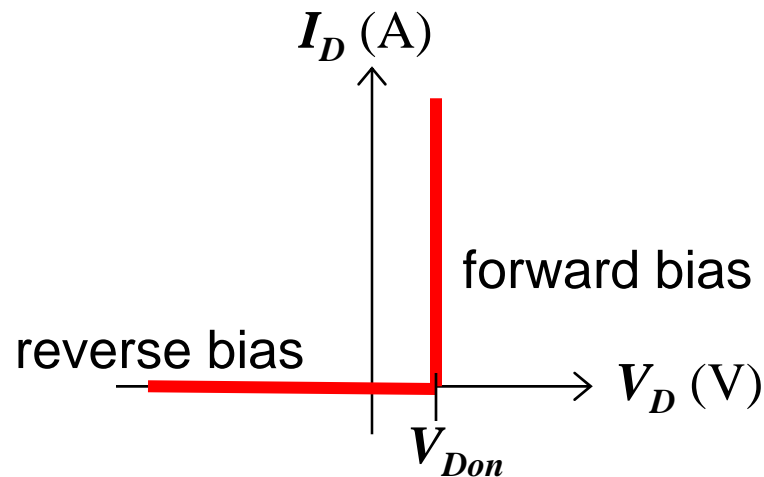

Switch model

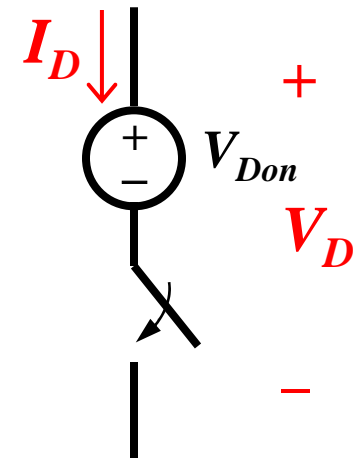

For a Si pn diode, $V_{Don} \cong 0.7 \text{ V}$

RULE 1: When $I_D > 0$, $V_D = V_{Don}$

RULE 2: When $V_D < V_{Don}$, $I_D = 0$

Diode behaves like a voltage source in series with a switch:

- closed in forward bias mode
- open in reverse bias mode