

Lecture 23

- Last time:
 - Introduction to amplifiers: a common-source MOS stage
- Today :
 - Small-signal model for the entire common-source amplifier
 - Limits to model

Dept. of EECS

1


University of California at Berkeley

EECS 105 Fall 2002 Lecture 23

C. J. Spanos

Small-Signal Analysis


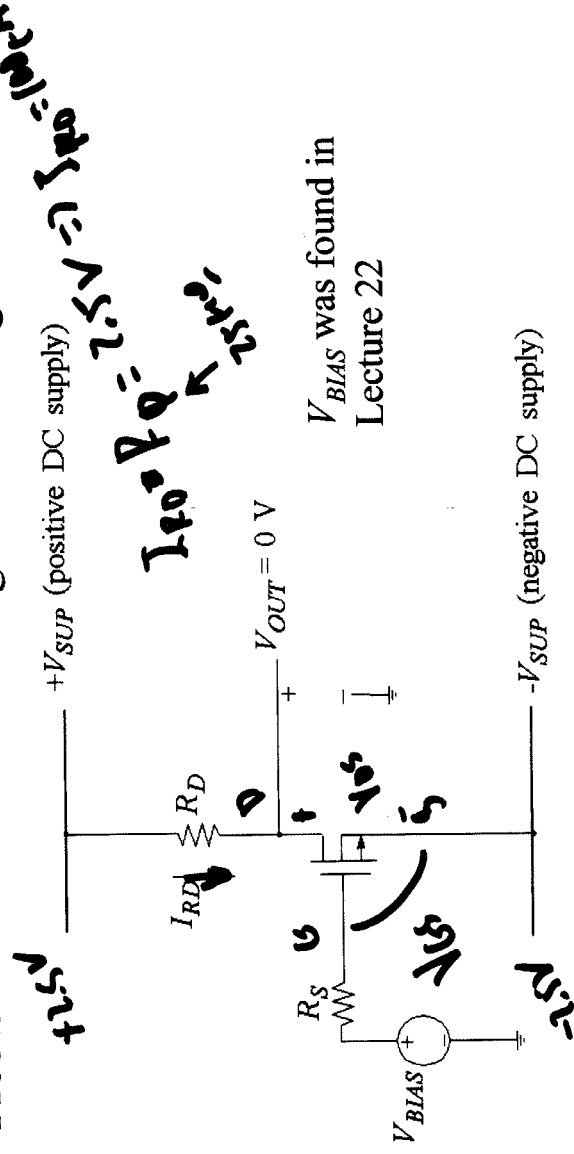
Problem 1. Find DC Bias – ignore small-signal source



Dept. of EECS

2


University of California at Berkeley

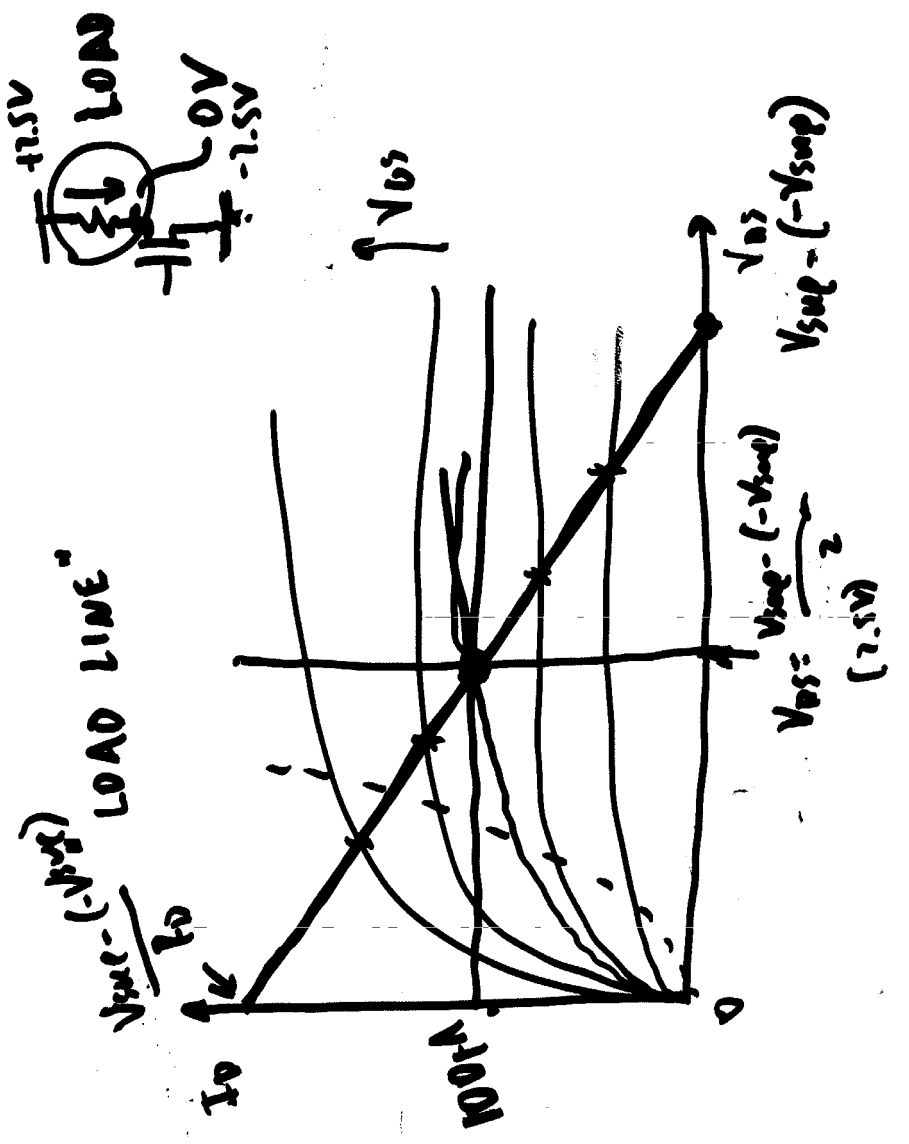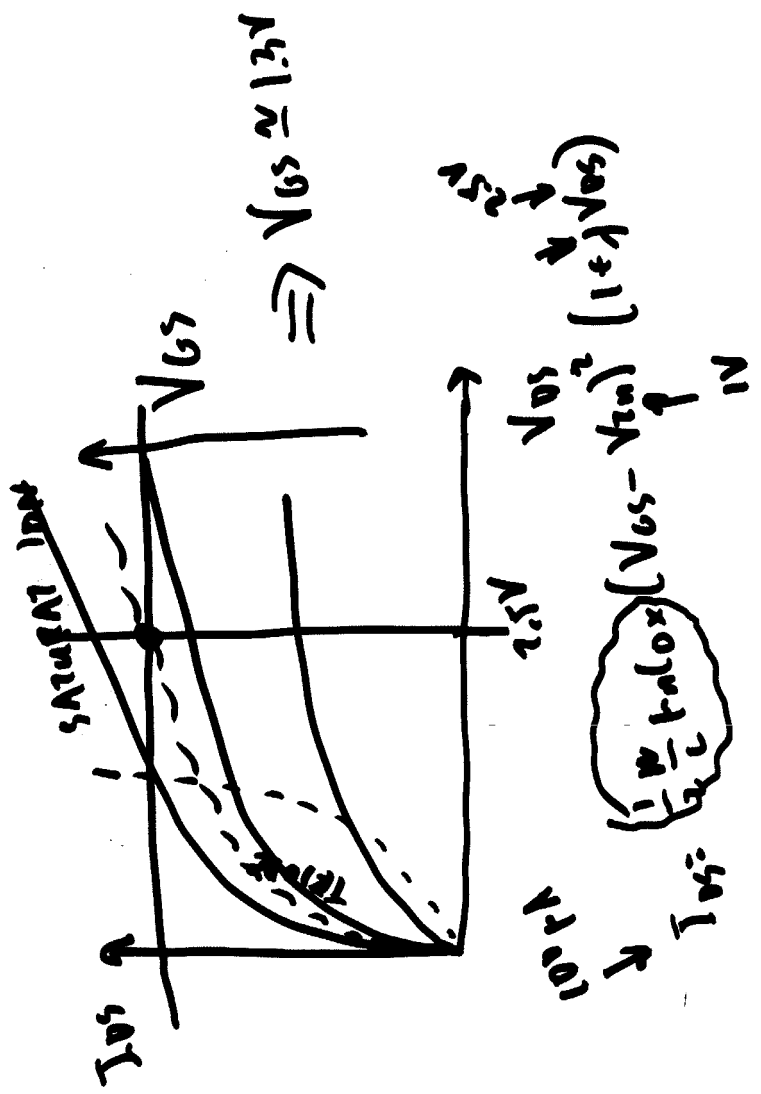

CHARACTERISTIC

2.5V INPUT - OUTPUT

YOUT = 40V

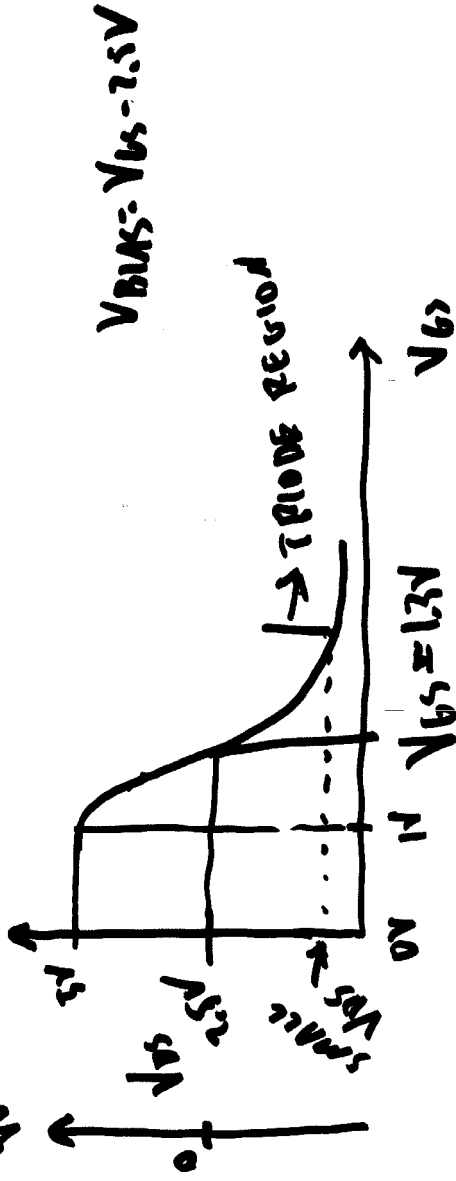

Small-Signal Models of Ideal Supplies

Small-signal model:

V_{BATT}

CLOSED

i_{SUP}

v_{SUP}

$$r_{small\ signal} = \frac{\partial v_{SUP}}{\partial i_{SUP}} = 0 \Omega$$

$$r_{small} = \frac{\partial i_{SUP}}{\partial v_{SUP}} = \infty$$

I_{BIAS}

OPEN


i_{SUP}

v_{SUP}




$$r_{small\ signal} = \frac{\partial v_{SUP}}{\partial i_{SUP}} = \infty \Omega$$

$$r_{small} = \frac{\partial i_{SUP}}{\partial v_{SUP}} = 0 S$$


LARGE

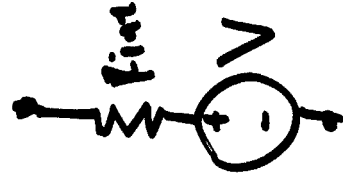

SMALL

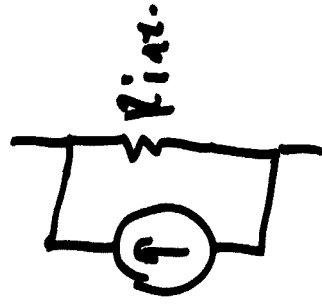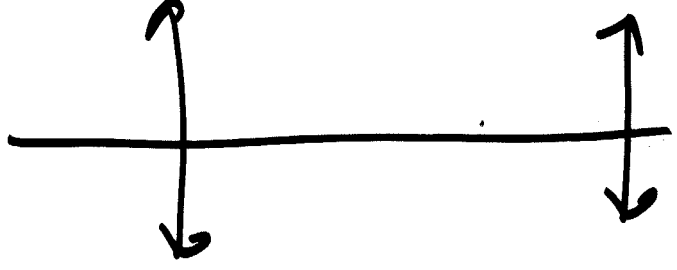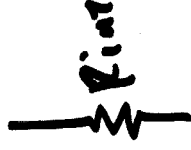


Small-Signal Modeling

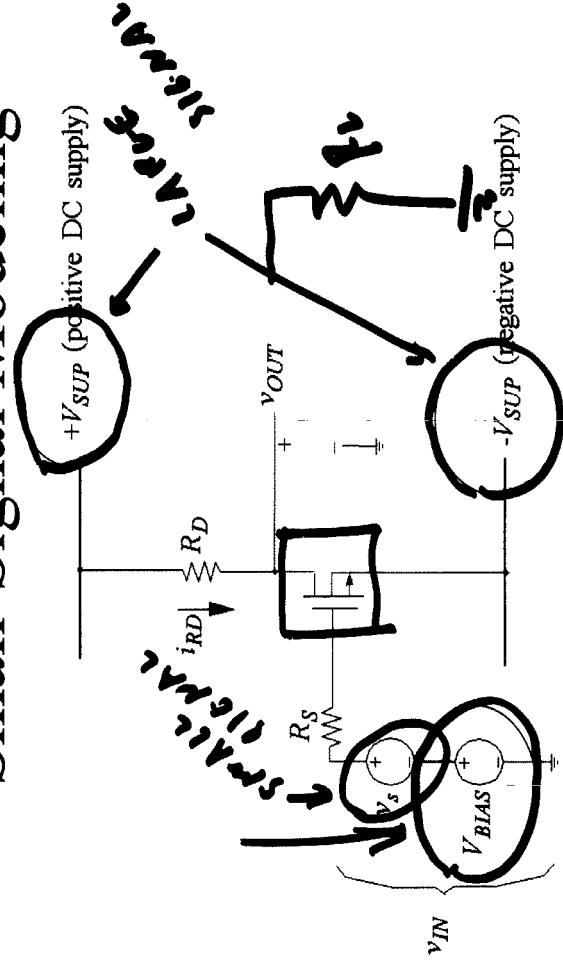

What are the small-signal models of the DC supplies?

Small-Signal Circuit for Amplifier

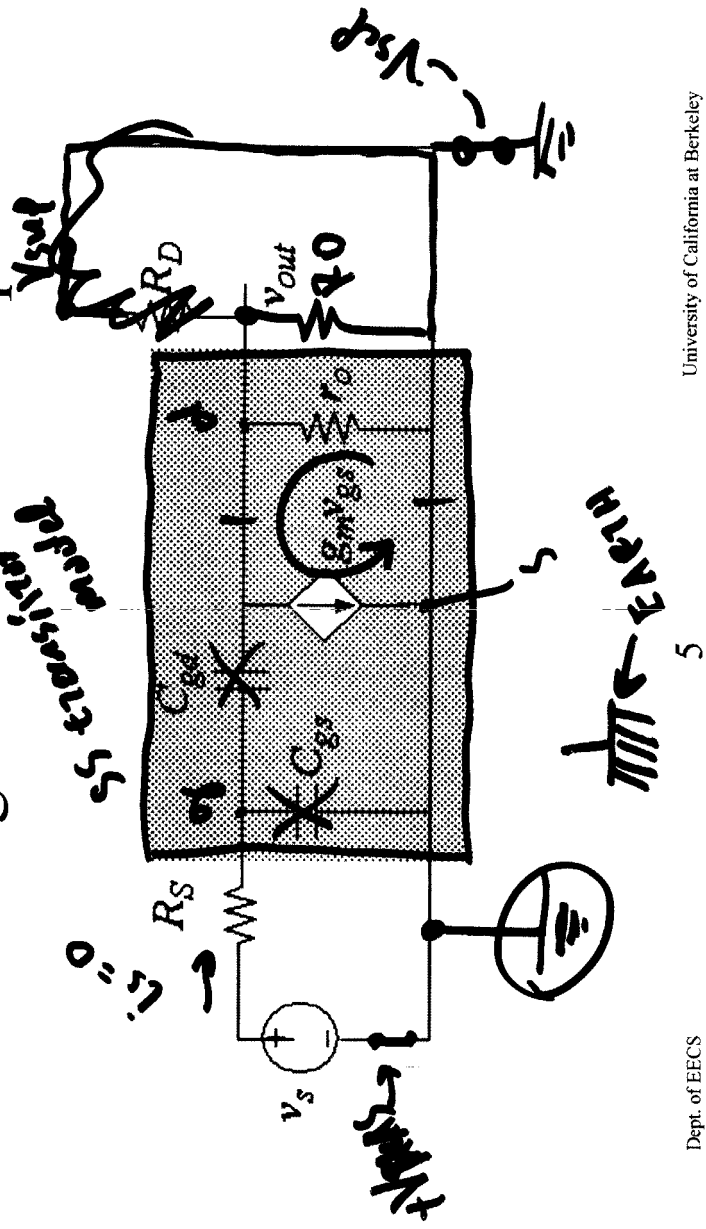


Dept. of EECS

University of California at Berkeley

Low-Frequency Voltage Gain

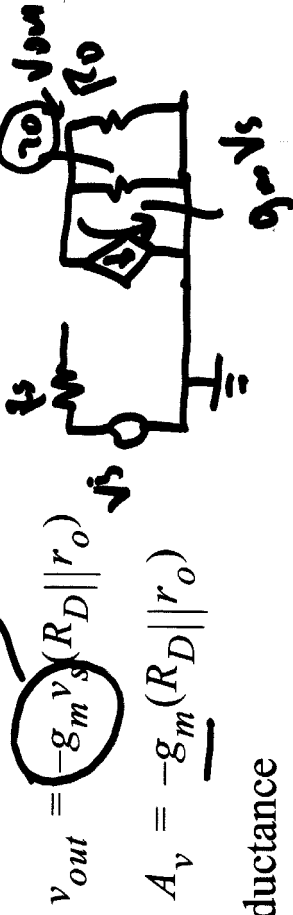Consider first $\omega \rightarrow 0$ case... capacitors are open-circuits



Transconductance


$$g_m = \mu_n C_{ox} (W/L) (V_{GS} - V_{Tn}) = \frac{2I_{D,SAT}}{V_{GS} - V_{Tn}}$$

$$i_{quor}(r_o \parallel R_D) \quad 6$$

Dept. of EECS

University of California at Berkeley

Voltage Gain (Cont.)

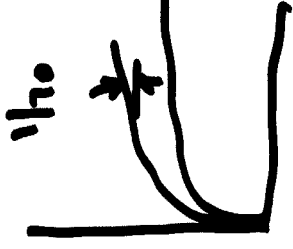

Substitute transconductance:

$$A_v = \left(-\frac{2I_{D,SAT}}{V_{GS} - V_{Th}} \right) (R_D \parallel r_o)$$

Output resistance: typical value $\lambda_n = 0.05 \text{ V}^{-1}$

$$r_o = \left(\frac{1}{\lambda_n I_{D,SAT}} \right) = \left(\frac{1}{0.05 \cdot 0.1} \right) \text{ k}\Omega = \underline{200 \text{ k}\Omega}$$

$$\text{Voltage gain: } A_v = - \left(\frac{2 \cdot 0.1}{0.31} \right) (25 \parallel \underline{200}) = \underline{-14.3}$$

(-16.1)

Dept. of EECS



7

University of California at Berkeley

Input and Output Waveforms

Input small-signal voltage amplitude: 25 mV

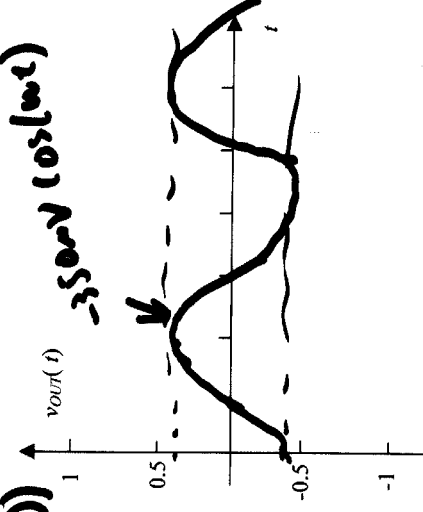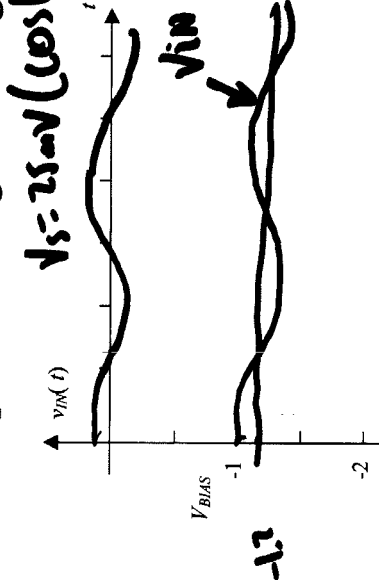Output small-signal voltage amplitude: $14 \times 25 \text{ mV} = 350 \text{ mV}$



Dept. of EECS

8

University of California at Berkeley

What Limits the Output Amplitude?

1. $v_{OUT}(t)$ reaches V_{SUP} or $-V_{SUP} \dots$ or
2. MOSFET leaves constant-current region and enters triode region **131V**
 $V_{DS} \leq V_{DS,SAT} = V_{GS} - V_{Tn} = \mathbf{0.31V}$
 $v_{OUT,MIN} = -V_{SUP} + V_{DS,SAT} = -2.5V + 0.31V$
-2.19V

Dept. of EECS

9

University of California at Berkeley


Maximum Output Amplitude

$$v_{out}(t) = -2.19 \text{ V} \cos(\omega t) \rightarrow v_s(t) = \underbrace{153 \text{ mV}}_{v_{\text{max input}}} \cos(\omega t)$$

How accurate is the small-signal (linear) model?

$$\frac{v_s}{V_{GS} - V_{Tn}} = \frac{0.15}{0.31} \approx 0.5$$

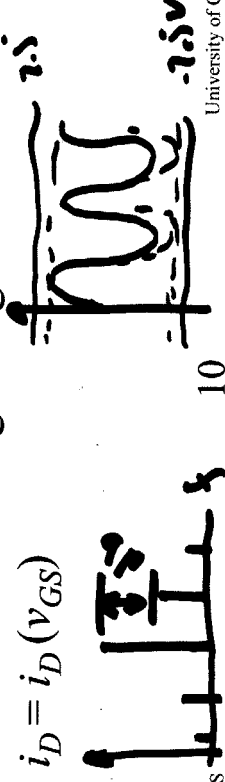Significant error in neglecting third term in expansion of $i_D = i_D(v_{GS})$



Dept. of EECS

10

University of California at Berkeley