

Lecture 23: Multistage Amps-Cascades and Cascode

Prof. Niknejad




Lecture Outline

 - Example 1: Cascodes Amp Design
- Example 2: Two Stage CS Amp


CG Cascade: DC Biasing

Two stages can have different supply currents




Extreme case:
 $I_{BIAS2} = 0$ A

CG Cascade: Sharing a Supply

 

First stage has no current supply of its own \rightarrow its output resistance is modified

The Cascode Configuration

 


Common source / common gate cascade is one version of a *cascode* (all have shared supplies)

DC bias:

Two-port model: first stage has no current supply of its own

Cascode Two-Port Model

 

Output resistance of first stage = $R_{out,CS^*} = R_{down,CS} = r_{o1}$

$$R_{out} \approx r_{oc2} \parallel (1 + g_m r_{o1}) r_{o2}$$


$$G_m = g_{m1}$$

$$R_{in} = \infty$$

Why is the cascode such an important configuration?


Miller Capacitance of Input Stage

Find the Miller capacitance for C_{gd1}

 

Input resistance to common-gate second stage is low \rightarrow gain across C_{gd1} is small.

Two-Port Model with Capacitors

 


Miller capacitance: $C_M = (1 - A_{vC_{gd1}})C_{gd1}$

$$A_{vC_{gd1}} = -g_{m1} \left(\frac{1}{g_{m2}} \parallel r_{o1} \right) \approx -\frac{g_{m1}}{g_{m2}} = -1$$

$$C_M = 2C_{gd1}$$


Generating Multiple DC Voltages

 

Stack-up diode-connected MOSFETs or BJTs and run a reference current through them \rightarrow pick off voltages from gates or bases as references


Multistage Amplifier Design Examples

 Start with basic two-stage transconductance amplifier:



Why do this combination?


Current Supply Design

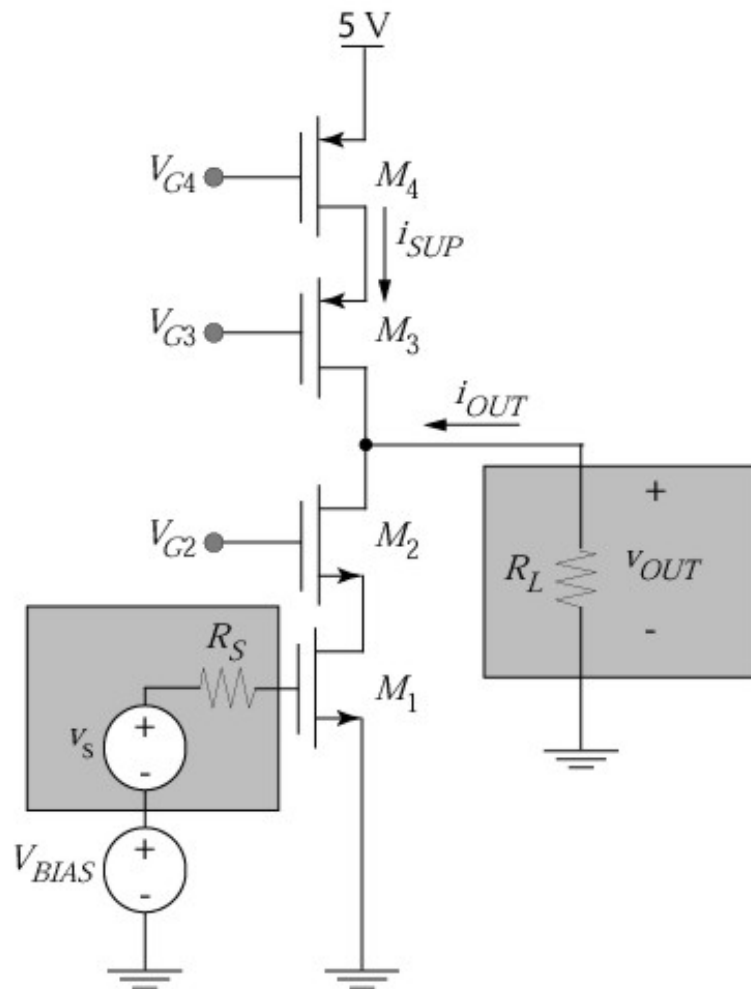

Output resistance
goal requires large
 $r_{oc} \rightarrow$
use cascode current
source


Totem Pole Voltage Supply

 DC voltages must be set for the cascode current supply transistors M_3 and M_4 , as well as the gate of M_2 .



Why include M_{2B} ?

Complete Amplifier Schematic

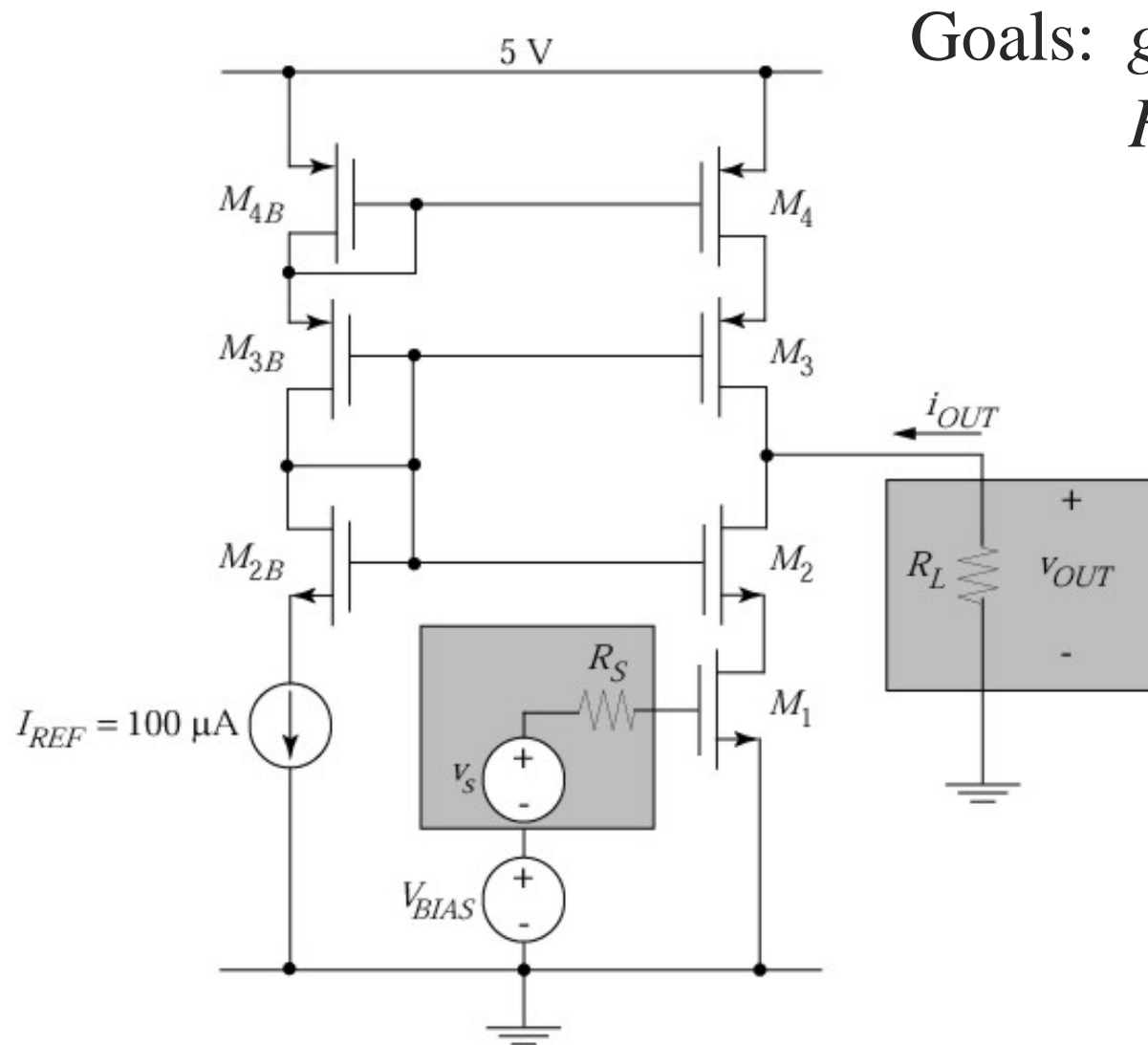

Goals: $g_{m1} = 1 \text{ mS}$,
 $R_{out} = 10 \text{ M}\Omega$

Device Sizes

M_1 : select $(W/L)_1 = 200/2$ to meet specified $g_{m1} = 1 \text{ mS}$
 \rightarrow find $V_{BIAS} = 1.2 \text{ V}$


Cascode current supply devices: select $V_{SG} = 1.5 \text{ V}$
 $(W/L)_4 = (W/L)_{4B} = (W/L)_3 = (W/L)_{3B} = 64/2$

M_2 : select $(W/L)_2 = 50/2$ to meet specified $R_{out} = 10 \text{ M}\Omega$
 \rightarrow find $V_{GS2} = 1.4 \text{ V}$

Match M_2 with diode-connected device M_{2B} .

Assuming perfect matching and zero input voltage,
 what is V_{OUT} ?

Output (Voltage) Swing

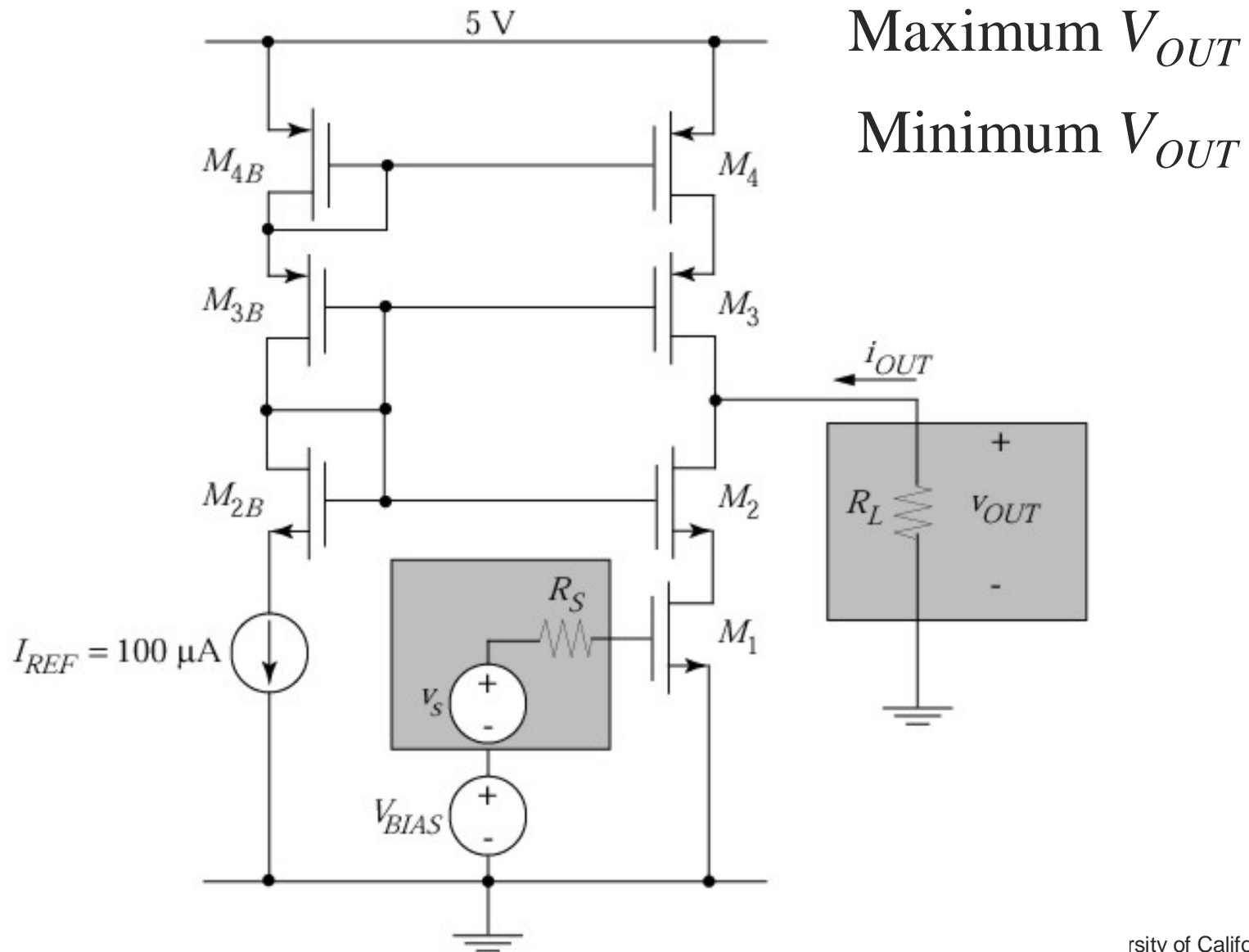

Two-Port Model

Find output resistance R_{out}

$$\lambda_n = (1/20) \text{ V}^{-1}, \lambda_p = (1/50) \text{ V}^{-1} \text{ at } L = 2 \mu\text{m} \rightarrow$$

$$r_{on} = (100 \mu\text{A} / 20 \text{ V}^{-1})^{-1} = 200 \text{ k}\Omega, r_{op} = 500 \text{ k}\Omega$$


$$g_{m2} = \frac{2I_{D2}}{V_{GS2} - V_{Tn}} = \frac{2(100\mu\text{A})}{1.4\text{V} - 1\text{V}} = 500\mu\text{S}$$

$$g_{m3} = \frac{2(-I_{D3})}{V_{SG3} + V_{Tp}} = \frac{2(100\mu\text{A})}{1.5\text{V} - 1\text{V}} = 400\mu\text{S}$$

$$R_{out} = r_{oc} \parallel r_{o2} (1 + g_{m2} R_{S2}) = r_{o3} (1 + g_{m3} R_{S3}) \parallel r_{o2} (1 + g_{m2} r_{o1})$$


Voltage Transfer Curve

 Open-circuit voltage gain: $A_v = v_{out} / v_{in} = -g_{m1}R_{out}$




Two-Stage Amplifier Topology

Direct DC connection: use NMOS then PMOS

 


Current Supply Design

 


Assume that the reference is a “sink” set by a resistor

Must mirror the reference current and generate a sink for $i_{SUP 2}$

Use Basic Current Supplies

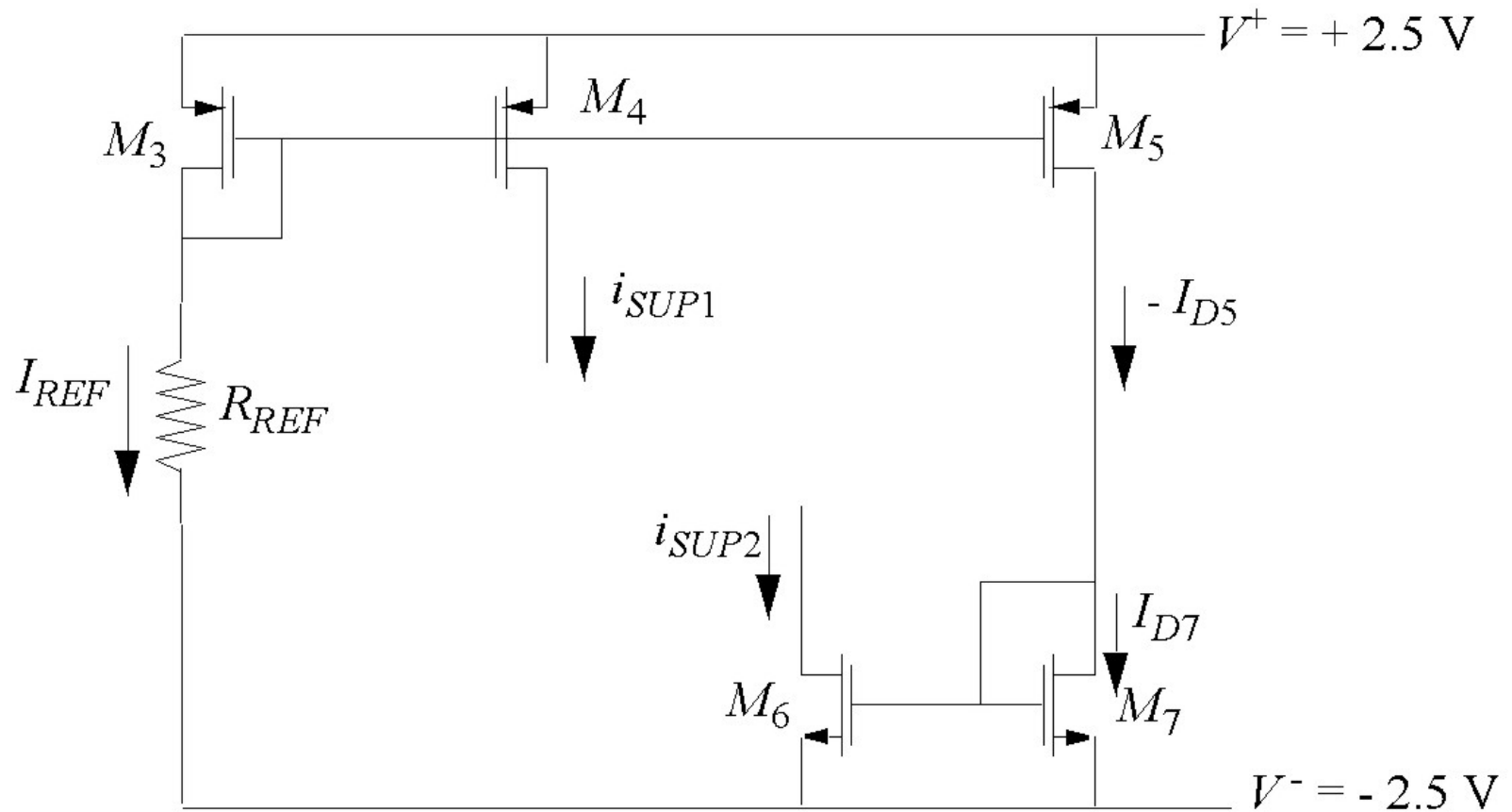

Complete Amplifier Topology

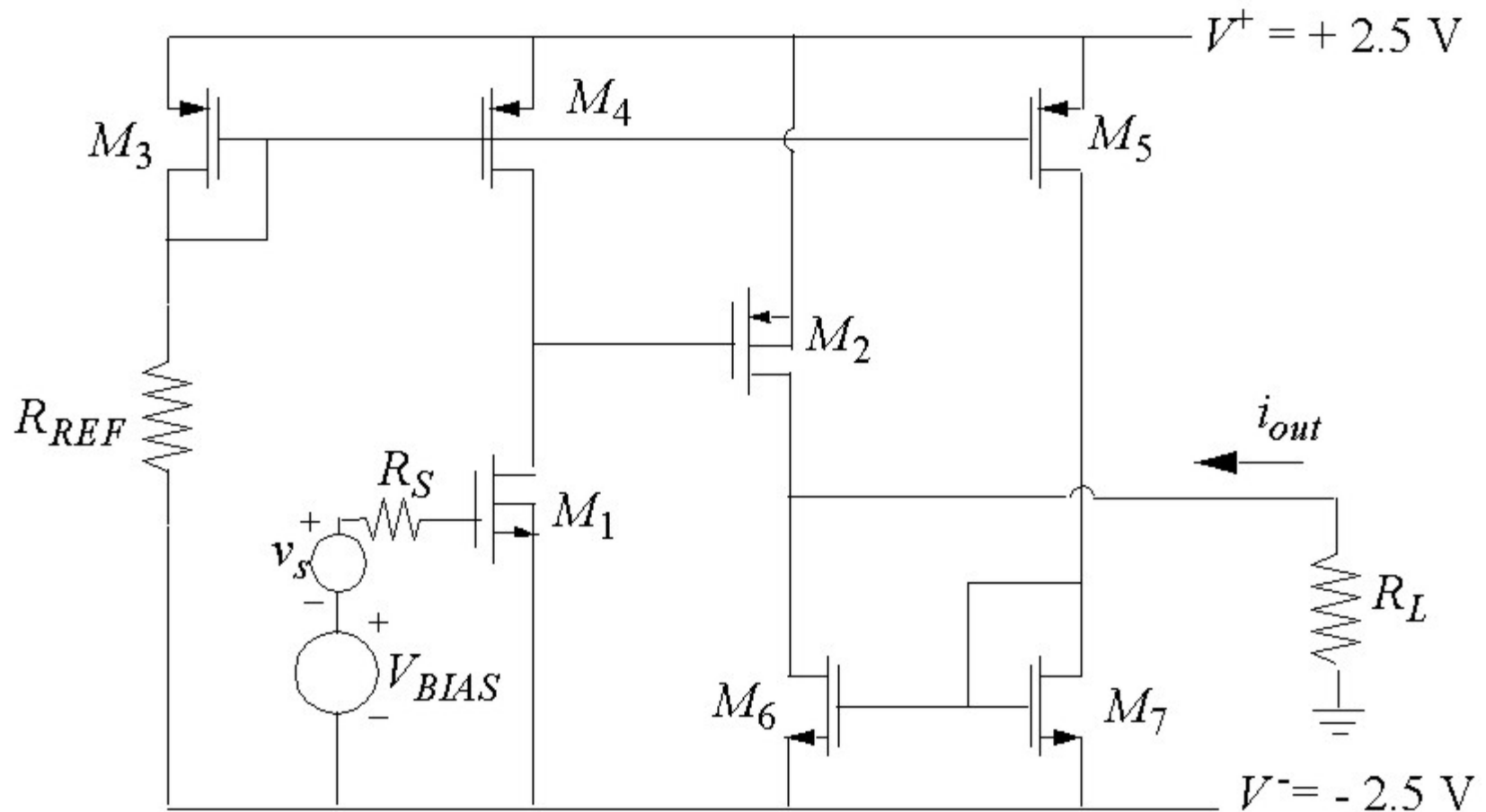

What's missing? The device dimensions and the bias voltage and reference resistor