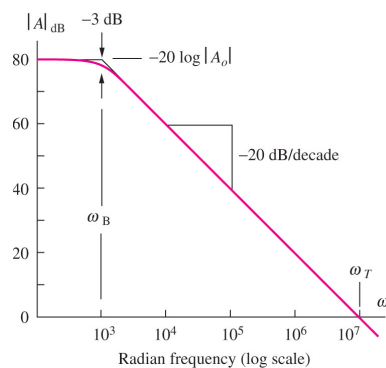


EE105 – Fall 2014 Microelectronic Devices and Circuits

Prof. Ming C. Wu
wu@eecs.berkeley.edu
511 Sutardja Dai Hall (SDH)



Op Amp Frequency Response Single-pole Amplifiers



General purpose op amps are typically low-pass amplifiers with high gain at dc and a single-pole frequency response.


$$A_v(s) = \frac{A_o \omega_B}{s + \omega_B} = \frac{\omega_T}{s + \omega_B}$$

$$|A(j\omega)| = \frac{A_o \omega_B}{\sqrt{\omega^2 + \omega_B^2}} = \frac{A_o}{\sqrt{1 + \frac{\omega^2}{\omega_B^2}}}$$

ω_B = open loop bandwidth of the op amp. ω_T = unity gain frequency or gain bandwidth product (frequency at which magnitude of gain is unity).



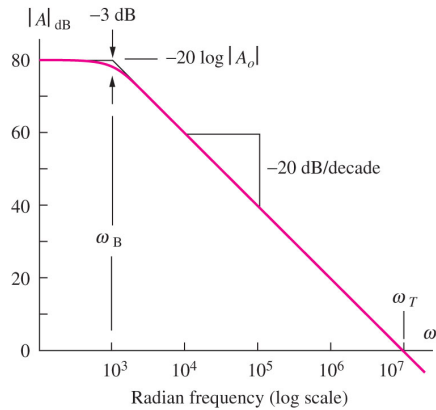Op Amp Frequency Response Single-pole Amplifiers (cont.)



$$\text{For } \omega \gg \omega_B, |A(j\omega)| = \frac{A_o \omega_B}{\omega} = \frac{\omega_T}{\omega}$$

$$\text{and } |A(j\omega)| \cdot \omega = \omega_T$$


$$\text{For } \omega = \omega_T, |A(j\omega)| = \frac{\omega_T}{\omega_T} = 1$$

For $\omega \gg \omega_B$, the product of magnitude of amplifier gain and frequency is a constant value equal to the unity-gain frequency.

Hence, ω_T is also called the gain-bandwidth product.



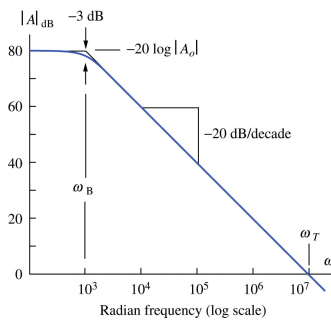Op Amp Frequency Response Single-Pole Amplifier Example



Single-pole amplifier response:

$$A_v(s) = \frac{A_o \omega_B}{s + \omega_B} = \frac{\omega_T}{s + \omega_B}$$

$$A_o = 10^{\frac{80 \text{ dB}}{20}} = 10^4 \quad \omega_B = 10^3 \text{ rad/s}$$

$$\omega_T = A_o \omega_B = 10^7 \text{ rad/s}$$

$$A_v(s) = \frac{10^7}{s + 10^3}$$

Frequency values are often expressed in Hz:

$$f_B = \frac{\omega_B}{2\pi} = 159 \text{ Hz} \quad f_T = \frac{\omega_T}{2\pi} = 1.59 \text{ MHz}$$

- **Problem:**
Find transfer function describing frequency-dependent amplifier voltage gain.



Frequency Response of Noninverting Amplifier

For a closed-loop feedback amplifier:


$$A_v(s) = \frac{A(s)}{1 + A(s)\beta} = \frac{A_o \omega_B}{s + \omega_B(1 + A_o\beta)}$$

$$A_v(s) = \frac{\frac{A_o}{1 + A_o\beta}}{\frac{s}{\omega_B(1 + A_o\beta)} + 1} = \frac{A_v(0)}{\frac{s}{\omega_H} + 1}$$

$$\omega_H = (1 + A_o\beta)\omega_B = \frac{\omega_T}{A_v(0)}$$

For $A_o\beta \gg 1$,
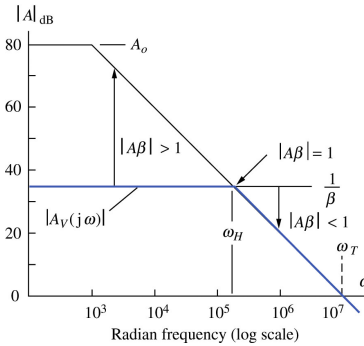
$$A_v(0) \cong \frac{1}{\beta} \quad \text{and} \quad \omega_H \cong \beta\omega_T$$



At low frequencies, gain is set by the feedback, but at high frequencies, it follows the gain of the amplifier.



Frequency Response of Noninverting Amplifier

- **Given data:** $A_o = 10^5 = 100 \text{ dB}$, $f_T = 10 \text{ MHz}$, desired $A_v = 1000$ or 60 dB
- **Assumptions:** Amplifier is described by a single-pole transfer function.
- **Analysis:**

$$f_B = \frac{f_T}{A_o} = \frac{10^7 \text{ Hz}}{10^5} = 100 \text{ Hz}$$

$$f_H = f_B(1 + A_o\beta) = f_B \left(1 + \frac{A_o}{A_v(0)} \right) = 100 \left(1 + \frac{10^5}{10^3} \right) = 10.1 \text{ kHz}$$

$$\text{Op amp transfer function: } A_v(s) = \frac{\omega_T}{s + \omega_B} = \frac{2 \times 10^7 \pi}{s + 200\pi}$$

$$\text{Close-loop amplifier transfer function: } A_v(s) = \frac{\omega_T}{s + \omega_B(1 + A_o\beta)} = \frac{2 \times 10^7 \pi}{s + 2.01 \times 10^4 \pi}$$



Frequency Response of Inverting Amplifier

$$A_v(s) = A_v^{ideal} \frac{T}{1+T} = A_v^{ideal} \frac{A(s)\beta}{1+A(s)\beta} = \left(-\frac{R_2}{R_1}\right) \frac{\frac{A_o\beta}{1+A_o\beta}}{\frac{s}{(1+A_o\beta)\omega_B} + 1}$$

For $A_o\beta \gg 1$,

$$A_v(s) \cong \left(-\frac{R_2}{R_1}\right) \frac{1}{\frac{s}{\omega_H} + 1} \quad \omega_H = \frac{\omega_T}{\frac{A_o}{1+A_o\beta}} \cong \beta\omega_T$$



Frequency Response of Inverting Amplifier

- **Given data:** $A_o = 2 \times 10^5$, $f_T = 5 \times 10^5$ Hz, desired $A_v = -100$ or 40 dB
- **Assumptions:** Amplifier is described by a single-pole transfer function.
- **Analysis:**

$$f_b = \frac{f_T}{A_o} = \frac{5 \times 10^5 \text{ Hz}}{2 \times 10^5} = 2.5 \text{ Hz} \quad \beta = \frac{1}{1+|A_v(0)|} = \frac{1}{101}$$

$$f_H = f_b(1+A_o\beta) = 2.5 \text{ Hz} \left(1 + \frac{2 \times 10^5}{101}\right) = 4.95 \text{ kHz}$$

$$\text{Op amp transfer function: } A_o(s) = \frac{\omega_T}{s + \omega_B} = \frac{10^6 \pi}{s + 5\pi}$$

Inverting amplifier transfer function:

$$A_v(s) = A_v(0) \frac{\beta\omega_T}{s + \omega_B(1+A_o\beta)} = -\frac{9.9 \times 10^5 \pi}{s + 9.91 \times 10^3 \pi}$$



Op Amp Frequency Response Summary


TABLE 11.3

Inverting and Noninverting Amplifier Frequency Response Comparison

$\beta = \frac{R_1}{R_1 + R_2}$	NONINVERTING AMPLIFIER	INVERTING AMPLIFIER
dc gain	$A_v(0) = 1 + \frac{R_2}{R_1}$	$A_v(0) = -\frac{R_2}{R_1}$
Feedback factor	$\beta = \frac{1}{A_v(0)}$	$\beta = \frac{1}{1 + A_v(0) }$
Bandwidth	$f_B = \beta f_T$	$f_B = \beta f_T$
Input resistance	$R_{ic} \parallel R_{id}(1 + A\beta)$	$R_1 + \left(R_{ID} \parallel \frac{R_2}{1 + A} \right)$
Output resistance	$\frac{R_o}{1 + A\beta}$	$\frac{R_o}{1 + A\beta}$



Feedback Control of Frequency Response

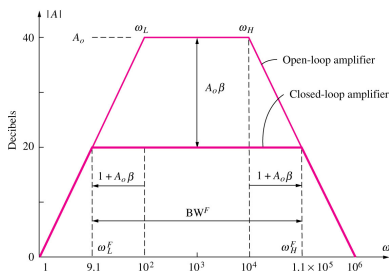

$$A_v(s) = A_o \frac{\omega_H s}{s^2 + [\omega_L + (1 + A_o \beta) \omega_H] s + \omega_L \omega_H}$$

For $\omega_H (1 + A_o \beta) \gg \omega_L$:

$$\omega_L^F \cong \frac{\omega_L}{1 + A_o \beta} \quad \omega_H^F \cong \omega_H (1 + A_o \beta)$$

$$BW_F \cong \omega_H (1 + A_o \beta)$$

Upper and lower cutoff frequencies as well as bandwidth of amplifier are improved, gain is stabilized at

$$A_v(s) = \frac{A(s)}{1 + A(s)\beta}$$

where $A(s) = A_o \frac{s}{(s + \omega_L) \left(1 + \frac{s}{\omega_H} \right)} = \frac{A_o \omega_H s}{(s + \omega_L)(s + \omega_H)}$


$$A_{mid} = \frac{A_o}{1 + A_o \beta}$$

$$GBW = A_{mid} \cdot BW_F = A_o \omega_H$$



Large Signal Limitations Slew Rate and Full-Power Bandwidth

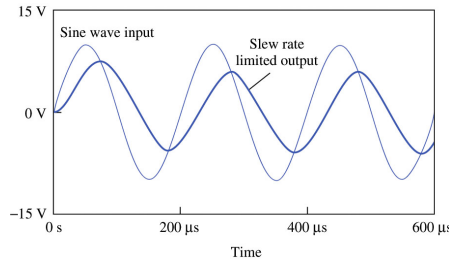- **Slew rate:** Maximum rate of change of voltage at the output of an op amp. Typical values range from 0.1V/μs to 10V/μs.



$$v_o = V_M \sin \omega t$$

$$\left. \frac{dv_o}{dt} \right|_{\max} = V_M \omega \cdot \cos \omega t \Big|_{\max} = V_M \omega$$

For no signal distortion,

$$V_M \omega \leq SR \rightarrow V_M \leq \frac{SR}{\omega}$$


Full-power bandwidth is highest frequency at which a full-scale signal can be developed.

$$f_M \leq \frac{SR}{2\pi V_{FS}}$$

- For given frequency, slew rate limits the maximum signal amplitude that can be amplified without distortion.



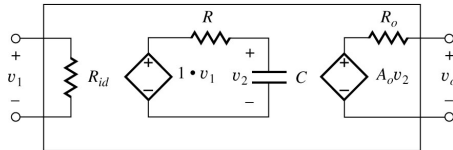Operational Amplifier Macro Model for Frequency Response



- Simplified circuit representations are available in most simulators to model the terminal behavior of op amps that include all nonideal limitations of op amps and a large number of parameters that can be adjusted to model op amp behavior.
- To model a single-pole roll-off, an auxiliary “dummy” loop (voltage controlled voltage source v_1 in series with R and C) is added to the original two-port model.

$$A_v(s) = \frac{V_o(s)}{V_1(s)} = \frac{A_o \omega_B}{s + \omega_B} = \frac{A_o}{\frac{s}{\omega_B} + 1} \quad \omega_B = \frac{1}{RC}$$

- The RC product is chosen to give the desired -3dB point for the open-loop amplifier.



General Purpose Op Amp Parameters Sample Values

TABLE 11.4
Typical Op Amp Macro Model Parameter Set

PARAMETER	TYPICAL VALUE
Differential-mode gain (dc)	106 dB
Differential-mode input resistance	2 M Ω
Input capacitance	1.5 pF
Common-mode rejection ratio	90 dB
Common-mode input resistance	2 G Ω
Output resistance	50 Ω
Input offset voltage	1 mV
Input bias current	80 nA
Input offset current	20 nA
Positive slew rate	0.5 V/ μ s
Negative slew rate	0.5 V/ μ s
Maximum output source current	25 mA
Maximum output sink current	25 mA
Input type (<i>n</i> - or <i>p</i> -type)	<i>n</i> -type
Frequency of first pole	5 Hz
Frequency of zero	5 MHz
Frequency of second pole	2 MHz
Frequency of third pole	20 MHz
Frequency of fourth pole	100 MHz
Power supply voltage (3-pin model)	15 V

Note the four-pole frequency response

