

EE105 – Fall 2014

Microelectronic Devices and Circuits

Prof. Ming C. Wu

wu@eecs.berkeley.edu

511 Sutardja Dai Hall (SDH)




Lecture 10: BJT Physics

1



NPN Bipolar Junction Transistor (BJT)

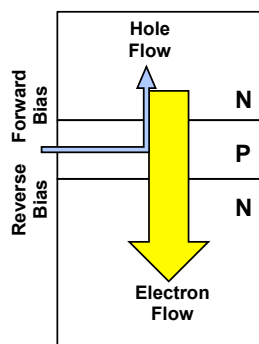

Note: BJT is NOT 2 back-to-back junction diodes.

- 3 layers of semiconductors
 - Emitter (N-type), Base (P-type), Collector (N-type)
 - B-E junction forward-biased
 - B-C junction reverse-biased
- Two important criteria
 - Emitter more heavily doped than base
 - Much more electrons injected into base than holes into emitter
 - Base very thin
 - Most electrons travel through base and reach collector
- Current gain
 - Small base current controls large collector current




Lecture 10: BJT Physics

2



Physical Construction of BJT

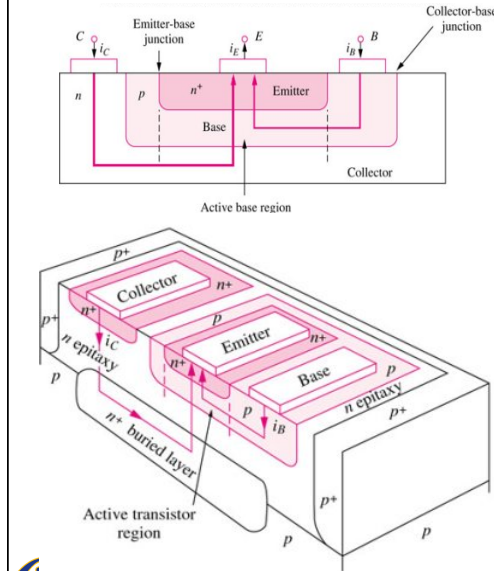

- The transistor is usually planar
 - All contacts are on the front side
- Emitter and base are created by “ion implantation”
- To facilitate electrons travel to collector contact, an n+ buried layer is usually employed to reduce collector resistance.
- Typical doping
 - $N_E > 10^{18} \text{ cm}^{-3}$
 - $N_B \sim 10^{16} \text{ cm}^{-3}$
 - $N_C \sim 10^{15} \text{ cm}^{-3}$





Lecture 10: BJT Physics

3



nnp Transistor Forward Characteristics

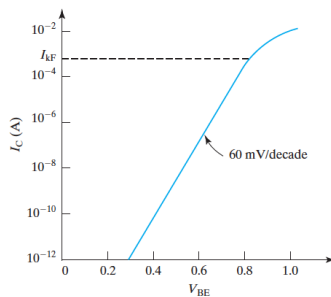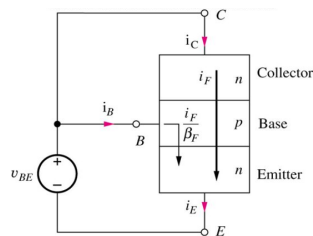

Collector current:

$$i_C = I_S \left[\exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right]$$

$$V_T = \frac{kT}{q} \quad (26\text{mV at room temp})$$

I_S : BJT saturation current

(note: different from pn junction's I_S)

Base current: $i_B = \frac{i_C}{\beta_F}$

Emitter current: $i_E = i_B + i_C = \left(\frac{1}{\beta_F} + 1 \right) i_C = \frac{i_C}{\alpha_F}$

β_F : current gain (typical value: ~ 100)

$\alpha_F = \frac{\beta_F}{\beta_F + 1}$: typical value 0.95 to 0.99




Lecture 10: BJT Physics

4



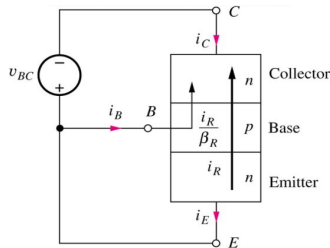npn Transistor Reverse Characteristics (Low Gain, Used Rarely in This Mode)



β_R is the reverse common-emitter current gain. β_R is typically small, even smaller than 1, because the doping profile is optimized for forward active gain.

Collector current i_C is given by

$$i_C = i_B - i_E = \frac{I_S}{\alpha_R} \left[\exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right]$$

Emitter current i_E is

$$i_E = -i_R = I_S \left[\exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right]$$

Base current i_B is given by

$$i_B = \frac{i_R}{\beta_R} = \frac{I_S}{\beta_R} \left[\exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right]$$

α_R is the reverse common-base current gain

$$\alpha_R = \frac{\beta_R}{\beta_R + 1}$$



npn Transistor Complete Transport Model - Valid for Any Bias

$$i_C = I_S \left[\exp\left(\frac{v_{BE}}{V_T}\right) - \exp\left(\frac{v_{BC}}{V_T}\right) \right] - \frac{I_S}{\beta_R} \left[\exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right]$$

$$i_E = I_S \left[\exp\left(\frac{v_{BE}}{V_T}\right) - \exp\left(\frac{v_{BC}}{V_T}\right) \right] + \frac{I_S}{\beta_F} \left[\exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right]$$


$$i_B = \frac{I_S}{\beta_F} \left[\exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right] - \frac{I_S}{\beta_R} \left[\exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right]$$

First term in both emitter and collector current expressions gives current transported completely across base region.

Symmetry exists between base-emitter and base-collector voltages in establishing dominant current in bipolar transistor.




pnp Transistor Structure

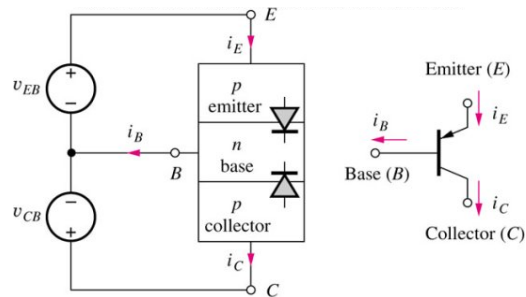

- Voltages v_{EB} and v_{CB} are positive when they forward bias their respective pn junctions.
- Collector current and base current exit transistor terminals and emitter current enters the device.



pnp Transistor Forward Characteristics

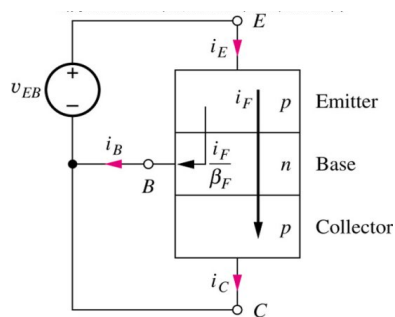

Collector current i_C equals the forward transport current is

$$i_C = i_F = I_S \left[\exp\left(\frac{v_{EB}}{V_T}\right) - 1 \right]$$

Base current i_B is given by


$$i_B = \frac{i_C}{\beta_F}$$

Emitter current i_E is given by

$$i_E = i_C + i_B = \frac{i_C}{\alpha_F}$$



Transport Model Circuit Representations

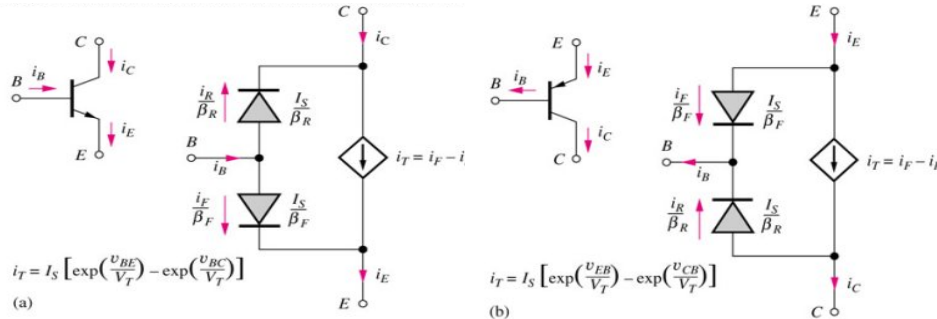

In *npn* transistor (expressions are analogous for *pnp* transistors), the total current traversing base is modeled by a current source given by:

$$i_T = i_F - i_R = I_S \left[\exp\left(\frac{v_{BE}}{V_T}\right) - \exp\left(\frac{v_{BC}}{V_T}\right) \right]$$

Diode currents correspond directly to the two components of base current.

$$i_B = \frac{I_S}{\beta_F} \left[\exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right] - \frac{I_S}{\beta_R} \left[\exp\left(\frac{v_{BC}}{V_T}\right) - 1 \right]$$





Lecture 10: BJT Physics

9




i-v Characteristics

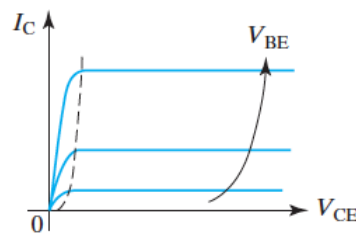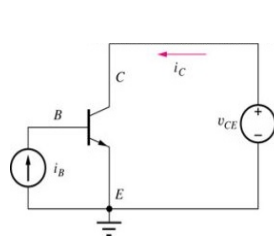

Collect current increases **exponentially** with V_{BE}

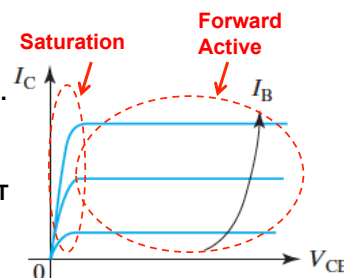- Flat part of the i-v curves is called “**forward active**” region.
- The non-flat part is called “**saturation**” region
 - Please note **Saturation** in BJT and MOSFET refers to opposite regions



Collect current increases **linearly** with I_B



Lecture 10: BJT Physics

10



Operation Regions of Bipolar Transistors

Base-Emitter Junction	Base-Collector Junction	
	Reverse Bias	Forward Bias
Forward Bias	Forward-Active Region (Good Amplifier)	Saturation Region (Closed Switch)
Reverse Bias	Cutoff Region (Open Switch)	Reverse-Active Region (Poor Amplifier)

Binary Logic States




Lecture 10: BJT Physics

11



Example 1

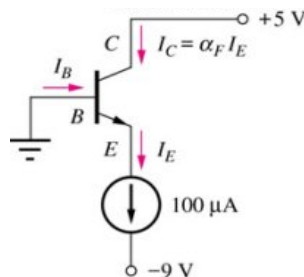- **Problem:** Estimate transistor terminal currents and base-emitter voltage
- **Given data:** $I_S = 10^{-16} \text{ A}$, $\alpha_F = 0.95$, $V_{BC} = V_B - V_C = -5 \text{ V}$, $I_E = 100 \mu\text{A}$
- **Assumption:** BJT in forward-active
- **Analysis:**



$$I_C = \alpha_F I_E = 0.95(100 \mu\text{A}) = 95 \mu\text{A}$$

$$\beta_F = \frac{\alpha_F}{1 - \alpha_F} = \frac{0.95}{1 - 0.95} = 19$$

$$I_B = \frac{I_C}{\beta_F} = \frac{95 \mu\text{A}}{19} = 5 \mu\text{A}$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.689 \text{ V}$$




Lecture 10: BJT Physics

12



Example 2

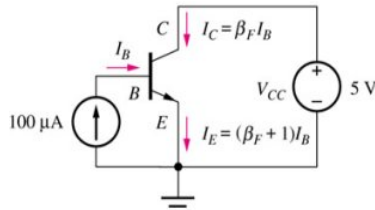- **Problem:** Estimate terminal currents and voltages
- **Given data:** $I_S = 10^{-16} \text{ A}$, $\alpha_F = 0.95$, $V_C = +5 \text{ V}$, $I_B = 100 \mu\text{A}$
- **Assumptions:** BJT in forward active
- **Analysis:**



$$\beta_F = \frac{\alpha_F}{1 - \alpha_F} = \frac{0.95}{1 - 0.95} = 19$$

$$I_C = \beta_F I_B = 19(100 \mu\text{A}) = 1.90 \text{ mA}$$


$$I_E = (\beta_F + 1) I_B = 20(100 \mu\text{A}) = 2.00 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.025 \text{ V} \ln\left(\frac{1.9 \text{ mA}}{0.1 \text{ fA}}\right) = 0.764 \text{ V}$$

$$V_{BC} = V_B - V_C = V_{BE} - V_C = 0.764 - 5 = -4.24 \text{ V}$$



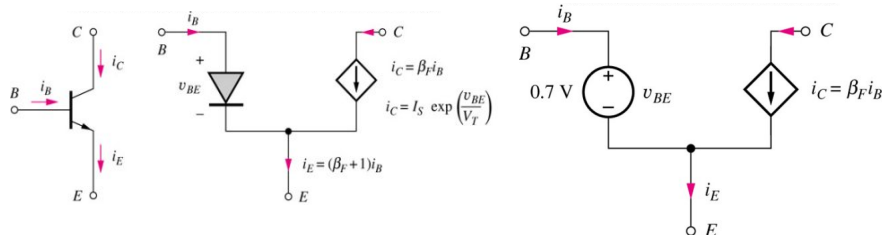Simplified Circuit Model Forward-Active Region





- Current in base-emitter diode is amplified by common-emitter current gain β_F and appears at collector; base and collector currents are exponentially related to base-emitter voltage.
- Base-emitter diode is replaced by constant voltage drop model ($V_{BE} = 0.7 \text{ V}$) since it is forward-biased in forward-active region.
- dc base and emitter voltages differ by 0.7-V diode voltage drop in forward-active region.



Simplified Forward-Active Region Model Example 3

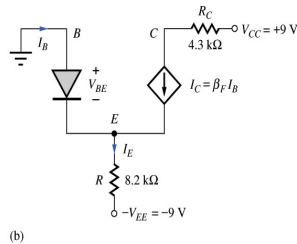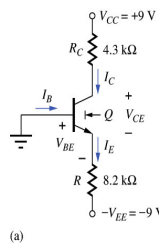- **Problem:** Find transistor Q-point
- **Given data:** $\beta_F = 50$, $\beta_R = 1$
- **Assumptions:** Forward-active region of operation, $V_{BE} = 0.7 \text{ V}$
- **Analysis:**



$$V_{BE} + 8200 I_E - V_{EE} = 0$$

$$\therefore I_E = \frac{9 - 0.7 \text{ V}}{8200 \text{ } \Omega} = 1.01 \text{ mA}$$

$$I_B = \frac{I_E}{\beta_F + 1} = \frac{1.01 \text{ mA}}{51} = 19.8 \text{ } \mu\text{A}$$

$$I_C = \beta_F I_B = 50(19.8 \text{ } \mu\text{A}) = 0.990 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C - (-V_{BE})$$

$$V_{CE} = 9 - 0.99 \text{ mA}(4.3 \text{ K}) + 0.7 = 5.44 \text{ V}$$

Forward-active region is correct.




Simplified Circuit Model Saturation Region

- In the saturation region, both junctions are forward-biased, and the transistor operates with a small voltage between collector and emitter. v_{CESAT} is the saturation voltage for the npn BJT.

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) - \frac{I_S}{\alpha_R} \exp\left(\frac{V_{BC}}{V_T}\right) \quad I_B = \frac{I_S}{\beta_F} \exp\left(\frac{V_{BE}}{V_T}\right) + \frac{I_S}{\beta_R} \exp\left(\frac{V_{BC}}{V_T}\right)$$

$$V_{CESAT} = V_{BE} - V_{BC} = V_T \ln \left[\left(\frac{1}{\alpha_R} \right) \frac{1 + \frac{I_C}{(\beta_R + 1) I_B}}{1 - \frac{I_C}{\beta_F I_B}} \right] \quad \text{for } I_B \geq \frac{I_C}{\beta_F}$$

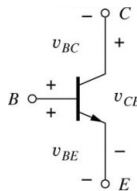No simplified expressions exist for terminal currents other than $i_C + i_B = i_E$.



Simplified Model

