

EE105 – Fall 2014

Microelectronic Devices and Circuits


Prof. Ming C. Wu

wu@eecs.berkeley.edu

511 Sutardja Dai Hall (SDH)



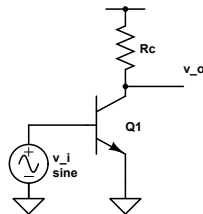Common-Emitter Amplifiers with Ideal Current Source Load



Voltage gain:


$$A_V = -g_m (R_C \parallel r_o) = -g_m R_C$$

$$A_V = -\frac{I_C}{V_T} R_C = -\frac{V_{RC}}{V_T}$$

Typical values:

$$I_C \sim 1\text{mA} \quad R_C \sim 5\text{k}\Omega$$

$$A_V \sim -200$$

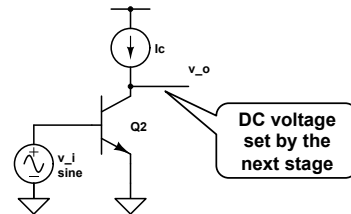

Voltage gain:

$$A_V = -g_m (\infty \parallel r_o) = -g_m r_o$$

$$A_V = -\frac{I_C}{V_T} \frac{V_A}{I_C} = -\frac{V_A}{V_T}$$

Typical values:

$$V_A = 100\text{V}$$


$$A_V \sim -4000$$



Simple Current Source – Current Mirror

Q₂ and Q₃ are matched (identical):

- Same I_S
- Same β

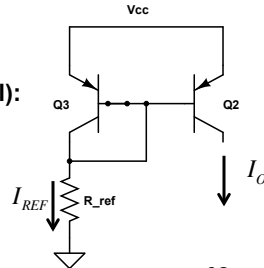

Since $I_O \approx I_{REF}$

this is called
"current mirror"

In this example,

$$I_{REF} = \frac{V_{CC} - V_{BE3}}{R_{REF}}$$

Note $V_{BE3} = V_{BE2}$

For simplicity, assume $V_A = \infty$

$$I_{C3} = I_S \exp\left(\frac{V_{BE3}}{V_T}\right) \quad I_{C2} = I_S \exp\left(\frac{V_{BE2}}{V_T}\right) = I_{C3}$$


$$I_{REF} = I_{C3} + I_{B3} + I_{B2} = I_{C2} + \frac{I_{C2}}{\beta} + \frac{I_{C2}}{\beta}$$

$$I_O = \frac{I_{REF}}{1 + 2/\beta} \approx I_{REF}$$



CE Amplifier with Current Mirror Bias

Q₂ and Q₃ form a current mirror pair

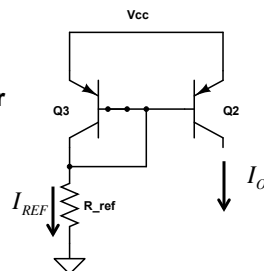

$$I_O = \frac{I_{REF}}{1 + 2/\beta} \approx I_{REF}$$

$$A_V = -g_{m1}(r_{o1} \parallel r_{o2})$$

Example:

$$I_{REF} = 1\text{mA}, \quad \beta_1 = \beta_2 = 100, \quad V_{A1} = V_{A2} = 100\text{V}$$

$$g_{m1} = 40\text{mS}$$


$$r_{o1} = r_{o2} = 100\text{V} / 1\text{mA} = 100\text{k}\Omega$$

$$A_V = -40\text{mS} \cdot 50\text{k}\Omega = -2000$$



Mirror with Multiple Current Sources

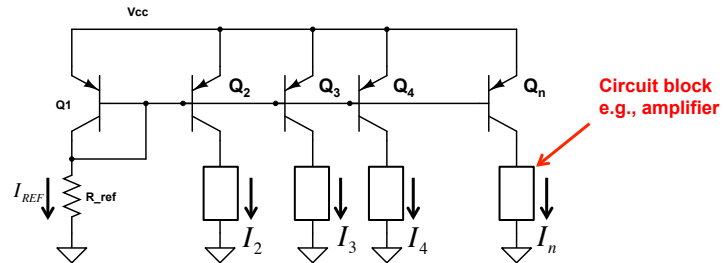One reference current can support multiple amplifiers:



For simplicity, assume $V_A = \infty$

All V_{BE} are equal

$$I_{C2} = I_{C3} = I_{C4} = \dots = I_{Cn}$$

$$I_{REF} = I_{C1} + I_{B1} + I_{B2} + \dots + I_{Bn}$$


$$I_i = \frac{I_{REF}}{1 + \frac{n}{\beta}}$$

When n is large, $\frac{n}{\beta}$ is not negligible



Mirror with Multiple Current Sources

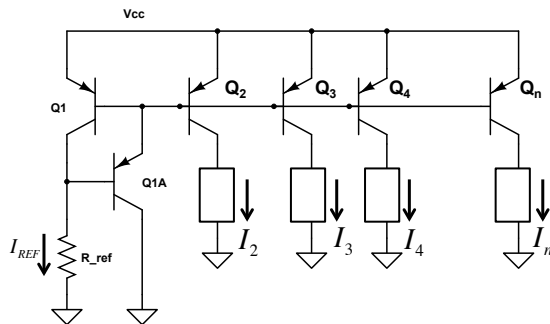Use a BJT to boost up supplies to multiple base currents:



$$V_A = \infty$$

$$I_{REF} = I_{C1} + I_{B1A} = I_{C1} + \frac{I_{E1A}}{1 + \beta}$$

$$= I_{C1} + \frac{I_{B2} + I_{B3} + \dots + I_{Bn}}{1 + \beta}$$


$$= I_{C1} + \frac{nI_B}{1 + \beta} = I_{C1} + \frac{I_{C1} / \beta}{1 + \beta}$$

$$I_i = I_{C1} = \frac{I_{REF}}{1 + \frac{n}{\beta(\beta + 1)}} \approx I_{REF}$$



Current Mirror with Different Currents

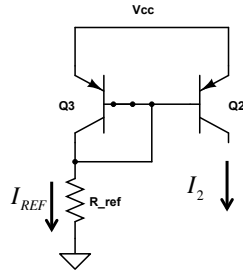Q₂ and Q₃ have same current gain, but different area.



$$I_{REF} = \frac{V_{CC} - V_{BE3}}{R_{REF}}$$

$$V_{BE3} = V_{BE2}$$

For simplicity, assume $V_A = \infty$

$$I_{C3} = I_{S3} \exp\left(\frac{V_{BE3}}{V_T}\right)$$

$$\text{Recall } I_S = \frac{qA_E D_n n_i^2}{W_B N_B} \propto A_E$$

$$I_{C2} = I_{S2} \exp\left(\frac{V_{BE2}}{V_T}\right) = \left(\frac{A_{E2}}{A_{E3}}\right) I_{C3}$$


$$I_{REF} = I_{C3} + I_{B3} + I_{B2} = I_{C3} + \frac{I_{C3}}{\beta} + \frac{I_{C2}}{\beta}$$

$$I_2 = \left(\frac{A_{E2}}{A_{E3}}\right) I_{C3} = \left(\frac{A_{E2}}{A_{E3}}\right) \frac{I_{REF}}{1 + 1/\beta + \eta/\beta} \approx \left(\frac{A_{E2}}{A_{E3}}\right) I_{REF}$$

$$\eta = \frac{A_{E2}}{A_{E3}}$$



Current Mirrors for PNP CE-Amplifiers

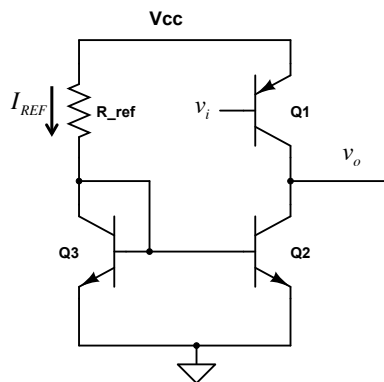

$$I_{REF} = \frac{V_{CC} - V_{BE3}}{R_{REF}}$$

$$A_V = -g_{m1}(r_{o1} \parallel r_{o2})$$

Example:

$$I_{REF} = 1\text{mA}, \beta_1 = \beta_2 = 100,$$

$$V_{A1} = V_{A2} = 100\text{V}$$


$$g_{m1} = 40\text{mS}$$

$$r_{o1} = r_{o2} = 100\text{V} / 1\text{mA} = 100\text{k}\Omega$$

$$A_V = -40\text{mS} \cdot 50\text{k}\Omega = -2000$$



MOS Current Mirrors dc Analysis

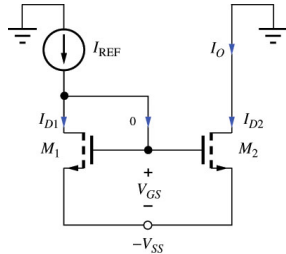

MOSFETs M_1 and M_2 are assumed to have identical V_{TN} , K_n' , I , and W/L ratios.

I_{REF} provides operating bias to mirror.

$$V_{DS1} = V_{GS1} = V_{GS2} = V_{GS}$$


$$V_{GS} = V_{TN} + \sqrt{\frac{2I_{REF}}{K_n(1 + \lambda V_{DS1})}}$$

$$I_O = I_{D2} = \frac{K_n}{2}(V_{GS} - V_{TN})^2$$

$$I_O = I_{REF}$$



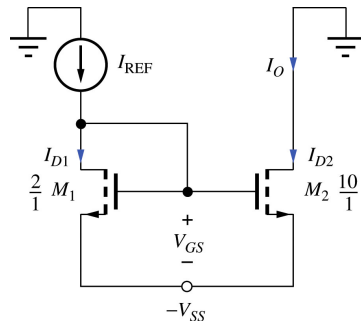MOS Current Mirrors Changing the Mirror Ratio



Mirror ratio can be changed by modifying W/L ratios of the two transistors forming the mirror.

In the given current mirror, $I_O = 5I_{REF}$.

For non-zero λ , the current ratio will vary slightly due to mismatch in V_{DS}

$$K_{n1} = K_n' \left(\frac{W}{L} \right)_1 \quad K_{n2} = K_n' \left(\frac{W}{L} \right)_2$$


$$I_O = I_{REF} \frac{K_{n2}(1 + \lambda V_{DS2})}{K_{n1}(1 + \lambda V_{DS1})}$$

For simplicity, $\lambda \approx 0$

$$I_O = I_{REF} \left(\frac{W/L}{W/L} \right)_2$$



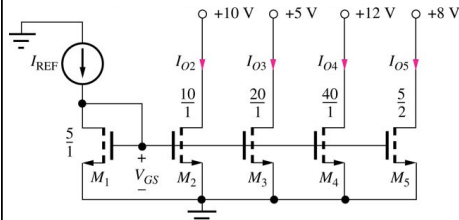
Current Mirrors with Multiple Current Sources



- Multiple sources can be operated from one reference transistor
- Reference current enters diode-connected transistor M1 establishing gate-source voltage to bias M2 through M5, each with a different W/L ratio.
- Absence of base current permits large numbers of MOSFETs to be driven by one reference transistor.




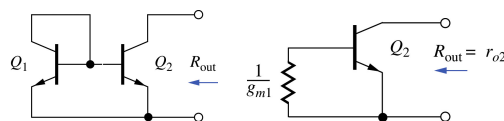Current Mirrors Input and Output Resistances



The input resistance of the current mirror is set by the diode connected transistors:
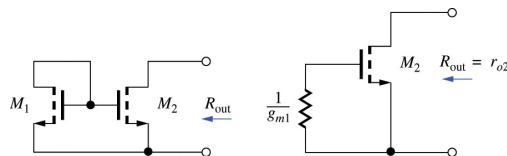
$$\therefore R_{in} \cong \frac{1}{g_{m1}}$$



The output resistance is equal to the output resistance of the Q_2 or M_2 :

$$\therefore R_{out} = r_{o2}$$

