

EE105 – Fall 2015 Microelectronic Devices and Circuits

Prof. Ming C. Wu

wu@eecs.berkeley.edu


511 Sutardja Dai Hall (SDH)



2-1



Amplifier Gain

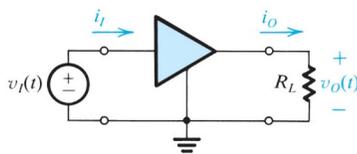


Voltage Gain: $A_v = \frac{v_o}{v_i}$

Current Gain: $A_i = \frac{i_o}{i_i}$

Power Gain: $A_p = \frac{\text{load power}}{\text{input power}} = \frac{v_o i_o}{v_i i_i}$

Note: $A_p = A_v A_i$

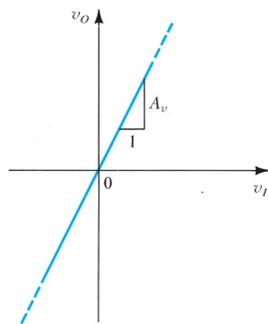

Note: A_v and A_i can be positive, negative, or even complex numbers. Negative gain means the output is 180° out of phase with input. However, power gain should always be a positive number.

Gain is usually expressed in Decibel (dB):

$$A_v(\text{dB}) = 10 \log |A_v|^2 = 20 \log |A_v|$$

$$A_i(\text{dB}) = 10 \log |A_i|^2 = 20 \log |A_i|$$


$$A_p(\text{dB}) = 10 \log |A_p|$$




2-2



Amplifier Power Supply and Dissipation

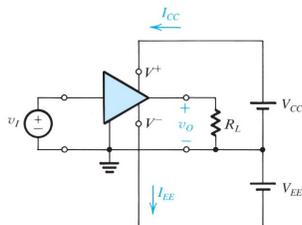

(a)

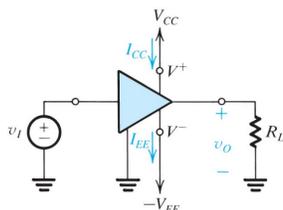

(b)

- Circuit needs dc power supplies (e.g., battery) to function.
- Typical power supplies are designated V_{CC} (more positive voltage supply) and $-V_{EE}$ (more negative supply).
- Total dc power dissipation of the amplifier

$$P_{dc} = V_{CC}I_{CC} + V_{EE}I_{EE}$$

- Power balance equation

$$P_{dc} + P_i = P_L + P_{dissipated}$$

P_i : power drawn from signal source

P_L : power delivered to the load (useful power)

$P_{dissipated}$: power dissipated in the amplifier circuit (not counting load)


- Amplifier power efficiency $\eta = \frac{P_L}{P_{dc}}$

Power efficiency is important for "power amplifiers"

such as output amplifiers for speakers or wireless transmitters.




Amplifier Saturation

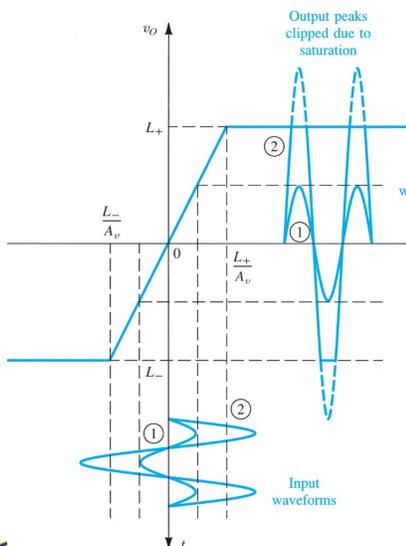

- **Amplifier transfer characteristics is linear only over a limited range of input and output voltages**
- **Beyond linear range, the output voltage (or current) waveforms saturates, resulting in distortions**
 - Lose fidelity in stereo
 - Cause interference in wireless system



Symbol Convention

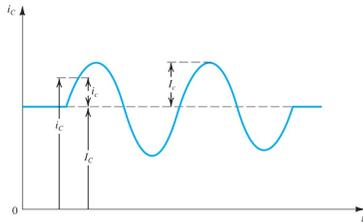

$$i_c(t) = I_C + i_c(t)$$

$i_c(t)$: total instantaneous current

I_C : dc current

$i_c(t)$: small signal current

Usually $i_c(t) = I_c \sin \omega t$

Please note case of the symbol:

lowercase-uppercase: total current

lowercase-lowercase: small signal ac component

uppercase-uppercase: dc component

uppercase-lowercase: amplitude of ac component

Similarly for voltage expressions.


These expressions are widely adopted, though occasionally you will find different convention. You should check carefully whenever you read a new book or paper.



2-5



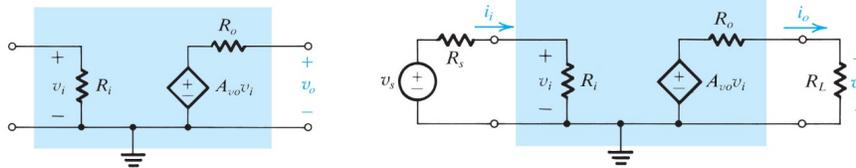Circuit Model of Voltage Amplifiers (Two-Port Model)



$$v_i = v_s \frac{R_i}{R_i + R_s}$$

$$v_o = A_{v0} v_i \frac{R_L}{R_L + R_o} = A_{v0} v_s \frac{R_i}{R_i + R_s} \frac{R_L}{R_L + R_o}$$

$$\text{Overall voltage gain: } A_v = \frac{v_o}{v_s} = A_{v0} \frac{R_i}{R_i + R_s} \frac{R_L}{R_L + R_o}$$

A_{v0} : open-circuit voltage gain (or voltage gain of "unloaded" amplifier)

R_i : input resistance of the amplifier

R_o : output resistance of the amplifier

R_s : source resistance


R_L : load resistance



2-6



Cascaded Amplifier

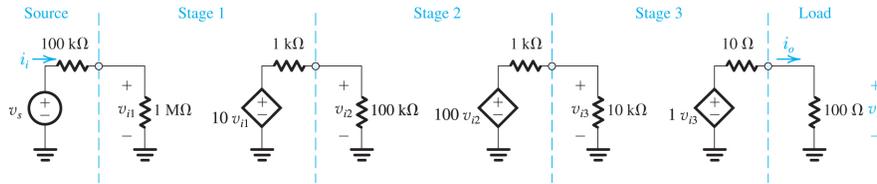

For most practical applications, multiple stages of amplifiers are cascaded to

- provide sufficient gain
- provide adequate input and output resistances

For example, in a voltage amplifier

- the input stage is designed to have high input impedance
- the output stage is designed to have low output impedance
- middle stage(s) provide the necessary gain



Amplifier Types

Table 1.1 The Four Amplifier Types


Type	Circuit Model	Gain Parameter	Ideal Characteristics
Voltage Amplifier		Open-Circuit Voltage Gain $A_{vo} \equiv \left. \frac{v_o}{v_i} \right _{i_o=0}$ (V/V)	$R_i = \infty$ $R_o = 0$
Current Amplifier		Short-Circuit Current Gain $A_{is} \equiv \left. \frac{i_o}{i_i} \right _{v_o=0}$ (A/A)	$R_i = 0$ $R_o = \infty$
Transconductance Amplifier		Short-Circuit Transconductance $G_m \equiv \left. \frac{i_o}{v_i} \right _{v_o=0}$ (A/V)	$R_i = \infty$ $R_o = \infty$
Transresistance Amplifier		Open-Circuit Transresistance $R_m \equiv \left. \frac{v_o}{i_i} \right _{v_o=0}$ (V/A)	$R_i = 0$ $R_o = 0$

Depending on the nature of the source signals and output loads, different types of amplifiers are needed

- Voltage amplifier
- Current amplifier
- Transconductance amp
 - Converts voltage to current
- Transimpedance amp
 - Converts current to voltage
- The 4 models here are interchangeable, though one is usually more convenient than others for analysis



Amplifier Frequency Response

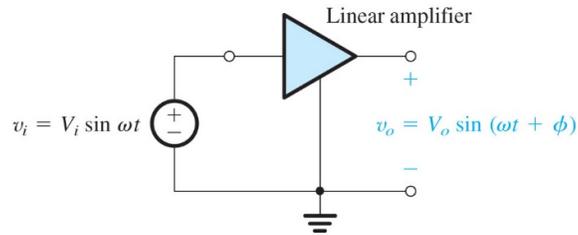

When a sinusoidal signal is applied to a linear circuit, the output is sinusoidal

- with the same frequency as the input
- but different amplitude and phase

Transfer function: $T(\omega) = \frac{V_o(\omega)}{V_i(\omega)}$

Amplitude response: $|T(\omega)| = \frac{V_o}{V_i}$


Phase response: $\angle T(\omega) = \phi$



2-9



Frequency Response

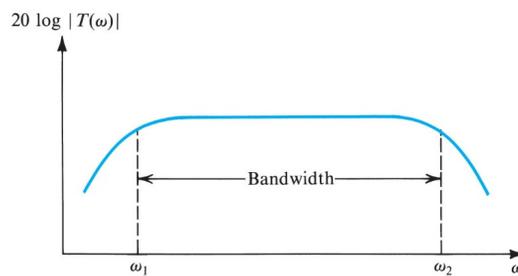


- **Log-log plot of the transfer function versus angular frequency, ω**
 - Vertical axis: $20 \log |T(\omega)|$
 - Horizontal axis: $10 \log \omega$
- **This is called Bode Plot**
- **Bandwidth**
 - Band of frequencies over which the gain response falls by 3dB



2-10



Frequency Response of Low-Pass Filters

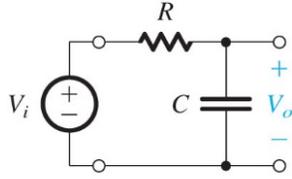

$$T(\omega) = \frac{1}{j\omega C} = \frac{1}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\omega / \omega_0}$$



$$\omega_0 = \frac{1}{RC}$$

$$|T(\omega)| = \frac{1}{\sqrt{1 + (\omega / \omega_0)^2}}$$

$$\angle T(\omega) = -\tan^{-1}(\omega / \omega_0)$$

$$\omega_{3dB} = \omega_0 \quad [\text{rad/sec}]$$

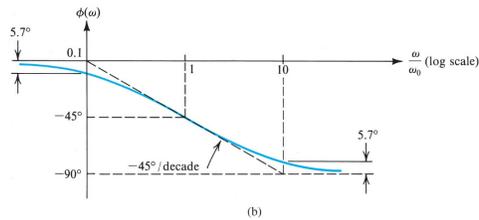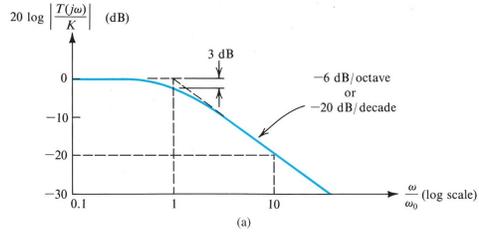
$$f_{3dB} = \frac{\omega_0}{2\pi} \quad [\text{Hz}]$$



2-11



Frequency Response of High-Pass Filters

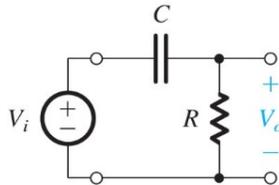

$$T(\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{1}{1 + \frac{1}{j\omega RC}} = \frac{1}{1 - j\omega_0 / \omega}$$



$$\omega_0 = \frac{1}{RC}$$

$$|T(\omega)| = \frac{1}{\sqrt{1 + (\omega_0 / \omega)^2}}$$

$$\angle T(\omega) = \tan^{-1}(\omega_0 / \omega)$$

$$\omega_{3dB} = \omega_0 \quad [\text{rad/sec}]$$

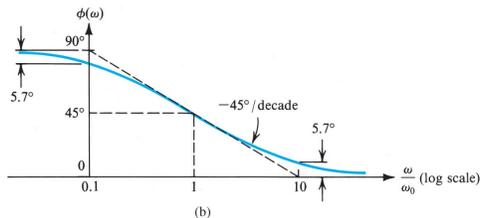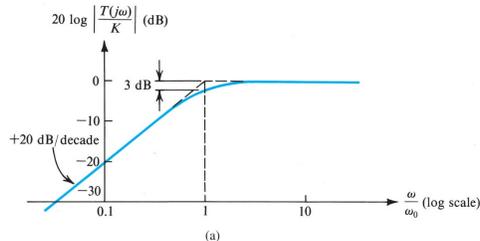
$$f_{3dB} = \frac{\omega_0}{2\pi} \quad [\text{Hz}]$$



2-12



Example: Amplifier Frequency Response

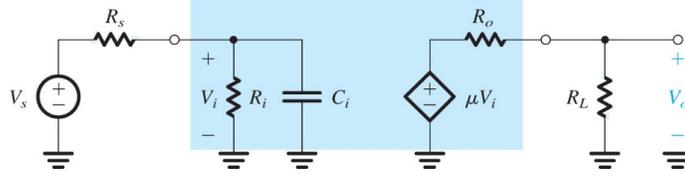

$$V_i = V_s \frac{Z_i}{R_s + Z_i}$$

$$Z_i = \frac{R_i / (j\omega C_i)}{R_i + 1 / (j\omega C_i)} = \frac{R_i}{1 + j\omega R_i C_i}$$

$$\frac{V_i}{V_s} = \frac{R_i}{R_s + R_i + j\omega R_i R_s C_i} = \frac{R_i}{R_s + R_i} \frac{1}{1 + j\omega R_i C_i}$$

$$R_{||} = R_s \parallel R_i = \frac{R_s R_i}{R_s + R_i}$$

$$T(\omega) = \frac{V_o}{V_s} = \frac{V_o}{V_i} \frac{V_i}{V_s}$$

$$= \mu \frac{R_L}{R_o + R_L} \frac{R_i}{R_s + R_i} \frac{1}{1 + j\omega R_i C_i}$$

$$= \frac{K}{1 + j(\omega / \omega_0)}$$

$$\omega_0 = \frac{1}{R_i C}$$


$$K = \mu \frac{R_L}{R_o + R_L} \frac{R_i}{R_s + R_i}$$



2-13



Typical Frequency Responses

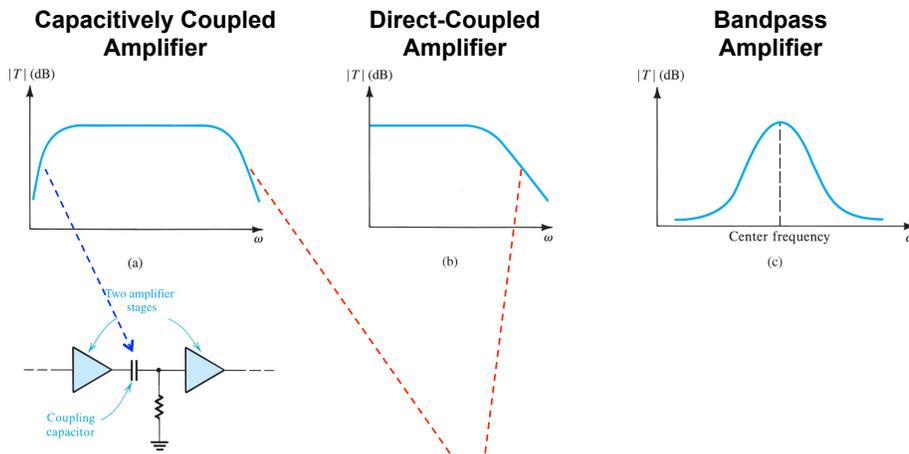

Low frequency roll-off due to coupling capacitor

High frequency cut-off due to intrinsic capacitors of the transistors



2-14

