

EE105 – Fall 2015

Microelectronic Devices and Circuits

Prof. Ming C. Wu

wu@eecs.berkeley.edu


511 Sutardja Dai Hall (SDH)



3-1




Ideal Op Amp

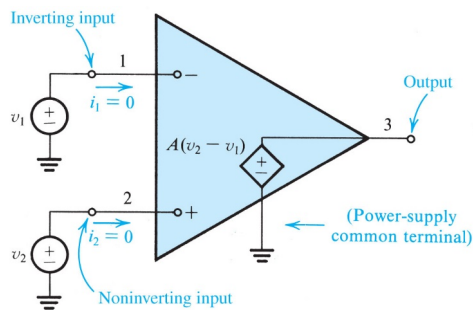

- Infinite input impedance
 - No current goes in
- Zero output impedance
- Infinite open-loop gain, A
 - How is this possible?
 - Use feedback to define circuit gain
- Infinite bandwidth
- Infinite common-mode rejection

Op-Amp with dc bias

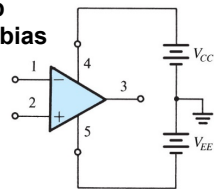


(b)

3-2



Inverting Amplifier


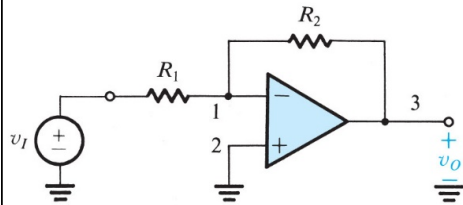


$$v_2 - v_1 = \frac{v_o}{A} = 0 \Rightarrow v_1 = v_2 = 0$$

$$i_1 = \frac{v_I}{R_1} = i_2$$

$$v_0 = 0 - i_2 R_2 = -\frac{R_2}{R_1} v_I$$

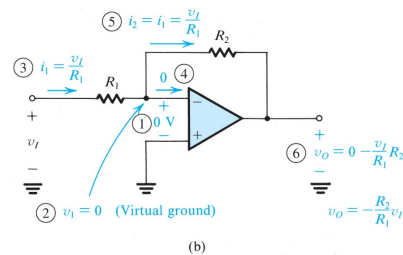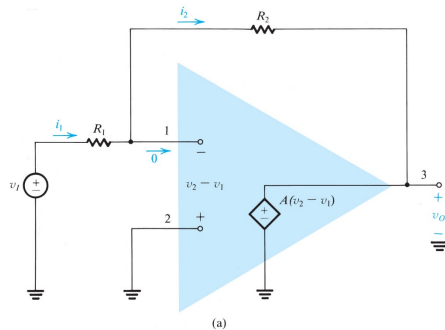
$$\text{Closed-loop gain: } G = \frac{v_o}{v_I} = -\frac{R_2}{R_1}$$



3-3



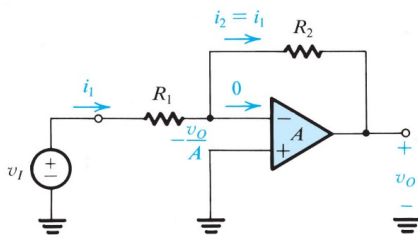Inverting Amplifier with Finite Open-Loop Gain



$$v_2 - v_1 = \frac{v_o}{A} \neq 0 \Rightarrow v_1 = -\frac{v_o}{A}$$

$$i_1 = \frac{v_I - v_1}{R_1} = i_2$$

$$v_0 = -\frac{v_o}{A} - i_2 R_2 = -\frac{v_o}{A} - \frac{R_2}{R_1} \left(v_I + \frac{v_o}{A} \right)$$

Closed-loop gain:

$$G = \frac{v_o}{v_I} = \left(-\frac{R_2}{R_1} \right) \frac{1}{1 + (1 + R_2/R_1)/A}$$

$$\text{As } A \rightarrow \infty, \quad G \rightarrow -\frac{R_2}{R_1}$$

$$\text{We should make } 1 + \frac{R_2}{R_1} \ll A$$

In other words, closed-loop gain should be much less than open-loop gain


- Define gain by resistor ratio, much more controllable than open-loop gain



3-4



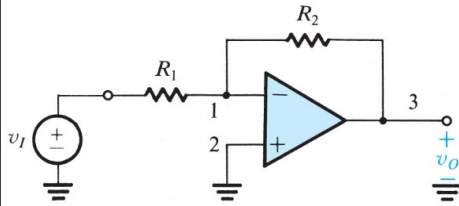Inverting Amplifier: Input and Output Resistances



Since $v_1 = 0$,
the input resistance is simply
 $R_i = R_1$

To find output resistance,

- Short-circuit the source,
- Apply a test source at the output,
and find the impedance


Since $v_o = A \cdot 0 = 0$
 $R_o = 0$



3-5



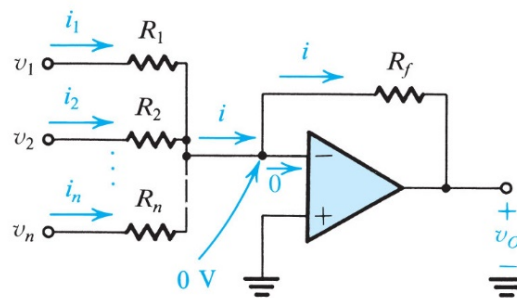Application of Inverting Amplifier: Weighted Summer




$$v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots + \frac{R_f}{R_n} v_n \right)$$



3-6



Non-Inverting Amplifier

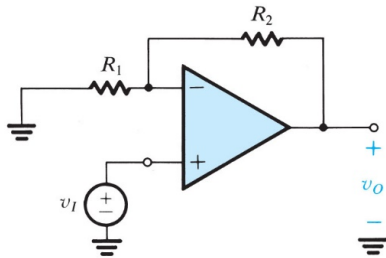


$$v_- = v_+ = v_I$$

$$i_1 = \frac{v_I}{R_1} = i_2$$

$$v_O = v_I + i_2 R_2 = \left(1 + \frac{R_2}{R_1}\right) v_I$$

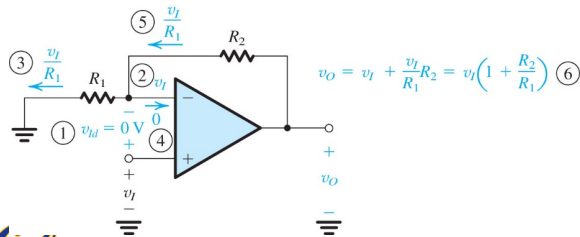
$$\text{Closed-loop gain: } G = \frac{v_O}{v_I} = 1 + \frac{R_2}{R_1}$$



3-7



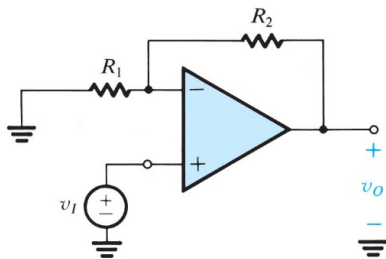Non-Inverting Amplifier: Effect of Finite Open-Loop Gain



Follow similar analysis of inverting amplifier, we can find the closed-loop gain with finite A :


$$G = \frac{v_O}{v_I} = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + \frac{1 + R_2/R_1}{A}}$$



3-8



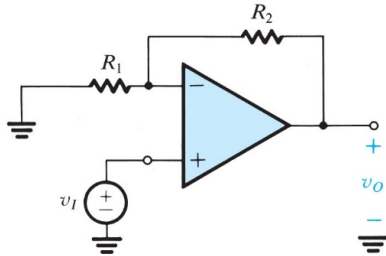Non-Inverting Amplifier: Input and Output Resistances



For ideal Op-Amp,
no current flows into the amplifier
 $R_i = \infty$



To find output resistance,
replace v_i with short circuit.
This is identical to the
case of inverting amplifier.
 $R_o = 0$



3-9



Voltage Follower: Unity Gain Amplifier

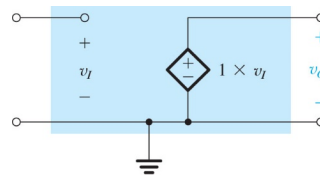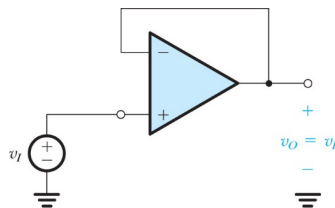

- **Unity voltage gain**
 - But large power gain
- **Purpose:**
 - **Provide impedance transformation:**
 - A buffer stage that present infinite input impedance to the source, and zero output impedance to the load
 - **Power amplifier**
 - Boost drive current



3-10

