

EE105 – Fall 2015

Microelectronic Devices and Circuits

Prof. Ming C. Wu
wu@eecs.berkeley.edu
511 Sutardja Dai Hall (SDH)



13-1



Purposes of Bias Circuit



- Provide a stable bias drain (collector) current
- Bias insensitive to variations in
 - Transistor parameters (β for BJT, V_t , k_n for MOS),
 - Temperature and other environmental changes
- Keep transistors in flat part of the I-V curves (Saturation for MOS, Active for BJT) for desired output swing



13-2



Example of Non-Ideal Bias

  



- Fixed v_{GS} from voltage divider
- Large variation in i_D due to device variations
- Large temperature dependence
 - μ_n and V_t are temperature sensitive



13-3



Adding Source Resistance R_S

  


- R_S provides negative feedback
 - If I_D increases, V_{GS} decreases \rightarrow reduce I_D
 - If I_D decreases, V_{GS} increases \rightarrow increase I_D
- Stabilize I_D w.r.t. device and temperature variations




13-4




Practical Implementations

 

Single Power Supply

 

Dual Power Supplies

 


Drain-to-Gate Feedback



13-5



 Coupling Capacitor to Separate AC Signal from DC Bias



- Coupling capacitor is DC -open and AC-short
- Prevent signal source to change bias condition
- The coupling capacitor creates a lower bound of operating frequency




13-6



Bias Design Example

 Goal: design bias for $I_D = 0.5 \text{ mA}$.
MOS has $V_t = 1 \text{ V}$ and $k_n = 1 \text{ mA/V}^2$



General rule of thumb:

Equal (1/3 each) voltage drop across R_D , R_S , and V_{DS}

$$\text{Choose } R_D = \frac{15\text{V} - 10\text{V}}{0.5 \text{ mA}} = 10 \text{ k}\Omega$$

$$\text{Choose } R_S = \frac{5\text{V} - 0\text{V}}{0.5 \text{ mA}} = 10 \text{ k}\Omega$$

Determine V_{GS} :

$$0.5 \text{ mA} = \frac{1}{2} k_n (V_{GS} - 1)^2 \Rightarrow V_{GS} = 2\text{V}$$

$$V_G = V_{GS} + 5\text{V} = 7\text{V}$$

We can choose any combination of voltage divider, R_{G1} and R_{G2} , that gives $V_G = 7\text{V}$.

Remember $R_{G1} \parallel R_{G2}$ becomes R_m


So use large R_{G1} and R_{G2} , in the $\text{M}\Omega$ range.



13-7



Non-Ideal Biasing Schemes for BJT

 

Since $i_C = I_S e^{\frac{v_{BE}}{V_T}}$ depends exponentially on v_{BE} , small variation in v_{BE} leads to large change in I_C

$$I_C = \beta \left(\frac{V_{CC} - 0.7}{R_B} \right)$$



is sensitive to variation in β



13-8



Good (Stable) Bias Circuits for BJT

  

Similar to MOSFET bias, but must consider finite base current:
First, find Thevenin equivalent circuit of bias circuit:

$$V_{BB} = V_{CC} \left(\frac{R_2}{R_1 + R_2} \right)$$

$$R_B = R_1 \parallel R_2$$

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{\beta + 1}}$$

Choose $V_{BB} \gg V_{BE}$ and $R_E \gg \frac{R_B}{\beta + 1}$

I_E is insensitive to variation in β and V_{BE}




13-9



Design Example of BJT Bias

 Goal: design bias circuit for $I_E = 1 \text{ mA}$ with $V_{CC} = 12 \text{ V}$ and $\beta = 100$



General rule of thumb:

Choose $V_{BB} = \frac{1}{3} V_{CC} = \frac{12}{3} = 4 \text{ V}$

$V_E \approx V_{BB} - 0.7 = 3.3 \text{ V} \Rightarrow R_E = \frac{V_E}{I_E} = \frac{3.3}{1 \text{ mA}} = 3.3 \text{ k}\Omega$

Choose $V_C = \frac{2}{3} V_{CC} = 8 \text{ V}$, $R_C = \frac{12 - 8}{1 \text{ mA}} = 4 \text{ k}\Omega$

Choose bias current through R_1, R_2 to be $10I_B$

$R_1 + R_2 = \frac{12}{0.1 \text{ mA}} = 120 \text{ k}\Omega$

$R_1 = 2R_2 \Rightarrow R_1 = 80 \text{ k}\Omega, R_2 = 40 \text{ k}\Omega$

Check resulting I_E :

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + \frac{R_B}{\beta + 1}} = \frac{4 - 0.7}{3.3 + \frac{40 \parallel 80}{101}} = 0.93 \text{ mA}$$

Adjust R_E : $I_E = 1 \text{ mA}$ when $R_E = 3 \text{ k}\Omega$



13-10

