

EE105 – Fall 2015 Microelectronic Devices and Circuits

Prof. Ming C. Wu

wu@eecs.berkeley.edu

511 Sutardja Dai Hall (SDH)



14-1




CS Amplifier with Bias Circuit

Both coupling and bypass capacitors are DC-open and AC-short

Capacitively Coupled Amplifier

DC:

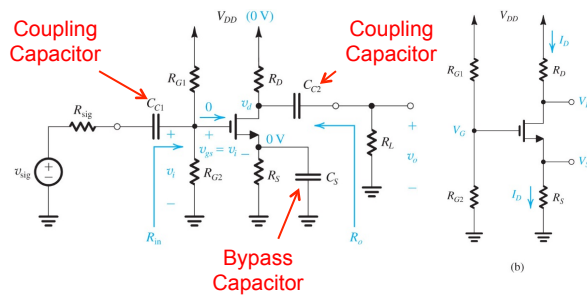


$$R_{in} = R_{G1} \parallel R_{G2}$$

$$R_o = R_D \parallel r_o$$

$$G_v = -\frac{R_{in}}{R_{sig} + R_{in}} g_m (R_o \parallel R_L)$$

AC:

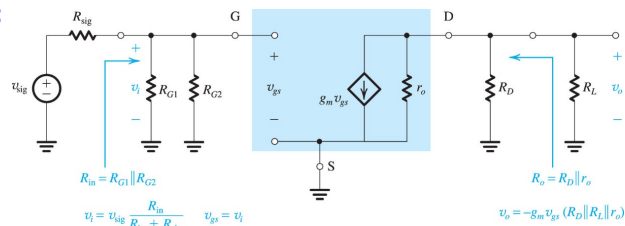


14-2



CE Amplifier with Bias Circuit

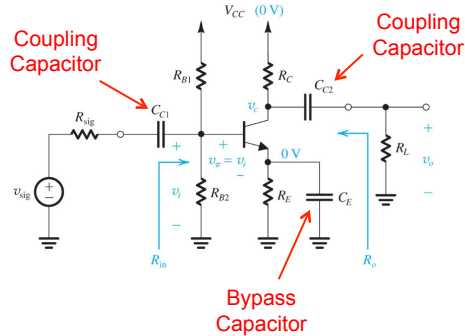
Both coupling and bypass capacitors are DC-open and AC-short



$$R_{in} = R_{B1} \parallel R_{B2} \parallel r_{\pi}$$

$$R_o = R_C \parallel r_o$$

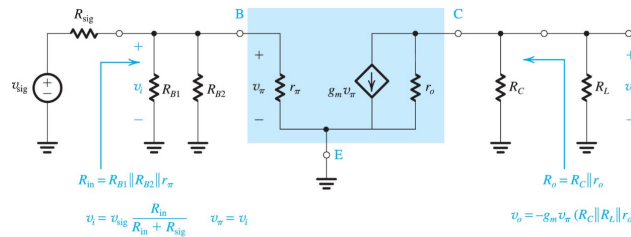
$$G_v = -\frac{R_{in}}{R_{sig} + R_{in}} g_m (R_o \parallel R_L)$$



14-3



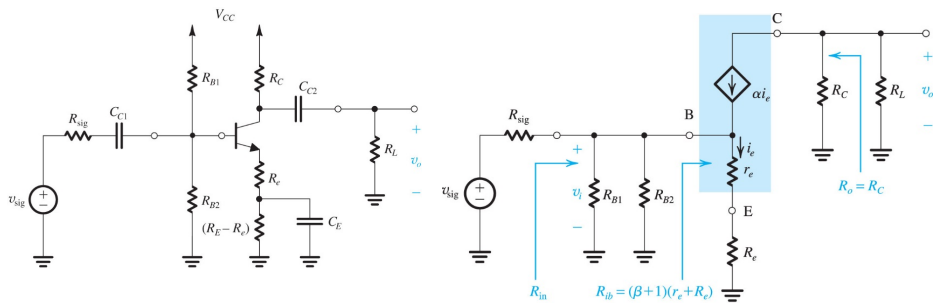Emitter-Degenerated CE Amplifier with Bias Circuit



$$R_{in} = R_{B1} \parallel R_{B2} \parallel \left[(1 + \beta) \left(\frac{1}{g_m} + R_e \right) \right]$$

$$R_o = R_C$$


$$G_v = \frac{R_{in}}{R_{sig} + R_{in}} \left(-\alpha \frac{R_C \parallel R_L}{\frac{1}{g_m} + R_e} \right)$$



14-4



CB Amplifier with Bias Circuit

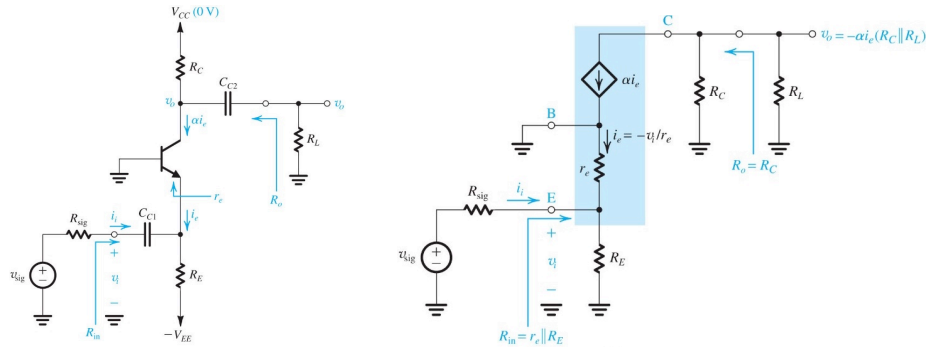

$$R_{in} = \frac{1}{g_m} \parallel R_E \approx \frac{1}{g_m}$$

$$R_o = R_C$$


$$G_v = \frac{R_{in}}{R_{sig} + R_{in}} \left(\frac{R_C \parallel R_L}{\frac{1}{g_m}} \right) = \frac{R_{in}}{R_{sig} + R_{in}} g_m (R_C \parallel R_L)$$



14-5



Emitter Follower with Bias Circuit

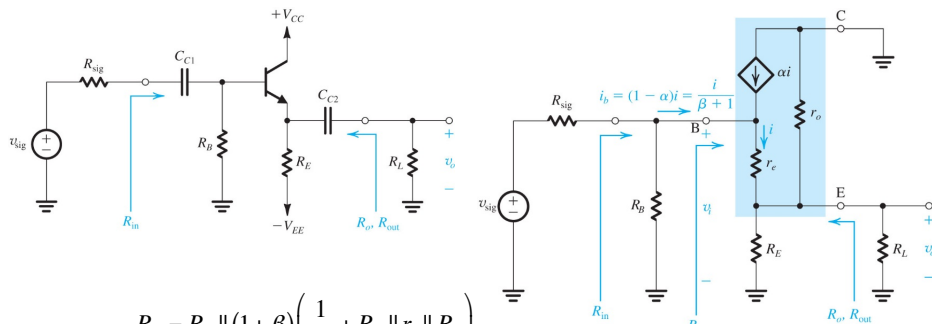

$$R_{in} = R_B \parallel (1 + \beta) \left(\frac{1}{g_m} + R_E \parallel r_o \parallel R_L \right)$$

$$R_o = r_o \parallel R_E \parallel \left(\frac{1}{g_m} + \frac{R_B \parallel R_{sig}}{1 + \beta} \right)$$

$$G_v = \frac{R_{in}}{R_{sig} + R_{in}} \left(\frac{r_o \parallel R_E \parallel R_L}{\frac{1}{g_m} + r_o \parallel R_E \parallel R_L} \right)$$



14-6



Typical Frequency Response of Capacitively Coupled CE Amplifier

