

# EE105 – Fall 2015 Microelectronic Devices and Circuits



Prof. Ming C. Wu  
wu@eecs.berkeley.edu  
511 Sutardja Dai Hall (SDH)



16-1


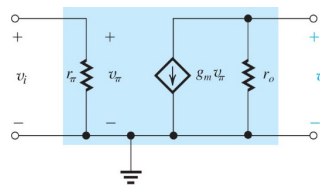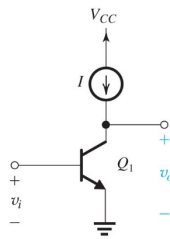
## Basic BJT Gain Cells with Ideal Current Source Load



$$\begin{aligned} R_{in} &= r_{\pi} \\ R_o &= r_o \\ A_{vo} &= -g_m r_o \end{aligned}$$

$$g_m = \frac{I_C}{V_T}, \quad r_o = \frac{V_A}{I_C}$$

$$A_{vo} = -\frac{V_A}{V_T}$$

In modern IC,  $V_A$  ranges from 5 to 35V

$|A_{vo}| \sim 200$  to 1400 V/V

In discrete BJT,  $V_A$  ranges from 100 to 130V


$|A_{vo}|$  up to 5000 V/V



16-2


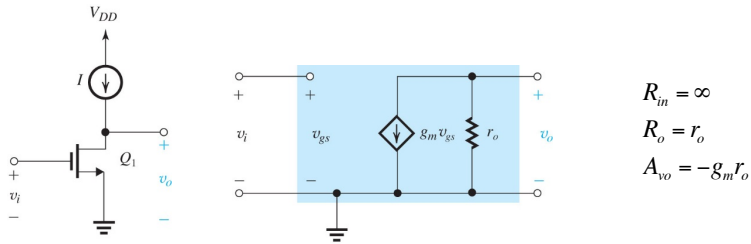
## Basic Gain Cells with Ideal Current Source Load



$$R_{in} = \infty$$

$$R_o = r_o$$

$$A_{vo} = -g_m r_o$$

$$g_m = \frac{2I_D}{V_{OV}} = \sqrt{2\mu_n C_{ox} (W/L) I_D}$$

$$r_o = \frac{V_A}{I_D}$$

$$|A_{vo}| = \frac{2V_A}{V_{OV}}$$

$V_{OV} \sim 0.15$  to  $0.3$  V  $\Rightarrow$  MOSFET gain is about 5x lower than BJT


Note: Early voltage in MOSFET is proportional to channel length,  $V_A = V'_A L$



16-3


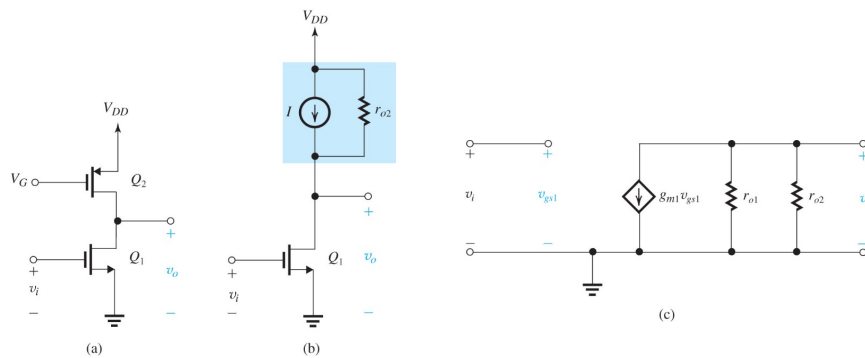
## Output Resistance of Current Source Load



Active load behaves like current source with finite output resistance,  $r_{o2}$



$$A_v = -g_{m1} (r_{o1} \parallel r_{o2})$$



16-4


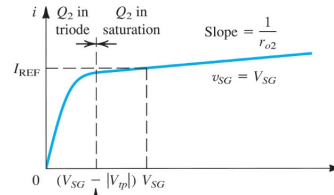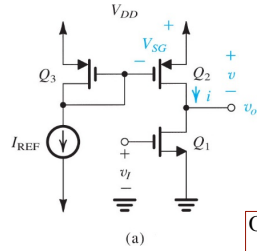
# Graphical Solution of Voltage Transfer Curve



Output Swing:  
 $V_{OV1} \leq v_o \leq V_{DD} - |V_{OV2}|$

Slope =  $\frac{\Delta v_o}{\Delta v_i} = \text{voltage gain}$   
 $= A_v = -g_{m1} (r_{o1} \parallel r_{o2})$

