

EE105 – Fall 2015



Microelectronic Devices and Circuits

Prof. Ming C. Wu

wu@eecs.berkeley.edu

511 Sutardja Dai Hall (SDH)

How To Increase Voltage Gain?

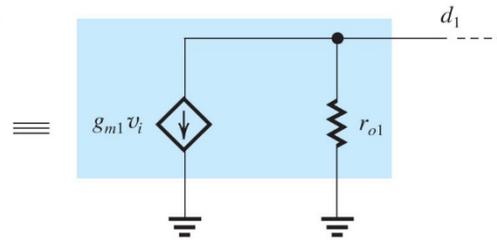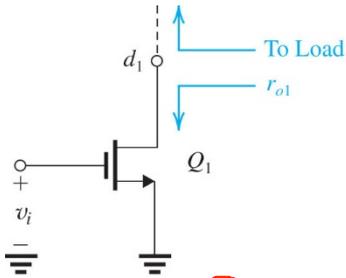



(a)

Voltage gain

$$|A_v| = g_{m1} (r_{o1} \parallel R_L) \leq \underline{g_{m1} r_{o1}}$$

limited by r_{o1}

∞

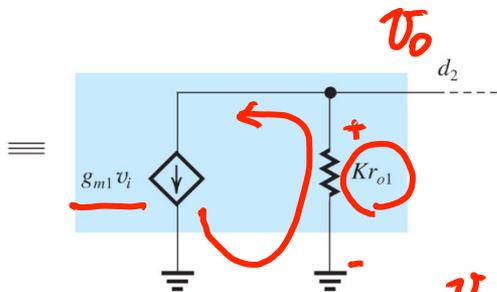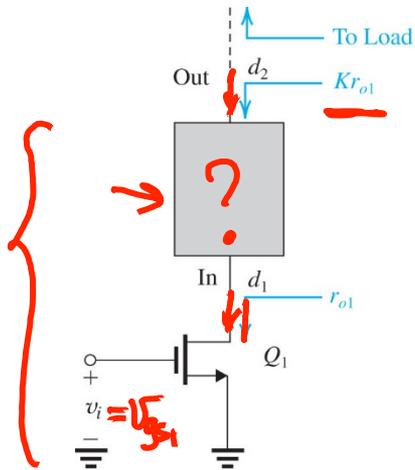

(b)



If we can boost up r_{o1} by a factor of K

$$|A_{v,max}| = g_{m1} K r_{o1}$$

$$v_o = -g_{m1} v_i K r_{o1}$$

$$A_v = \frac{v_o}{v_i} = -g_{m1} K r_{o1}$$

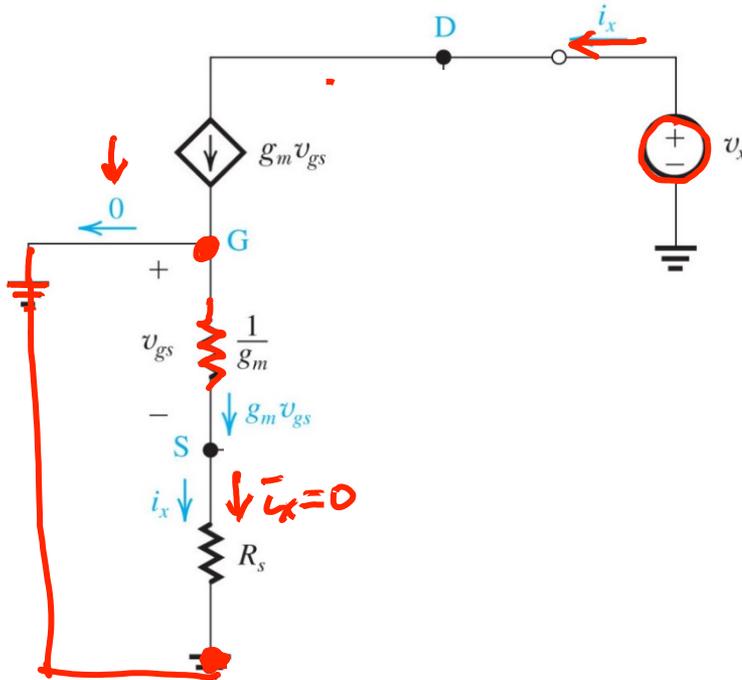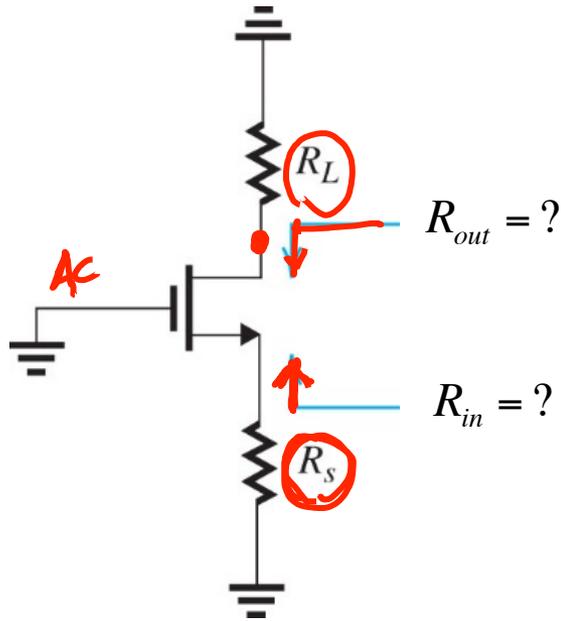Common Gate Amplifier is an Impedance Transformer




Using T-model

If we don't consider r_o :


$i_x = 0$ since G is grounded

$$R_{out} = \frac{v_x}{i_x} = \infty$$


To find R_{out} we have to include r_o

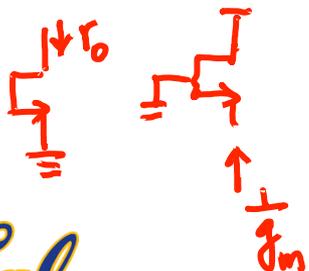

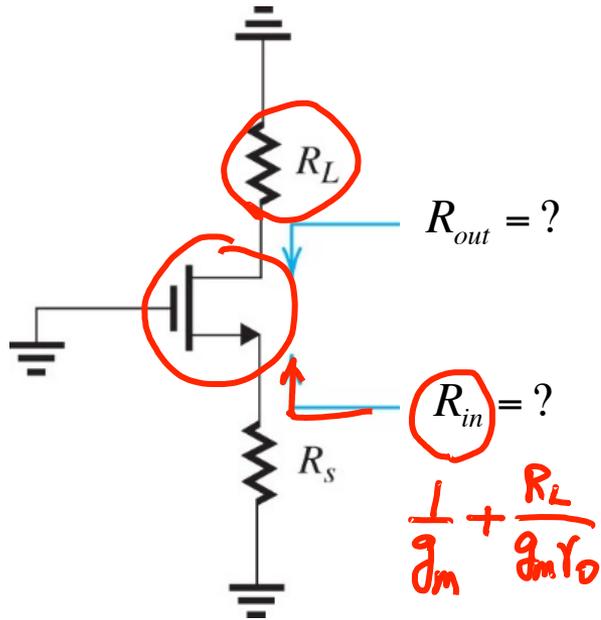Common Gate Amplifier is an Impedance Transformer



$$\frac{1}{g_m} + \frac{R_L}{g_m r_o}$$

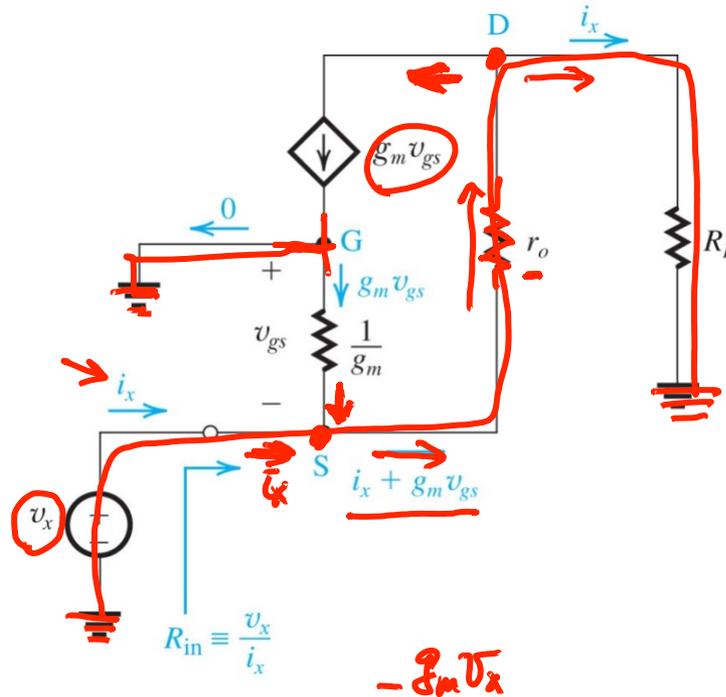

$$\text{KVL: } v_x = (i_x + g_m v_{gs})r_o + i_x R_L$$


$$v_{gs} = 0 - v_s = -v_x$$

$$(1 + g_m r_o)v_x = (r_o + R_L)i_x$$

$$R_{in} = \frac{v_x}{i_x} = \frac{r_o + R_L}{1 + g_m r_o} \approx \frac{1}{g_m} + \frac{R_L}{g_m r_o}$$

$$g_m r_o \gg 1$$

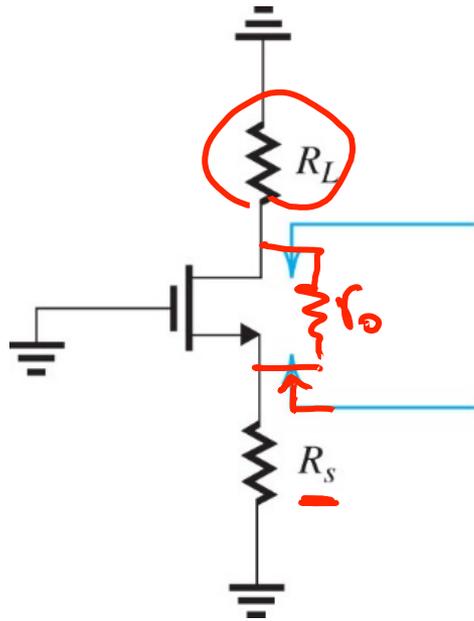Impedance Transformation of Common Gate Amplifier



$$R_{\text{out}} = r_o + R_s + g_m r_o R_s$$

$$\approx r_o + (g_m r_o) R_s$$

$$R_{\text{in}} = \frac{r_o + R_L}{1 + g_m r_o}$$


$$\approx \frac{1}{g_m} + \frac{R_L}{g_m r_o}$$

Impedance transformation:

Look into Drain : R_s amplified by $(g_m r_o)$

Look into Source : R_L reduced by $(g_m r_o)$

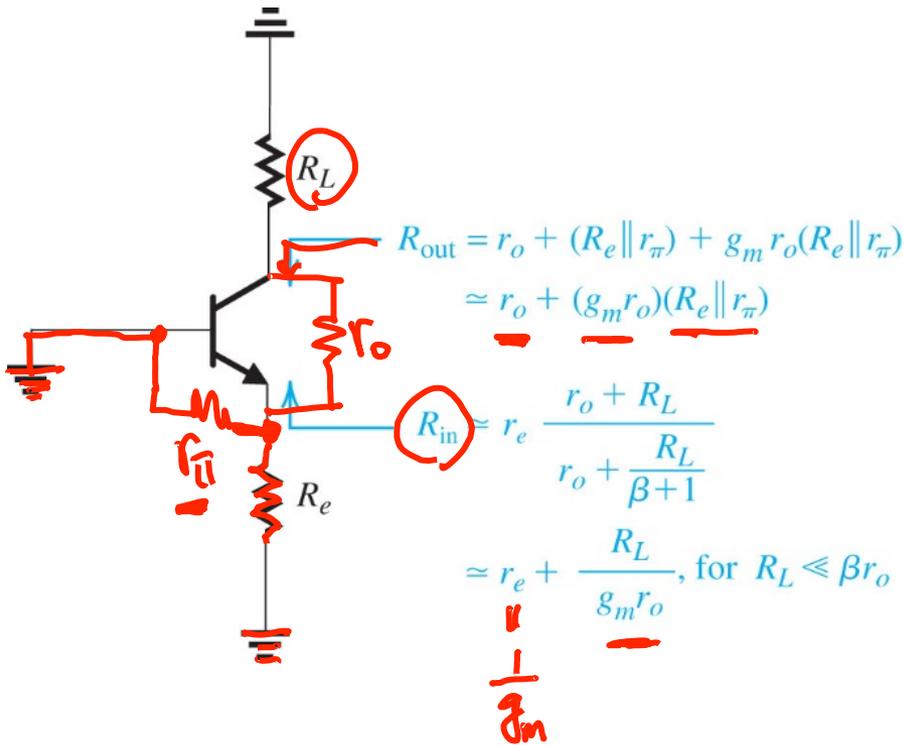Impedance Transformation of Common Base Amplifier




Similar impedance transformation in Common-Base BJT:

Look into Collector : $R_e \parallel r_{\pi}$ amplified by $(g_m r_o)$



Look into Source : R_L reduced by $(g_m r_o)$

Note R_s in MOS is replaced by $R_e \parallel r_{\pi}$ in BJT

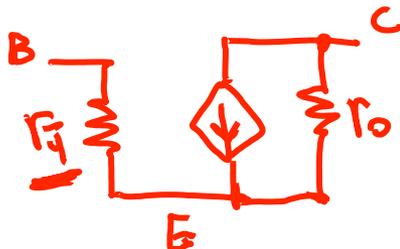Note: for $\beta = \infty$, these formulas reduce to those for the MOSFET



MOS Cascode Amplifier

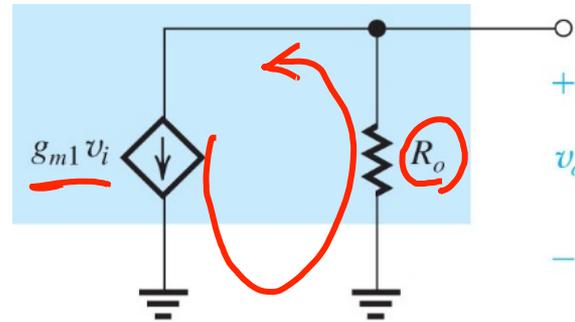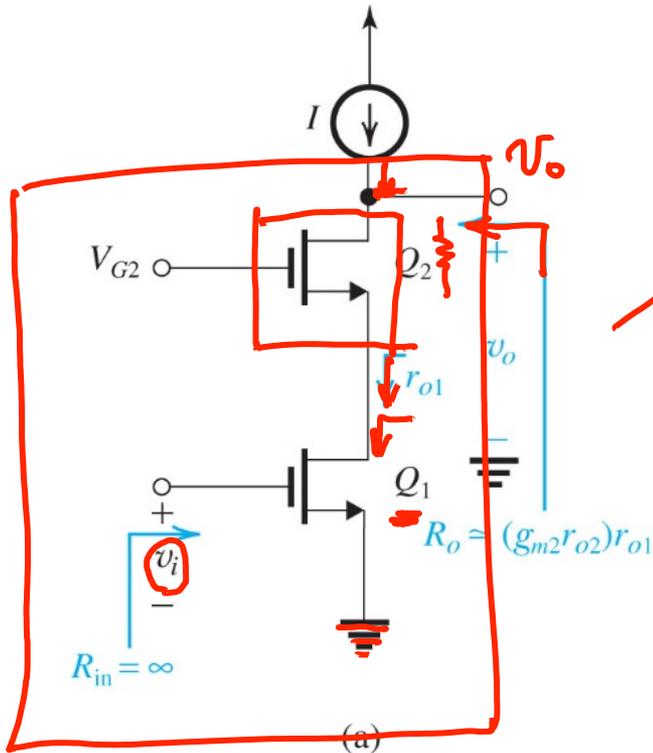

$$R_o = r_{o2} + \overbrace{(g_{m2}r_{o2})r_{o1}}^K \approx \overbrace{(g_{m2}r_{o2})r_{o1}}^{\sim 100}$$



$$A_{vo} = -g_{m1}R_o = -g_{m1}(g_{m2}r_{o2})r_{o1}$$

$$A_{vo} = -\underbrace{(g_{m1}r_{o1})}_{\sim 100} \underbrace{(g_{m2}r_{o2})}_{\sim 100}$$

Voltage gain is much higher than single-stage common source (CS) amplifier.

The gain of cascode is almost the square of that of CS

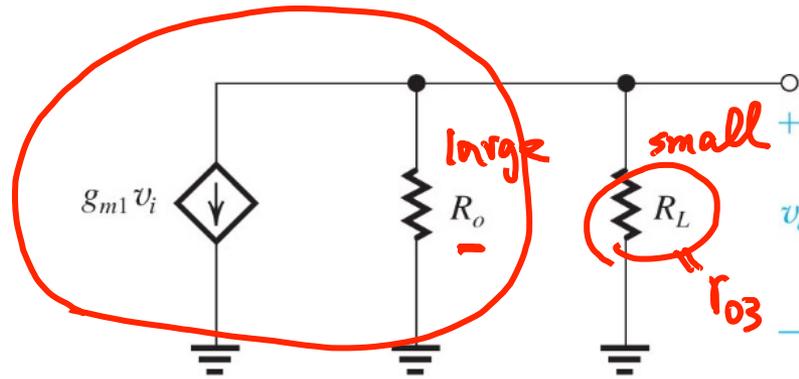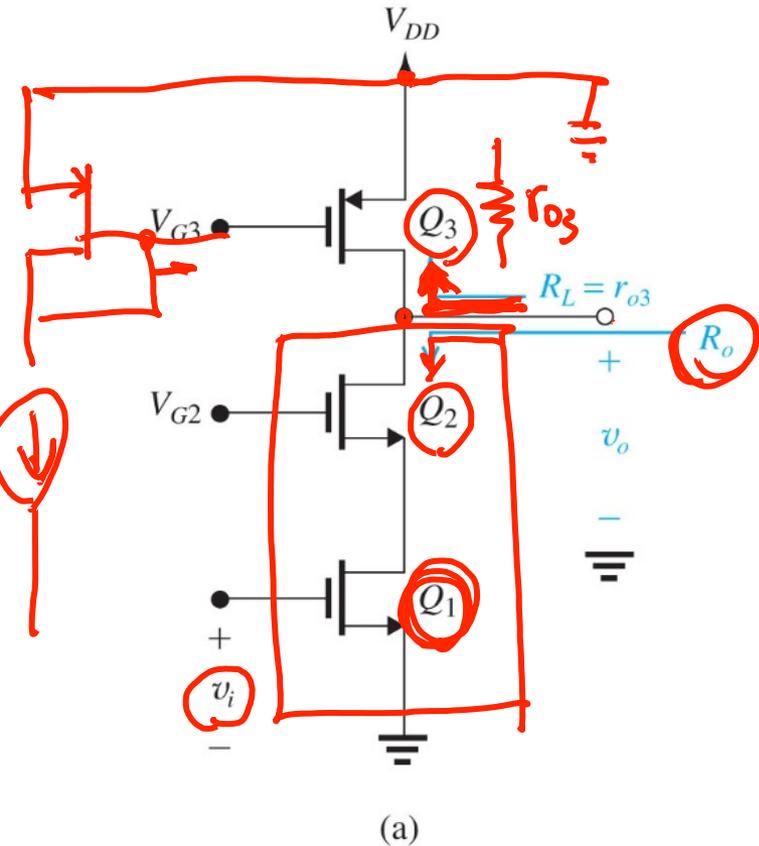Cascode Amplifier with Simple Active Load



$$A_v = -g_{m1}(R_o \parallel R_L)$$

$$R_o \approx (g_{m2}r_{o2})r_{o1}$$

$$R_L = r_{o3} \ll R_o$$



$$A_v = -g_{m1}r_{o3}$$

Similar gain as CS amplifier.

No gain boosting.

$$R_o = r_{o1} \cdot 100 \gg r_{o3} \parallel R_L$$

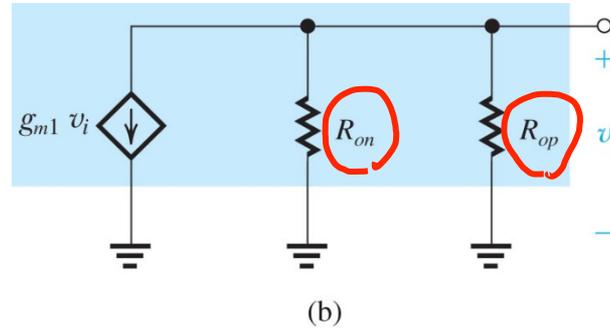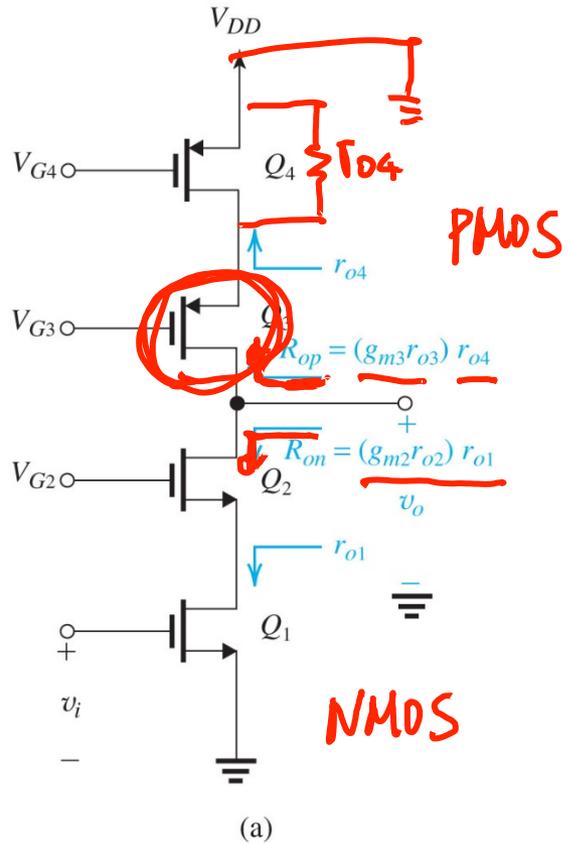Cascode Amplifier with Cascode Current-Source Load



$$A_v = -g_{m1} (R_{on} \parallel R_{op})$$

$$R_{on} \approx (g_{m2} r_{o2}) r_{o1} > \frac{1}{2}$$

$$R_{op} \approx (g_{m3} r_{o3}) r_{o4}$$


If all transistors are similar :

$$A_v = -\frac{1}{2} (g_m r_o)^2$$


--> High gain!

Thank of Cascode as Multistage Amplifier with CS followed by CG

CS + CG

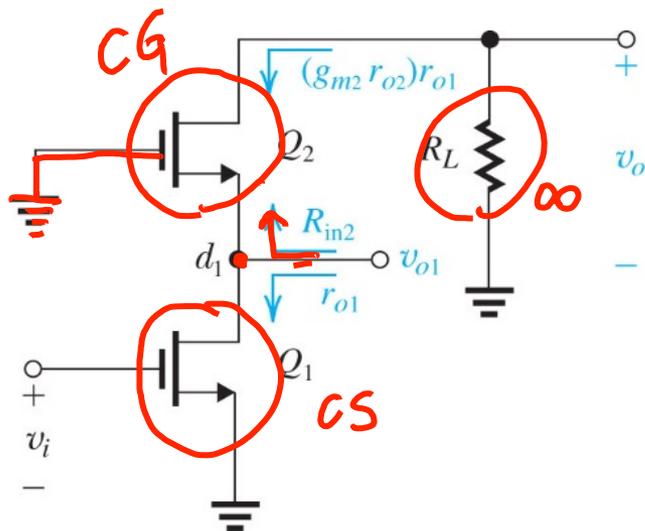

(a)

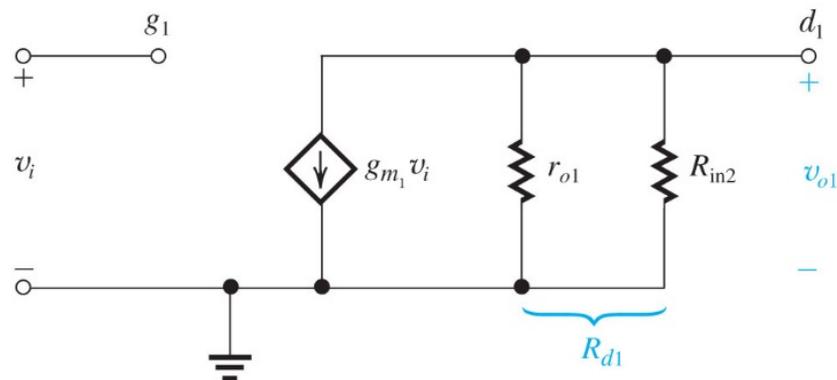

First stage: common source

$$A_{v1} = -g_{m1}(r_{o1} \parallel R_{in2}) = -g_{m1}r_{o1}$$

$$R_{in2} = \frac{R_L}{g_{m2}r_{o2}} + \frac{1}{g_{m2}} = \infty$$

Second stage: common gate

$$A_{v2} = g_{m2}r_{o2}$$


$$A_v = A_{v1}A_{v2}$$

For ideal current source load $R_L = \infty$

$$A_v = (-g_{m1}r_{o1})(g_{m2}r_{o2})$$

Folded Cascode

CS + CG
NMOS PMOS

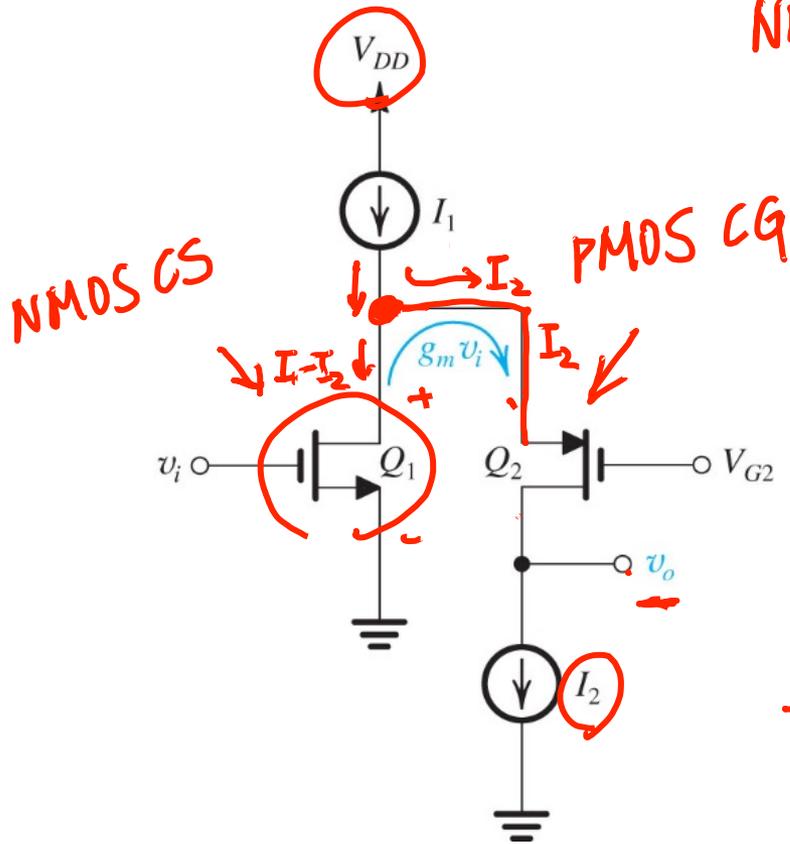


"Folding" the CG stage using PMOS.


Q_1 is biased with $I_1 - I_2$

Q_2 is biased with I_2

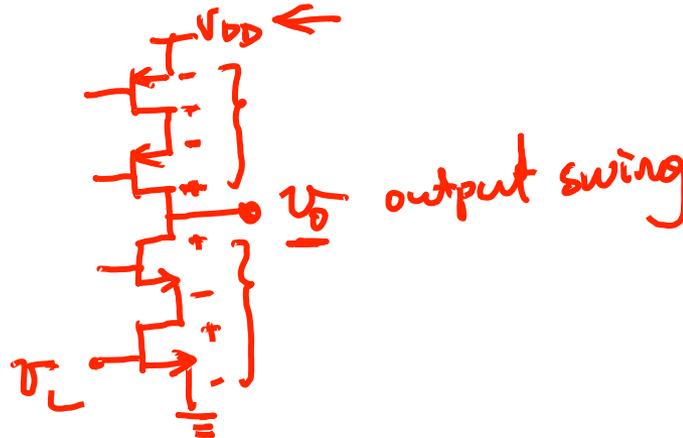Folded cascode avoids stacking too many transistors vertically, which will be difficult for low power supply voltage V_{DD}




Useful Transistor Pairings

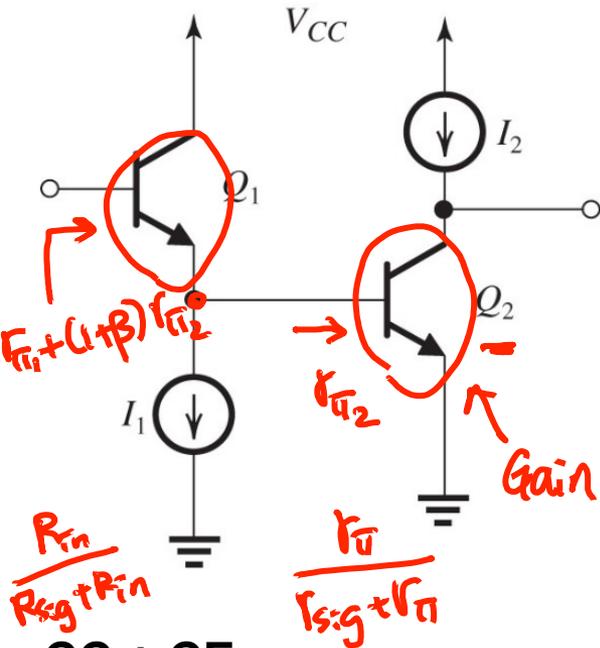


CC + CE

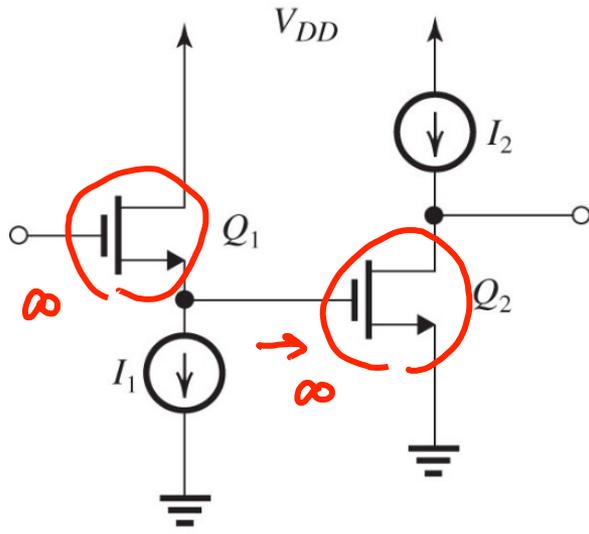- High input resistance
- Much wider bandwidth than single CE amplifier (To be discussed later)



CD + CS



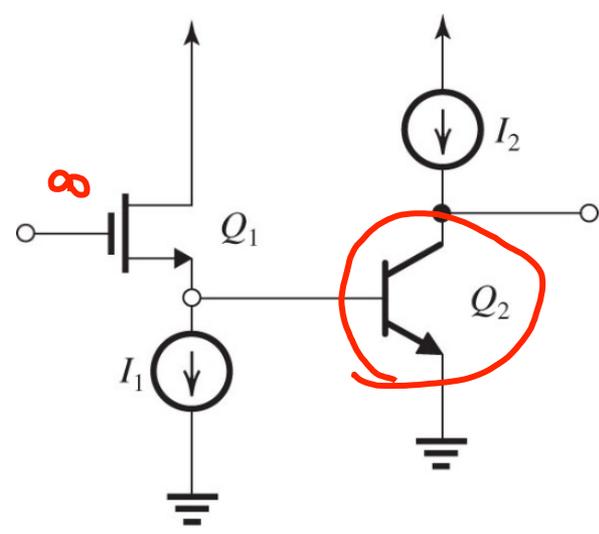
- Main benefit is wider bandwidth than single CE amplifier



CD + CE (BiCMOS technology,

- or BJT+CMOS)
- Similar to MOS version but BJT has higher g_m

Darlington Pair

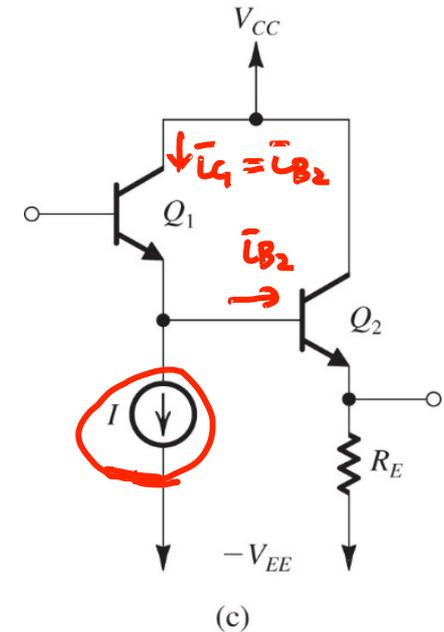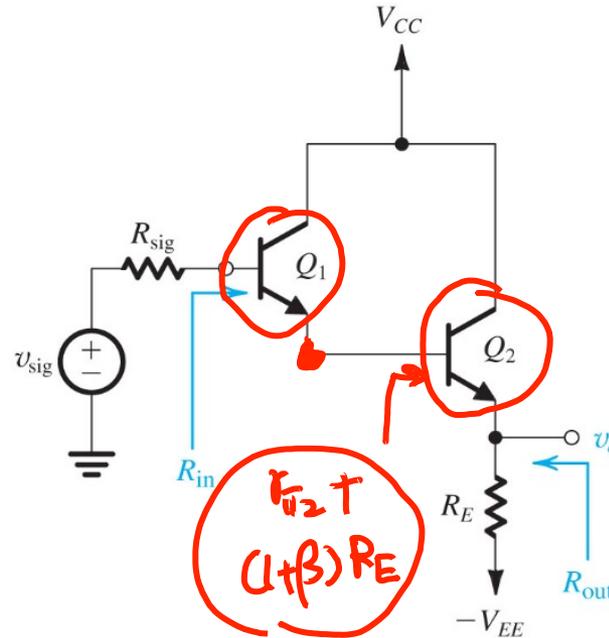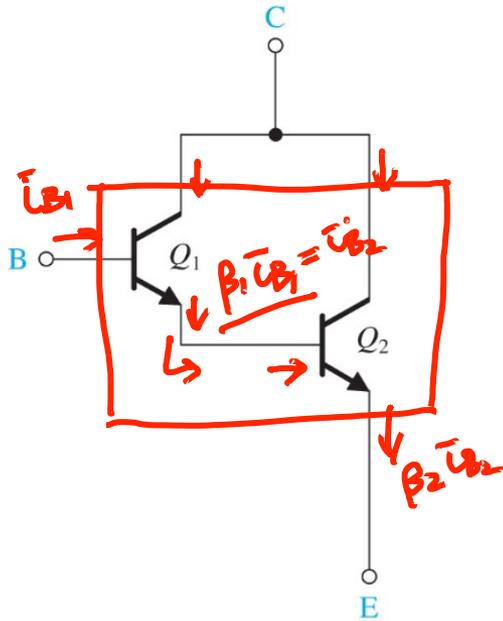

Darlington pair:
 • Composite BJT
 with $\beta = \beta_1 \beta_2$

$$\begin{aligned} \bar{I}_{C2} &= \beta_2 \bar{I}_{B2} \\ &= \beta_2 \beta_1 \bar{I}_{B1} \\ &= \beta \bar{I}_{B1} \end{aligned}$$

CC+CC: high performance source follower *emitter*

$$R_{in} = r_{\pi 1} + (\beta_1 + 1) [r_{\pi 2} + (\beta_2 + 1) R_E]$$

$$> \beta_1 \beta_2 R_E$$

CC+CC: high performance source follower with separate current bias for Q1 \rightarrow high β_1 *emitter*