

# EE105 – Fall 2015

## Microelectronic Devices and Circuits

Prof. Ming C. Wu

wu@eecs.berkeley.edu


511 Sutardja Dai Hall (SDH)



20-1




## Two-Stage CMOS Op-Amp Circuit

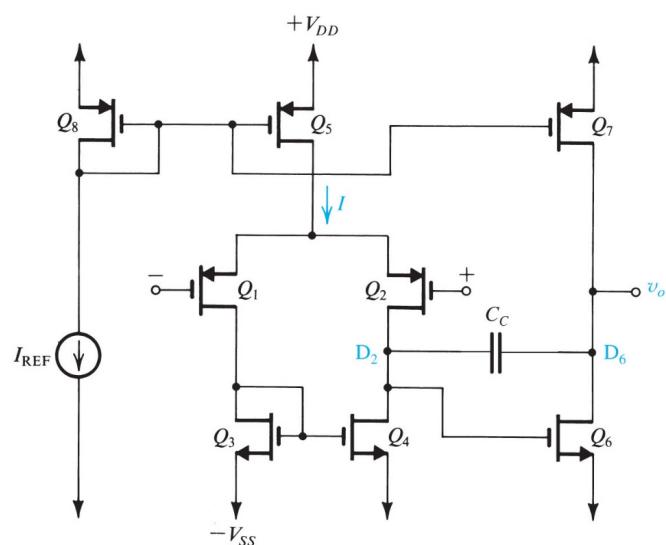


20-2



## Two-Stage CMOS Op-Amp Circuit

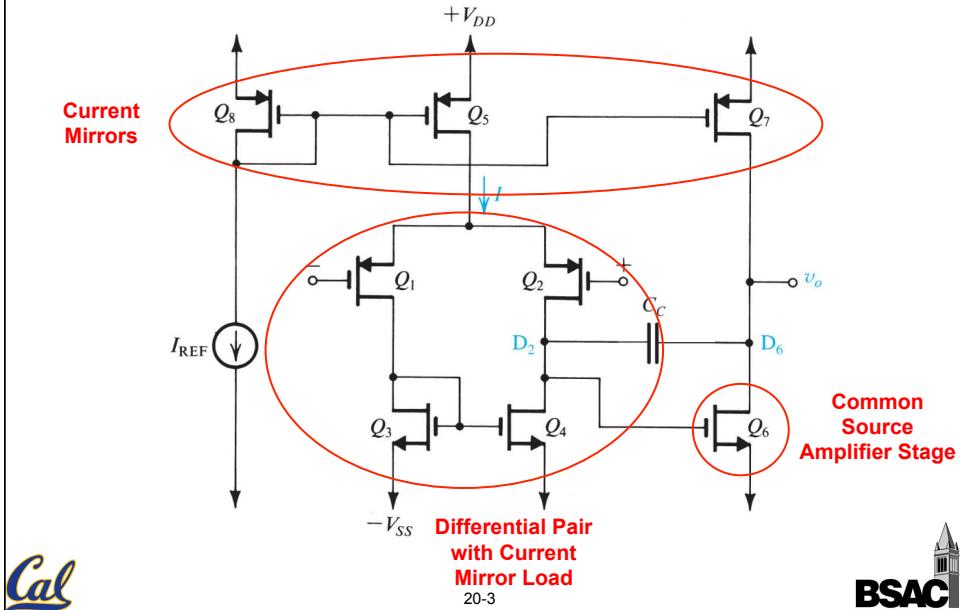

## Two-Stage CMOS Op-Amp Circuit

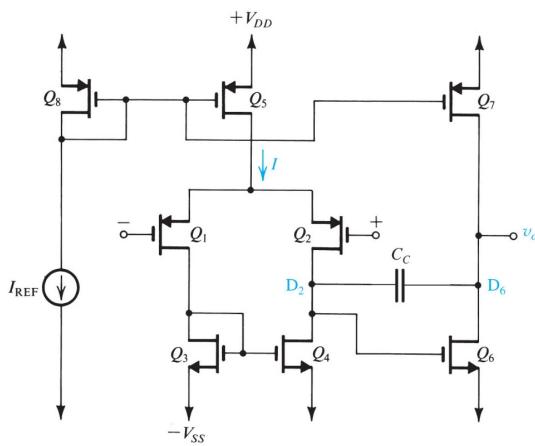

Voltage gain of the first stage

( $Q_1, Q_2$ ): Differential input, single-ended output:

$$A_1 = -g_{m1} (r_{o2} \parallel r_{o4})$$

Voltage gain of the 2nd stage


( $Q_6$ ): Common source with current source load:

$$A_2 = -g_{m6} (r_{o6} \parallel r_{o7})$$

Total gain

$$A_o = A_1 A_2$$

## Example:

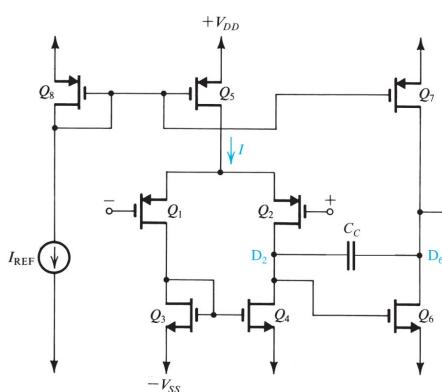

	Q1	Q2	Q3	Q4
W/L in um	20/0.8	20/0.8	5/0.8	5/0.8
Q5				

	Q6	Q7	Q8
W/L in um	40/0.8	10/0.8	4/0.8
Q5			

$I_{REF} = 90 \mu A$ ,  $V_{tn} = 0.7V$ ,  $V_{tp} = -0.8V$   
 $\mu_n C_{ox} = 160 \mu A/V^2$ ,  $\mu_p C_{ox} = 40 \mu A/V^2$   
 $|V_A| = 10V$  for all devices  
 $V_{DD} = V_{SS} = 2.5V$


Find  $I_D$ ,  $|V_{ov1}|$ ,  $|V_{gs1}|$ ,  $g_m$ ,  $r_o$  for all Q's,  
 voltage gain,  
 input common mode range,  
 output voltage range.

*Cal*

20-5



## Solution: DC Parameters

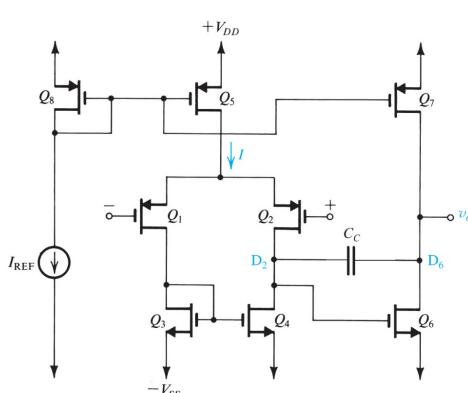


$$\begin{aligned}
 I_{REF} &= 90 \mu A \\
 I_{D5} &= \frac{(W/L)_5}{(W/L)_8} = 90 \mu A \\
 I_{D7} &= \frac{(W/L)_7}{(W/L)_8} = 90 \mu A \\
 I_{D1} &= I_{D2} = I_{D3} = I_{D4} = \frac{I_{D5}}{2} = 45 \mu A \\
 I_{Di} &= \frac{1}{2} \mu_i C_{ox} \left( \frac{W}{L} \right) |V_{ov}|^2 \\
 |V_{ov1}| &= |V_{ov2}| = |V_{ov3}| = |V_{ov4}| = 0.3 \\
 |V_{ov5}| &= |V_{ov6}| = |V_{ov7}| = |V_{ov8}| = 0.3 \\
 |V_{GS}| &= |V_{ov}| + |V_t| \\
 \text{NMOS : } |V_{GS}| &= 0.3 + 0.7 = 1.0V \\
 \text{PMOS : } |V_{GS}| &= 0.3 + 0.8 = 1.1V
 \end{aligned}$$

*Cal*

20-6



## Solution: AC Parameters

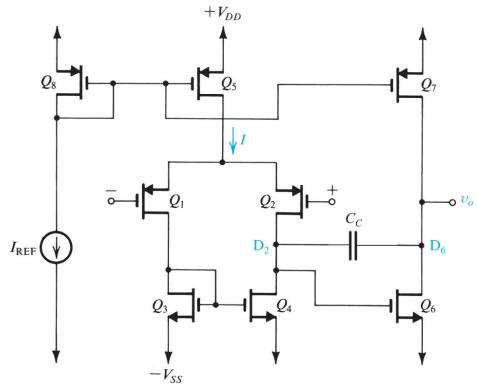

$$g_m = \frac{2I_D}{|V_{OV}|}$$

$$g_{m1-4} = 2 \times 45\mu A / 0.3V = 0.3mA / V$$

$$g_{m5-8} = 2 \times 90\mu A / 0.3V = 0.6mA / V$$

$$r_o = \frac{|V_A|}{I_D}$$

$$r_{o1-4} = \frac{10V}{45\mu A} = 222k\Omega$$

$$r_{o5-8} = \frac{10V}{90\mu A} = 111k\Omega$$

$$A_1 = -g_{m1}(r_{o2} \parallel r_{o4}) \\ = -0.3 \times 222 / 2 = -33.3V / V$$

$$A_2 = -g_{m6}(r_{o6} \parallel r_{o7}) \\ = -0.6 \times 111 / 2 = -33.3V / V$$


$$A_o = A_1 A_2 = 1109V / V \\ = 20 \log(1109) = 61dB$$

*Cal*

20-7



## Solution: Input Common-Mode Ranges

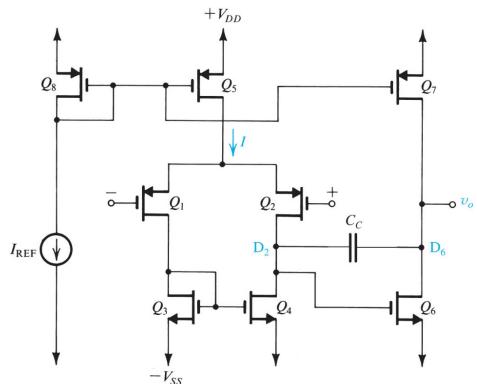

Input common-mode voltage range:

Maximum:  $Q_5$  near edge of saturation  
 $|V_{DS5}| = |V_{OV5}| = 0.3V$

$$v_{icm\max} = 2.5 - |V_{OV5}| - |V_{GS5}| \\ = 2.5 - 0.3 - 1.1 = 1.1V$$

Minimum:  $Q_1$  near edge of saturation

$$v_{D1} = -V_{SS} + V_{GS3} = -2.5 + 1 = -1.5V$$

$$|v_{DS1}| = |v_{GS1}| - |v_{tp}|$$

$$-v_{DS1} = -v_{GS1} - 0.8$$

$$-v_{D1} = -v_{G1} - 0.8$$


$$v_{icm\min} = v_{G1} = v_{D1} - 0.8 = -2.3V$$

*Cal*

20-8



## Solution: Output Ranges

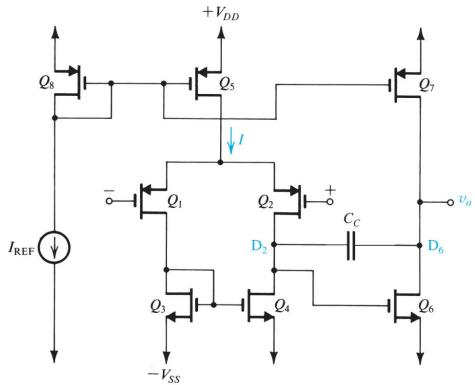

Output voltage range:

Maximum:  $Q_7$  near edge of saturation

$$|V_{OV7}| = 0.3V$$

Minimum:  $Q_6$  near edge of saturation

$$v_{o\max} = 2.5 - |V_{OV7}| = 2.2V$$


$$v_{o\min} = -V_{SS} + |V_{OV6}| = -2.5 + 0.3 = -2.2V$$

*Cal*

20-9



## A Four-Stage Bipolar Op-Amp

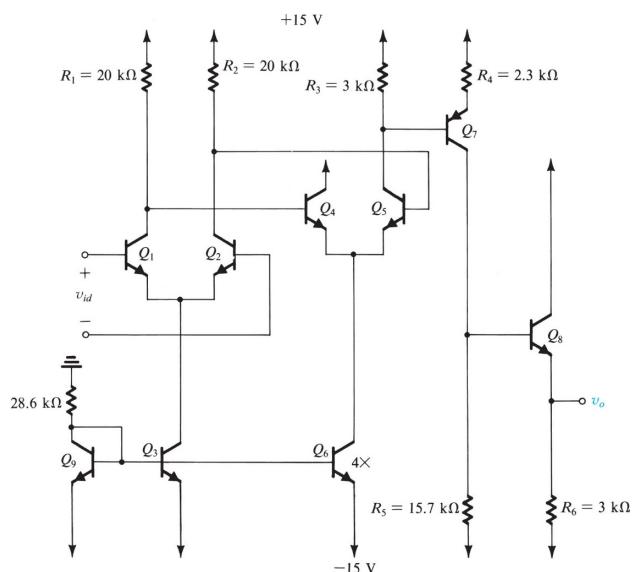


*Cal*

20-10



## A Four-Stage Bipolar Op-Amp

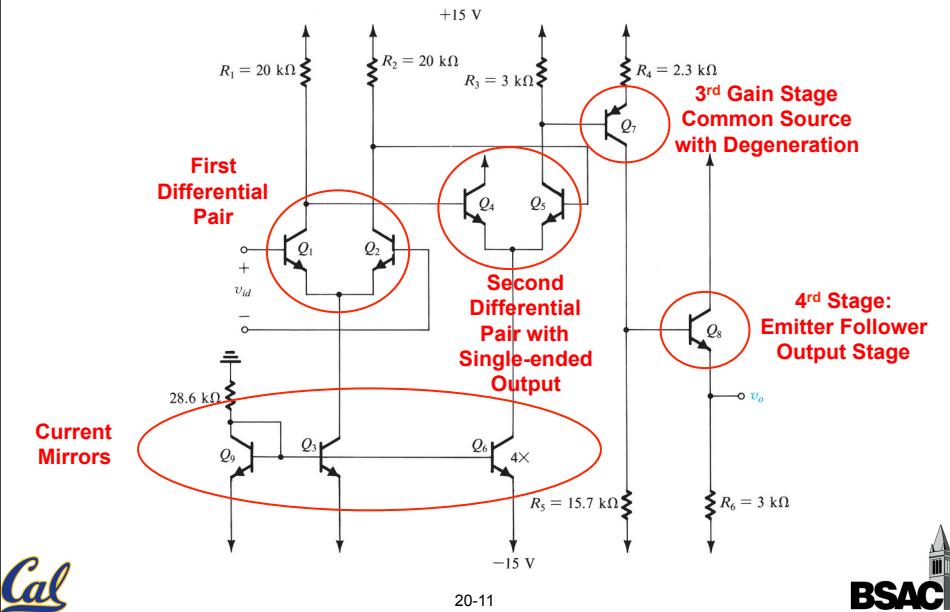

## DC Solution

