


EE 105 | Discussion 12

Kieran Peleaux & Qianyi Xie

Discussion Outline

- Midterm 2 Solutions
 - Problem 1(b)
 - Problem 1(c)
- Diode-connected Transistors
- Current Mirrors

MT2: Problem 1(b)

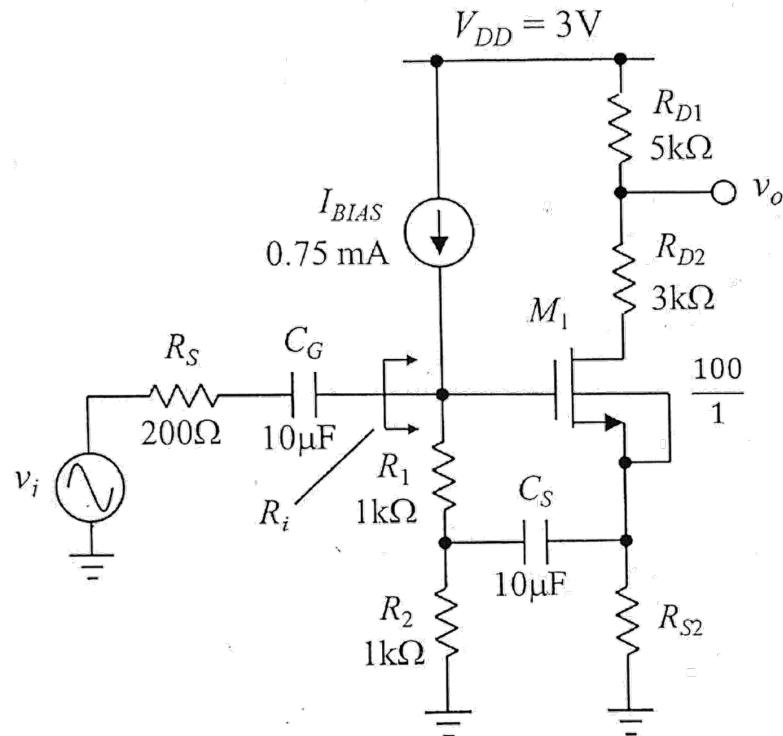

Device Parameters:

NMOS:

$$V_{tn0} = 0.7\text{V}$$

$$2|\phi| = 0.6\text{V}$$

$$\mu_n C_{ox} = 200\mu\text{A/V}^2$$

$$\lambda_n = 0.01 \text{ V}^{-1}$$


- Find R_{S2} to get $I_C = 100 \mu\text{A}$
- Find R_i
- Find an expression for f_H

MT2: Problem 1(b) – Find R_{S2}

(DC analysis
open all C's)

$$V_{tn} = V_{tn0},$$

b/c B & S are shorted

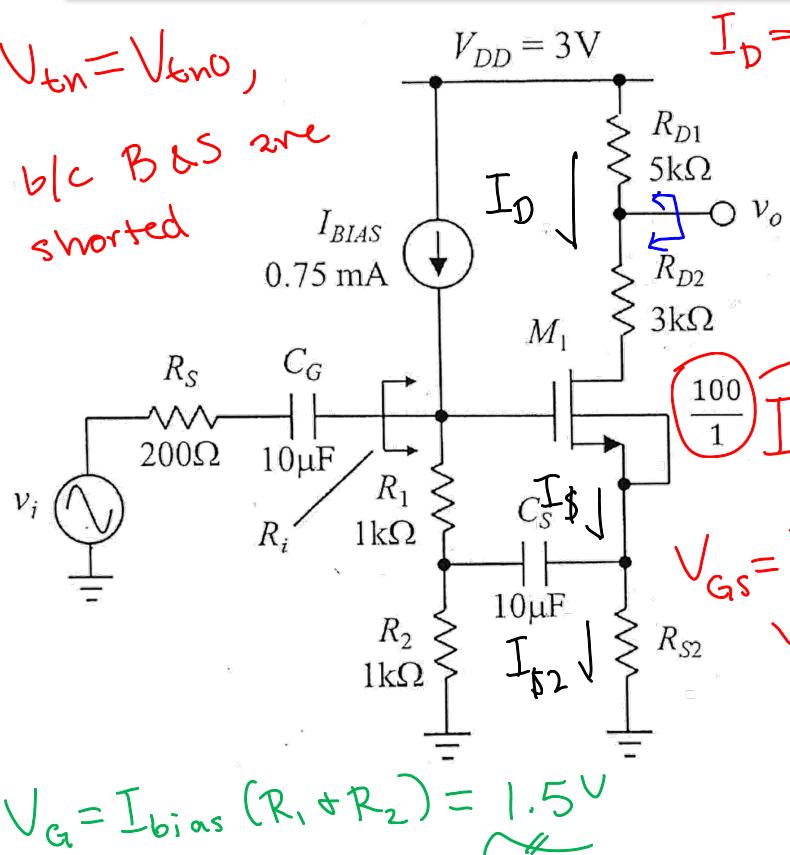

$$I_D = 100 \mu\text{A} \text{ (given)}$$

Device Parameters:

NMOS:

$$V_{tn0} = 0.7\text{V}$$

$$2|\phi_f| = 0.6\text{V}$$

$$\mu_n C_{ox} = 200 \mu\text{A/V}^2$$

$$\lambda_n = 0.01 \text{ V}^{-1}$$

$$I_D = \frac{\mu_n C_{ox} W}{2} (V_{GS} - V_{tn})^2$$


$$V_{GS} = \sqrt{2 I_D + V_{tn0}} = 0.8\text{V}$$

$$(I_{S2} = I_S = I_D)$$

$$V_G = I_{bias} (R_1 + R_2) = 1.5\text{V}$$




$$R_{S2} = \frac{V_S}{I_D} = \frac{V_G - V_{GS}}{I_D} = \frac{0.7\text{V}}{100 \mu\text{A}}$$

$$R_{S2} = 7 \text{ k}\Omega$$

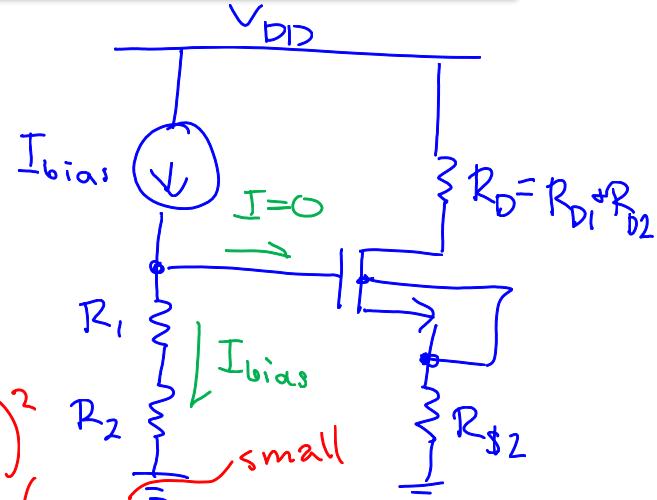

MT2: Problem 1(b) – Find R_i

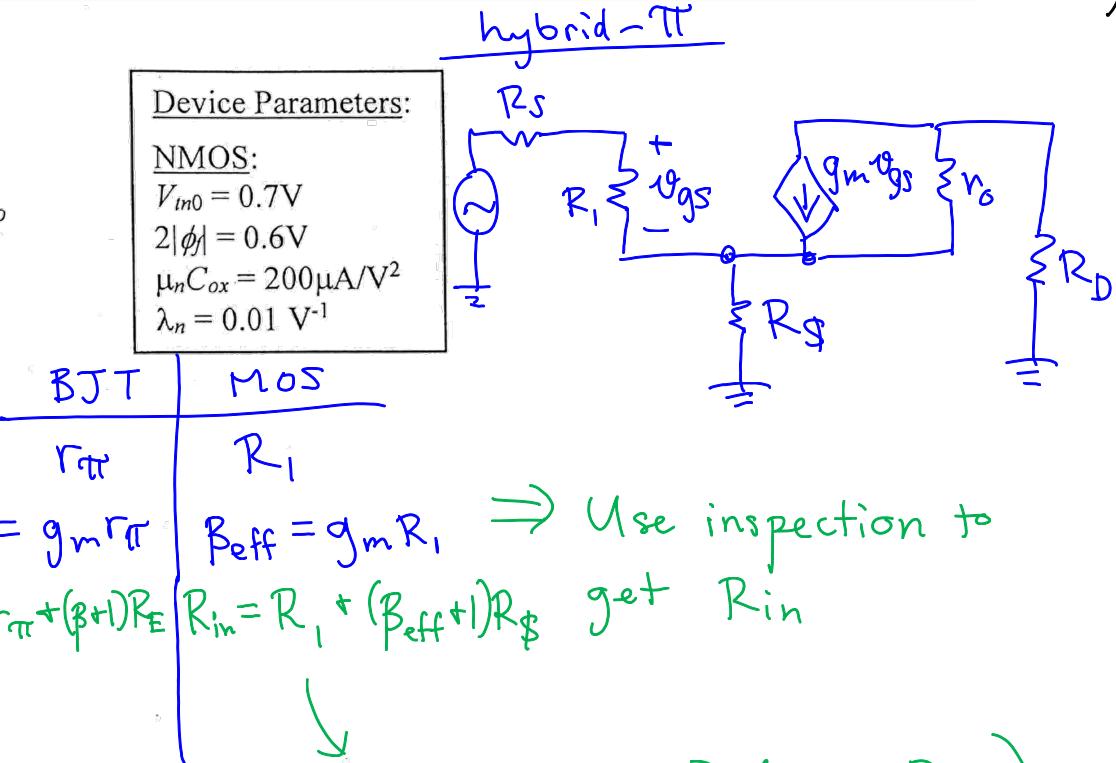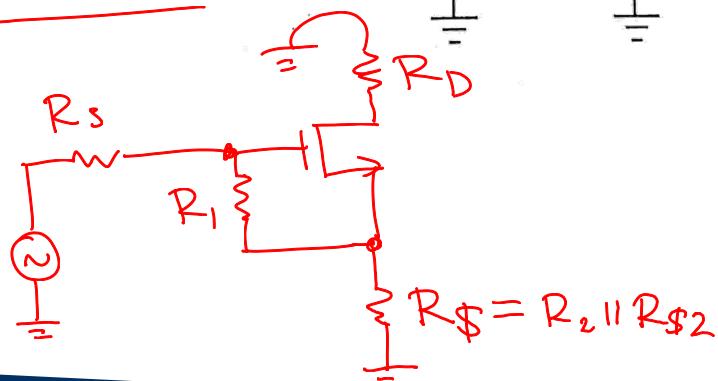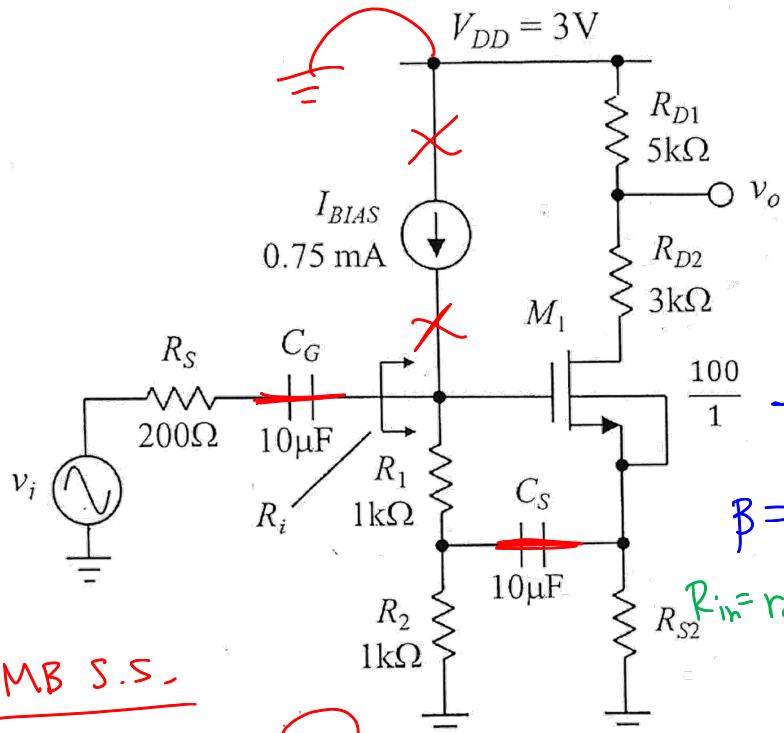
midband, so
short large caps,
open small caps,
turn off DC sources



$$R_{in} = R_1 + (g_m R_1 + 1)(R_2 \parallel R_{\$2})$$

$$R_{in} = 3.625 k\Omega$$

MT2: Problem 1(b) – Find f_H (OCTC)

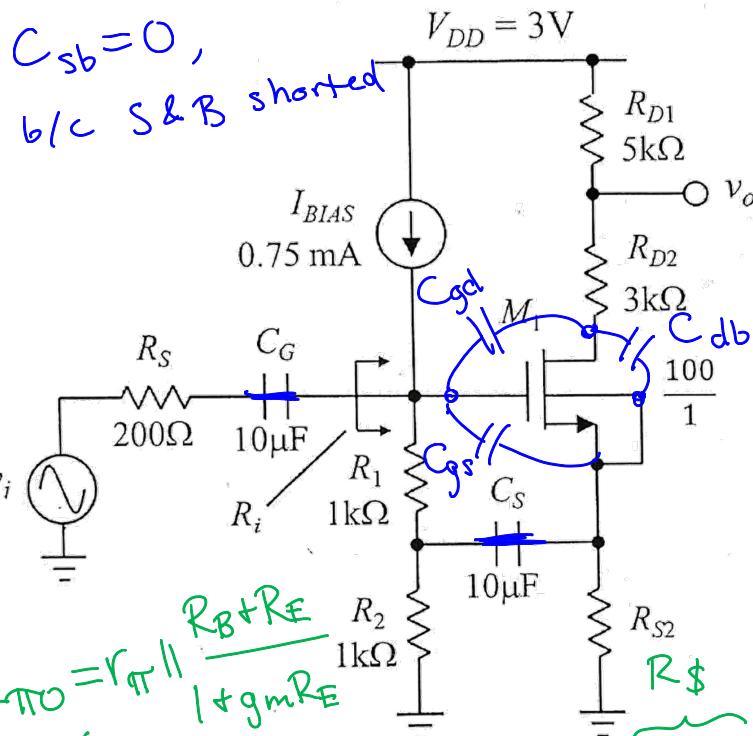

Device Parameters:

NMOS:
$V_{tn0} = 0.7V$
$2 \phi_f = 0.6V$
$\mu_n C_{ox} = 200 \mu\text{A/V}^2$
$\lambda_n = 0.01 \text{ V}^{-1}$

$$f_H = \frac{1}{2\pi \sum C}$$


$$\mathcal{L}_{g_s} = C_{gs} R_{gso}$$

$$R_{\pi O} = r_\pi \parallel \frac{R_B + R_E}{1 + g_m R_E}$$

$$R_{gso} = R_1 \parallel \frac{R_s + (R_2 \parallel R_{s2})}{1 + g_m (R_2 \parallel R_{s2})}$$

$$g_m = \frac{2I_D}{V_{ov}}$$

MT2: Problem 1(b) – Find f_H

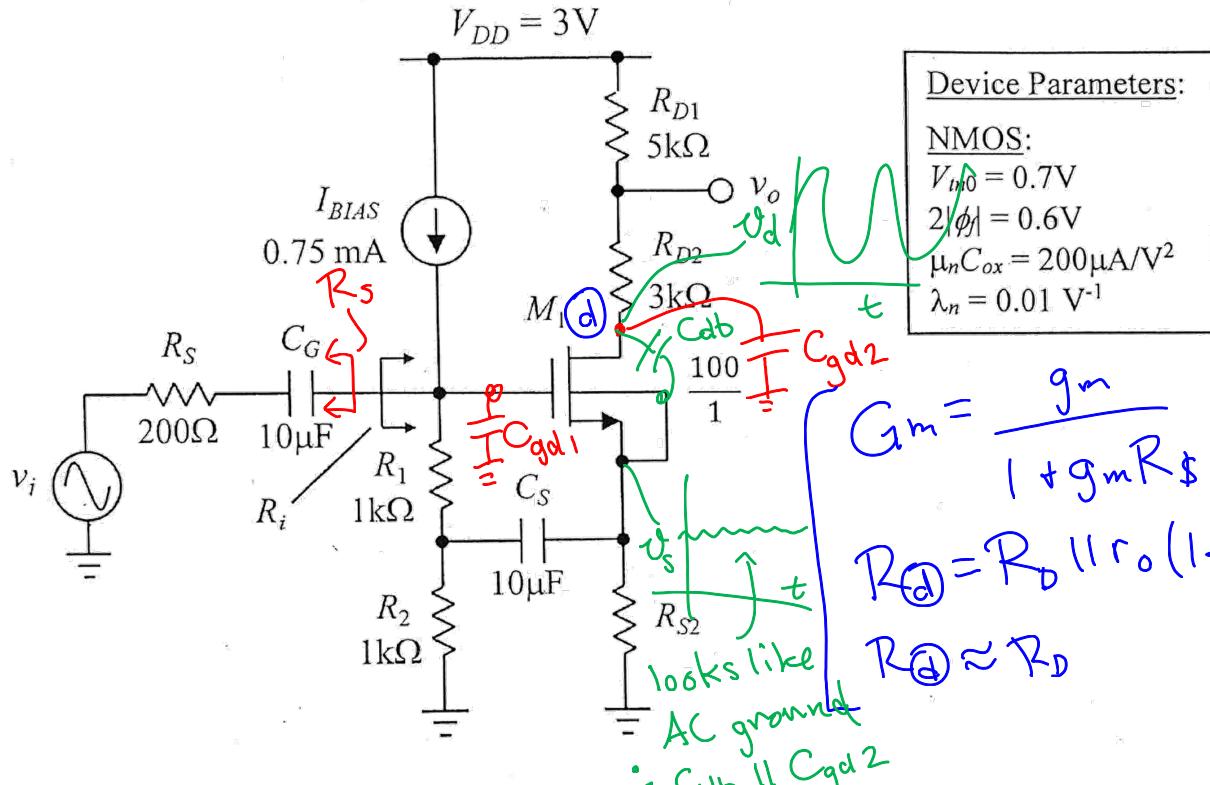

$$\gamma_g = C_{gd1} (R_s \parallel R_{in}) \quad \gamma_d = (C_{db} + C_{gd2})(R_D)$$

Miller equiv. C_{gd1}

$$C_{gd1} = C_{gd} \left(1 - \frac{v_d}{V_g}\right)$$


$$= C_{gd} (1 + G_m R_{D1})$$

$$C_{gd1} = \left(1 + \frac{g_m R_D}{1 + g_m R_s}\right) C_{gd}$$

$$C_{gd2} \approx C_{gd}$$

$$f_H \approx \frac{1}{2\pi(\gamma_{gs} + \gamma_g + \gamma_d)}$$

MT2: Problem 1(c) (SCTC)

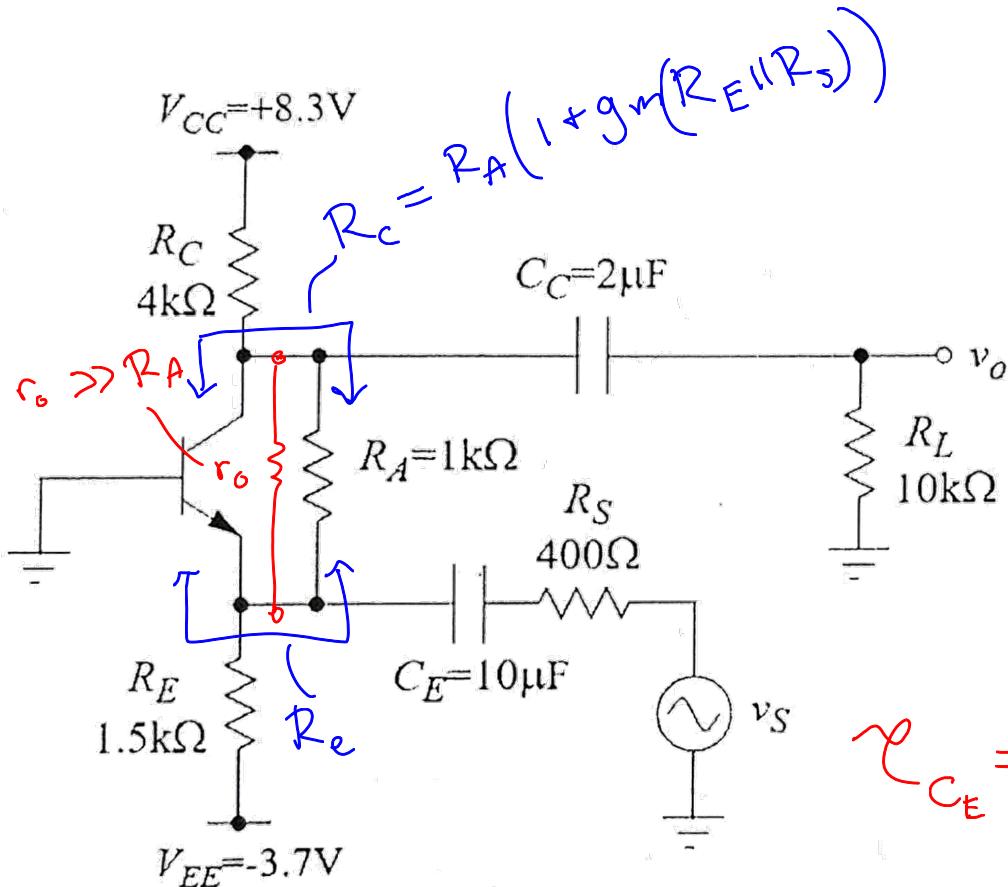

Device Parameters:

- $\beta = 200$
- $V_A = 200V$
- $C_\mu = 4pF$
- $f_T = 400MHz$
- $I_C = 1mA$

- Find f_L


find by applying
test source

$$\mathcal{Z}_{C_E} = C_E (R_s + R_E \parallel R_e)$$

$$f_L \approx 38 \text{ Hz}$$

$$\mathcal{Z}_{C_C} = C_C (R_L \parallel R_A \parallel R_c)$$

Diode Connected Transistors

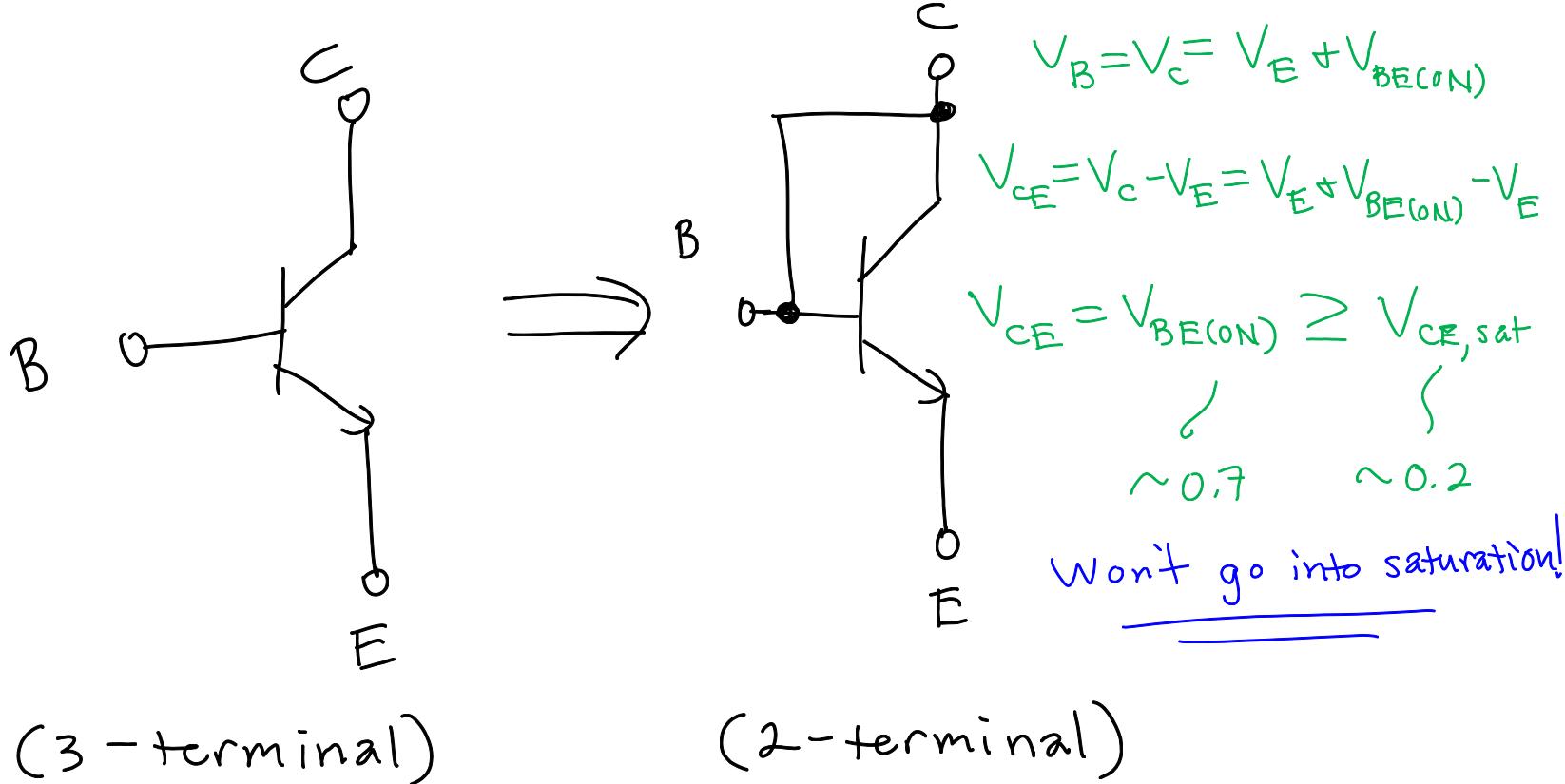


Diode Connected Transistors

What's happening?

Normal BJTs are actually voltage-controlled current sources ($I_c = I_S e^{\frac{v_{BE}}{V_T}}$), where we approximate v_{BE} as constant.

To set a specific I_c , we need to choose V_B, V_E, R_E, R_C
carefully.
*↑
stay in F.A.*

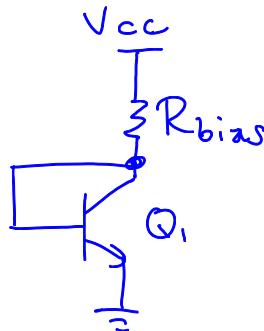Diode-connected BJTs allow us to set I_C with a single resistor!



$$I_{C1} \approx \frac{V_{cc} - V_c}{R_{bias}} = \frac{V_{cc} - V_{BE(\text{CON})}}{R_{bias}}$$

*↑
equal if $\beta = \infty$*

Current Mirrors

