

EE 105 | Discussion 13


Kieran Peleaux & Qianyi Xie

Discussion Outline

- Bandgap Reference
- Toward a High Gain

Bandgap Reference

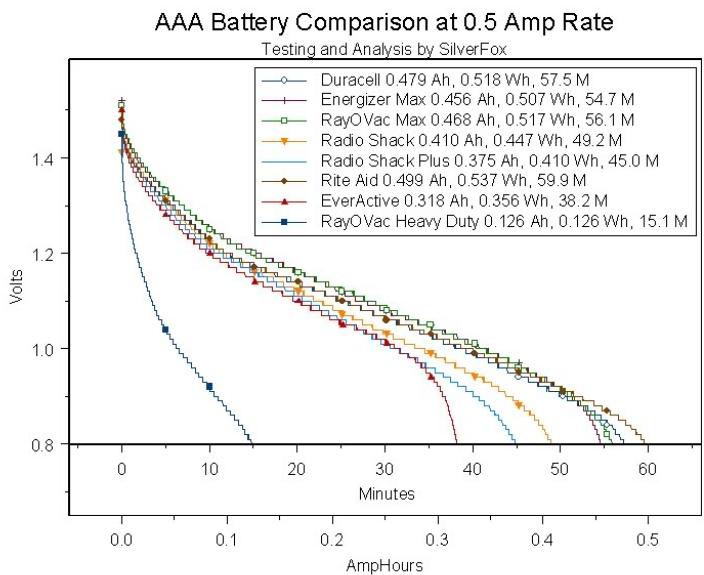- How to get ‘1V’ on-chip?
 - AAA battery as power supply



Bandgap Reference

- Supply-independent reference voltage

Bandgap Reference

- Supply/Temperature independent reference voltage


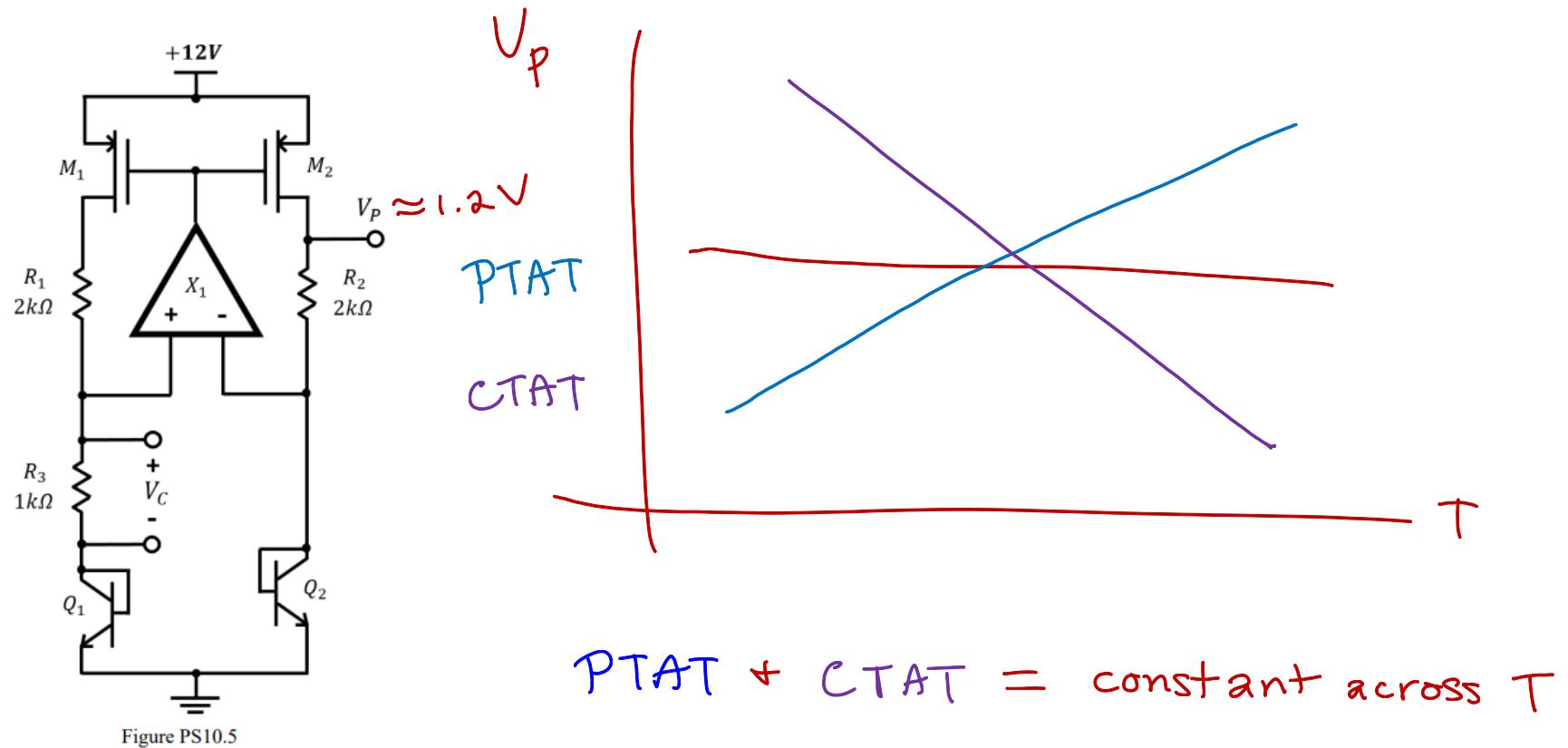


Figure PS10.5

Bandgap Reference

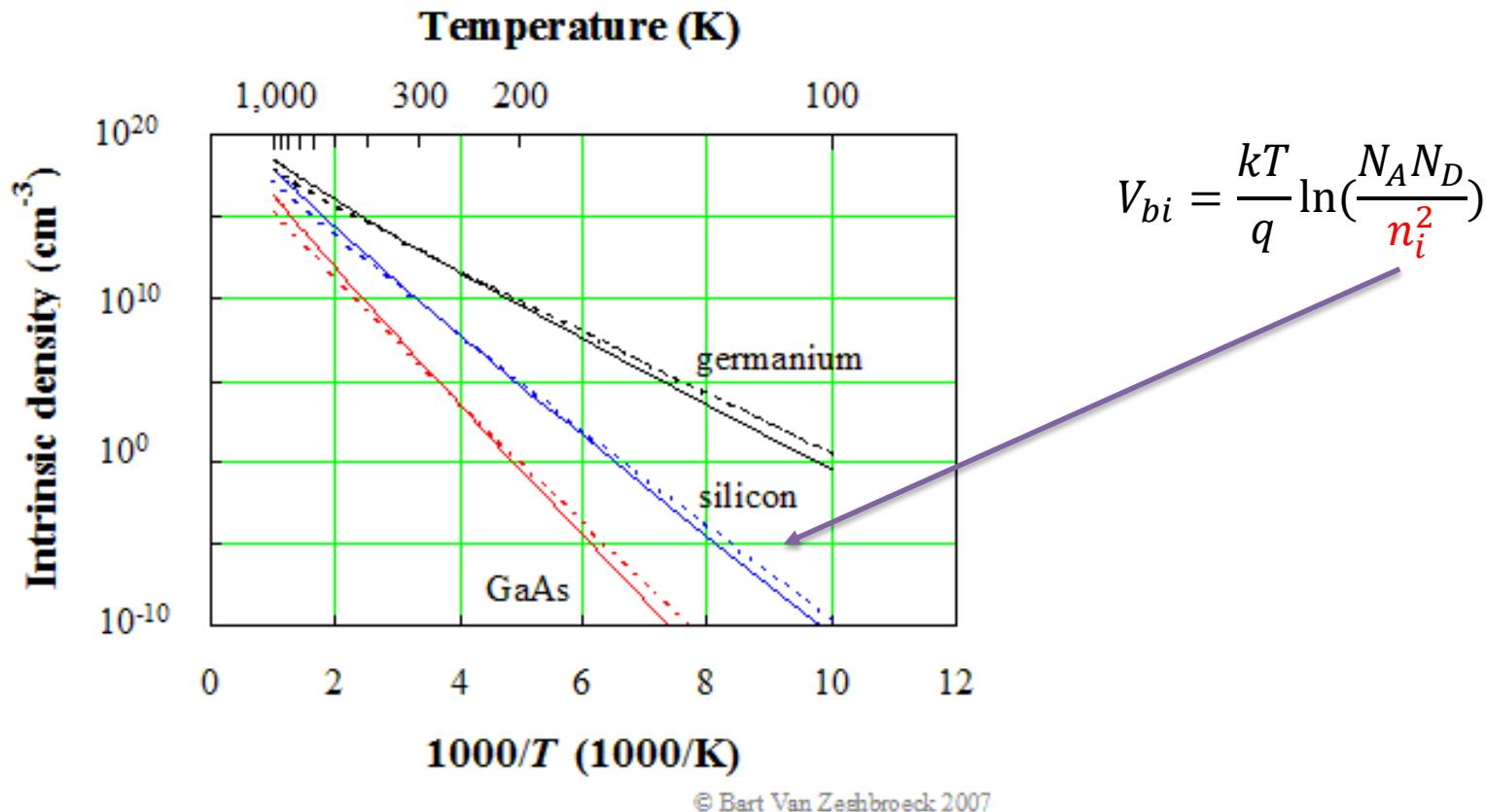
- Supply/Temperature independent reference voltage



Bandgap Reference


- Supply/Temperature independent reference voltage
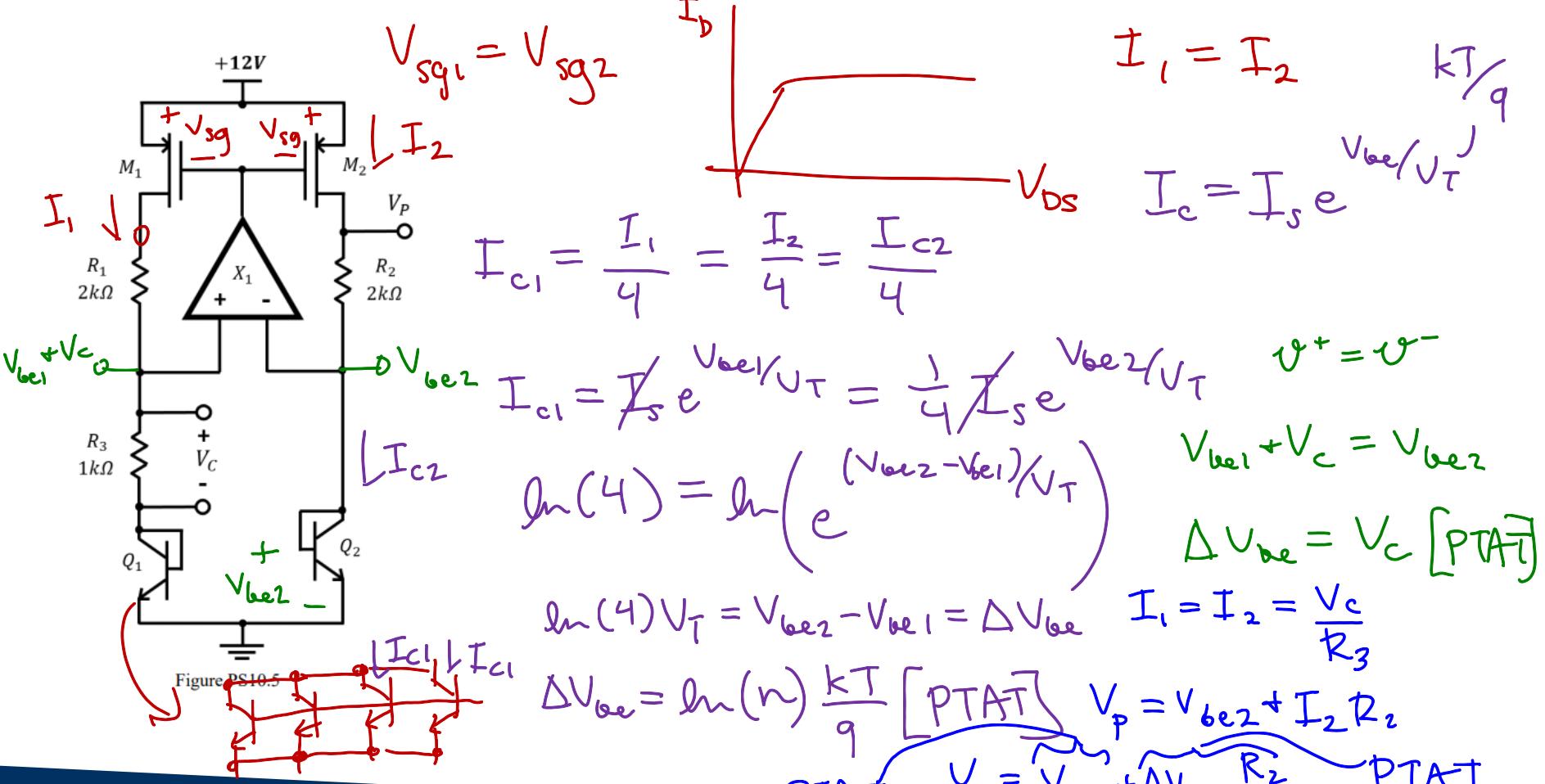
$$I_c = I_s e^{V_{be}/N_T} \quad I_c \text{ const}, \quad T \uparrow, V_{be}$$



Toward a High Gain


- Need more gain than CS/CE provides

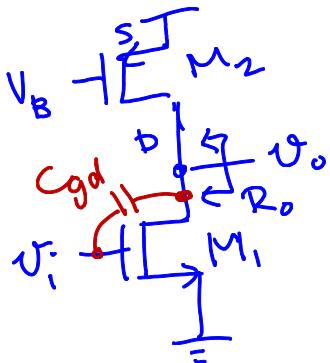

$$A_v = -g_m R_o = -g_m (r_{o1} // r_{o2})$$

$$A_v = -\frac{g_m r_o}{2}$$


$$A_o = g_m r_o$$

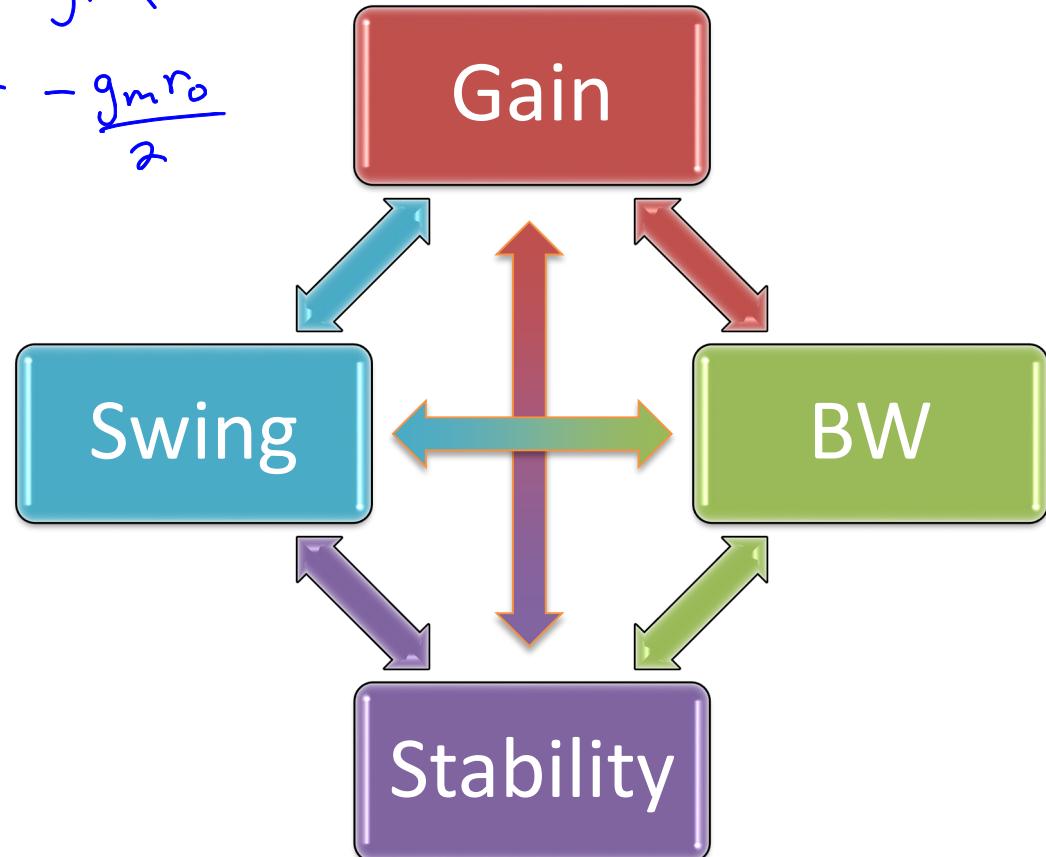

$$C_{dom} = C_{gs1} + C_{gd1} \left(1 + \frac{g_m r_o}{2}\right)$$


Multi-Stage Amplifier
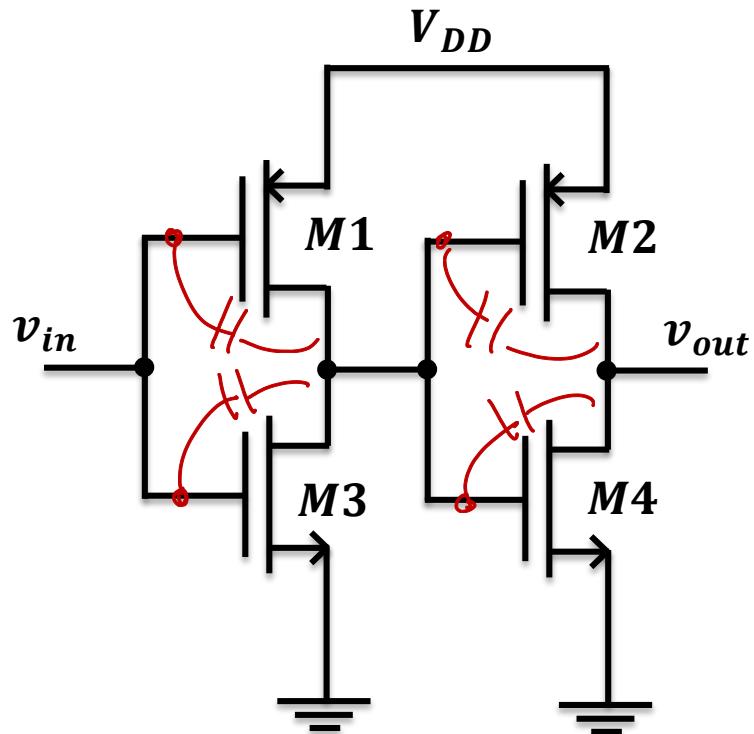
$$A_v = -(g_{m1} + g_{m3})(r_{o1} // r_{o3}) = -g_m r_o \quad \frac{V_o}{V_i} = (g_m r_o)^2$$




$$C_{in} = C_{gs1} + C_{gc3} + (1 + g_m r_o)(C_{gd1} + C_{gd3})$$

2-Stage CS w/ FB

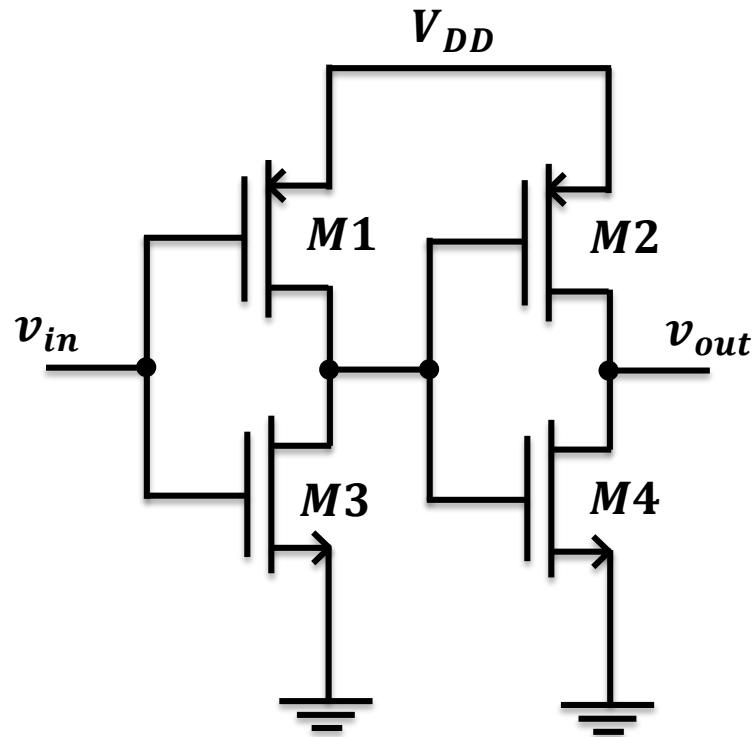


2-Stage CS w/ Miller Compensation

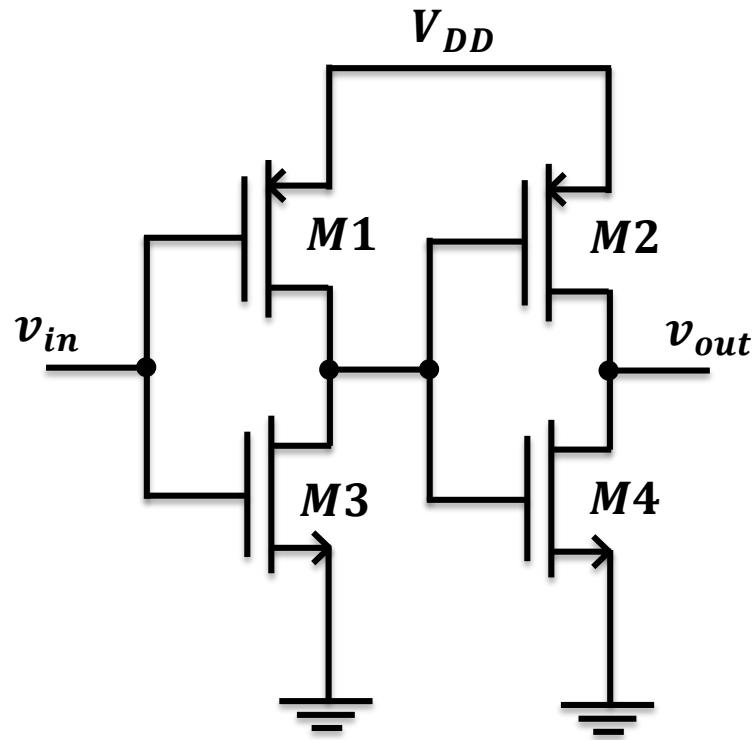

Cascode Amplifier

$g_m r_o \gg 1$

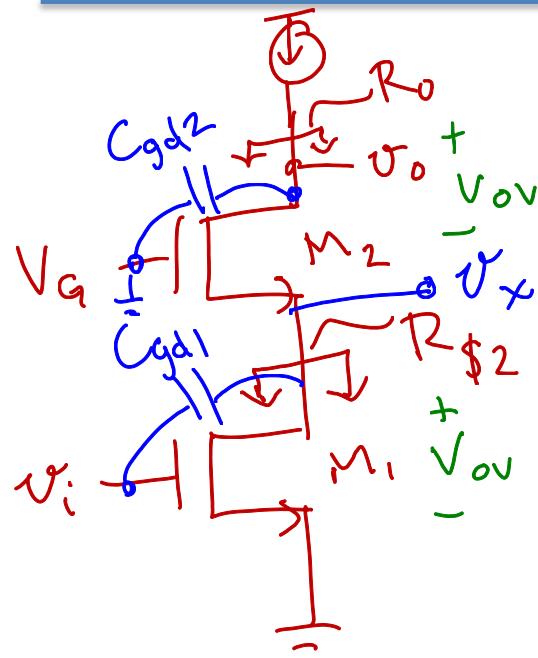

$$\frac{v_o}{v_i} = -g_{m1} \left[R_{o2} \left(1 + g_{m2} R_{\$2} \right) \right] R_{\$2} = r_{o1}$$

$$= -g_{m1} r_{o2} g_{m2} r_{o1} = -(g_m r_o)^2$$

$$(A_v) = g_m r_o$$

Advantages: gain $\uparrow\uparrow$
BW \uparrow

~~$$= 2V_D \frac{V_A}{V_{ov}} \frac{1}{2V_D}$$~~

$$\frac{v_x}{v_i} = -g_{m1} \left[r_{o1} \parallel \frac{1}{g_{m2}} \right] \approx -1$$

$$C_{in} = C_{gs1} + C_{gd1}(1+1)$$

$$V_{DD} \geq 2V_{ov} + V_{o,PP}$$

Disadvantages: $V_{o,min} = 2V_{ov}$


$$V_{DD} = 0.8V, V_{o,PP} = 0.4V$$

$$V_{ov,max} = ? = 200mV$$

Cascode Amplifier

Cascode Amplifier

Differential Pairs

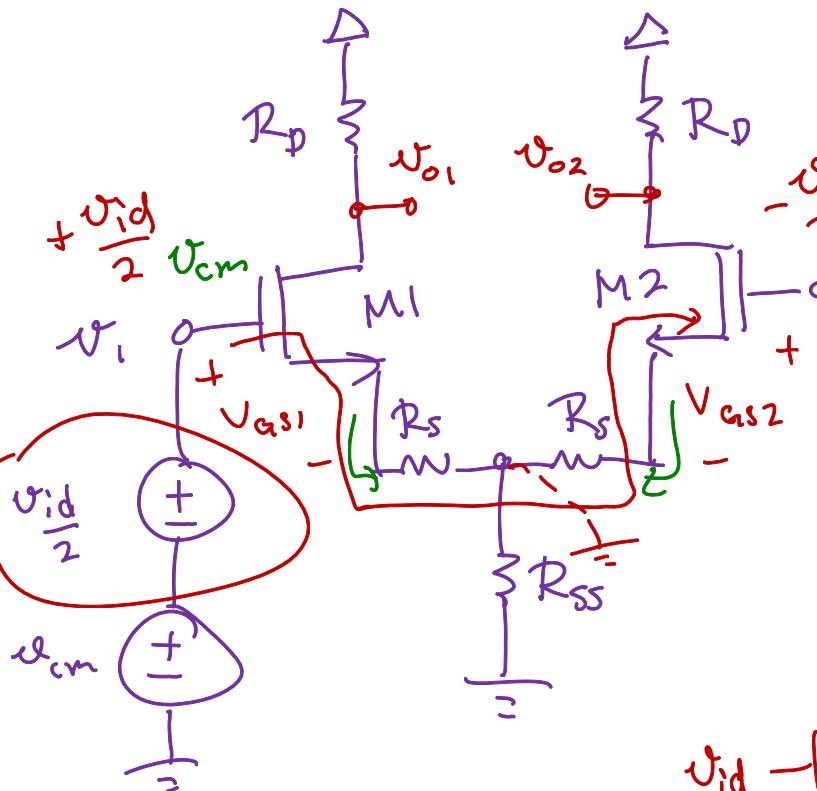

$$v_i - v_2$$


$$v_{od} = v_{o1} - v_{o2}$$

$$v_i = v_{cm} + \frac{v_{id}}{2}, \quad v_2 = v_{cm} - \frac{v_{id}}{2}$$

$$\begin{cases} v_{cm} = \frac{v_1 + v_2}{2} \\ v_{id} = (v_1 - v_2) \end{cases}$$

$$v_{gs1} = v_{gs2}$$
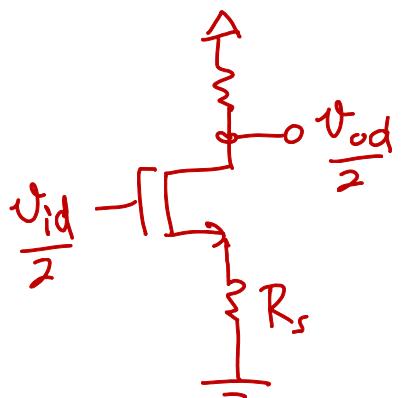
$$\frac{v_{id}}{2} - v_{gs} + v_{gs} = -\frac{v_{id}}{2}$$




$$Av_{dm} = \frac{v_{od}/2}{v_{id}/2} = \frac{v_{od}}{v_{id}}$$

↖ differential-mode
↙ det.

Differential Pairs


Common-mode ½ det.

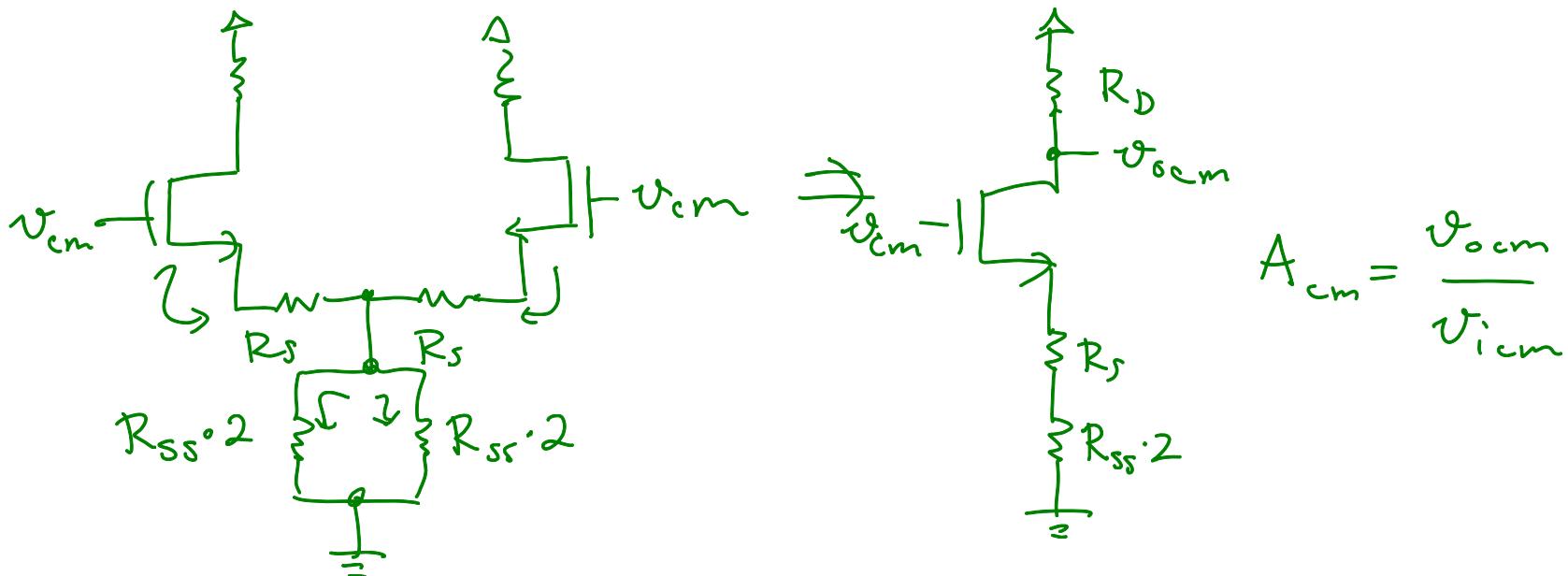

Differential Pairs


Frequency Compensation

Stage 2(?)


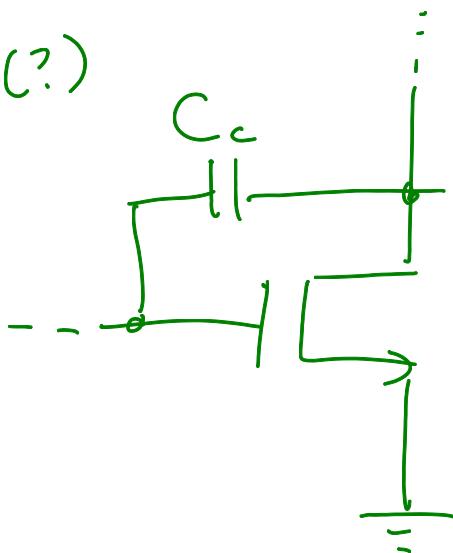


$$A_{v2} = -G_{m2} R_{D2}$$

$$C_{in2} = C_c (1 + G_{m2} R_{D2})$$

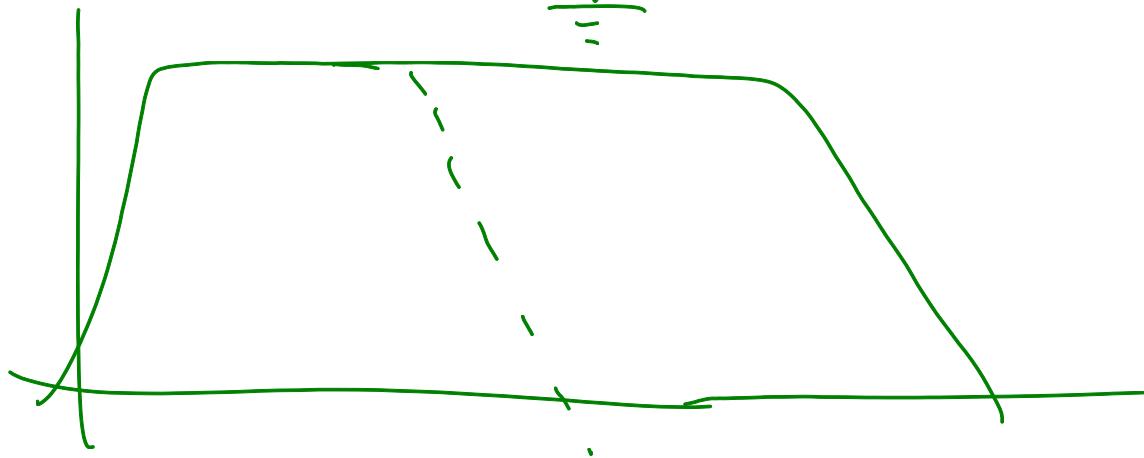

Frequency Compensation

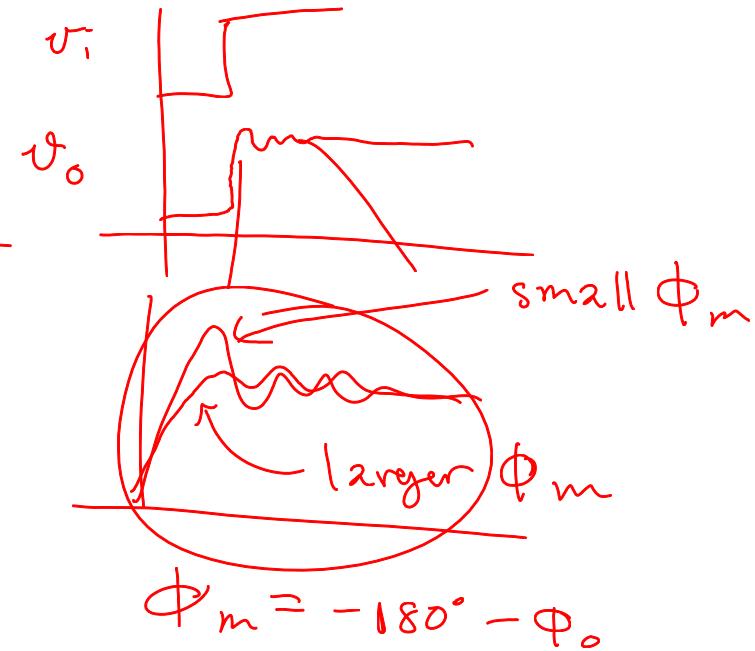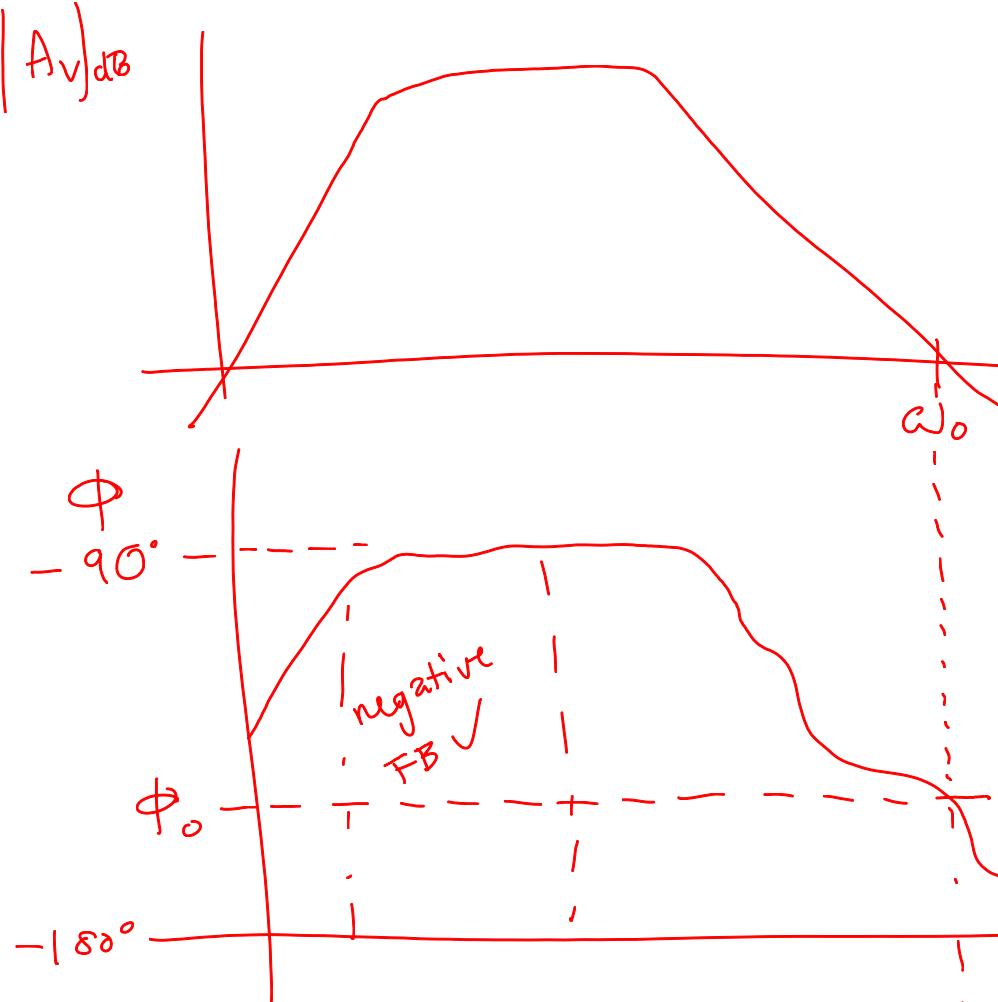

Frequency Compensation
