

EE 105 Discussion Welcome!


K. Peleaux & Qianyi Xie

Today


- Linearize a non-linear device
- Selected homework problems
- Selected S&S exercises

$\forall f(f(x) = ax + b \Rightarrow a, b - \text{const.})$
 f is a linear function $f(x) = ax + b, a, b \text{ const.}$


Linearize a non-linear Device

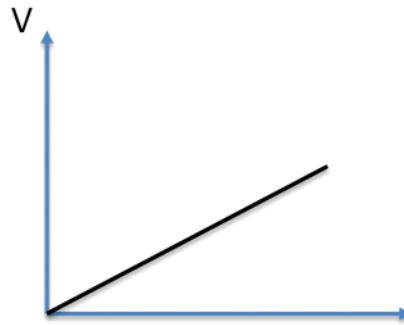

Resistor

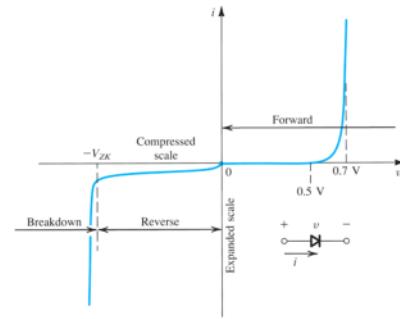

Diode

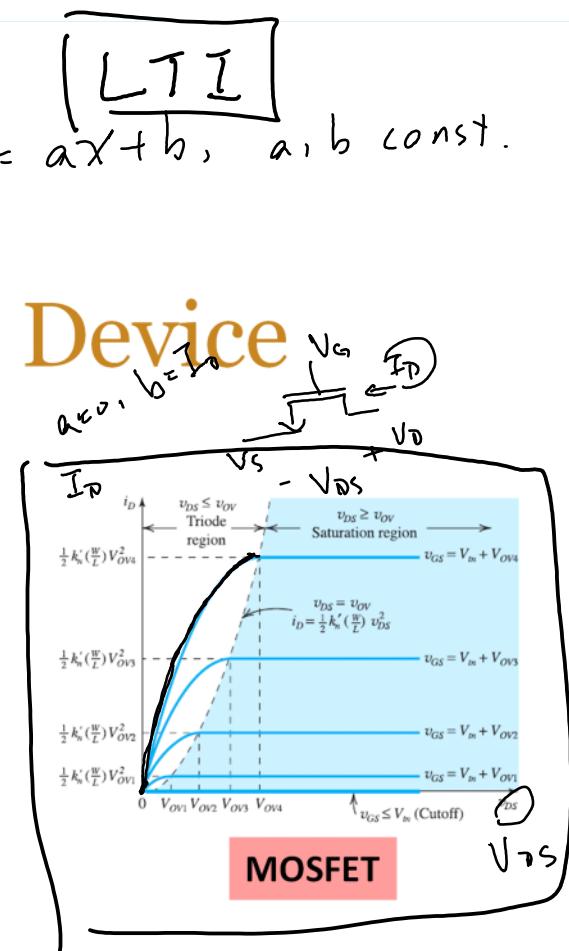



MOSFET

$$\begin{aligned} \text{Resistor: } R &= \frac{V}{I} \\ \text{Capacitor: } SC &= \frac{I}{V} \\ \text{Inductor: } SL &= \frac{V}{I} \end{aligned}$$


$$+ \quad - \Rightarrow \boxed{V - C - U - S}$$

2-Port Device

MOSFET

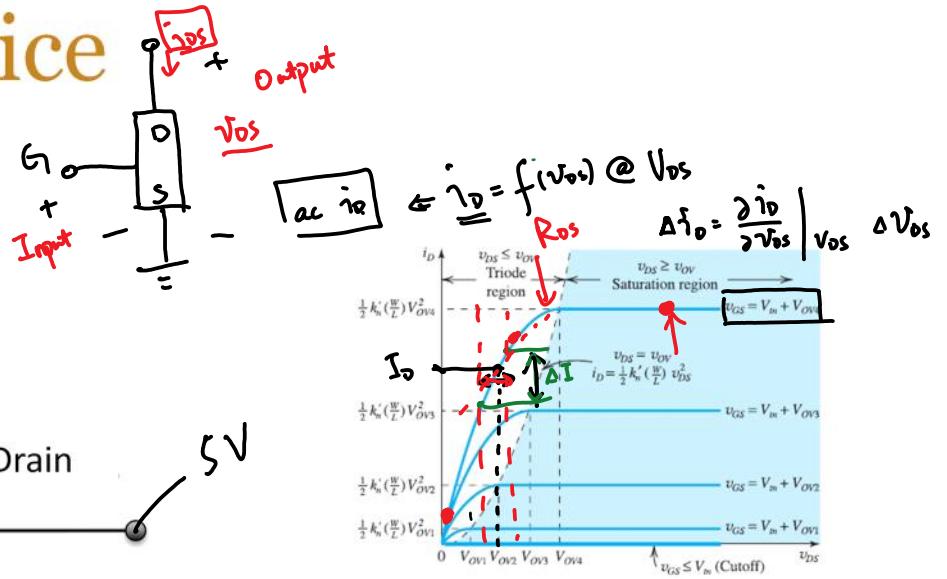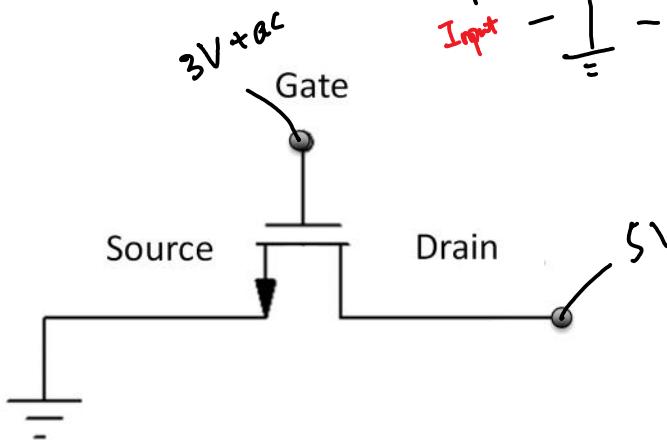

A random 2-Port Device

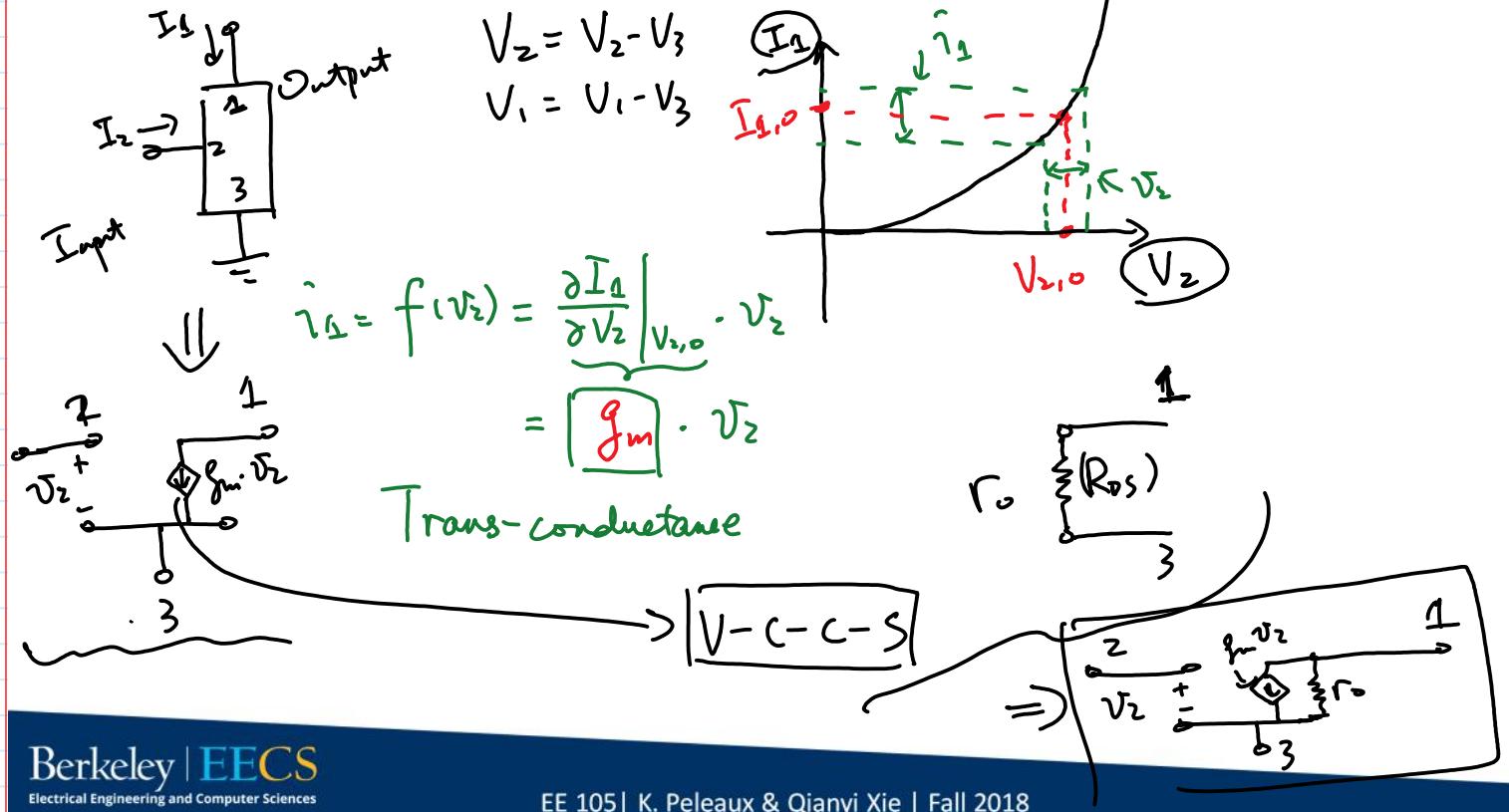

HW2 Q5

5. Derive an expression for the current I_L in terms of I_S , R_1 , and R_2 for the circuit in Figure PS2.1. Calculate the input and output resistance of this circuit if the OpAmp is ideal.



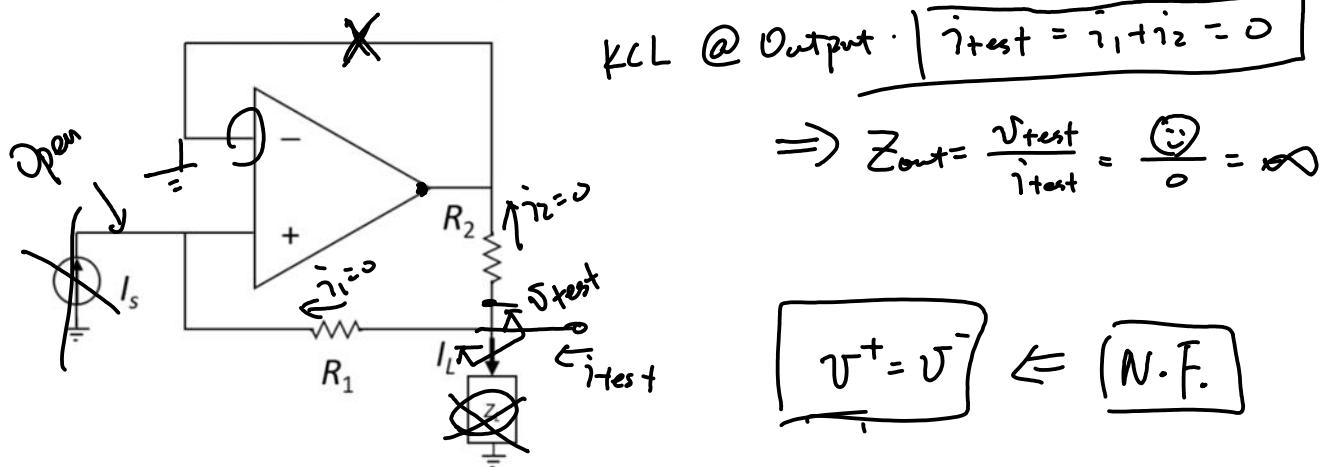


Figure PS2.1

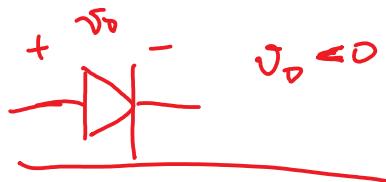

S&S 4.9

Ideal Diode:

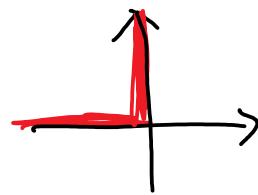

- 1) Assumption $\Rightarrow \# = 2^n$ # Diode
- 2) Solve with assumptions
- 3) Only 1 will work.

4.9 Assuming that the diodes in the circuits of Fig. P4.9 are ideal, find the values of the labeled voltages and currents.

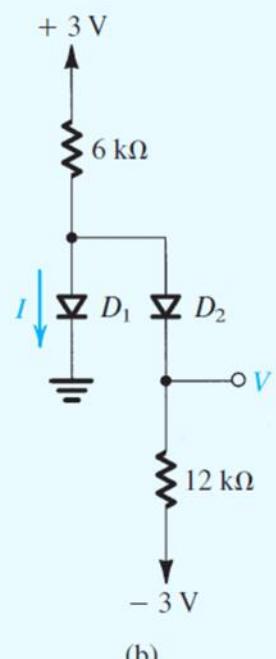
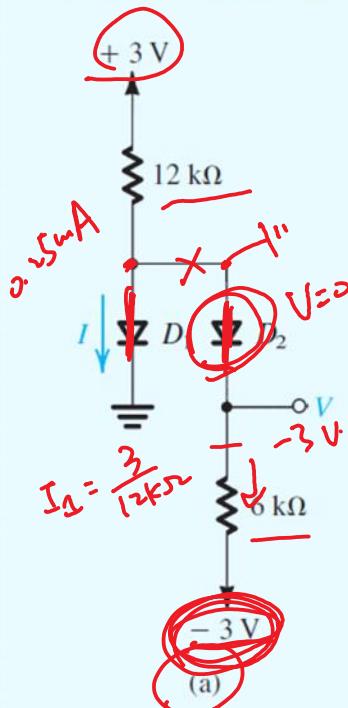


Figure P4.9