

**PROBLEM SET #2**

Issued: Friday, August 31, 2018

Due: Friday, September 07, 2018, 12:00 noon via **Gradescope**.

1. Sedra & Smith, Problem 2.78
2. Sedra & Smith, Problem 2.84
3. Sedra & Smith, Problem 2.87
4. Sedra & Smith, Problem 2.93
5. Derive an expression for the current  $I_L$  in terms of  $I_S$ ,  $R_1$ , and  $R_2$  for the circuit in Figure PS2.1. Calculate the input and output resistance of this circuit if the OpAmp is ideal.
6. Find expressions for the voltage  $v_{o1}$  and  $v_{o2}$  in terms of  $v_s$ ,  $R_1$ ,  $R_2$ , and  $R_3$  for the circuit in Figure PS2.2. The OpAmps are ideal.

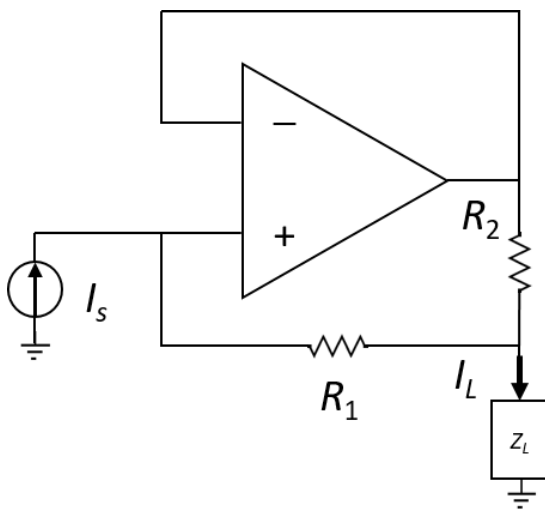


Figure PS2.1

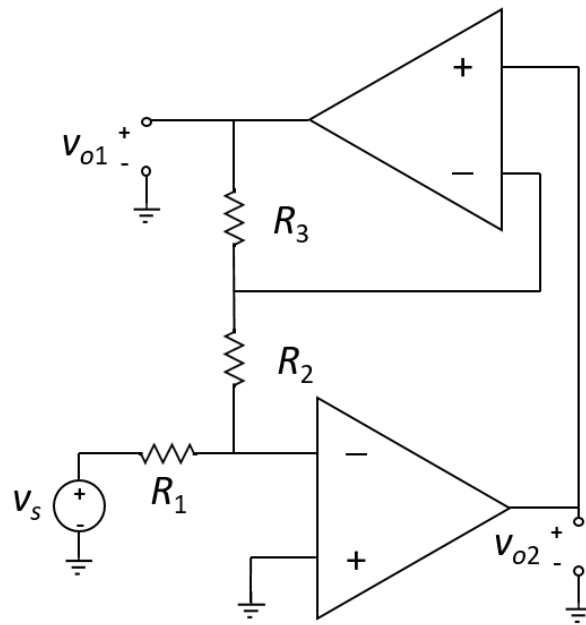


Figure PS2.2

7. Create a SPICE netlist for the circuit shown in Figure PS2.3 by following the procedures described in the handout "HSPICE Tutorial". Run a transient analysis. Attach the plot of  $V_{out}$  and  $I_{Diode}$  versus time for 5 periods.
  - (a) What is the magnitude of the peak-to-peak voltage ripple across the load resistor  $R_L$ ?
  - (b) What is the peak current drawn through the diode?
  - (c) Suppose that the load resistor  $R_L$  and the input voltage are fixed, but the value of capacitor  $C$  varies. What value of capacitance  $C$  would you choose to reduce the output ripple to

$0.5V \pm 0.01V$  peak-to-peak? (Estimate using hand analysis before you verify with simulation. Show your hand analysis.)

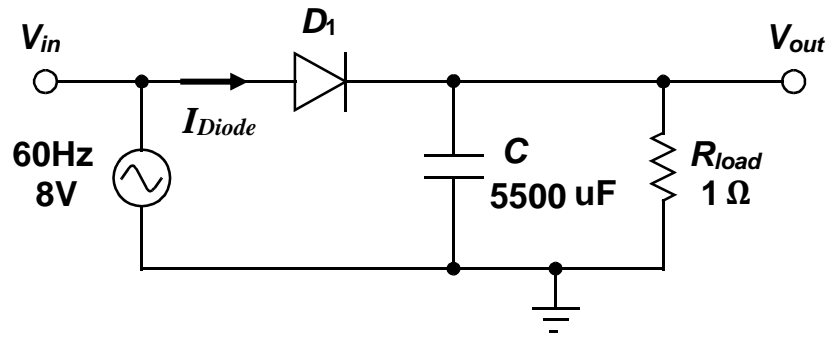


Figure PS2.3