

PROBLEM SET #4

Issued: Friday, September 14, 2018

*Due: Friday, September 21, 2018, 12:00 noon via **Gradescope**.*

1. Sedra & Smith, Problem 2.116
2. Sedra & Smith, Problem 2.118
3. Sedra & Smith, Problem 2.122
4. A diode is doped with $N_A = 10^{19}/\text{cm}^3$ on the p -type side and $N_D = 10^{18}/\text{cm}^3$ on the n -type side.
 - (a) What is the depletion-layer width w_d ?
 - (b) What are the values of x_p and x_n ?
 - (c) What is the value of the built-in potential of the junction?
 - (d) What is the value of E_{MAX} ?
5. A diode has $I_S = 10^{-17}A$ and $n = 1$.
 - (a) What is the diode voltage if the diode current is $100\mu A$?
 - (b) What is the diode voltage if the diode current is $10\mu A$?
 - (c) What is the diode current for $v_D = 0$?
 - (d) What is the diode current for $v_D = -0.06V$?
 - (e) What is the diode current for $v_D = -4V$?
6. What is the zero-bias junction capacitance per cm^2 for a diode with $N_A = 10^{15}/\text{cm}^3$ on the p -type side and $N_D = 10^{20}/\text{cm}^3$ on the n -type side? What is the diode capacitance with a $5V$ reverse bias if the diode area is 0.01cm^2 ?
7. Calculate the worst-case output voltage for the circuit in Figure PS4.1 if $V_{OS} = 1\text{mV}$, $I_{B+} = 100\text{nA}$, and $I_{B-} = 95\text{nA}$. What would the ideal output voltage be? What is the total error in this circuit? Is there a better choice for the value of R_1 ? If so, what is the value?
8. The op amp in the circuit of Figure PS4.2 has an open-loop gain of 10,000, an offset voltage of 1mV , and an input-bias current of 100nA .
 - (a) What would be the output voltage for an ideal op amp?
 - (b) What is the actual output voltage for the worst-case polarity of offset voltage?
 - (c) What is the percentage error in the output voltage compared to the ideal output voltage?

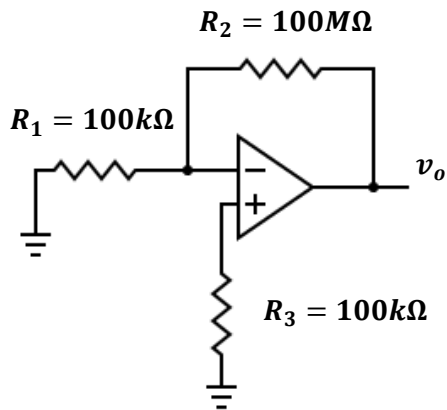


Figure PS4.1

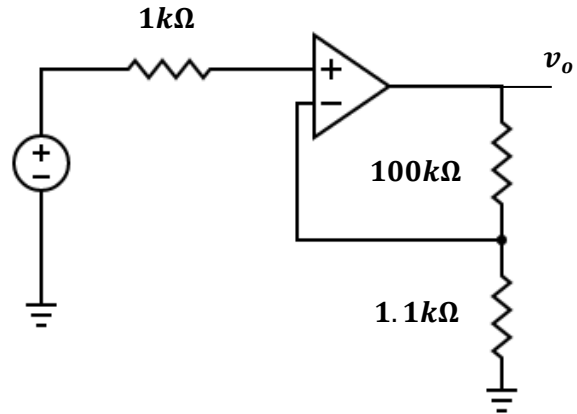


Figure PS4.2