

transistor  $\beta$  is specified to lie in the range 50 to 150, find the corresponding range of  $R_{out}$  and  $G_v$ .

**7.87** An emitter follower, when driven from a 5-k $\Omega$  source, was found to have an output resistance  $R_{out}$  of 150  $\Omega$ . The output resistance increased to 250  $\Omega$  when the source resistance was increased to 10 k $\Omega$ . Find the overall voltage gain when the follower is driven by a 10-k $\Omega$  source and loaded by a 1-k $\Omega$  resistor.

**7.88** For the general amplifier circuit shown in Fig. P7.88 neglect the Early effect.

- (a) Find expressions for  $v_c/v_{sig}$  and  $v_e/v_{sig}$ .
- (b) If  $v_{sig}$  is disconnected from node X, node X is grounded, and node Y is disconnected from ground and connected to  $v_{sig}$ , find the new expression for  $v_c/v_{sig}$ .

 


Figure P7.88

**7.89** When the Early effect is neglected, the overall voltage gain of a CE amplifier with a collector resistance  $R_C = 10$  k $\Omega$  is calculated to be  $-100$  V/V. If the BJT is biased at  $I_C = 1$  mA and the Early voltage is 100 V, provide a better estimate of the voltage gain  $G_v$ .

**\*7.90** Show that when  $r_o$  is taken into account, the voltage gain of the source follower becomes

$$G_v \equiv \frac{v_o}{v_{sig}} = \frac{R_L \parallel r_o}{(R_L \parallel r_o) + \frac{1}{g_m}}$$

Now, with  $R_L$  removed, the voltage gain is carefully measured and found to be 0.98. Then, when  $R_L$  is connected and its value is varied, it is found that the gain is halved at  $R_L = 500$   $\Omega$ . If the amplifier remained linear throughout this measurement, what must the values of  $g_m$  and  $r_o$  be?

**D 7.91** In this problem, we investigate the effect of changing the bias current  $I_C$  on the overall voltage gain  $G_v$  of a CE amplifier. Consider the situation of a CE amplifier operating with a signal source having  $R_{sig} = 10$  k $\Omega$  and having  $R_C \parallel R_L = 10$  k $\Omega$ . The BJT is specified to have  $\beta = 100$  and  $V_A = 25$  V. Use Eq. (7.114) (with  $r_o$  included in parallel with  $R_C$  and  $R_L$  in the numerator) to find  $|G_v|$  at  $I_C = 0.1$  mA, 0.2 mA, 0.5 mA, 1.0 mA, and 1.25 mA. Observe the effect of  $r_o$  on limiting  $|G_v|$  as  $I_C$  is increased. Find the value of  $I_C$  that results in  $|G_v| = 50$  V/V.

### Section 7.4: Biasing

**D 7.92** Consider the classical biasing scheme shown in Fig. 7.48(c), using a 9-V supply. For the MOSFET,  $V_t = 1$  V,  $\lambda = 0$ , and  $k_n = 2$  mA/V<sup>2</sup>. Arrange that the drain current is 1 mA, with about one-third of the supply voltage across each of  $R_S$  and  $R_D$ . Use 22 M $\Omega$  for the larger of  $R_{G1}$  and  $R_{G2}$ . What are the values of  $R_{G1}$ ,  $R_{G2}$ ,  $R_S$ , and  $R_D$  that you have chosen? Specify them to two significant digits. For your design, how far is the drain voltage from the edge of saturation?


**D 7.93** Using the circuit topology displayed in Fig. 7.48(e), arrange to bias the NMOS transistor at  $I_D = 0.5$  mA with  $V_D$  midway between cutoff and the beginning of triode operation. The available supplies are  $\pm 5$  V. For the NMOS transistor,  $V_t = 1.0$  V,  $\lambda = 0$ , and  $k_n = 1$  mA/V<sup>2</sup>. Use a gate-bias resistor of 10 M $\Omega$ . Specify  $R_S$  and  $R_D$  to two significant digits.

**D \*7.94** In an electronic instrument using the biasing scheme shown in Fig. 7.48(c), a manufacturing error reduces  $R_S$  to zero. Let  $V_{DD} = 15$  V,  $R_{G1} = 10$  M $\Omega$ , and  $R_{G2} = 5.1$  M $\Omega$ . What is the value of  $V_G$  created? If supplier specifications allow  $k_n$  to vary from 0.2 to 0.3 mA/V<sup>2</sup> and  $V_t$  to vary from 1.0 V to 1.5 V, what are the extreme values of  $I_D$  that may result? What value of  $R_S$  should have been installed to limit the maximum value of  $I_D$  to 1.5 mA? Choose an appropriate standard 5% resistor value (refer to Appendix J). What extreme values of current now result?

**7.95** An NMOS transistor is connected in the bias circuit of Fig. 7.48(c), with  $V_G = 5$  V and  $R_S = 3$  k $\Omega$ . The transistor has  $V_t = 1$  V and  $k_n = 2$  mA/V<sup>2</sup>. What bias current results? If a transistor for which  $k_n$  is 50% higher is used, what is the resulting percentage increase in  $I_D$ ?

**SIM 7.96** The bias circuit of Fig. 7.48(c) is used in a design with  $V_G = 5$  V and  $R_S = 2$  k $\Omega$ . For a MOSFET with

**SIM** = Multisim/PSpice; \* = difficult problem; \*\* = more difficult; \*\*\* = very challenging; D = design problem

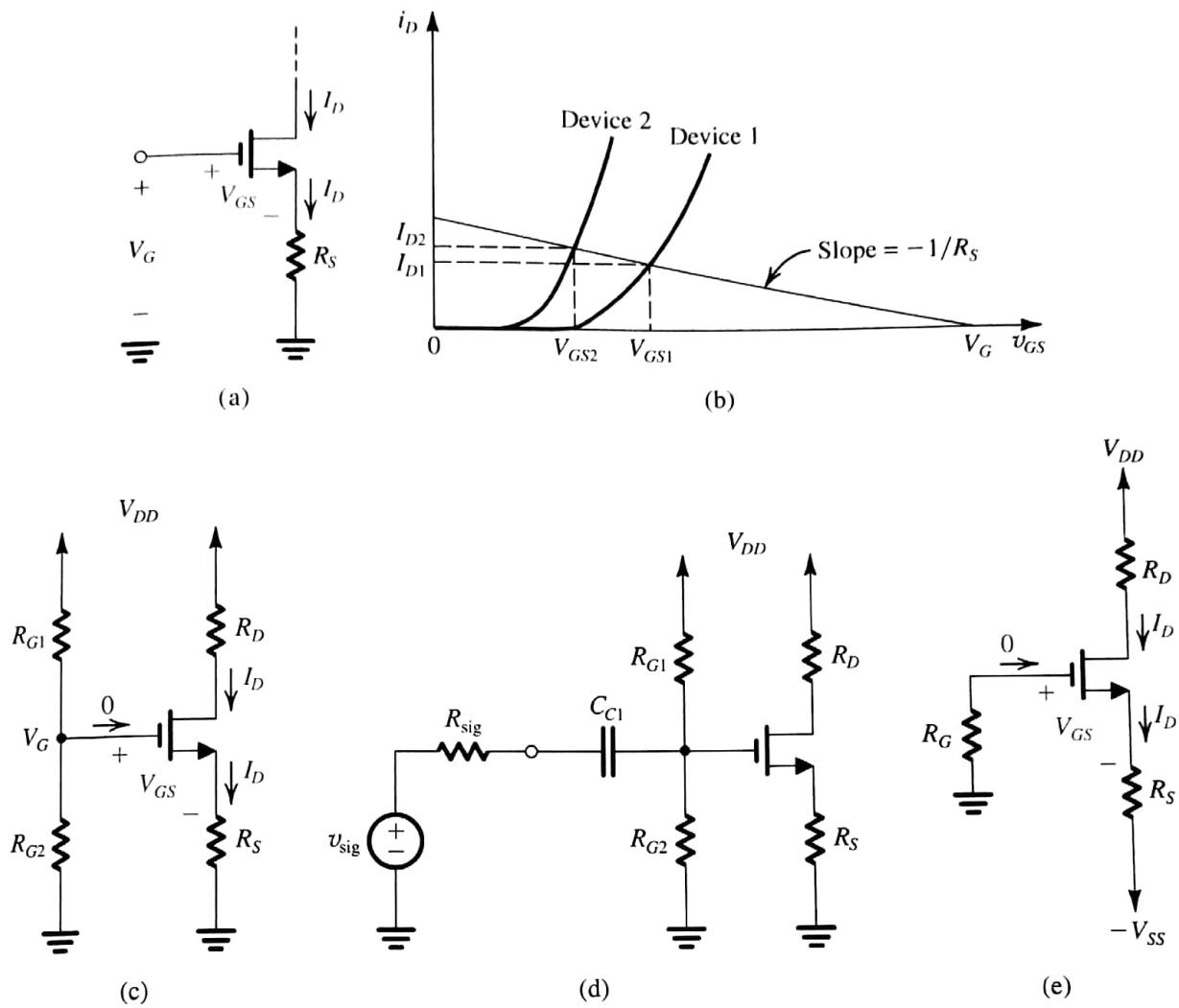

**Figure 7.48** Biasing using a fixed voltage at the gate,  $V_G$ , and a resistance in the source lead,  $R_S$ : (a) basic arrangement; (b) reduced variability in  $I_D$ ; (c) practical implementation using a single supply; (d) coupling of a signal source to the gate using a capacitor  $C_{C1}$ ; (e) practical implementation using two supplies.

through a voltage divider ( $R_{G1}$ ,  $R_{G2}$ ). Since  $I_G = 0$ ,  $R_{G1}$  and  $R_{G2}$  can be selected to be very large (in the megohm range), allowing the MOSFET to present a large input resistance to a signal source that may be connected to the gate through a coupling capacitor, as shown in Fig. 7.48(d). Here capacitor  $C_{C1}$  blocks dc and thus allows us to couple the signal  $v_{sig}$  to the amplifier input without disturbing the MOSFET dc bias point. The value of  $C_{C1}$  should be selected large enough to approximate a short circuit at all signal frequencies of interest. We shall study capacitively coupled MOSFET amplifiers, which are suitable only in discrete-circuit design, in Section 7.5. Finally, note that in the circuit of Fig. 7.48(c), resistor  $R_D$  is selected to be as large as possible to obtain high gain but small enough to allow for the desired signal swing at the drain while keeping the MOSFET in saturation at all times.

When two power supplies are available, as is often the case, the somewhat simpler bias arrangement of Fig. 7.48(e) can be utilized. This circuit is an implementation of Eq. (7.137), with  $V_G$  replaced by  $V_{SS}$ . Resistor  $R_G$  establishes a dc ground at the gate and presents a high input resistance to a signal source that may be connected to the gate through a coupling capacitor.

**SIM 7.101** In the circuit of Fig. 7.50, let  $R_G = 10\text{ M}\Omega$ ,  $R_D = 10\text{ k}\Omega$ , and  $V_{DD} = 10\text{ V}$ . For each of the following two transistors, find the voltages  $V_D$  and  $V_G$ .

- (a)  $V_t = 1\text{ V}$  and  $k_n = 0.5\text{ mA/V}^2$
- (b)  $V_t = 2\text{ V}$  and  $k_n = 1.25\text{ mA/V}^2$

**D 7.102** Using the feedback bias arrangement shown in Fig. 7.50 with a 5-V supply and an NMOS device for which  $V_t = 1\text{ V}$  and  $k_n = 10\text{ mA/V}^2$ , find  $R_D$  to establish a drain current of 0.2 mA.

**D 7.103** Figure P7.103 shows a variation of the feedback-bias circuit of Fig. 7.50. Using a 5-V supply with an NMOS transistor for which  $V_t = 0.8\text{ V}$ ,  $k_n = 8\text{ mA/V}^2$ , and  $\lambda = 0$ , provide a design that biases the transistor at  $I_D = 1\text{ mA}$ , with  $V_{DS}$  large enough to allow saturation operation for a 2-V negative signal swing at the drain. Use  $22\text{ M}\Omega$  as the largest resistor in the feedback-bias network. What values of  $R_D$ ,  $R_{G1}$ , and  $R_{G2}$  have you chosen? Specify all resistors to two significant digits.

 


Figure P7.103

**D 7.104** For the circuit in Fig. 7.51(a), neglect the base current  $I_B$  in comparison with the current in the voltage divider. It is required to bias the transistor at  $I_C = 1\text{ mA}$ , which requires selecting  $R_{B1}$  and  $R_{B2}$  so that  $V_{BE} = 0.710\text{ V}$ . If  $V_{CC} = 3\text{ V}$ , what must the ratio  $R_{B1}/R_{B2}$  be? Now, if  $R_{B1}$  and  $R_{B2}$  are 1% resistors, that is, each can be in the range of 0.99 to 1.01 of its nominal value, what is the range obtained for  $V_{BE}$ ? What is the corresponding range of  $I_C$ ? If  $R_C = 2\text{ k}\Omega$ , what is

the range obtained for  $V_{CE}$ ? Comment on the efficacy of this biasing arrangement.

**D 7.105** It is required to bias the transistor in the circuit of Fig. 7.51(b) at  $I_C = 1\text{ mA}$ . The transistor  $\beta$  is specified to be nominally 100, but it can fall in the range of 50 to 150. For  $V_{CC} = +3\text{ V}$  and  $R_C = 2\text{ k}\Omega$ , find the required value of  $R_B$  to achieve  $I_C = 1\text{ mA}$  for the “nominal” transistor. What is the expected range for  $I_C$  and  $V_{CE}$ ? Comment on the efficacy of this bias design.

**D 7.106** Consider the single-supply bias network shown in Fig. 7.52(a). Provide a design using a 9-V supply in which the supply voltage is equally split between  $R_C$ ,  $V_{CE}$ , and  $R_E$  with a collector current of 0.6 mA. The transistor  $\beta$  is specified to have a minimum value of 90. Use a voltage-divider current of  $I_E/10$ , or slightly higher. Since a reasonable design should operate for the best transistors for which  $\beta$  is very high, do your initial design with  $\beta = \infty$ . Then choose suitable 5% resistors (see Appendix J), making the choice in a way that will result in a  $V_{BB}$  that is slightly higher than the ideal value. Specify the values you have chosen for  $R_E$ ,  $R_C$ ,  $R_1$ , and  $R_2$ . Now, find  $V_B$ ,  $V_E$ ,  $V_C$ , and  $I_C$  for your final design using  $\beta = 90$ .

**D 7.107** Repeat Problem 7.106, but use a voltage-divider current that is  $I_E/2$ . Check your design at  $\beta = 90$ . If you have the data available, find how low  $\beta$  can be while the value of  $I_C$  does not fall below that obtained with the design of Problem 7.106 for  $\beta = 90$ .

**D \*7.108** It is required to design the bias circuit of Fig. 7.52 for a BJT whose nominal  $\beta = 100$ .

- (a) Find the largest ratio  $(R_B/R_E)$  that will guarantee  $I_E$  remains within  $\pm 5\%$  of its nominal value for  $\beta$  as low as 50 and as high as 150.
- (b) If the resistance ratio found in (a) is used, find an expression for the voltage  $V_{BB} \equiv V_{CC}R_2/(R_1 + R_2)$  that will result in a voltage drop of  $V_{CC}/3$  across  $R_E$ .
- (c) For  $V_{CC} = 5\text{ V}$ , find the required values of  $R_1$ ,  $R_2$ , and  $R_E$  to obtain  $I_E = 0.5\text{ mA}$  and to satisfy the requirement for stability of  $I_E$  in (a).
- (d) Find  $R_C$  so that  $V_{CE} = 1.0\text{ V}$  for  $\beta$  equal to its nominal value.

Check your design by evaluating the resulting range of  $I_E$ .

**SIM** = Multisim/PSpice; \* = difficult problem; \*\* = more difficult; \*\*\* = very challenging; D = design problem

- (g) What is the value of the dc base current  $I_B$  at the bias point? Assume  $\beta = 100$ . Characterize the signal current  $i_b$  that will be superimposed on the base current  $I_B$ .
- (h) Dividing the amplitude of  $v_{be}$  by the amplitude of  $i_b$ , evaluate the incremental (or small-signal) input resistance of the amplifier.
- (i) Sketch and clearly label correlated graphs for  $v_{BE}$ ,  $v_{CE}$ ,  $i_C$ , and  $i_B$  versus time. Note that each graph consists of a dc or average value and a superimposed sine wave. Be careful of the phase relationships of the sine waves.

**7.20** The essence of transistor operation is that a change in  $v_{BE}$ ,  $\Delta v_{BE}$ , produces a change in  $i_C$ ,  $\Delta i_C$ . By keeping  $\Delta v_{BE}$  small,  $\Delta i_C$  is approximately linearly related to  $\Delta v_{BE}$ ,  $\Delta i_C = g_m \Delta v_{BE}$ , where  $g_m$  is known as the transistor transconductance. By passing  $\Delta i_C$  through  $R_C$ , an output voltage signal  $\Delta v_o$  is obtained. Use the expression for the small-signal voltage gain in Eq. (7.20) to derive an expression for  $g_m$ . Find the value of  $g_m$  for a transistor biased at  $I_C = 0.5$  mA.

**7.21** The purpose of this problem is to illustrate the application of graphical analysis to the circuit shown in Fig. P7.21. Sketch  $i_C - v_{CE}$  characteristic curves for the BJT for  $i_B = 10 \mu\text{A}$ ,  $20 \mu\text{A}$ ,  $30 \mu\text{A}$ , and  $40 \mu\text{A}$ . Assume the lines to be horizontal (i.e., neglect the Early effect), and let  $\beta = 100$ . For  $V_{CC} = 5$  V and  $R_C = 1$  k $\Omega$ , sketch the load line. What peak-to-peak collector voltage swing will result for  $i_B$  varying

over the range  $10 \mu\text{A}$  to  $40 \mu\text{A}$ ? If the BJT is biased at  $V_{CE} = \frac{1}{2} V_{CC}$ , find the value of  $I_C$  and  $I_B$ . If at this current  $V_{BE} = 0.7$  V and if  $R_B = 100$  k $\Omega$ , find the required value of  $V_{BB}$ .

**\*7.22** Sketch the  $i_C - v_{CE}$  characteristics of an *npn* transistor having  $\beta = 100$  and  $V_A = 100$  V. Sketch characteristic curves for  $i_B = 20 \mu\text{A}$ ,  $50 \mu\text{A}$ ,  $80 \mu\text{A}$ , and  $100 \mu\text{A}$ . For the purpose of this sketch, assume that  $i_C = \beta i_B$  at  $v_{CE} = 0$ . Also, sketch the load line obtained for  $V_{CC} = 10$  V and  $R_C = 1$  k $\Omega$ . If the dc bias current into the base is  $50 \mu\text{A}$ , write the equation for the corresponding  $i_C - v_{CE}$  curve. Also, write the equation for the load line, and solve the two equations to obtain  $V_{CE}$  and  $I_C$ . If the input signal causes a sinusoidal signal of  $30\text{-}\mu\text{A}$  peak amplitude to be superimposed on  $I_B$ , find the corresponding signal components of  $i_C$  and  $v_{CE}$ .

### Section 7.2: Small-Signal Operation and Models

**\*7.23** This problem investigates the nonlinear distortion introduced by a MOSFET amplifier. Let the signal  $v_{gs}$  be a sine wave with amplitude  $V_{gs}$ , and substitute  $v_{gs} = V_{gs} \sin \omega t$  in Eq. (7.28). Using the trigonometric identity  $\sin^2 \theta = \frac{1}{2} - \frac{1}{2} \cos 2\theta$ , show that the ratio of the signal at frequency  $2\omega$  to that at frequency  $\omega$ , expressed as a percentage (known as the second-harmonic distortion) is

$$\text{Second-harmonic distortion} = \frac{1}{4} \frac{V_{gs}}{V_{ov}} \times 100$$

If in a particular application  $V_{gs}$  is 10 mV, find the minimum overdrive voltage at which the transistor should be operated so that the second-harmonic distortion is kept to less than 1%.

**7.24** Consider an NMOS transistor having  $k_n = 10$  mA/V<sup>2</sup>. Let the transistor be biased at  $V_{ov} = 0.2$  V. For operation in saturation, what dc bias current  $I_D$  results? If a 0.02-V signal is superimposed on  $V_{GS}$ , find the corresponding increment in collector current by evaluating the total collector current  $i_D$  and subtracting the dc bias current  $I_D$ . Repeat for a  $-0.02\text{-V}$  signal. Use these results to estimate  $g_m$  of the FET at this bias point. Compare with the value of  $g_m$  obtained using Eq. (7.33).

 


Figure P7.21

**SIM** = Multisim/PSpice; \* = difficult problem; \*\* = more difficult; \*\*\* = very challenging; D = design problem

**The Signal Current in the Drain Terminal** Next, consider the situation with the input signal  $v_{gs}$  applied. The total instantaneous gate-to-source voltage will be

$$v_{GS} = V_{GS} + v_{gs} \quad (7.27)$$

resulting in a total instantaneous drain current  $i_D$ ,

$$\begin{aligned} i_D &= \frac{1}{2} k_n (V_{GS} + v_{gs} - V_t)^2 \\ &= \frac{1}{2} k_n (V_{GS} - V_t)^2 + k_n (V_{GS} - V_t) v_{gs} + \frac{1}{2} k_n v_{gs}^2 \end{aligned} \quad (7.28)$$

The first term on the right-hand side of Eq. (7.28) can be recognized as the dc bias current  $I_D$  (Eq. 7.25). The second term represents a current component that is directly proportional to the input signal  $v_{gs}$ . The third term is a current component that is proportional to the square of the input signal. This last component is undesirable because it represents *nonlinear distortion*. To reduce the nonlinear distortion introduced by the MOSFET, the input signal should be kept small so that

$$\frac{1}{2} k_n v_{gs}^2 \ll k_n (V_{GS} - V_t) v_{gs}$$

resulting in

$$v_{gs} \ll 2(V_{GS} - V_t) \quad (7.29)$$

or, equivalently,

$$v_{gs} \ll 2V_{OV} \quad (7.30)$$

If this **small-signal condition** is satisfied, we may neglect the last term in Eq. (7.28) and express  $i_D$  as

$$i_D \simeq I_D + i_d \quad (7.31)$$

where

$$i_d = k_n (V_{GS} - V_t) v_{gs}$$

The parameter that relates  $i_d$  and  $v_{gs}$  is the MOSFET **transconductance**  $g_m$ ,

$$g_m \equiv \frac{i_d}{v_{gs}} = k_n (V_{GS} - V_t) \quad (7.32)$$

or in terms of the overdrive voltage  $V_{OV}$ ,

$$g_m = k_n V_{OV} \quad (7.33)$$

Figure 7.11 presents a graphical interpretation of the small-signal operation of the MOSFET amplifier. Note that  $g_m$  is equal to the slope of the  $i_D$ - $v_{GS}$  characteristic at the bias point,

$$g_m \equiv \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS}=V_{GS}} \quad (7.34)$$

This is the formal definition of  $g_m$ , which can be shown to yield the expressions given in Eqs. (7.32) and (7.33).



**7.25** Consider the FET amplifier of Fig. 7.10 for the case  $V_t = 0.4$  V,  $k_n = 5$  mA/V<sup>2</sup>,  $V_{GS} = 0.6$  V,  $V_{DD} = 1.8$  V, and  $R_D = 10$  k $\Omega$ .

- (a) Find the dc quantities  $I_D$  and  $V_{DS}$ .
- (b) Calculate the value of  $g_m$  at the bias point.
- (c) Calculate the value of the voltage gain.
- (d) If the MOSFET has  $\lambda = 0.1$  V<sup>-1</sup>, find  $r_o$  at the bias point and calculate the voltage gain.

**D \*7.26** An NMOS amplifier is to be designed to provide a 0.20-V peak output signal across a 20-k $\Omega$  load that can be used as a drain resistor. If a gain of at least 10 V/V is needed, what  $g_m$  is required? Using a dc supply of 1.8 V, what values of  $I_D$  and  $V_{OV}$  would you choose? What  $W/L$  ratio is required if  $\mu_n C_{ox} = 200$   $\mu$ A/V<sup>2</sup>? If  $V_t = 0.4$  V, find  $V_{GS}$ .

**D \*7.27** In this problem we investigate an optimum design of the CS amplifier circuit of Fig. 7.10. First, use the voltage gain expression  $A_v = -g_m R_D$ , together with Eq. (7.42) for  $g_m$  to show that

$$A_v = -\frac{2I_D R_D}{V_{OV}} = -\frac{2(V_{DD} - V_{DS})}{V_{OV}}$$

Next, let the maximum positive input signal be  $\hat{v}_i$ . To keep the second-harmonic distortion to an acceptable level, we bias the MOSFET to operate at an overdrive voltage  $V_{OV} \gg \hat{v}_i$ . Let  $V_{OV} = m\hat{v}_i$ . Now, to maximize the voltage gain  $|A_v|$ , we design for the lowest possible  $V_{DS}$ . Show that the minimum  $V_{DS}$  that is consistent with allowing a negative signal voltage swing at the drain of  $|\hat{v}_i|$  while maintaining saturation-mode operation is given by

$$V_{DS} = \frac{V_{OV} + \hat{v}_i + 2V_{DD}(\hat{v}_i/V_{OV})}{1 + 2(\hat{v}_i/V_{OV})}$$

Now, find  $V_{OV}$ ,  $V_{DS}$ ,  $A_v$ , and  $\hat{v}_o$  for the case  $V_{DD} = 2.5$  V,  $\hat{v}_i = 20$  mV, and  $m = 15$ . If it is desired to operate this transistor at  $I_D = 200$   $\mu$ A, find the values of  $R_D$  and  $W/L$ , assuming that for this process technology  $k'_n = 100$   $\mu$ A/V<sup>2</sup>.

**7.28** In the table below, for MOS transistors operating under a variety of conditions, complete as many entries as possible. Although some data is not available, it is always possible to calculate  $g_m$  using one of Eqs. (7.40), (7.41), or (7.42). Assume  $\mu_n = 500$  cm<sup>2</sup>/V $\cdot$ s,  $\mu_p = 250$  cm<sup>2</sup>/V $\cdot$ s, and  $C_{ox} = 0.4$  fF/ $\mu$ m<sup>2</sup>.

Case	Type	$I_D$ (mA)	Voltages (V)			Dimensions ( $\mu$ m)				
			$ V_{GS} $	$ V_t $	$V_{OV}$	$W$	$L$	$W/L$	$k'(W/L)$	$g_m$ (mA/V)
a	N	1	3	2	0.5	50	1	25	0.5	
b	N	1		0.7						
c	N	10								
d	N	0.5			0.5					
e	N	0.1				10	2			
f	N		1.8	0.8		40	4			
g	P	0.5				4000	2	25	0.5	
h	P		3	1						
i	P	10			4					
j	P	10			1	30	3			
k	P				5					
l	P								0.08	

**SIM** = Multisim/PSpice; \* = difficult problem; \*\* = more difficult; \*\*\* = very challenging; D = design problem

7.29 An NMOS technology has  $\mu_n C_{ox} = 250 \mu\text{A}/\text{V}^2$  and  $V_t = 0.5 \text{ V}$ . For a transistor with  $L = 0.5 \mu\text{m}$ , find the value of  $W$  that results in  $g_m = 2 \text{ mA}/\text{V}$  at  $I_D = 0.25 \text{ mA}$ . Also, find the required  $V_{GS}$ .

7.30 For the NMOS amplifier in Fig. P7.30, replace the transistor with its T equivalent circuit, assuming  $\lambda = 0$ . Derive expressions for the voltage gains  $v_s/v_i$  and  $v_d/v_i$ .

 


Figure P7.30

**SIM 7.31** In the circuit of Fig. P7.31, the NMOS transistor has  $|V_t| = 0.5 \text{ V}$  and  $V_A = 50 \text{ V}$  and operates with  $V_D = 1 \text{ V}$ . What is the voltage gain  $v_o/v_i$ ? What do  $V_D$  and the gain become for  $I$  increased to  $1 \text{ mA}$ ?

 


Figure P7.31

7.32 For a  $0.18\text{-}\mu\text{m}$  CMOS fabrication process:  $V_m = 0.5 \text{ V}$ ,  $V_p = -0.5 \text{ V}$ ,  $\mu_n C_{ox} = 400 \mu\text{A}/\text{V}^2$ ,  $\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$ ,  $C_{ox} = 8.6 \text{ fF}/\mu\text{m}^2$ ,  $V_A$  ( $n$ -channel devices)  $= 5L$  ( $\mu\text{m}$ ), and  $|V_A|$  ( $p$ -channel devices)  $= 6L$  ( $\mu\text{m}$ ). Find the small-signal model parameters ( $g_m$  and  $r_o$ ) for both an NMOS and a PMOS transistor having  $W/L = 10 \mu\text{m}/0.5 \mu\text{m}$  and operating at  $I_D = 100 \mu\text{A}$ . Also, find the overdrive voltage at which each device must be operating.

\*7.33 Figure P7.33 shows a discrete-circuit amplifier. The input signal  $v_{sig}$  is coupled to the gate through a very large capacitor (shown as infinite). The transistor source is connected to ground at signal frequencies via a very large capacitor (shown as infinite). The output voltage signal that develops at the drain is coupled to a load resistance via a very large capacitor (shown as infinite). All capacitors behave as short circuits for signals and as open circuits for dc.

- (a) If the transistor has  $V_t = 1 \text{ V}$ , and  $k_n = 4 \text{ mA}/\text{V}^2$ , verify that the bias circuit establishes  $V_{GS} = 1.5 \text{ V}$ ,  $I_D = 0.5 \text{ mA}$ , and  $V_D = +7.0 \text{ V}$ . That is, assume these values, and verify that they are consistent with the values of the circuit components and the device parameters.
- (b) Find  $g_m$  and  $r_o$  if  $V_A = 100 \text{ V}$ .
- (c) Draw a complete small-signal equivalent circuit for the amplifier, assuming all capacitors behave as short circuits at signal frequencies.
- (d) Find  $R_m$ ,  $v_{gs}/v_{sig}$ ,  $v_o/v_{gs}$ , and  $v_o/v_{sig}$ .

 


Figure P7.33

**SIM** = Multisim/PSpice; \* = difficult problem; \*\* = more difficult; \*\*\* = very challenging; D = design problem