

**PROBLEM SET #8**

Issued: Friday, October 19, 2018

Due: Friday, October 26, 2018 at 12:00 noon via **Gradescope**.

1. Sedra & Smith, Problem 7.38
2. Sedra & Smith, Problem 7.58
3. Sedra & Smith, Problem 10.16
4. Sedra & Smith, Problem 10.17
5. Sedra & Smith, Problem 10.25
6. a) Find the Q-point for the amplifier in Figure PS8.1.  $V_A = 100V$ ,  $\beta_F = 100$ ,  $V_{CC} = +12V$ ,  $V_{EE} = -12V$ ,  $R_S = 1k\Omega$ ,  $R_1 = 10k\Omega$ ,  $R_2 = 5k\Omega$ ,  $R_3 = 24k\Omega$ ,  $R_E = 4k\Omega$ ,  $R_C = 6k\Omega$  and  $R_F = 100M\Omega$ . Assume all the capacitors have infinite capacitance. b) Determine the gain  $\frac{v_o}{v_s}$ . (Hint: Make proper approximation).
7. Figure PS8.1 shows a CE amplifier with a feedback resistor  $R_F$ .  $V_A = 100V$ ,  $\beta_F = 100$ ,  $V_{CC} = 12V$ ,  $V_{EE} = -12V$ ,  $R_S = 1k\Omega$ ,  $R_1 = 10k\Omega$ ,  $R_2 = 5k\Omega$ ,  $R_3 = 24k\Omega$ ,  $R_E = 4k\Omega$ ,  $R_C = 6k\Omega$ ,  $R_F = 10k\Omega$ . Assume all the capacitors have infinite capacitance. Determine the gain  $\frac{v_o}{v_s}$ .
8. A BJT with  $C_{\mu 0} = 2pF$  is biased at a Q-point of (2mA, 5V). What is the forward-transit time  $\tau_F$  if  $f_T = 500MHz$ ,  $\phi_{jc} = 0.9V$ , and  $C_{je} = 7pF$ ?

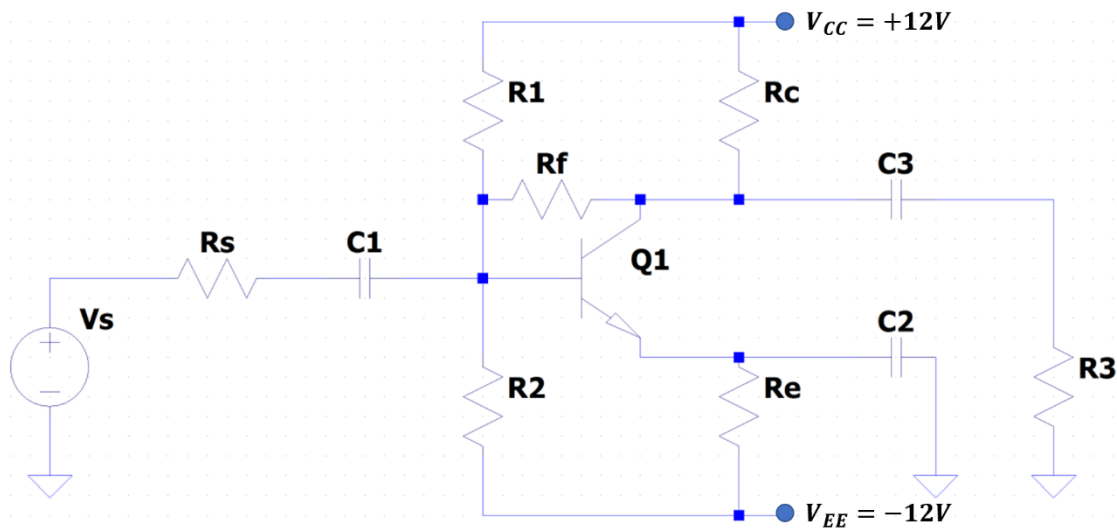


Figure PS8.1