

PROBLEM SET #9*Issued: Friday, October 26, 2018**Due: Friday, November 2, 2018, at 12:00 noon via Gradescope.*

1. Sedra & Smith, Problem 10.2
2. Sedra & Smith, Problem 10.6
3. Sedra & Smith, Problem 10.29
4. For the amplifier in Figure PS9.1, assume that M_1 has the properties listed in Table PS9.1. First, find values for each of the MOSFET internal capacitances C_{GS} , C_{GD} , C_{DB} and C_{SB} assuming that the body terminal is grounded. Then find the voltage gain A_v , the current gain A_i , input and output resistances R_{in} & R_{out} , upper and lower corner frequencies f_L & f_H , and the maximum amplitude of the signal source v_s .

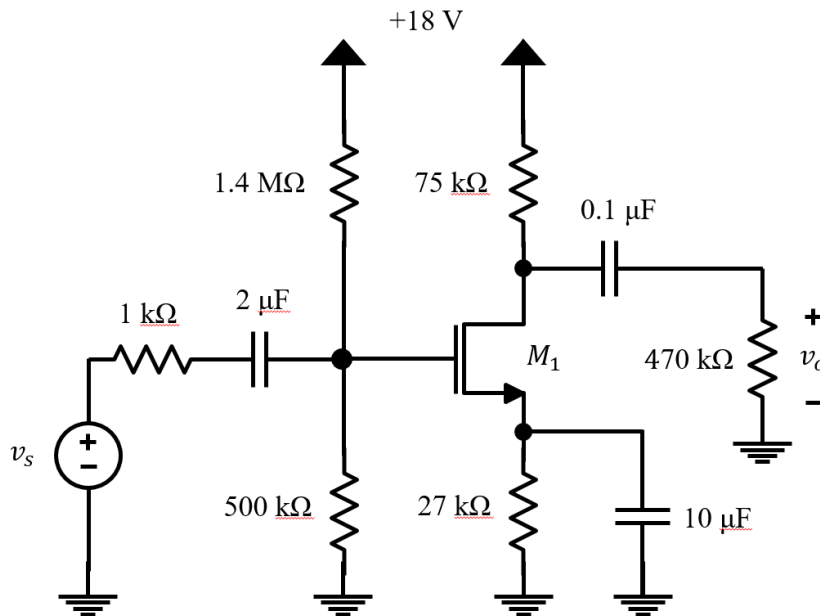


Figure PS9.1

PARAMETER	VALUE	UNIT
W	10	μm
L	1	μm
μ_n	450	$\text{cm}^2/(\text{V}\cdot\text{s})$
C_{ox}''	0.5	$\text{fF}/\mu\text{m}^2$
V_{tn}	1	V
L_{ov}	0.05	μm
C_{db0}	20	fF
C_{sb0}	20	fF
V_0	0.7	V

Table PS9.1

5. For the amplifier in Figure PS9.2, assume that Q_1 has $\beta = 125$, $V_A = 50$ V, $C_{jc,0} = 1.0$ pF, $C_{je,0} = 3.5$ pF, $V_{bi,c} = 0.9$ V, $V_{bi,e} = 1.0$ V, and $\tau_F = 1$ ns. You should also calculate the collector-to-substrate capacitance C_{CS} assuming $C_{CS0} = 20$ fF and $V_{bi(\text{collector-substrate})} = 0.65$ V. Find A_v , A_i , R_{in} , R_{out} , f_L , f_H and the maximum amplitude of the signal source v_s .

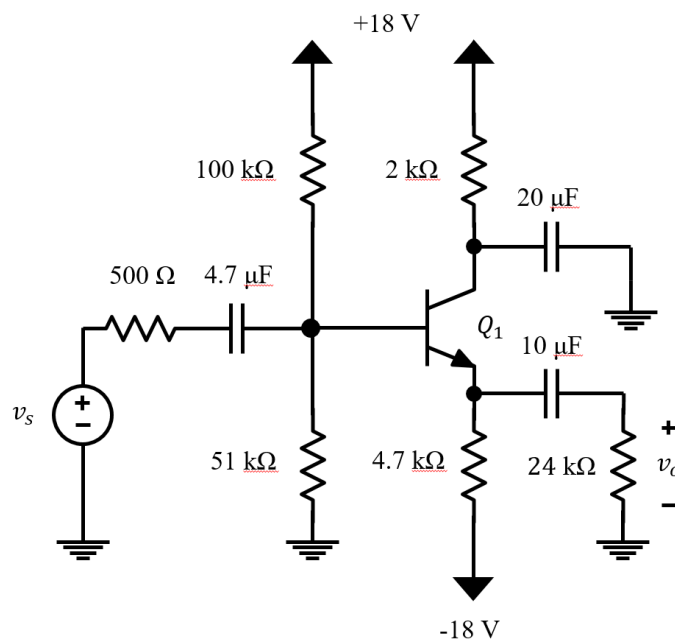


Figure PS9.2

6. For the amplifier in Figure PS9.3, assume that M_1 has $k_p = 200 \mu\text{A}/\text{V}^2$ and $V_{tp} = -1 \text{ V}$. Find A_v , A_i , R_{in} , R_{out} and the maximum amplitude of the signal source v_s .

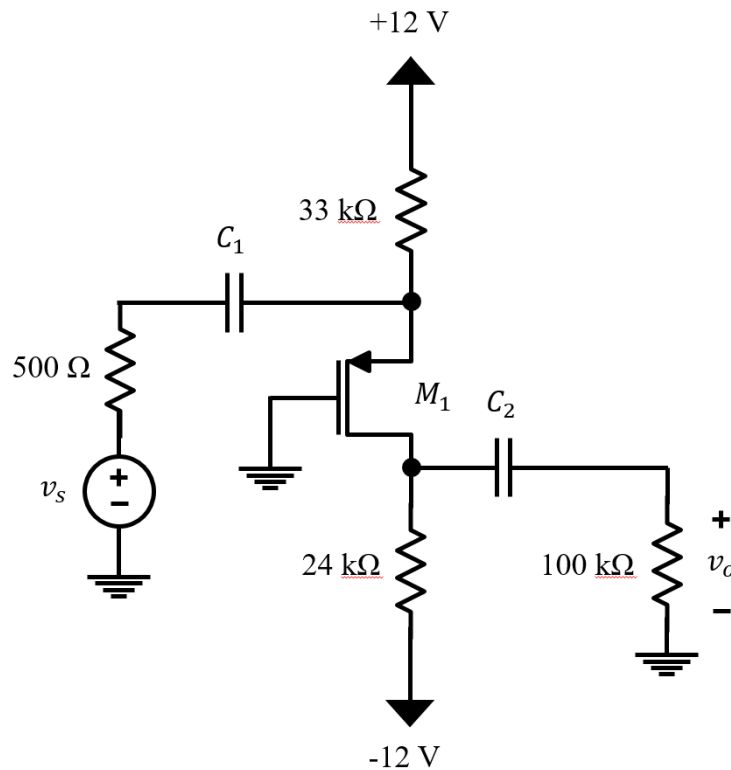


Figure PS9.3

7. A single-transistor amplifier is needed that has a gain of 52 dB and an input resistance of 1 M Ω . What is the preferred choice of amplifier topology? Explain your reasoning for making this selection.
8. A single-transistor amplifier is needed that has a gain of approximately 0 dB and an input resistance of 25 M Ω with a load resistor of 10 k Ω . What is the preferred choice of amplifier topology? Explain your reasoning for making this selection.
9. A single-transistor amplifier is needed that has a gain of approximately +10 V/V and an input resistance of 2 k Ω . What is the preferred choice of amplifier topology? Explain your reasoning for making this selection.