

EE 105 | Discussion 10

Kieran Peleaux & Ali Ameri

Discussion Outline

- [Lab 5] Attenuation network
- [Homework 8] Problem 7 – Feedback Resistor
- [Exercises]

Attenuation Network

First, let's assume our amplifier meets the gain spec.

→ Need to determine max input signal amplitude

$$|v_o| = 1.5\text{V} \rightarrow 3\text{V}_{pp}$$

$$|v_i| = \frac{|v_o|}{A_v} = \frac{3\text{V}_{pp}}{(270\text{V/V})} = 0.011\text{V} < V_{sig, min} = 50\text{mV}$$

→ We need a smaller input amplitude than the minimum setting on our function generators!

→ Solution:

- Insert an attenuation network



$$V_{out} = a V_{in}$$


where $a < 1$

Attenuation Network


- Don't forget ~~input~~ ^{source} impedance!

Ideally, $R_s = 0$

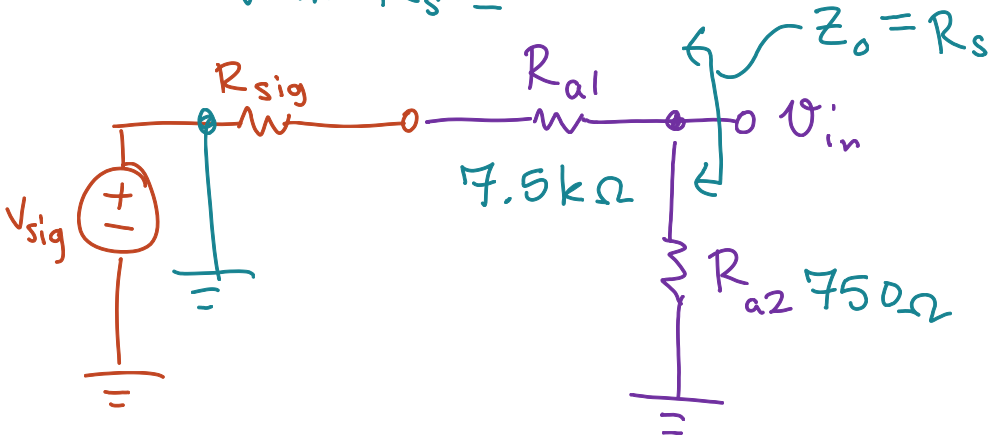→ Need to demonstrate that amplifier works with $R_s \geq 680\Omega$


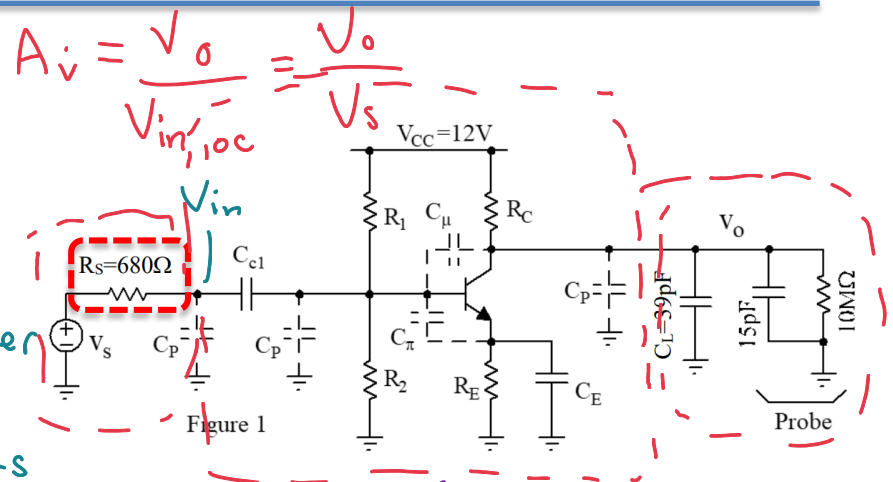
$$R_s = (R_1 + R_{sig}) \parallel R_2 \approx 700\Omega$$



$$A_v = \frac{V_o}{V_{in,loc}} \approx \frac{V_o}{V_s}$$

$$v_{in} = a V_{sig} \quad (|V_{sig}| = 50\text{mV})$$

$$a \leq 0.22$$

$$a = \frac{R_2}{R_1 + R_2} = \frac{1}{10}$$

Attenuation Network

$$v_{in,loaded} = \frac{(R_1 \parallel R_2)}{R_s + (R_1 \parallel R_2)} (a v_{sig})$$

- How to determine the gain of the amplifier
 - Measure the **CORRECT** input signal


× Don't use $v_{in}/v_{atten.}$ as your input signal when calculating A_v (i.e. $A_v \neq \frac{v_o}{v_{in}}$)

✓ Do use $a \cdot v_{sig}$ as input signal when calculating gain

Because when amplifier is connected, v_{in} is loaded & $\neq a v_{sig}$

$$A_v = \frac{v_o}{(a v_{sig})} = \left(\frac{v_o}{v_{in}} \right) \left(\frac{v_{in}}{a v_{sig}} \right)$$

$> A_v$ < 1

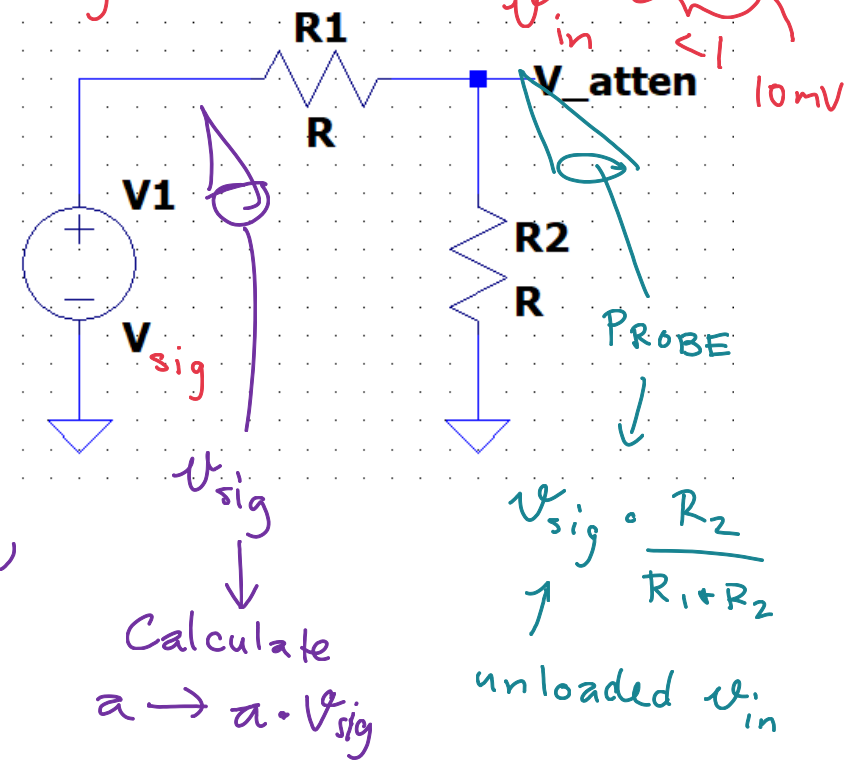

Miller Effect



$$C_{in} = (1 - A_v) * C_{ft} \quad \text{feed-through}$$

$$C \triangleq \frac{\Delta Q}{\Delta V} \rightarrow C_{ft} = \frac{\Delta Q}{v_i - v_o}$$

$$v_o = \underbrace{-g_m r_o}_{A_v} v_i = A_v v_i$$

$$\Delta Q = C_{ft} (-A_v v_i + v_i) = C_{ft} v_i (1 - A_v)$$
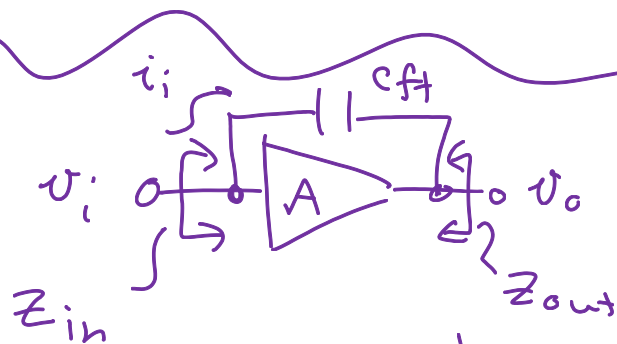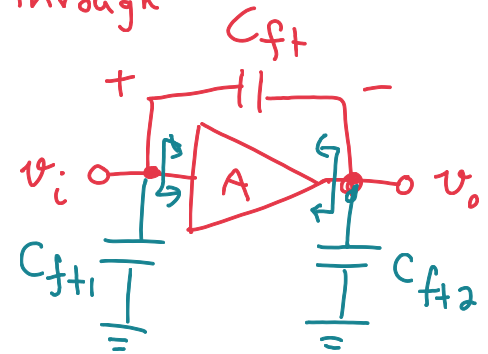
$$C_{ft1} = \frac{\Delta Q}{\Delta v_i} = C_{ft} (1 - A_v) / C_{ft} = C_{ft} (1 - \frac{1}{A_v}) = C_{ft} \left(\frac{A-1}{A} \right)$$



$$Z_{in} = \frac{v_i}{i_i} = \frac{v_i}{(v_i - v_o) \left(\frac{1}{s C_{ft}} v_i (1 - A_v) \right) \cdot s C_{ft}} = \frac{v_i}{v_i (1 - A_v) \cdot s C_{ft}}$$

$$Z_{out} = \frac{1}{s [C_{ft} (1 - \frac{1}{A_v})]}$$

$$Z_{in} = \frac{1}{s (C_{ft} \cdot (1 - A_v))}$$

Miller Effect

$$C_{in} = (1 - A_v) * C_{ft}$$

$$A_v = -g_m (r_o \parallel R) \approx -g_m R$$

$$C_{in} = C_{gs} + C_{gd}(1 - A_v)$$



$$= C_{gs} + C_{gd}(1 + g_m R)$$

$$g_m \triangleq \frac{i_d}{v_{gs}}, v_1 \neq v_{gs}$$

$$G_m = \frac{g_m}{1 + g_m R_2}$$

$$G_m \triangleq \frac{i_d}{v_1} \approx \frac{1}{R_2}$$

if $g_m R_2 \gg 1$

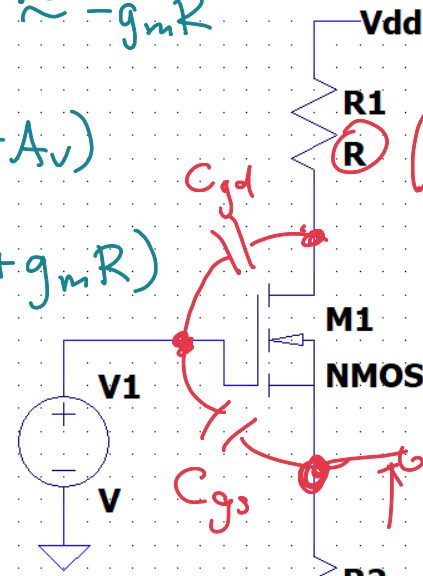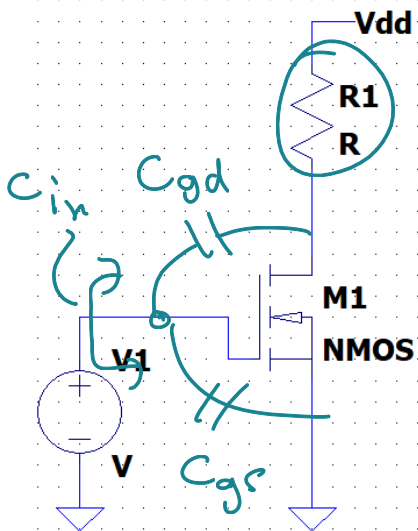

$$C_{gs1} = C_{gs}(1 - A_v)$$

$$= 0$$

$$C_{gd1} = C_{gd}(1 - (-1)) = 2C_{gd}$$


$$\frac{v_s}{v_g} \approx 1$$

$$C_{in} = 2C_{gd}$$

$$A_v = -G_m R_1 = -\frac{1}{R_2} R_1 = -1$$


Miller Effect

$$C_{in} = (1 - A_v) * C_{ft}$$

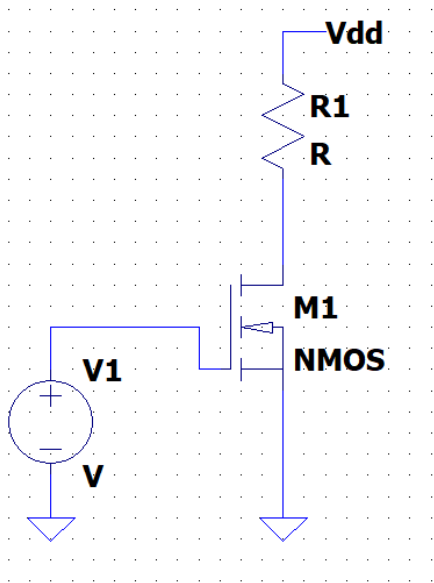


Miller Effect

$$C_{in} = (1 - A_v) * C_{ft}$$

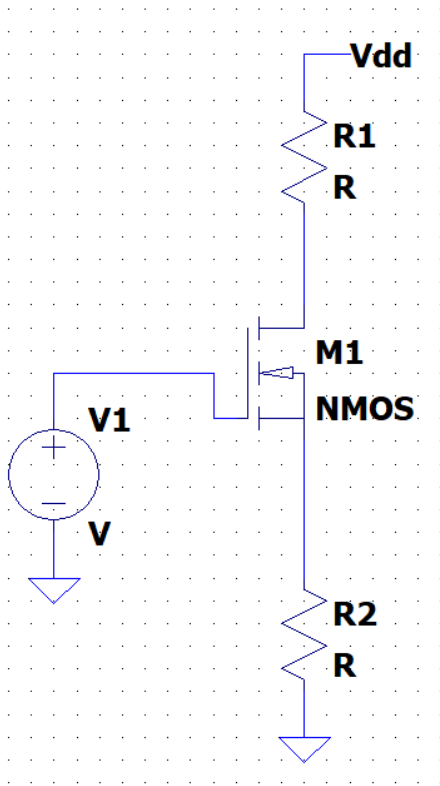

Miller Effect

$$C_{in} = (1 - A_v) * C_{ft}$$

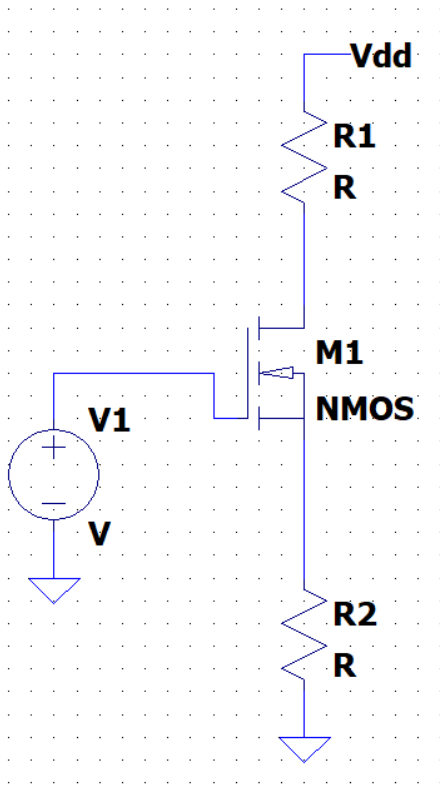

CE Amp w/ Feedback Resistor

- Impact of adding a feedback resistor
 - Change the Q-point
 - Change the small-signal gain

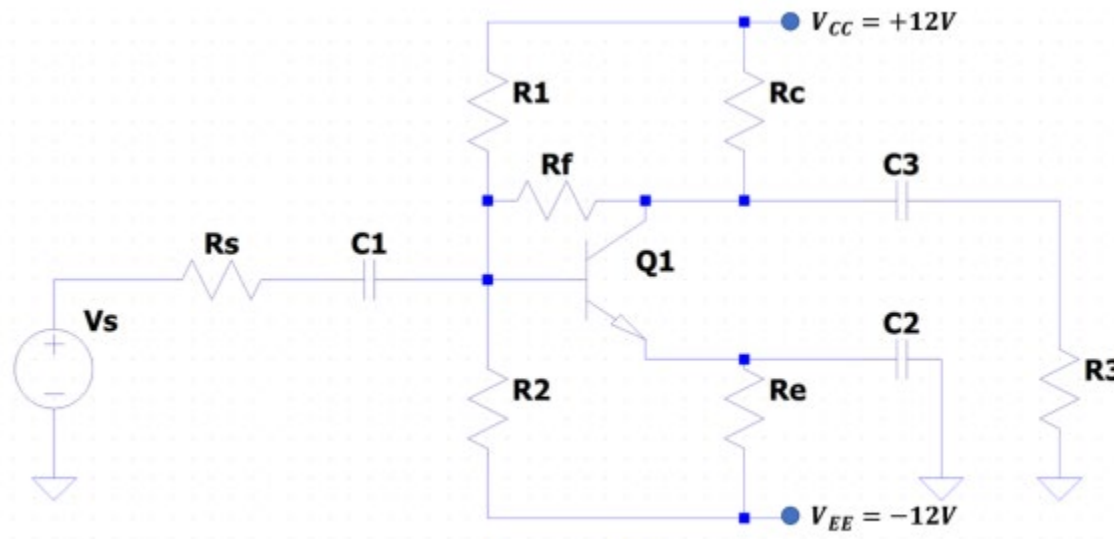


Figure PS8.1

CE Amp w/ Feedback Resistor

- Common use of this circuit
 - Trans-Impedance Amplifier

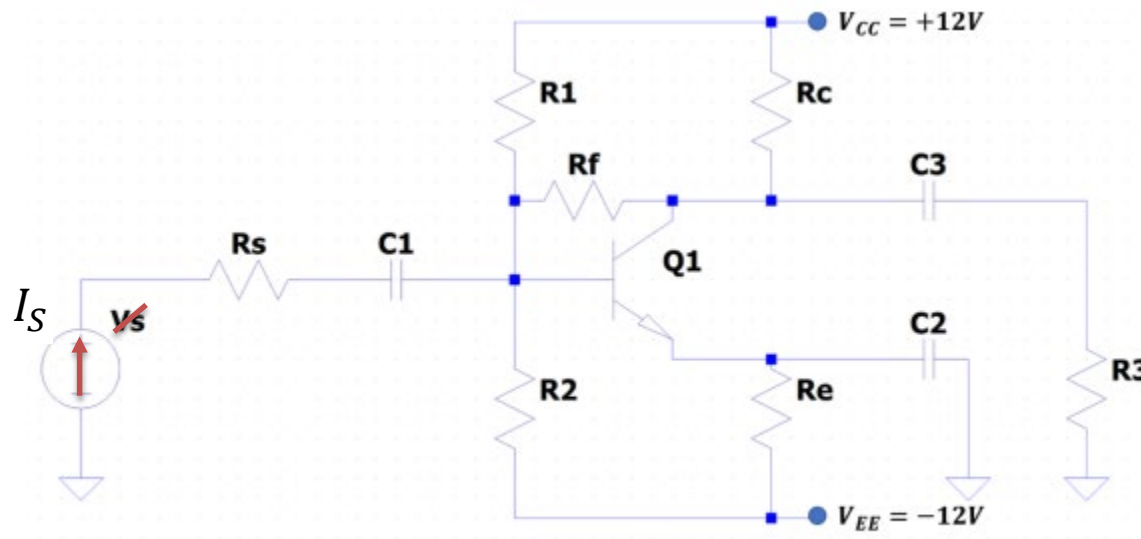


Figure PS8.1