

# EE 105 | Discussion 4

Ali Ameri & Kieran Peleaux


# Discussion Outline

---

- Offset current (i.e., what happens when we have different input bias currents on each input?)
- Design constraints


# Nonideal Op Amps | Input Bias Current

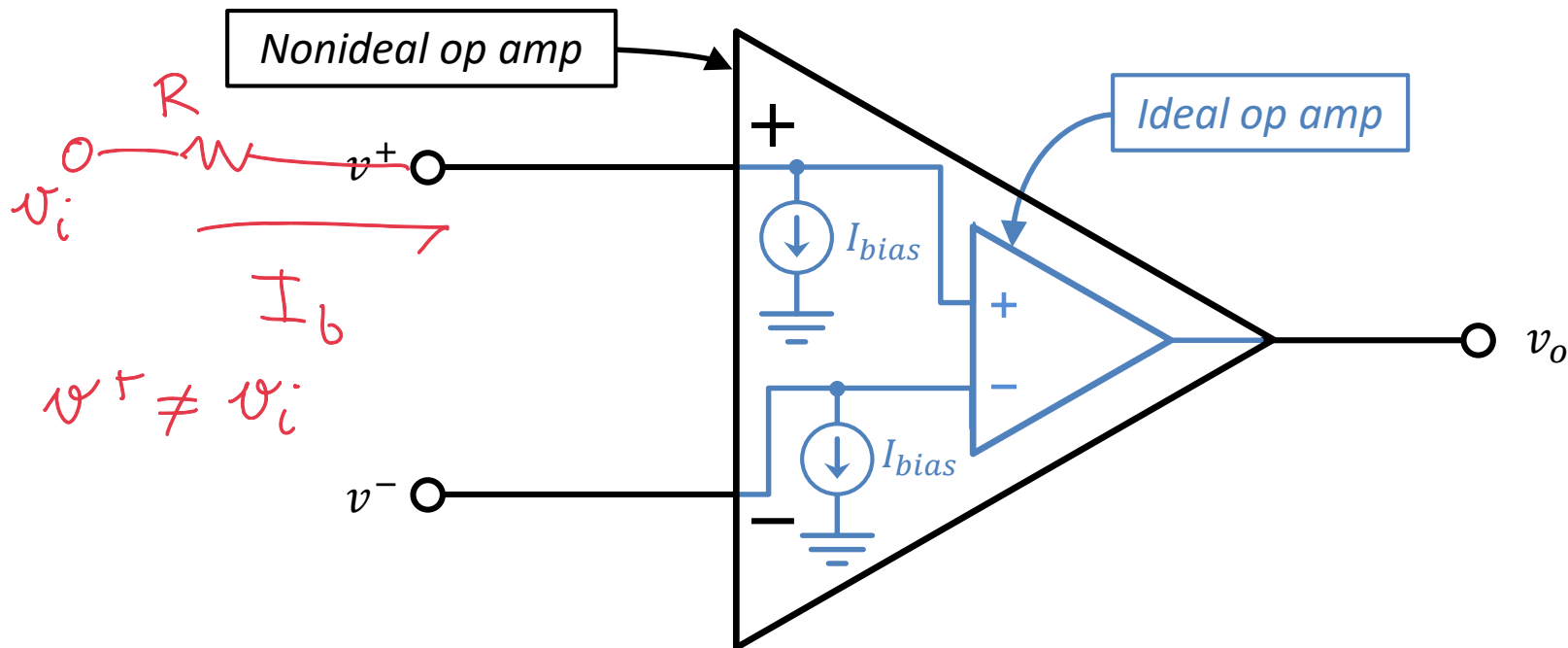Remember the model for input bias current



# Nonideal Op Amps | Bias Current Compensation

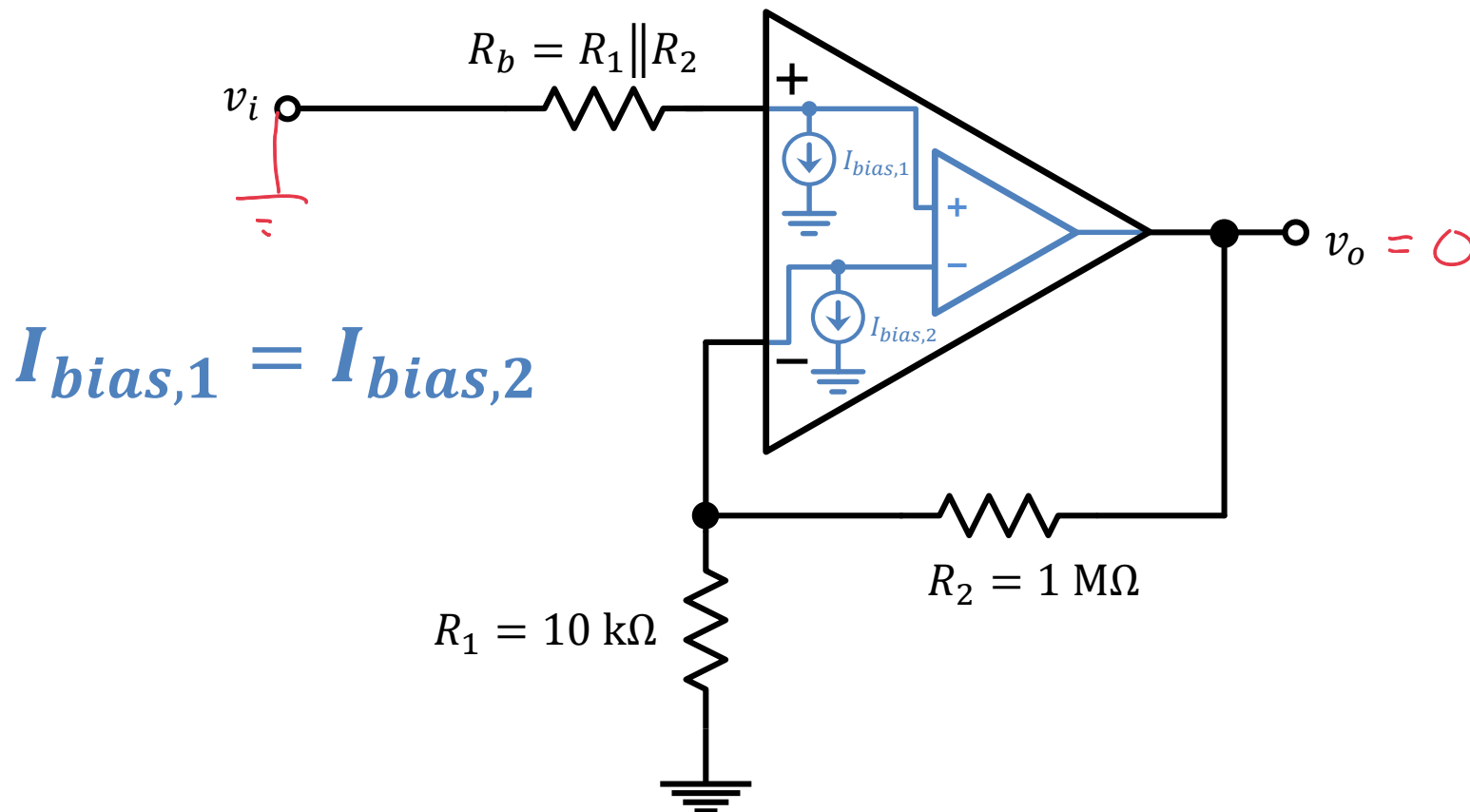
Last week, we found out we could compensate for this bias current—*this only works if the currents are matched!*



# Nonideal Op Amps | Offset Current

Now, consider an offset current that is 10% of  $I_{bias,1}$   
→ What's the resulting  $v_o$  (ignoring any  $V_{OS}$ )?

$$I_{bias,1} = 200 \text{ nA}$$

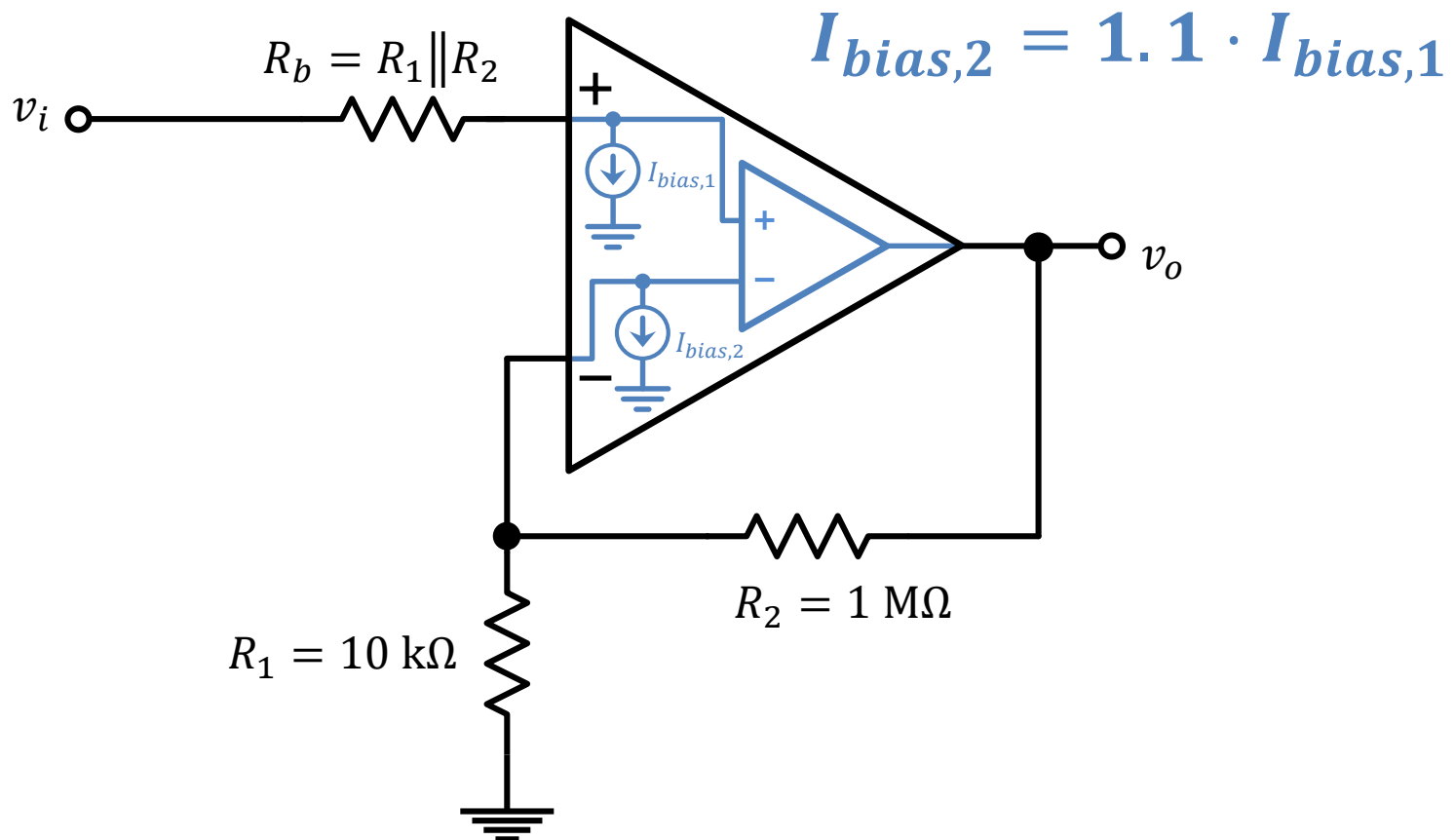


# Nonideal Op Amps | Current Offset

Now, consider an offset current that is 10% of  $I_{bias}$   
 → What's the resulting  $v_o$  (ignoring any  $V_{OS}$ )?

Using superposition:


① OC  $I_{b,1}$  sources

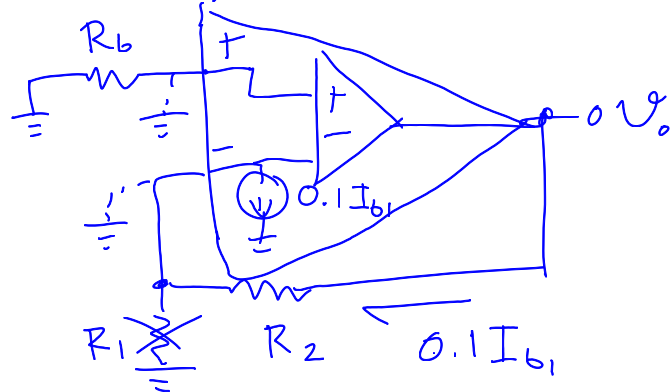

$$v_o = v^- + (0.1 I_{b,1}) R_2 = 20 \text{ mV}$$

② OC red I sources

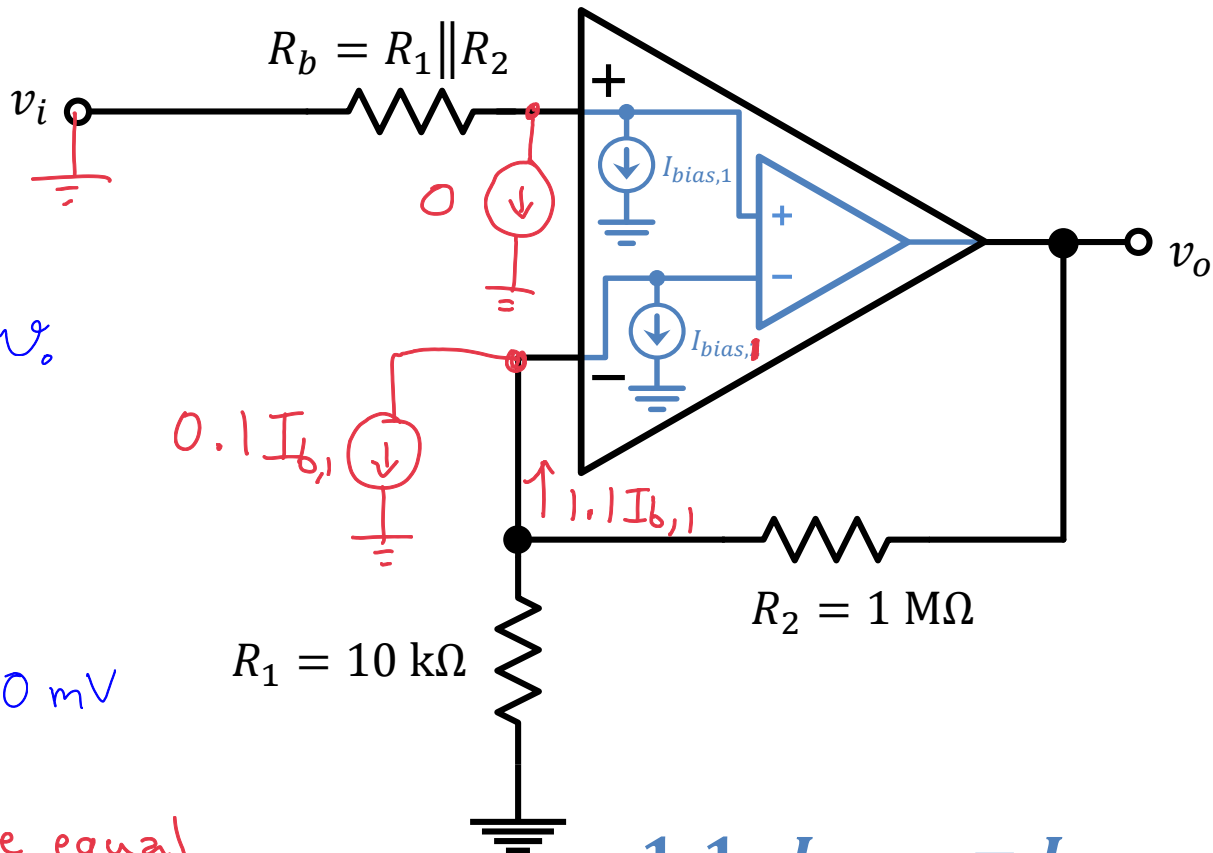↳ input bias currents are equal  
 w/  $R_b \rightarrow v_o = 0$



$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 1 \text{ M}\Omega$$

$$1.1 \cdot I_{bias,1} = I_{bias,2}$$

$$v_{o,total} = 20 \text{ mV} + 0 = \underline{20 \text{ mV}}$$

# Nonideal Op Amps | Voltage & Current Offsets

Now include previous  $V_{OS} = 2 \text{ mV}$  &  $I_{OS} = 0.1 \cdot I_{bias}$  to find the **worst-case** dc voltage at the output in this compensated circuit




From last week:

if  $V_{OS} = 2 \text{ mV}$

$\hookrightarrow v_o = 200 \text{ mV}$

worst-case  $v_o = 200 + 20 \text{ mV}$

$= 220 \text{ mV}$

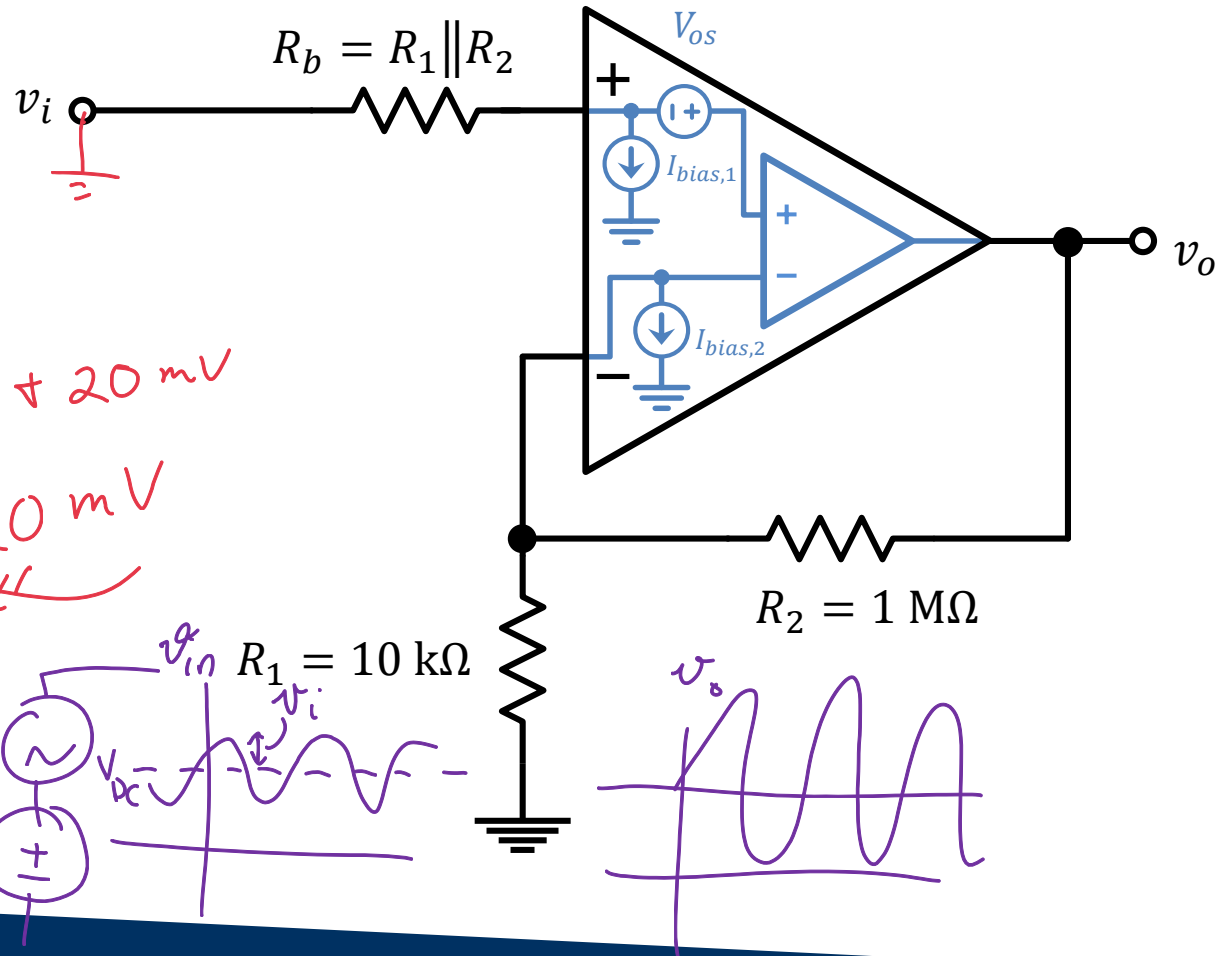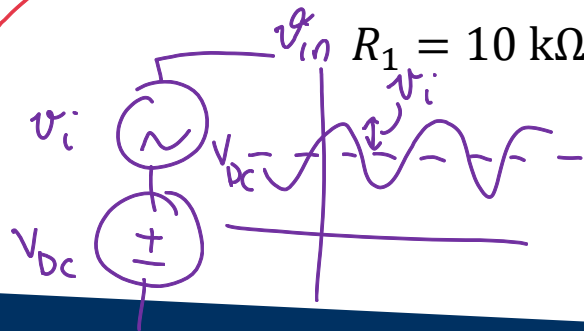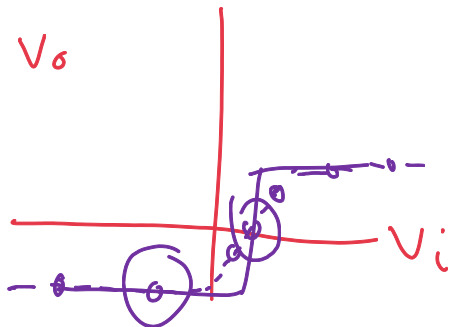


# Constrained Op Amp Design

---

Let's look at how you might be constrained by a COTS (commercial off-the-shelf) part when trying to design a circuit

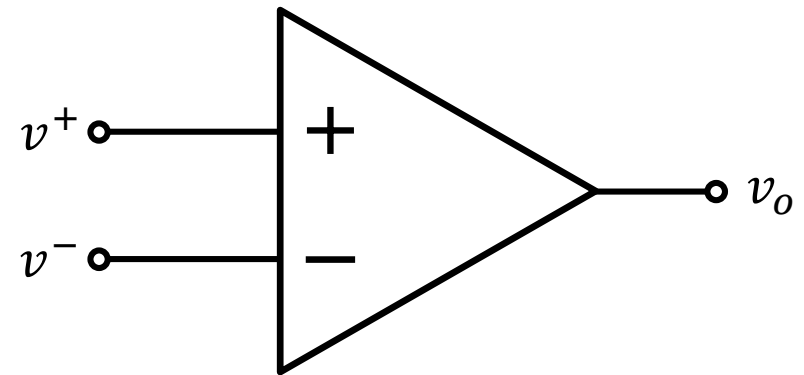- ❑  $f_t = 20 \text{ MHz}$
- ❑ Slew rate,  $SR = 10 \frac{V}{\mu s}$
- ❑ Output saturation,  $V_{o,max} = 10 \text{ V}$





# Constrained Op Amp Design

Using the noninverting configuration with

- $A_v = 10 \frac{V}{V}$
- $v_i = 0.5 V \rightarrow v_o = 5 V$

$f_t = 20 \text{ MHz}$      $v_o(t) = (5V) \sin(\omega t)$

$SR = 10 \frac{V}{\mu s}$

$V_{o,max} = 10 V$


$$SR \geq \frac{dv_o(t)}{dt} = \omega v_o \cos(\omega t) = \omega (A_v v_i) \cos(\omega t)$$

$$\left. \frac{dv_o(t)}{dt} \right|_{\max} = \omega_{\max} A_v v_i = 10 \text{ V}/\mu s$$

$$\omega_{\max} = 2 \times 10^6 \text{ rad/sec}$$

$$f_{\max} = 318 \text{ kHz} \ll f_t$$

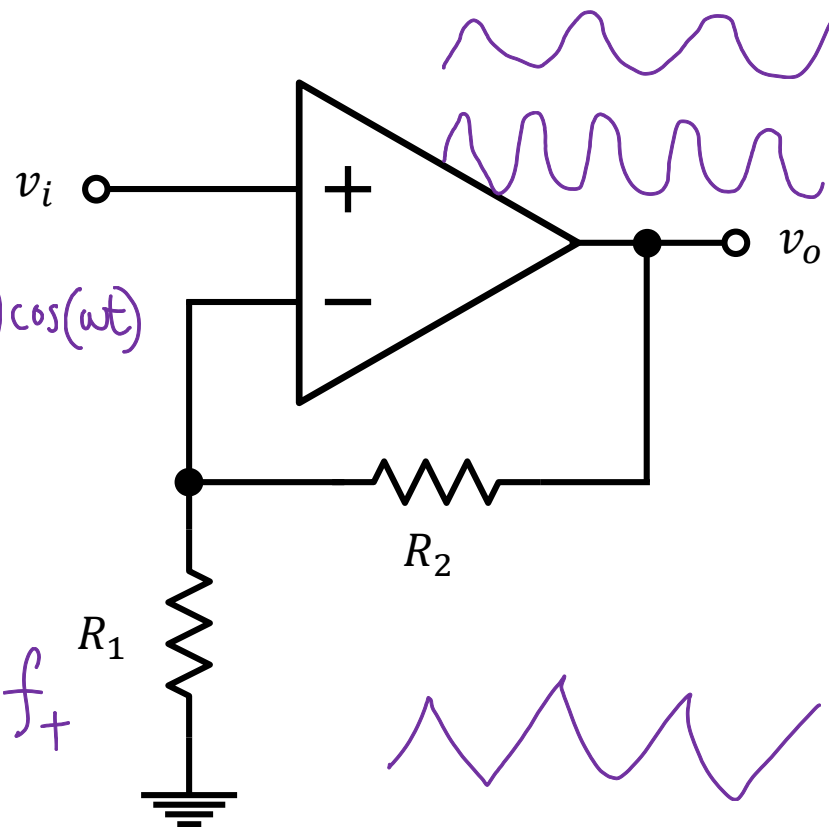What's the maximum frequency signal that can be amplified before output distortion occurs?



# Constrained Op Amp Design

Using the noninverting configuration with

- $f = 200 \text{ kHz} \ll f_t$

What's the maximum input signal amplitude that can be amplified before output distortion occurs?

✗   $f_t = 20 \text{ MHz}$

✓   $SR = 10 \frac{\text{V}}{\mu\text{s}}$

✗   $V_{o,max} = 10 \text{ V}$



$V_{i,max} = 1 \text{ V}$


$SR = (2\pi f) (A_v v_i)$

$\frac{10 \text{ V}}{\mu\text{s}} = (2\pi \cdot 200 \text{ kHz}) (10 v_i)$

$v_i = 796 \text{ mV}$

$\hookrightarrow v_o = (10)(796 \text{ mV}) = 7.96 \text{ V}$

$v_o < V_{o,max}$

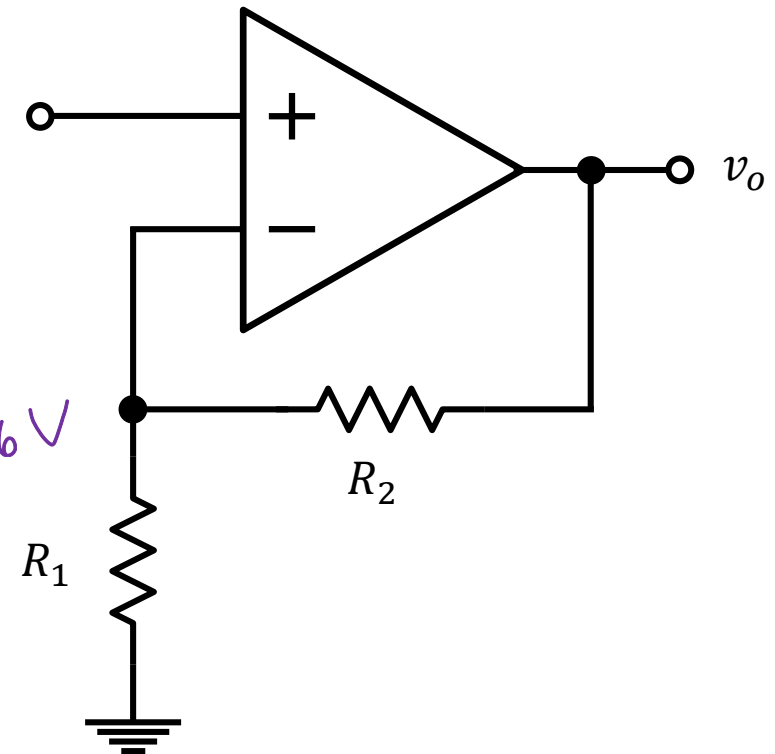

# Constrained Op Amp Design

Using the noninverting configuration with

- $v_i = 50 \text{ mV} \rightarrow v_o = 0.5 \text{ V}$

- $f_t = 20 \text{ MHz}$


- $\text{SR} = 10 \frac{\text{V}}{\mu\text{s}}$

- $V_{o,max} = 10 \text{ V}$

$$(1) \cdot f_T = \text{GBW} = A_v f_{3\text{dB}}$$
$$f_{3\text{dB}} = \frac{f_T}{A_v} = 2 \text{ MHz}$$

$$10 \frac{\text{V}}{\text{ms}} = (2\pi f)(A_v v_i)$$
$$f = \frac{(10 \times 10^6 \text{ V/s})}{2\pi \cdot 0.5 \text{ V}} = 3.18 \text{ MHz}$$

What's the useable frequency range?

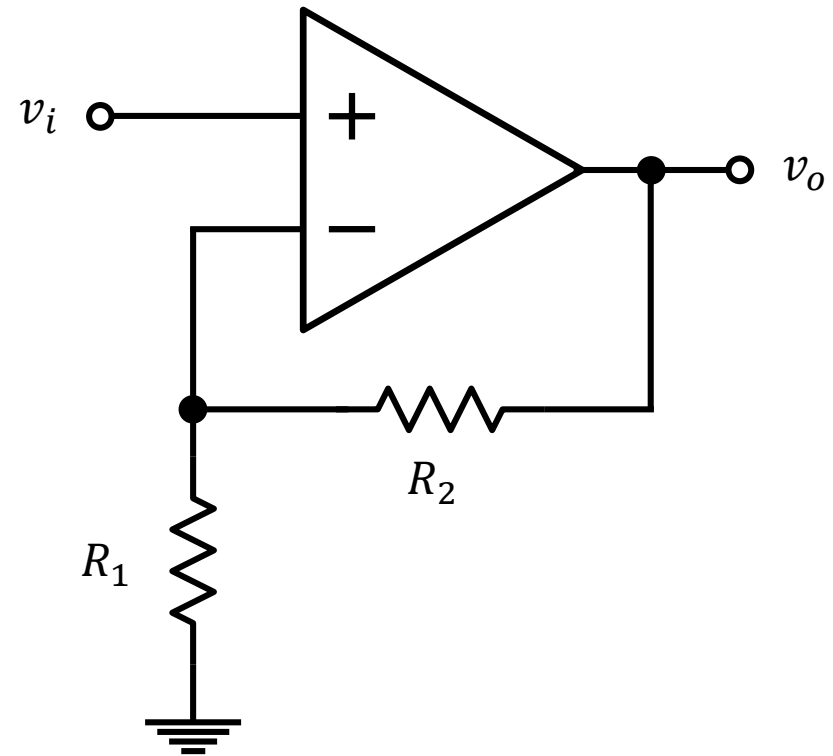

# Constrained Op Amp Design

Using the noninverting configuration with

- $f = 50 \text{ kHz}$

✗   $f_t = 20 \text{ MHz} \rightarrow f_{3dB} = 2 \text{ MHz} > f$

✗   $SR = 10 \frac{\text{V}}{\mu\text{s}}$


$V_{o,max} = 10 \text{ V}$

$$10 \frac{\text{V}}{\mu\text{s}} = (2\pi \cdot 50 \text{ kHz})(10 \cdot v_{i,max})$$


$$v_{i,max} = 3.18 \text{ V} \rightarrow v_o = 31.8 \text{ V}$$



What's the useable input voltage range?

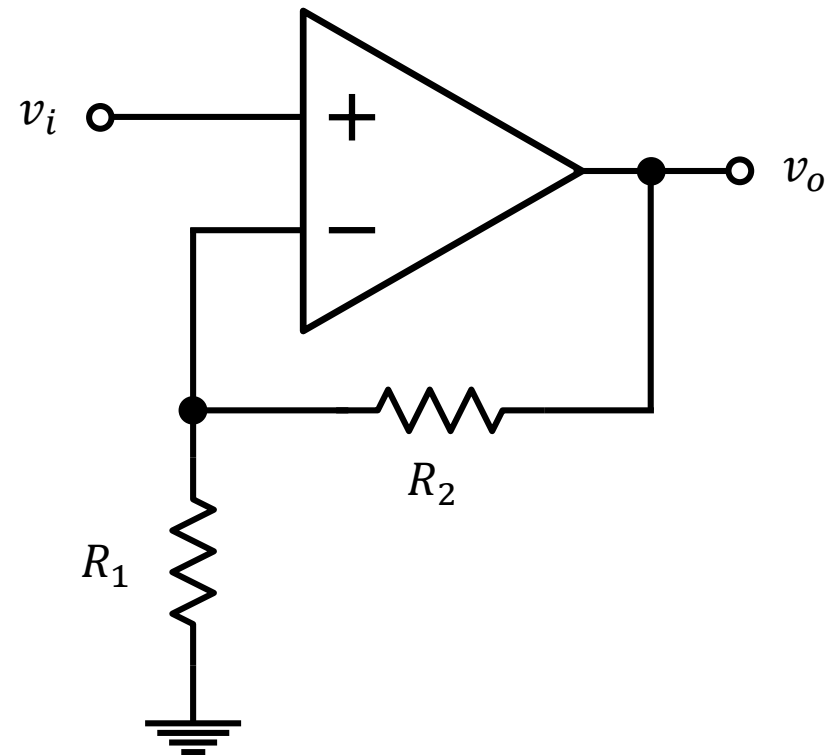

# Homework 2, SPICE Diode circuit

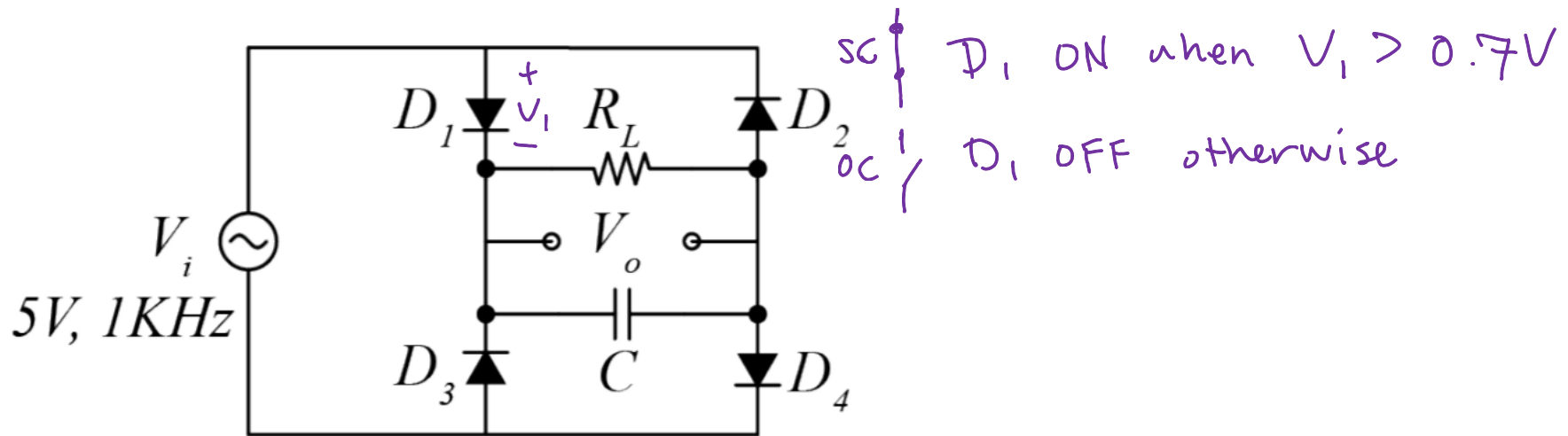

Example SPICE file

```
TA Version of Homework 2 SPICE Problem
* $\$$ 
vs vi gnd sin(0 5 1kHz)
d1 vi vop D1N4148
d2 vi von D1N4148
d3 gnd vop D1N4148
d4 gnd von D1N4148
r1 vop von 1kOhm
c1 vop von 1uF
.tran lus 5ms
.model D1N4148 D(Is=5.84n N=1.94 Rs=.7017 Ikf=44.17m Xti=3 Eg=1.11
Cjo=.95p M=.55 Vj=.75 Fc=.5 Isr=11.07n Nr=2.088 Bv=100 Ibv=100u Tt
=11.07n)
.options post=2 nomod
.end
```

# Homework 2, SPICE Diode circuit

## Simulation Output

