

D 2.35 Design the circuit shown in Fig. P2.35 to have an input resistance of $100\text{ k}\Omega$ and a gain that can be varied from -1 V/V to -100 V/V using the $100\text{-k}\Omega$ potentiometer R_4 . What voltage gain results when the potentiometer is set exactly at its middle value?

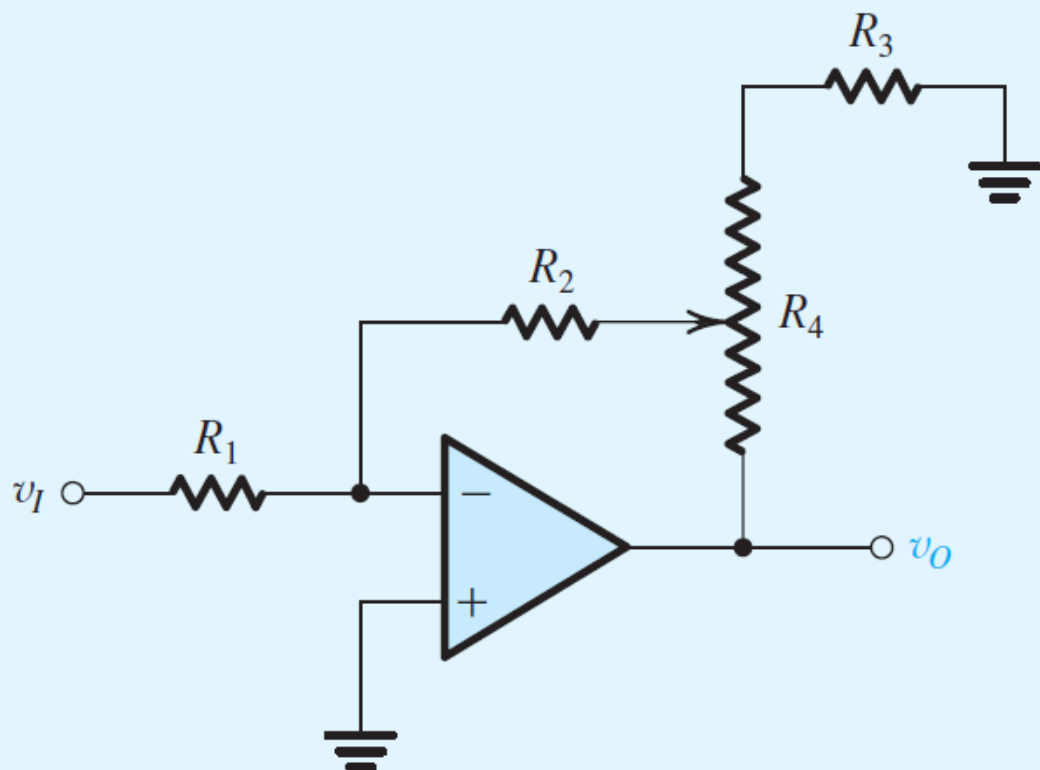


Figure P2.35

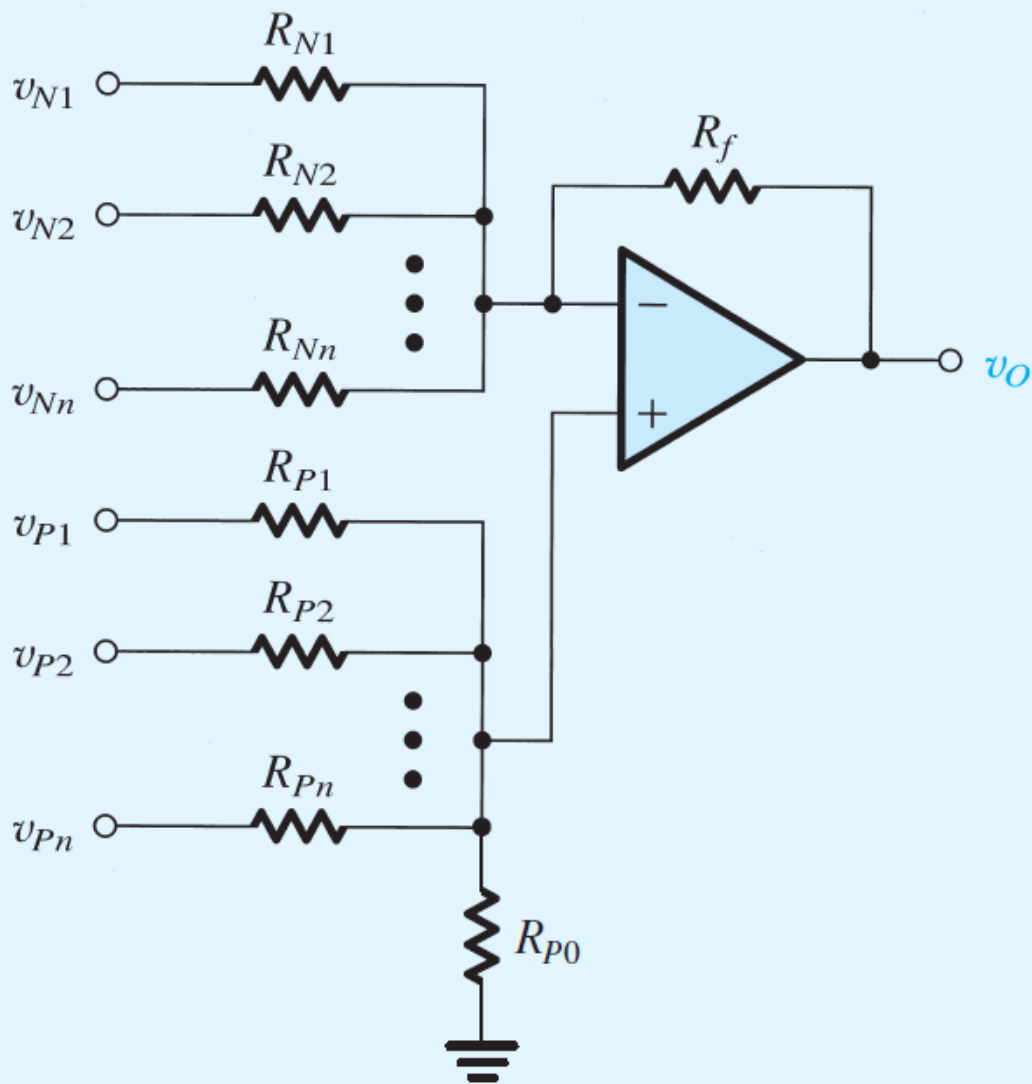


Figure P2.47

D *2.48 Design a circuit, using one ideal op amp, whose output is $v_O = v_{I1} + 2v_{I2} - 9v_{I3} + 4v_{I4}$. (*Hint: Use a structure similar to that shown in general form in Fig. P2.47.*)

2.62 For the circuit shown in Fig. P2.62, express v_o as a function of v_1 and v_2 . What is the input resistance seen by v_1 alone? By v_2 alone? By a source connected between the two input terminals? By a source connected to both input terminals simultaneously?

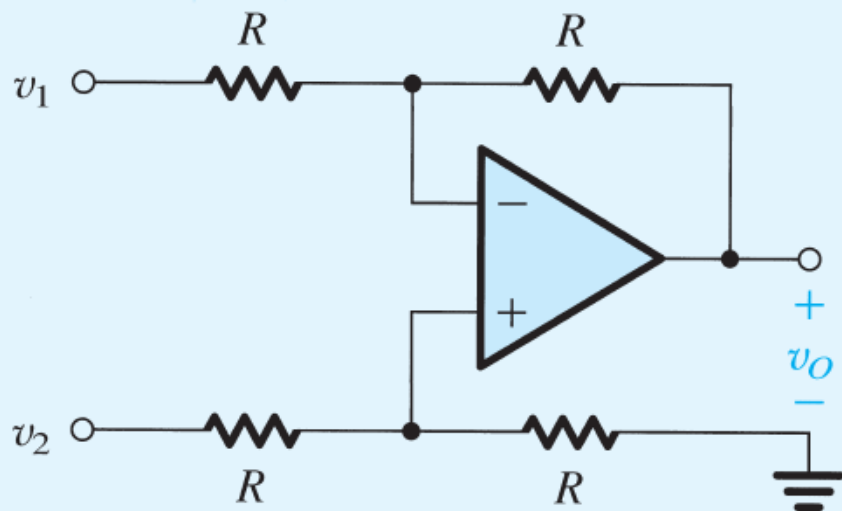


Figure P2.62