

**2.98** A particular inverting amplifier with nominal gain of  $-100$  V/V uses an imperfect op amp in conjunction with  $100\text{-k}\Omega$  and  $10\text{-M}\Omega$  resistors. The output voltage is found to be  $+5.3$  V when measured with the input open and  $+5$  V with the input grounded.

- What is the bias current of this amplifier? In what direction does it flow?
- Estimate the value of the input offset voltage.
- A  $10\text{-M}\Omega$  resistor is connected between the positive-input terminal and ground. With the input left floating (disconnected), the output dc voltage is measured to be  $-0.6$  V. Estimate the input offset current.

**2.119** Consider the use of an op amp with a unity-gain frequency  $f_t$  in the realization of:

- (a) An inverting amplifier with dc gain of magnitude  $K$ .
- (b) A noninverting amplifier with a dc gain of  $K$ .

In each case find the 3-dB frequency and the gain–bandwidth product ( $\text{GBP} \equiv |\text{Gain}| \times f_{3\text{dB}}$ ). Comment on the results.

**\*2.120** Consider an inverting summer with two inputs  $V_1$  and  $V_2$  and with  $V_o = -(V_1 + 3V_2)$ . Find the 3-dB frequency of each of the gain functions  $V_o/V_1$  and  $V_o/V_2$  in terms of the op amp  $f_t$ . (*Hint:* In each case, the other input to the summer can be set to zero—an application of superposition.)

**3.4** For a silicon crystal doped with phosphorus, what must  $N_D$  be if at  $T = 300$  K the hole concentration drops below the intrinsic level by a factor of  $10^8$ ?