

PROBLEM SET #5*Issued: Friday, September 27, 2019**Due: Friday, October 4, 2019 at 12:00 noon via Gradescope.*

1. Sedra & Smith, Problem 3.25
2. Sedra & Smith, Problem 3.26
3. Given a *pn* junction with doping $N_A = 10^{17} \text{ cm}^{-3}$, $N_D = 10^{16} \text{ cm}^{-3}$, cross-sectional area, $A = 200 \text{ } \mu\text{m}^2$, $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$, diffusion lengths $L_p = 4 \text{ } \mu\text{m}$ & $L_n = 12 \text{ } \mu\text{m}$, and diffusion constants $D_p = 8 \text{ cm}^2/\text{s}$ & $D_n = 20 \text{ cm}^2/\text{s}$, find I_S . If a forward voltage $V = 800 \text{ mV}$ is applied across this junction, what is the resulting forward current?
4. Sedra & Smith, Problem 4.37
5. Sedra & Smith, Problem 4.43
6. Sedra & Smith, Problem 5.23
7. Sedra & Smith, Problem 5.27

For problems 8 and 9 below, use the parameters in Table PS5.1 as needed.

| <i>PARAMETER</i> | <i>NMOS VALUE</i> | <i>PMOS VALUE</i> | <i>UNIT</i> |
|------------------|-------------------|-------------------|--------------------------|
| V_{t0} | 0.75 | -0.75 | V |
| γ | 0.75 | 0.5 | $\sqrt{\text{V}}$ |
| $2\phi_f$ | 0.6 | 0.6 | V |
| K' | 25 | 10 | $\mu\text{A}/\text{V}^2$ |

Table PS5.1

8. Identify the source, drain, gate and bulk terminals, and find the current I in the transistors in Figure PS5.1. Assume $V_{tn} = 0.75$ V.

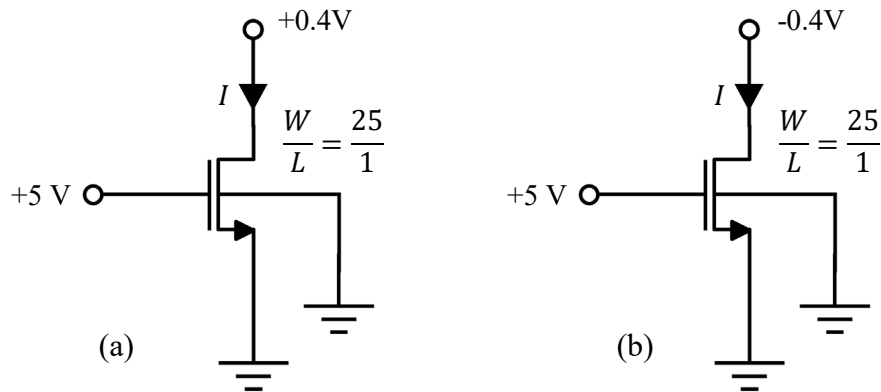


Figure PS5.1

9. Consider transistors operating in their linear regions for the questions below.
- What is the W/L ratio required for an NMOS transistor to have an on-resistance of 2 k Ω when $V_{GS} = 5$ V and $V_{SB} = 0$ V?
 - Repeat for a PMOS transistor with $V_{GS} = -5$ V and $V_{SB} = -3$ V.
10. Sedra & Smith, Problem 5.24