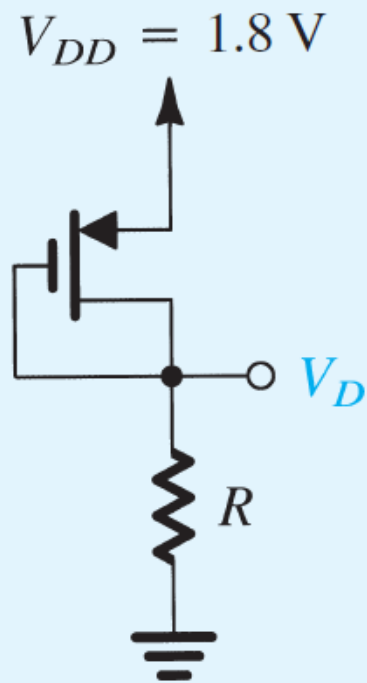


**D 5.49** The PMOS transistor in the circuit of Fig. P5.49 has  $V_t = -0.5$  V,  $\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$ ,  $L = 0.18 \mu\text{m}$ , and  $\lambda = 0$ . Find the values required for  $W$  and  $R$  in order to establish a drain current of  $180 \mu\text{A}$  and a voltage  $V_D$  of 1 V.



**Figure P5.49**

**5.47** The transistor in the circuit of Fig. P5.47 has  $k'_n = 0.4 \text{ mA/V}^2$ ,  $V_t = 0.4 \text{ V}$ , and  $\lambda = 0$ . Show that operation at the

**D 5.50** The NMOS transistors in the circuit of Fig. P5.50 have  $V_t = 0.5 \text{ V}$ ,  $\mu_n C_{ox} = 250 \text{ } \mu\text{A/V}^2$ ,  $\lambda = 0$ , and  $L_1 = L_2 = 0.25 \text{ } \mu\text{m}$ . Find the required values of gate width for each of  $Q_1$

**SIM** = Multisim/PSpice; \* = difficult problem; \*\* = more difficult; \*\*\* = very challenging; D = design problem

### 300 Chapter 5 MOS Field-Effect Transistors (MOSFETs)

and  $Q_2$ , and the value of  $R$ , to obtain the voltage and current values indicated.

the drain current is  $0.5 \text{ mA}$  and the drain voltage is  $+7 \text{ V}$ . If the transistor is replaced with another having  $V_t = 1.5 \text{ V}$  with  $k'_n(W/L) = 1.5 \text{ mA/V}^2$ , find the new values of  $I_D$  and  $V_D$ . Comment on how tolerant (or intolerant) the circuit is to changes in device parameters.

**D 5.53** Using a PMOS transistor with  $V_t = -1.5 \text{ V}$ ,  $k'_p(W/L) = 4 \text{ mA/V}^2$ , and  $\lambda = 0$ , design a circuit that resembles that in Fig. 5.24(a). Using a  $10\text{-V}$  supply, design for a gate voltage of  $+6 \text{ V}$ , a drain current of  $0.5 \text{ mA}$ , and a drain voltage of  $+5 \text{ V}$ . Find the values of  $R_S$  and  $R_D$ . Also, find the values of the resistances in the voltage divider feeding the gate, assuming a  $1\text{-}\mu\text{A}$  current in the divider.

**5.54** The MOSFET in Fig. P5.54 has  $V_t = 0.4 \text{ V}$ ,  $k'_n = 500 \text{ } \mu\text{A/V}^2$ , and  $\lambda = 0$ . Find the required values of  $W/L$  and of  $R$  so that when  $v_i = V_{DD} = +1.3 \text{ V}$ ,  $r_{DS} = 50 \text{ } \Omega$  and

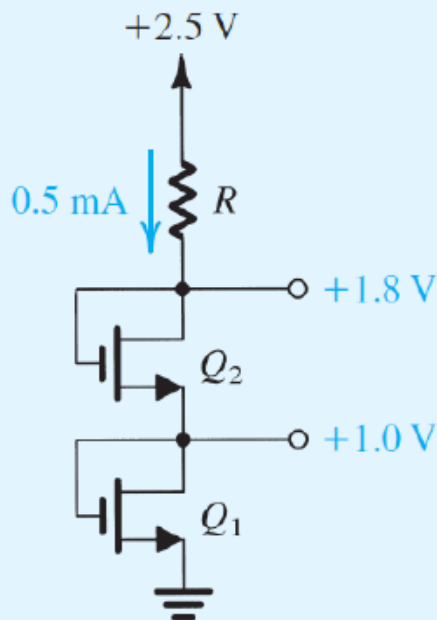


Figure P5.50

transistor that conducts  $i_C = 1 \text{ mA}$  with  $v_{EB} = 0.70 \text{ V}$ . How much larger is it?

**6.26** While Fig. 6.5 provides four possible large-signal equivalent circuits for the *npn* transistor, only two equivalent circuits for the *pnp* transistor are provided in Fig. 6.11. Supply the missing two.

**6.27** By analogy to the *npn* case shown in Fig. 6.9, give the equivalent circuit of a *pnp* transistor in saturation.

## Section 6.2: Current–Voltage Characteristics

**6.28** For the circuits in Fig. P6.28, assume that the transistors have very large  $\beta$ . Some measurements have been made on these circuits, with the results indicated in the figure. Find the values of the other labeled voltages and currents.

**6.29** Measurements on the circuits of Fig. P6.29 produce labeled voltages as indicated. Find the value of  $\beta$  for each transistor.

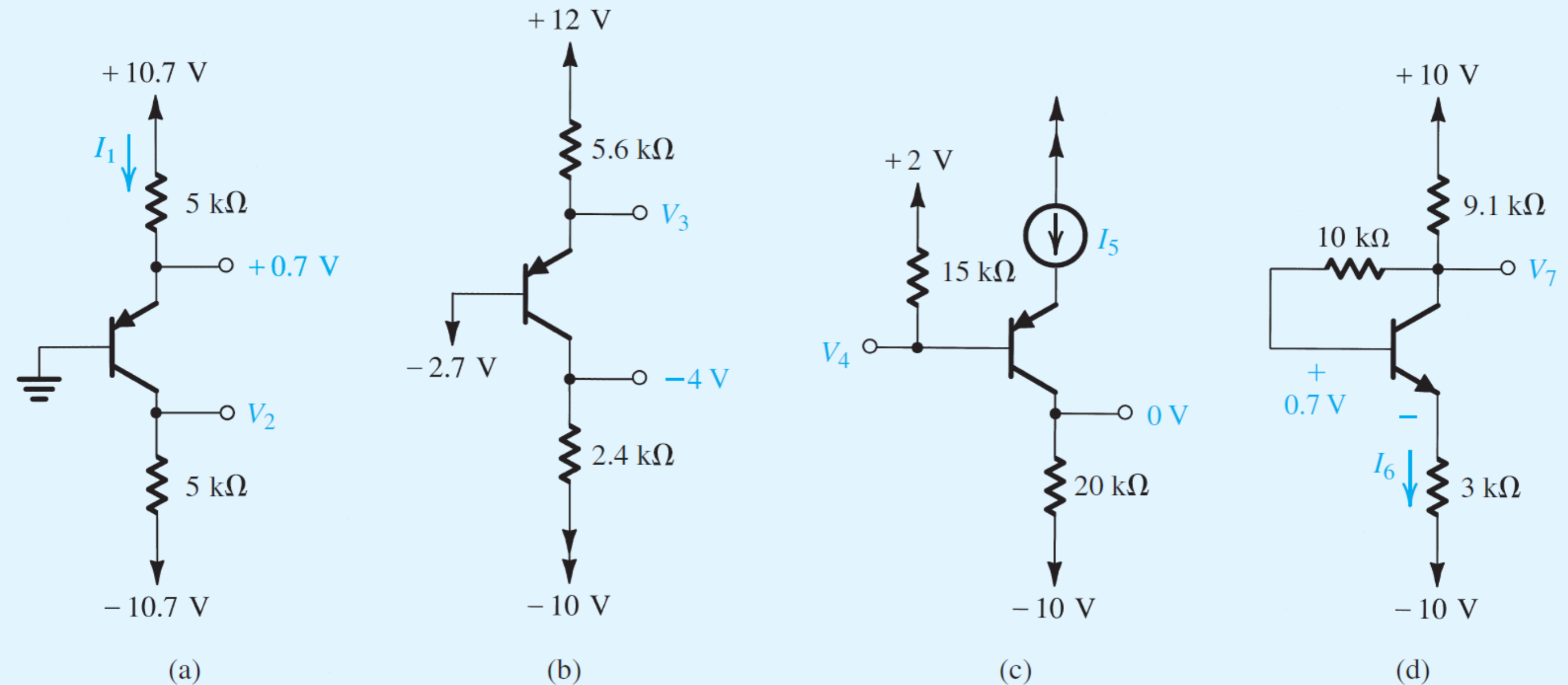


Figure P6.28

**6.56** A single measurement indicates the emitter voltage of the transistor in the circuit of Fig. P5.56 to be 1.0 V. Under the assumption that  $|V_{BE}| = 0.7$  V, what are  $V_B$ ,  $I_B$ ,  $I_E$ ,  $I_C$ ,  $V_C$ ,  $\beta$ , and  $\alpha$ ? (Note: Isn't it surprising what a little measurement can lead to?)

