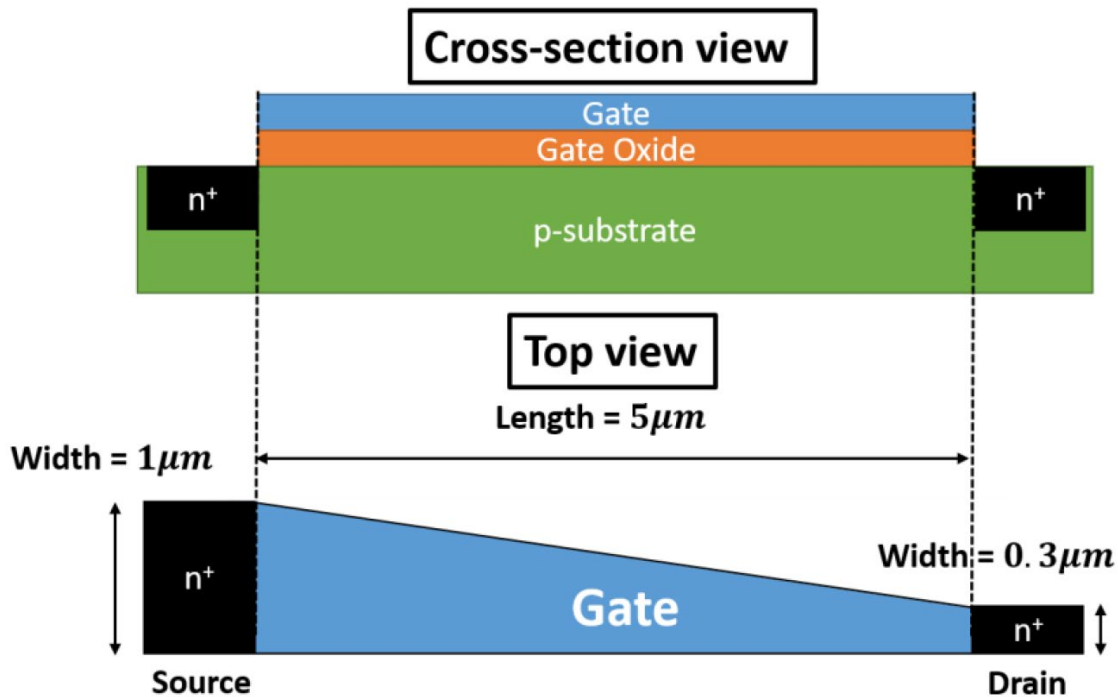


PROBLEM SET #6


Issued: Friday, October 4, 2019

Due: Friday, October 18, 2019, 12:00 noon via **Gradescope**.


1. Sedra & Smith, Problem 5.49
2. Sedra & Smith, Problem 5.50
3. The cross-section and top-view of an NMOS transistor are shown below. The length of the channel is $5\mu\text{m}$. The width of the channel changes linearly from $1\mu\text{m}$ at the source to $0.3\mu\text{m}$ at the drain. Derive the expression for the device current when operating in the saturation region as a function of μ_n , C_{ox} , V_{GS} , V_{DS} and V_{th} . Assume $\lambda=0$.



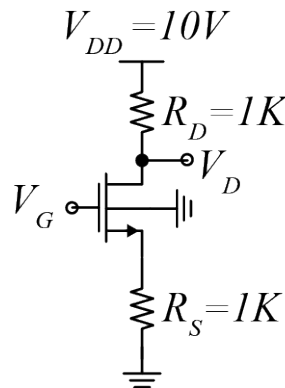4. In the following circuit, find V_G to set $V_D=8V$. Device parameters: $K'=100\mu\text{A}/\text{V}^2$, $V_T=0.7V$, $2\phi_F=0.6V$, $\gamma=0.75\sqrt{V}$.



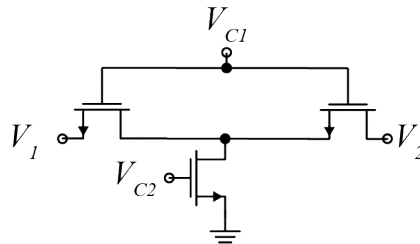5. (a) Calculate the on-resistance for an NMOS transistor having $W/L = 100/1$ and operating with $V_{GS} = 5V$ and $V_{TN} = 0.75V$. (b) Repeat for a similar PMOS transistor with $V_{GS} = -5V$ and $V_{TP} = -0.75V$. (c) What W/L is required for the PMOS transistor to have the same R_{on} as the NMOS transistor in (a)?
6. What is the impedance between V_1 and V_2 under following conditions. Device parameters: $K' = 100\mu A/V^2$, $V_T = 0.7V$.
- (a) $V_1 = 0V$, $V_{C1} = 5V$, $V_{C2} = 0V$.
- (b) $V_1 = 2.5V$, $V_{C1} = 5V$, $V_{C2} = 1V$.
- (c) $V_1 = 2.5V$, $V_{C1} = 2.5V$, $V_{C2} = 5V$.



7. Indicate the region of operation for an npn transistor biased as follows:
- (a) $V_{BE} = -5.0V$, $V_{BC} = 0.7V$.
- (b) $V_{BE} = -5.0V$, $V_{BC} = -5.0V$.
- (c) $V_{BE} = 0.7V$, $V_{BC} = 0.7V$.
- (d) $V_{BE} = 0.7V$, $V_{BC} = -5.0V$.
8. Indicate the region of operation for a pnp transistor biased as follows:
- (a) $V_{EB} = 0.7V$, $V_{CB} = 0.7V$.
- (b) $V_{EB} = 0.7V$, $V_{CB} = -0.65$.
- (c) $V_{EB} = -0.65V$, $V_{CB} = 0.7V$.
- (d) $V_{EB} = -0.65V$, $V_{CB} = -0.65V$.
9. Sedra & Smith, Problem 6.28
10. Sedra & Smith, Problem 6.56
11. Find the transistor operating points, V_C , and V_E in the following circuits. $\beta = 50$, $V_{BE} = 0.7V$.

